

ELEC301 Problem Set #3

1) For the circuit shown in figure 1, use the $1/3^{rd}$ rule with $V_B = V_{CC}/3$ to find R_{B1} , R_{B2} , R_C , and R_E given that $V_{CC} = 15V$ and $I_C = 2mA$.

2) For the circuit shown in figure 1, use the $1/3^{rd}$ rule with $V_E = V_{CC}/3$ to find R_{B1} , R_{B2} , R_C , and I_C given that $R_E = 8k\Omega$ and $V_{CC} = 12V$.

(Answers: $R_{B1} \approx 146k\Omega$, $R_{B2} \approx 104k\Omega$, $R_C \approx 8k\Omega$, and $I_C \approx 0.5mA$)

3) What are g_m and r_{π} for the transistors in P1 and P2 above?

(Answers: P1 $g_m = 80m\Omega^{-1}$ and $r_{\pi} = 1.25k\Omega$; P2 $g_m = 20m\Omega^{-1}$ and $r_{\pi} = 5k\Omega$)

4) Assuming that a small-signal a.c. voltage source with a 50Ω source impedance is coupled to the amplifier of P2 above via a $10\mu F$ coupling capacitor and that R_E is bypassed using a $50\mu F$ capacitor and that the hybrid-model has the following parameters $c_{\pi} = 10pF$, $c_{\mu} = 2pF$, and $r_o = \infty$, what are A_M , $\omega_{3dB L}$, and $\omega_{3dB H}$?

(Answers: $A_M \approx -158$, $\omega_{3dB L} \approx 400/s$, and $\omega_{3dB H} \approx 4.4 \times 10^7/s$)

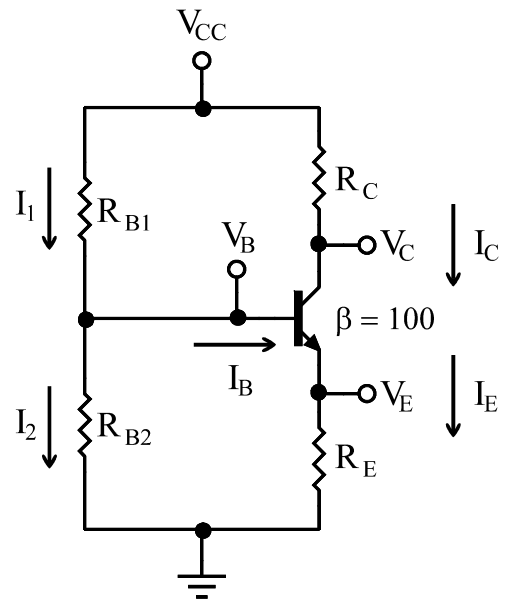


Figure 1.

5) For the circuit shown in figure 2:

- i. Draw the low frequency circuit, the midband circuit and the high frequency circuit and
- ii. Derive the complete transfer function using $I_E \approx I_C = 2mA$, $c_{\pi} = 10pF$, and $c_{\mu} = 2pF$.

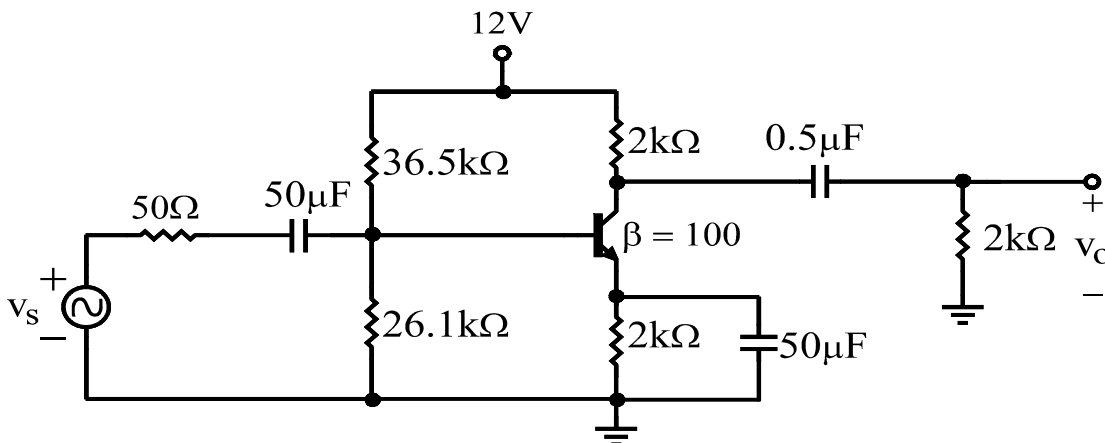


Figure 2.