
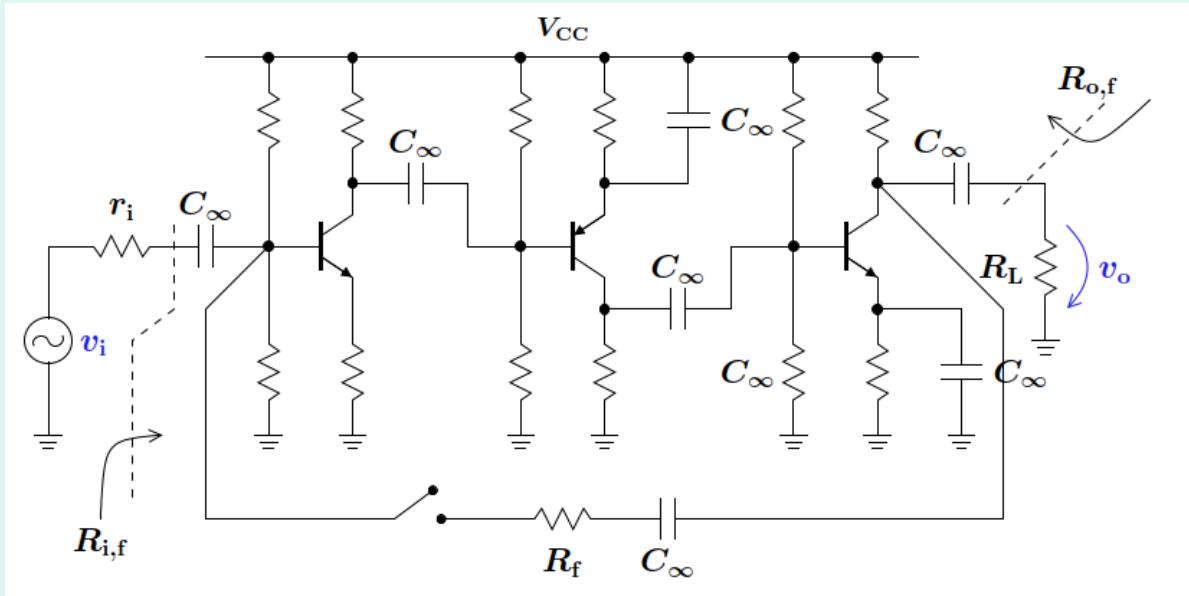


# ELEC 301 - BJT small signal model, biasing circuit

L11 - Sep 29

Instructor: Edmond Cretu

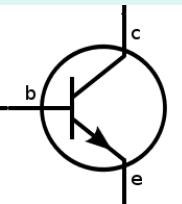



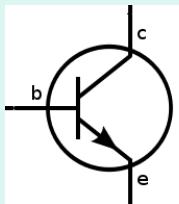
# Last time



- Large signal models vs small signal models
- Diodes - large signal, small signal model
- BJTs - operating principle, operating modes, large signal model, simple small signal model






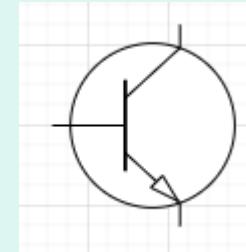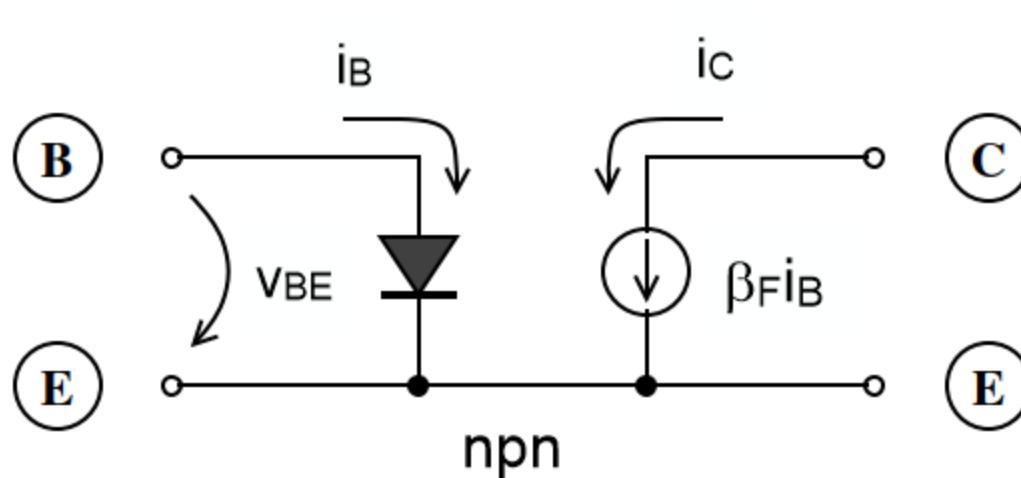
# Large-signal model for BJT


- REM: controlled current source orientation


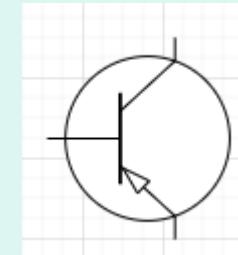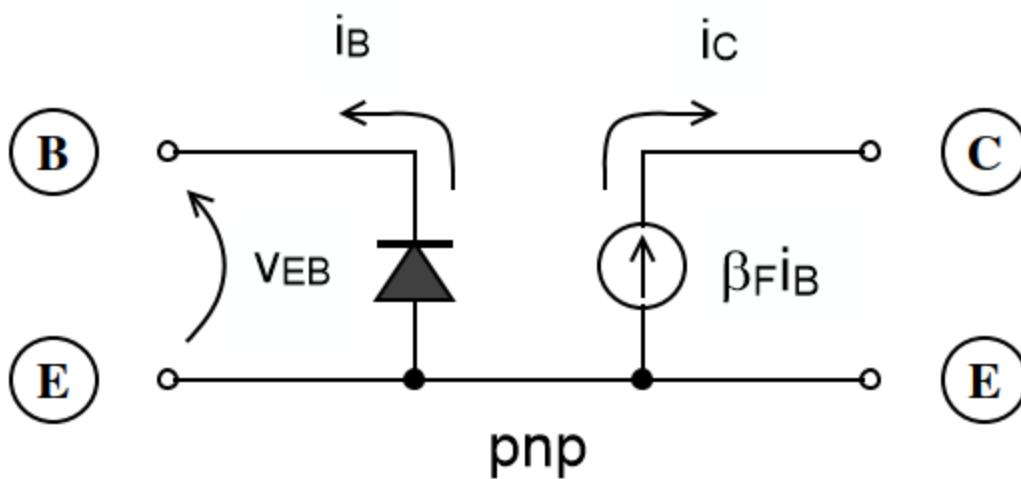
$$i_C = I_S e^{\frac{v_{BE}}{V_T}}, i_B = \frac{I_S}{\beta} e^{\frac{v_{BE}}{V_T}}$$




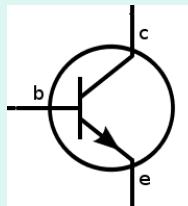
$$i_C = I_S e^{\frac{v_{EB}}{V_T}}, i_B = \frac{I_S}{\beta} e^{\frac{v_{EB}}{V_T}}$$


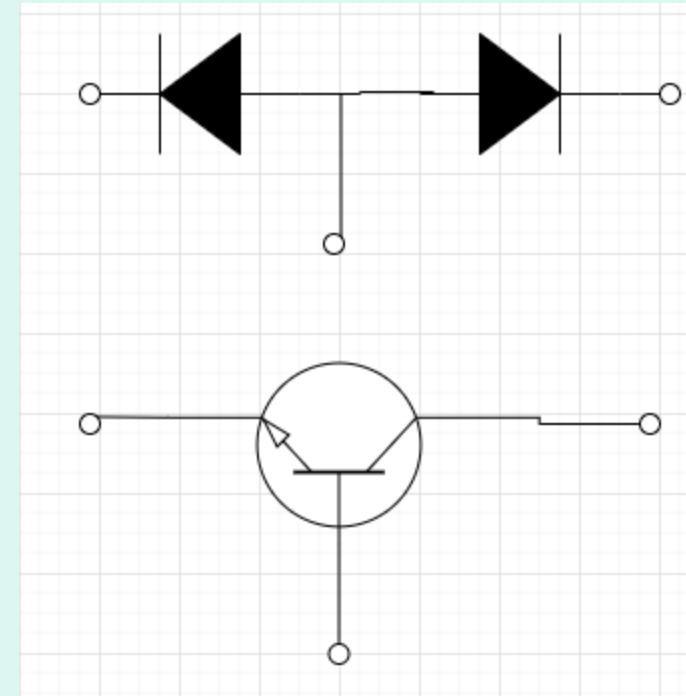
## L11 Q01 - diodes and BJT

- Which one is the **wrong** statement when comparing two back-to-back diodes with a BJT structure?
  - A. They are the same three-terminal device
  - B. If we increase the base width significantly, they become the same device
  - C. A BJT is characterized by two coupled junctions



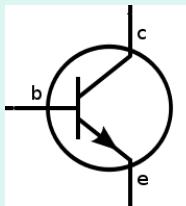



# Basic Hybrid- $\pi$ model for BJT

- Small signal model without considering capacitive effects, nor the Early effect

$$r_\pi = \frac{v_{be}}{i_{be}} = \frac{\beta}{g_m} = \beta \frac{V_T}{I_C} = \frac{V_T}{I_B}$$


$$g_m = \frac{I_C}{V_T}$$

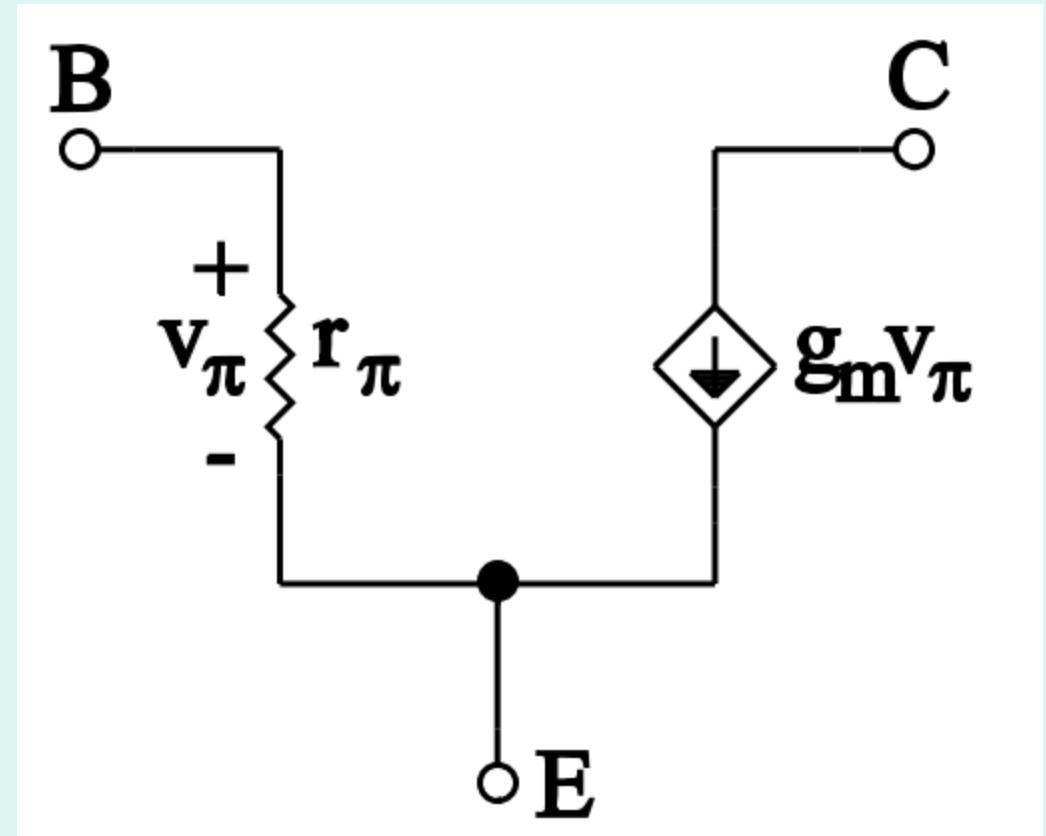


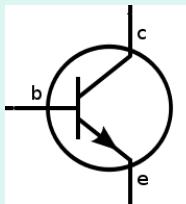
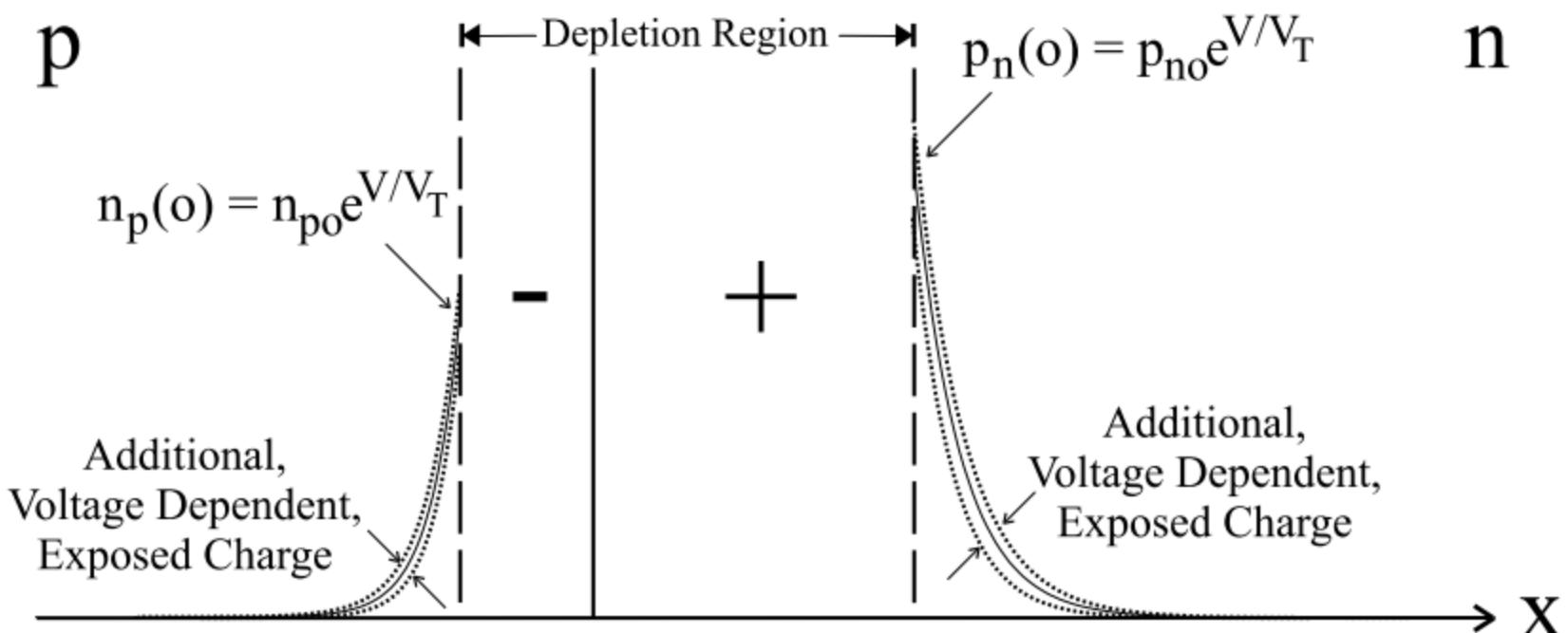
# Junction capacitance EBJ


- $C = dQ/dV$
- EBJ - forward biased - diffusion capacitance (change in minority carrier concentrations on either side of junction)




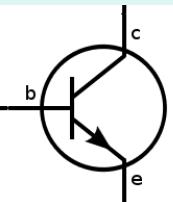
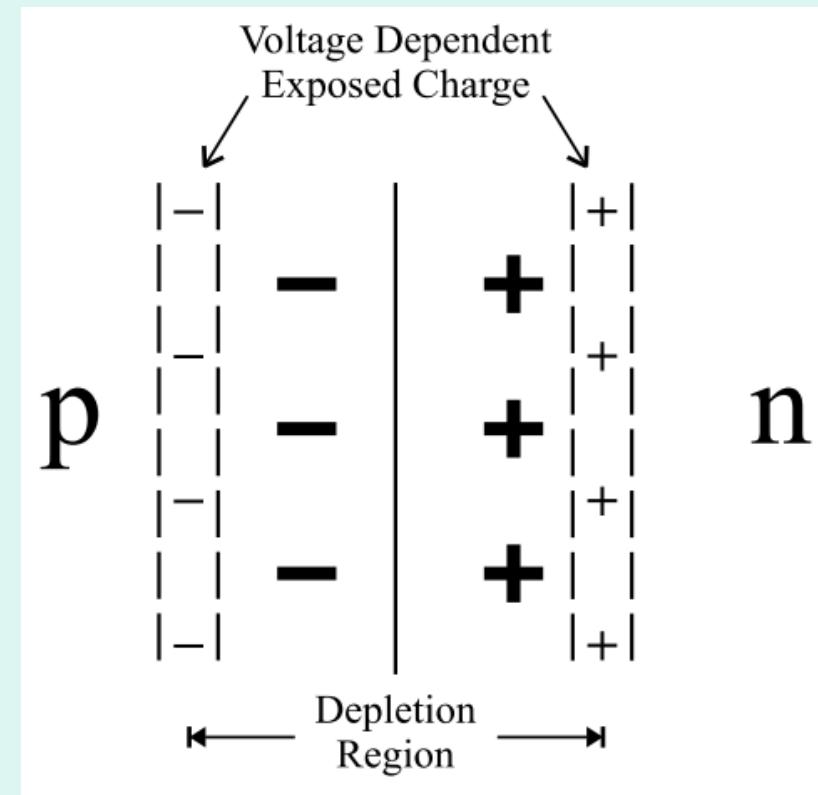
# Junction capacitance CBJ


- Active mode => reverse biased CBJ
- “Space-charge capacitance” - dominant mechanism is the change in exposed charge on either side of the depletion region -  $Q=f(V_{CB})$
- For small-signals the relation charge-voltage is linear => constant capacitance




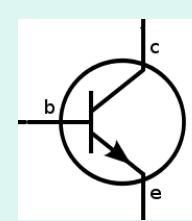

# Hybrid-p model with junction capacitances


- Improved small-signal model

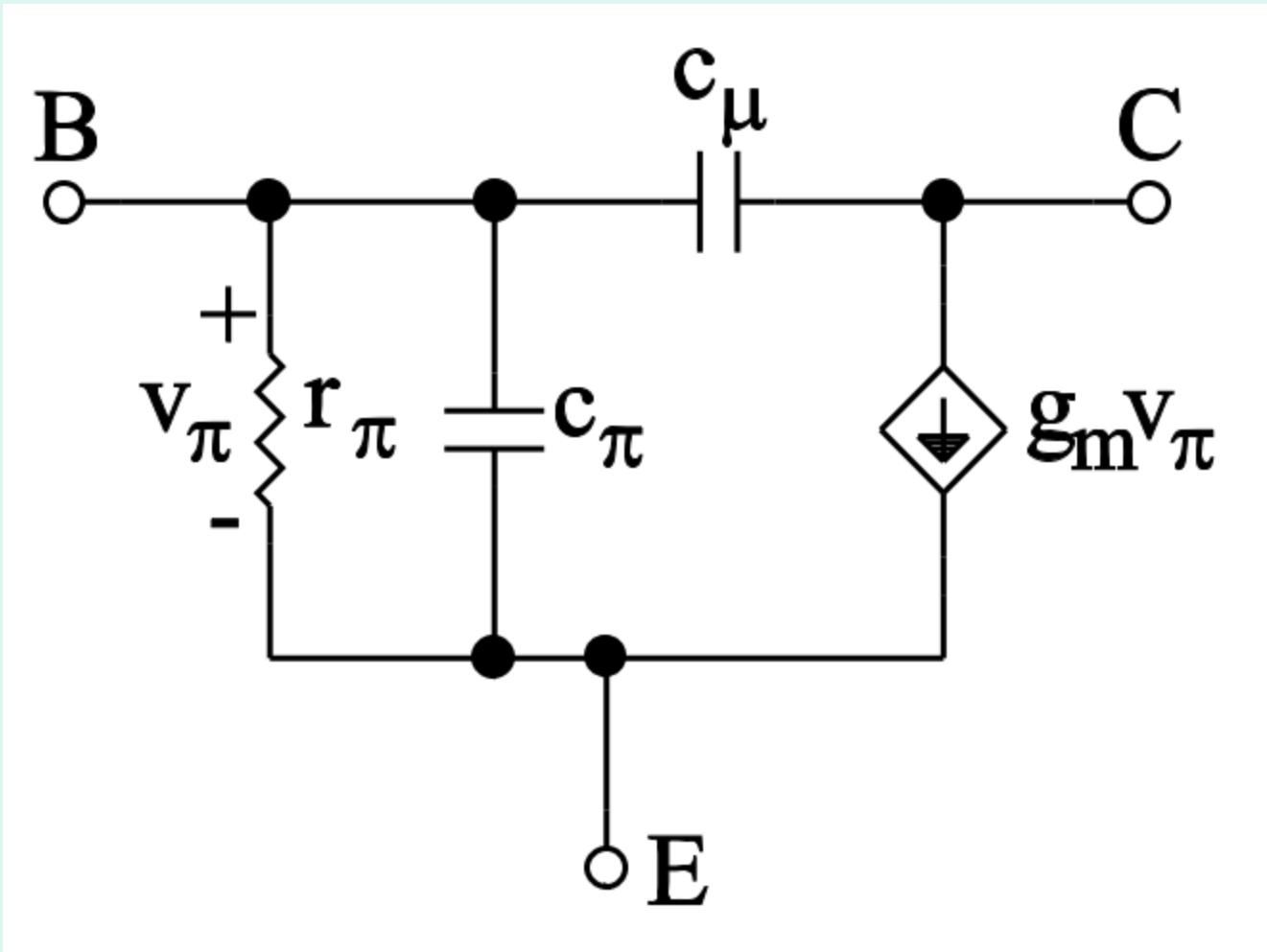


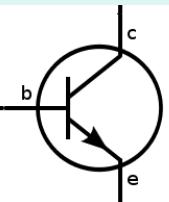
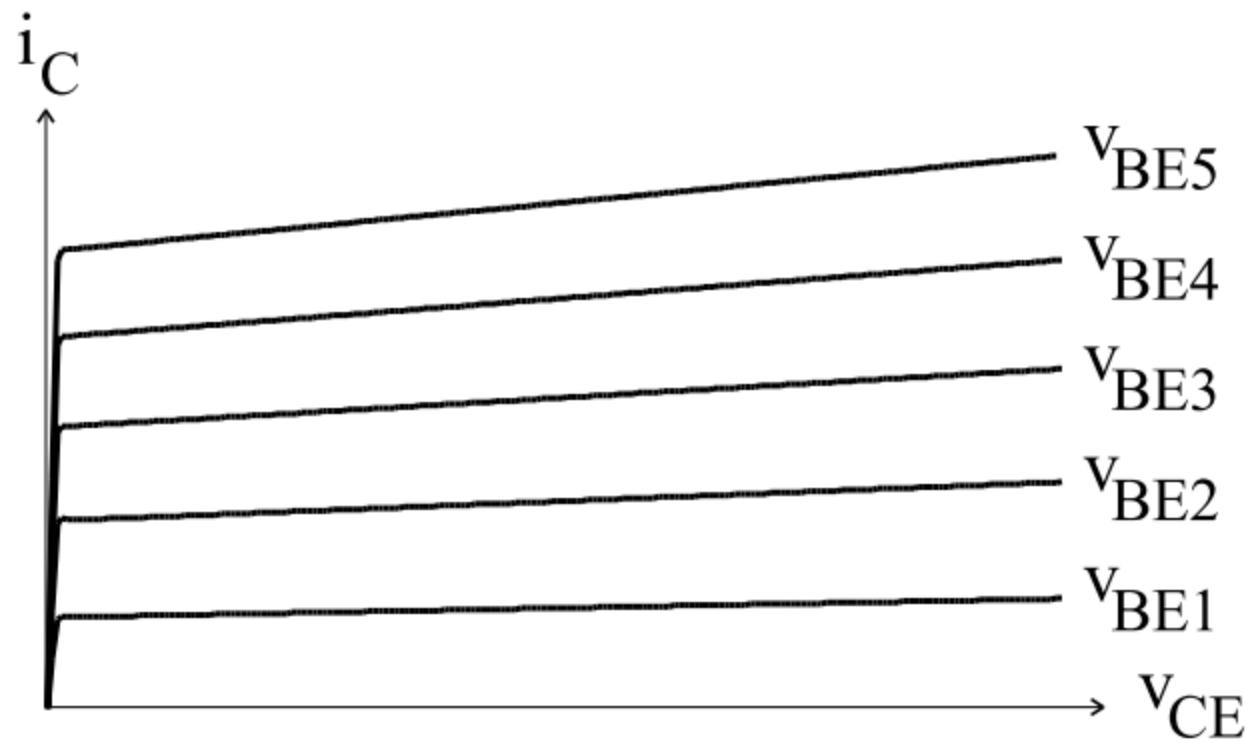
# Further refinement - output resistance


- Ideally  $i_C$  depends solely on  $v_{BE}$ , but it shows as well a dependence on  $v_{CE}$



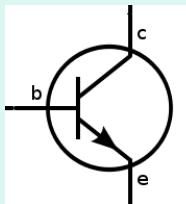
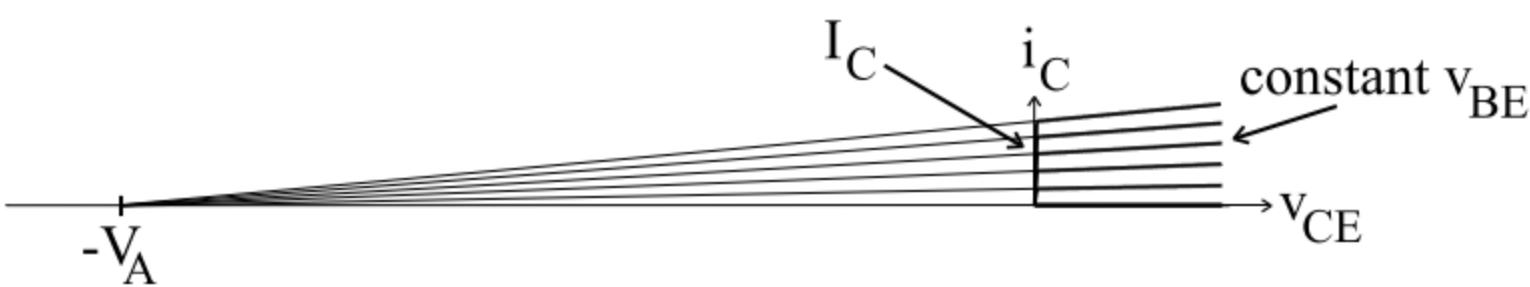
# Early voltage and output resistance


- Early effect - widening of the CB depletion region as  $V_{BC}$  increases
- $V_A$  = Early voltage - for modern BJTs  $\sim 50..500V$ , lower for pnp



$$i_C = i_C(v_{BE}, v_{CE}) = I_S e^{\frac{v_{BE}}{V_T}} \left( 1 + \frac{v_{CE}}{V_A} \right)$$

$$r_o \simeq \frac{V_A}{I_C}$$



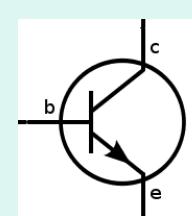


# Complete Hybrid- $\pi$ small-signal model


- Adding all the effects so far

$$r_\pi = \frac{v_{be}}{i_{be}} = \frac{\beta}{g_m} = \beta \frac{V_T}{I_C} = \frac{V_T}{I_B}$$

$$g_m = \frac{I_C}{V_T}$$


$$r_o \simeq \frac{V_A}{I_C}$$

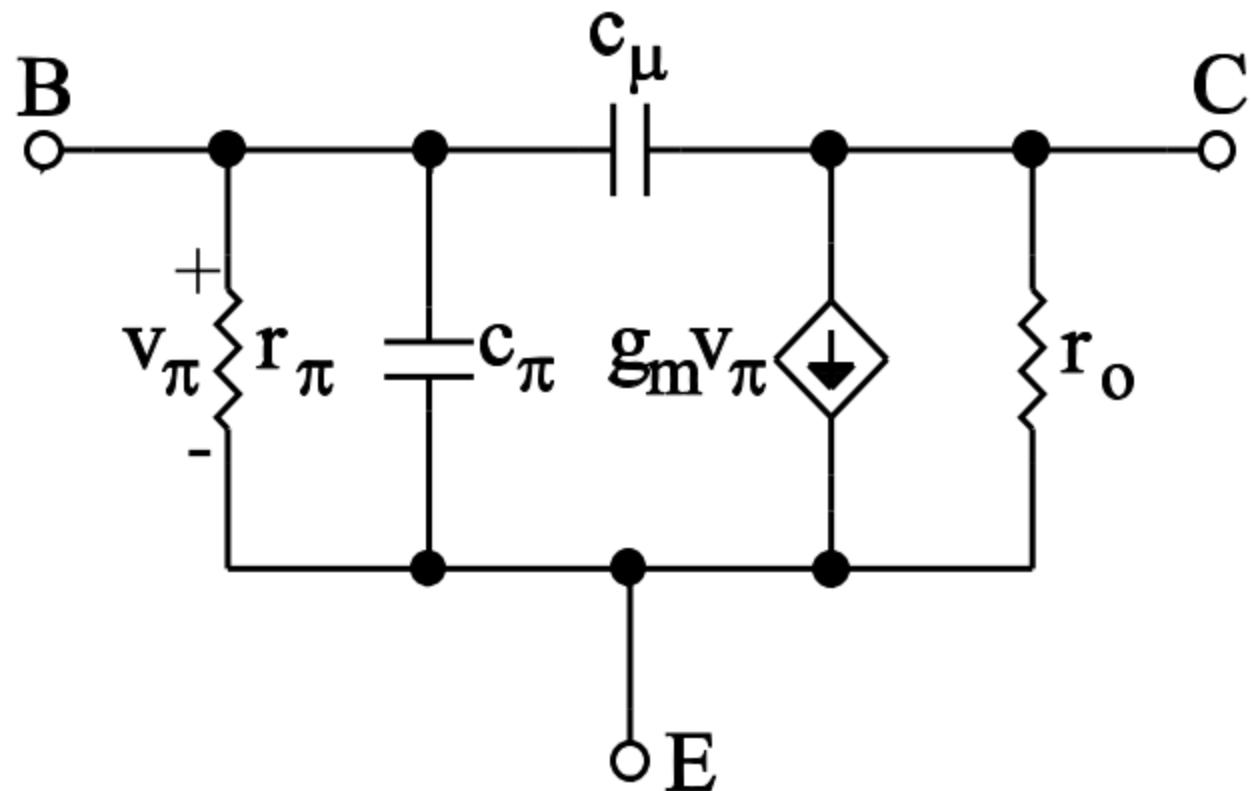


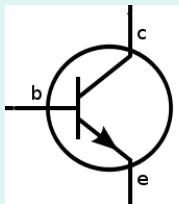
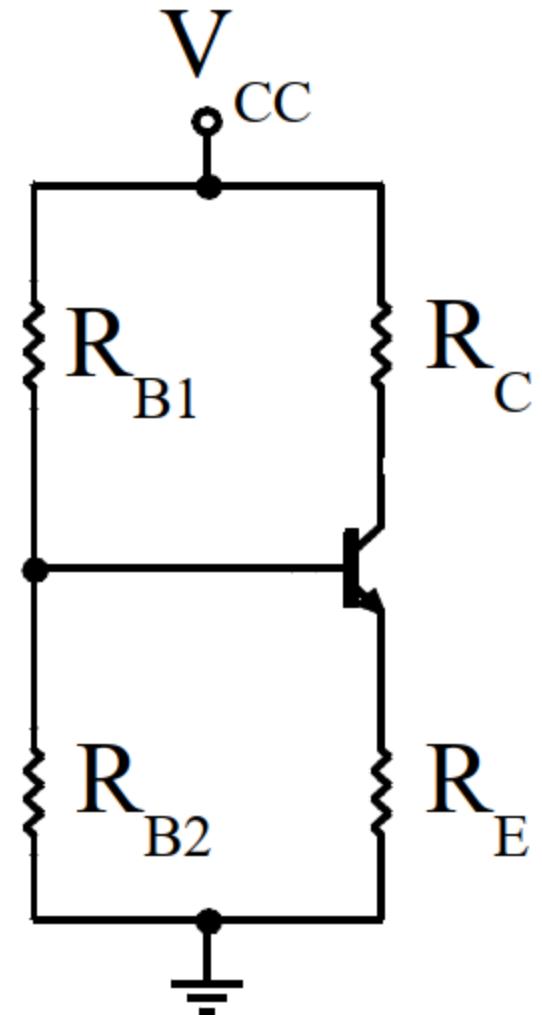
# BJT biasing


- The basic bias circuit
- $V_{CC}$  often imposed by application
- Biasing trade-off:
  - operation in active mode
  - gain
  - dynamic operating range
  - power consumption
  - input impedance
  - quiescent point stability



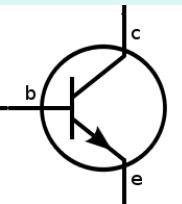
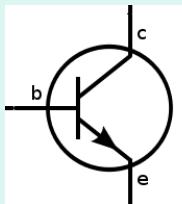
## L11 Q02 - $R_C$ role


- What happens if, for given  $V_{CC}$ ,  $R_{B1}$ ,  $R_{B2}$ ,  $R_E$ , and  $\beta$ , we increase  $R_C$  ?
  - A. we decrease the voltage gain
  - B. we increase the power consumption
  - C. BJT gets closer to operating in the saturation regime




## L11 Q03 - bias current

- How do we want the current through  $R_{B2}$  to be, in comparison with the base current  $I_B$ ?


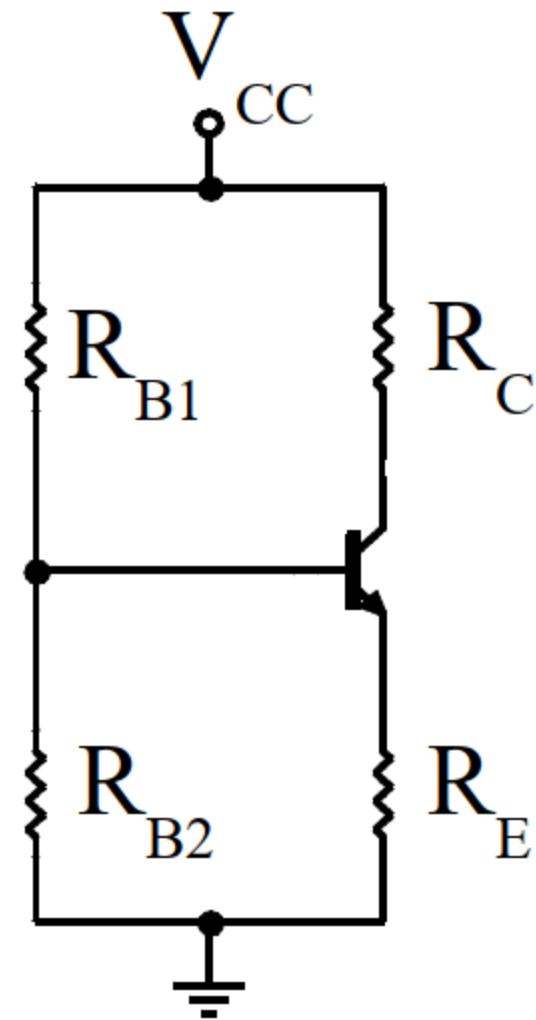
- A.  $I_{RB2} \gg I_B$
- B.  $I_{RB2} \approx I_B$
- C.  $I_{RB2} \ll I_B$



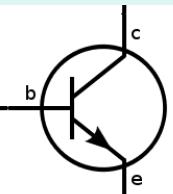
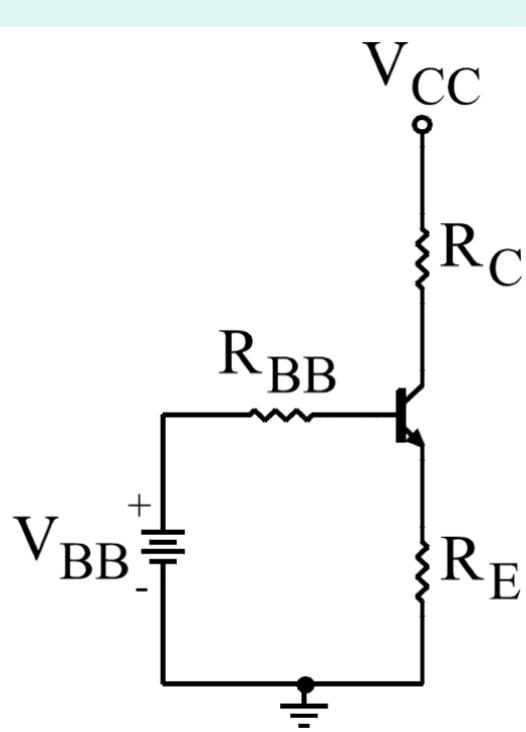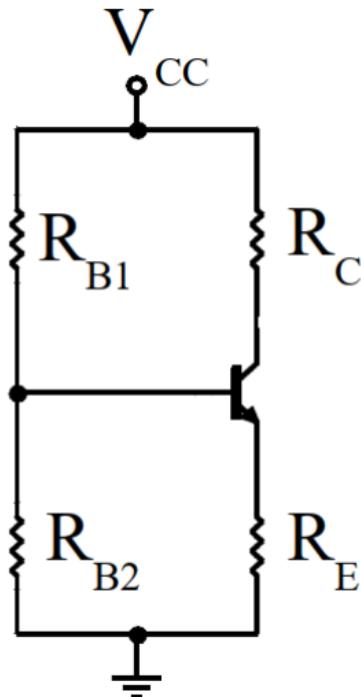
# BJT biasing


$$I_B = - \frac{V_{BE}}{(1+\beta) R_E + R_{BB}} + \frac{V_{BB}}{(1+\beta) R_E + R_{BB}}$$



$$I_B = \frac{I_C}{\beta} = \frac{I_S}{\beta} e^{\frac{V_{BE}}{V_T}}$$

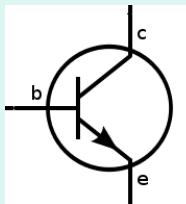
$$V_{BB} = V_{CC} \frac{R_{B2}}{R_{B1} + R_{B2}}, \quad R_{BB} = R_{B1} \parallel R_{B2}$$







# Operating point - $(V_{BE}, I_B)$

- $I_B$  vs  $V_{BE}$

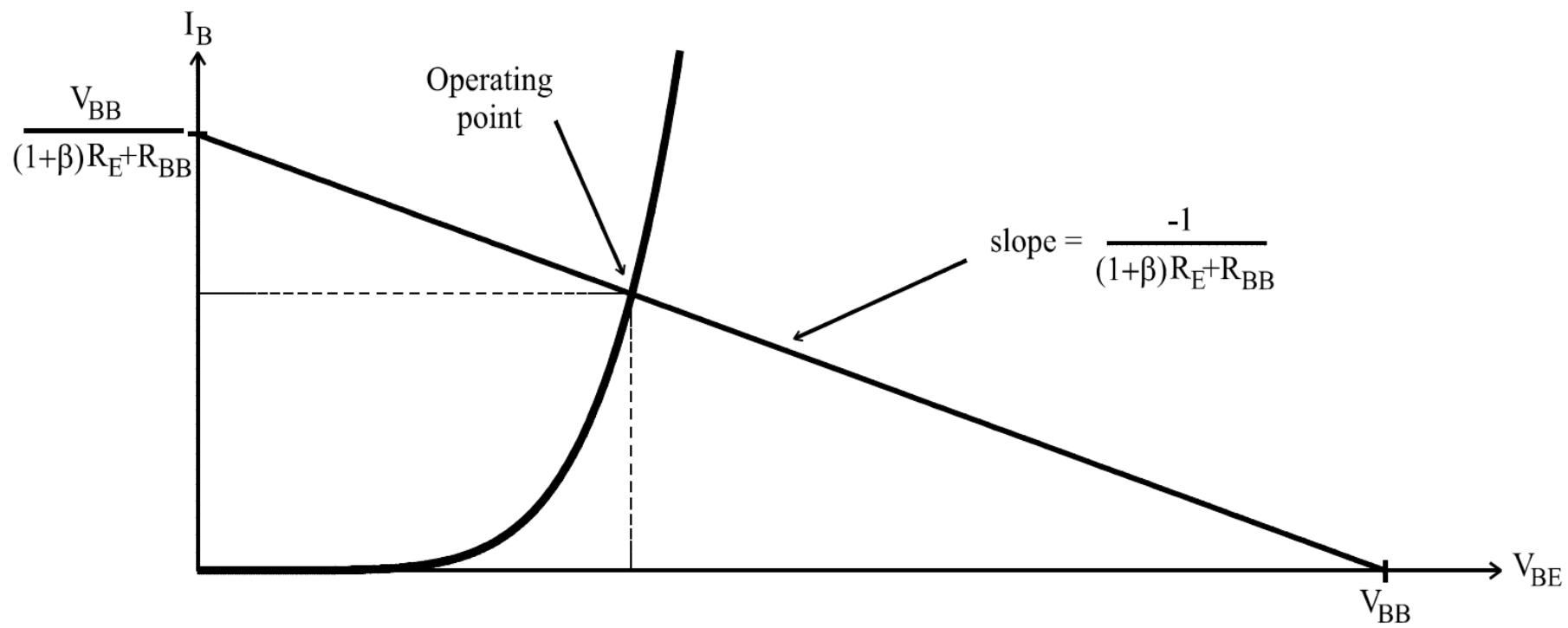

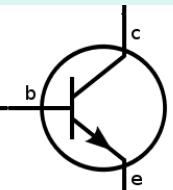

# Operating point ( $V_{CE}$ , $I_C$ )

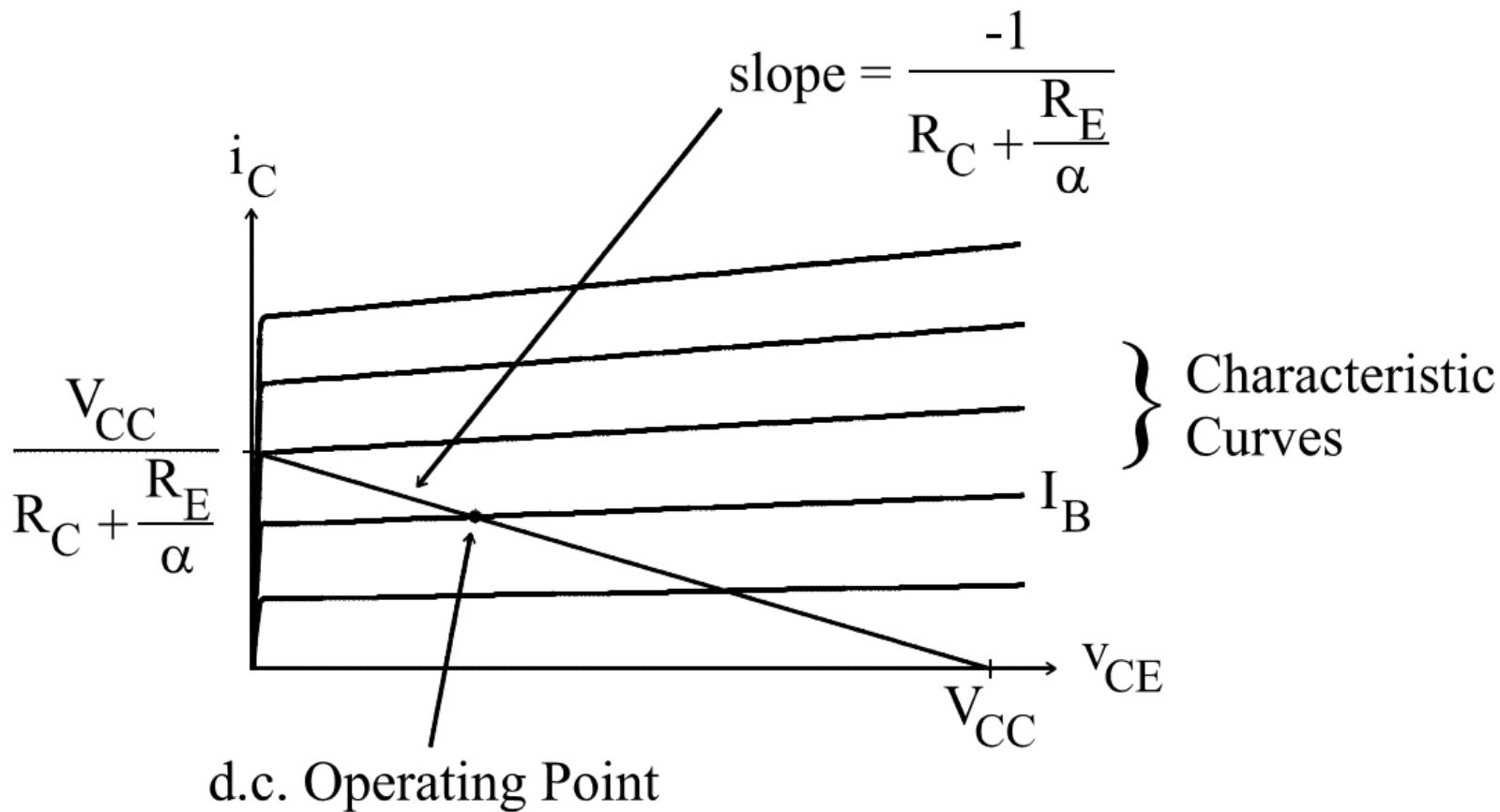

$$I_C = - \frac{V_{CE}}{\left( R_C + \frac{R_E}{\alpha} \right)} + \frac{V_{CC}}{\left( R_C + \frac{R_E}{\alpha} \right)}$$

