
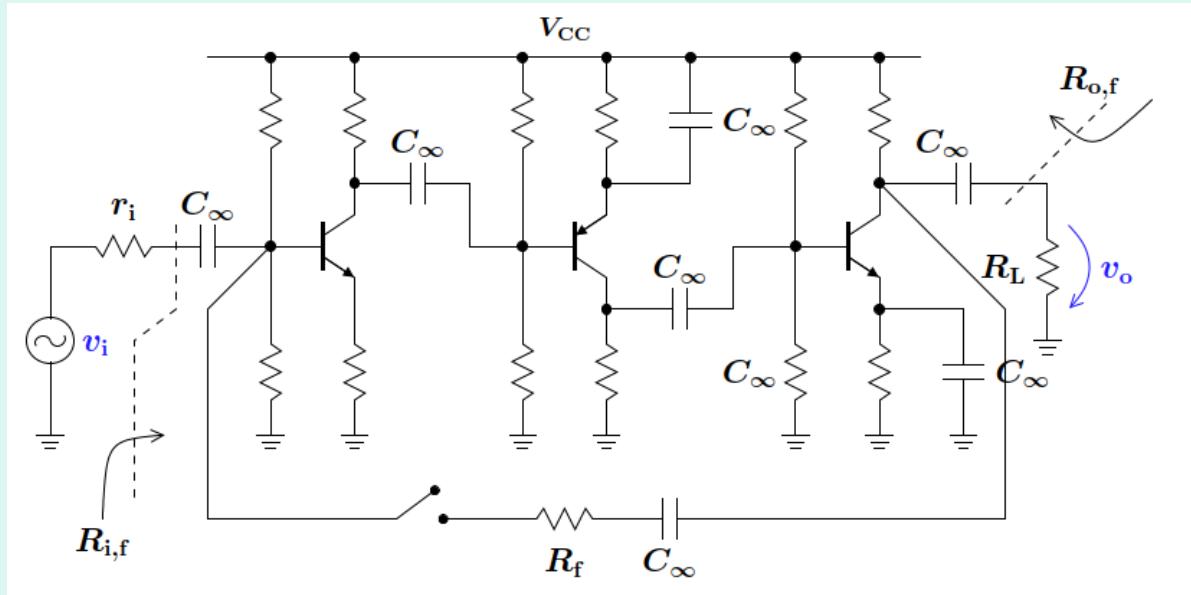


ELEC 301 - CE amplifier configuration

L13 - Oct 06

Instructor: Edmond Cretu

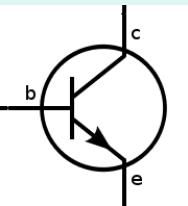




Administrative aspects


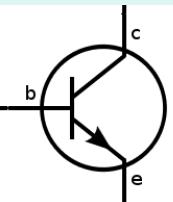
- Midterm - October 20, 3:30pm
- preparatory problems to be posted
- Topics - L01 - L15






Last time

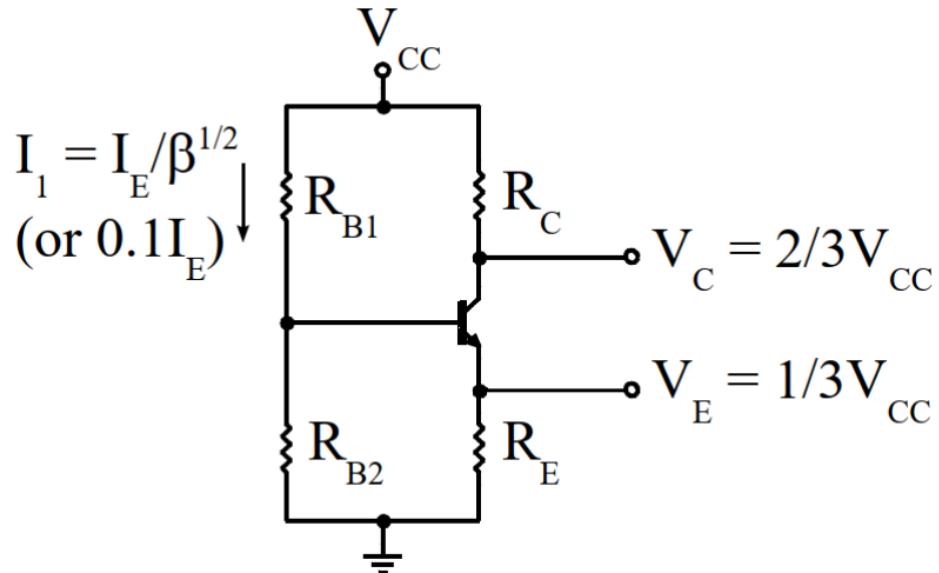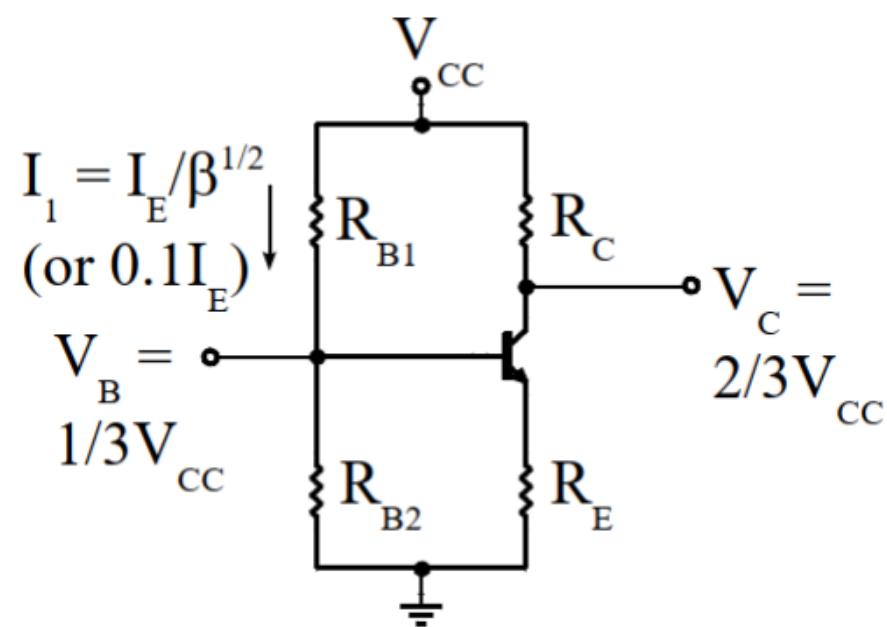- How to choose component values for setting the quiescent point of a BJT
- $\frac{1}{3}$ rd rule - two possible choices




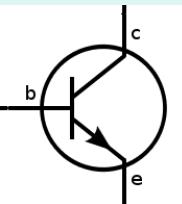

L13 Q01 - $\frac{1}{3}$ rule

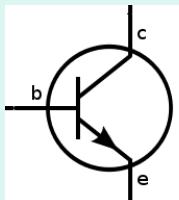
- What is the role of the $\frac{1}{3}$ rule?
 - A. To maximize the gain of the amplifier stage
 - B. To maximize the bandwidth of the amplifier stage
 - C. To simplify the computation of the resistor values that ensure a good quiescent point with a reasonable dynamic range
 - D. To compute the values of the capacitors for the AC gain






Common-emitter amplifier

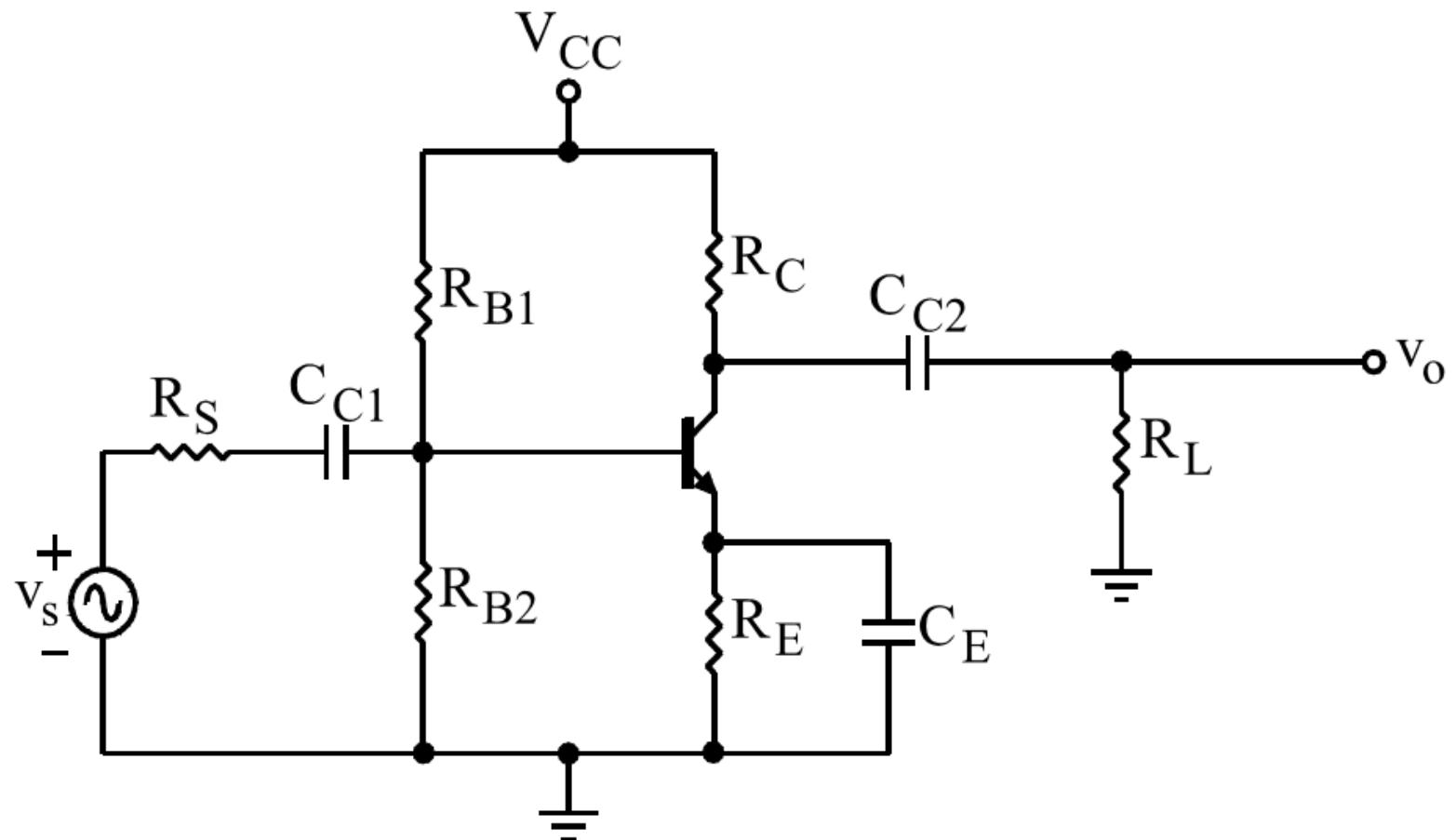
- We assume we have established the quiescent point (I_C , R_C , R_E , R_{B1} , R_{B2} are known)
- Focus now on small signal analysis - choosing C_{C1}, C_E, C_{C2}



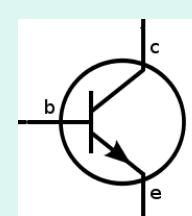


Complete small-signal model

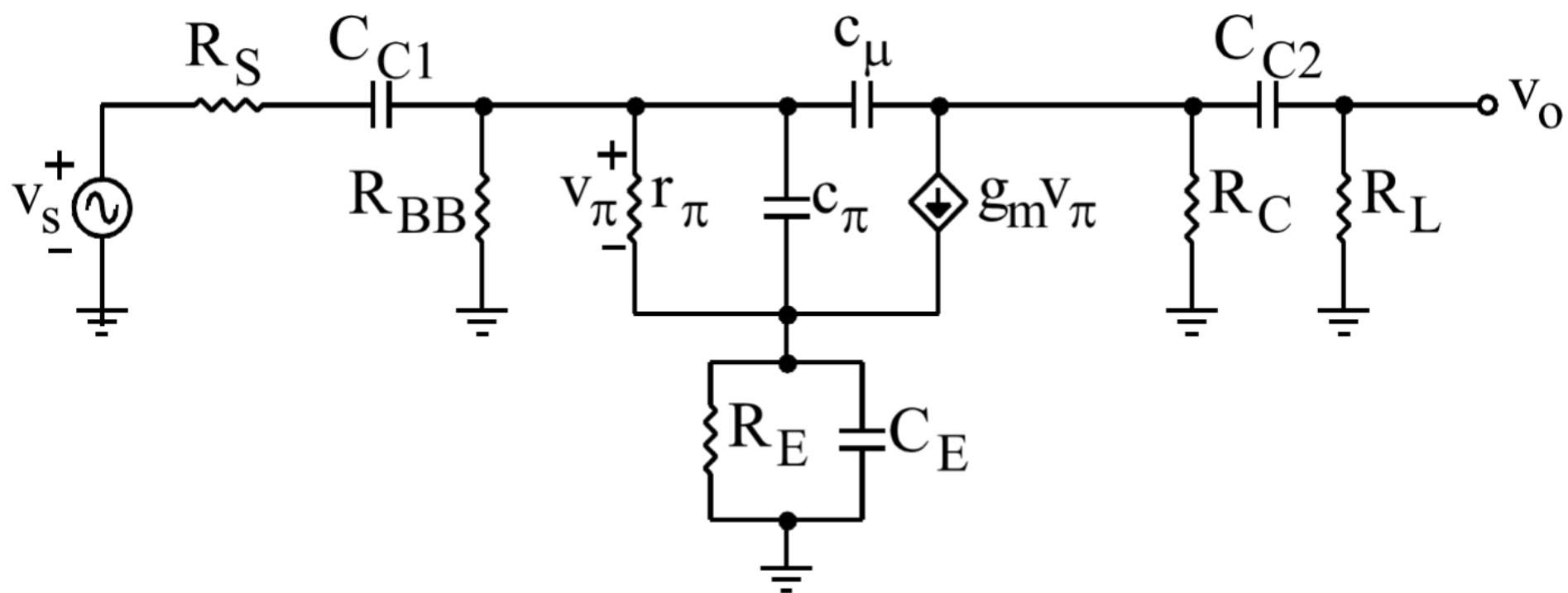- We use the hybrid- π BJT model ($r_o = \infty$)



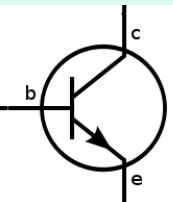
$$F(s) = \underbrace{F_L(s)}_{LF \text{ part}} \underbrace{A_M}_{Midband} \underbrace{F_H(s)}_{HF \text{ part}}$$
$$A_M = -g_m R_C \parallel R_L \frac{R_{BB} \parallel r_\pi}{R_{BB} \parallel r_\pi + R_S}$$






The HF small-signal model

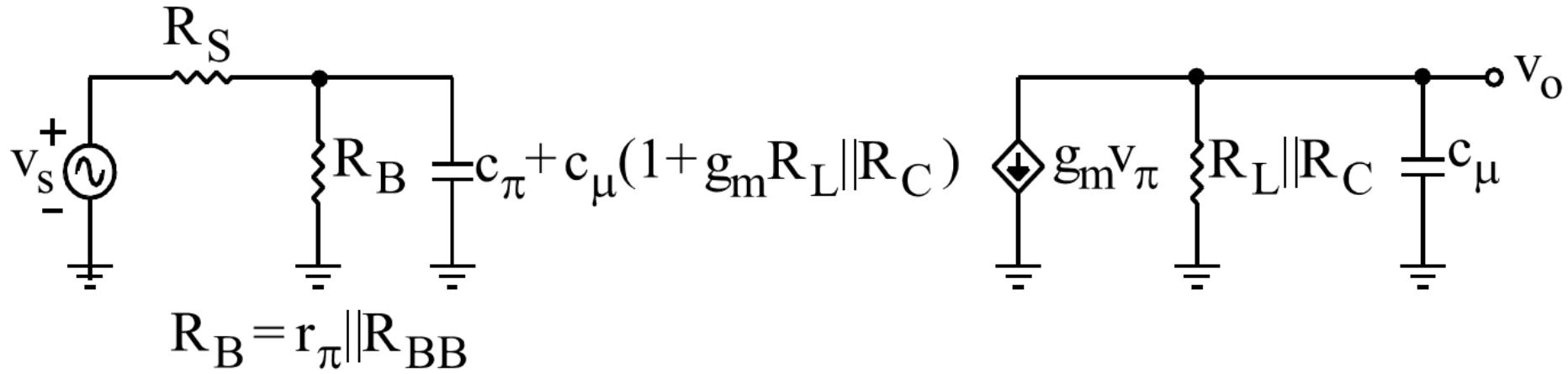- LF capacitances are short-circuited, Miller theorem applied




$$F_H(s) = \frac{\frac{1}{R_{BB} || r_\pi || R_S [c_\pi + c_\mu (1 + g_m R_C || R_L)]}}{\left(s + \frac{1}{R_{BB} || r_\pi || R_S [c_\pi + c_\mu (1 + g_m R_C || R_L)]} \right)} \cdot \frac{\frac{1}{R_C || R_L c_\mu}}{\left(s + \frac{1}{R_C || R_L c_\mu} \right)}$$



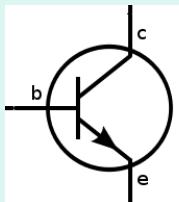

LF response $F_L(s)$

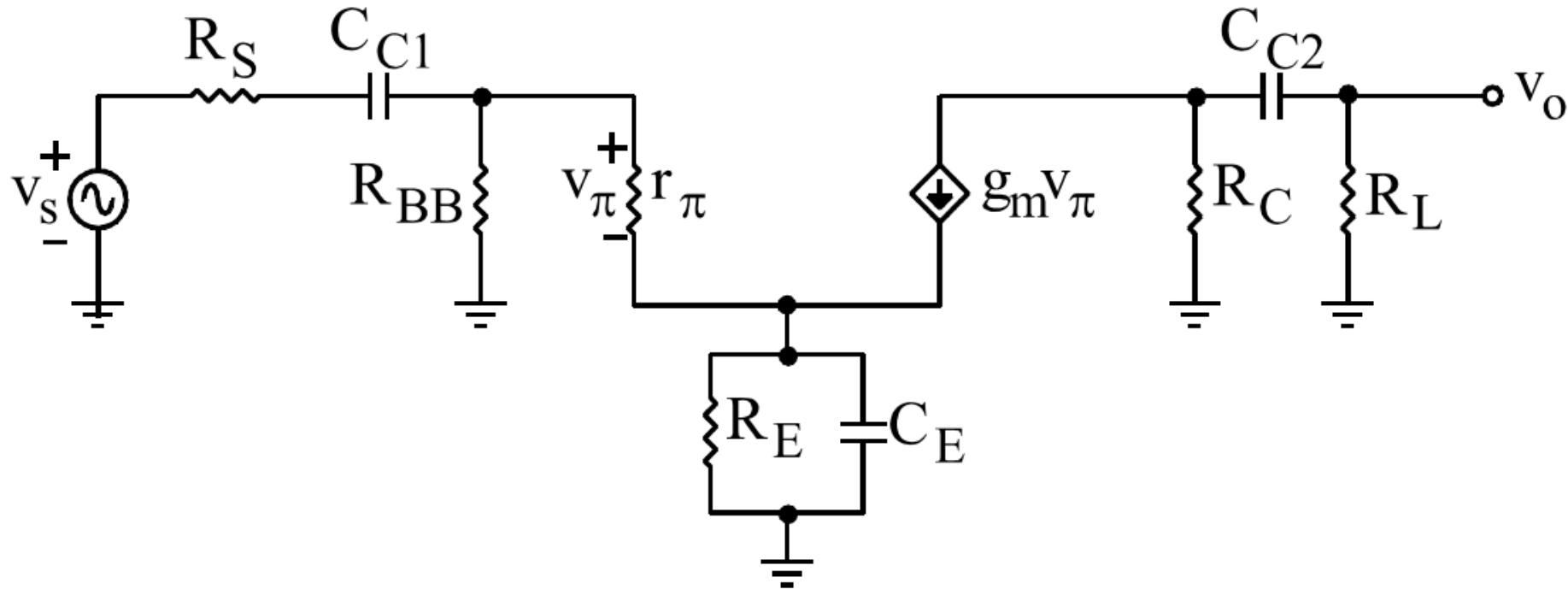
- $FL(s)$ is not straightforward - 3 poles + 3 zeros



$$F_L(s) \approx \left(\frac{s}{s + \omega_{Lp1}} \right) \left(\frac{s}{s + \omega_{Lp2}} \right) \left(\frac{s + \omega_{Lz3}}{s + \omega_{Lp3}} \right)$$




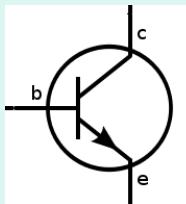C_{C1}, C_{C2} - introduce zeros at $\omega=0 \Rightarrow \omega_{Lz1}=\omega_{Lz2}=0$
 - For C_E - zero when $Y_E=0$



$F_L(s)$ - zeros (2)


- Compute the 3rd zero:

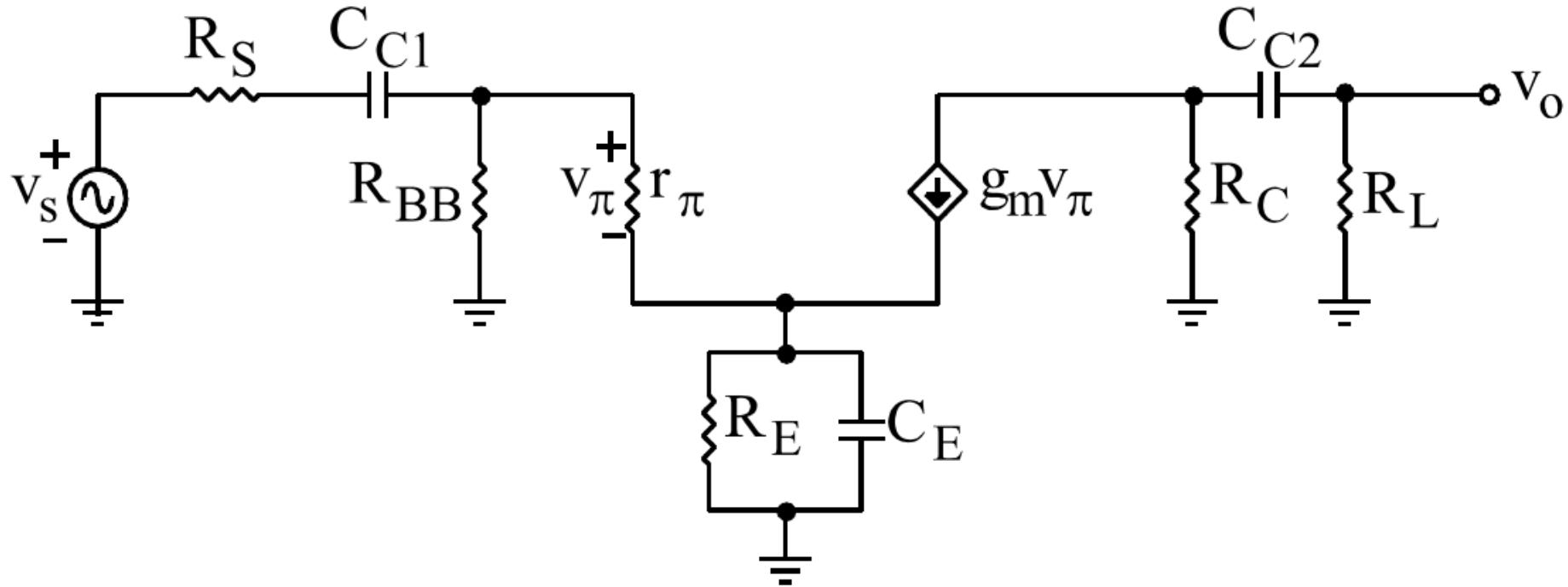

$$\omega_{Lz1} = \omega_{Lz2} = 0$$

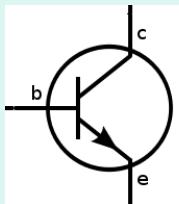
$$Y_E = \frac{1}{R_E} + sC_E = 0 \Leftrightarrow s_z = -\frac{1}{R_E C_E} \Rightarrow \omega_{Lz3} = \frac{1}{R_E C_E}$$






$F_L(s)$ - poles

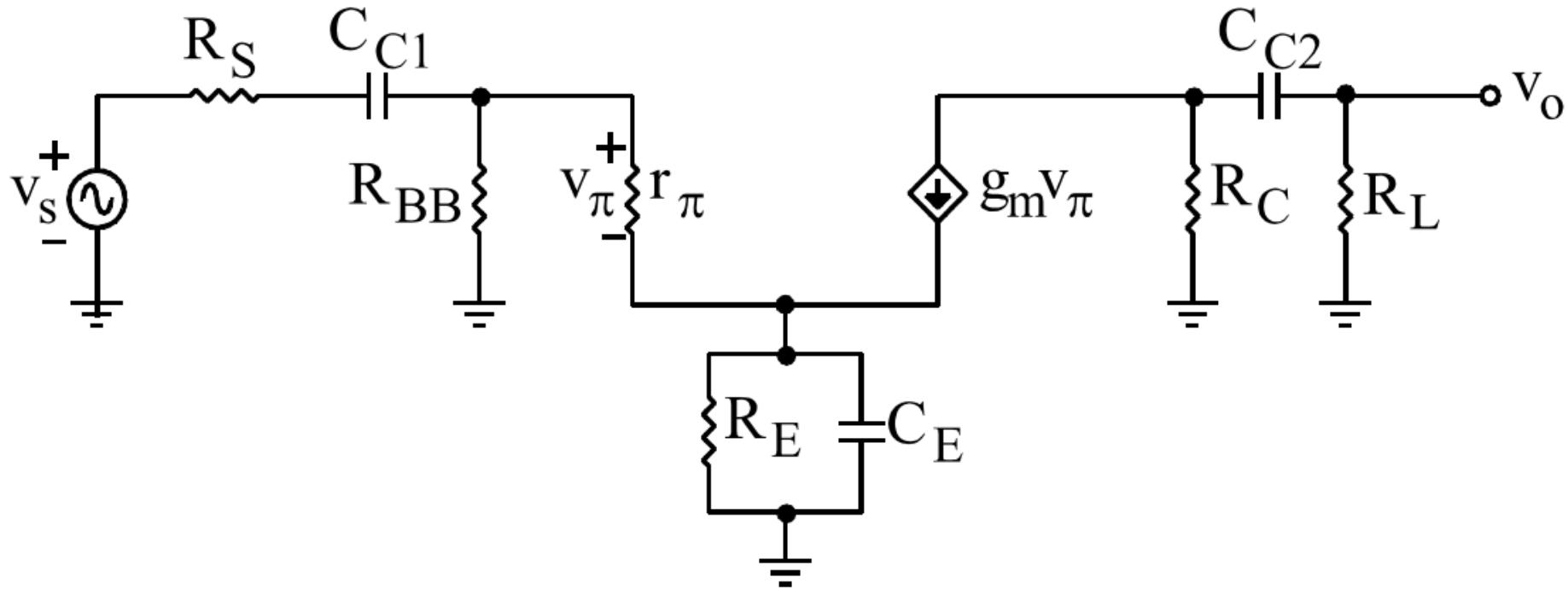- Simple for C_{C2} - output section decoupled from the rest



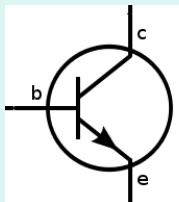
$$\tau_{C_{C2}} = (R_C + R_L) C_{C2} \Rightarrow \omega_{Lp1} = \frac{1}{(R_C + R_L) C_{C2}}$$




FL(s) - poles (2)

- We use the SC time-constant method

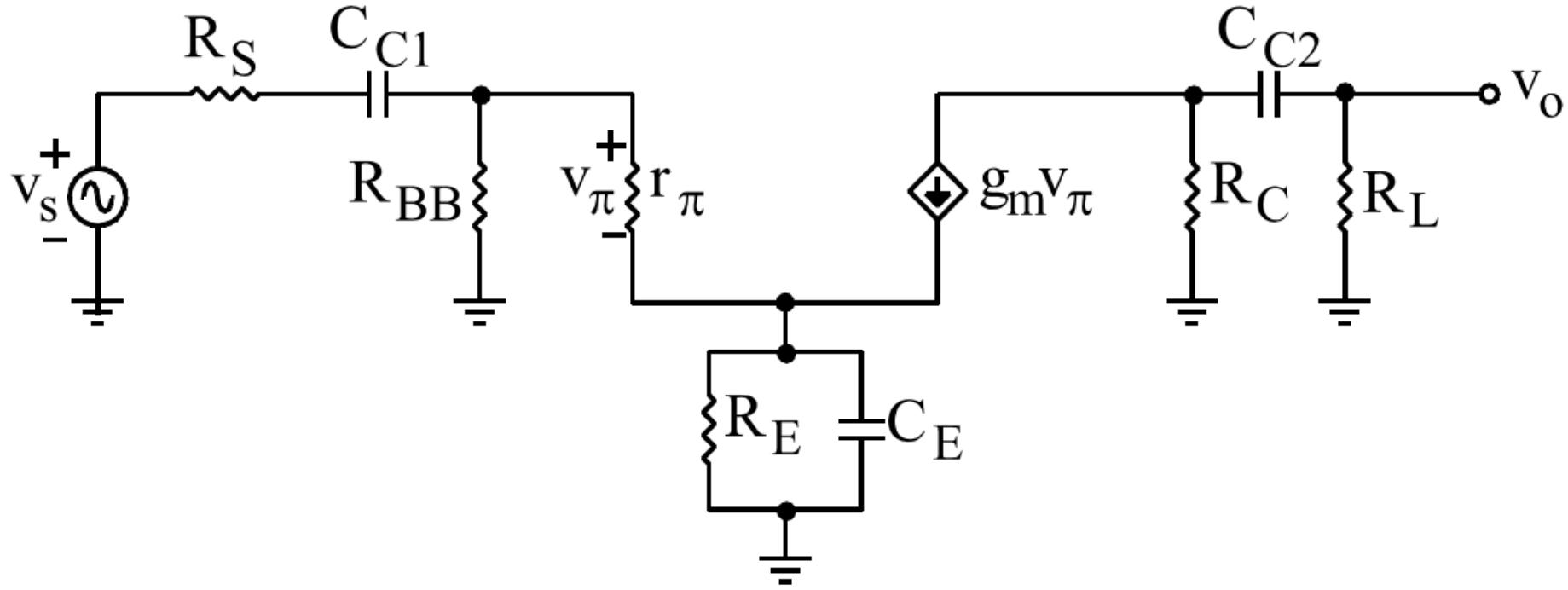

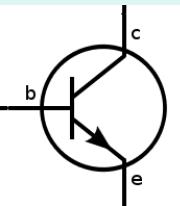
$$\tau_{C_{C1}}^{sc} = (R_S + R_{BB} \parallel r_\pi) C_{C1}$$





L13 Q02 - controlled sources

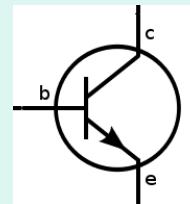- When we ‘passivate’ all the independent sources in the circuit, in order to compute an equivalent resistance, can we treat the controlled sources in the same way?
 - A. Yes, the same treatment applies to both independent and controlled sources
 - B. No, we should not ‘passivate’ the controlled sources




FL(s) - poles (3)

- The resistance seen across C_E :

$$\begin{cases} I_{Test} = \frac{V_{Test}}{R_E} - (\beta + 1)i_b \\ i_b = -\frac{V_{Test}}{r_\pi + R_S \parallel R_{BB}} \end{cases}$$


$$\Rightarrow I_{Test} = V_{Test} \left(\frac{1}{R_E} + (\beta + 1) \frac{1}{r_\pi + R_S \parallel R_{BB}} \right)$$
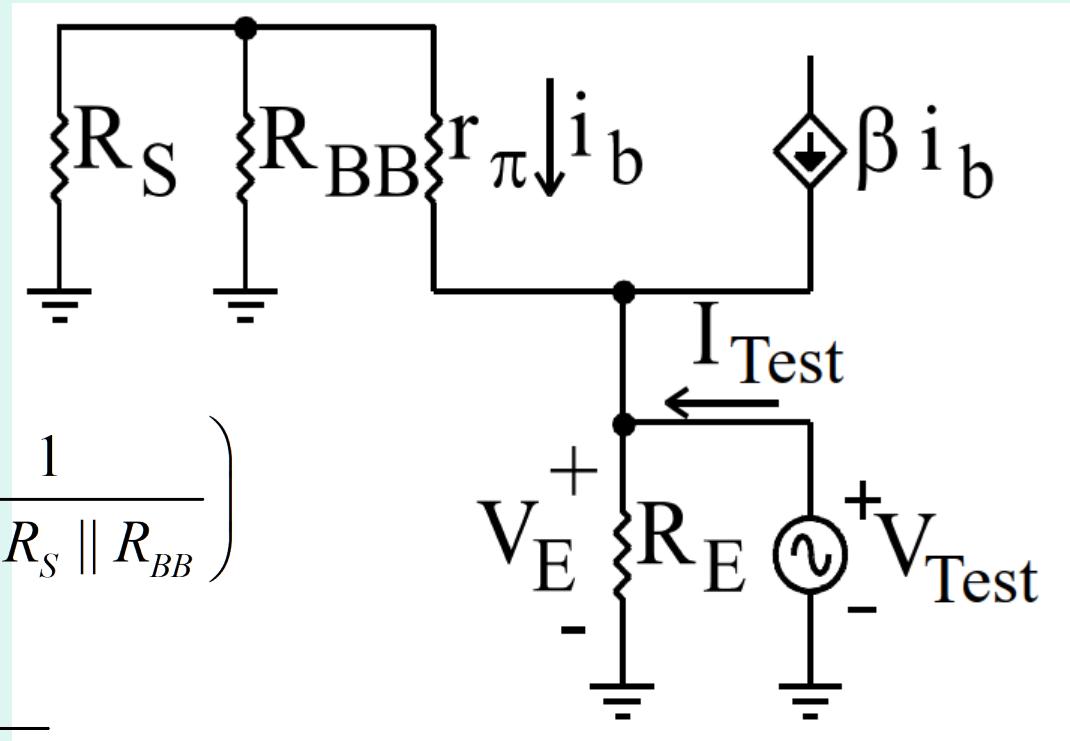
$$\frac{1}{R_{C_E}^{sc}} = \frac{1}{R_E} + (\beta + 1) \frac{1}{r_\pi + R_S \parallel R_{BB}}$$


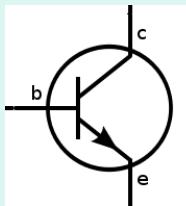
$$\tau_{C_E}^{sc} = \left(R_E \parallel \frac{r_\pi + R_S \parallel R_{BB}}{\beta + 1} \right) C_E$$





FL(s) - SC method

- Short-circuit time constant method for LF part:

$$\omega_{Lp1} + \omega_{Lp2} + \omega_{Lp3} = \frac{1}{\tau_{C_{c2}}^{sc}} + \frac{1}{\tau_{C_{cl}}^{sc}} + \frac{1}{\tau_{C_E}^{sc}}$$

$$\omega_{Lp1} = \frac{1}{\tau_{C_{c2}}^{sc}}$$

The output part of the circuit is decoupled from the input:


- It remains to compute only for the other two poles:
- Typically the smallest time constant is for C_E

$$\omega_{Lp2} + \omega_{Lp3} = \frac{1}{\tau_{C_{cl}}^{sc}} + \frac{1}{\tau_{C_E}^{sc}}$$

$$\tau_{C_E}^{sc} \ll \tau_{C_{cl}}^{sc}$$

$$\omega_{Lp2} + \omega_{Lp3} \approx \omega_{Lp3}$$

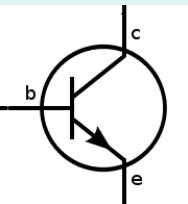
$$\omega_{Lp3} \approx \frac{1}{\tau_{C_E}^{sc}} = \frac{1}{\left(R_E \parallel \frac{r_\pi + R_{BB}}{1 + \beta} \parallel R_S \right) C_E}$$



L13 Q03 - pole approximation

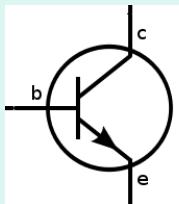- Can we automatically approximate the remaining sub-dominant pole with $1/\tau_{CC1}$?
 - A. Yes
 - B. No
 - C. It does not matter





FL(s) - finding last pole


- We cannot automatically say that:
- When C_{C1} is starting to conduct, C_E must still look like an OC \Rightarrow we need to treat C_E as an OC (OC time constant)


$$\omega_{Lp2} \approx \frac{1}{\tau_{C_{C1}}^{sc}}$$

$$\frac{V_{TEST}}{I_{TEST}} = r_\pi + (1 + \beta)R_E$$

$$\tau_{C_{C1}}^{oc} = [R_s + R_{BB}] \parallel [r_\pi + (1 + \beta)R_E] C_{C1}$$

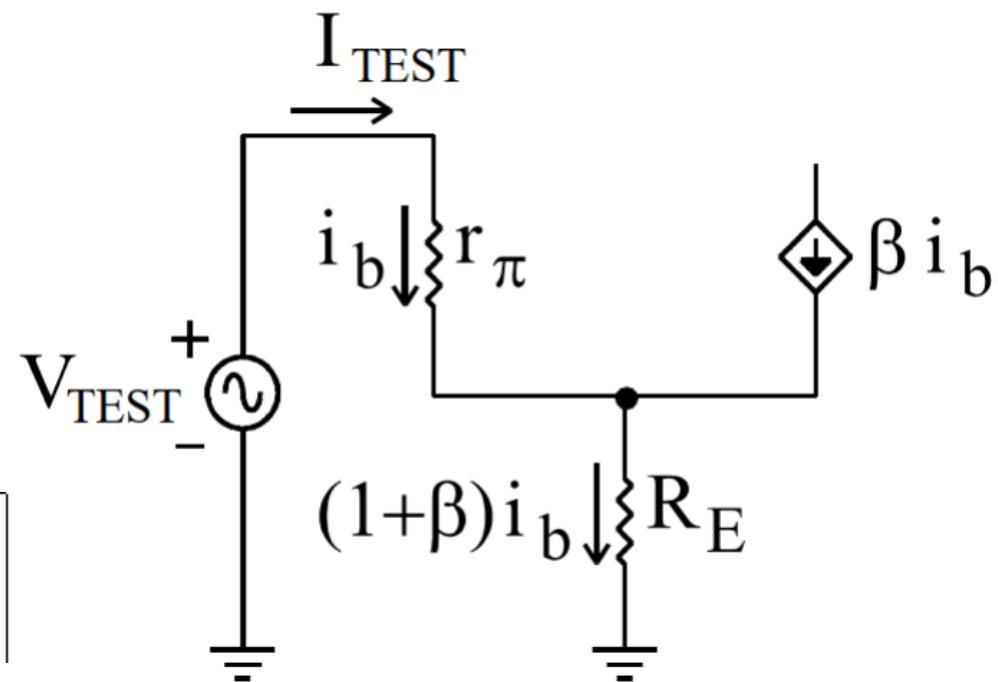
$$\omega_{Lp2} = \frac{1}{[R_s + R_{BB}] \parallel [r_\pi + (1 + \beta)R_E] C_{C1}}$$



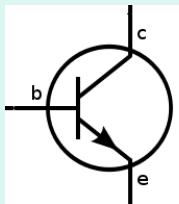


$$F_L(s)$$

- Final form:

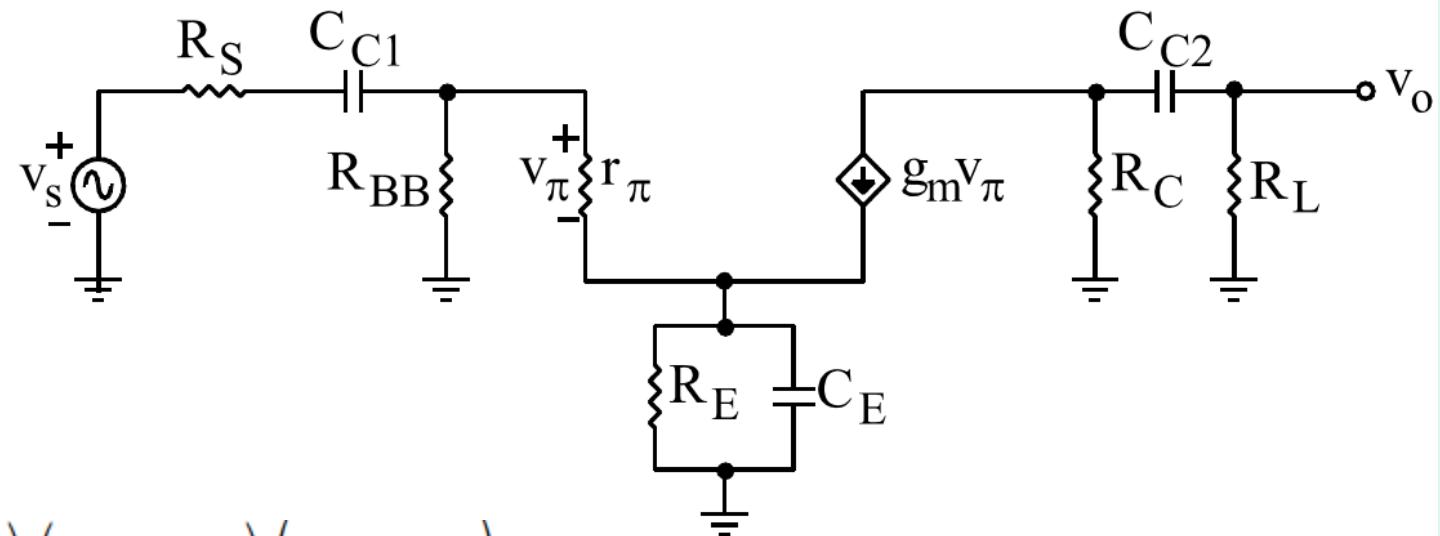

$$F_L(s) \approx \left(\frac{s}{s + \omega_{Lp1}} \right) \left(\frac{s}{s + \omega_{Lp2}} \right) \left(\frac{s + \omega_{Lz3}}{s + \omega_{Lp3}} \right)$$
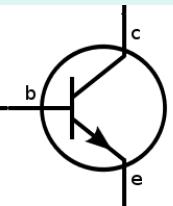
$$F_L(s) \approx \left(\frac{s}{s + \frac{1}{(R_C + R_L)C_{C2}}} \right) \left(\frac{s}{s + \frac{1}{(R_S + R_{BB})[(r_\pi + (1 + \beta)R_E)]C_{C1}}} \right) \left(\frac{s + \frac{1}{R_E C_E}}{s + \frac{1}{(R_E \parallel \frac{r_\pi + R_{BB}}{1 + \beta} R_S) C_E}} \right)$$



Choosing capacitor values

- We made the choice $C_E - \omega_{Lp3}$ and $C_{C1} - \omega_{Lp2}$, assuming $\omega_{Lp3} \gg \omega_{Lp2}$
- C_E typically ‘sees’ the smallest resistance $\Rightarrow \omega_{Lp3}$ gives the dominant LF pole (highest frequency)
- C_{C1} typically ‘sees’ the largest resistance $\Rightarrow \omega_{Lp2}$ is typically chosen to be the lowest frequency
- C_{C2} typically ‘sees’ an intermediate resistance $\Rightarrow \omega_{Lp1}$ is typically chosen so that $\omega_{Lp3} > \omega_{Lp1} > \omega_{Lp2}$ (first sub-dominant pole)
- We can choose the values for C_E, C_{C1}, C_{C2} (with a reasonable spacing between poles) - the approach typically results in the lowest circuit cost



