
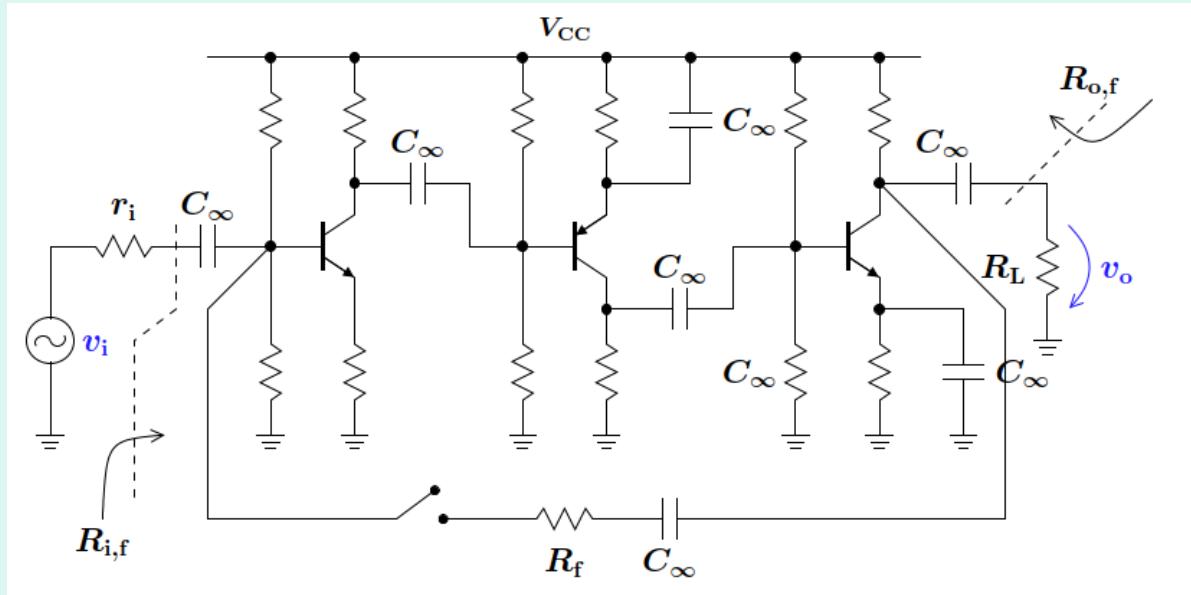


# ELEC 301 - Real opamps

L20 - Oct 27


Instructor: Edmond Cretu

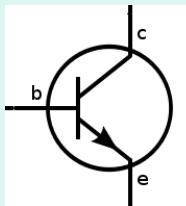



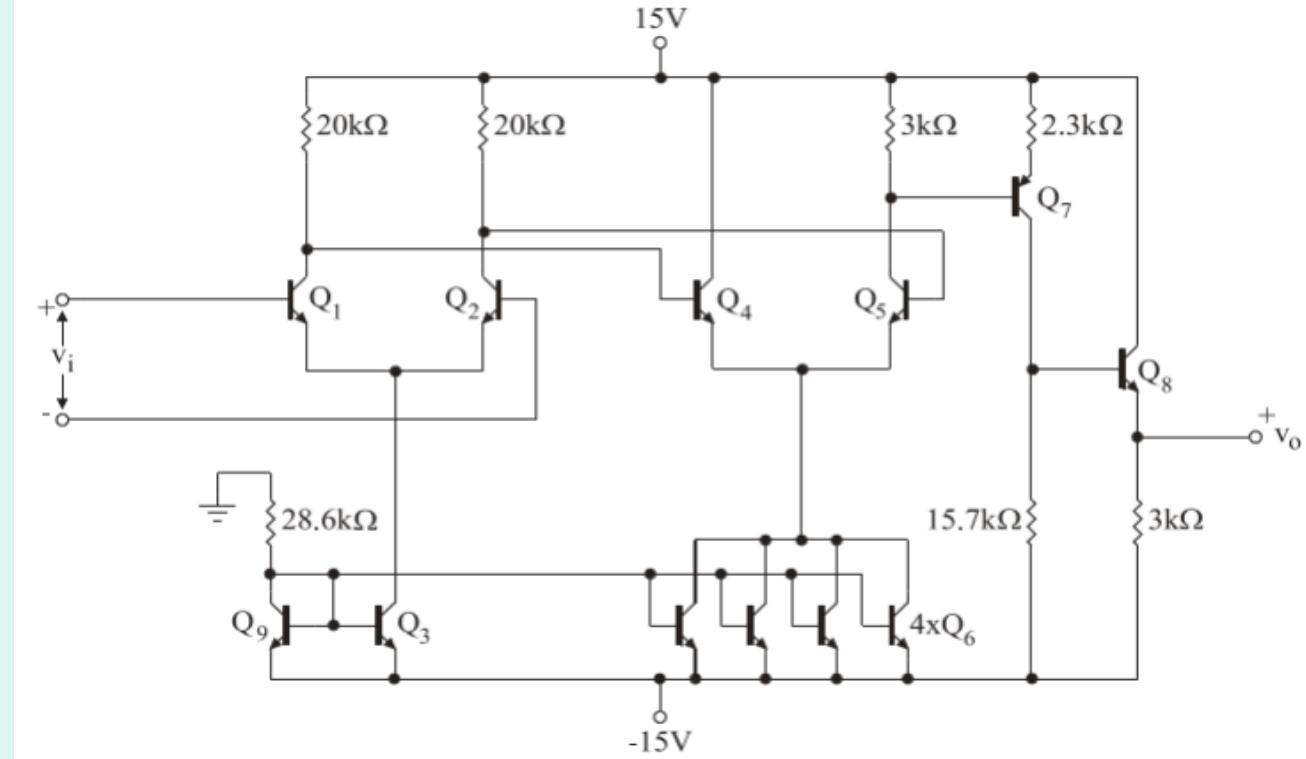
## Last time

- Frequency behavior of differential amplifier stage
- Example - analysis of a simple BJT operational amplifier




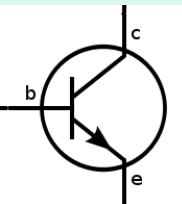
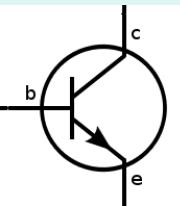
## L20 Q01 opamp

- Why did we use a common-collector configuration for the output stage?
  - A. Because it has a current amplification
  - B. Because it has a voltage amplification
  - C. Because it gives the lowest output resistance
  - D. Because it gives the highest output resistance





# Opamp non-idealities


- A real opamp circuit - measures of imperfections (deviations from the ideal opamp model)
- **Slew-rate** = maximum rate of change of the output waveform  
$$SR = (dv_O/dt)_{\max}$$
- Exm: unity-gain buffer configuration, harmonic input voltage  $\Rightarrow$  max input signal slope when  $\sin(\omega t) = 0$

$$\max \left( \frac{dv_i}{dt} \right) \Bigg|_{v_i = V_i \sin \omega t} = \omega V_i \leq SR$$

The maximum input frequency that will generate distortions in the output signal:

$$\omega_{Max} = \frac{SR}{V_i}$$



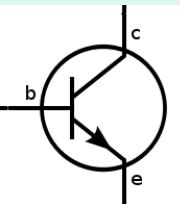

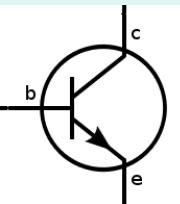
# Full-power bandwidth

- **Full-power bandwidth** = the bandwidth at which the amplifier can deliver maximum power to the load without distortions, for a given maximum output voltage

$$\omega_m V_{\max} = SR \Rightarrow f_m = \frac{SR}{2\pi V_{\max}}$$






# Common-mode rejection ratio

- Only a CM voltage is applied as input - ideally the output  $v_o = 0$
- In a real opamp there are both gains for the DM and the CM input voltage (cause: asymmetries in the input stage)

$$\left. \begin{array}{l} v_+ = v_{icm} + \frac{v_{id}}{2} \\ v_- = v_{icm} - \frac{v_{id}}{2} \end{array} \right\} \rightarrow \left. \begin{array}{l} v_{icm} = \frac{v_+ + v_-}{2} \\ v_{id} = v_+ - v_- \end{array} \right\} \rightarrow v_o = A_d v_{id} + A_{cm} v_{icm}$$


Common-mode rejection ratio (CMRR):

$$CMRR \stackrel{\text{def}}{=} \frac{|A_d|}{|A_{cm}|} \Leftrightarrow CMRR_{dB} = 20 \log \frac{|A_d|}{|A_{cm}|}$$

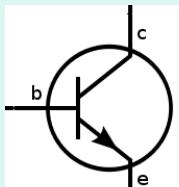
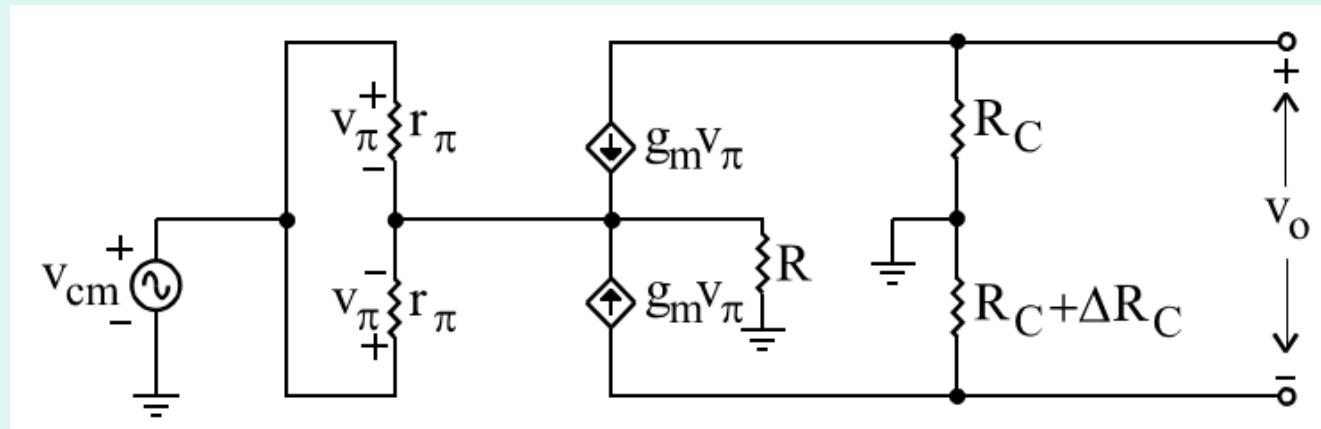
# CM excitation of the differential stage

- Small signal model,  $R_C$  asymmetry, equivalent transistors, finite output resistance  $R$  of the current source
- Evaluate the CM gain:



$$v_o = -g_m v_\pi [R_C - (R_C + \Delta R_C)]$$


$$v_o = g_m v_{cm} \frac{\Delta R_C}{1 + 2g_\pi R(\beta + 1)} = v_{cm} \frac{\Delta R_C}{\frac{1}{g_m} + 2R} \frac{\beta + 1}{r_\pi} \frac{r_\pi}{\beta}$$

$$v_o \approx \alpha \frac{\Delta R_C}{2R} v_{cm} \Rightarrow A_{cm} \approx \frac{\Delta R_C}{2R}$$

$$v_\pi = \frac{\frac{r_\pi}{2} v_{cm}}{\frac{r_\pi}{2} + R(\beta + 1)}$$

$$CMMR = \frac{|A_d|}{|A_{cm}|} = \frac{g_m R_C}{\frac{\Delta R_C}{2R}} = g_m 2R \frac{R_C}{\Delta R_C}$$




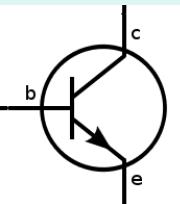
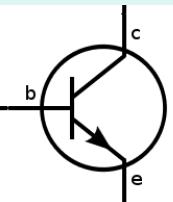
# Introduction to feedback networks


- Feedback uses:
  - de-sensitize gain
  - reduced distortion
  - extend bandwidth
  - control input and output impedances
  - increase signal-to-noise ratio
  - (positive feedback) - active oscillators




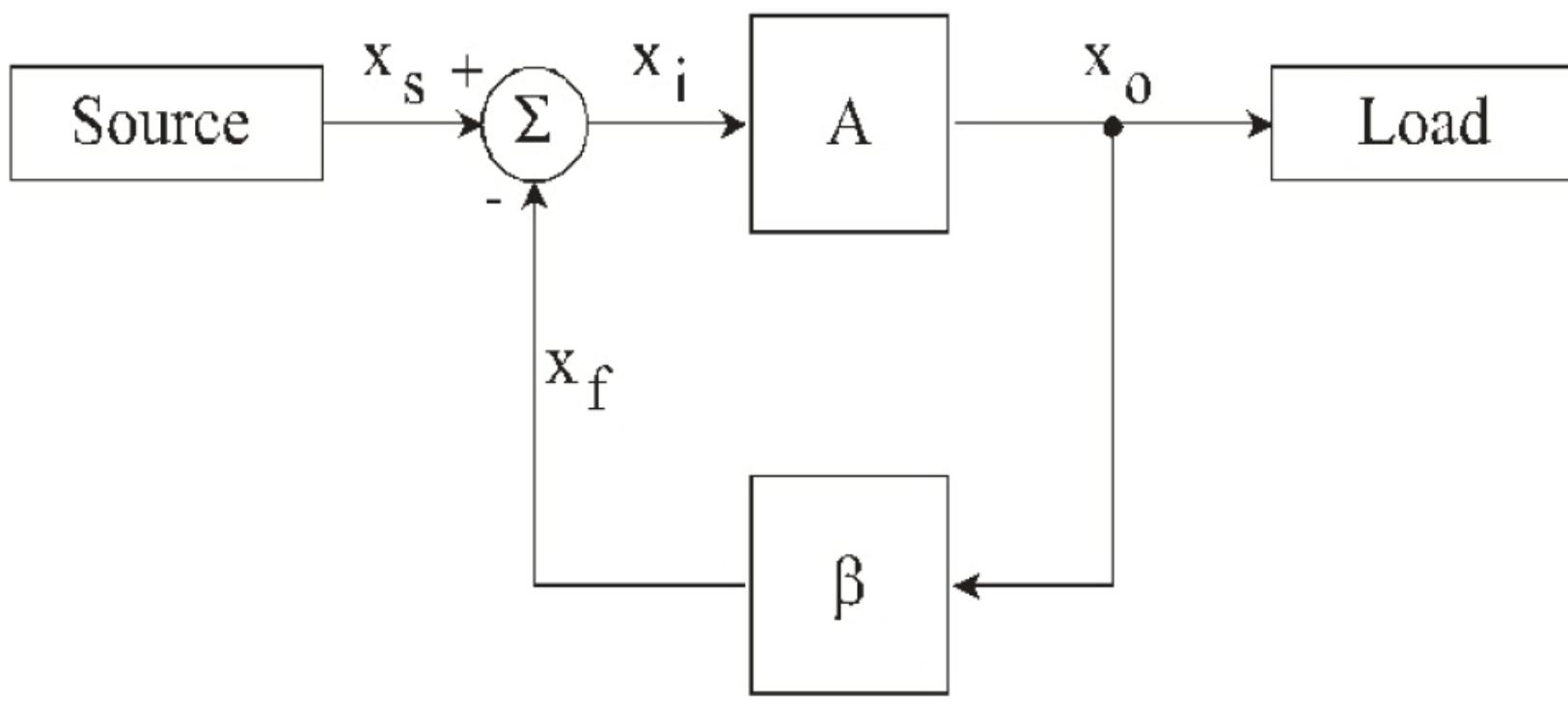
# Information flow perspective


- The signal  $x_s$  can be a voltage or a current
- Generic signal flowchart



$$\left. \begin{array}{l} x_o = Ax_i \\ x_f = \beta x_o \\ x_i = x_s - x_f \end{array} \right\} \Rightarrow A_f = \frac{x_o}{x_s} = \frac{Ax_i}{x_i + x_f} = \frac{A}{1 + A\beta}$$

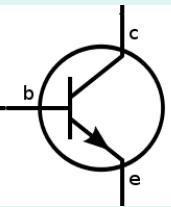$A\beta$  = "the loop gain"  
 $1 + A\beta$  = "the amount of feedback"





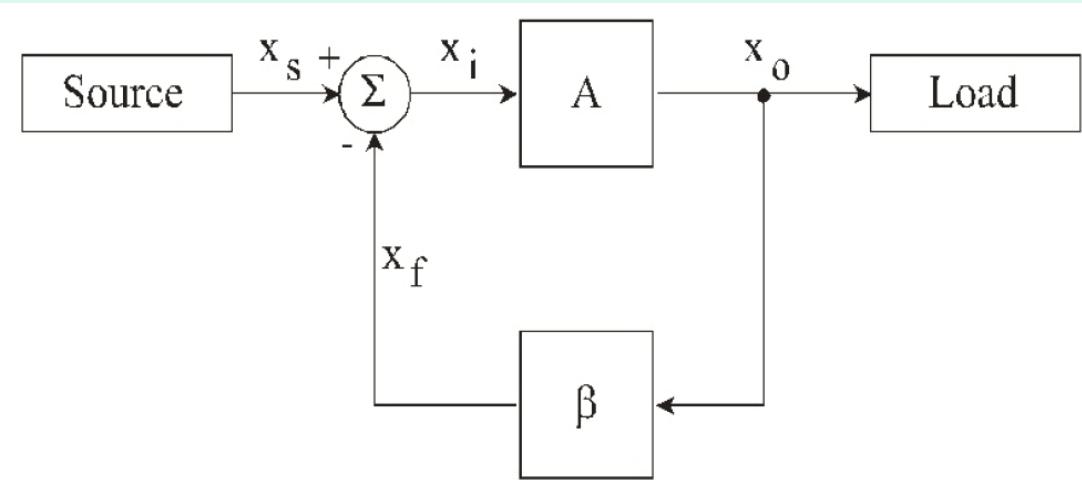
# Information flow - negative feedback amplifiers

- Usually the loop gain is very large due to A:  $A\beta \gg 1 \Rightarrow$  the gain is the feedback amplifier is entirely determined by the feedback network

$$A_f = \frac{A}{1 + A\beta} = \frac{1}{\beta + \frac{1}{A}} = \frac{1}{\beta} \frac{1}{1 + \frac{1}{A\beta}} \underset{A\beta \gg 1}{\approx} \frac{1}{\beta} \left(1 - \frac{1}{A\beta}\right) \approx \frac{1}{\beta}$$



$$x_i = \frac{x_o}{A} = \frac{x_s}{1 + A\beta} = \frac{x_s}{A\beta} \frac{1}{1 + \frac{1}{A\beta}} \underset{A\beta \gg 1}{\approx} 0$$

$$x_f = \beta x_o \underset{A\beta \gg 1}{\approx} \beta \frac{x_s}{\beta} = x_s$$



