
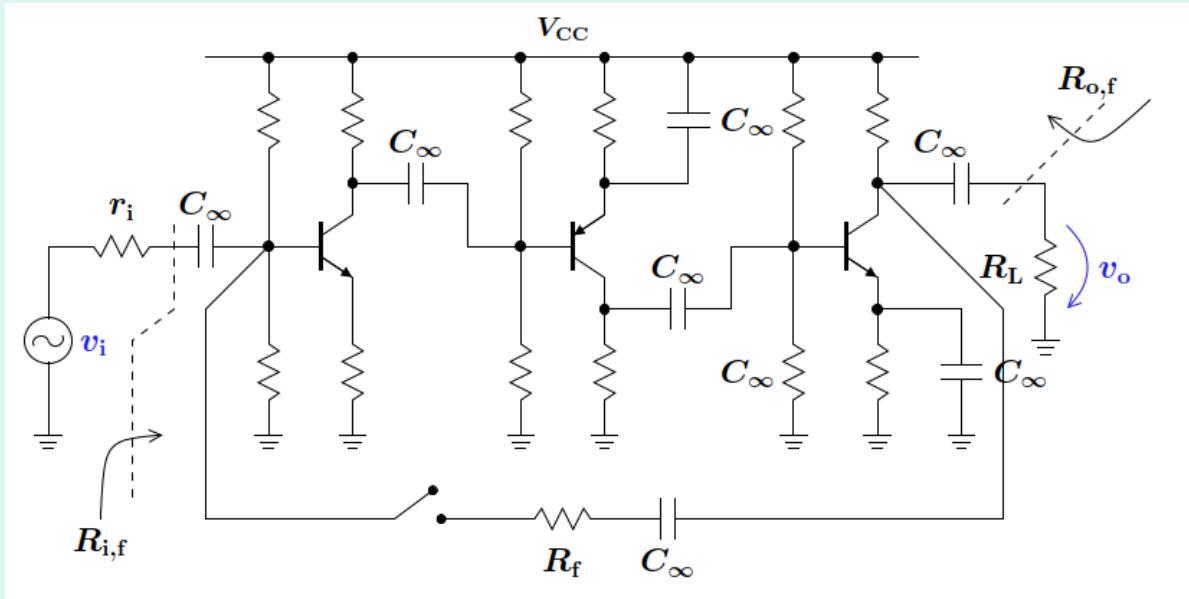


ELEC 301 - Feedback in circuits

L21 - Oct 28

Instructor: Edmond Cretu

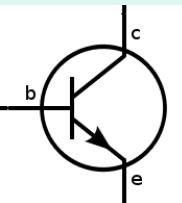




Last time: feedback networks


- Feedback theory:
 - Harold Black (Western Electric Co.), 1928 - amplifiers with stable gain for transatlantic telephone repeaters
 - Negative (degenerative) vs. positive (regenerative) feedback
- Feedback uses:
 - de-sensitize gain (gain less sensitive to variations in the values of components)
 - reduced nonlinear distortion (constant gain, independent of signal level)
 - extend operating bandwidth
 - control input and output impedances (Z_{in} , Z_{out})
 - increase signal-to-noise ratio
 - (positive feedback) - active oscillators



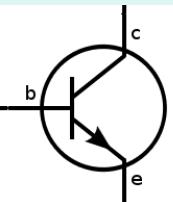

Information flow perspective

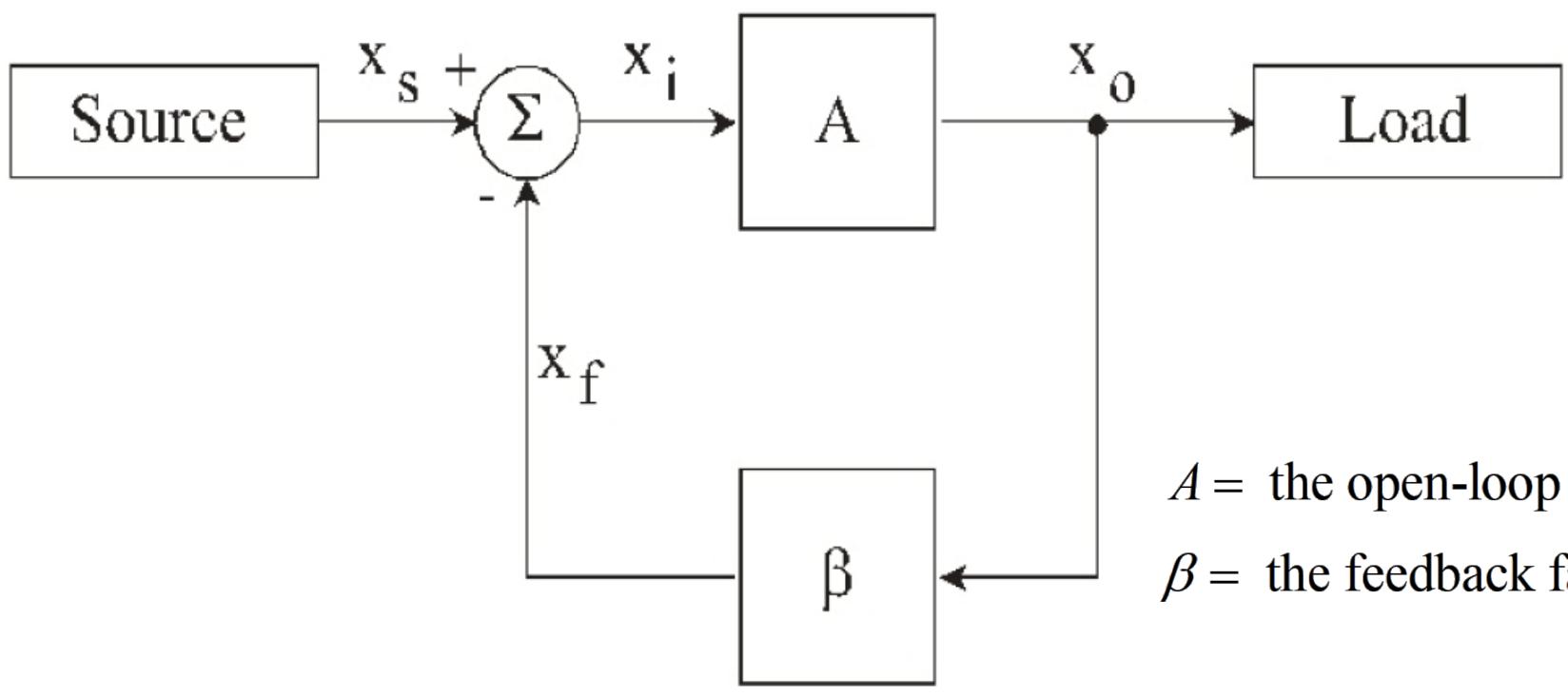
- The signal x_s can be a voltage or a current
- Generic signal flowchart



$$\left. \begin{array}{l} x_o = Ax_i \\ x_f = \beta x_o \\ x_i = x_s - x_f \end{array} \right\} \Rightarrow A_f = \frac{x_o}{x_s} = \frac{Ax_i}{x_i + x_f} = \frac{A}{1 + A\beta}$$

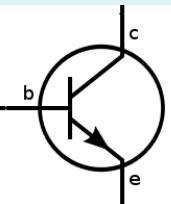$A\beta = \text{"the loop gain"}$
 $1 + A\beta = \text{"the amount of feedback"}$





Information flow - negative feedback amplifiers

- Usually the loop gain is very large due to A: $A\beta \gg 1 \Rightarrow$ the gain is the feedback amplifier is entirely determined by the feedback network


$$A_f = \frac{A}{1 + A\beta} = \frac{1}{\beta + \frac{1}{A}} = \frac{1}{\beta} \frac{1}{1 + \frac{1}{A\beta}} \underset{A\beta \gg 1}{\approx} \frac{1}{\beta} \left(1 - \frac{1}{A\beta}\right) \approx \frac{1}{\beta}$$


A_f = the closed-loop gain

x_i = the "error signal"

$$x_i = \frac{x_o}{A} = \frac{x_s}{1 + A\beta} = \frac{x_s}{A\beta} \frac{1}{1 + \frac{1}{A\beta}} \underset{A\beta \gg 1}{\approx} 0$$

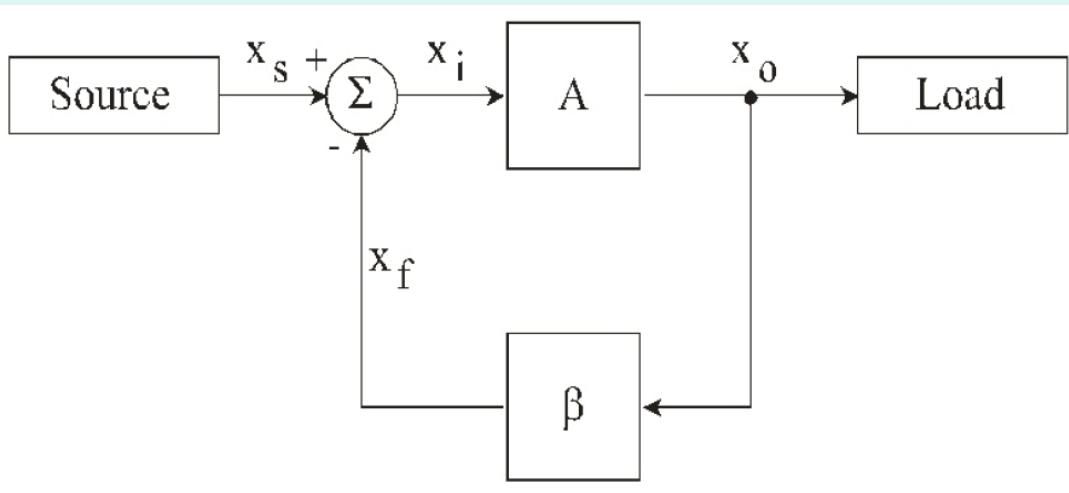
$$x_f = \beta x_o \underset{A\beta \gg 1}{\approx} \beta \frac{x_s}{\beta} = x_s$$



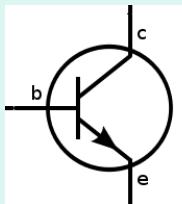


Loop gain

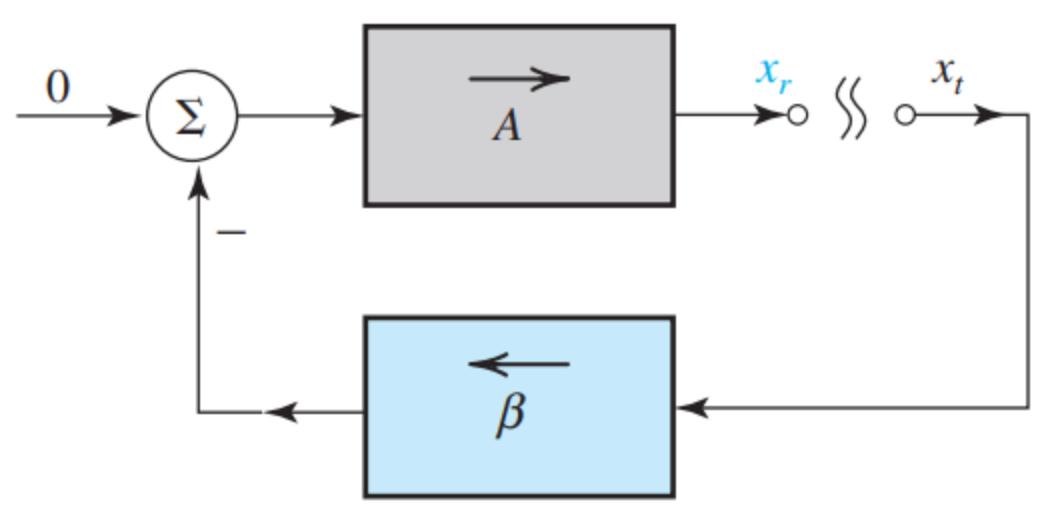- Breaking the feedback loop to determine the loop gain
- set $x_s = 0$




$$A\beta = -\frac{x_r}{x_t}$$

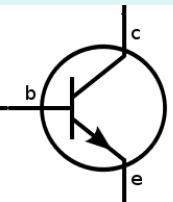

Information flow to energy flow


- signals mapped into voltages/currents => 4 categories of feedback circuit architectures


Input signal x_s	Output signal x_o	Feedback type	Remarks
voltage v_s	voltage v_o	series-shunt	Voltage amplifier A_{vf} (Z_{in} high, Z_{out} low)
current i_s	voltage v_o	shunt-shunt	Transimpedance amplifier Z_f (Z_{in} low, Z_{out} low)
voltage v_s	current i_o	series-series	Transadmittance amplifier Y_f (Z_{in} high, Z_{out} high)
current i_s	current i_o	shunt-series	Current amplifier A_{if} (Z_{in} low, Z_{out} high)

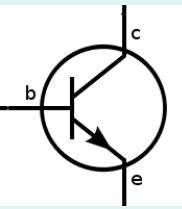

Series-shunt (series-parallel) feedback topology

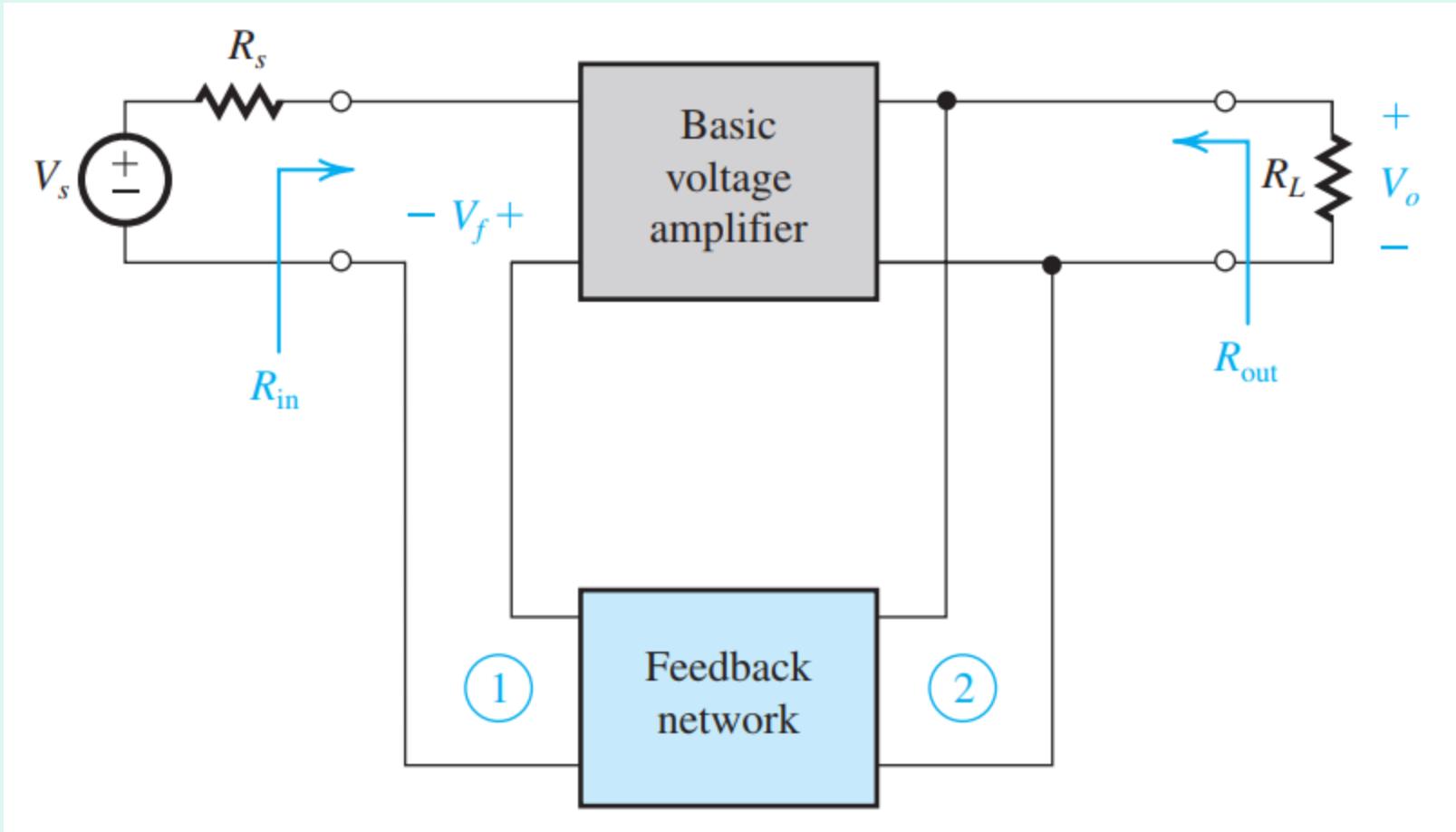
- Feedback voltage amplifier (voltage-mixing, voltage sampling)




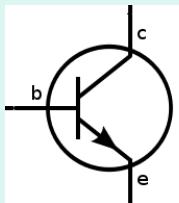

Series-series feedback

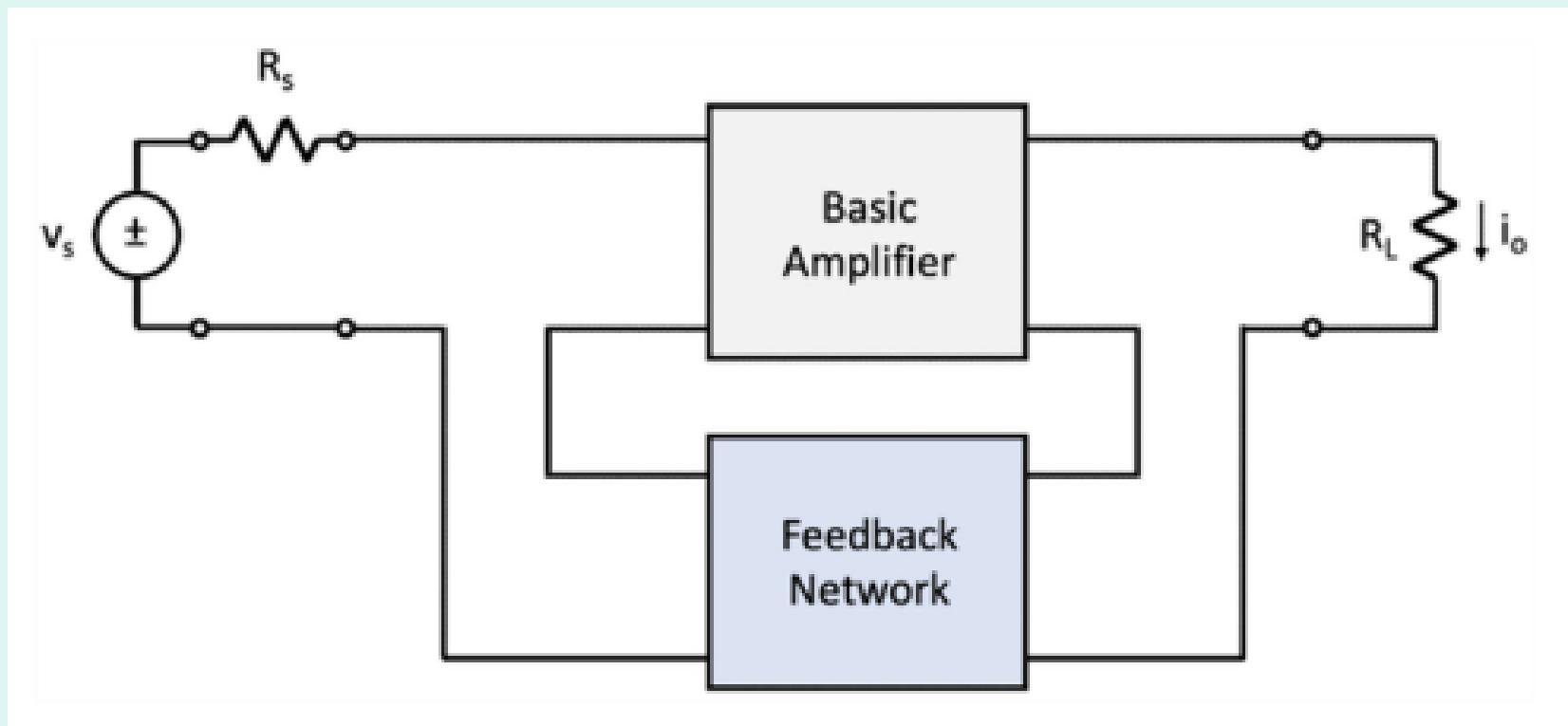
- Transadmittance amplifier (voltage-mixing/current sampling)




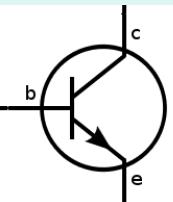

Shunt-series feedback

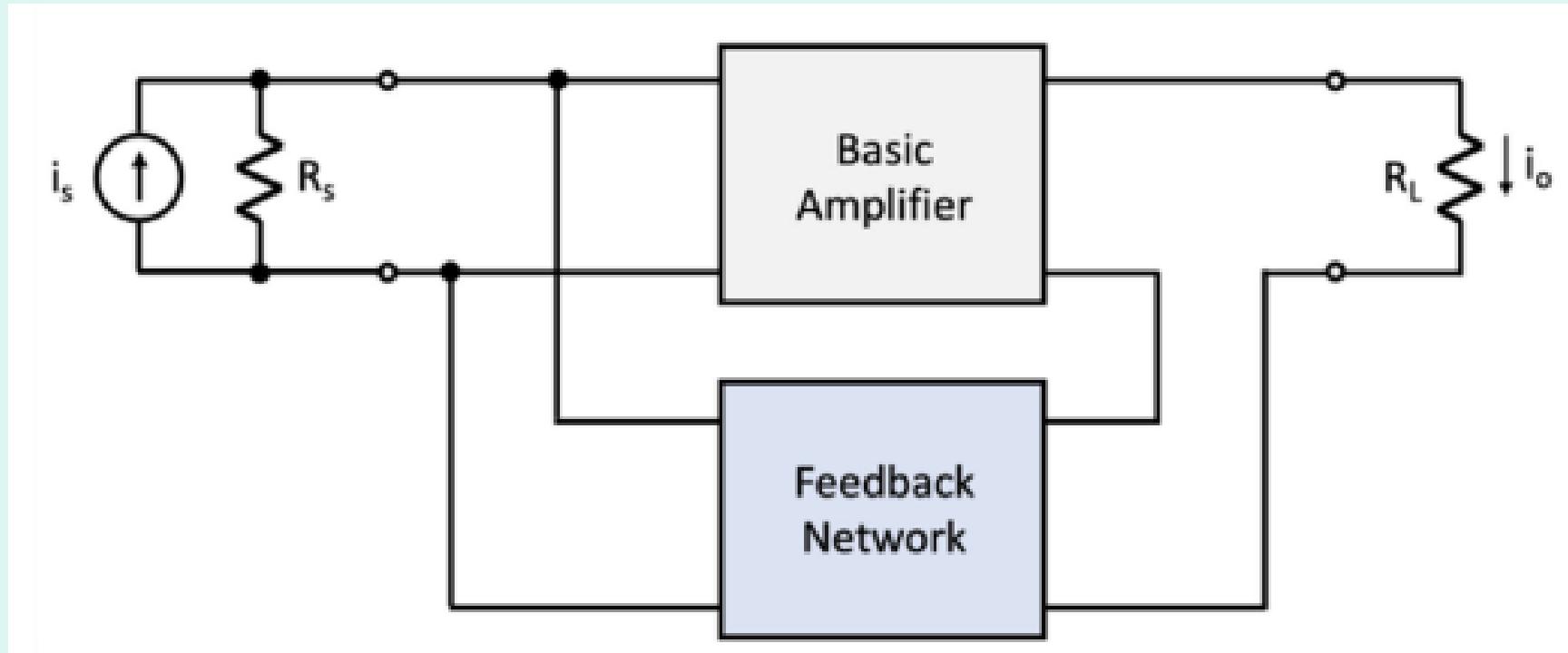
- Current amplifier - current-mixing/current sampling




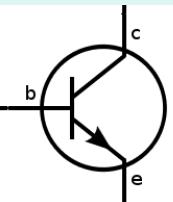

Shunt-shunt feedback

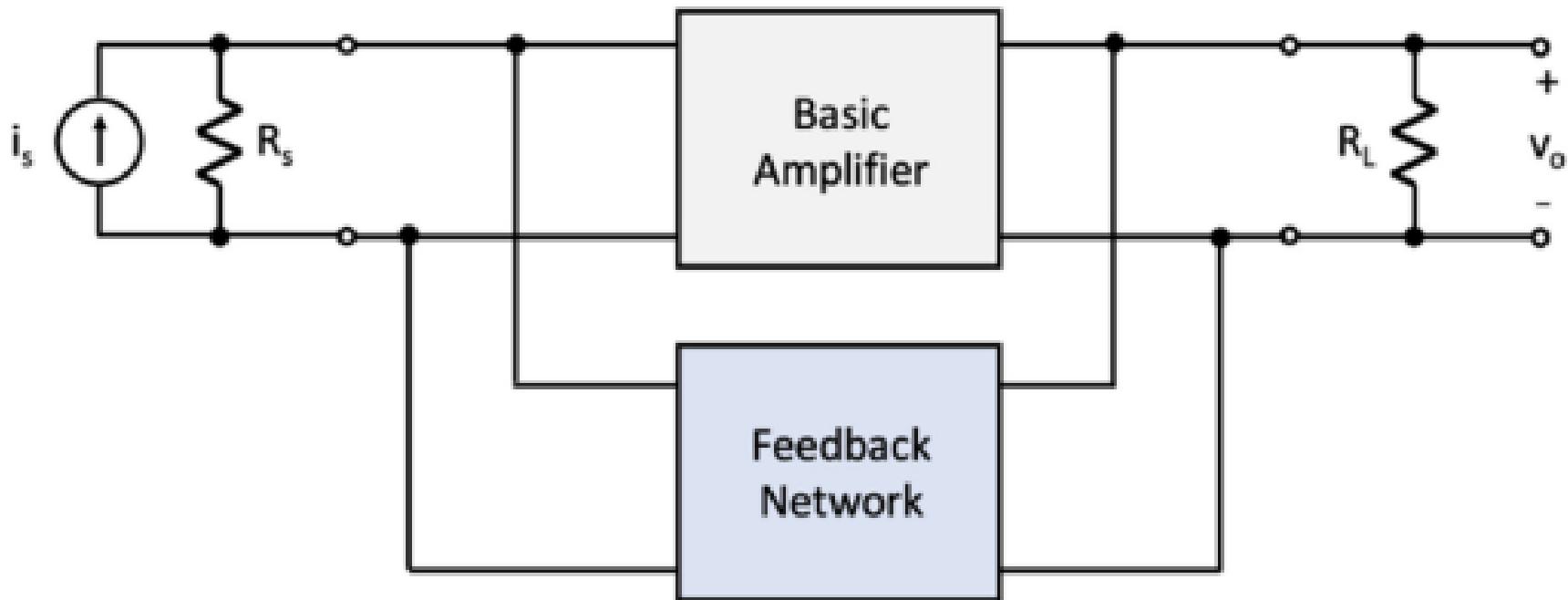
- Transimpedance amplifier (current-mixing/voltage-sampling)




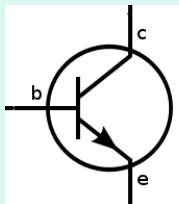

L21 Q01 Feedback amplifier

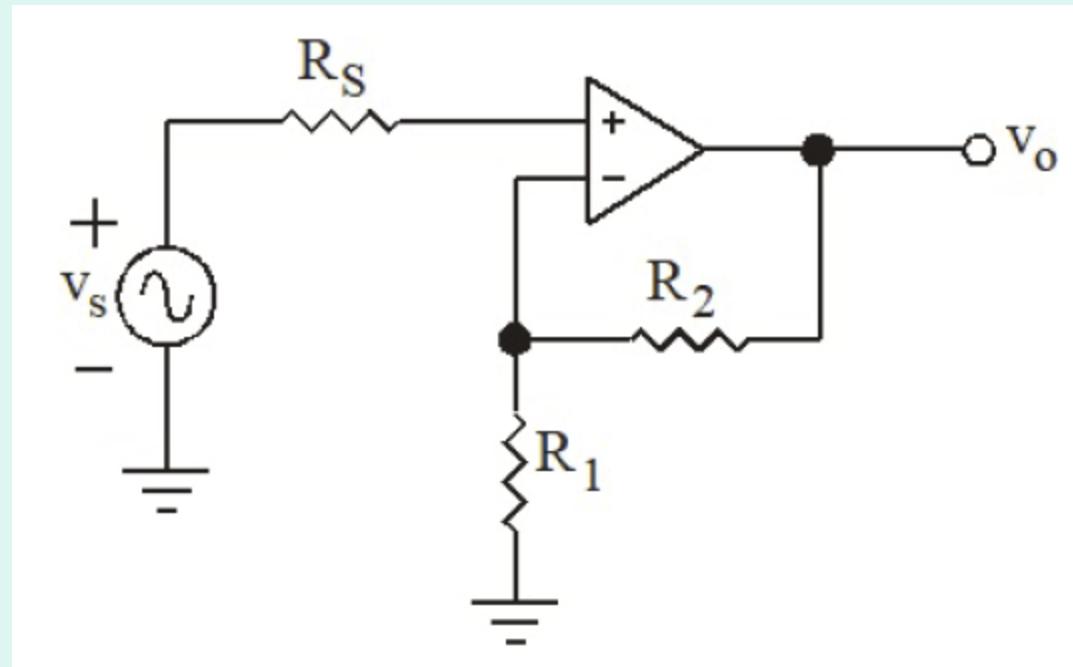
- What type of feedback the following circuit has?
A. series-series
B. series-shunt
C. shunt-series
D. shunt-shunt




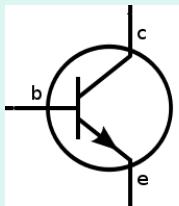

L21 Q02 inverting opamp

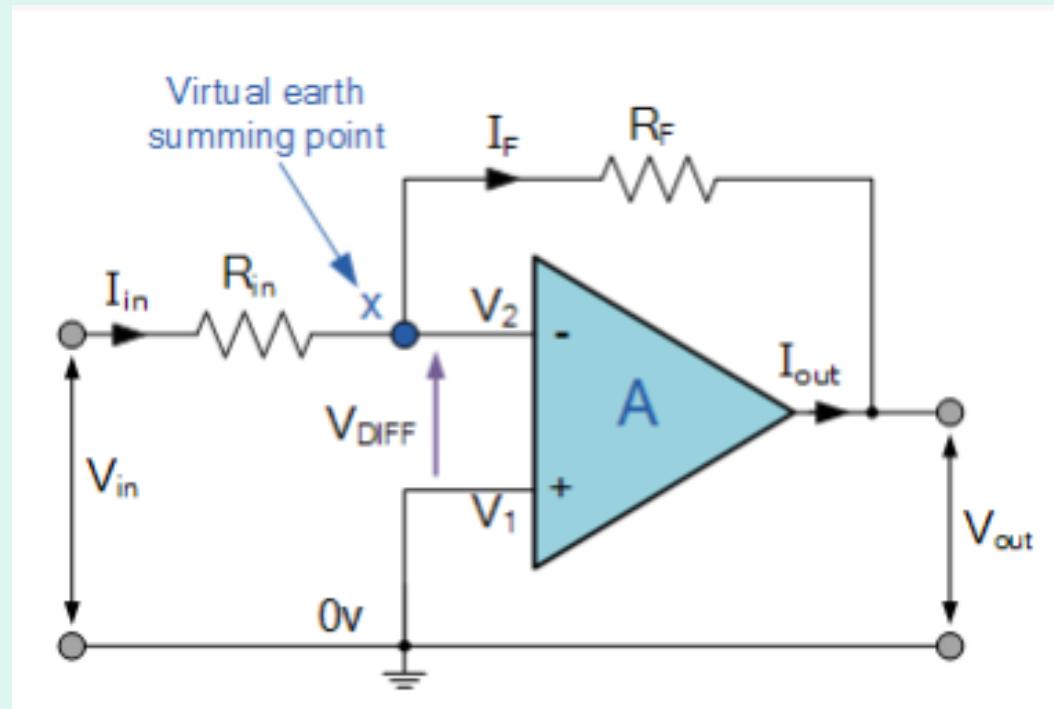
- What feedback topology is present in the following circuit?
A. series-series
B. series-shunt
C. shunt-series
D. shunt-shunt



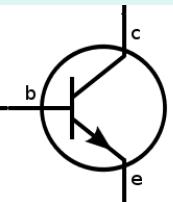

Circuit example

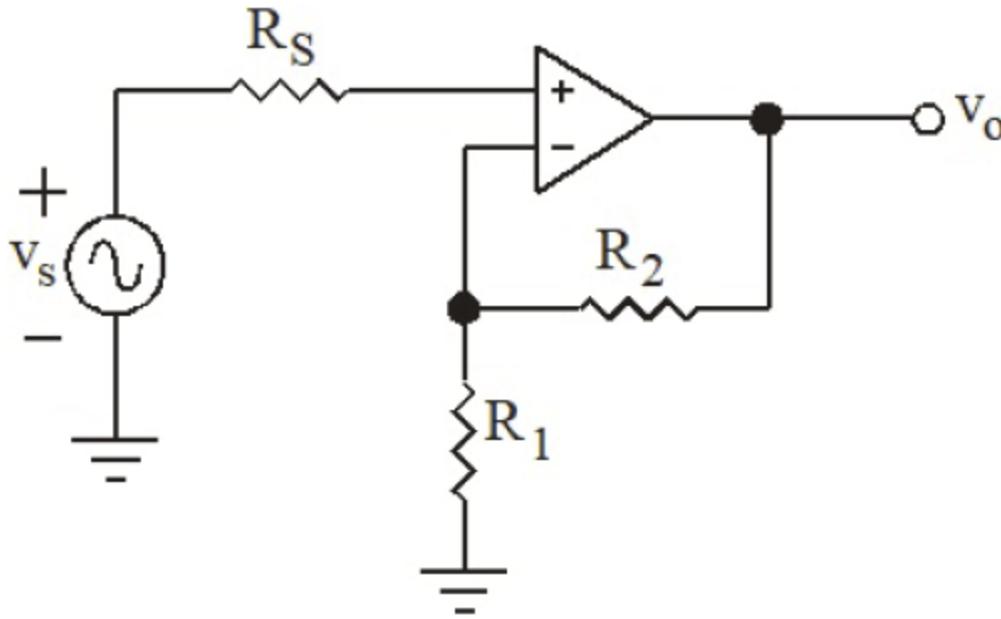- (a) For $A=\infty$, find an expression for A_f



$$v_+ = v_s, v_- = \frac{R_1}{R_1 + R_2} v_o$$

$$A_f = \frac{v_o}{v_s} = \frac{v_- \frac{R_1 + R_2}{R_1}}{v_+} = \frac{R_1 + R_2}{R_1} = \frac{1}{\beta}$$

$$\beta = \frac{R_1}{R_1 + R_2}$$


- (b) For $A=10^4$, find the value of R_2/R_1 for which A_f equals 100

$$100 = \frac{A}{1 + A\beta} \Rightarrow \beta = \frac{\frac{A}{100} - 1}{A} = \frac{1}{100} - \frac{1}{A}$$

$$\frac{R_1}{R_1 + R_2} = \frac{1}{100} - \frac{1}{10000} = \frac{99}{10000}$$
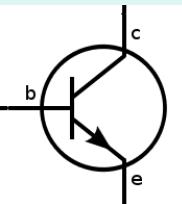
$$\frac{1}{1 + \frac{R_2}{R_1}} = \frac{99}{10000} \Rightarrow \frac{R_2}{R_1} = \frac{10000}{99} - 1 = 100.01$$






Circuit example (2)

- (c) Parameter variation: What happens to A_f if A decreases by 25%?

$$A_f = \frac{A}{1 + A\beta} = \frac{7500}{1 + \frac{7500}{1 + 100/01}} = 99.67$$

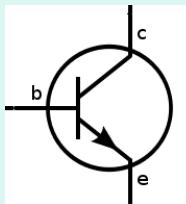- (d) The amount of feedback for (b)

$$1 + A\beta = 1 + \frac{10000}{101.01} = 100 \rightarrow 20 \log(1 + A\beta) = 40 \text{ dB}$$



Gain de-sensitivity


- In the previous exm: for $A=10000$ and $\beta=1/101.01$, a 25% change in A gave a 0.33% change in A_f
- In general:

$$A_f = \frac{A}{1+A\beta} \Rightarrow \frac{dA_f}{dA} = \frac{1}{1+A\beta} - \frac{A\beta}{(1+A\beta)^2} = \frac{1}{(1+A\beta)^2}$$

$$\frac{dA_f}{A_f} = \frac{1+A\beta}{A} \frac{dA}{(1+A\beta)^2} = \frac{1}{1+A\beta} \frac{dA}{A}$$

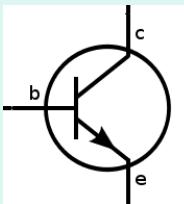The amount of feedback $(1+A\beta)$ is also called the **de-sensitivity factor**





Bandwidth extension

- We consider a single-pole LP amplifier (open-loop gain):

$$A(s) = A_M \frac{1}{1 + \frac{s}{\omega_H}}$$


The closed-loop gain: extended BW

$$A_f(s) = \frac{A(s)}{1 + A(s)\beta} = \frac{\frac{A_M}{1 + \frac{s}{\omega_H}}}{1 + \frac{A_M}{1 + \frac{s}{\omega_H}} \beta} = \frac{A_M}{1 + \frac{s}{\omega_H} + A_M \beta}$$

$$A_f(s) = \underbrace{\frac{A_M}{1 + A_M \beta}}_{A_{Mf}} \frac{1}{1 + \frac{s}{\omega_H (1 + A_M \beta)}}$$
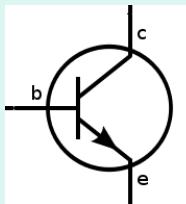
$$A_{Mf} = \frac{A_M}{1 + A_M \beta}, \omega_{Hf} = \omega_H (1 + A_M \beta)$$





Bandwidth extension (2)


- The case of a high-pass single-pole amplifier

$$A(s) = A_M \frac{s}{s + \omega_L}$$

The closed-loop gain: again, the BW is extended

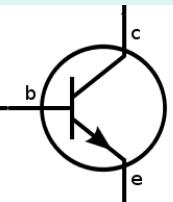
$$A_f(s) = \frac{A(s)}{1 + A(s)\beta} = \frac{A_M \frac{s}{s + \omega_L}}{1 + A_M \beta \frac{s}{s + \omega_L}} = \underbrace{\frac{A_M}{1 + A_M \beta}}_{A_{Mf}} \frac{s}{s + \underbrace{\frac{\omega_L}{1 + A_M \beta}}_{\omega_{Lf}}}$$





Bandwidth extension (3)

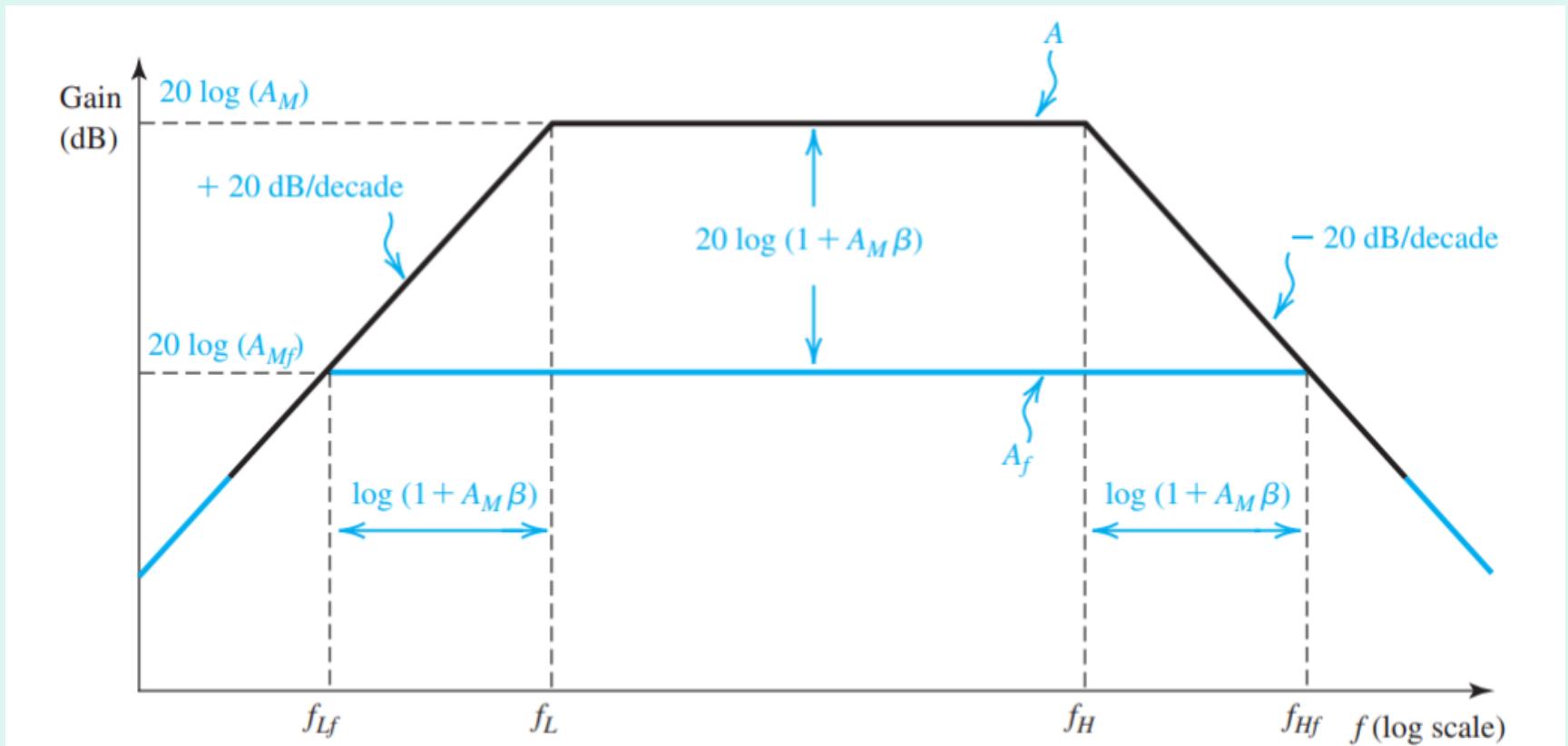- Negative feedback => A_M reduces, f_H increases, f_L reduces by the same $(1+A_M\beta)$ factor




$$f_{Lf} = \frac{f_L}{1 + A_M \beta}$$

$$A_{Mf} = \frac{A_M}{1 + A_M \beta}$$

$$f_{Hf} = f_H (1 + A_M \beta)$$

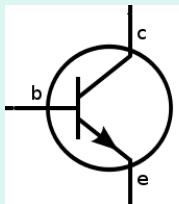
(Source: Sedra and Smith[2014]Microelectronic circuits)





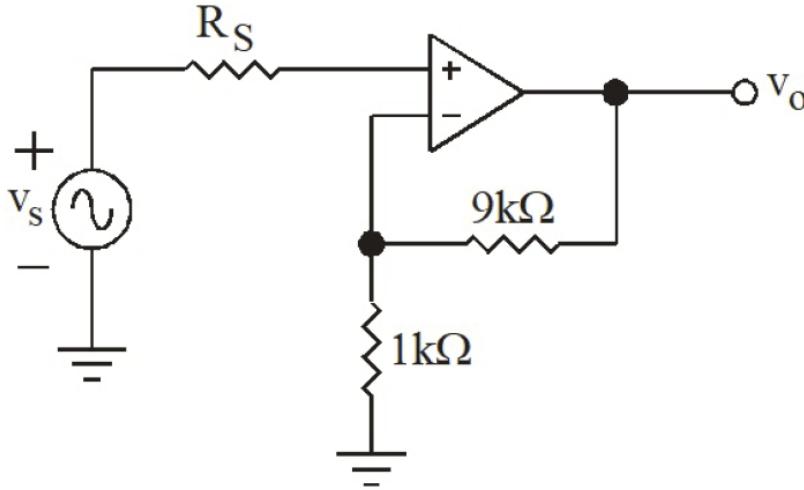Example

- Assume $A=10^6$, 10Hz bandwidth and a roll-off of -20dB/decade (single-pole LP)




$$A(s) = \frac{A_M}{1 + \frac{s}{\omega_H}} = \frac{10^6}{1 + \frac{s}{2\pi 10}}$$

$$A_{fM} = \frac{v_o}{v_s} = 1 + \frac{9k\Omega}{1k\Omega} = 10 \approx \frac{1}{\beta}$$

$$A_f(s) = \frac{A_M}{1 + A_M \beta} \frac{1}{1 + \frac{s}{\omega_H (1 + A_M \beta)}} = \frac{10^6}{1 + 0.1 \cdot 10^6} \frac{1}{1 + \frac{s}{2\pi 10 (1 + 0.1 \cdot 10^6)}}$$
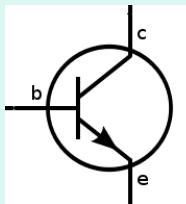
$$A_{Mf} = \frac{10^6}{1 + 0.1 \cdot 10^6} \approx 9.9999, f_{Hf} = 10 (1 + 0.1 \cdot 10^6) = 1.00001 \text{ MHz}$$






Nonlinear distortion reduction

- An open-loop amplifier with a piecewise linear transfer function, and feedback gain $\beta=0.05$

$$A = \begin{cases} 10^4 & \text{if } 0 \leq |v_o| < 8V \\ 10^3 & \text{if } 8V \leq |v_o| < 11V \\ 10^2 & \text{if } 11V \leq |v_o| < 14V \\ 0 & \text{if } 14V \leq |v_o| \end{cases} \Rightarrow A_f = \begin{cases} \frac{10^4}{1 + 0.05 \cdot 10^4} = 19.96 & \text{if } 0 \leq |v_o| < 8V \\ \frac{10^3}{1 + 0.05 \cdot 10^3} = 19.61 & \text{if } 8V \leq |v_o| < 11V \\ \frac{10^2}{1 + 0.05 \cdot 10^2} = 16.67 & \text{if } 11V \leq |v_o| < 14V \\ 0 & \text{if } 14V \leq |v_o| \end{cases}$$


$$A_f = \frac{A}{1 + A\beta} = \frac{1}{\beta + \frac{1}{A}} = \frac{1}{\beta} \frac{1}{1 + \frac{1}{A\beta}}$$

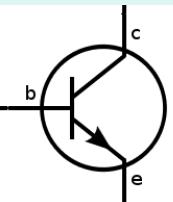The differences in the slopes between regions (1)-(3) have been much reduced through the feedback action




Distortion reduction (2)

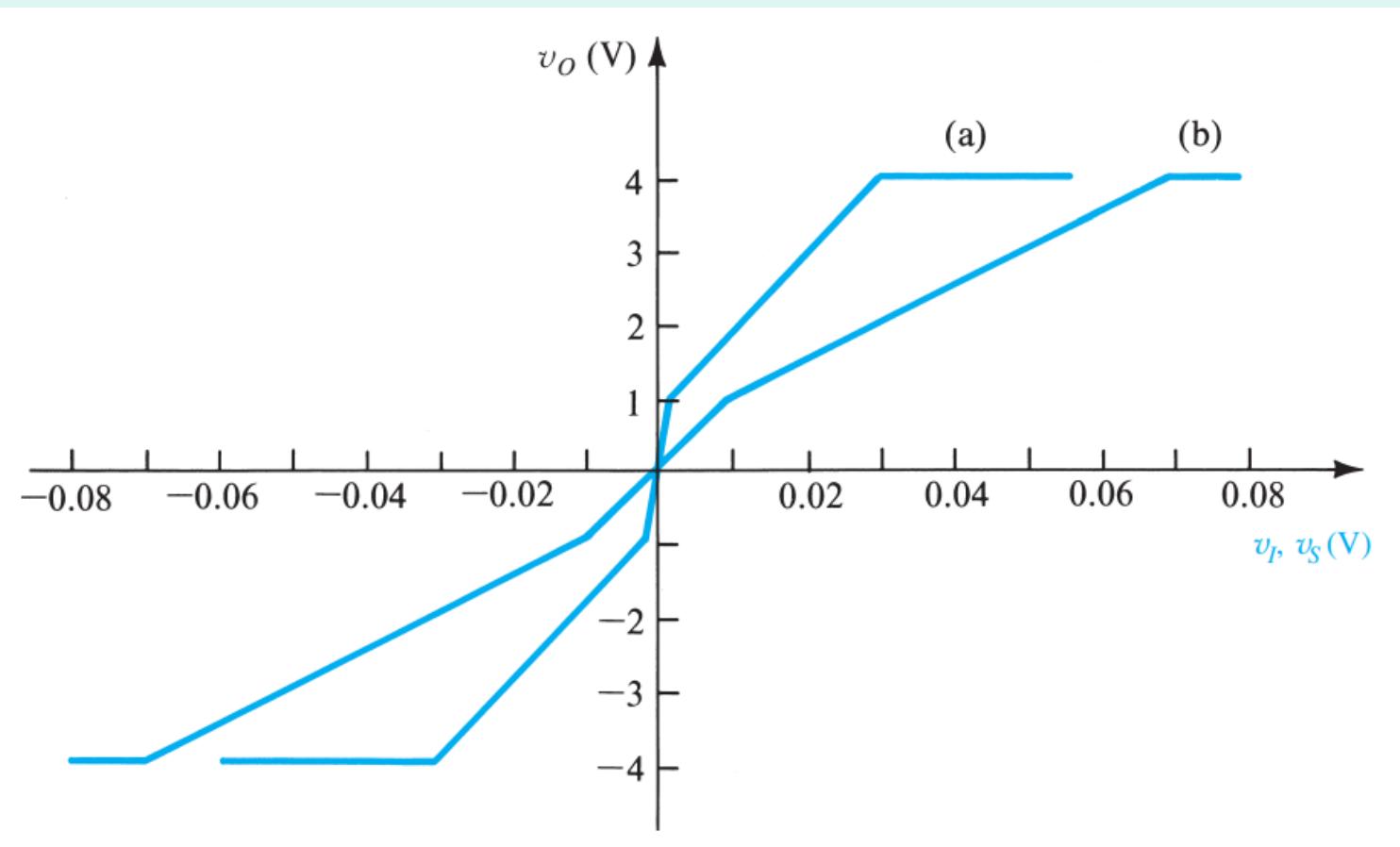- The amplifier transfer characteristics can be linearized (made less nonlinear) through negative feedback



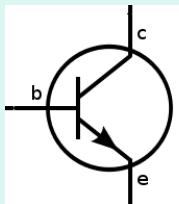
(a) without feedback; (b) with negative feedback ($\beta=0.01$)






Feedback effect on impedances

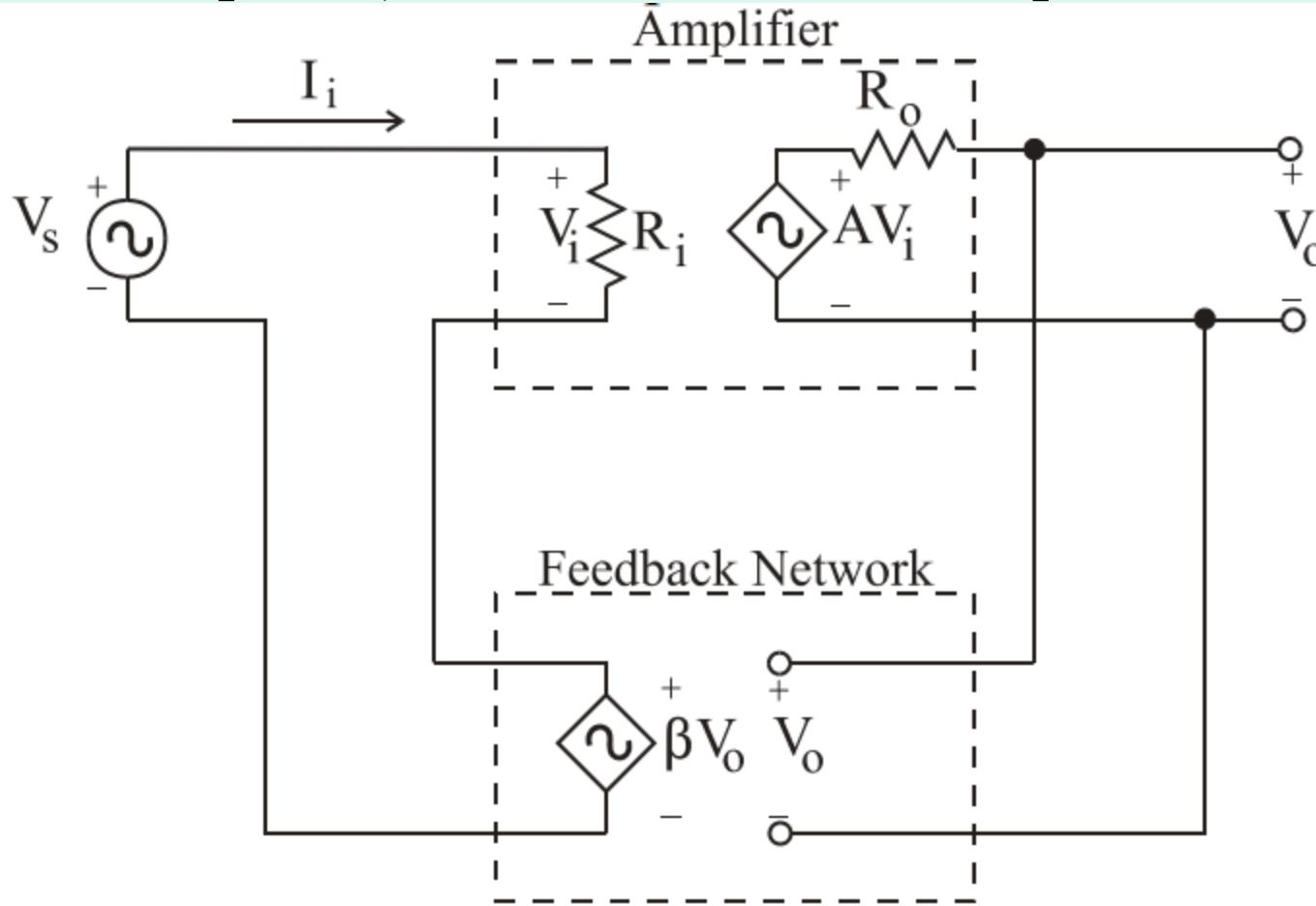- Consider the series-shunt feedback amplifier (voltage amplifier), with ideal feedback diport




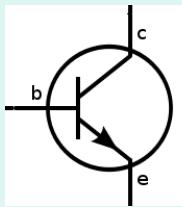
$$A_{vf} = \frac{V_o}{V_s} = \frac{A}{1 + A\beta}$$






Voltage amplifier

- equivalent diport model

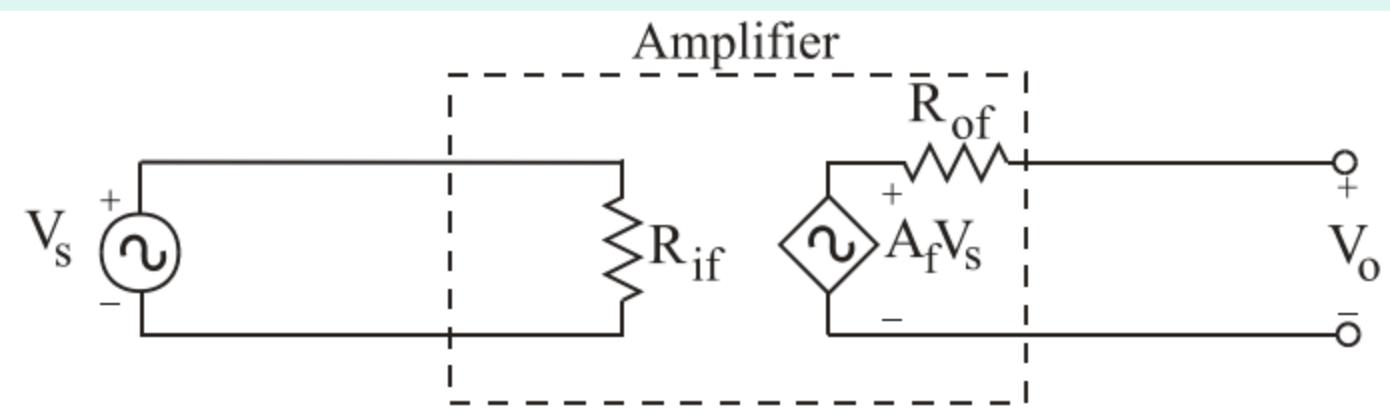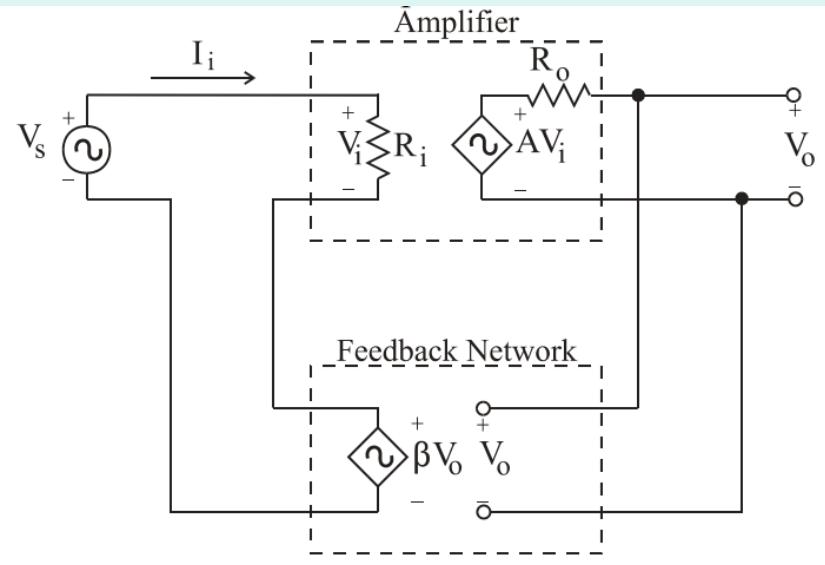


$$R_{if}, R_{of} = ?$$



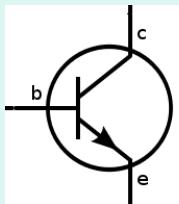


Finding R_{if}

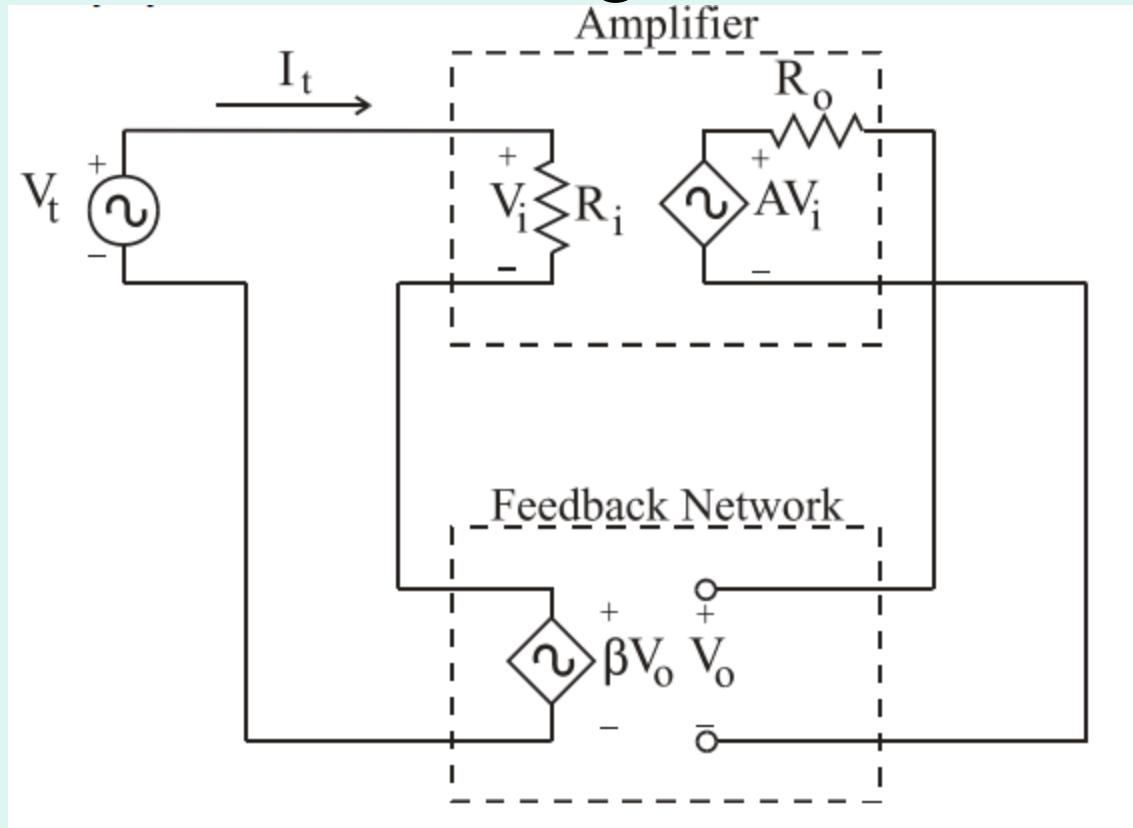- Replace source with a test voltage source



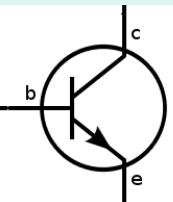
$$R_{if} = \frac{V_t}{I_t} = \frac{V_t}{\frac{V_i}{R_i}} = R_i \frac{V_i + \beta V_o}{V_i} = R_i (1 + A\beta)$$





Finding R_{of}

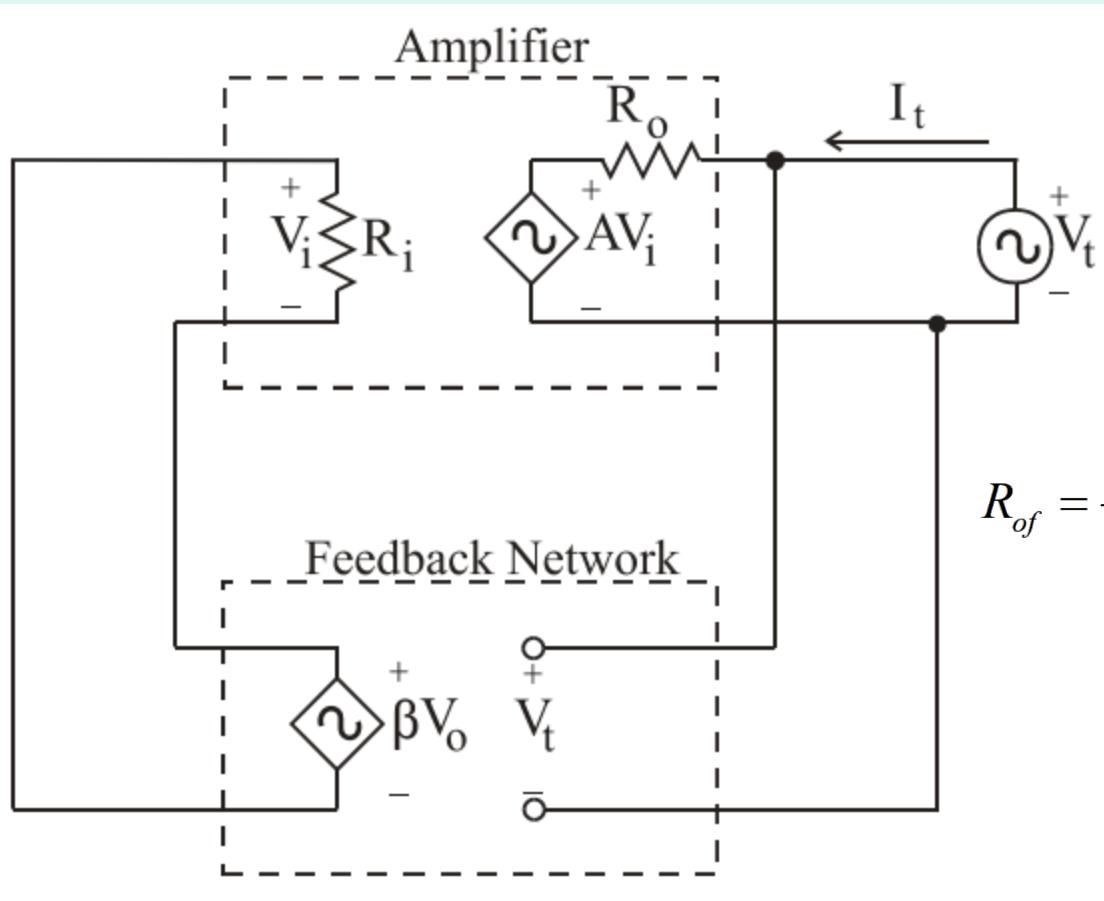- Apply a test voltage source at the output



$$R_{of} = \frac{V_t}{I_t} = \frac{V_t}{\frac{V_t - AV_i}{R_o}} = R_o \frac{V_t}{V_t + A\beta V_t} = \frac{R_o}{1 + A\beta}$$



Concl: negative feedback brings the diport closer to an ideal diport (voltage amplifier)

