
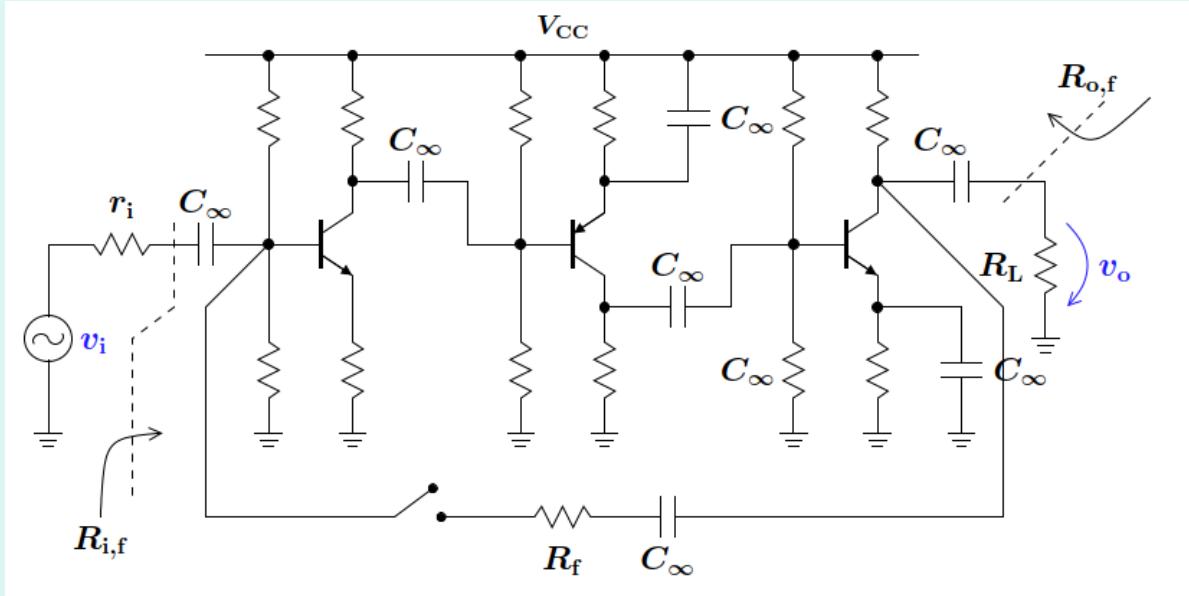


ELEC 301 - Real feedback networks

L22 - Oct 30

Instructor: Edmond Cretu

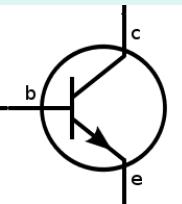




Last time

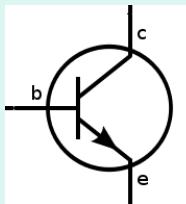- From information flow to energy flow: 4 circuit feedback topologies
- The effect of negative feedback on amplifier stages: extends BW, de-sensitivation to amplifier parameter variations, linearization of the transfer function (reduced distortions)






L22 Q01 current amplifier

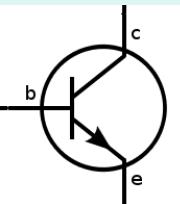- What type of feedback topology is suitable for a current amplifier? ($A_i = I_{out}/I_{in}$)
 - series-series
 - series-shunt
 - shunt-series
 - shunt-shunt






L22 Q02 positive feedback

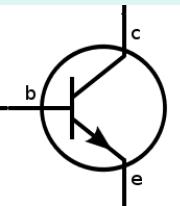- Assume a voltage amplifier stage with a single pole frequency response (ω_H) has a **slightly positive** feedback network. Which statement is right?
 - A. The gain and the BW do not change
 - B. Both the closed-loop gain and the BW increase
 - C. The closed-loop gain decreases and the BW increases
 - D. The closed-loop gain increases and the BW decreases






Information flow to energy flow


- signals mapped into voltages/currents => 4 categories of feedback circuit architectures

Input signal x_s	Output signal x_o	Feedback type	Remarks
voltage v_s	voltage v_o	series-shunt	Voltage amplifier A_{vf} (Z_{in} high, Z_{out} low)
current i_s	voltage v_o	shunt-shunt	Transimpedance amplifier Z_f (Z_{in} low, Z_{out} low)
voltage v_s	current i_o	series-series	Transadmittance amplifier Y_f (Z_{in} high, Z_{out} high)
current i_s	current i_o	shunt-series	Current amplifier A_{if} (Z_{in} low, Z_{out} high)

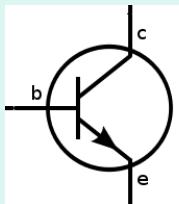


Feedback effect on impedances

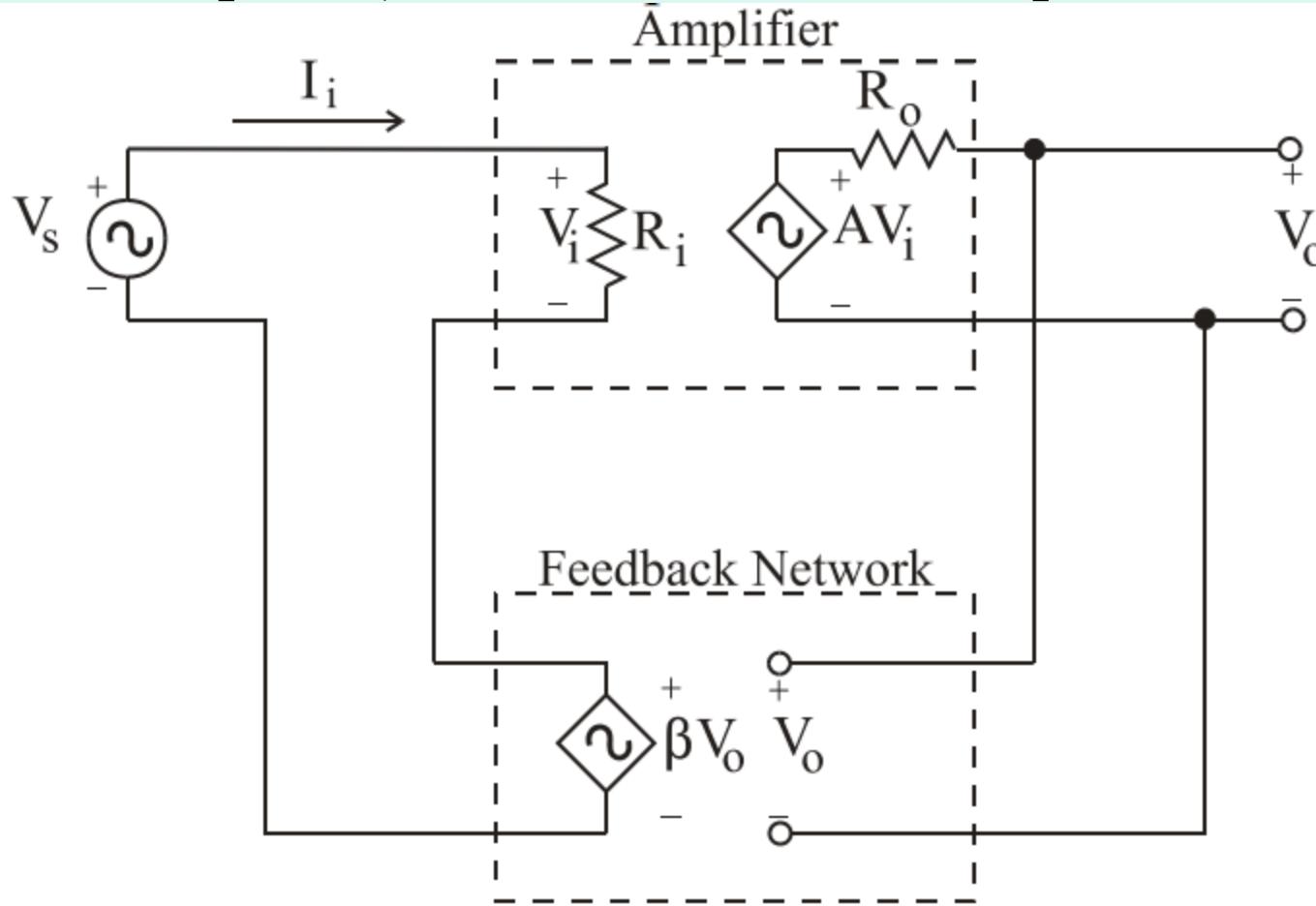- Consider the series-shunt feedback amplifier (voltage amplifier), with ideal feedback diport




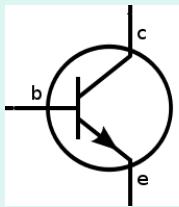
$$A_{vf} = \frac{V_o}{V_s} = \frac{A}{1 + A\beta}$$






Voltage amplifier

- equivalent diport model

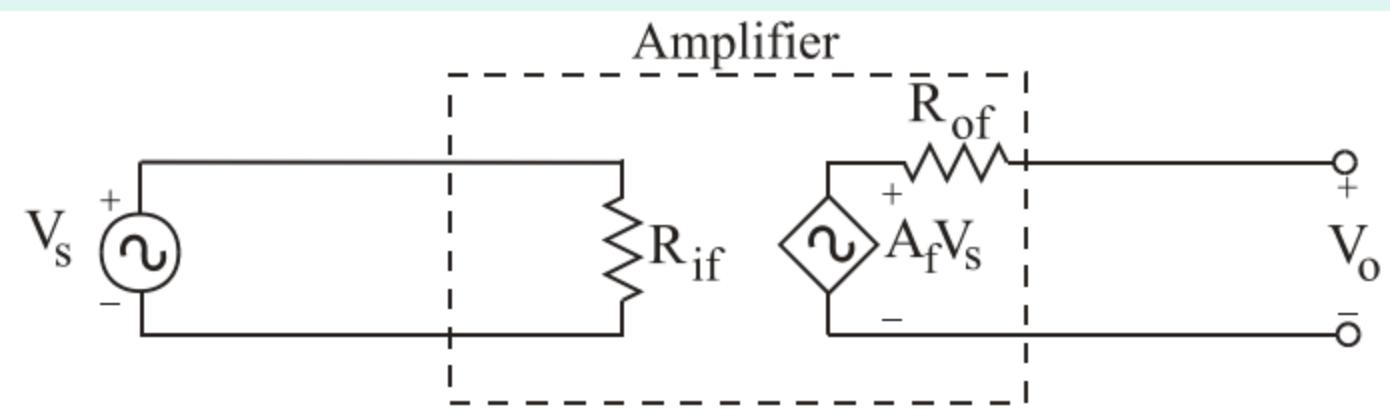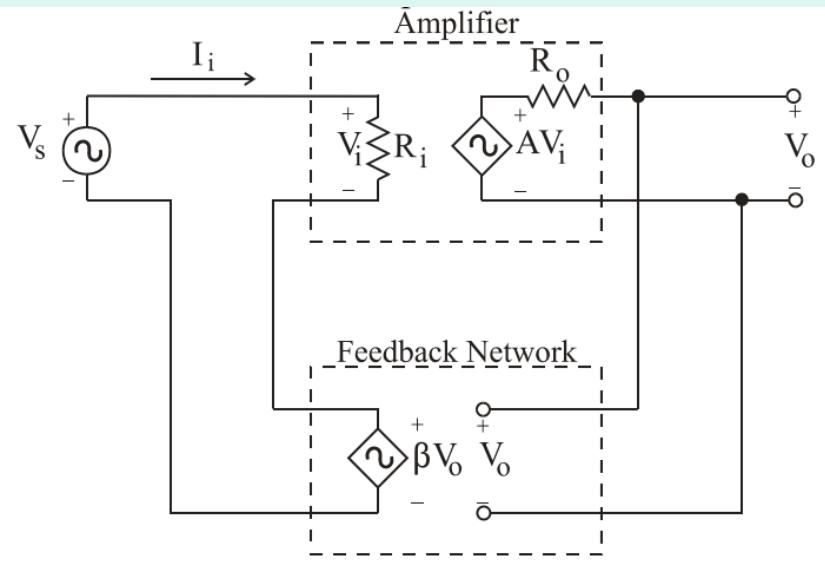


$$R_{if}, R_{of} = ?$$



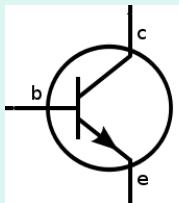


Finding R_{if}

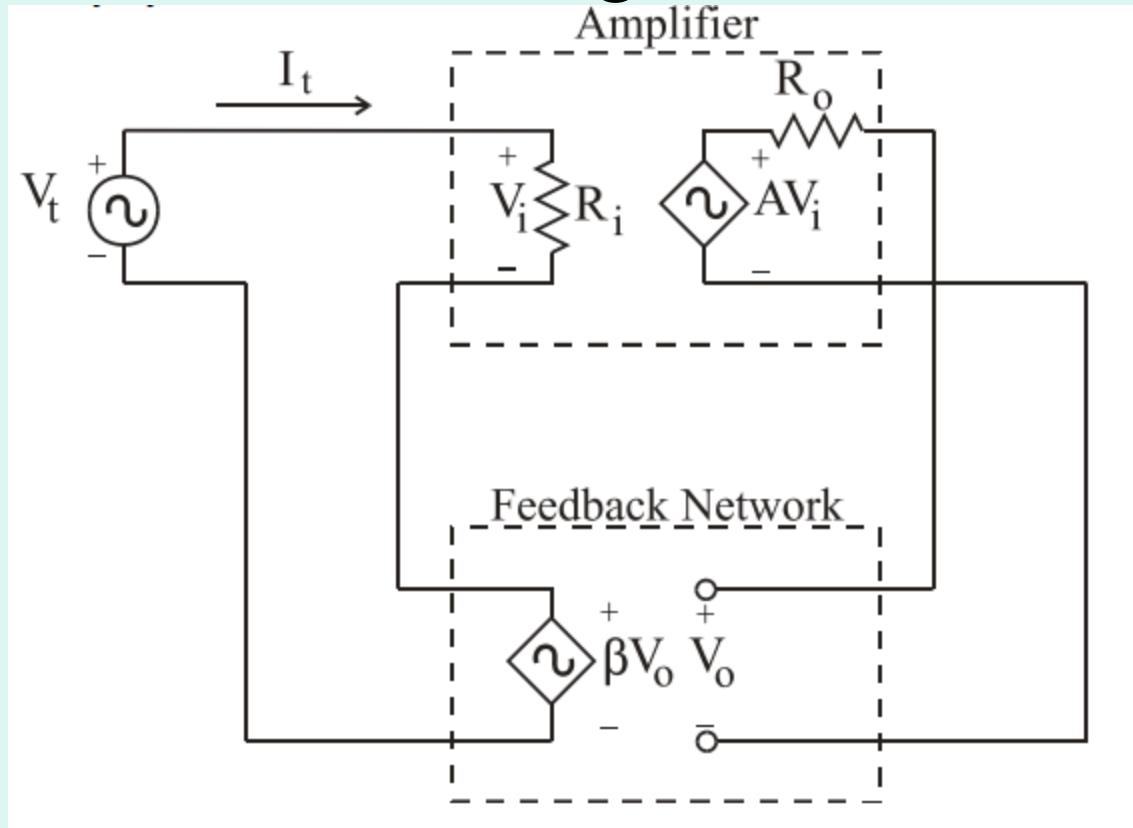- Replace source with a test voltage source



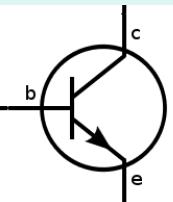
$$R_{if} = \frac{V_t}{I_t} = \frac{V_t}{\frac{V_i}{R_i}} = R_i \frac{V_i + \beta V_o}{V_i} = R_i (1 + A\beta)$$





Finding R_{of}

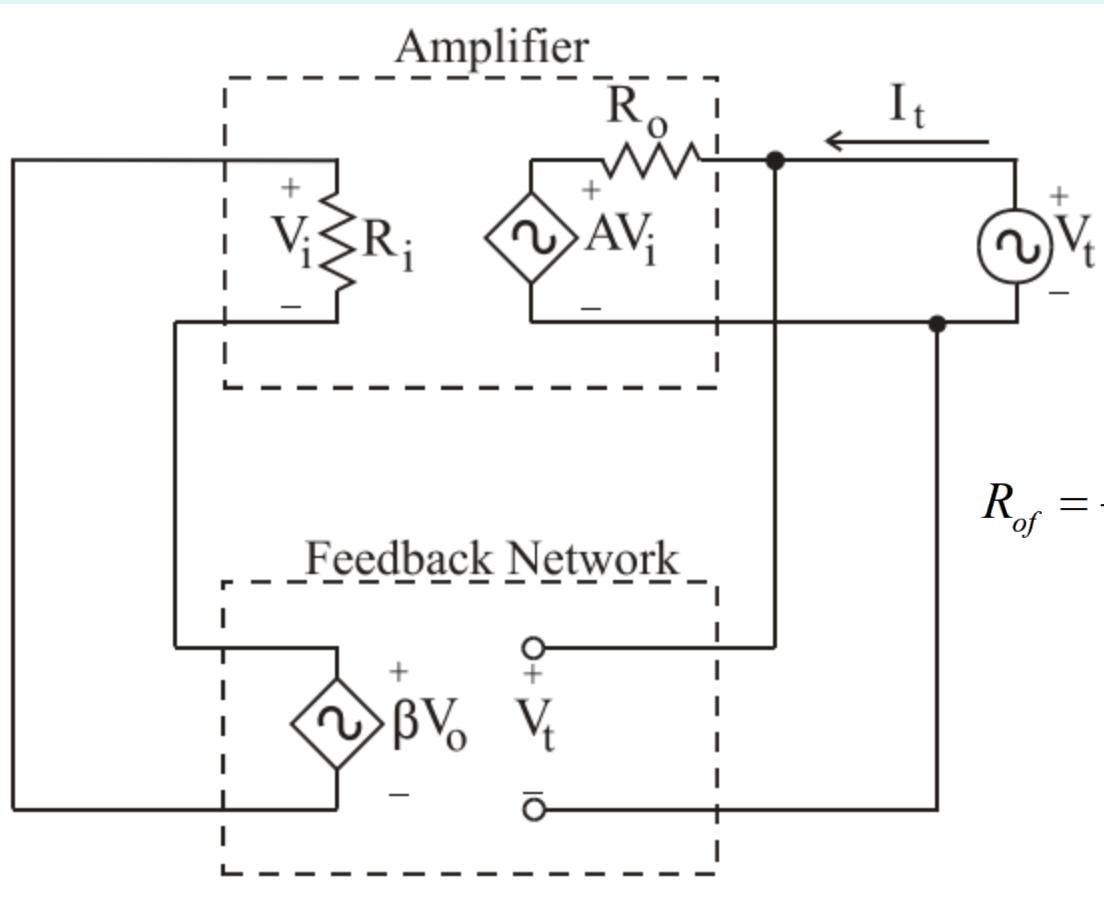
- Apply a test voltage source at the output



$$R_{of} = \frac{V_t}{I_t} = \frac{V_t}{\frac{V_t - AV_i}{R_o}} = R_o \frac{V_t}{V_t + A\beta V_t} = \frac{R_o}{1 + A\beta}$$




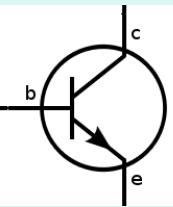
Concl: negative feedback brings the diport closer to an ideal diport (voltage amplifier)



Current amplifier case



- Shunt-series feedback topology

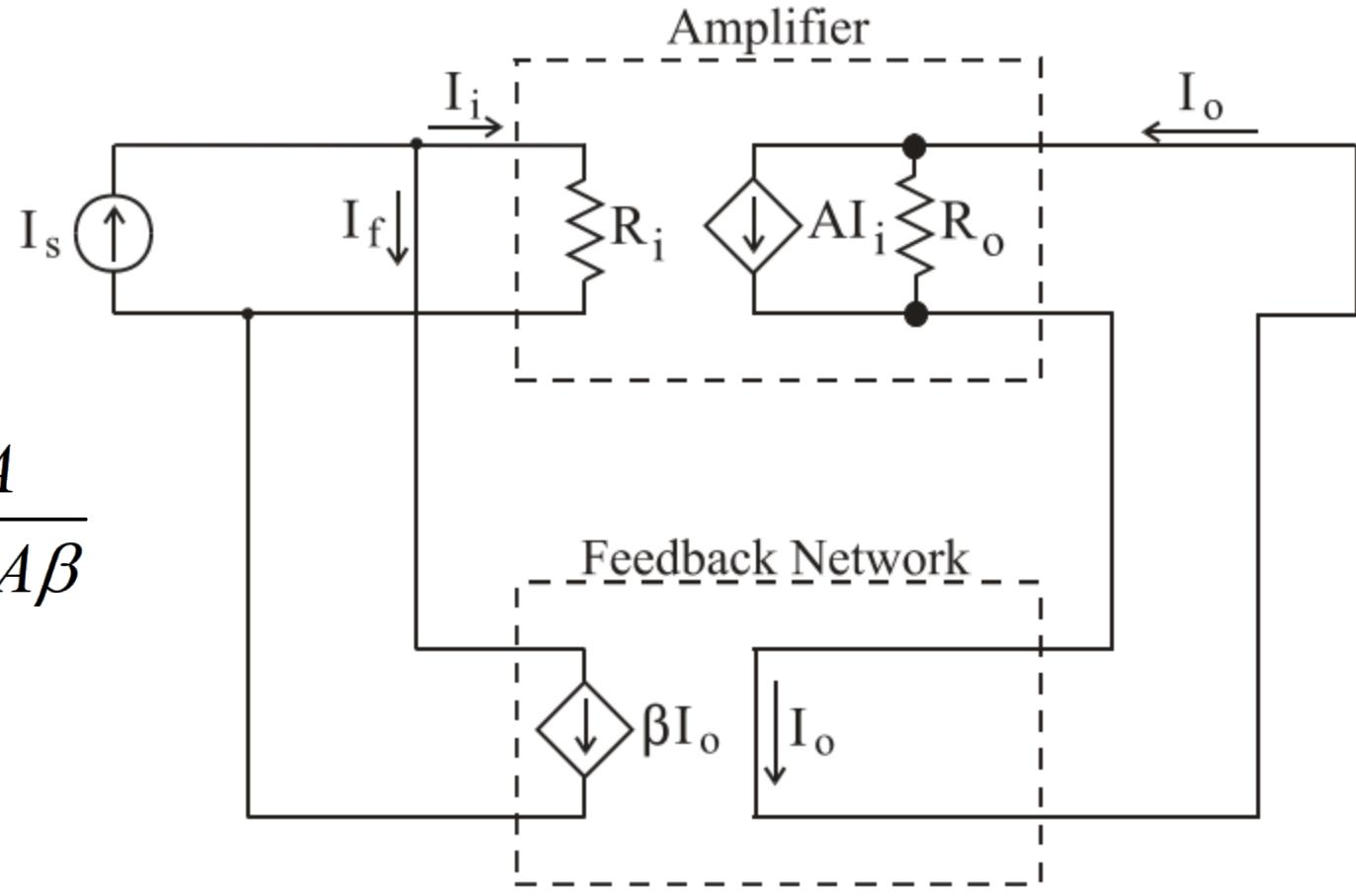


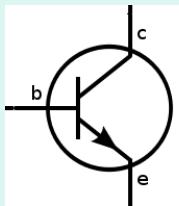

Current amplifier diport model


- Equivalent circuit model

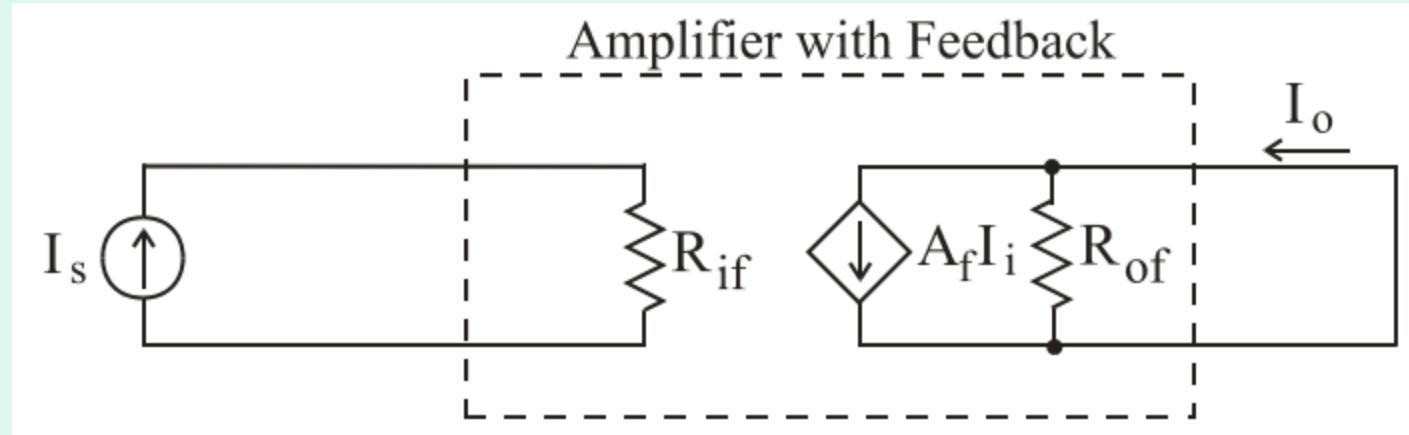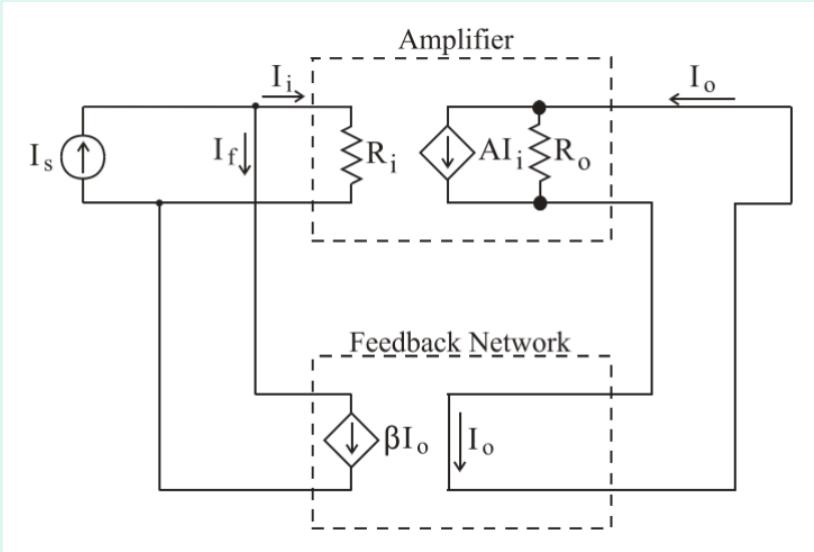

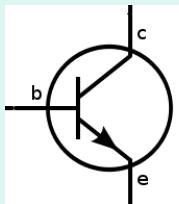


Current amplifier - input impedance

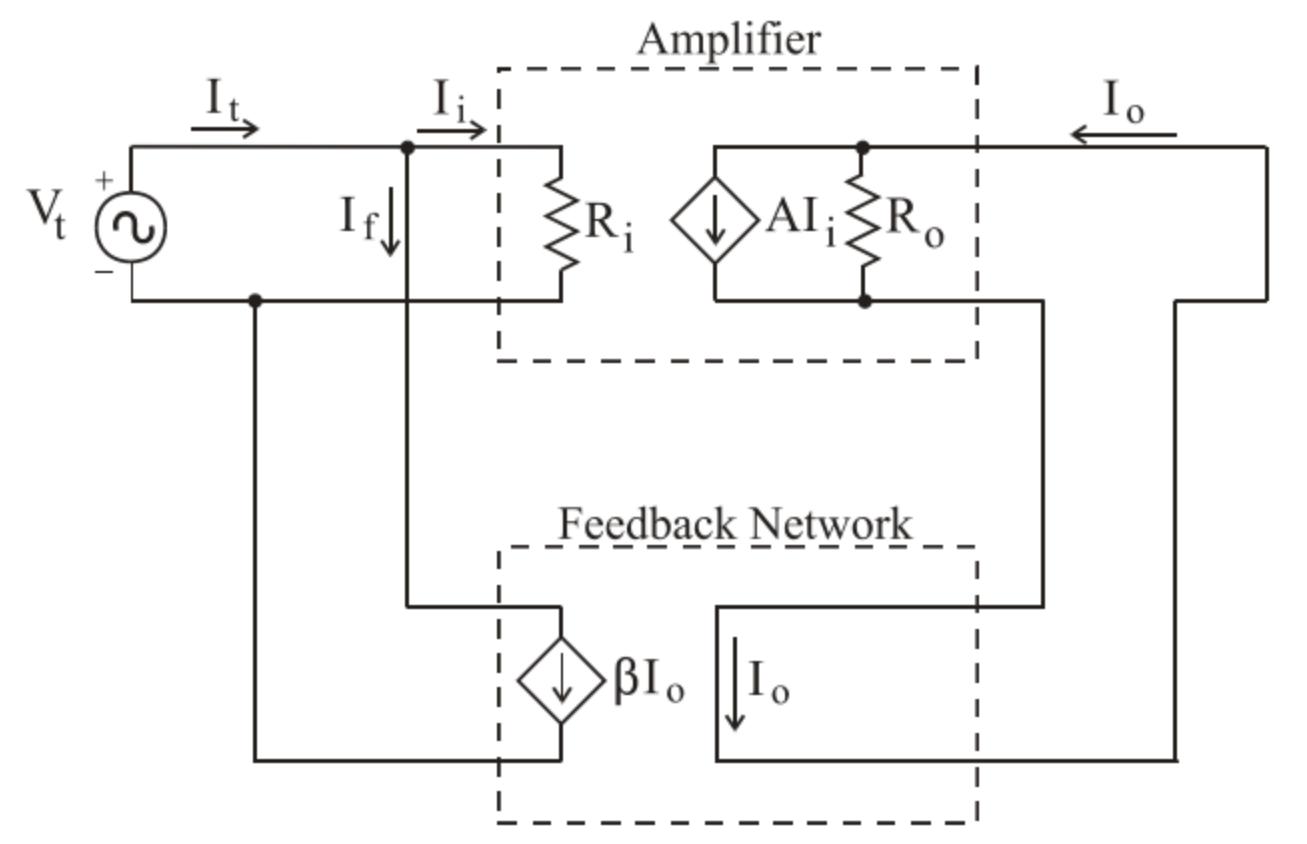- Replace the input current source with a test voltage source V_t



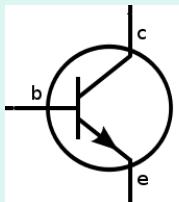
$$R_{if} = \frac{V_t}{I_t} = \frac{V_t}{\frac{V_t}{R_i} + \beta I_o} = \frac{V_t}{\frac{V_t}{R_i} + A\beta I_i} = \frac{R_i}{1 + A\beta}$$






Current amplifier - output impedance

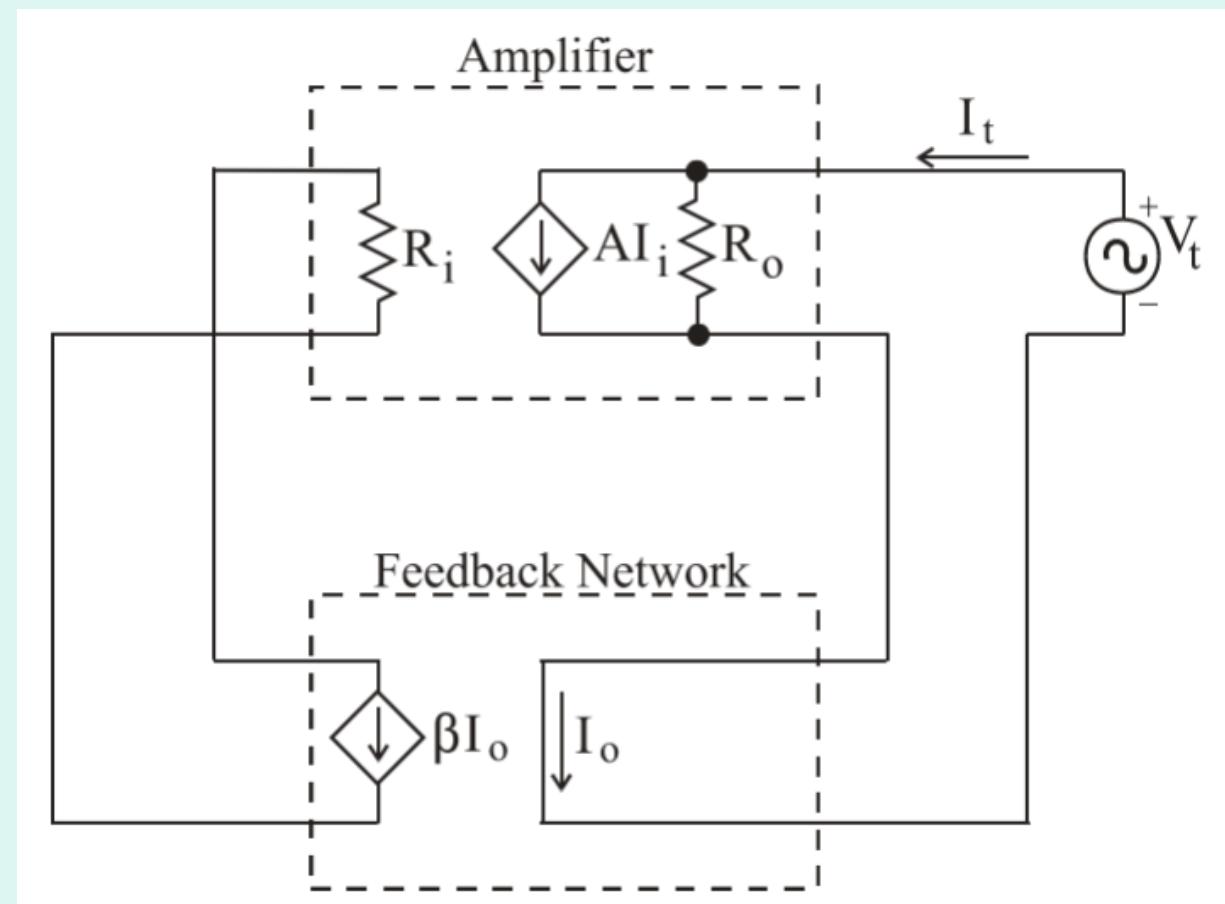- Cancel input independent current source, apply test voltage source at output


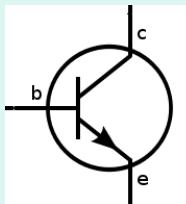
$$R_{of} = \frac{V_t}{I_t} = \frac{(I_t - AI_i)R_o}{I_t} = R_o \frac{I_t - A(-\beta I_t)}{I_t} = R_o (1 + A\beta)$$






Current amplifier - conclusions

- Ideal current amplifier - zero R_{in} , infinite R_{out}
- The shunt-series feedback drives a current amplifier closer to the ideal corresponding diport
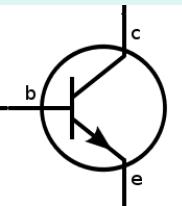
$$\begin{cases} R_{if} = \frac{R_i}{1 + A\beta} \\ R_{of} = R_o (1 + A\beta) \end{cases}$$





Remaining amplifier types


- Transimpedance amplifier - shunt-shunt feedback topology:

$$\text{Transimpedance } (i \rightarrow u): \begin{cases} A_{zf} = \frac{V_o}{I_s} = \frac{A}{1 + A\beta} \\ R_{if} = \frac{R_i}{1 + A\beta} \\ R_{of} = \frac{R_o}{1 + A\beta} \end{cases}$$

Transadmittance amplifier - series-series feedback topology:
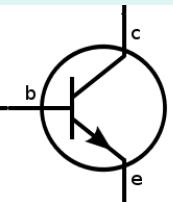
$$\text{Transadmittance } (u \rightarrow i): \begin{cases} A_{yf} = \frac{I_o}{V_s} = \frac{A}{1 + A\beta} \\ R_{if} = R_i (1 + A\beta) \\ R_{of} = R_o (1 + A\beta) \end{cases}$$






Four feedback topologies

- Summary of closed-loop parameters

Topology	Closed-Loop Gain A_f	Input Resistance R_{if}	Output Resistance R_{of}
Voltage-Sampling Series-Mixing	$A / (1 + A\beta)$	$R_i(1 + A\beta)$	$R_o / (1 + A\beta)$
Current-Sampling Series-Mixing	$A / (1 + A\beta)$	$R_i(1 + A\beta)$	$R_o(1 + A\beta)$
Voltage-Sampling Shunt-Mixing	$A / (1 + A\beta)$	$R_i / (1 + A\beta)$	$R_o / (1 + A\beta)$
Current-Sampling Shunt-Mixing	$A / (1 + A\beta)$	$R_i / (1 + A\beta)$	$R_o(1 + A\beta)$




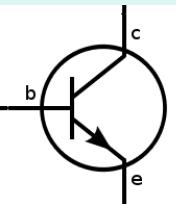

Non-ideal feedback networks

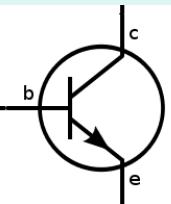
- So far we used an implicit assumption: the feedback network is ideal: it does not load the amplifier (it does not change the open-loop gain)+ there is no forward feed through
- Reality: a feedback network will affect A , R_i and R_o






Exm: voltage amplifier with feedback


- Series-shunt feedback topology

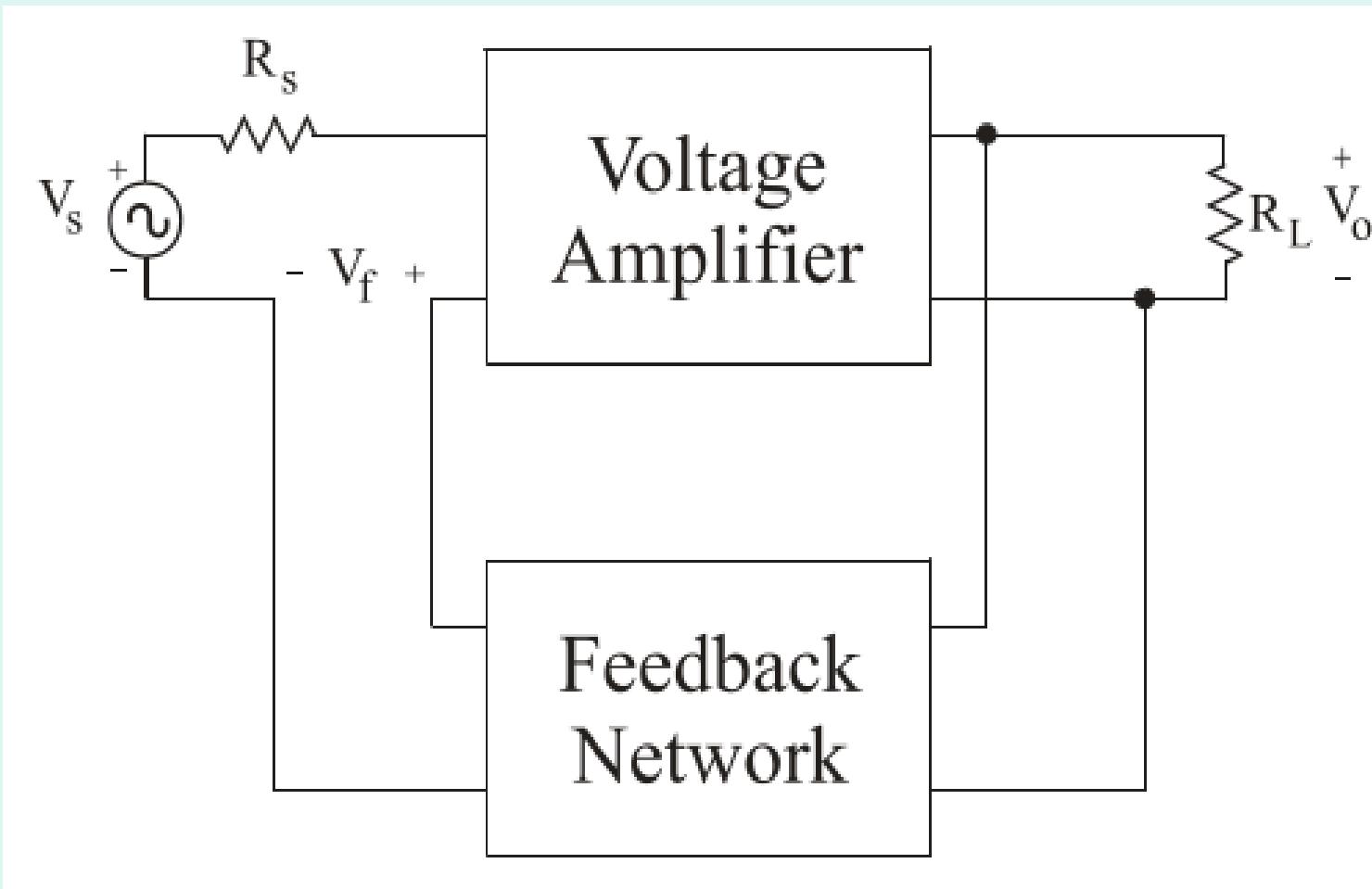

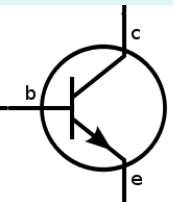


Series-shunt feedback network

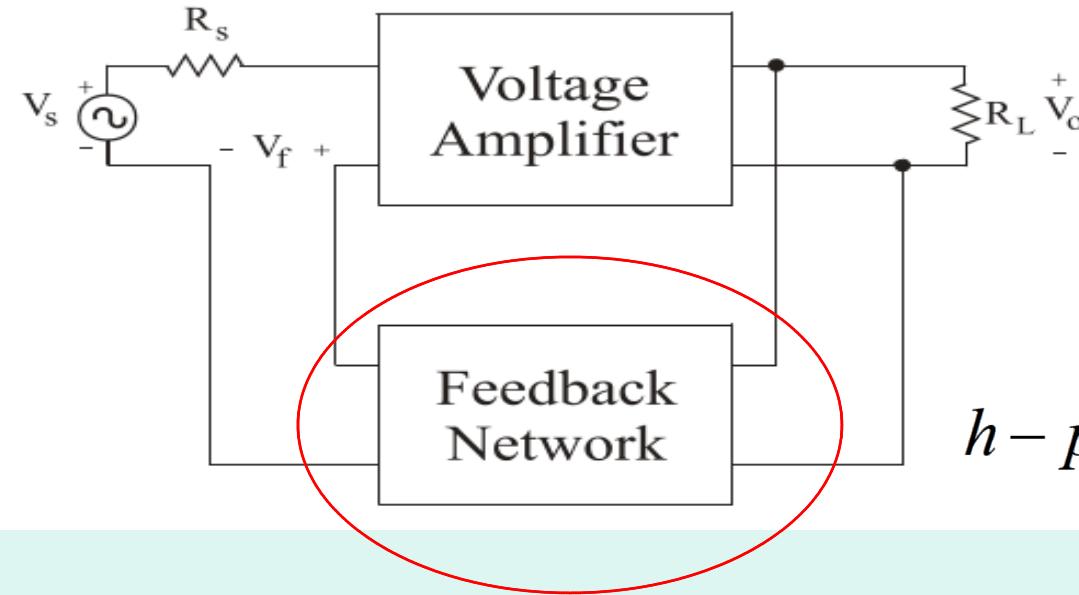
- General diport representation: the **h-parameter network**



$$h - \text{parameters} : \begin{cases} V_1 = h_{11}I_1 + h_{12}V_2 \\ I_2 = h_{21}I_1 + h_{22}V_2 \end{cases}$$

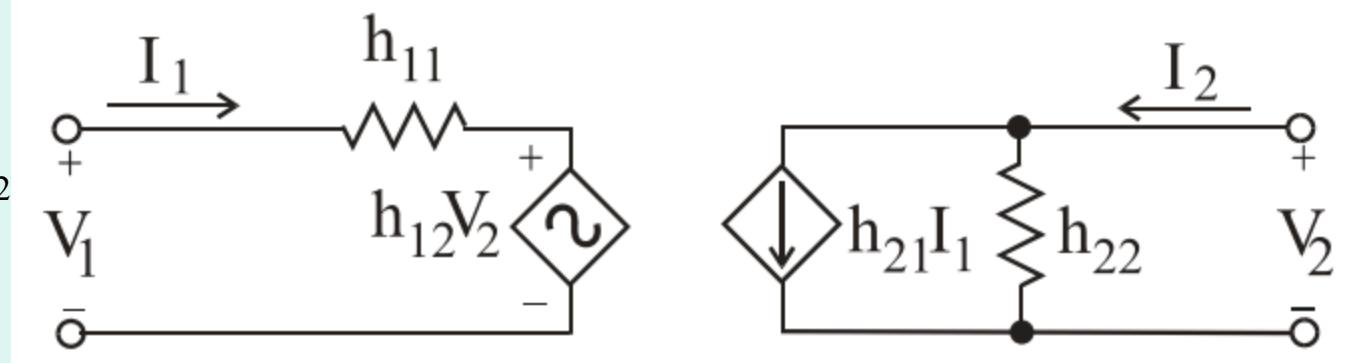
Independent var: I_1, V_2
Dependent var: V_1, I_2



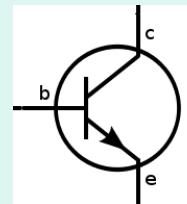


Measuring the h-parameters

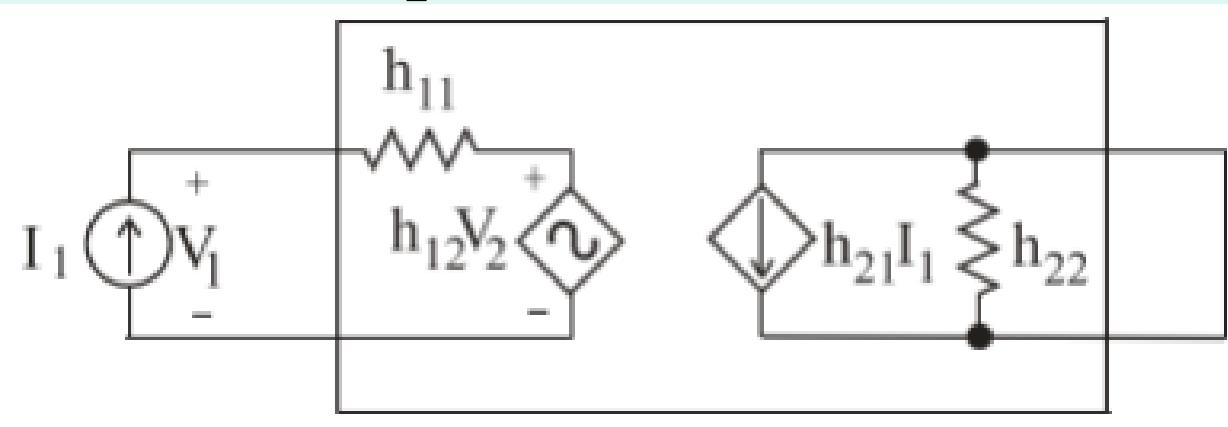- Equations result directly from the linear diport description




$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

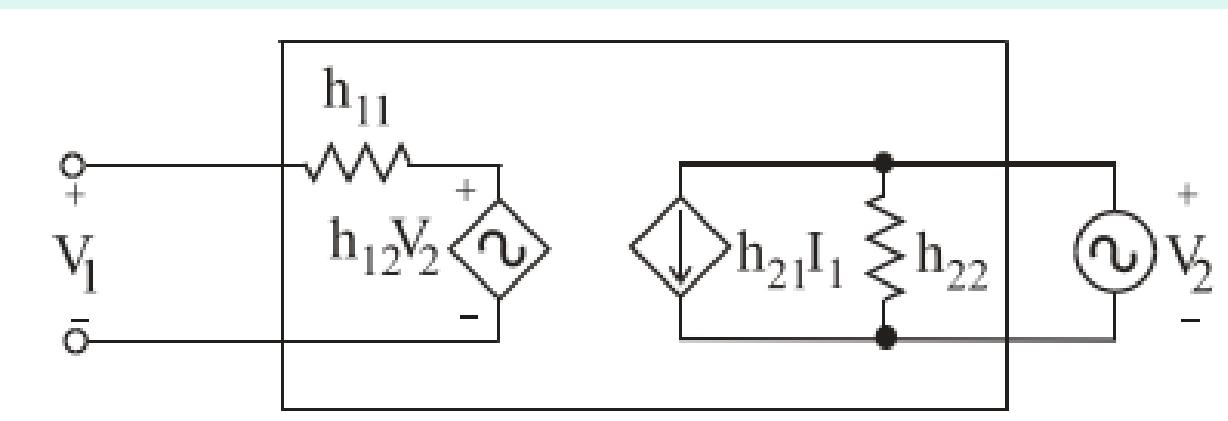


$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$



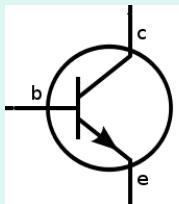


Measuring h-parameters (2)

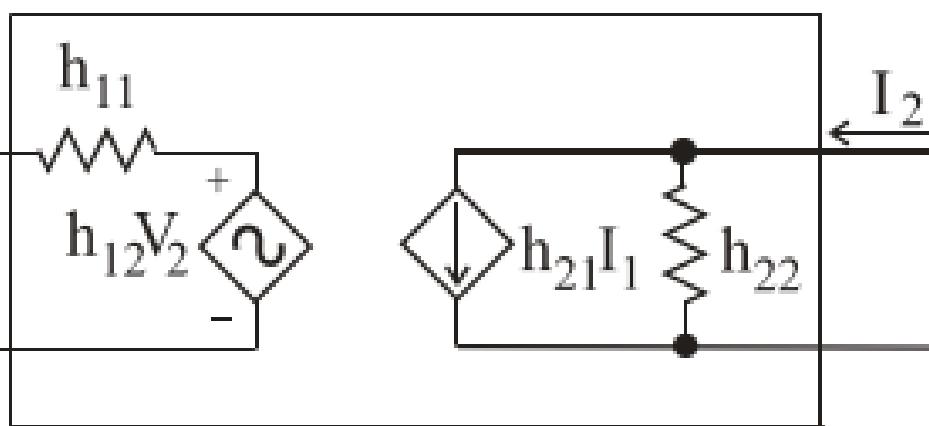- Linear diport \rightarrow superposition of effects
- $h_{21} = \text{forward transmission}$




$$\begin{cases} V_1 = h_{11}I_1 + h_{12}V_2 \\ I_2 = h_{21}I_1 + h_{22}V_2 \end{cases}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

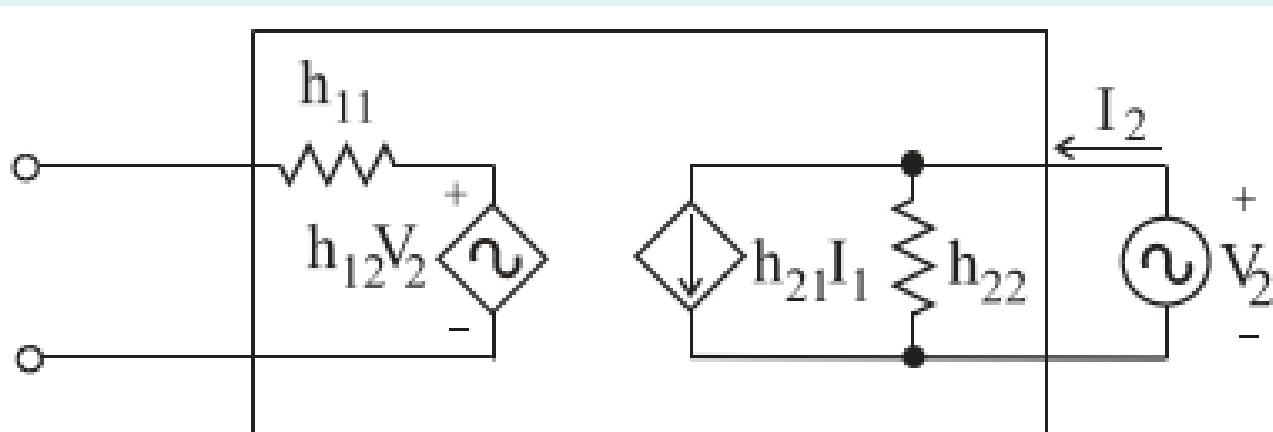



$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

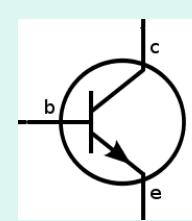

Voltage amplifier with a real β -network


- The series-shunt feedback case

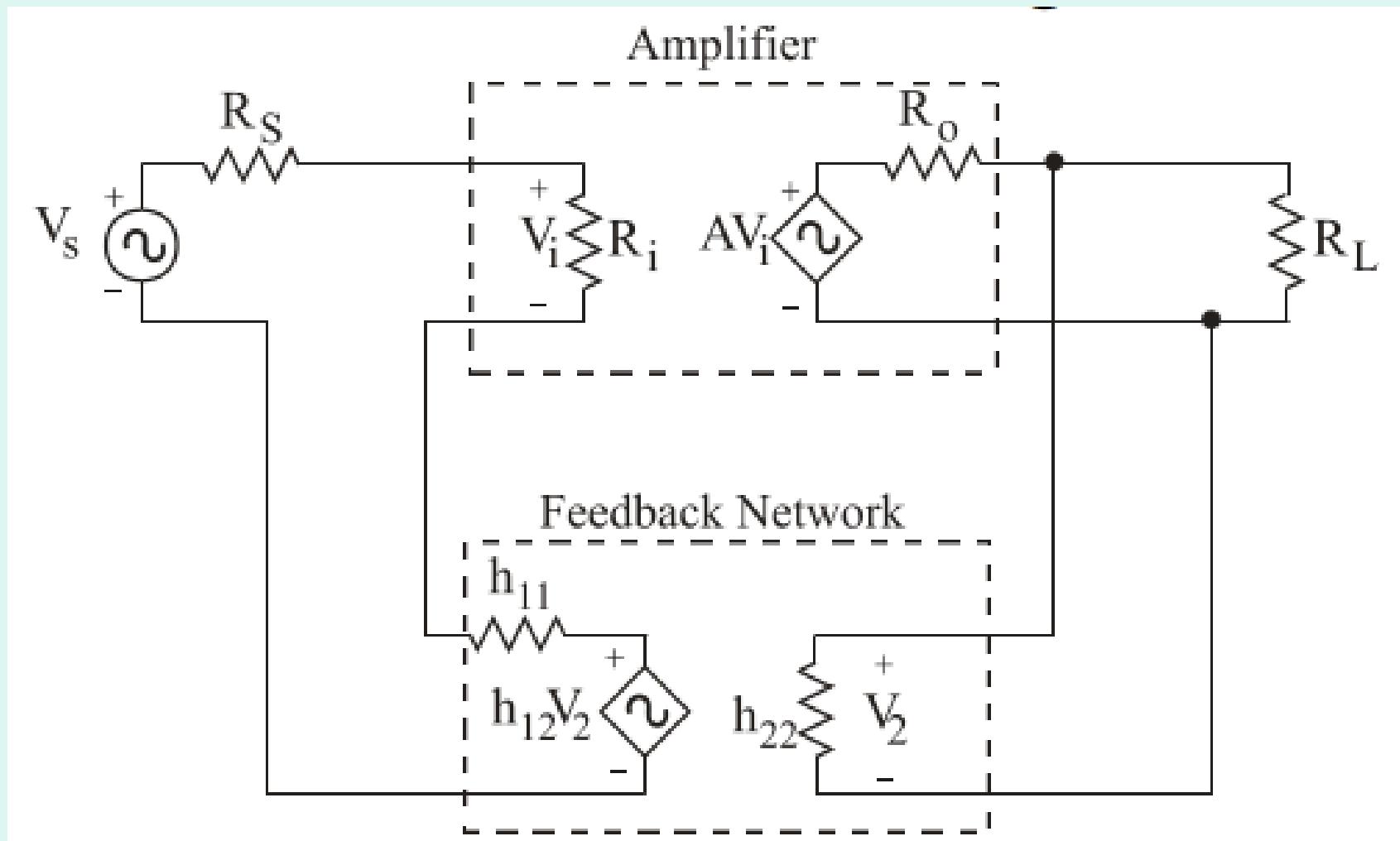


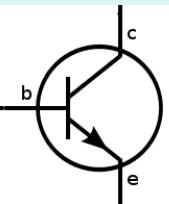

Real β -network \rightarrow Ideal β -network

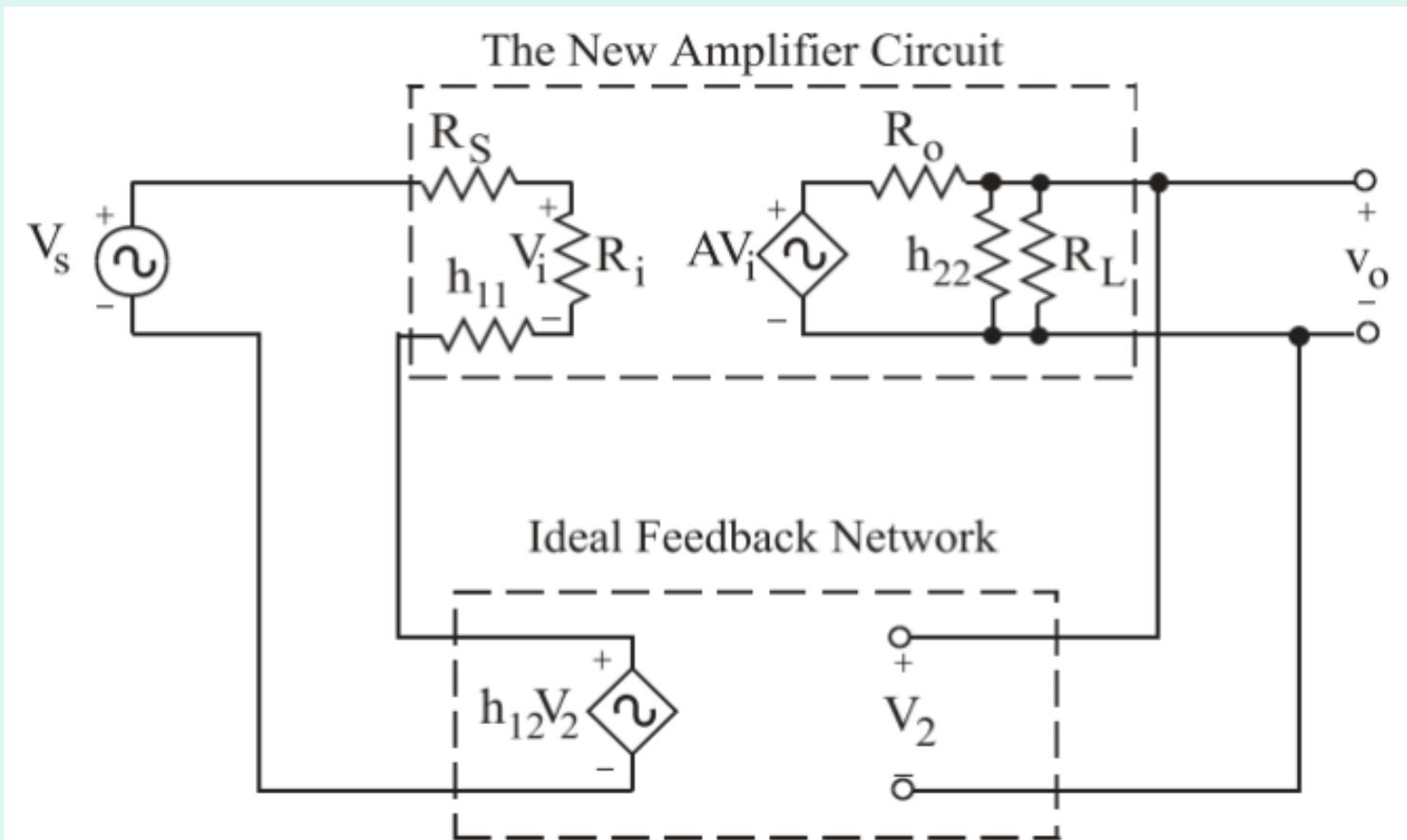
- Absorb the non-ideal terms in the β -network as part of the forward amplifier, to reduce to the ideal feedback case \Rightarrow we can apply the formulas from the ideal case




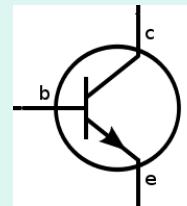

Modified diports: back to ideal feedback

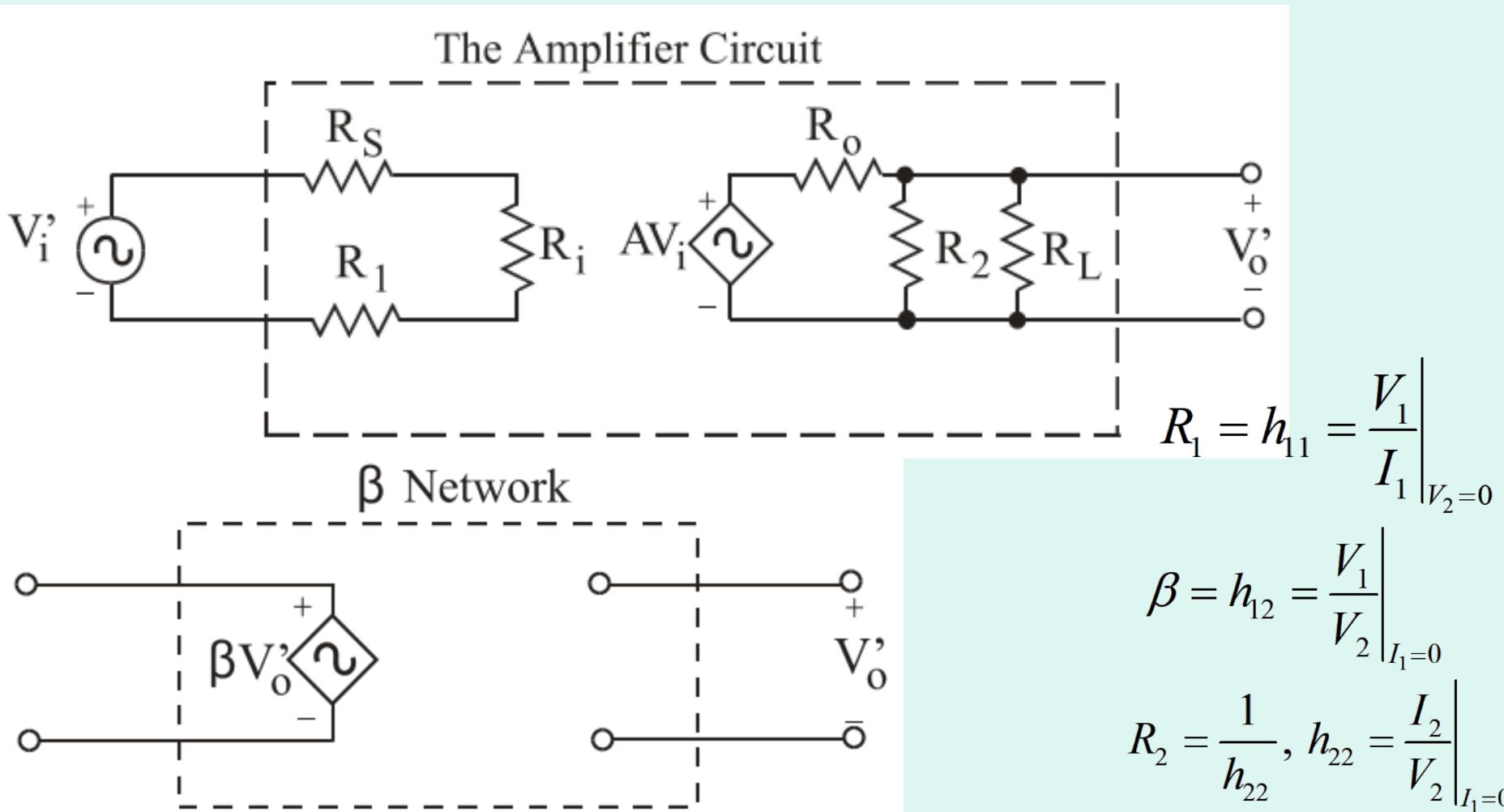
- Circuit transformation: modified amplifier + ideal feedback diport



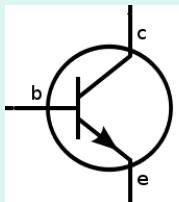

Series-shunt feedback

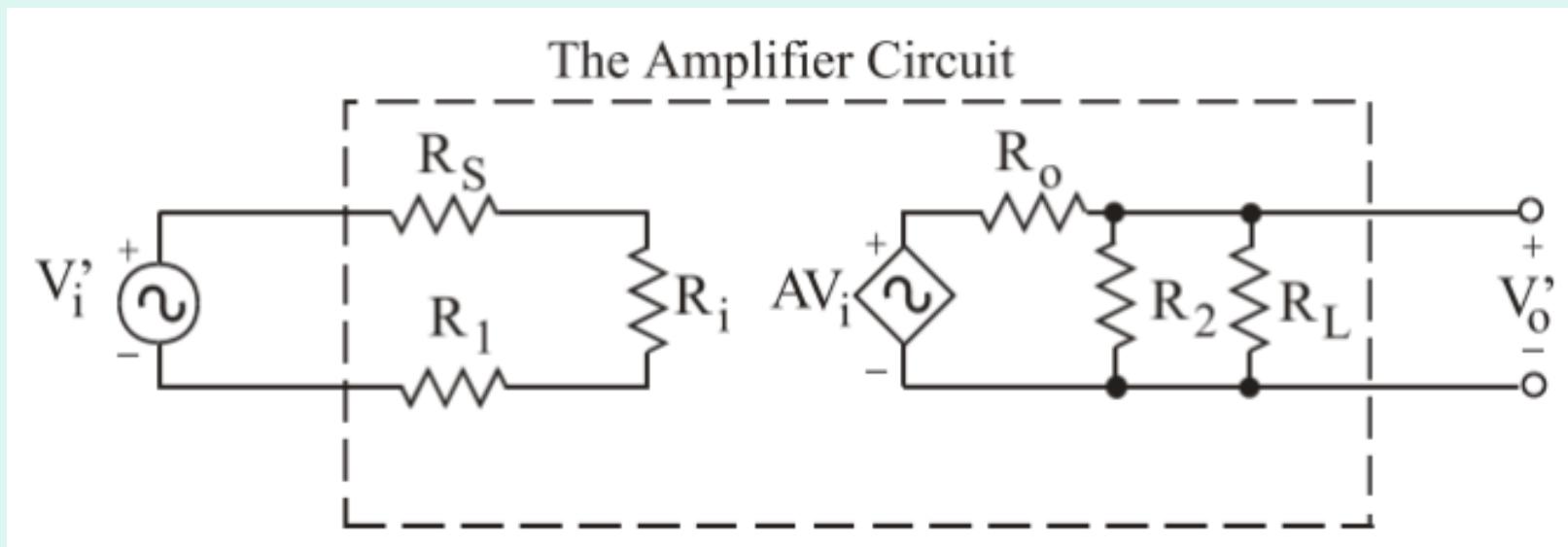- We can apply the feedback formulas for the modified amplifier+ideal feedback case



$$A' = \frac{V_o'}{V_i'} \Rightarrow A_f = \frac{A'}{1 + \beta A'} \quad R_{if} = R_i' (1 + \beta A')$$

$$R_{of} = \frac{R_o}{1 + \beta A'}$$

