
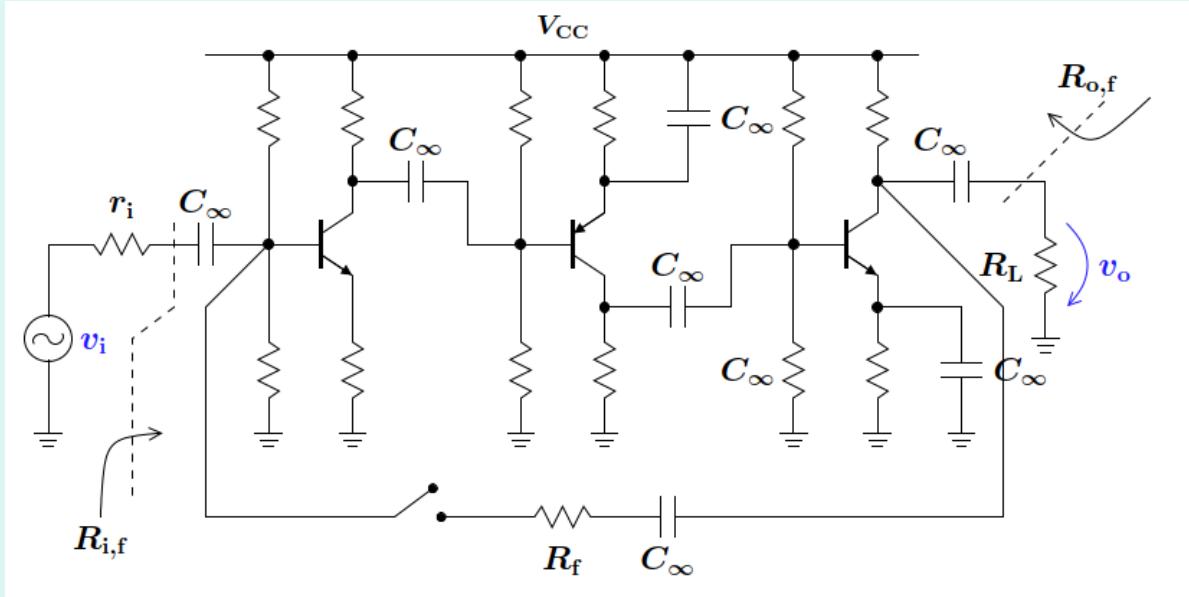


# ELEC 301 - CT and DT filters

L34 - Dec 2, 2025

Instructor: Edmond Cretu

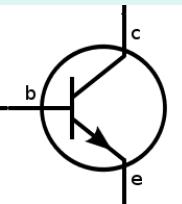



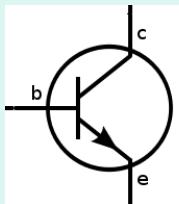
# Recall



- CT active oscillators: phase-shift (RC), RLC (resonator), Wien bridge (RC), quadrature (inverting + noninverting integrators), LC (Hartley, Colpitts)
- Discrete-time approach - switched-capacitors (SC) circuits - emulate large  $R = C +$  fast switching




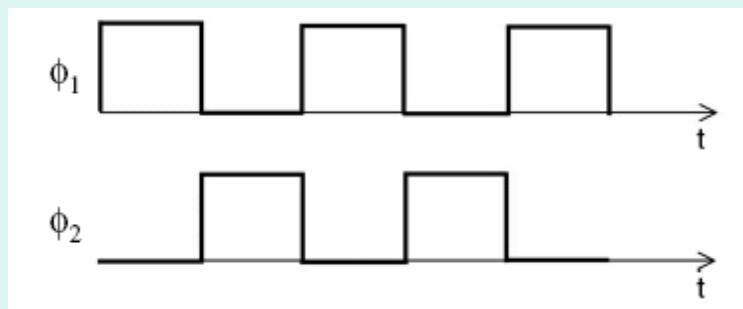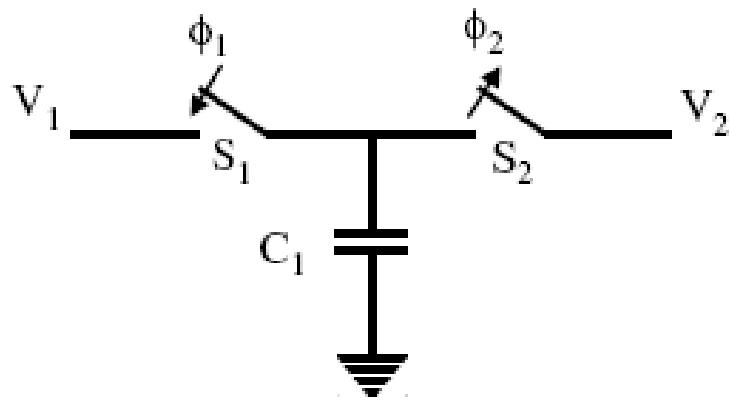
# Switched-capacitor resistor

- Important: non-overlapping clock phases
- small  $C \Rightarrow$  large  $R_{eq,LF}$  + Equivalent resistance value changed by clock frequency




- Charge transfer from  $V_1$  to  $V_2$  as dictated by clock

$$i = \frac{\Delta Q}{\Delta t} = \frac{N \cdot C_1 (V_1 - V_2)}{\Delta t}$$
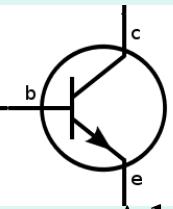
$$\Rightarrow R_{eq,LF} = \frac{V_1 - V_2}{i_{LF}} = \frac{1}{C_1 f_{clk}}$$






# SC resistor emulation circuits

- Alternative ways to mimic a LF resistor through charge transfer


Circuit	Schematic	$R_{eq}$	$Q(\phi_1)$	$Q(\phi_2)$
Parallel		$\frac{T}{C}$	$V_{in}C$	$V_{out}C$
Series		$\frac{T}{C}$	0	$(V_{in} - V_{out})C$
Series-Parallel		$\frac{T}{C_1 + C_2}$	0	$(V_{in} - V_{out})C_1$
Bilinear		$\frac{1}{4} \frac{T}{C}$	$(V_{in} - V_{out})C$	$(V_{out} - V_{in})C$



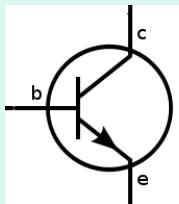


# Exm: integrator circuit



Continuous-time active integrator:

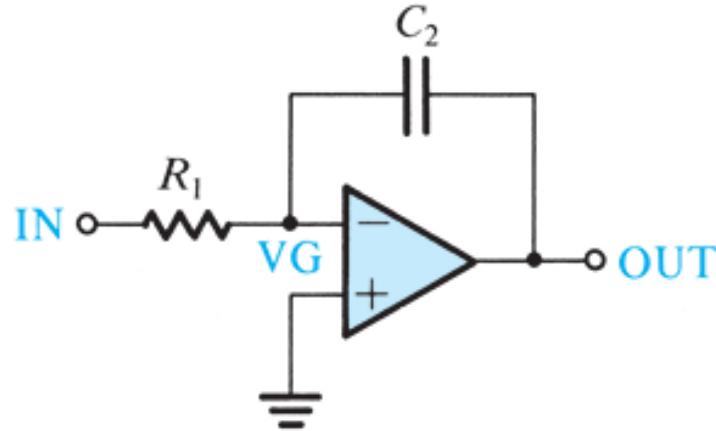

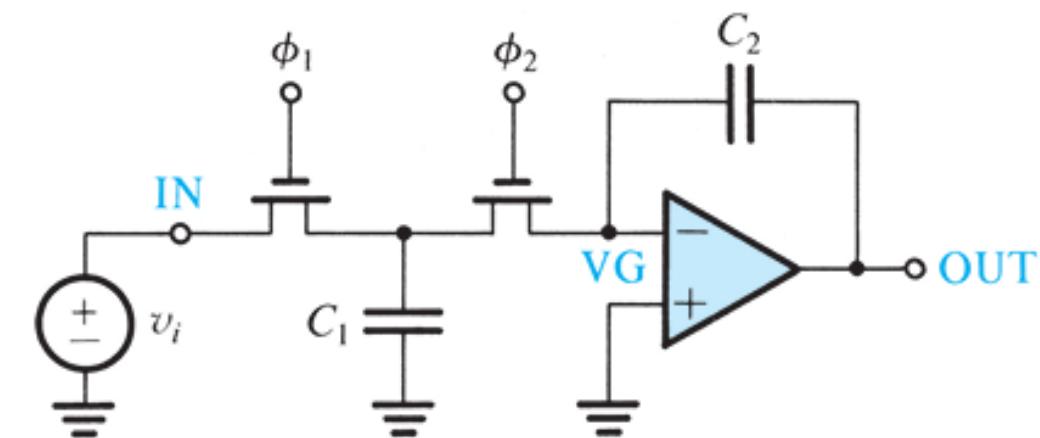Switched-capacitor integrator ( $f_C \gg f_H$ ):




$$\varphi_1 : q_{C1}[n] = C_1 v_i[n]$$

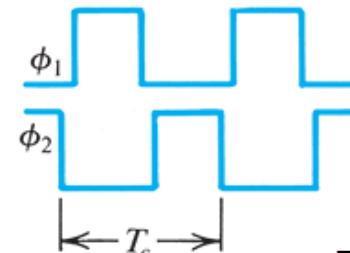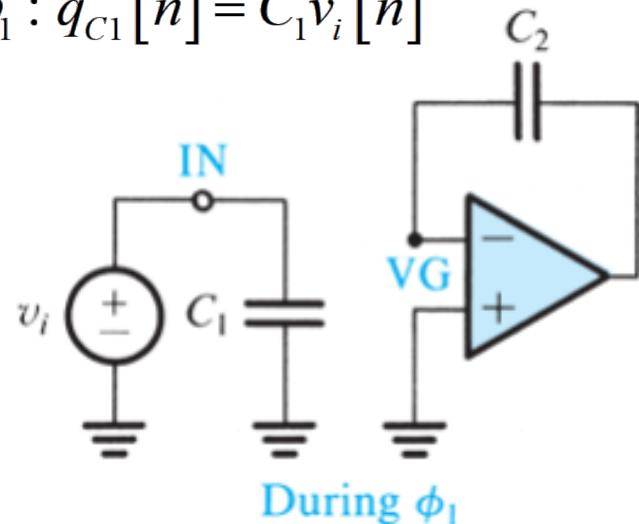


$$\varphi_2 : q_{C2}\left[n + \frac{1}{2}\right] = q_{C1}[n]$$
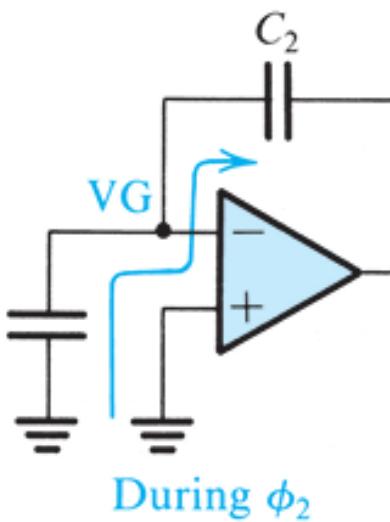
$$v_o\left[n + \frac{1}{2}\right] = v_o[n] - \frac{C_1}{C_2} v_i[n]$$




During  $\phi_2$

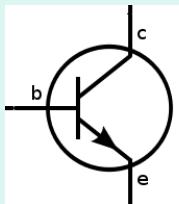
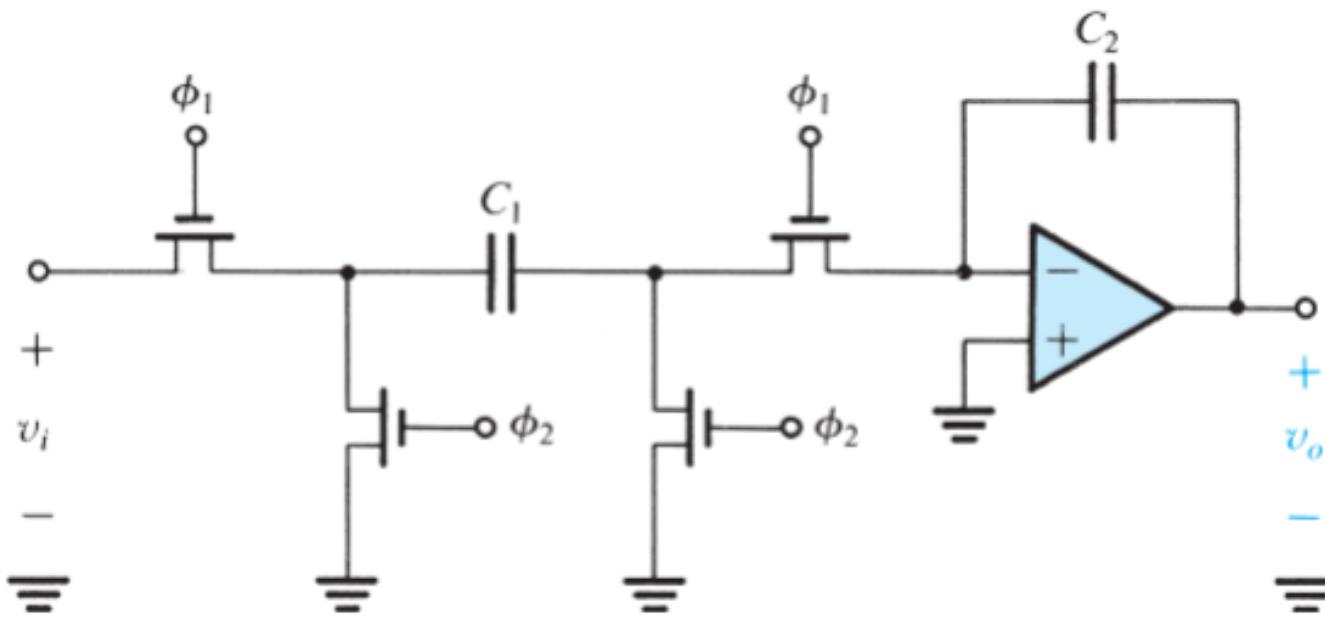
# Improved SC inverting integrator


- SC integrator insensitive to stray capacitances



$$\varphi_1 : q_1[n] = C_1 v_i[n], q_2[n] = q_2\left[n - \frac{1}{2}\right] + q_1[n]$$

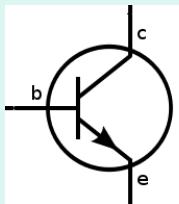
$$\varphi_2 : q_1\left[n + \frac{1}{2}\right] = 0, q_2\left[n + \frac{1}{2}\right] = -C_2 v_o\left[n + \frac{1}{2}\right]$$





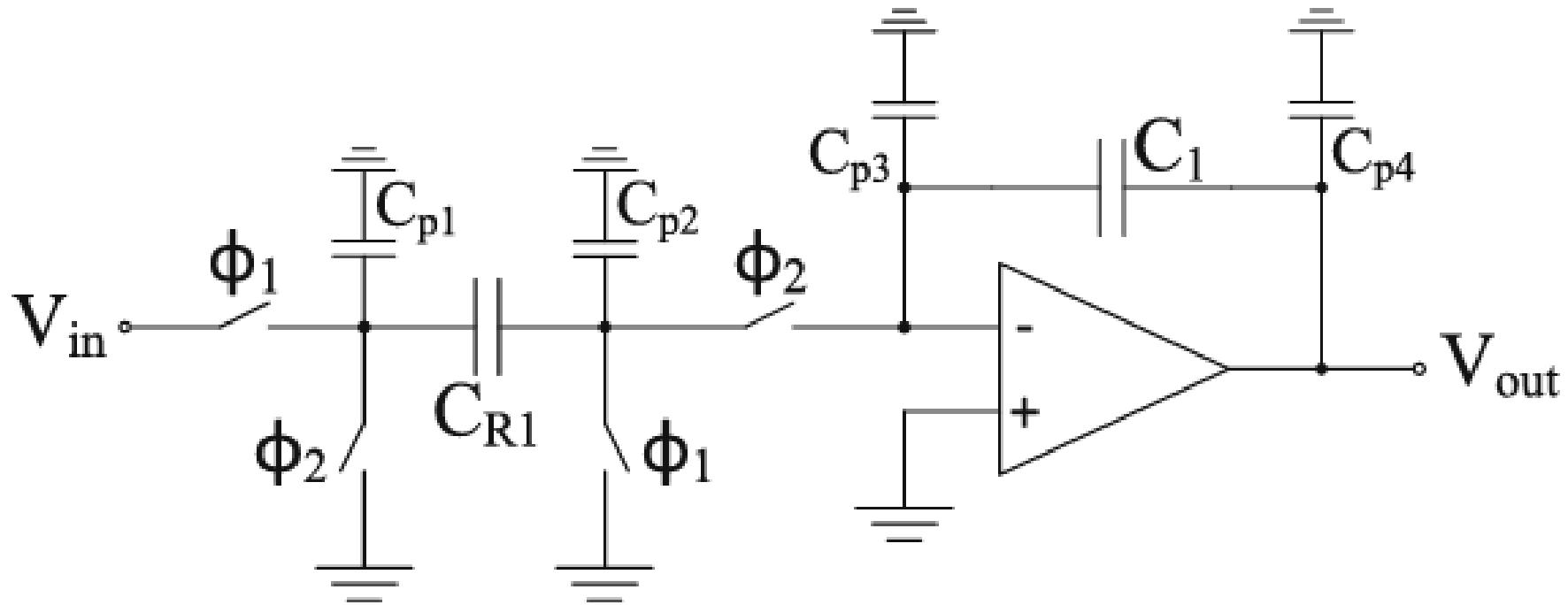
# SC parasitic insensitive integrator

- $C_{pi}$  - stray (parasitic capacitances)



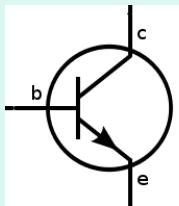


# Improved non-inverting SC integrator

- Two-integrator-loop active filter - pair of complementary SC integrators (inverting + non-inverting)
- circuit insensitive to stray capacitances

$$\varphi_1 : q_1[n] = v_i[n]C_1$$

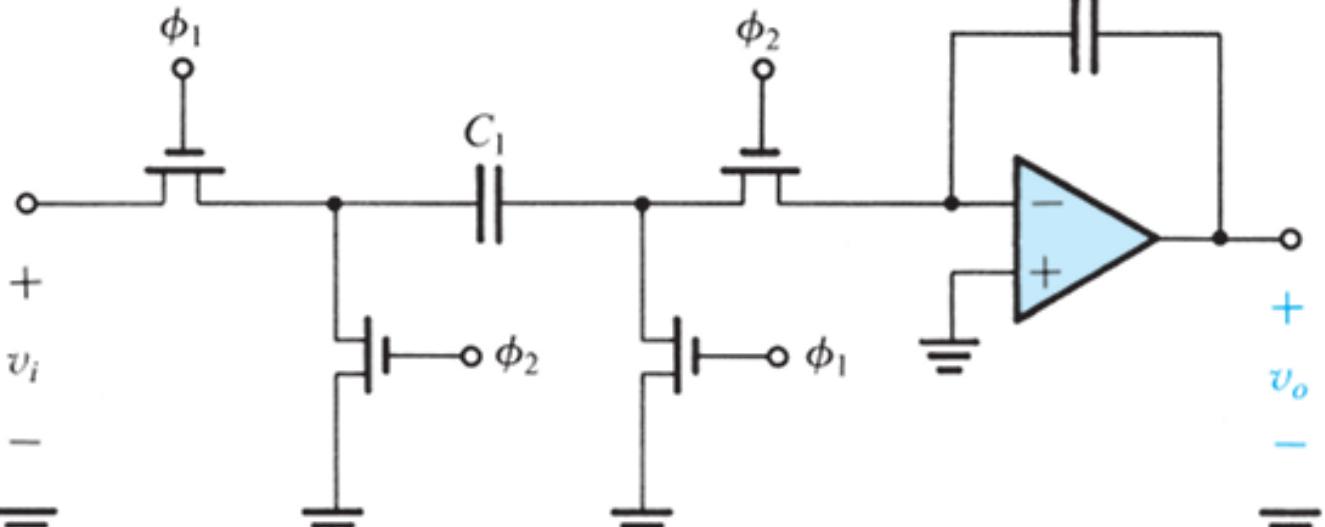
$$\varphi_2 : \Delta q_2\left[n + \frac{1}{2}\right] = -q_1[n] = -C_1 v_i[n]$$



Non-inverting SC integrator:
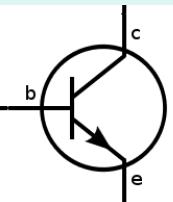
$$v_o\left[n + \frac{1}{2}\right] = v_o[n] - \frac{\Delta q_2\left[n + \frac{1}{2}\right]}{C_2} = v_o[n] + v_i[n] \frac{C_1}{C_2}$$






# Comparison of active RC and SC filters

	Active RC (conventional)	SC
-Integrate on an MOS Chip?	Not possible for precision filter.	Readily possible.
-Is tuning necessary?	Yes.	No.
-Noise?	Depends on impedance level and amplifiers.	Depends on capacitance level and amplifiers. Generally larger than with Active RC.

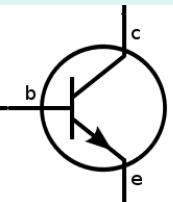Source: Moschytz[2019]Analog circuit theory and filter design






# Active RC integrator block

The integrator is a basic building block for MOS VLSI networks and filters.

## 1. Active RC Integrator

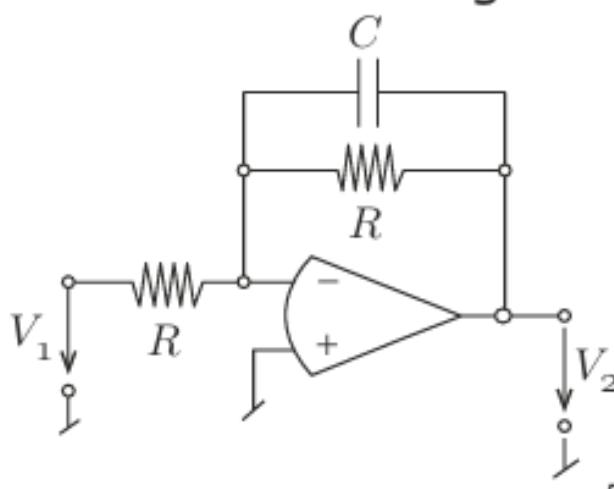

$$T = 1ms, C = 10 \text{ pF} \Rightarrow R = \frac{T}{C} = 100 M\Omega$$

$$\frac{V_2}{V_1} = \frac{1}{1+sT}$$


$$T = RC$$

Required Chip area:

Opamp:	$0.04 \text{ mm}^2$
Resistors (100 MΩ):	$2 \times 3 \text{ mm}^2$
Capacitor (10 pF):	$0.02 \text{ mm}^2$
Total Chip Area:	<u><math>6.06 \text{ mm}^2</math></u>

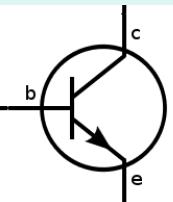
Source: Moschytz[2019] Analog circuit theory and filter design





# Active SC integrator block

## 2. Active SC Integrator

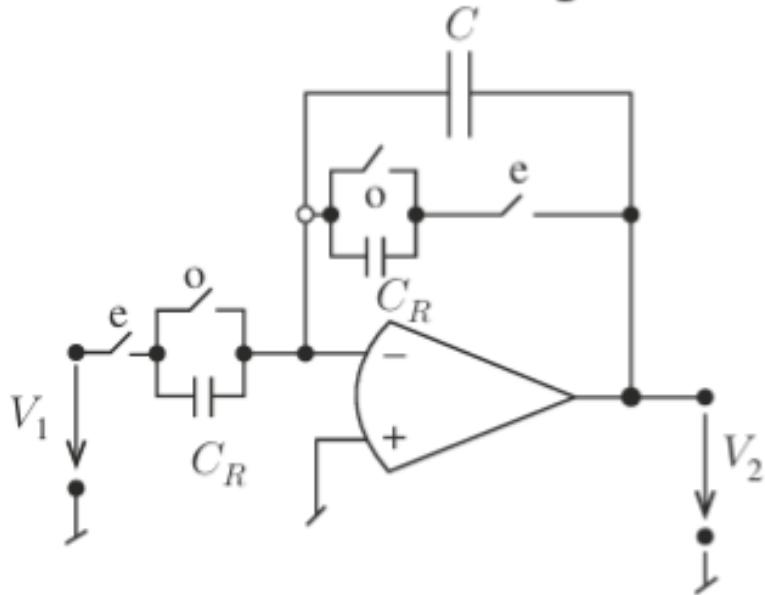

$$\frac{V_2^e}{V_1^e} = \frac{1}{1 + pC \frac{\tau}{C_R}} = \frac{1}{1 + (1 - z^{-2}) \frac{C}{C_R}}$$


$$f_s = \frac{1}{T} = 10 \text{ kHz}$$

$$p = \frac{1 - z^{-2}}{\tau}$$

$$T = 2\tau$$

Required Chip area: Opamp:	$0.04 \text{ mm}^2$
Resistors ( $100 \text{ M}\Omega$ )	$0.02 \text{ mm}^2$
Capacitor ( $10 \text{ pF}$ )	$2 \times 0.002 \text{ mm}^2$
Switch:	$4 \times 0.005 \text{ mm}^2$
Total Chip Area:	<u><u><math>0.084 \text{ mm}^2</math></u></u>

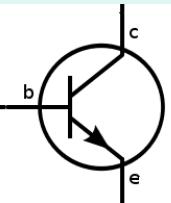Source: Moschytz[2019] Analog circuit theory and filter design



# Comparison of active RC and SC integrators

## Active RC Integrator

Large Tolerance on  
R and C:

$$\frac{\Delta R}{R} \sim 25\%$$

$$\frac{\Delta C}{C} \sim 10\%$$

Large TCR and  
voltage dependence of R

## Active SC Integrator

$\tau$  determined  
by quartz oscillator;


$$\frac{C}{C_R} \quad \text{accurate to less than} \\ 0.005 \%$$

Active SC circuit requires much smaller chip area (almost two orders of magnitude) and is far more accurate than Active RC circuits on MOS chip.


Remember: MOS chip circuits cannot be tuned on-chip.

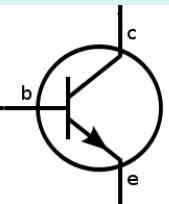Source: Moschytz[2019] Analog circuit theory and filter design





# SC charge transfer - sensor interfaces

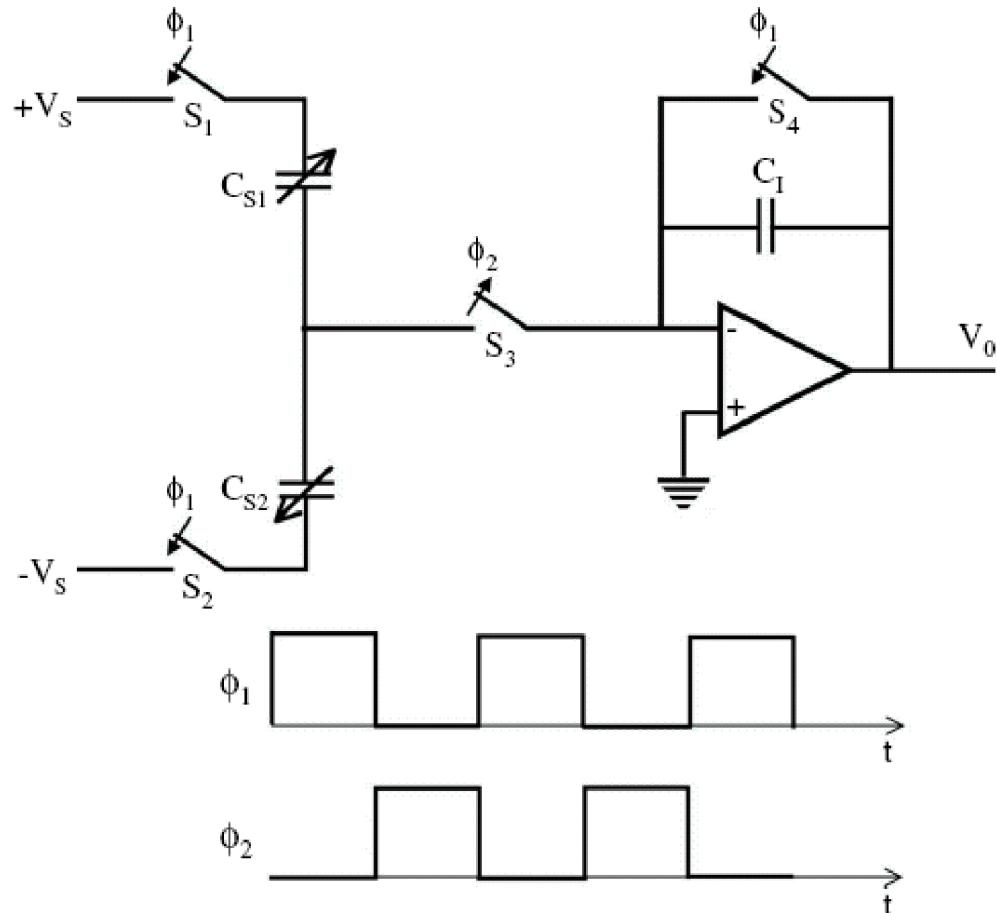


$$V_o = V_s \frac{C_{s1} - C_{s2}}{C_I}$$

$f_{clk} \gg f_{\text{analog signals}}$


Homework: deduce the transfer function




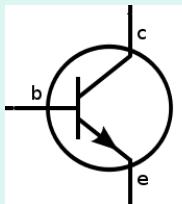
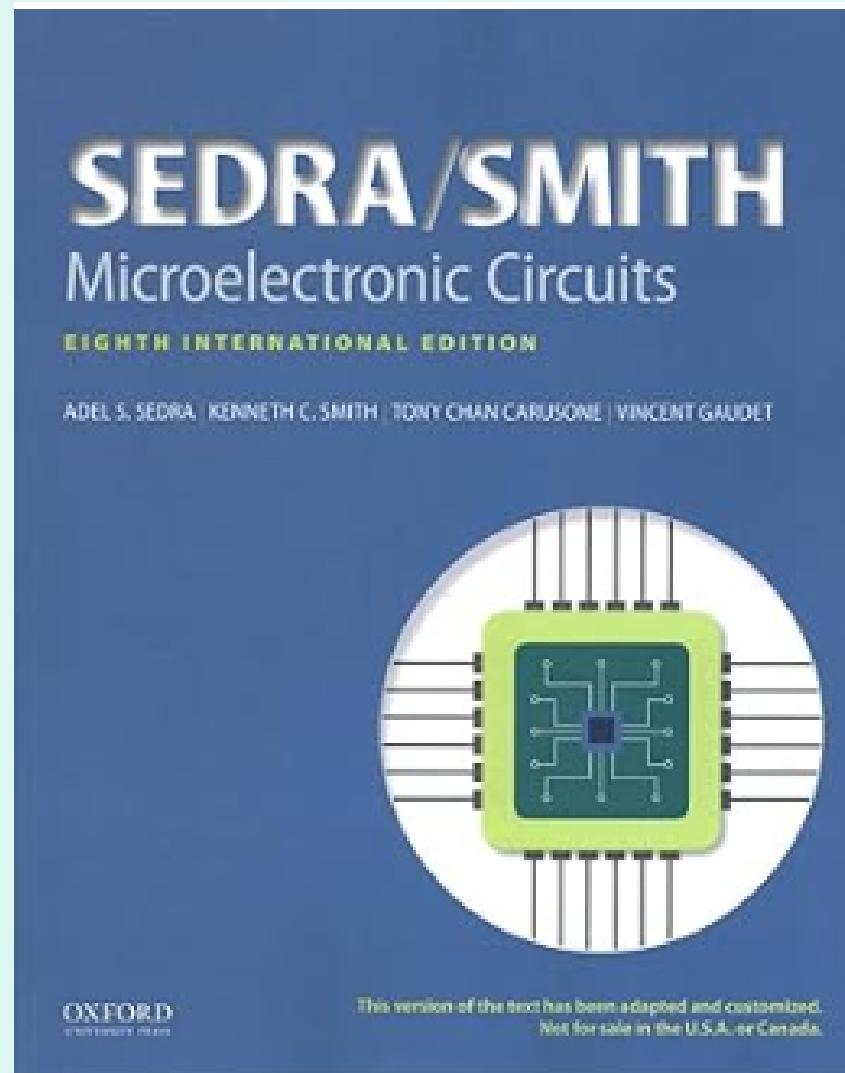
# Supplementary resources


- Sedra&Smith - Microelectronic Circuits, OUP




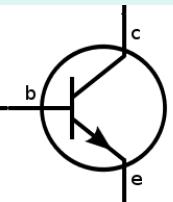
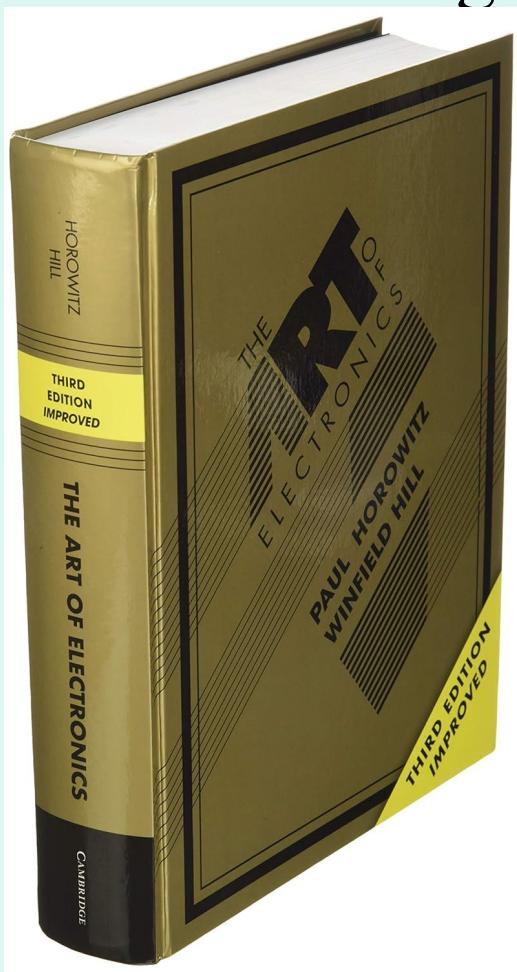
# Horowitz - The Art of Electronics


- Another comprehensive book
- Cambridge University Press




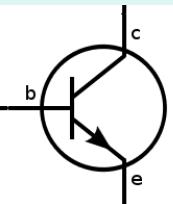
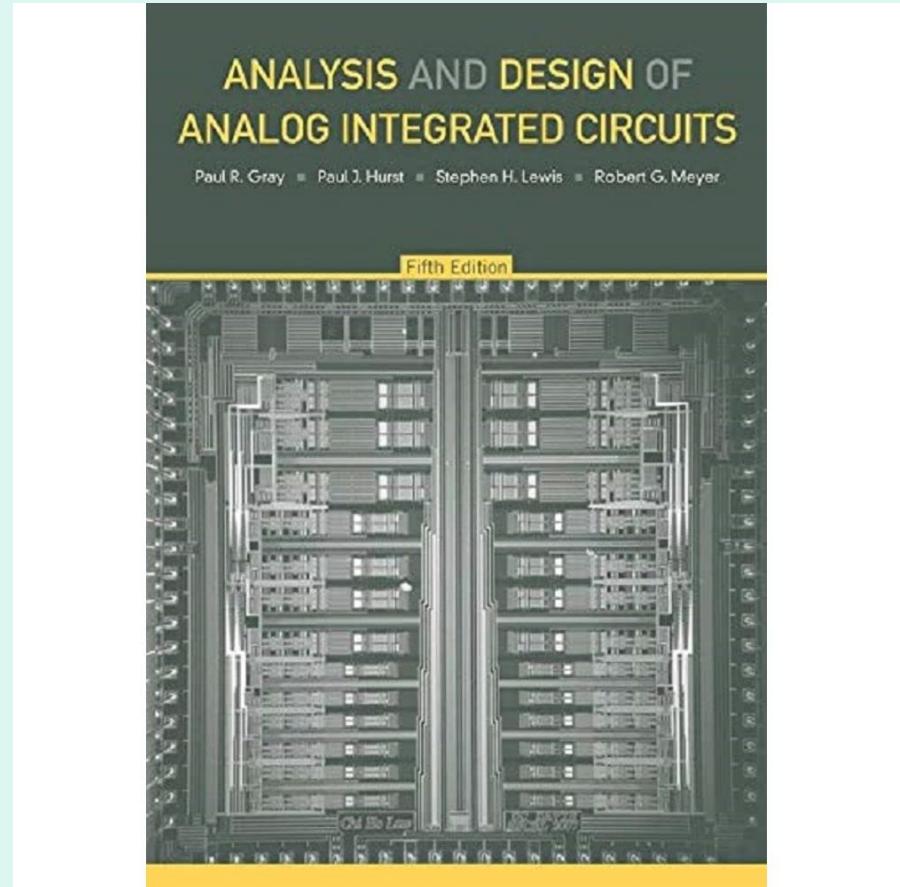
# Analog integrated circuits


- Gray&Meyer[2000] Analysis and design of analog integrated circuits, 5ed, Wiley
- Covers the design of both bipolar and CMOS analog ICs




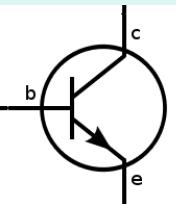
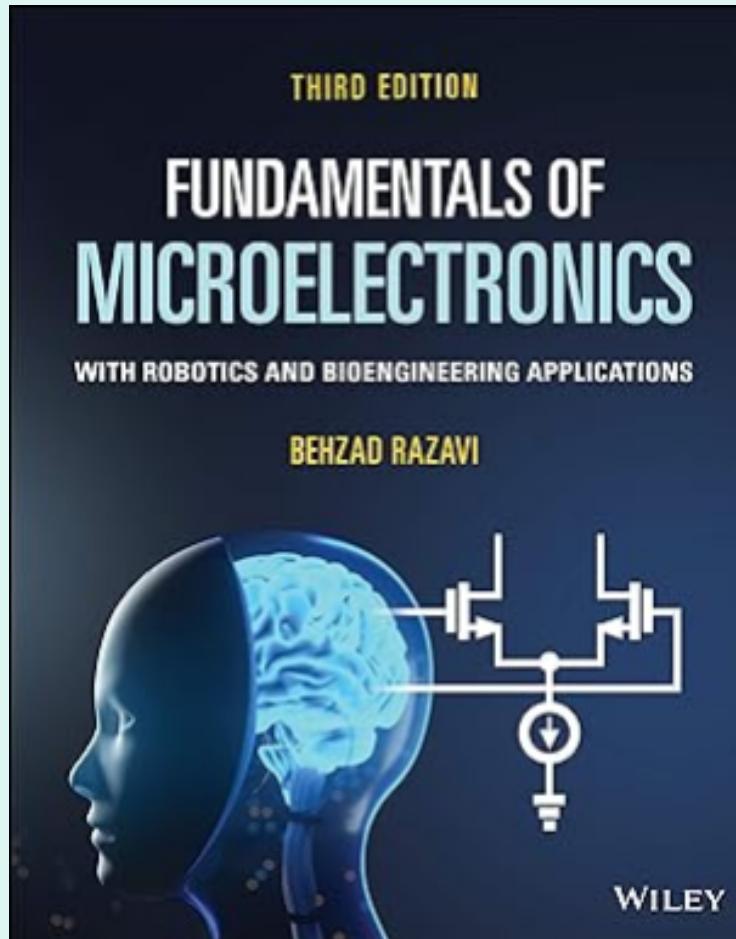
# Microelectronics


- Razavi[2021] Fundamentals of microelectronics, 3ed, Wiley




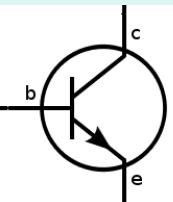
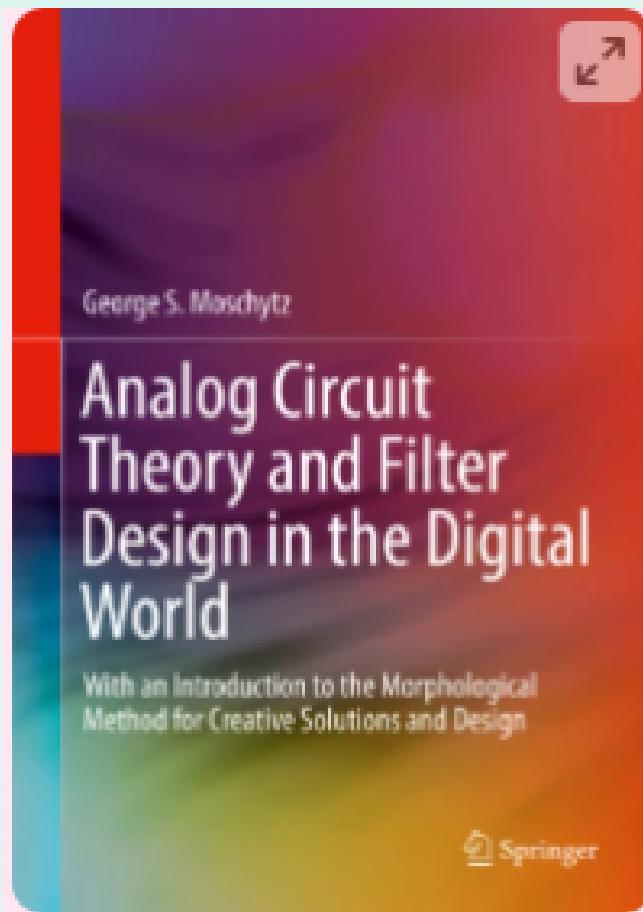
# Filter design


- Moschytz[2019] Analog Circuit Theory and Filter Design in the Digital World, Springer
- <https://link.springer.com/book/10.1007/978-3-030-00096-7>




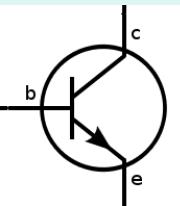
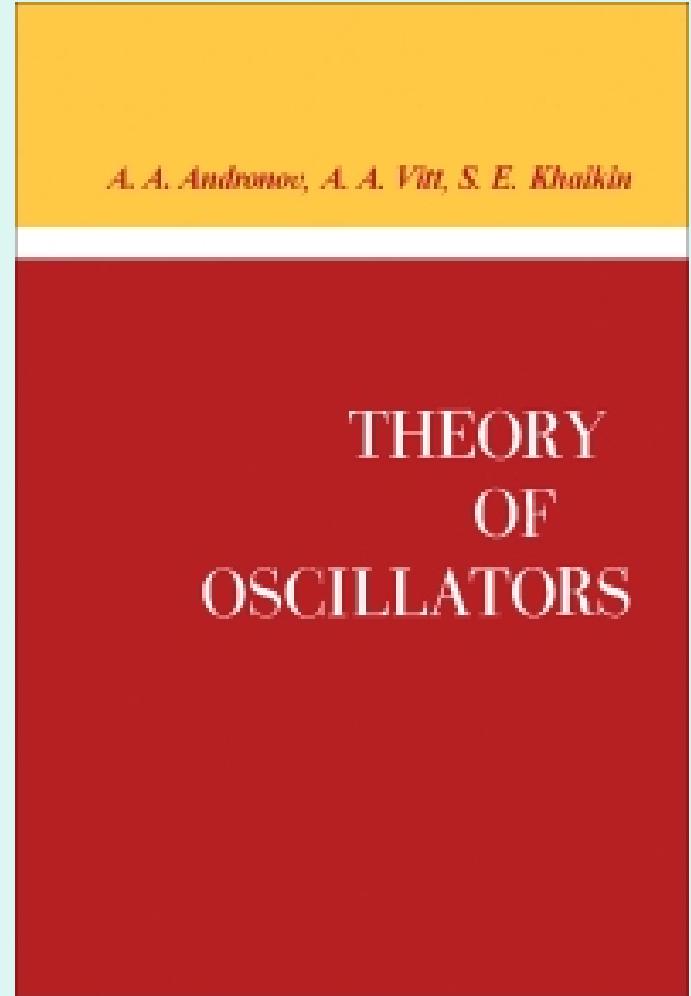
# Oscillators


- Andronov[2013] Theory of oscillators, Elsevier
- Analysis from the physical perspective (conservative systems, dissipative systems, self-oscillating systems), stability, differential equations (time domain)



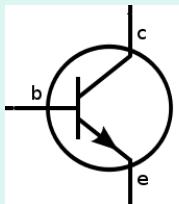

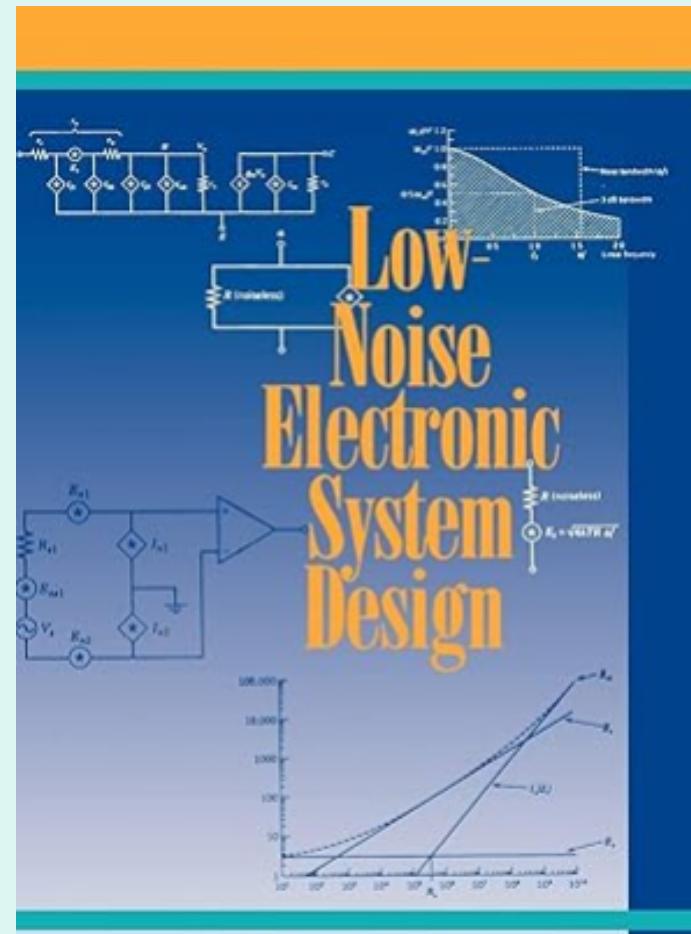
# Low-noise design

- Motchenbacher[1993]  
Low-noise electronic  
system design, Wiley




C. D. Motchenbacher  
J. A. Connelly




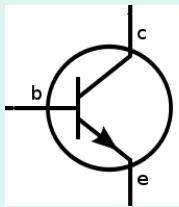
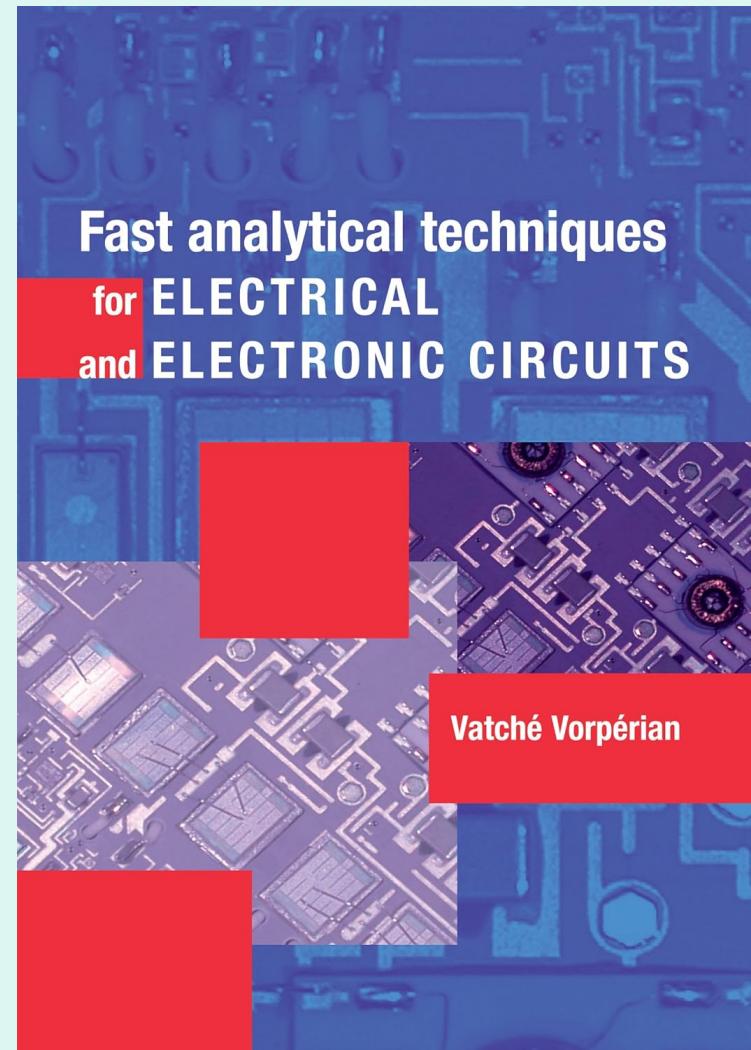
# Fast approximations in circuit computation

- Vorperian[2002]Fast analytical techniques for electrical and electronic circuits, CUP



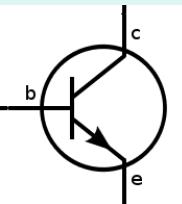

# Generalized circuits

- Extension to multiphysics systems - design, analysis, synthesis
- Information flow (signals, block diagrams, SFG) vs. energy/power flow (generalized voltage/current ports)



