
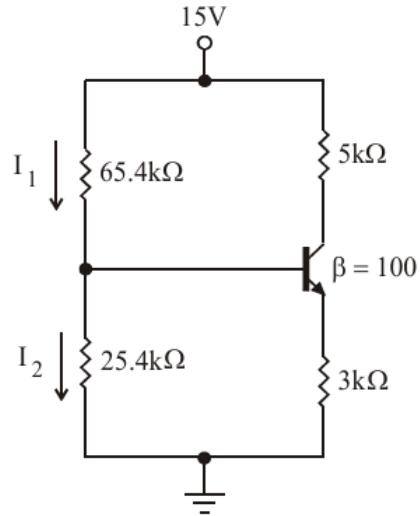


Problem set 2

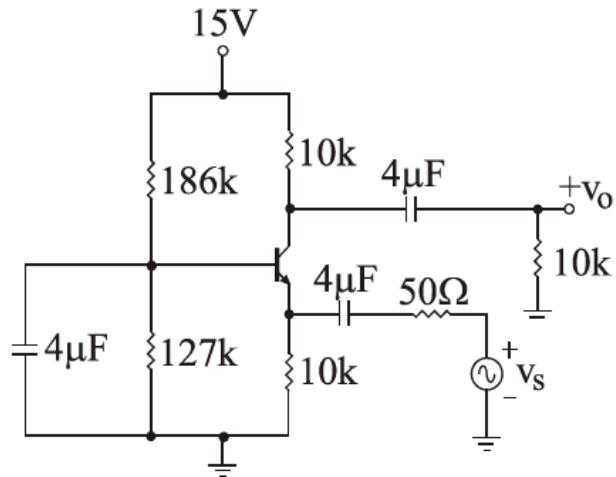1. For the circuit shown below, find I_1 , I_2 , I_C , I_E , g_m and r_π .




2. For the circuit below, find A_M , $\omega_{3\text{dB}_L}$ and $\omega_{3\text{dB}_H}$, given that $\beta=100$ and the hybrid- π model has the parameters $c_\pi=10\text{pF}$, $c_\mu=2\text{pF}$ and $r_o=\infty$.



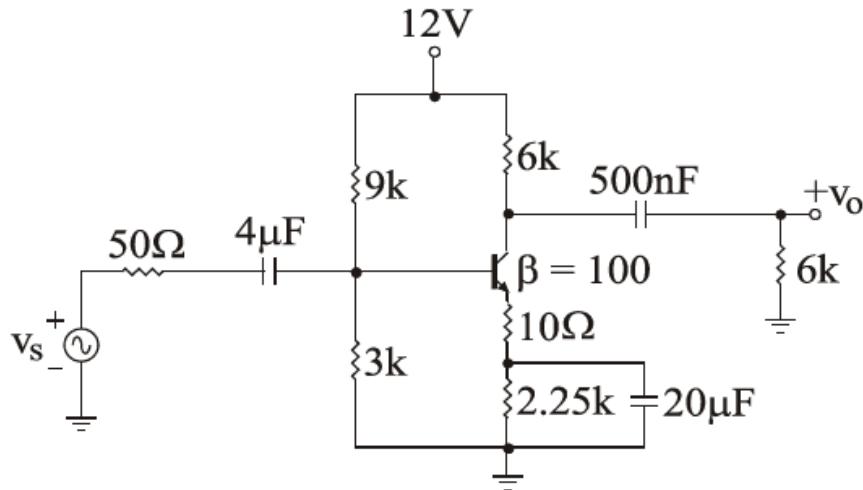
3. For the circuit below:

3a. draw the low-frequency circuit, the mid-band circuit and the high-frequency circuit
 3b. derive the mid-band gain A_M and $F_L(s)$




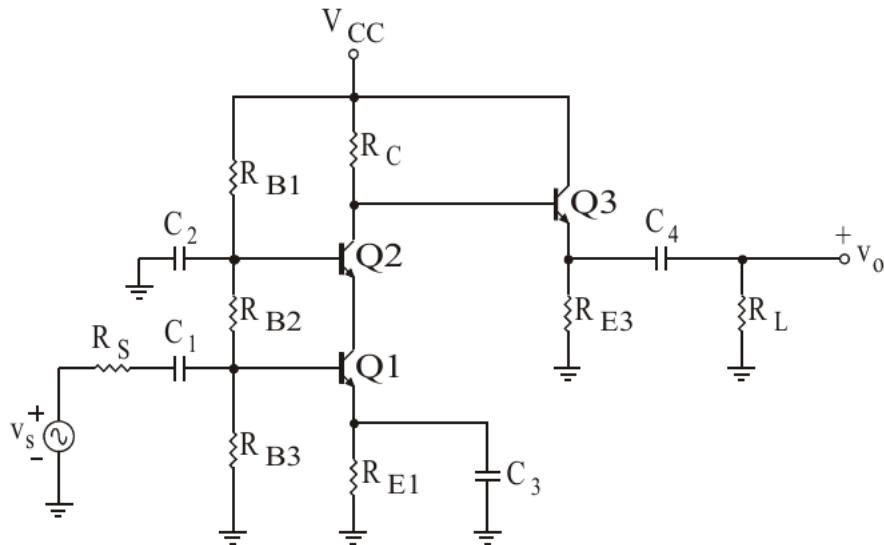4. For the circuit below, do the following:


- Draw the high-frequency small-signal model
- Show that $v_{p1}=v_{p2}$ at mid-band, irrespective of whether $b_1=b_2$ or not
- find the expressions for the three high-frequency poles. Which one do you think will be the dominant pole.



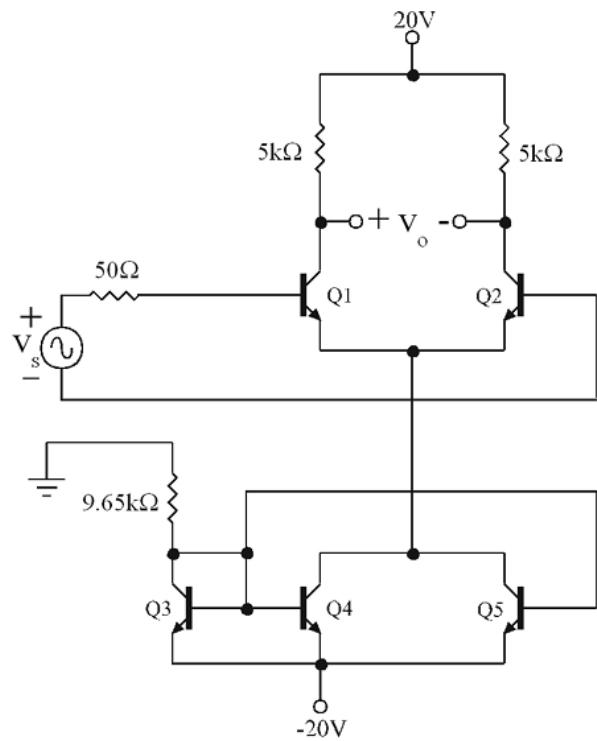
5. Assuming that the differential amplifier shown below is attached to a load consisting of a $10k\Omega$ resistor in parallel with a $100pF$ capacitor, find the value of the mid-band gain and the high-frequency 3dB point (A: $A_M=-196V/V$, $\omega_{3dBH}=1.98\times 10^6$ rad/s)



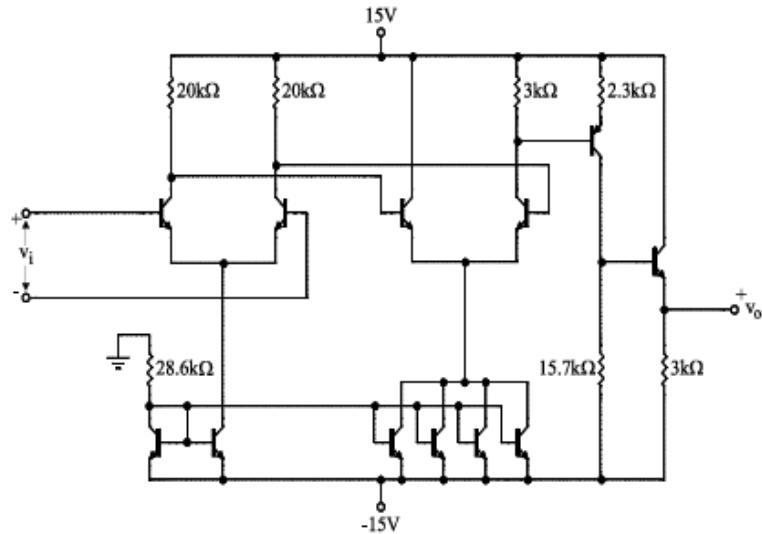
6. For the circuit below calculate A_m for $\beta=200$ for all of the transistors



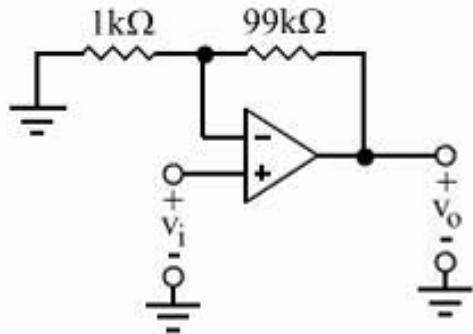
7. The op-amp shown below has an open-loop gain of 10^5 and a bandwidth of 10Hz (single-pole transfer function approximation). Use feedback techniques to calculate the gain and bandwidth of the circuit. What would the gain and bandwidth be if the open-loop gain of the op-amp was 5×10^4 instead of 10^5 ?



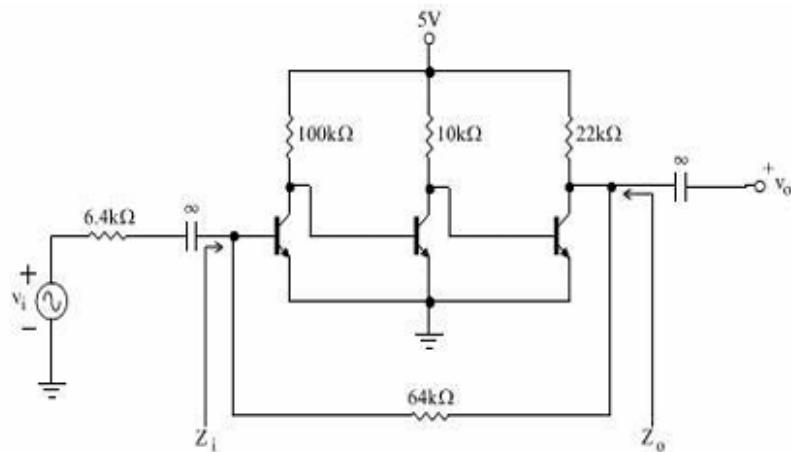8. For the circuit below, calculate A_M , Z_i , and Z_o , all at mid-band



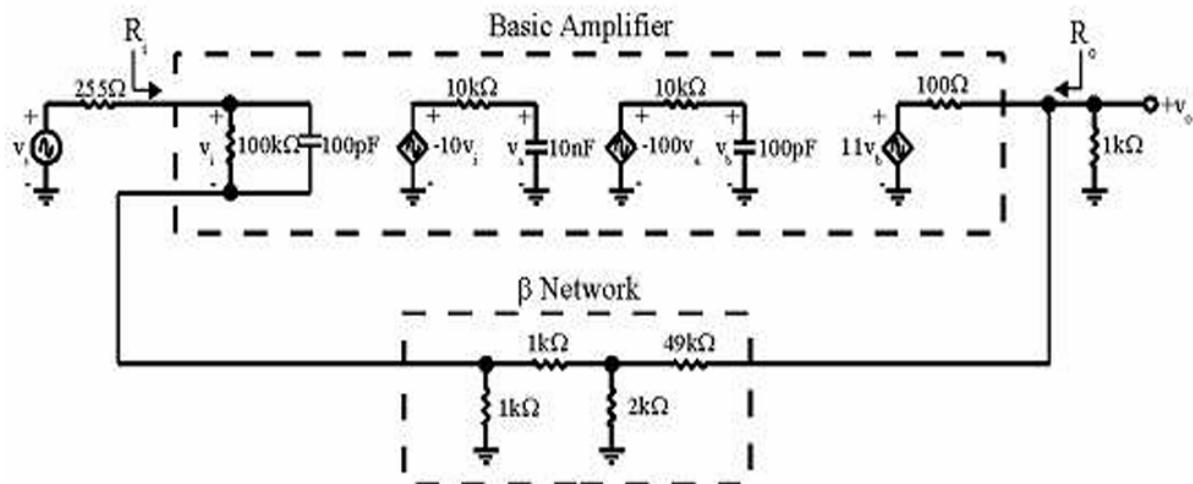9. For the circuit below use feedback techniques to find the mid-band gain $A_M = v_o/v_s$, the gain margin (GM), the phase margin (PM = $\phi_1 - \phi_{180}$), the input resistance R_i and the output resistance R_o of the amplifier (Hint: use the series-shunt feedback topology).



10. For the circuit below find the loop gain $L(s)$, the frequency of oscillation and R_2/R_1 for oscillation. Assume the op-amp to be ideal.

