

THE UNIVERSITY OF BRITISH COLUMBIA  
Department of Electrical and Computer Engineering


ELEC 311 – Electromagnetic Fields and Waves

Smith Chart Practice

The high-frequency lossless transmission system shown below operates at 700 MHz with a phase velocity in each line section of  $2.1 \times 10^8$  m/s. Use the Smith Chart to find the VSWR on each section of line and the input impedance to line #1 at the drive point.

There are three distinct transmission line problems to be solved. In the figure below,  $R_0$  is equivalent to  $Z_0$ .

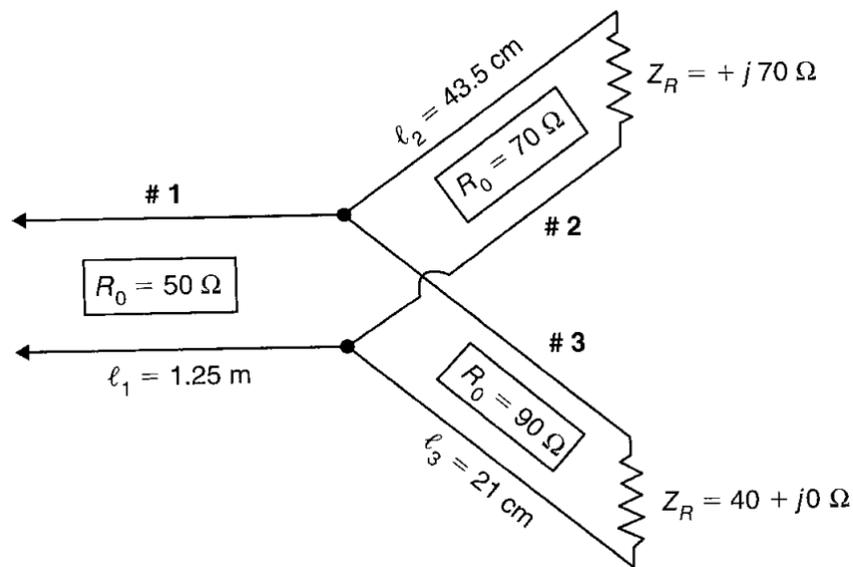- VSWR of Line #2 [10]
- VSWR of Line #3 [10]
- VSWR of Line #1 and the input impedance [10]



## Solution

For the three lines the wavelength is  $\lambda = (2.1 \times 10^8) / (7 \times 10^8) = 30$  cm. For line #2 the length is  $(43.5/30)\lambda = 1.45\lambda$  and the normalized load is  $(0 + j70)/70 = j1$ . Plot this value as point 1 in Fig. 15-23. Note the reference position,  $0.125\lambda$  and  $VSWR = \infty$ . Move on the VSWR circle  $1.45\lambda$  toward the generator to point 2 and read the value  $z_{in} = 0 + j0.51$ . The input impedance to line #2,

$$Z_{in2} = z_{in}R_{02} = 0 + j35.7 \Omega$$

is one part of the load on line #1.

For line #3 the length is  $\frac{21}{30} = 0.7\lambda$  and the normalized load is  $(40 + j0)/90 = 0.44 + j0$ . Plot this value as point 3 and note the reference position of  $0\lambda$  and the  $VSWR = 2.25$ . Move on the VSWR circle  $0.7\lambda$  toward the generator to point 4, and read off

$$z_{in} = 1.62 + j0.86 \quad \text{or} \quad Z_{in3} = z_{in}R_{03} = 145.8 + j77.4 \Omega$$

This is the second part of the load on line #1.

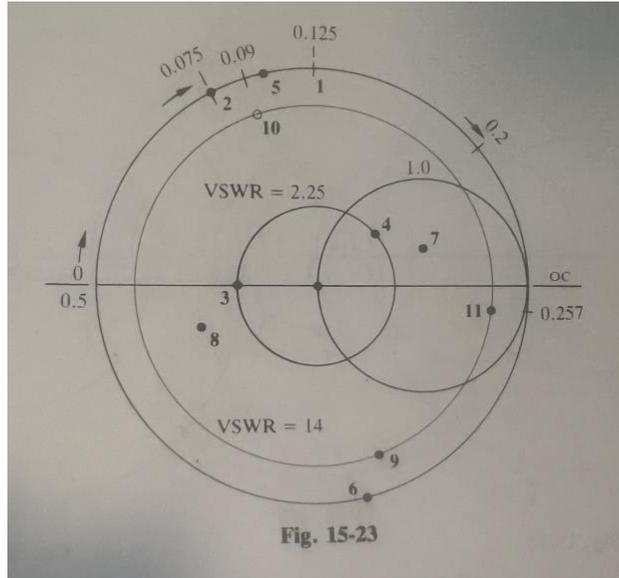


Fig. 15-23

For line #1: the length is  $1.25/0.30 = 4.167\lambda$  and the load is the parallel combination of  $Z_{in2}$  and  $Z_{in3}$ . Normalize each impedance to the  $50\text{-}\Omega$  line, find each admittance, add the admittances for  $y_R$ , and then find  $z_R$ .

$$z_2 = j\left(\frac{35.7}{50}\right) = 0 + j0.714 \quad (\text{point 5}) \quad \text{and} \quad y_2 = 0 - j1.41 \quad (\text{point 6})$$

$$z_3 = \frac{145.8 + j77.4}{50} = 2.92 + j1.55 \quad (\text{point 7}) \quad \text{and} \quad y_3 = 0.27 - j0.14 \quad (\text{point 8})$$

$$y_R = 0.27 - j1.55 \quad (\text{point 9}) \quad \text{with} \quad VSWR = 14$$

Invert by moving a diameter across to point 10 for  $z_R = 0.1 + j0.63$  at the reference position  $0.09\lambda$ . Now move  $4.167\lambda$  toward the generator from  $z_R$  on the  $VSWR = 14$  circle to point 11, and read  $z_{in} = 9.5 - j6.3$ . The input impedance to line #1 is

$$50(9.5 - j6.3) = 475 - j315 \Omega$$