

# ELEC 342

# Electromechanical Energy Conversion and Transmission

2025-26 Winter Term 2

Lecture 2

January 8, 2026

Zhi Jin (Justin) Zhang

# Course logistics

- Labs: Need to work in pairs, find your partner now
- TA office hour poll:

## ☒ Poll Results

Poll is now closed

### Monday afternoon



7 votes (47%)

### Tuesday afternoon



2 votes (13%)

### Wednesday morning



3 votes (20%)

### ☒ Wednesday afternoon



12 votes (80%)

### Thursday afternoon



2 votes (13%)

A total of 15 voter(s) in 48 hours


# Module 1, Part 1: Review of AC Circuits & Phasors

# Objectives & important concepts

- Concept of phasors & notations
- RMS value
- Phasor diagrams for basic RLC circuits
- Balanced 3-phase system, source, load, Y /  $\Delta$  connection, line-to-line and phase voltages and currents, phase shifts
- Real, reactive, and apparent power in 1-phase and 3-phase systems, power factor
- Read Appendix B, get ready for Lab 1
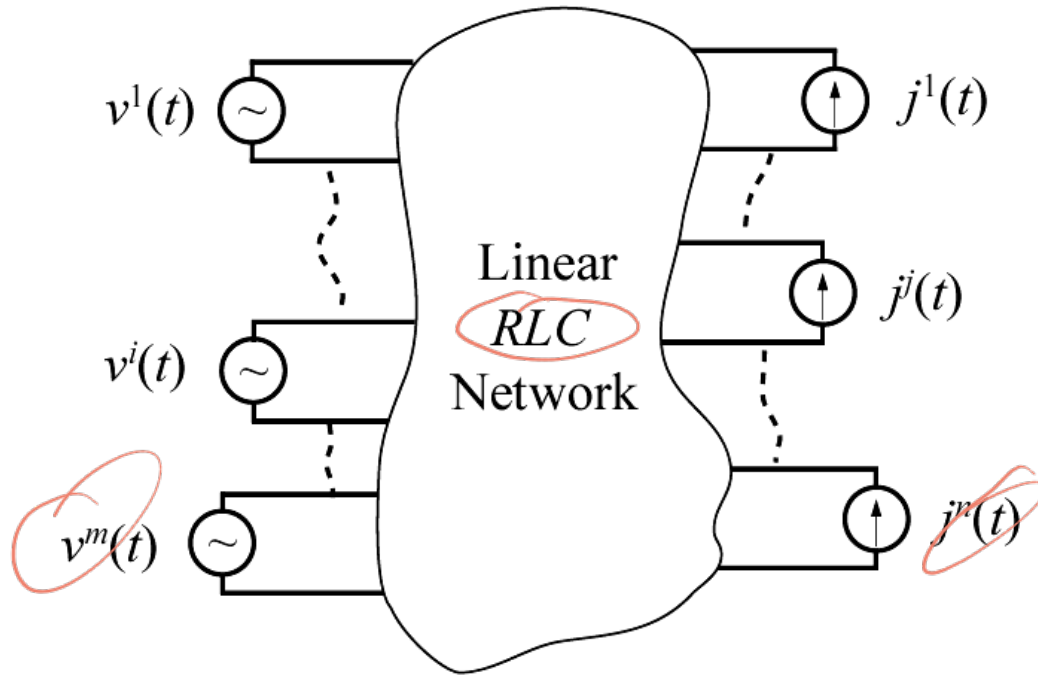
# AC circuits

- Consider arbitrary network
  - With voltage and current sources



$$v^i(t) = V^i \cos(\omega t + \varphi^i)$$

$$j^j(t) = J^j \cos(\omega t + \varphi^j)$$

Steady state solution?

For all circuit branches the currents & voltages are sinusoidal

$$i_k(t) = I_k \cos(\omega t + \theta_i^k)$$


$$v_k(t) = V_k \cos(\omega t + \theta_v^k)$$

**Note:**

For Steady State analysis we need to know only amplitudes  $J^k, V^k$  & phases  $\theta_i^k, \theta_v^k$
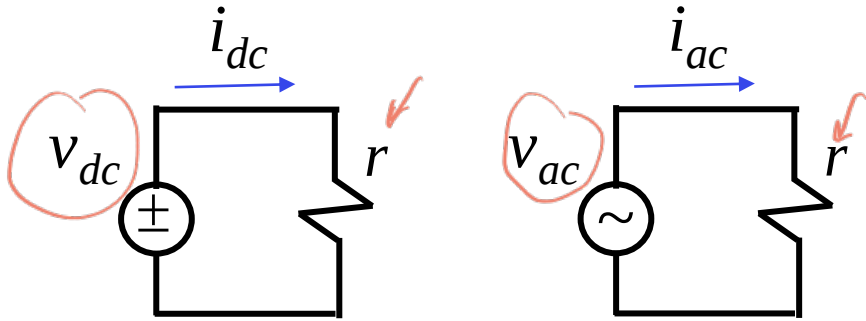
# Root-Mean-Square (RMS) Value

\* Value equivalent to the DC voltage (current) that, when applied to a resistor, dissipates the same average power as the given AC value



Instantaneous power in terms of **voltage**

$$P(t) = vi = v \frac{v}{r} = \frac{1}{r} v^2$$

Average power over period  $T$

$$P_{ave} = \frac{1}{T} \int_0^T P(t) dt = \frac{1}{r} \cdot \frac{1}{T} \int_0^T v^2(t) dt$$

Instantaneous power in terms of **current**

$$P(t) = vi = rii = ri^2$$

Average power over period  $T$

$$P_{ave} = \frac{1}{T} \int_0^T P(t) dt = r \cdot \frac{1}{T} \int_0^T i^2(t) dt$$


Therefore, RMS values are defined as

$$V_{(rms)} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$


$$I_{(rms)} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$
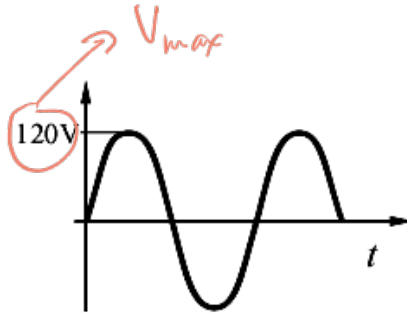
# Root-Mean-Square (RMS) Value


$$V_{(rms)} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$
$$I_{(rms)} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$



$$V_{rms} = \frac{120}{\sqrt{2}} V$$

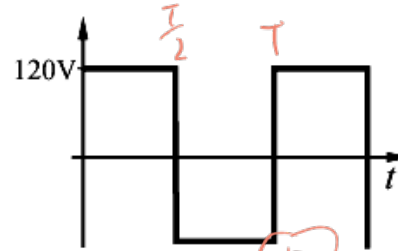

$$V_{rms} = 120 V$$

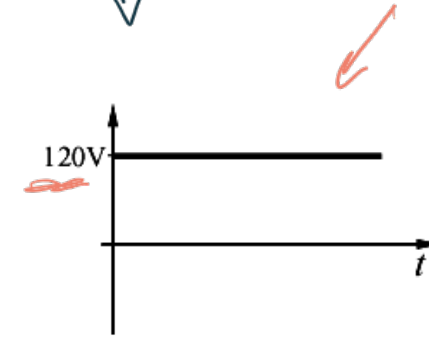


$$V_{rms} = 120 V$$

$$\sqrt{\frac{1}{T} \int_0^T 120^2 dt} = 120V$$
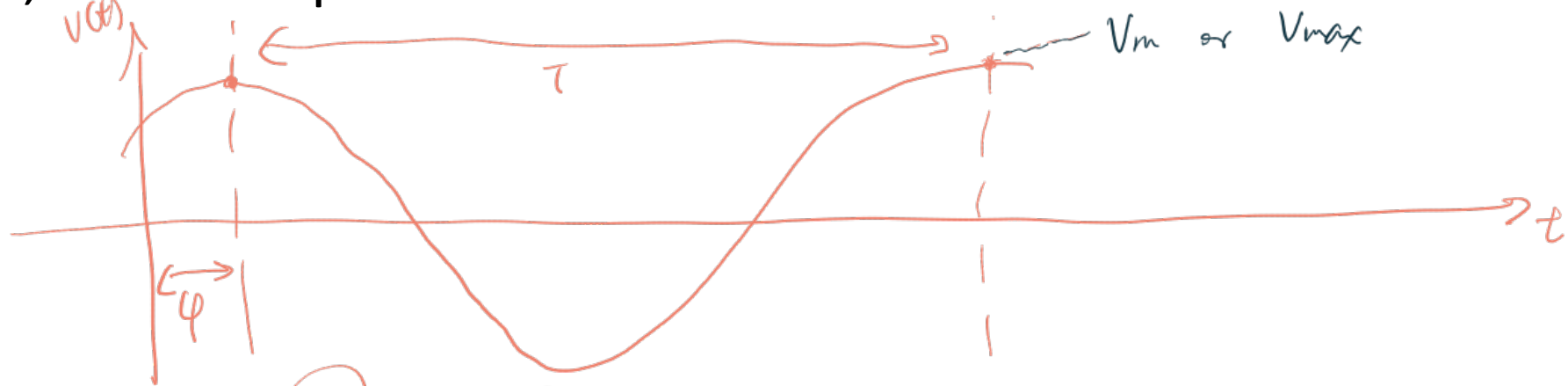
# Root-Mean-Square (RMS) Value

Therefore, we can represent a sinusoidal waveform as:



$$v(t) = V_m \cos(\omega t + \varphi) = \sqrt{2} V_{rms} \cos(\omega t + \varphi)$$

→ Period:  $T$  [s]

Frequency:  $f = \frac{1}{T}$  [Hz]

Angular frequency:  $\omega = 2\pi f$  [rad/s]

Phase:  $\varphi$  [rad]

Amplitude:  $V_m = \sqrt{2} V_{rms}$

# Phasor representation

## Euler's Identity

$$e^{j\omega t} = \cos(\omega t) + j \sin(\omega t)$$

- Only for steady-state  $\Rightarrow$  Amplitude + phase

- It is like an abbreviation:  $\rightarrow$  lower case to represent time-domain signal

$$v(t) = \sqrt{2}V_{rms} \cos(\omega t + \varphi)$$

$$= \sqrt{2}V_{rms} \text{Re}[e^{j(\omega t + \varphi)}]$$

$$= \sqrt{2}V_{rms} \text{Re}[e^{j\omega t} e^{j\varphi}]$$

$\rightarrow$  Always common in all sinusoidal signals

Upper case  $\rightarrow$

- Phasor notation:  $V = V_{rms} e^{j\varphi} = V_{rms} \angle \varphi$

$\rightarrow$  complex number

- Therefore, you can also express the phasor as  $V = V_{rms} \cos(\varphi) + jV_{rms} \sin(\varphi)$

# Phasor representation

- You can use phasor to express both current and voltage:

$$\underline{v(t)} = \sqrt{2} \cdot \underline{V_{rms}} \cos(\omega t + \varphi_v)$$

$$\underline{i(t)} = \sqrt{2} \cdot \underline{I_{rms}} \cos(\omega t + \varphi_i)$$

$$\tilde{V} = V_{rms} \angle \varphi_v$$
$$\tilde{I} = I_{rms} \angle \varphi_i$$

What is the advantage  
of using phasors?


- ① Phasor algebra
- ② Visualization

# Advantage of phasor analysis

| Linear Passive Elements                                                                           | Complex Impedance                                                                                              |
|---------------------------------------------------------------------------------------------------|----------------------------------------------------------------------------------------------------------------|
|  $R$             | $Z = \underline{R}$ ← Resistance                                                                               |
|  $\underline{L}$ | $Z = \underline{j\omega L} = (\omega L) \angle 90^\circ = jX_L$ ← Reactance                                    |
|  $C$             | $Z = \underline{\frac{1}{j\omega C}} = \left( \frac{1}{\omega C} \right) \angle -90^\circ = \underline{-jX_C}$ |

$$Z = \frac{V}{I} = \frac{V_m \angle \theta_v}{I_m \angle \theta_i} = \frac{V_m}{I_m} \angle \theta_v - \theta_i = \underline{Z_m \angle \theta_z}$$

RL Circuit

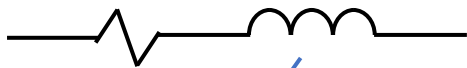


$$Z = R + jX, \quad |Z| = \sqrt{R^2 + X^2}, \quad \theta_z = \arctan\left(\frac{X}{R}\right)$$

**(Note:  $Z$  is a complex number but not a phasor)**

# Qualitative Phasor Diagrams


Use phasors (vectors) to represent voltage and/or current equations (relationship)

Consider **RL Circuit**

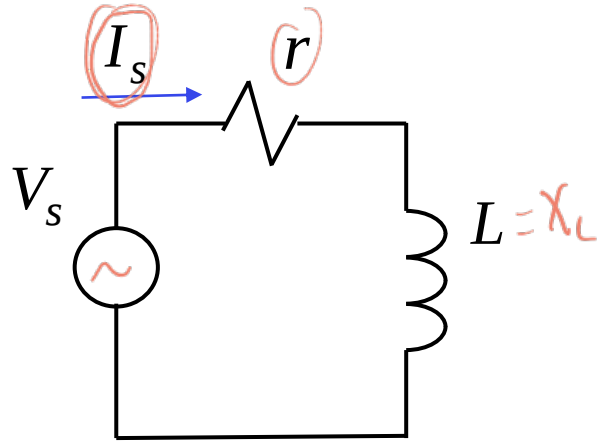

$$\underline{V_s} = \underline{rI_s} + \underline{j\omega LI_s} = \underline{rI_s} + \underline{jX_L I_s}$$



*perpendicular*

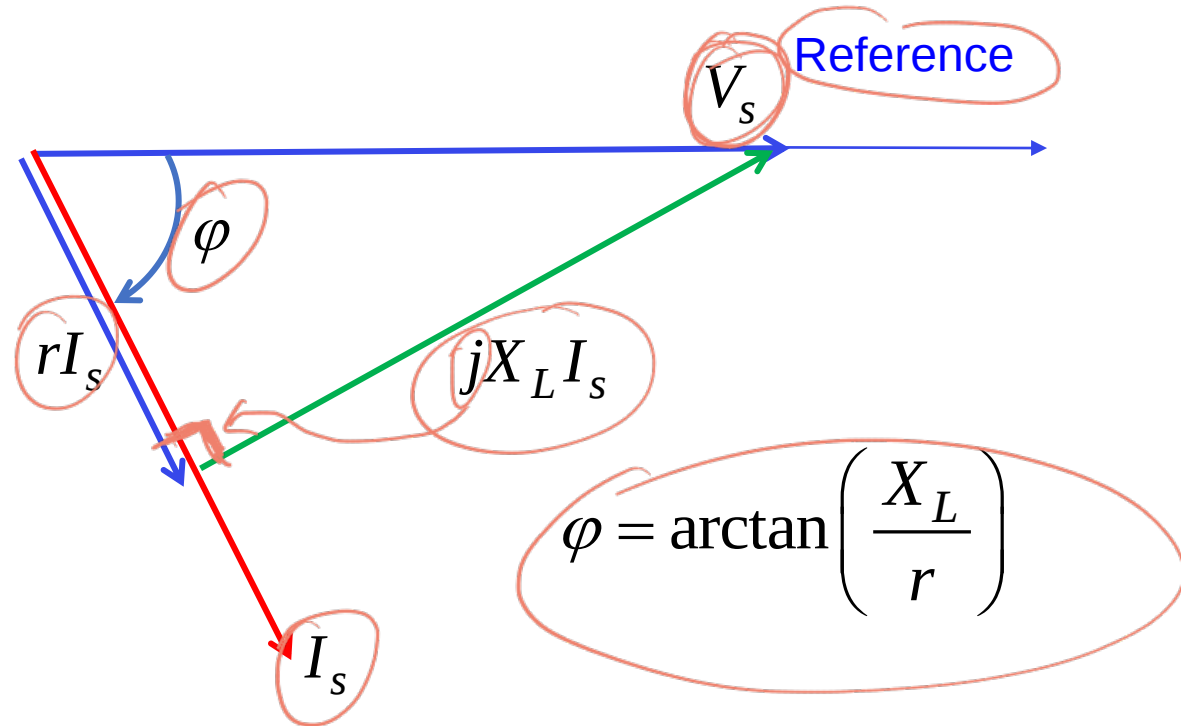
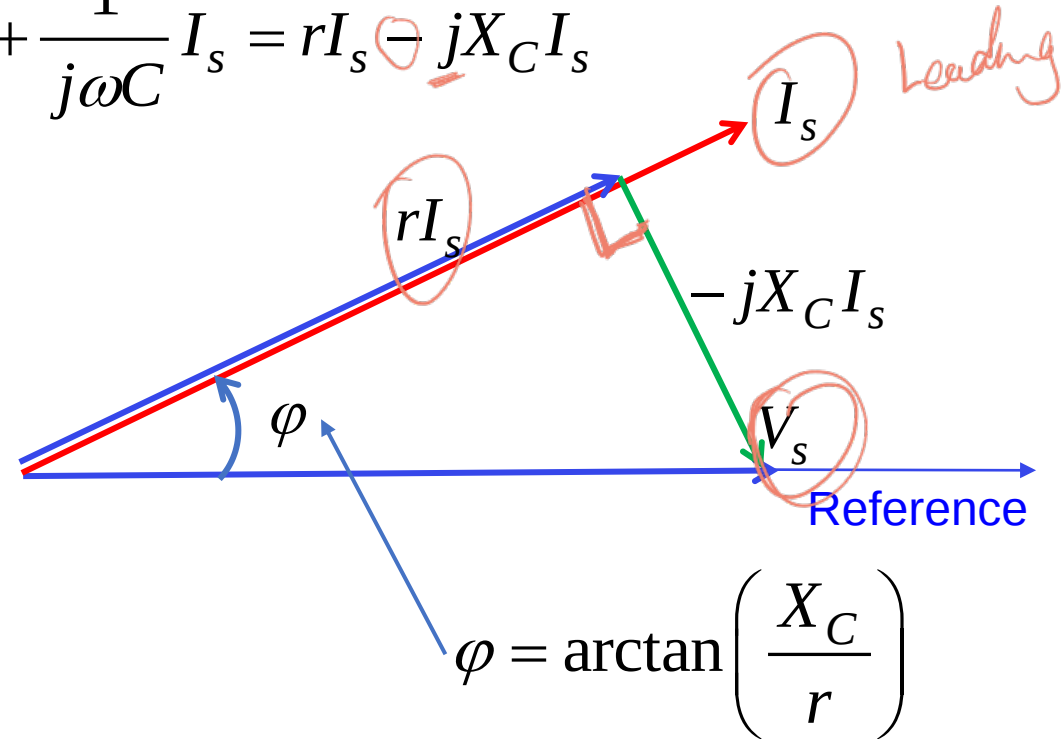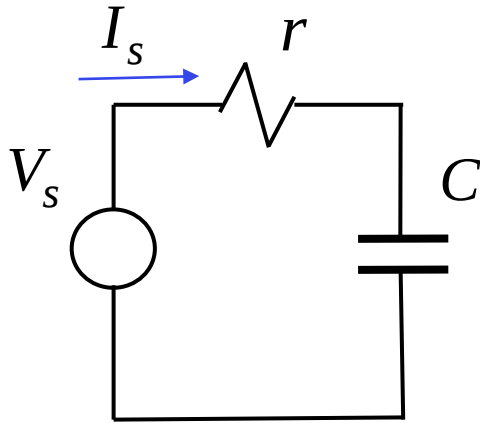
# Qualitative Phasor Diagrams

Use phasors (vectors) to represent voltage and/or current equations (relationship)


Consider **RC Circuit**  $V_s = rI_s + \frac{1}{j\omega C} I_s = rI_s - jX_C I_s$



# Qualitative Phasor Diagram Problem


Use phasors (vectors) to represent voltage and/or current equations (relationship)

Consider RLC Circuit

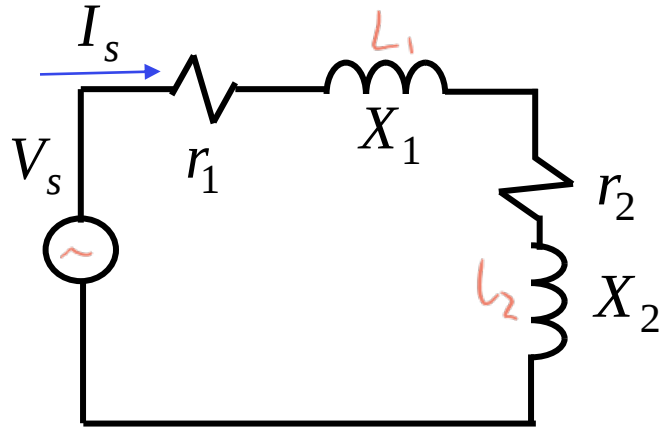

$$X_1 = \omega L_1, \quad X_2 = \omega L_2$$

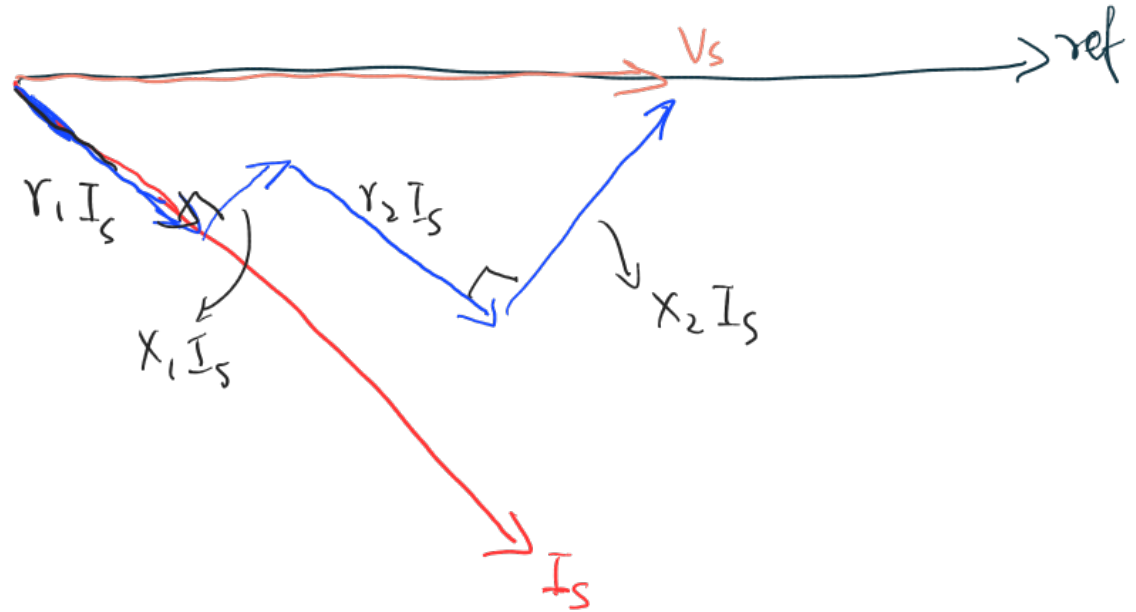
$$V_s = r_1 I_s + jX_1 I_s + r_2 I_s + jX_2 I_s \quad (\text{KVL})$$





# Qualitative Phasor Diagram Problem

Use phasors (vectors) to represent voltage and/or current equations (relationship)

Consider RLC Circuit

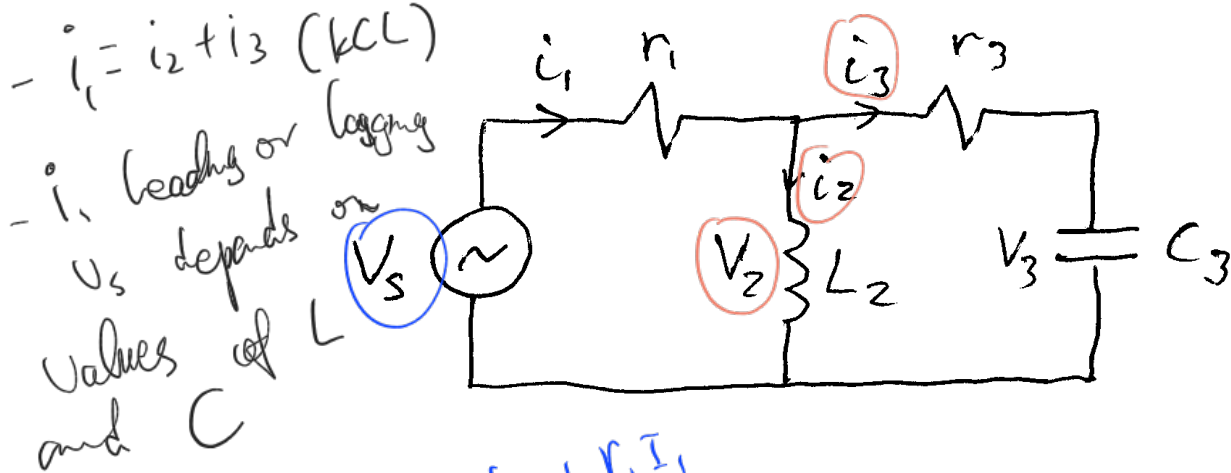

$$V_s = V_2 + r_1 I_1$$

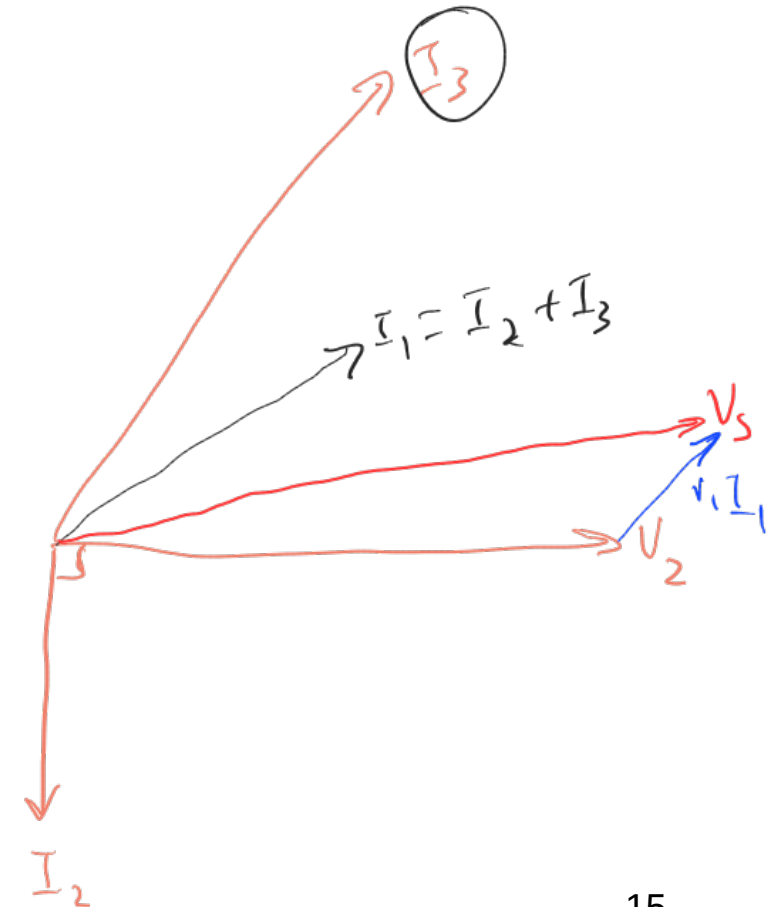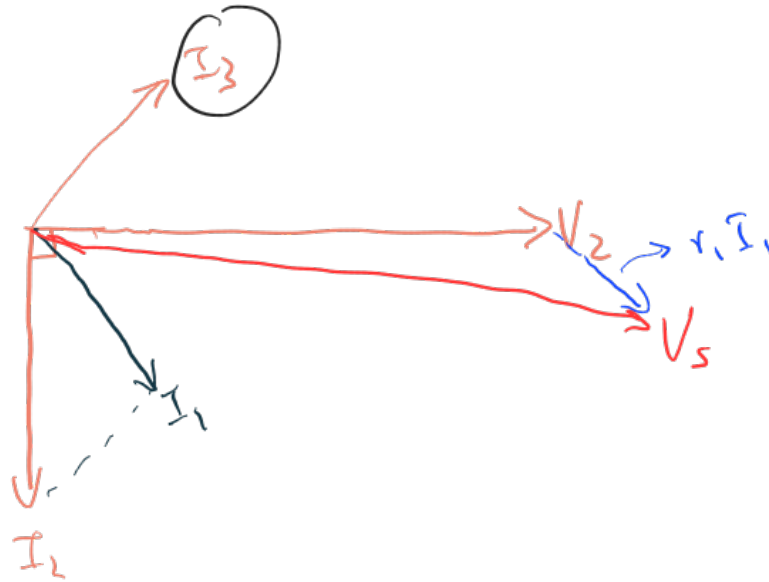


# Power in AC Circuits

Assume inductive load

$$\underline{v(t)} = \sqrt{2} \cdot V \cos(\omega t) \quad i(t) = \sqrt{2} \cdot I \cos(\omega t + \varphi)$$

*rms is dropped*

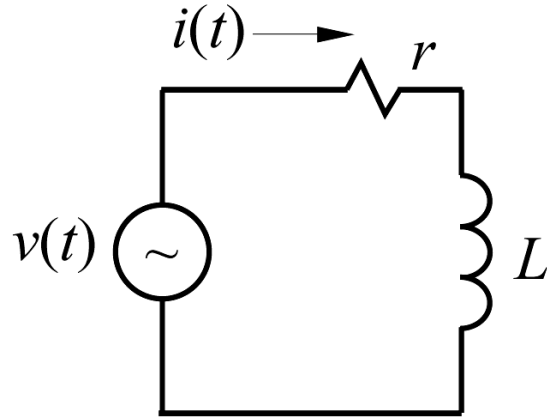

Instantaneous power is always voltage times current

$$p(t) = \underline{vi} = 2VI \cos(\omega t) \cos(\omega t + \varphi)$$

Recall

$$\cos \alpha \cos \beta = \frac{1}{2} (\cos(\alpha - \beta) + \cos(\alpha + \beta))$$


$$\underline{p(t)} = VI \cos(\varphi) + VI \cos(2\omega t + \varphi)$$

*Average  $\neq \phi$*

*Average power =  $\phi$*





# Power in AC Circuits

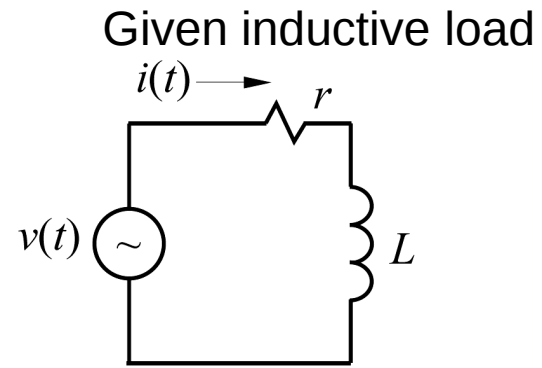


$$v(t) = \sqrt{2} \cdot V \cos(\omega t) \quad i(t) = \sqrt{2} \cdot I \cos(\omega t + \varphi)$$

Instantaneous power is always this
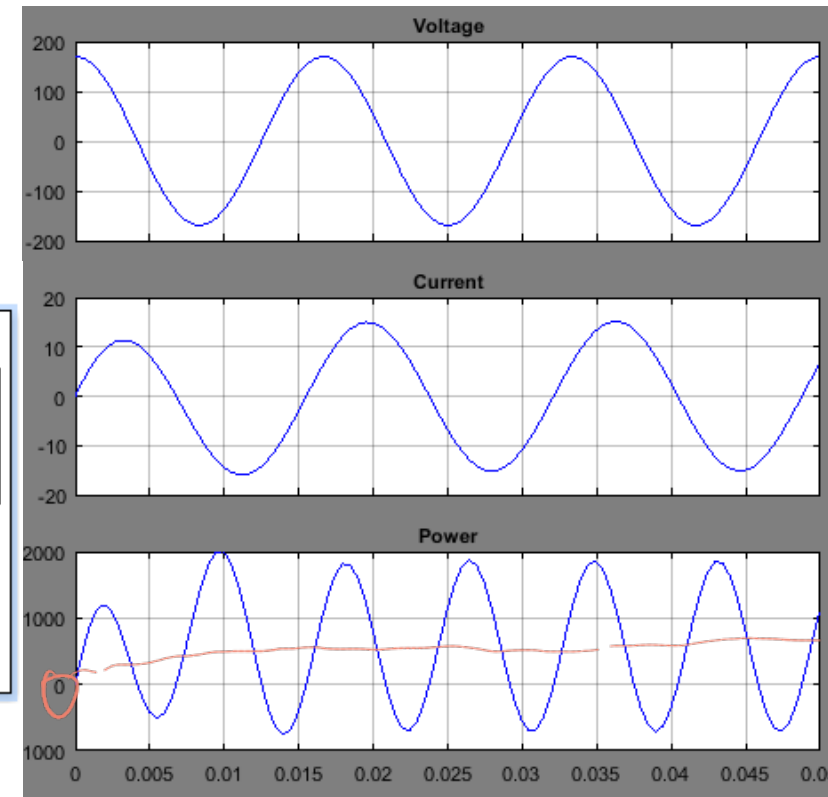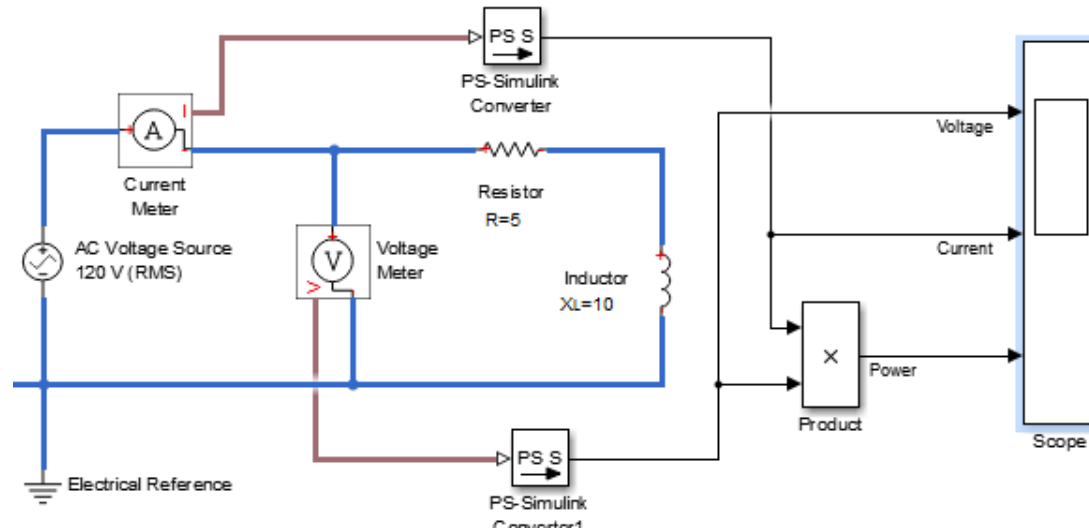
$$\begin{aligned} p(t) &= vi = 2VI \cos(\omega t) \cos(\omega t + \varphi) \\ &= VI \cos(\varphi) + VI \cos(2\omega t + \varphi) \end{aligned}$$





# Power in AC Circuits

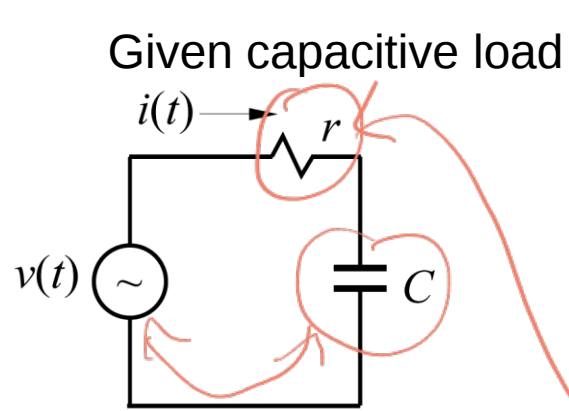

$$v(t) = \sqrt{2} \cdot V \cos(\omega t) \quad i(t) = \sqrt{2} \cdot I \cos(\omega t + \varphi)$$


Instantaneous power is always this
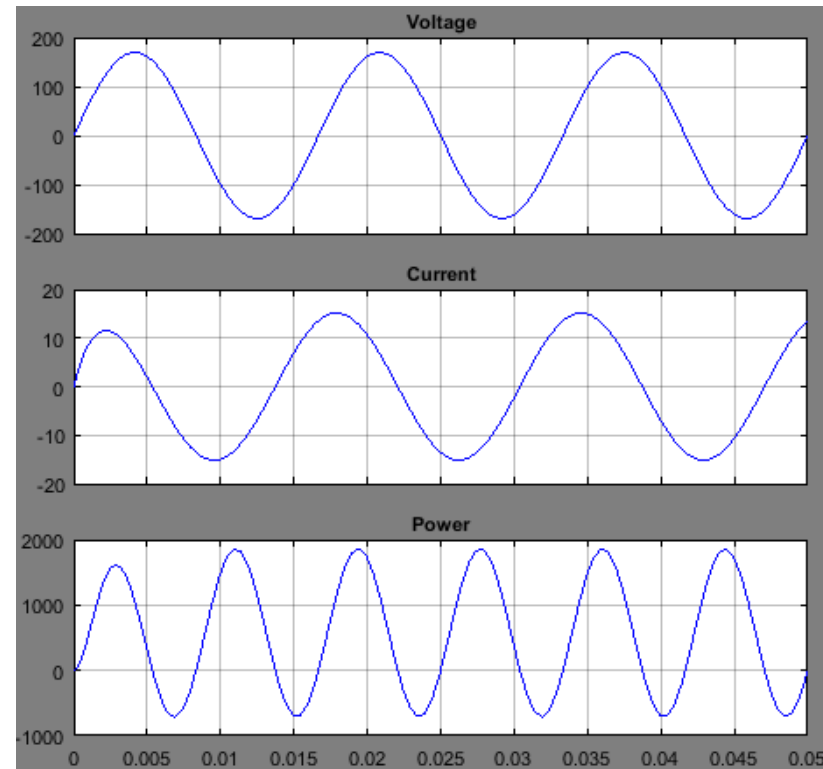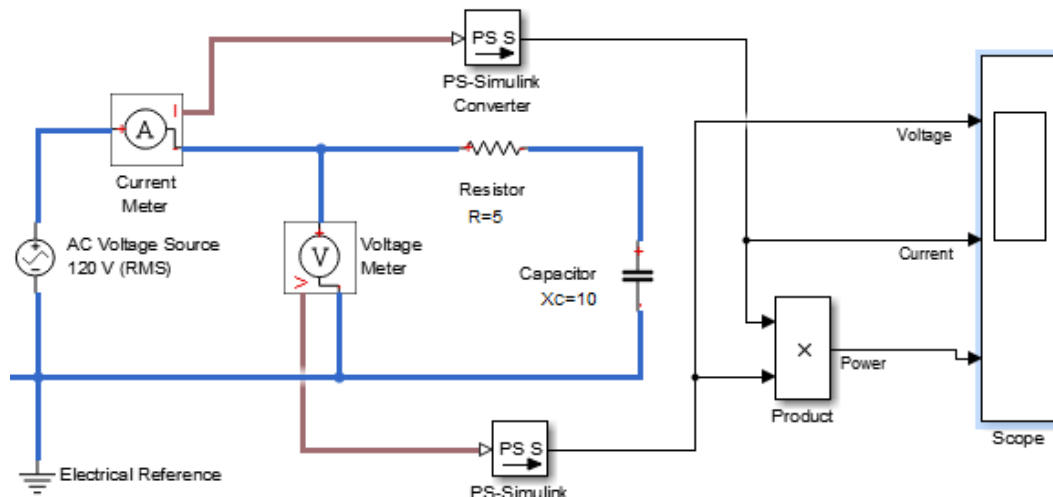
$$p(t) = vi = 2VI \cos(\omega t) \cos(\omega t + \varphi) \\ = \underbrace{VI \cos(\varphi)} + \underbrace{VI \cos(2\omega t + \varphi)}$$



# Power in AC Circuits

Given inductive load

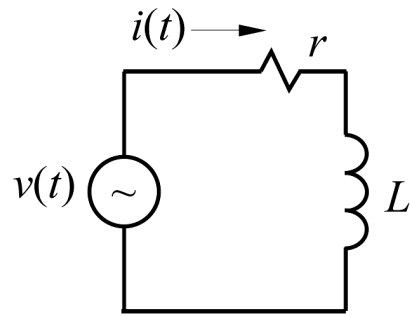

$$v(t) = \sqrt{2} \cdot V \cos(\omega t) \quad i(t) = \sqrt{2} \cdot I \cos(\omega t + \varphi)$$

Instantaneous power is always this

$$p(t) = vi = 2VI \cos(\omega t) \cos(\omega t + \varphi) \\ = VI \cos(\varphi) + VI \cos(2\omega t + \varphi)$$



Constant part –  
average power  
over cycle

Pulsating part -  
oscillating with  
double frequency


Note: Average  
power depends on  
 $V$ ,  $I$ , and  $\varphi$

Average power over cycle
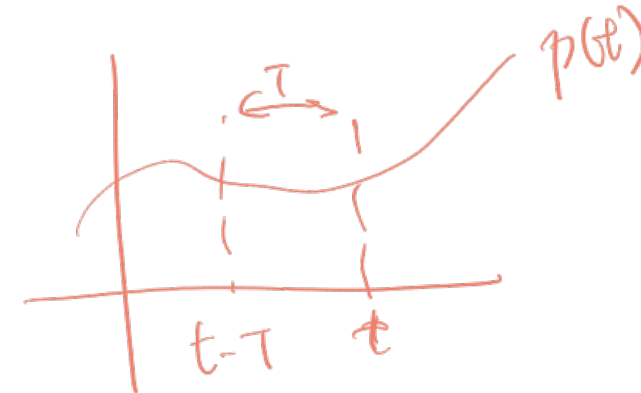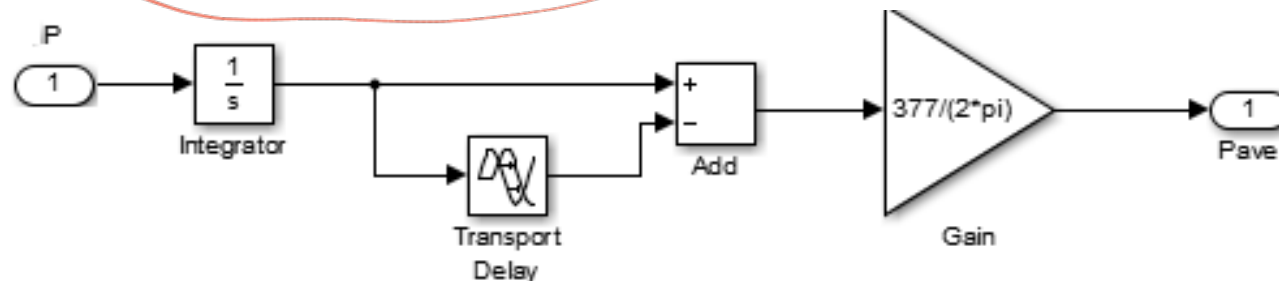
$$P = \frac{1}{T} \int_{t-T}^t p(t) d\tau$$



# Power in AC Circuits



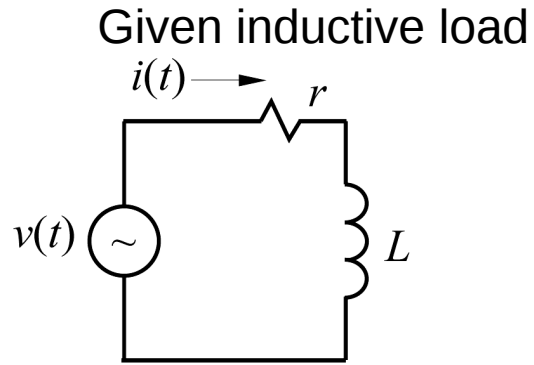


$$v(t) = \sqrt{2} \cdot V \cos(\omega t) \quad i(t) = \sqrt{2} \cdot I \cos(\omega t + \varphi)$$

Instantaneous power is always this

$$p(t) = vi = 2VI \cos(\omega t) \cos(\omega t + \varphi)$$
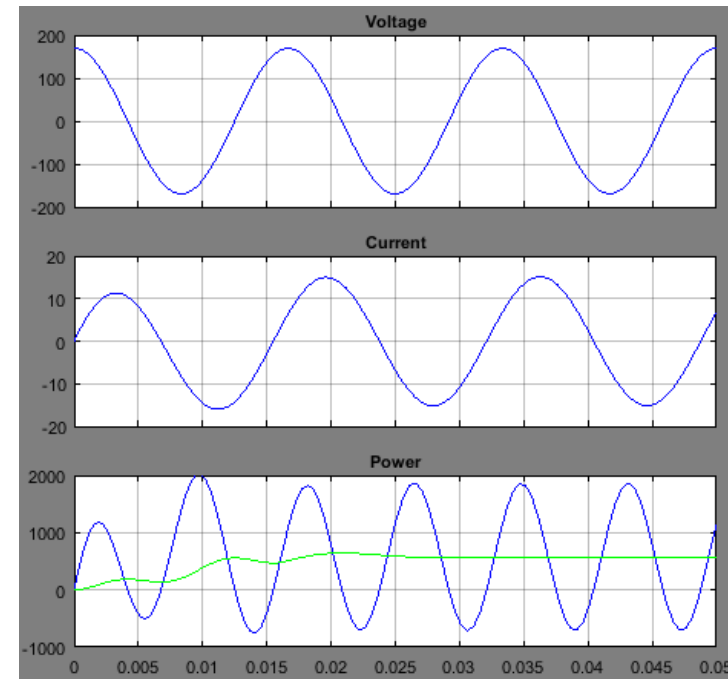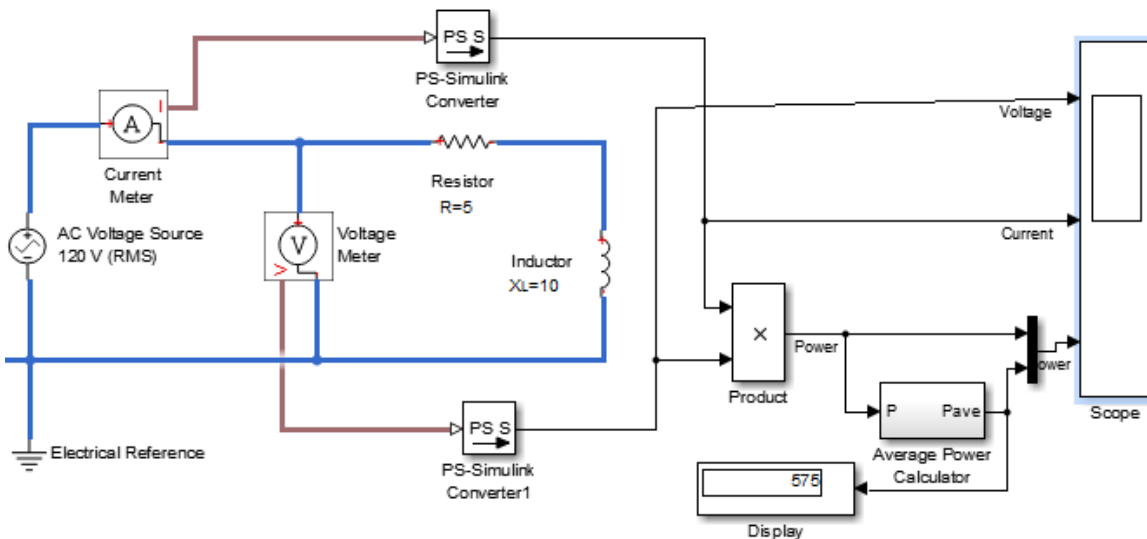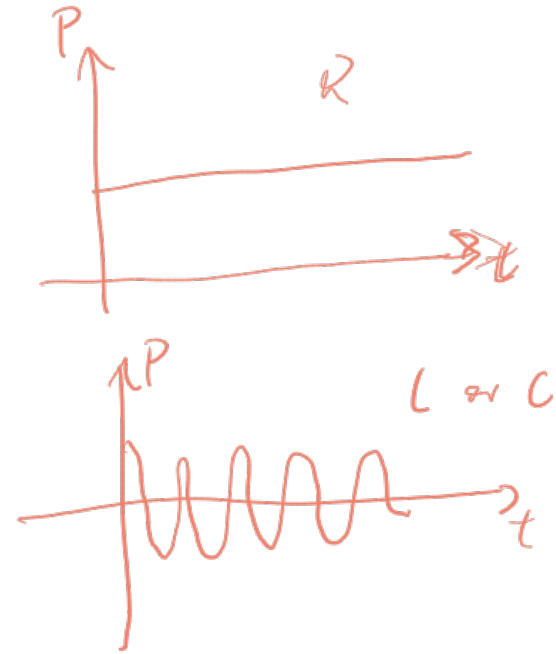
$$= \underbrace{VI \cos(\varphi)}_{\text{Constant part - average power over cycle}} + \underbrace{VI \cos(2\omega t + \varphi)}_{\text{Pulsating part - oscillating with double frequency}}$$



# Power in AC Circuits

trig identity  $\Rightarrow$

$$\begin{aligned}\cos(\alpha) \cos(\beta) &= \frac{1}{2} [\cos(\alpha + \beta) + \cos(\alpha - \beta)] \\ \sin(\alpha) \sin(\beta) &= \frac{1}{2} [\cos(\alpha - \beta) - \cos(\alpha + \beta)]\end{aligned}$$

14

Define general voltage and current expressions:

$$v(t) = \sqrt{2}V_{rms} \cos(\omega t + \theta)$$

$$i(t) = \sqrt{2}I_{rms} \cos(\omega t + \varphi)$$

Then instantaneous power is:

$$p(t) = V_{rms}I_{rms} [\cos(\theta - \varphi) + \cos(2\omega t + \theta + \varphi)]$$

$$\Rightarrow = V_{rms}I_{rms} \cos(\theta - \varphi) + V_{rms}I_{rms} \cos(2\omega t + \theta + \varphi)$$

$$= V_{rms}I_{rms} \cos(\theta - \varphi) + V_{rms}I_{rms} \cos(2(\omega t + \theta) - (\theta - \varphi))$$

$$= V_{rms}I_{rms} \cos(\theta - \varphi) + V_{rms}I_{rms} \cos(\theta - \varphi) \cos(2(\omega t + \theta)) + V_{rms}I_{rms} \sin(\theta - \varphi) \sin(2(\omega t + \theta))$$

$$= V_{rms}I_{rms} \cos(\theta - \varphi) \{1 + \cos[2(\omega t + \theta)]\} + V_{rms}I_{rms} \sin(\theta - \varphi) \sin[2(\omega t + \theta)]$$

# Power in AC Circuits

The instantaneous power is:

$$p(t) = \underbrace{V_{rms} I_{rms} \cos(\theta - \varphi) \{1 + \cos[2(\omega t + \varphi)]\}}_{\text{Non-zero average}} + \underbrace{V_{rms} I_{rms} \sin(\theta - \varphi) \sin[2(\omega t + \varphi)]}_{\text{zero average}}$$

Based on this expression, we define:

- **Active/real power:**  $P = V_{rms} I_{rms} \cos(\theta - \varphi)$  [W]
- **Power factor angle:**  $\theta - \varphi$ 
  - Leading (current leads voltage):  $\theta - \varphi < 0$
  - Lagging (current lags voltage):  $\theta - \varphi > 0$
- **Power factor:**  $\text{pf} = \cos(\theta - \varphi)$ 
  - Note that power factor is positive by convention
  - So if power factor angle is larger than  $90^\circ$ , then reverse current direction
- **Reactive power:**  $Q = V_{rms} I_{rms} \sin(\theta - \varphi)$  [var] (although [VAR] and [VAr] are also commonly used)
- **Complex power:**  $S = P + jQ = V_{rms} I_{rms} \cos(\theta - \varphi) + j V_{rms} I_{rms} \sin(\theta - \varphi)$  [VA] ↗ not Watt

# Power in AC Circuits

Based on this expression, we define:

- **Active/real power:**  $P = V_{rms} I_{rms} \cos(\theta - \varphi)$  [W]
- **Power factor angle:**  $\theta - \varphi$ 
  - Leading (current leads voltage):  $\theta - \varphi < 0$
  - Lagging (current lags voltage):  $\theta - \varphi > 0$
- **Power factor:**  $\text{pf} = \cos(\theta - \varphi)$ 
  - Note that power factor is positive by convention
  - So if power factor angle is larger than  $90^\circ$ , then reverse current direction
- **Reactive power:**  $Q = V_{rms} I_{rms} \sin(\theta - \varphi)$  [var] (although [VAR] and [VAr] are also commonly used)
- **Complex power:**  $S = P + jQ = V_{rms} I_{rms} \cos(\theta - \varphi) + jV_{rms} I_{rms} \sin(\theta - \varphi)$  [VA]
- **Apparent power:**  $|S| = \sqrt{P^2 + Q^2} = V_{rms} I_{rms}$  [VA]

↑  
magnitude of  $S$

# Power in AC Circuits

In phasor domain:

- $\underline{V} = V_{rms} \angle \theta$ ,  $\underline{I} = I_{rms} \angle \varphi$

- We can get the same complex power by defining:

$$\underline{S} = VI^* = VI \angle (\theta - \varphi)$$


**(note that the subscript *rms* is now dropped hereafter)**

$$P = \text{Re}(\underline{S}) = |\underline{S}| \cos(\theta - \varphi)$$

(this means that only the current component in phase with voltage produces real power)

$$Q = \text{Im}(\underline{S}) = |\underline{S}| \sin(\theta - \varphi)$$

- We have the famous power triangle:

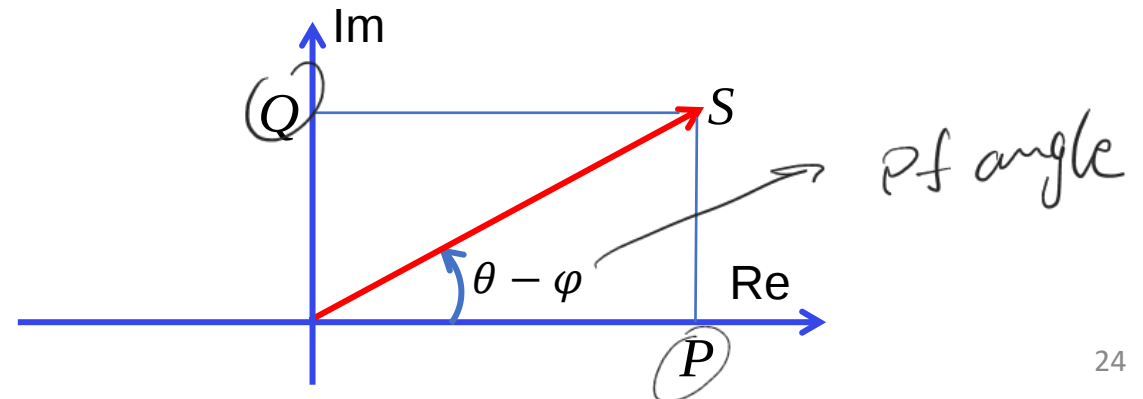


# Power in resistor, inductor, capacitor

| Component | Power                                                        | Comments                                                                                                  |
|-----------|--------------------------------------------------------------|-----------------------------------------------------------------------------------------------------------|
| Resistor  | $\frac{p(t) = VI\{1 + \cos[2(\omega t + \delta)]\}}{P = VI}$ | Absorbs positive real power, zero reactive power                                                          |
| Inductor  | $\frac{p(t) = VI \sin[2(\omega t + \delta)]}{Q = VI}$        | Absorbs zero real power, positive reactive power, lagging power factor                                    |
| Capacitor | $\frac{p(t) = -VI \sin[2(\omega t + \delta)]}{Q = -VI}$      | Absorbs zero real power, negative reactive power (delivers positive reactive power), leading power factor |

# What is reactive power?



- We know that reactive power does not contribute to useful work – why it is called power?
- In case of purely resistive loads, electrical energy is directly converted into useful work (e.g., light and heat), no intermediate electric or magnetic field is required in between
  - Hence no power is used to create these fields – total power is entirely active power
- In case of inductive or capacitive loads, electrical energy can't directly be converted into useful work (e.g., rotation of a motor)
  - This is because these loads require electric or magnetic field
  - The work going into creating the field is called reactive power
  - From efficiency point of view, reactive power is seen as power loss because it contributes to the creation of the field and does not contribute to driving the load

# What is reactive power?

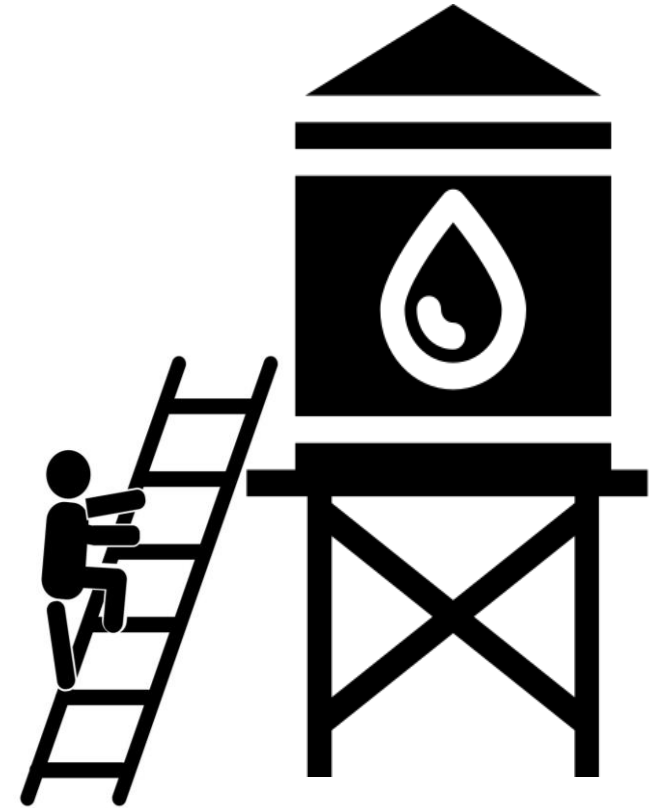
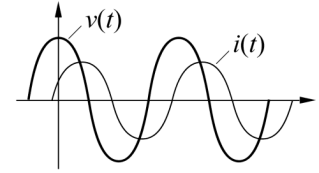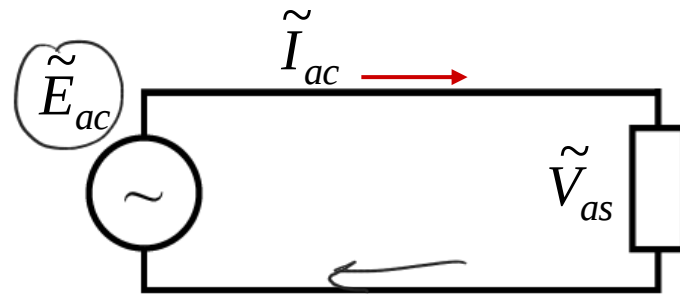
# Single vs. Three-Phase Systems

$$e_{ac}(t) = \sqrt{2} \cdot \underline{V_{rms}} \cos(\omega_e t)$$




$$P_{load} = V_{ac} I_{ac} \cos(\varphi)$$

Need to have 2 conductors!

1 unit of power  
2 cables/wires
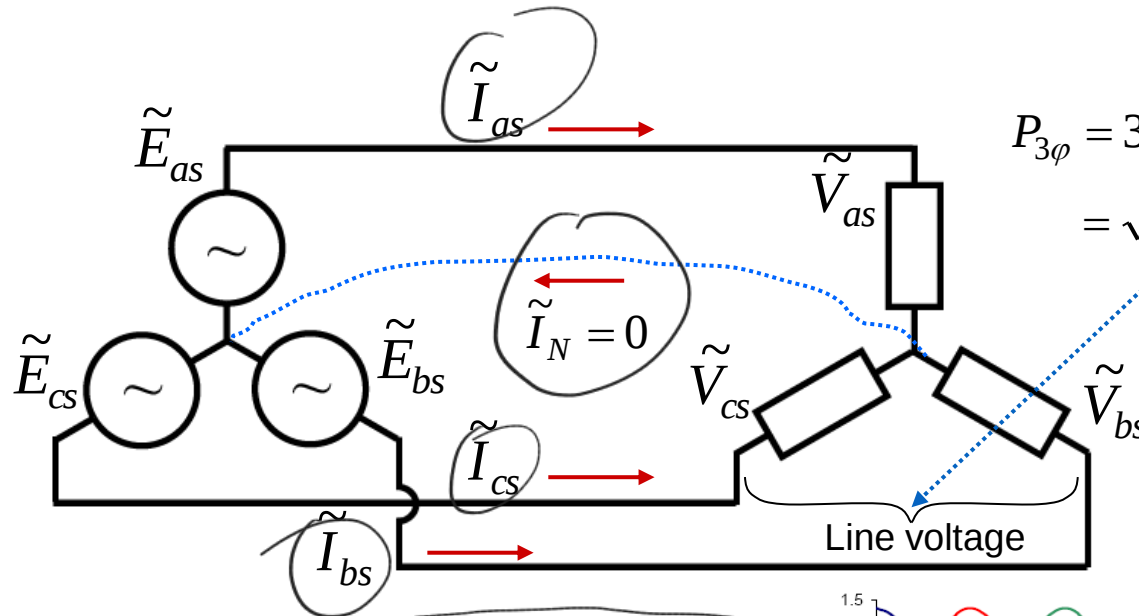
$$\begin{aligned} e_{as}(t) &= \sqrt{2} \cdot V_{rms} \cos(\omega_e t) \\ e_{bs}(t) &= \sqrt{2} \cdot V_{rms} \cos(\omega_e t - 120^\circ) \\ e_{cs}(t) &= \sqrt{2} \cdot V_{rms} \cos(\omega_e t + 120^\circ) \end{aligned}$$



$$\begin{aligned} P_{3\varphi} &= 3V_{as} I_{as} \cos(\varphi) \\ &= \sqrt{3} V_{line} I_{line} \cos(\varphi) \end{aligned}$$

$$V_{LL} = \sqrt{3} V_{LN}$$

Need to have 3 conductors, but can transmit 3-times the power!


3 units of power  
3 cables/wires

For balanced three phase system

$$e_{as} + e_{bs} + e_{cs} = 0$$

$$v_{as} + v_{bs} + v_{cs} = 0$$

$$i_{as} + i_{bs} + i_{cs} = 0$$

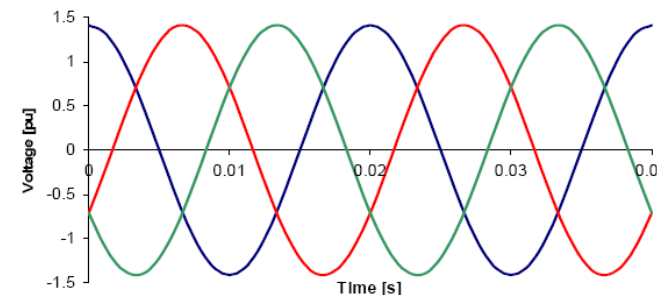

# Balanced Three-Phase ( $\phi$ ) Systems

- A balanced three-phase ( $\phi$ ) system has
  - Three voltage sources with equal magnitude, but with an angle shift of  $120^\circ$
  - Equal loads on each phase
  - Equal impedance on the lines connecting the generators to the loads
- Can transmit more power for same amount of wire (twice as much as single phase)
- Bulk power systems are almost exclusively  $3\phi$
- Single-phase is used primarily only in low voltage, low power settings, such as residential and some commercial

# Balanced Three-Phase ( $\phi$ ) Systems


- There are two ways to connect 3 $\phi$  systems
  - Wye (Y)
  - Delta ( $\Delta$ )



- Terminology:
  - Define voltage/current across/through device to be **phase** voltage/current
  - Define voltage/current across/through lines to be **line** voltage/current

line to line

# Wye (Y) - Connection

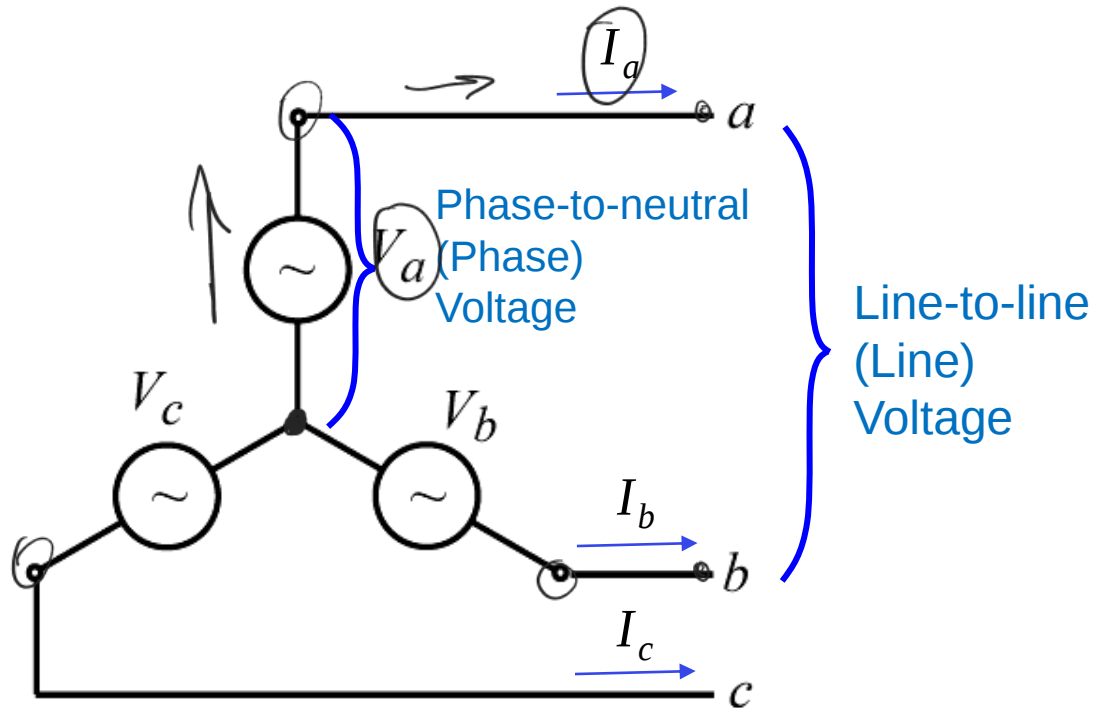

$$|V_{line}| = \sqrt{3} |V_{phase}|$$


Line-to-line (Line) voltage is larger

$$|I_{line}| = |I_{phase}|$$

Line Voltages

$$\underline{V_{ab}} = \underline{V_a} - \underline{V_b}$$
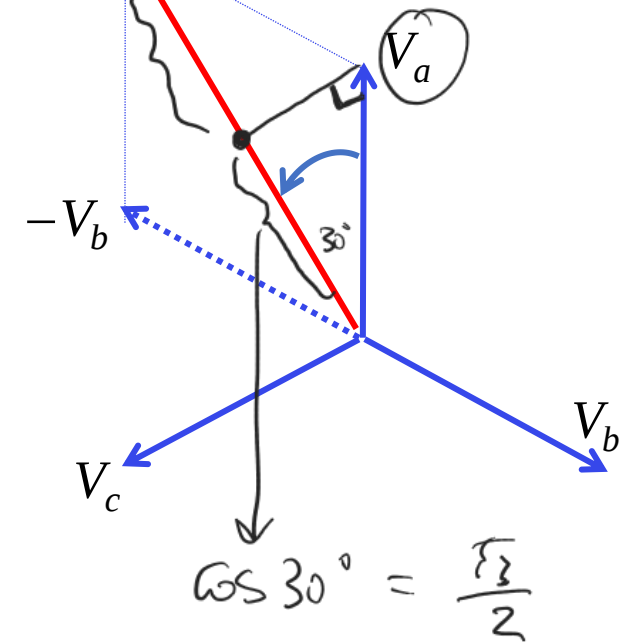
$$\underline{V_{ab}} = \sqrt{3} V_a \angle +30^\circ$$




# Wye (Y) - Connection

Line Voltages


$$V_{ab} = V_a - V_b$$

$$V_{bc} = V_b - V_c$$

$$V_{ca} = V_c - V_a$$

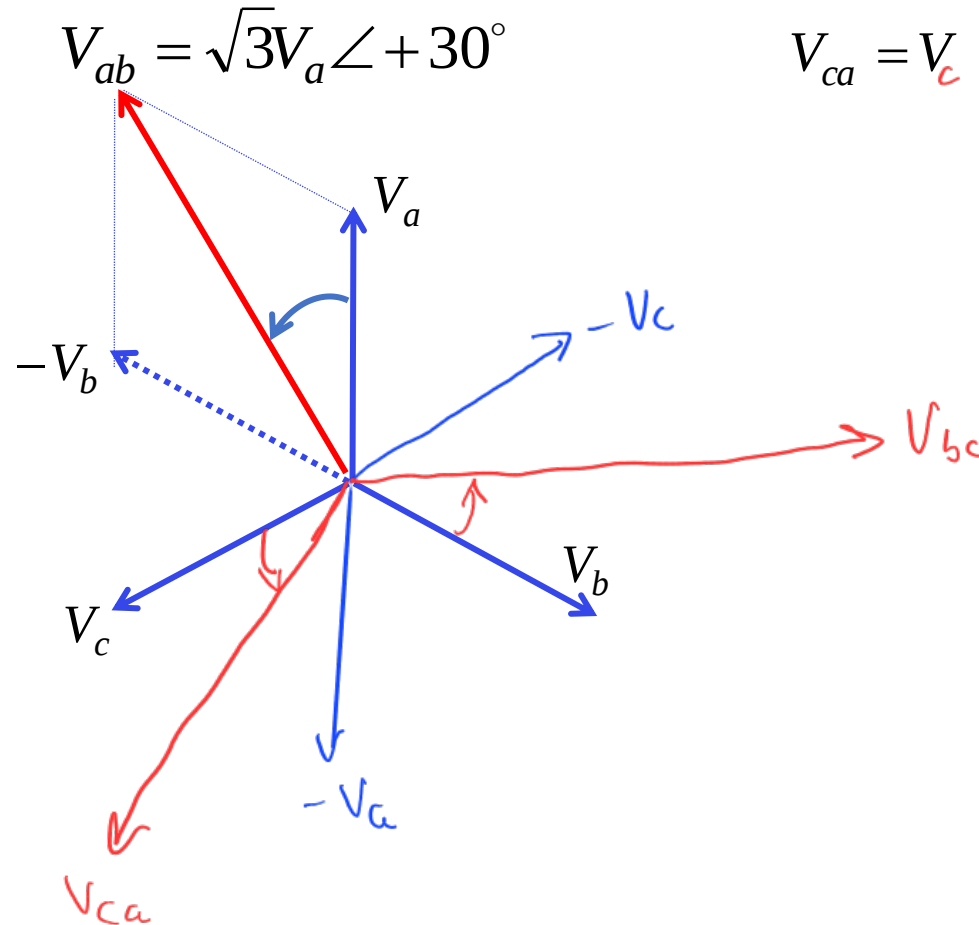


# Delta ( $\Delta$ ) - Connection

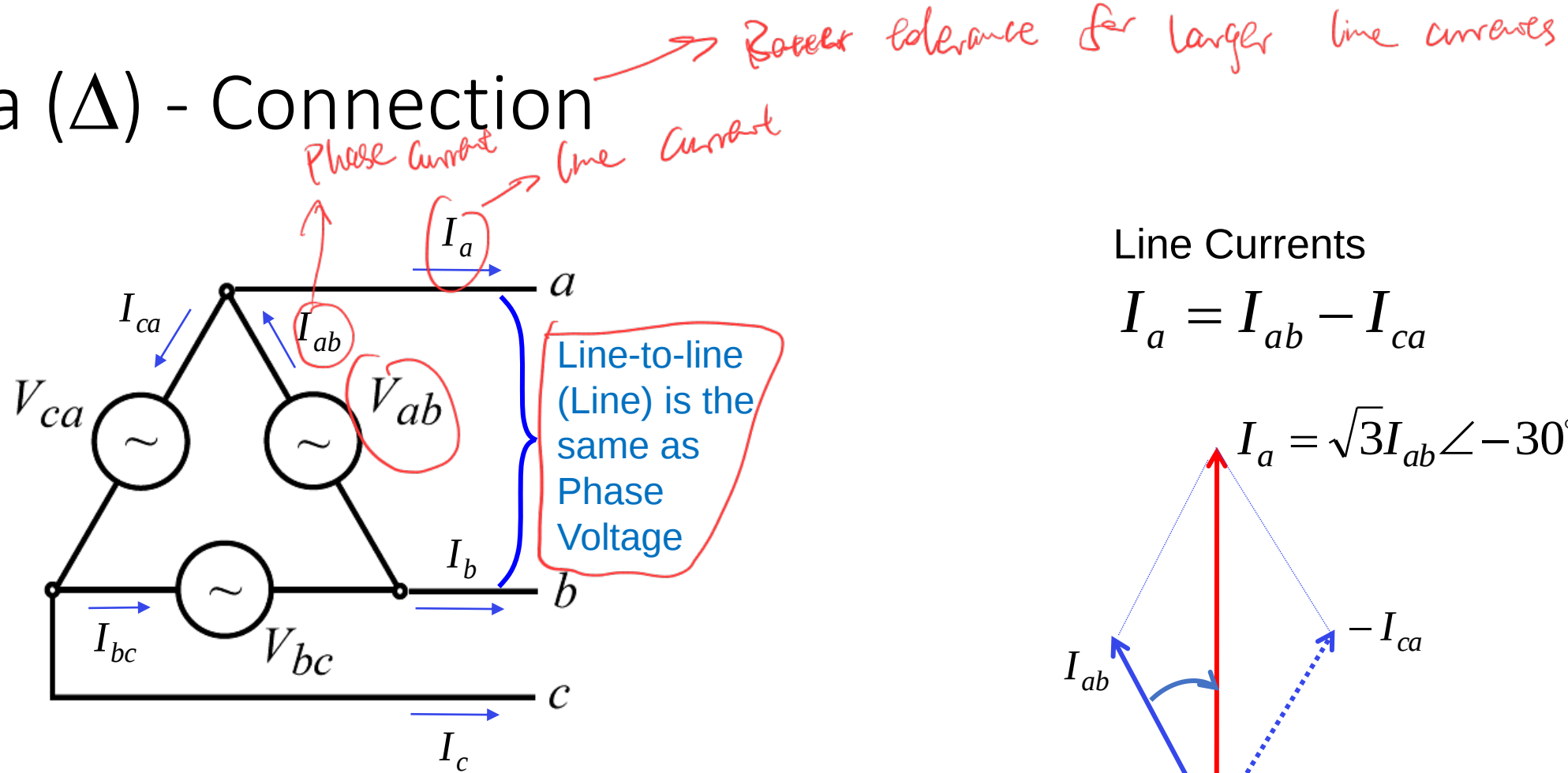

Line Currents

$$I_a = I_{ab} - I_{ca}$$

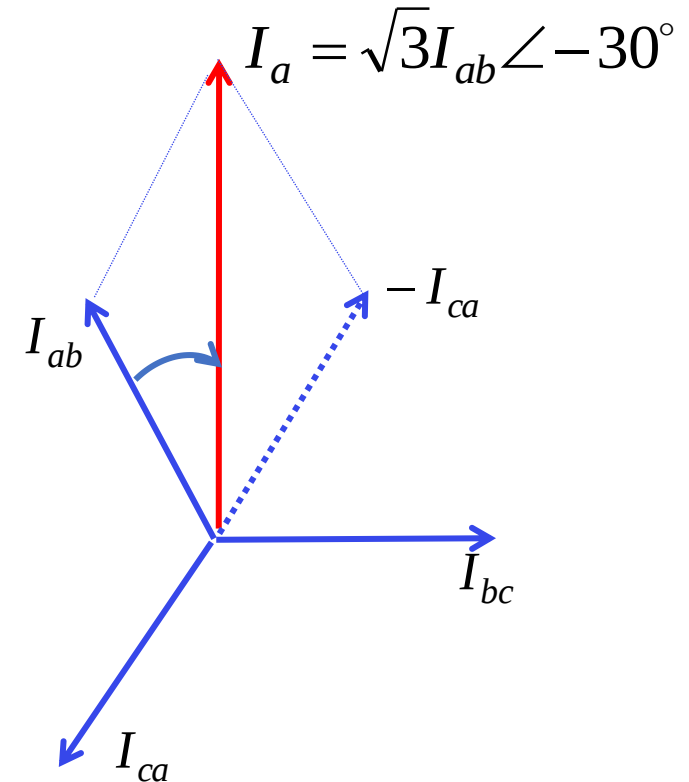

$$|I_{line}| = \sqrt{3}|I_{phase}| \quad \text{Line current is larger}$$

$$|V_{line}| = |V_{phase}|$$


# Delta ( $\Delta$ ) - Connection

Line Currents


$$I_a = I_{ab} - I_{ca}$$

$$I_b = I_{bc} - I_{ab}$$

$$I_c = I_{ca} - I_{bc}$$

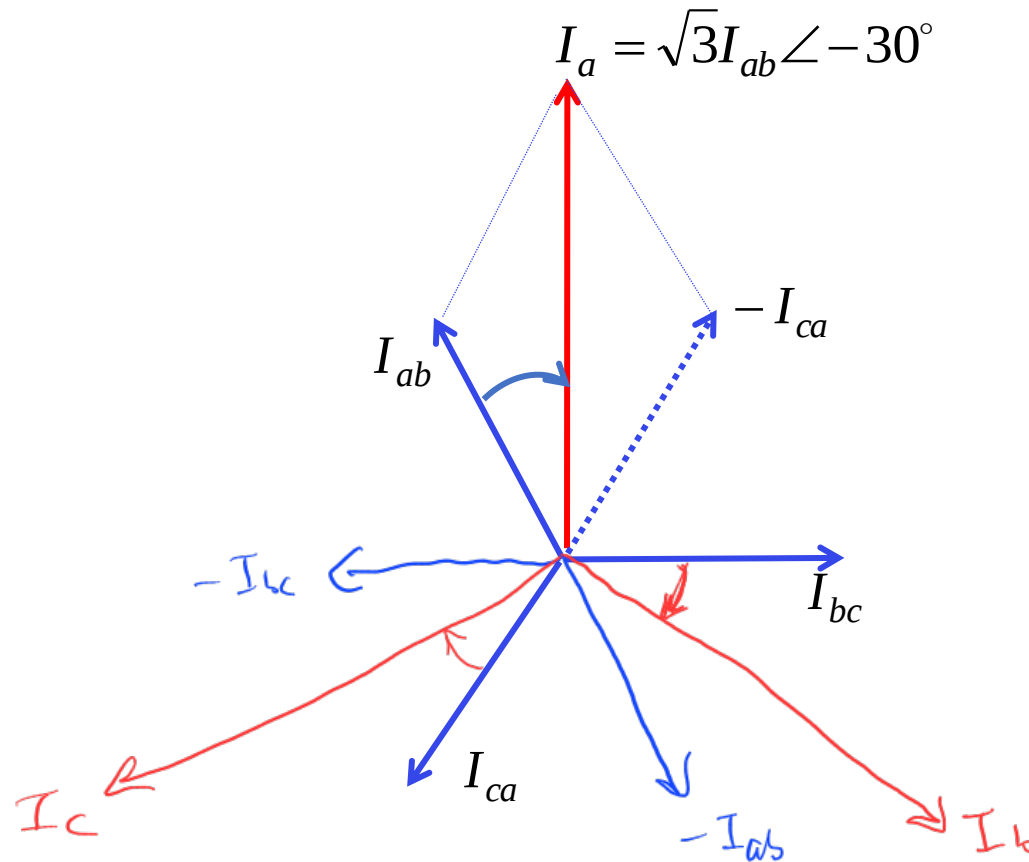

# Power in Three-Phase Systems

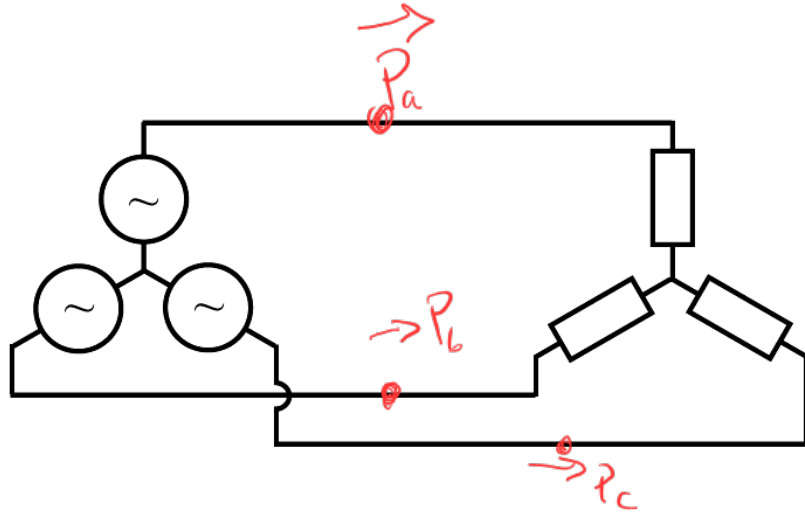

Instantaneous Power can always be calculated as

$$P_{3\phi}(t) = P_a + P_b + P_c$$
$$= \underline{i_a v_a} + \underline{i_b v_b} + \underline{i_c v_c}$$

For balanced system we have

$$v_a(t) = \sqrt{2}V_{ph} \cos(\omega t)$$

$$v_b(t) = \sqrt{2}V_{ph} \cos(\omega t - 120^\circ)$$

$$v_c(t) = \sqrt{2}V_{ph} \cos(\omega t + 120^\circ)$$

$$i_a(t) = \sqrt{2}I_{ph} \cos(\omega t - \varphi)$$

$$i_b(t) = \sqrt{2}I_{ph} \cos(\omega t - 120^\circ - \varphi)$$

$$i_c(t) = \sqrt{2}I_{ph} \cos(\omega t + 120^\circ - \varphi)$$

# Power in Three-Phase Systems

- In terms of phase quantities

$$P_{3\phi}(t) = 3P_{ph} = 3V_{ph} I_{ph} \cos(\varphi_{ph})$$

$$Q_{3\phi}(t) = 3Q_{ph} = 3V_{ph} I_{ph} \sin(\varphi_{ph})$$



Y - connection

$$I_{ph} = I_L, \quad V_{ph} = V_L / \sqrt{3}$$

$\Delta$  - connection


$$I_{ph} = I_L / \sqrt{3}, \quad V_{ph} = V_L$$

- In terms of line-to-line quantities

$$P_{3\phi} = \sqrt{3} V_L I_L \cos(\varphi_{ph})$$

$$Q_{3\phi} = \sqrt{3} V_L I_L \sin(\varphi_{ph})$$

# Power in Three-Phase Systems

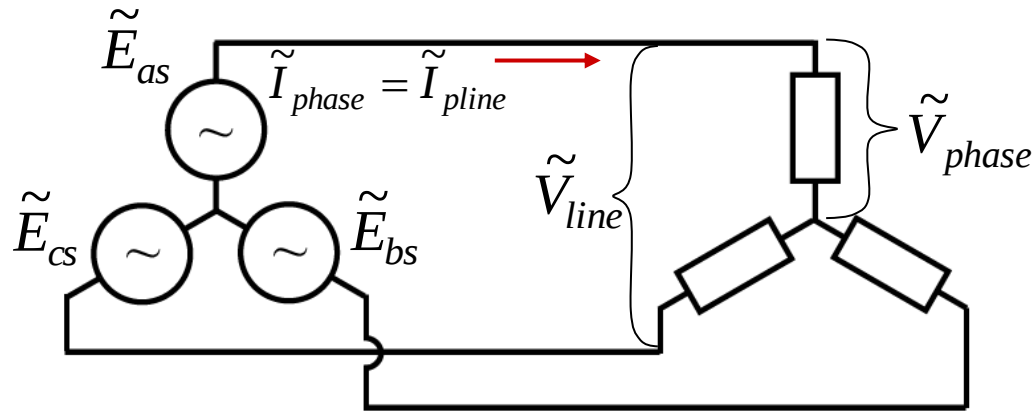

For balanced three phase system

$$V_{line} = \sqrt{3} \cdot V_{phase}$$

$$\rightarrow S_{3\phi} = 3V_{as}I_{as} = \sqrt{3}V_{line}I_{line}$$

$$\rightarrow P_{3\phi} = 3V_{as}I_{as} \cos(\varphi) \\ = \sqrt{3}V_{line}I_{line} \cos(\varphi)$$

$$\rightarrow Q_{3\phi} = 3V_{as}I_{as} \sin(\varphi) \\ = \sqrt{3}V_{line}I_{line} \sin(\varphi)$$

$$|S| = 3 V_{ph} I_{ph} = \sqrt{3} V_L I_L$$

# Looking ahead...

- **Module 1**, part 2