

ELEC 342

Electromechanical Energy Conversion and Transmission

2025-26 Winter Term 2

Lecture 5

January 20, 2026

Zhi Jin (Justin) Zhang


Course Logistics

- Lab 0 and Lab 1 materials posted
 - There will be a safety quiz during Lab 0
 - Pre-Labs: Bring them to actual lab so TA can check you off, but also include them in your lab report submission
 - Reminder: Lab 0 starts next week – go to your enrolled sections
- Assignment 2 will be posted this Thursday
 - Covers magnetic circuits (Module 1, Part 2)
- Quiz 1
 - Coverage: up to and including end of Module 1
 - Date: January 30 (Friday) at the beginning of the tutorial
 - Closed book and notes
 - Calculators allowed

Module 2: Transformers

 TX or TF

Ideal Transformer Impedance Transfer

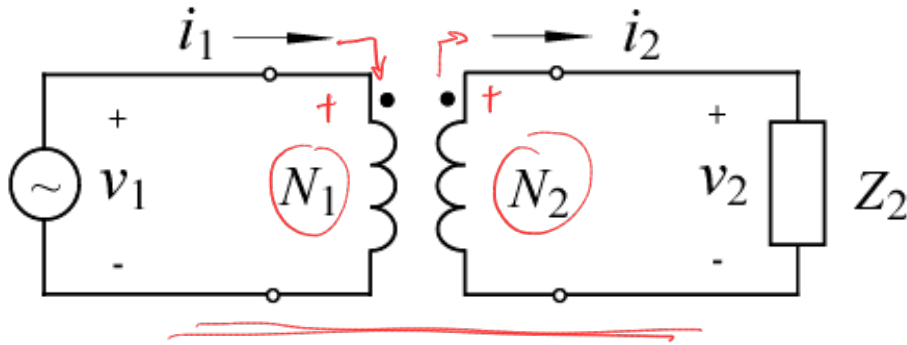

$$V_1 = \frac{N_1}{N_2} V_2 \quad I_1 = \frac{N_2}{N_1} I_2$$

$$Z_1 = Z_2 a^2 = Z_2'$$

Example 1: Consider ideal transformer loaded with impedance $Z_2 = 1 + j4 \Omega$.

Assume the turns ratio $a = 5$, and source voltage $V_1 = 120V(\text{rms}) \rightarrow 120 \angle 0^\circ$

1) Determine secondary current; 2) Determine primary current

$$1) \quad I_2 = \frac{V_2}{Z_2} = \frac{V_1}{a \cdot Z_2} = \frac{120}{5(1 + j4)} = 1.412 - j5.647 \text{ A (rms)}$$

$$2) \quad I_1 = \frac{I_2}{a} = 0.28 - j1.13 \text{ A (rms)}$$

$$I_1 = \frac{V_1}{a^2 \cdot Z_2} = \frac{120}{25 + j100} = 0.28 - j1.13 \text{ A (rms)}$$

Ideal Transformer Example 2

Consider a 100W audio (voltage) amplifier designed to work with 4Ω speaker. Assume you have only 8Ω speaker


- 1) Determine the output power
- 2) Determine the turns-ratio for appropriate matching impedance transformer

Assume the amplifier is voltage-source output

$$P = i \cdot V = \frac{V^2}{R}$$



$$V = \sqrt{P \cdot R} = \sqrt{400} = 20V$$
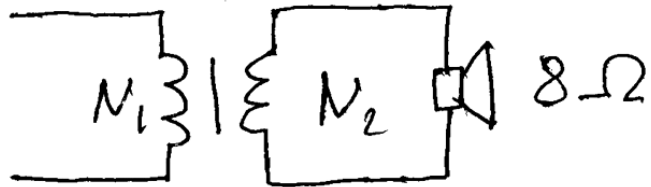
$$P = \frac{V^2}{R} = \frac{400}{8} = 50W$$




$$R_2' = R_2 \cdot a^2 = 4\Omega$$
$$a^2 = \frac{4}{8} = \frac{1}{2} \quad ; \quad a = \frac{1}{\sqrt{2}}$$
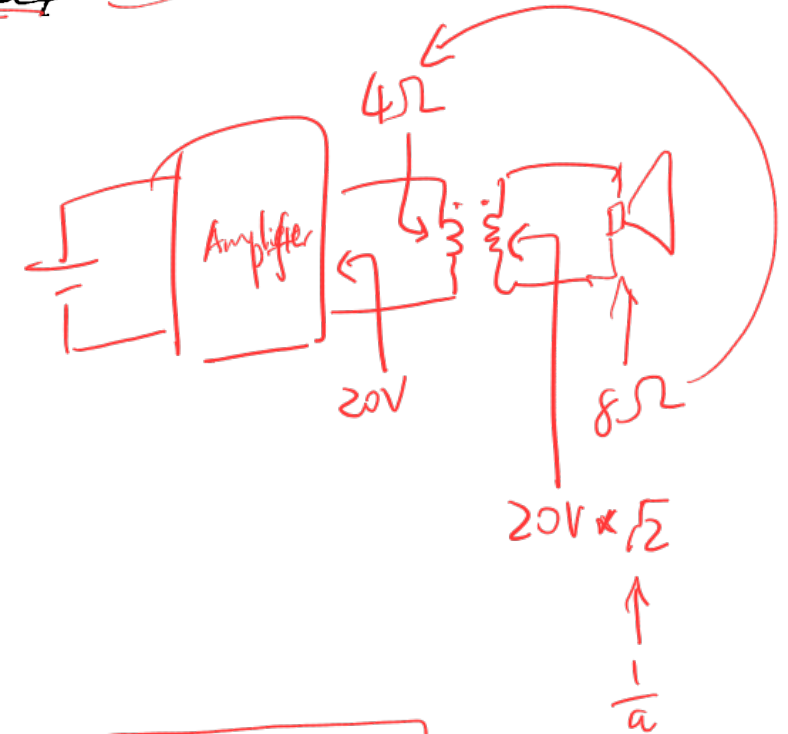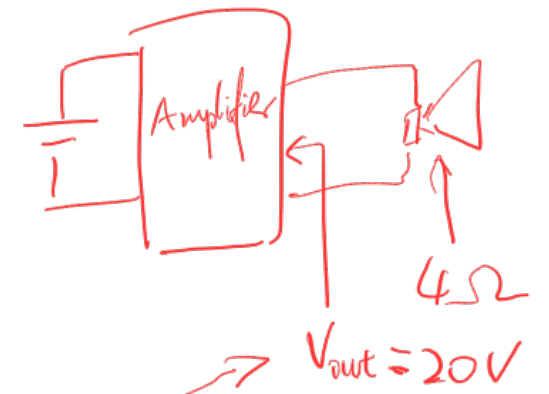
$$N_1 = 100 \text{ turns} \quad N_2 = 141 \text{ turns}$$



Non-Ideal (Practical) Transformer

$$R_m \neq \phi$$

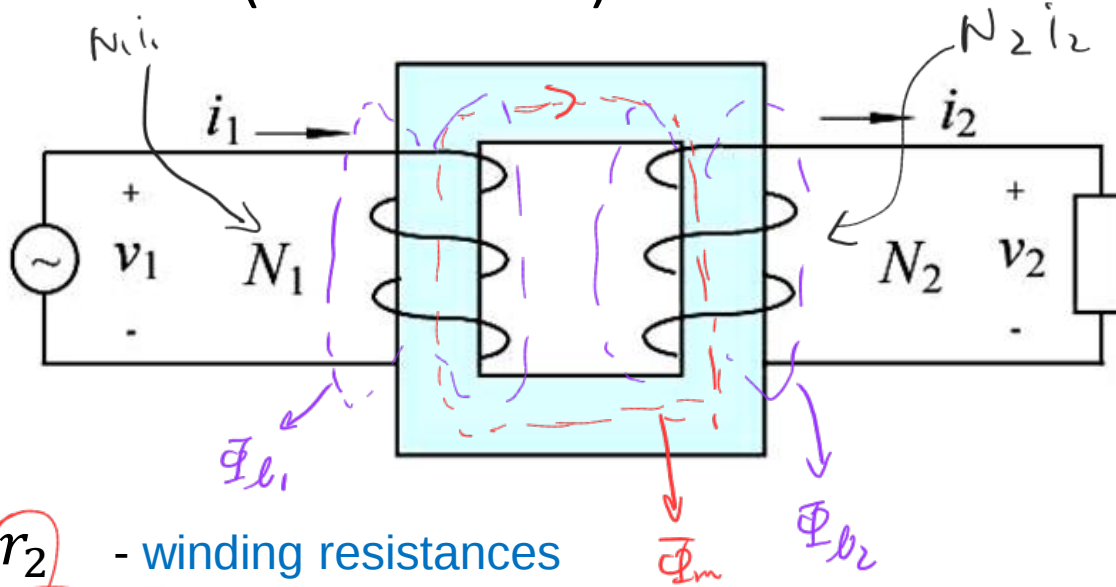


r_1, r_2 - winding resistances

Equivalent Magnetic Circuit:

Φ_m - mutual or magnetizing flux
(goes inside the core and links both windings)

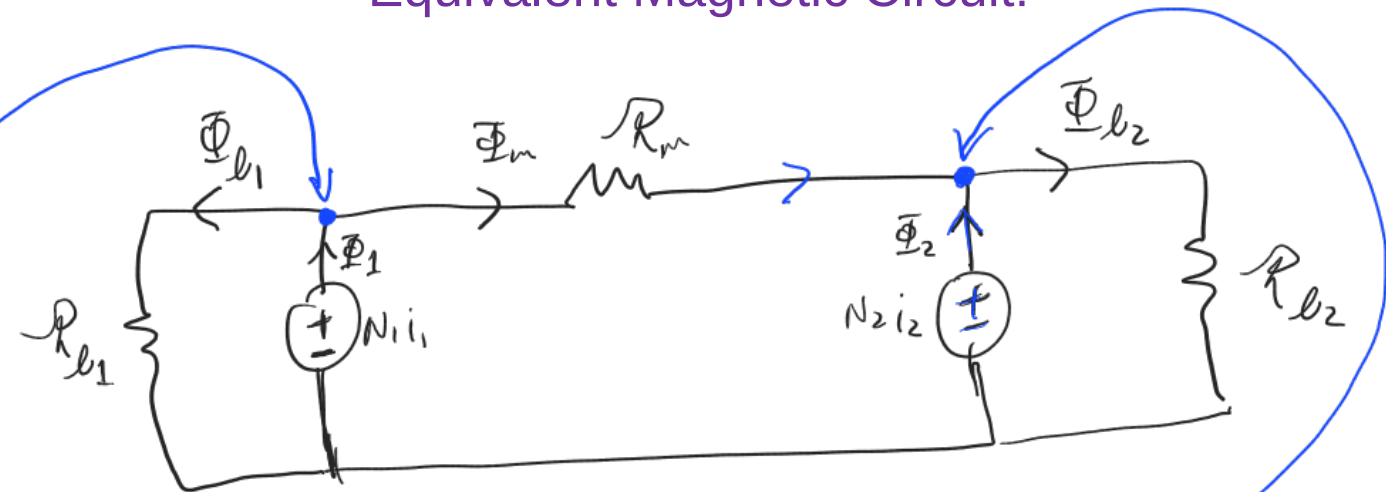
Φ_{l1}, Φ_{l2} - flux leakage (goes in the air and links only one winding)



$$\Phi_1 = \Phi_m + \Phi_{l1}$$

$$\Phi_2 = -\Phi_m + \Phi_{l2}$$

Non-Ideal (Practical) Transformer

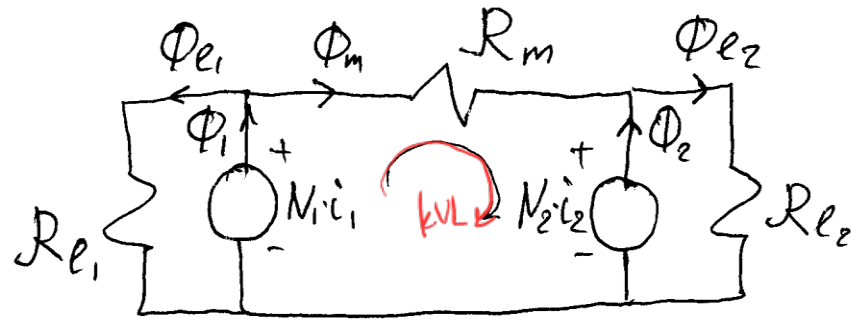

Consider Fluxes

$$\Rightarrow \Phi_1 = \Phi_{l1} + \Phi_m = \frac{N_1 i_1}{\mathcal{R}_{l1}} + \frac{N_1 i_1 - N_2 i_2}{\mathcal{R}_m}$$

$$\Rightarrow \Phi_2 = \Phi_{l2} - \Phi_m = \frac{N_2 i_2}{\mathcal{R}_{l2}} - \frac{N_1 i_1 - N_2 i_2}{\mathcal{R}_m}$$

Consider Flux Linkages

$$\lambda_1 = N_1 \Phi_1 = \frac{N_1^2}{\mathcal{R}_{l1}} i_1 + \frac{N_1^2}{\mathcal{R}_m} i_1 - \frac{N_1 N_2}{\mathcal{R}_m} i_2$$

Contribution to λ_1 by i_2

$$= L_{l1} i_1 + L_{m1} i_1 - L_{m12} i_2$$

Recall inductance

$$L = \frac{N^2}{\mathcal{R}}$$

$$\lambda_2 = N_2 \Phi_2 = \frac{N_2^2}{\mathcal{R}_{l2}} i_2 + \frac{N_2^2}{\mathcal{R}_m} i_2 - \frac{N_2 N_1}{\mathcal{R}_m} i_1$$

Contribution to λ_2 by i_1

$$= L_{l2} i_2 + L_{m2} i_2 - L_{m21} i_1$$

(leakage)

$$L_{l1} = \frac{N_1^2}{\mathcal{R}_{l1}} \quad L_{l2} = \frac{N_2^2}{\mathcal{R}_{l2}}$$

(core inductance)

$$L_{m1} = \frac{N_1^2}{\mathcal{R}_m} \quad L_{m2} = \frac{N_2^2}{\mathcal{R}_m}$$

$$L_{m12} = L_{m21} = \frac{N_1 N_2}{\mathcal{R}_m}$$


mutual inductance

T – Equivalent Circuit for Practical Transformer


Define reactance $X = L\omega$, $\left[H \frac{\text{rad}}{\text{sec}} = \Omega \right]$

$$\begin{aligned} X_{l1} &= L_{l1}\omega \\ X_{l2} &= L_{l2}\omega \end{aligned} \quad \left. \vphantom{\begin{aligned} X_{l1} &= L_{l1}\omega \\ X_{l2} &= L_{l2}\omega \end{aligned}} \right\} \text{leakage inductance}$$

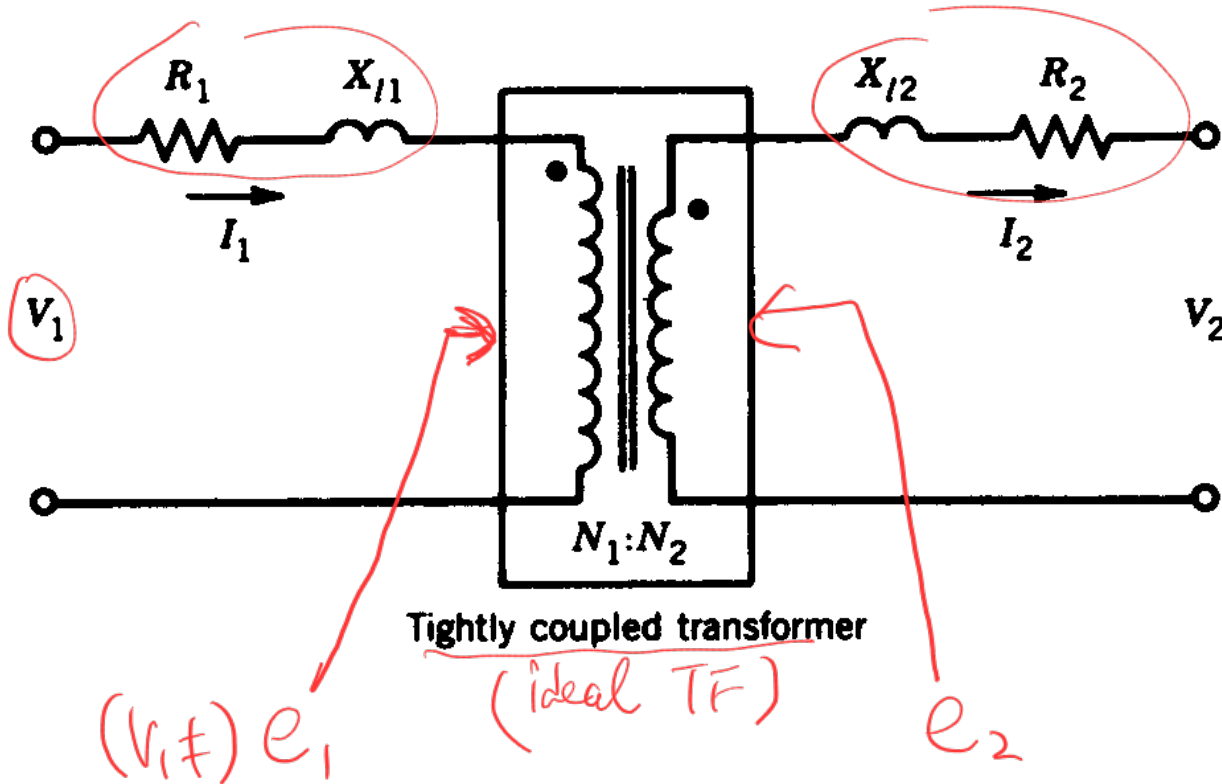R_1 and $R_2 \rightarrow$ winding resistance





How to model core non-idealities?

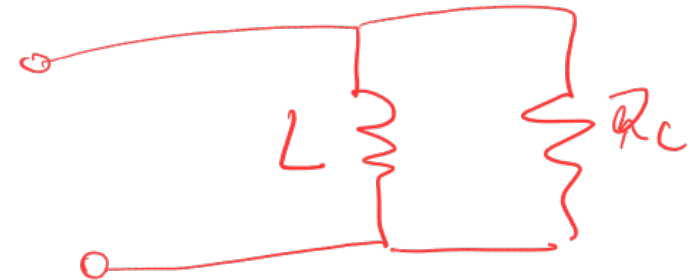

T – Equivalent Circuit for Practical Transformer

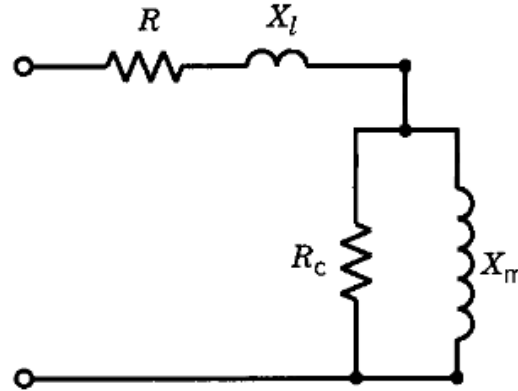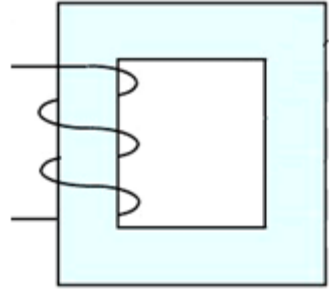
- Recall the equivalent circuit (model) of a non-ideal core and **one** coil:



Use reactances instead
or inductances (to obtain
impedances in Ohms)

$$X = L\omega$$

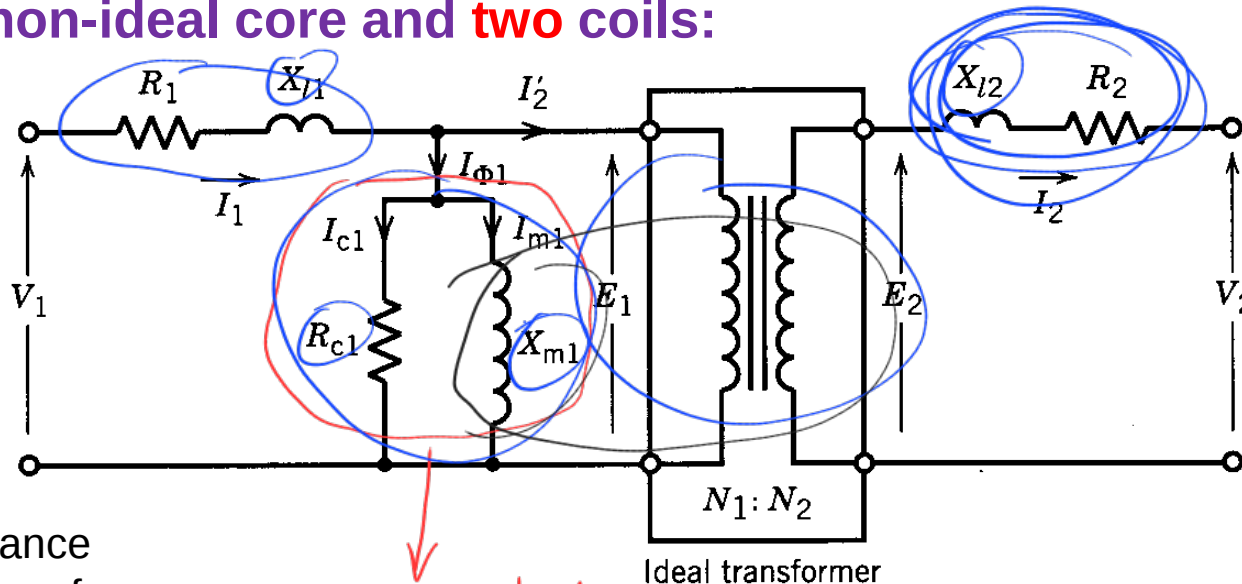- Model of a non-ideal core and **two** coils:



where


$$X_{m1} = L_{m1}\omega$$

magnetizing reactance
(inductance) as seen from
the primary side

Core nonidealities

Ignore leakage:

$$\lambda_1 = L_{m1} i_1 - L_{m12} i_2$$

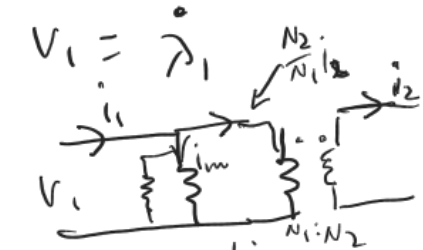

$$V_1 = L_m \frac{di_1}{dt}$$

$$= L_m \frac{d}{dt} \left(i_1 + \frac{N_2}{N_1} i_2 \right)$$

$$= L_m \frac{d}{dt} i_1 + L_m \frac{N_2}{N_1} \frac{d}{dt} i_2$$

$$= \left(\frac{N_1^2}{L_m} \right) \frac{d}{dt} i_1 + \left(\frac{N_1 N_2}{L_m} \right) \frac{d}{dt} i_2$$

$$L_{m1}$$


$$L_{m12}$$



(sign not strictly followed)

T – Equivalent Circuit for Practical Transformer

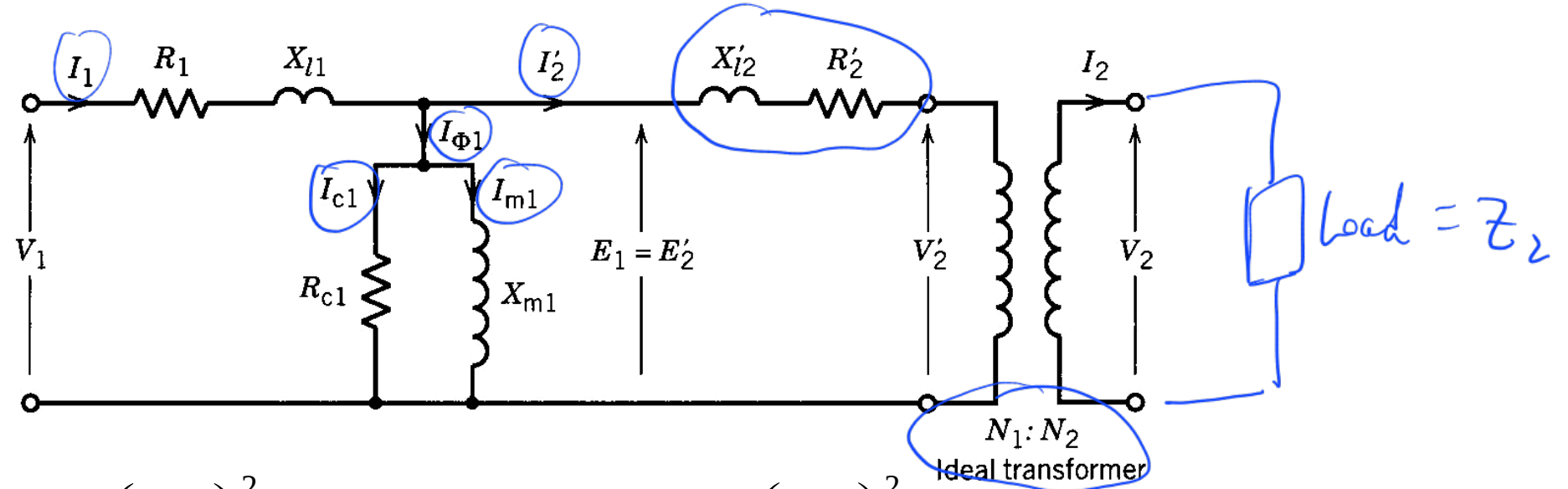Move the Secondary Side parameters to the Primary Side



where
$$R_2' = R_2 \left(\frac{N_1}{N_2} \right)^2 = R_2 a^2 \text{ and } X_{l2}' = X_{l2} \left(\frac{N_1}{N_2} \right)^2 = X_{l2} a^2$$

R_{c1} - represents core losses (Eddy current + Hysteresis)


$I_{\Phi 1}$ - exciting current

I_{m1} - magnetizing current

T – Equivalent Circuit for Practical Transformer

□ Equivalent circuit (model) referred to the primary side:

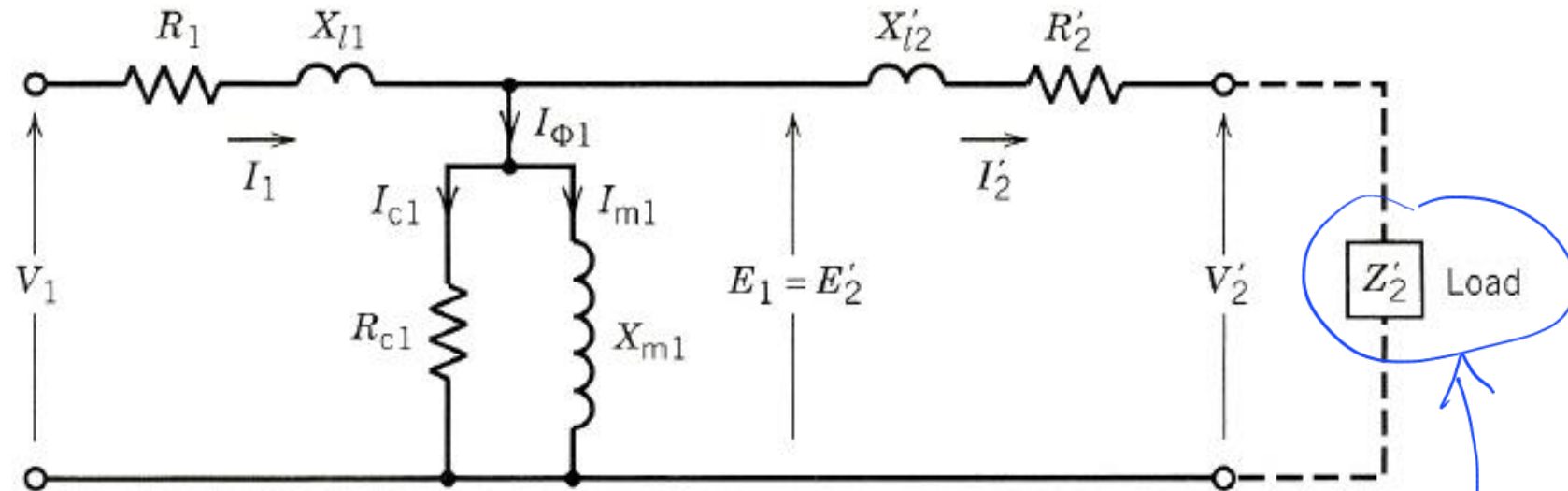➤ Transfer (re-scale) the secondary variables/parameters to the primary:



$$X = L\omega$$


$$\begin{cases} E'_2 = aE_2 = E_1 \\ V'_2 = aV_2 \\ I'_2 = I_2 / a \end{cases}$$

$$\begin{cases} X'_{l2} = a^2 X_{l2} \\ R'_2 = a^2 R_2 \\ Z'_2 = a^2 Z_2 \end{cases}$$

T – Equivalent Circuit for Practical Transformer

□ Equivalent circuit (model) referred to the secondary side:

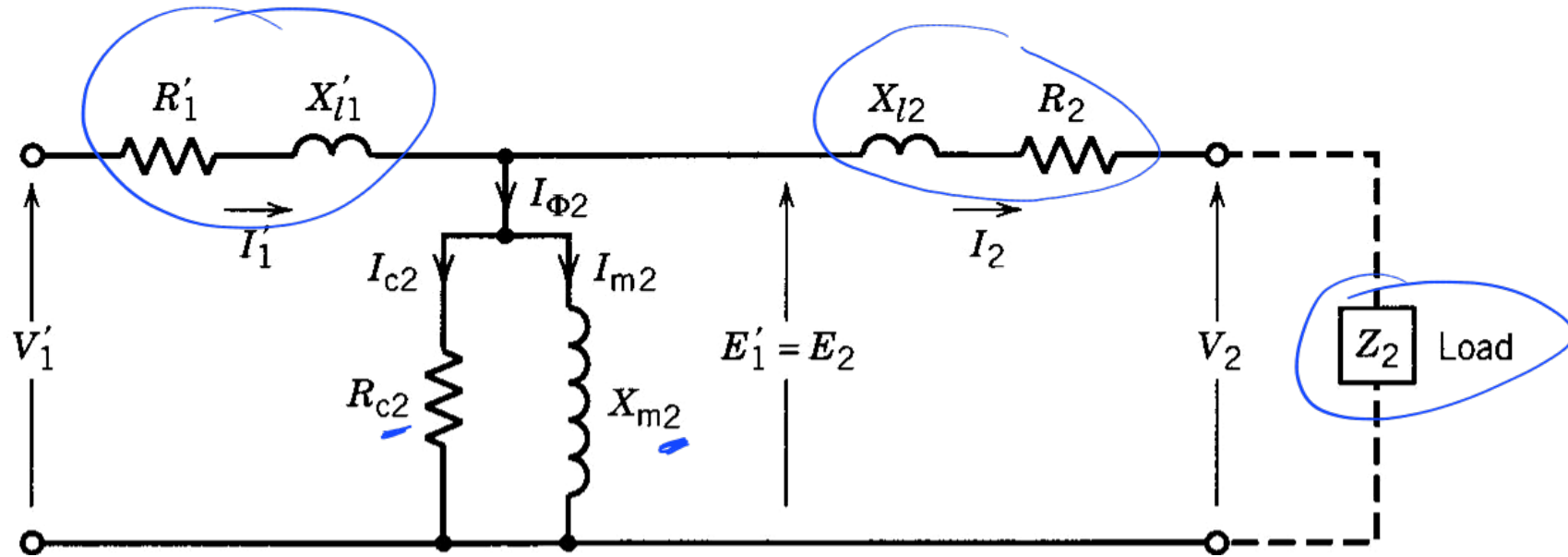➤ Transfer (re-scale) the primary variables/parameters to the secondary:



$$X = L\omega$$

$$\begin{cases} E'_1 = E_1 / a = E_2 \\ V'_1 = V_1 / a \\ I'_1 = aI_1 \end{cases}$$

$$\begin{cases} X'_{l1} = X_{l1} / a^2 \\ R'_1 = R_1 / a^2 \\ X_{m2} = X_{m1} / a^2 \\ R_{c2} = R_{c1} / a^2 \end{cases}$$


T – Equivalent Circuit for Practical Transformer

Most commonly considered **T- equivalent circuit** (Referred to Primary)

Resistances of the primary and secondary windings

Leakage reactances of the primary and secondary windings

for consistency

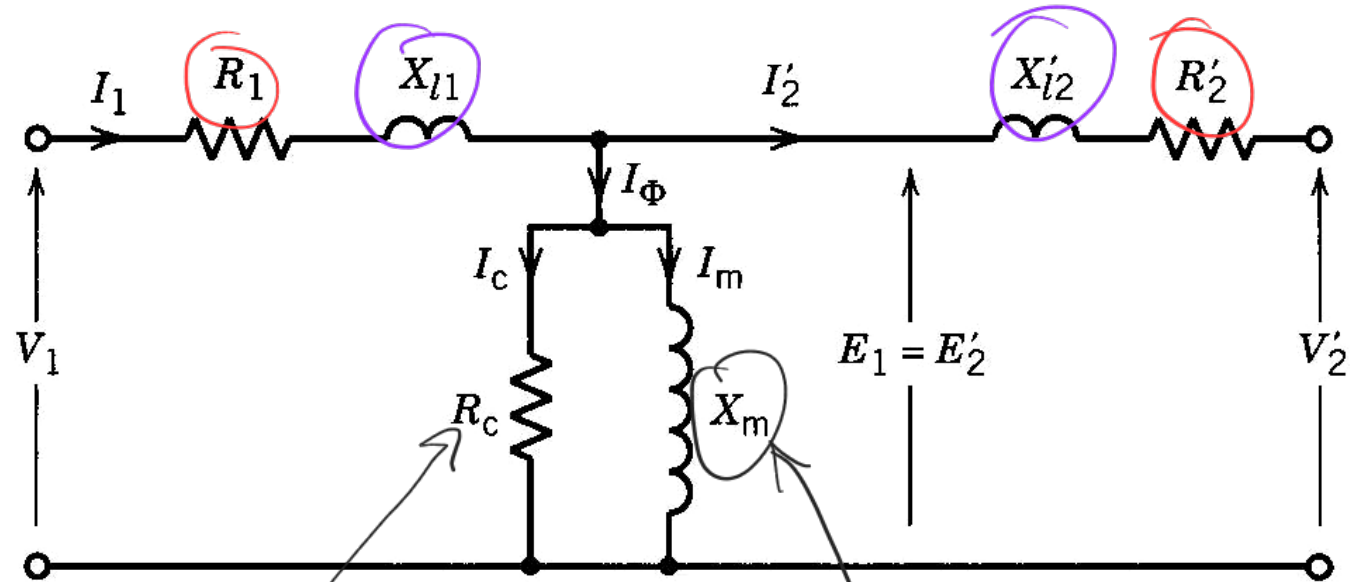




Core losses

Magnetizing reactance


Approximate Equivalent Circuits

not 100% accurate

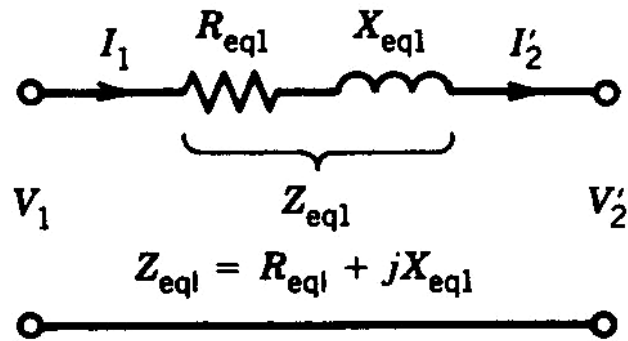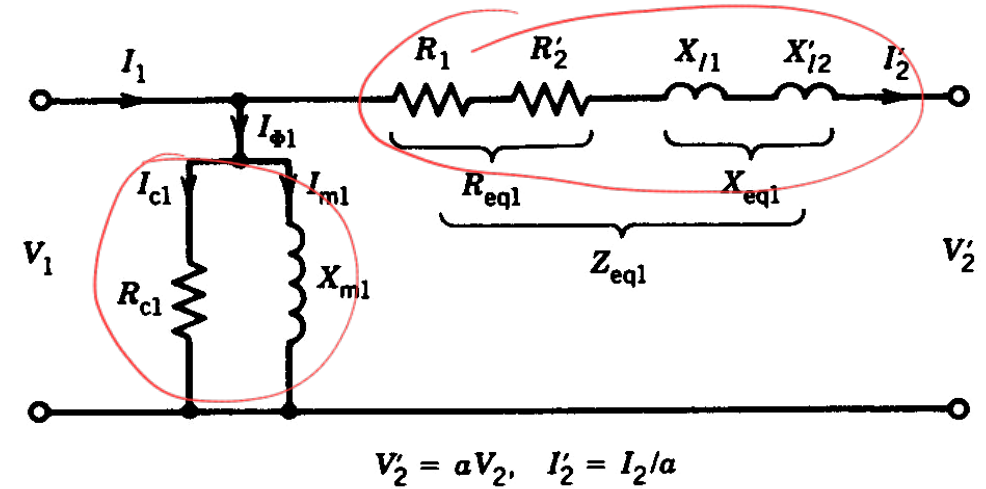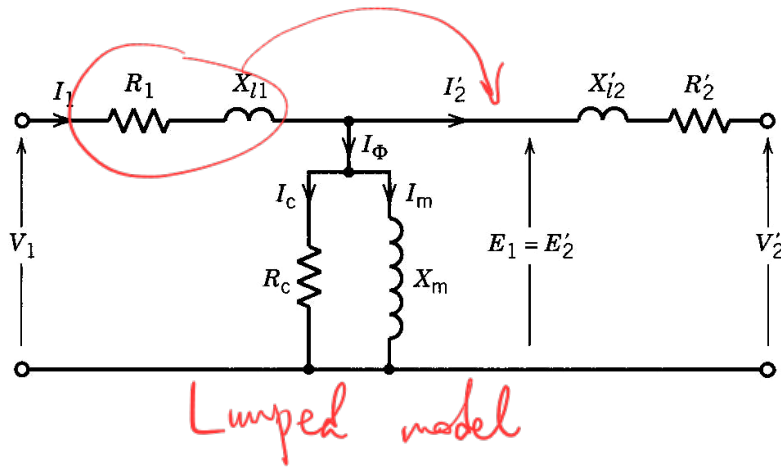Sometimes used to simplify (approximate) calculations



ignore shunt branch

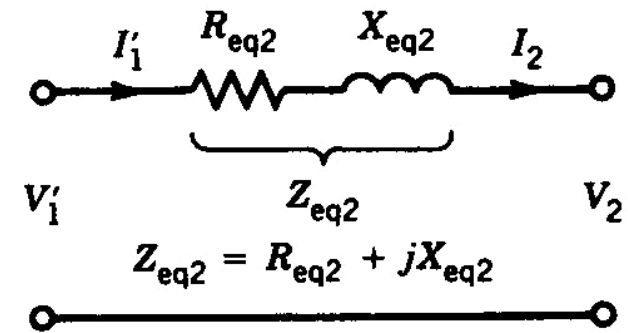

Example: T – Equivalent Circuit for Practical Transformer


❖ **Example 4:** Consider a 50 kVA, 2400/240 V transformer with leakage impedances $Z_{l1} = 0.72 + j0.92 \, \Omega$, $Z_{l2} = 0.007 + j0.009 \, \Omega$, and shunt impedance combined as $Z_{m2} = 6.3 + j43 \, \Omega$.

➤ Draw the equivalent circuits referred to the HV and LV sides and label parameters.


➤ **Solution:**

Compute turns ratio: $a = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{2400}{240} = 10$

Model Referred to HV Side

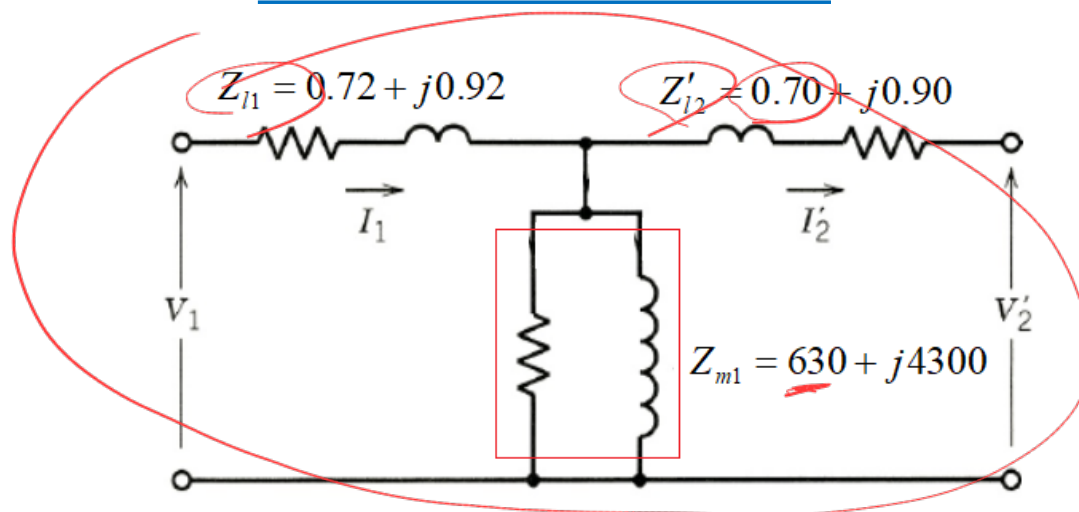

Model Referred to LV Side

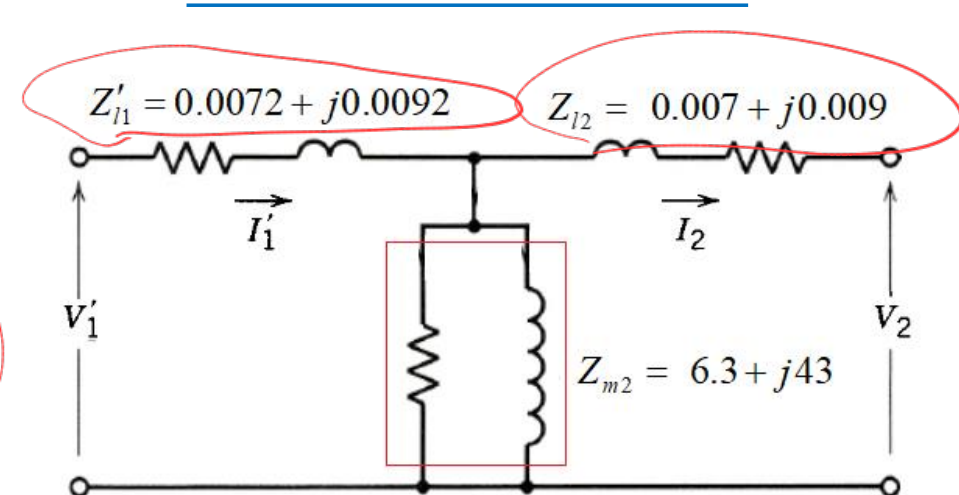


Tests for Determination of Parameters

How to find TF parameters without a datasheet?

- 1) Use **DC Measurements** to get **R_1** and **R_2**
- 2) Open-Circuit (OC) No Load Test to get **R_c** and **X_m**
- 3) Short-Circuit (SC) Test to get **R_{eq}** and **X_{eq}**

*R_c ? Not in parallel
→ AC flux*

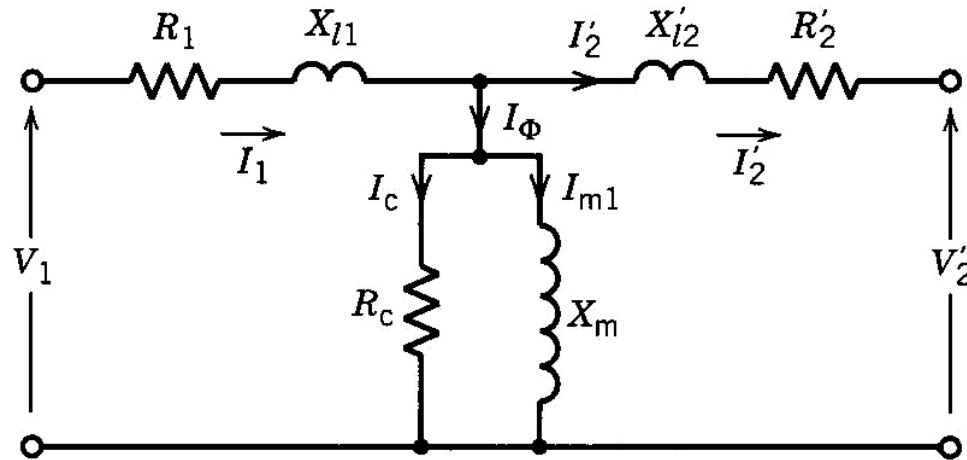

Tests for Determination of Parameters


Open-Circuit (OC) Test:

Leave one side open circuit


Apply nominal voltage to the other side

Read voltmeter, ammeter, wattmeter




Calculate parameters R_c and X_m

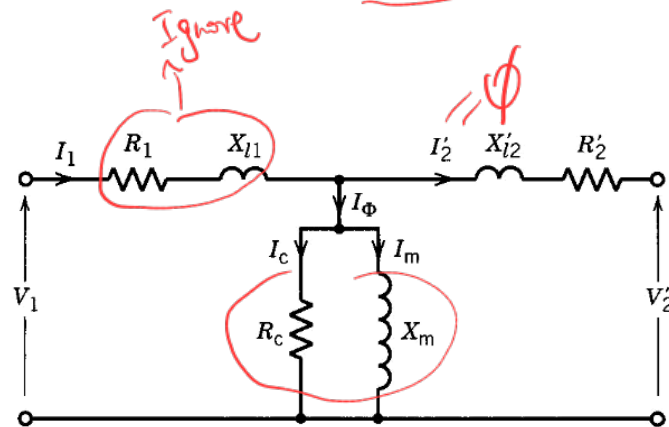

measure
 V_{oc} , I_{oc} , P_{oc}

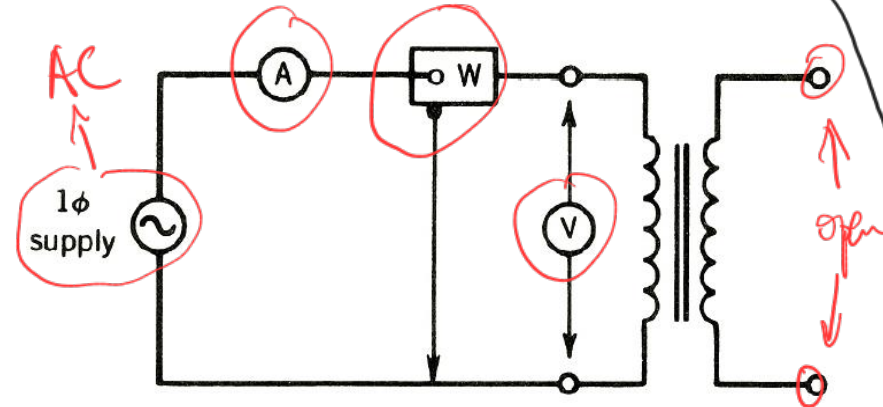

How to empirically find nominal voltage?

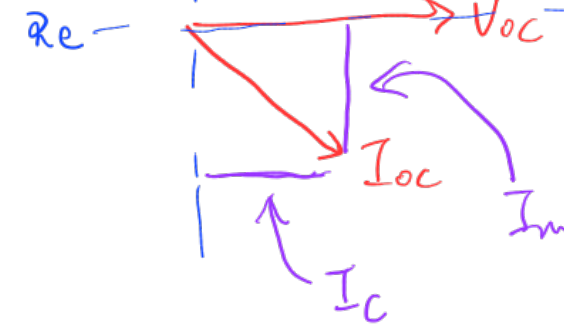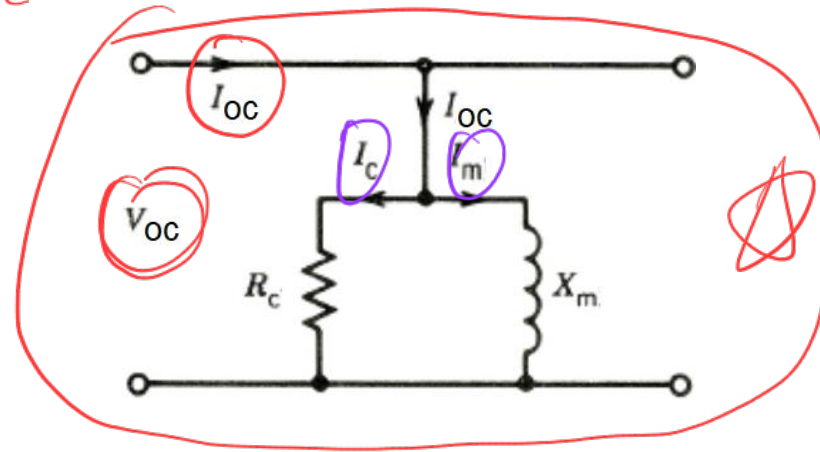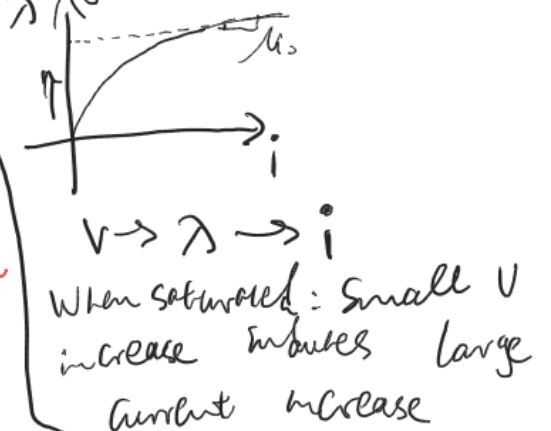

$$P_{oc} = \frac{V_{oc}^2}{R_c} \Rightarrow R_c = \frac{V_{oc}^2}{P_{oc}}$$



$$I_c = \frac{V_{oc}}{R_c} \Rightarrow I_m = \sqrt{I_{oc}^2 - I_c^2}$$



$$X_m = \frac{V_{oc}}{I_m}$$

Assume short $Z \gg$ series Z

$\rightarrow$ WL

Tests for Determination of Parameters

Short-Circuit (SC) Test:



Apply nominal current

Short circuit one winding




Apply nominal current to the other side

Read voltmeter, ammeter, wattmeter

Calculate parameters R_{eq} and X_{eq}

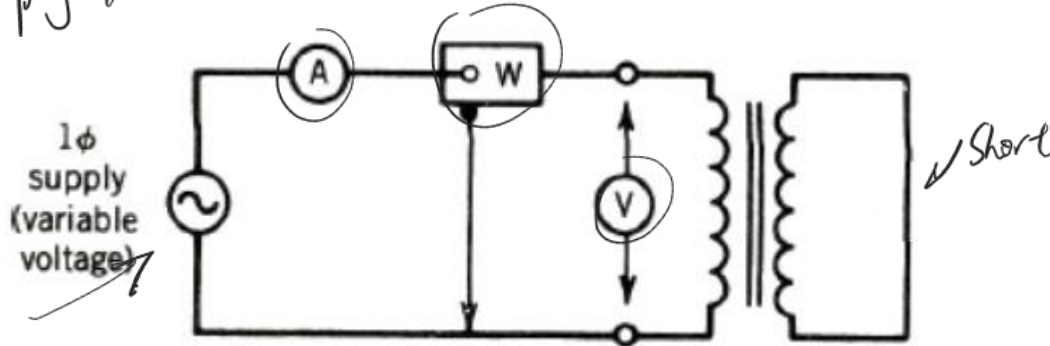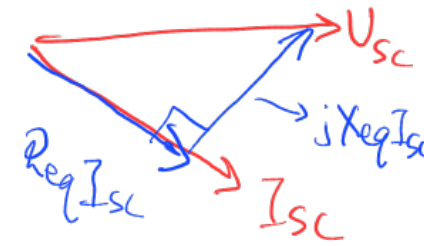

measure I_{sc}, V_{sc}, P_{sc}

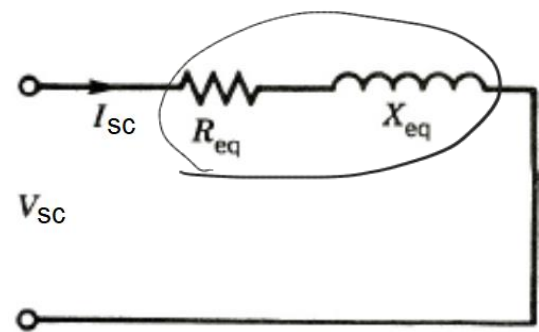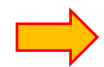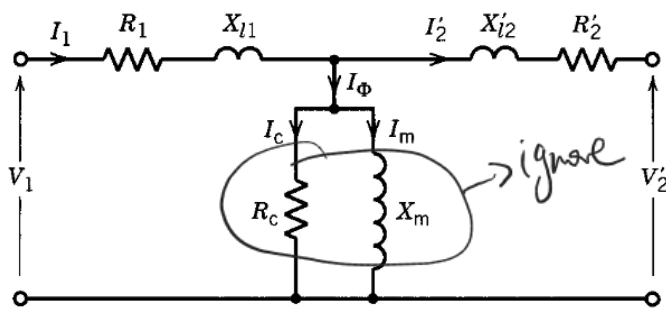

$$\begin{cases} X_{eq} = X_{l1} + X'_{l2} \\ R_{eq} = R_1 + R'_2 \end{cases}$$

$$Z_{eq} = R_{eq} + jX_{eq}$$


$$P_{sc} = I_{sc}^2 R_{eq} \Rightarrow R_{eq} = \frac{P_{sc}}{I_{sc}^2} \Rightarrow Z_{eq} = \frac{V_{sc}}{I_{sc}} \Rightarrow X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2}$$

We may assume


$$\begin{cases} X_{l1} = X'_{l2} = 0.5X_{eq} \\ R_1 = R'_2 = 0.5R_{eq} \end{cases}$$

Assume equal referred when to one side

Efficiency of a transformer

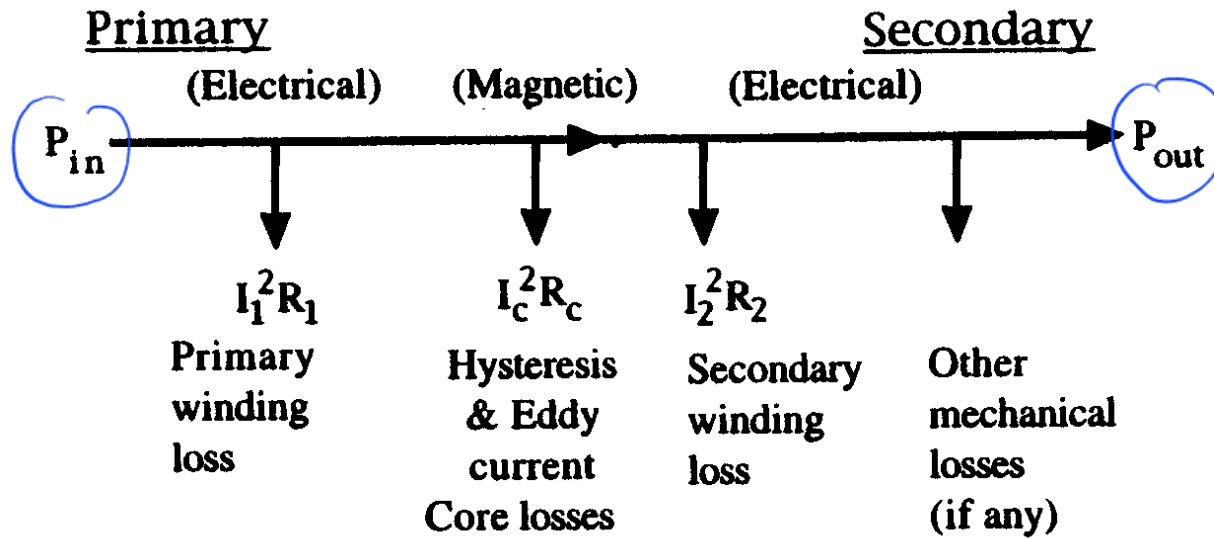

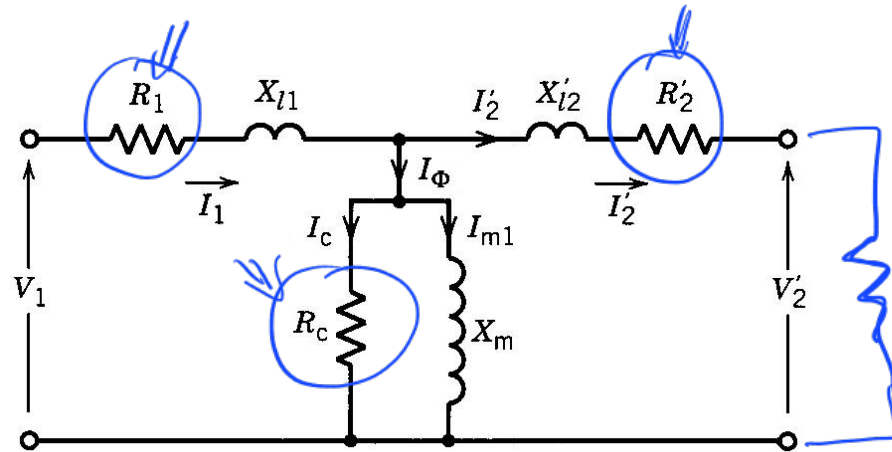
$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{core} + P_{resistive}}$$



Most power transformers are designed for max efficiency at 60-80% of the rated power (current)

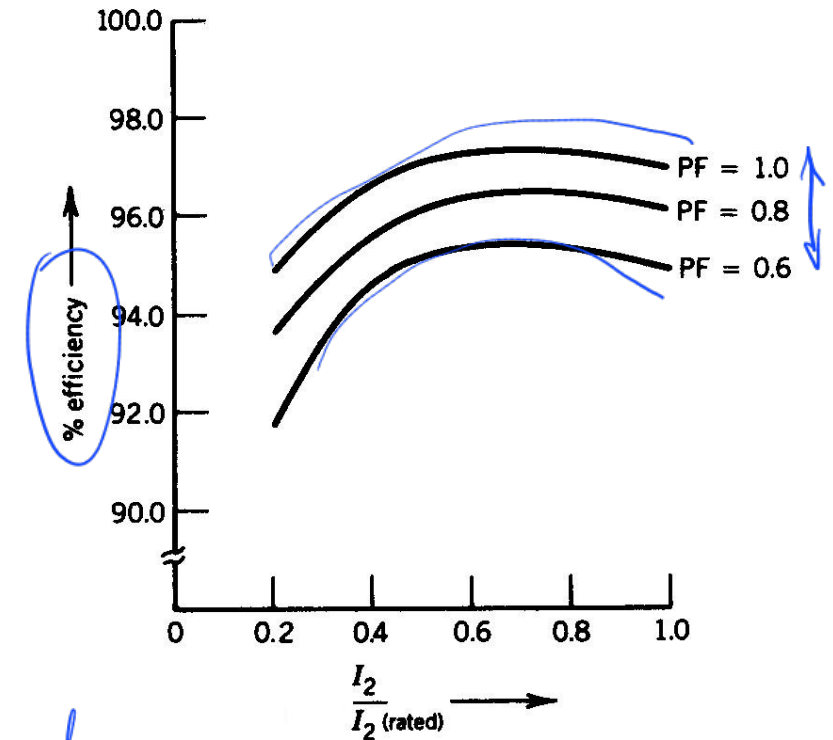vs. R and L in series
↑
Increases current magnitude



Looking ahead...

- Finish **Module 2**