

ELEC 342

Electromechanical Energy Conversion and Transmission

2025-26 Winter Term 2

Lecture 11

February 10, 2026


Zhi Jin (Justin) Zhang

Course Logistics


- **Labs:**
 - **Please be on time and come prepared**
 - **Each person needs to complete prelab and submit as a part of the final lab report**
 - **You need to submit all five (5) lab reports in order to write the final exam**
- Quiz 2 will take place on Feb. 13
 - Detailed information already announced on Canvas
 - Beginning of tutorial and you will be given 20 minutes
 - Closed book and notes, calculators allowed
 - Coverage: Modules 2 and 3 (Hint: review transformers and energy/co-energy/areas)
- Midterm will take place on Feb. 26 *→ no tutorial during that week*

DC-DC Converters Quadrants


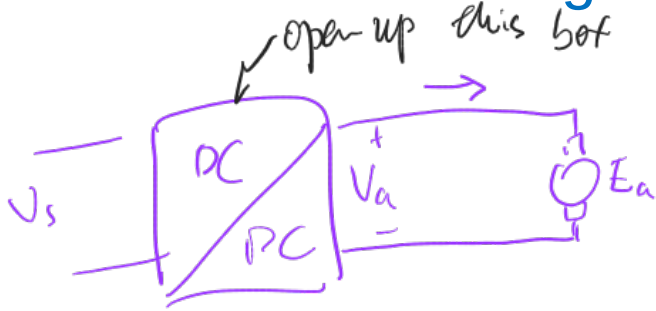
Assume a DC voltage source wherein the averaged output voltage can be controlled



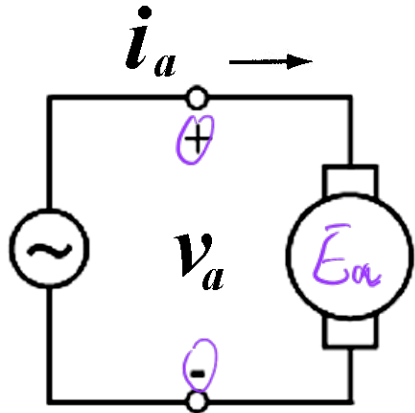Positive direction of current:
from source to machine


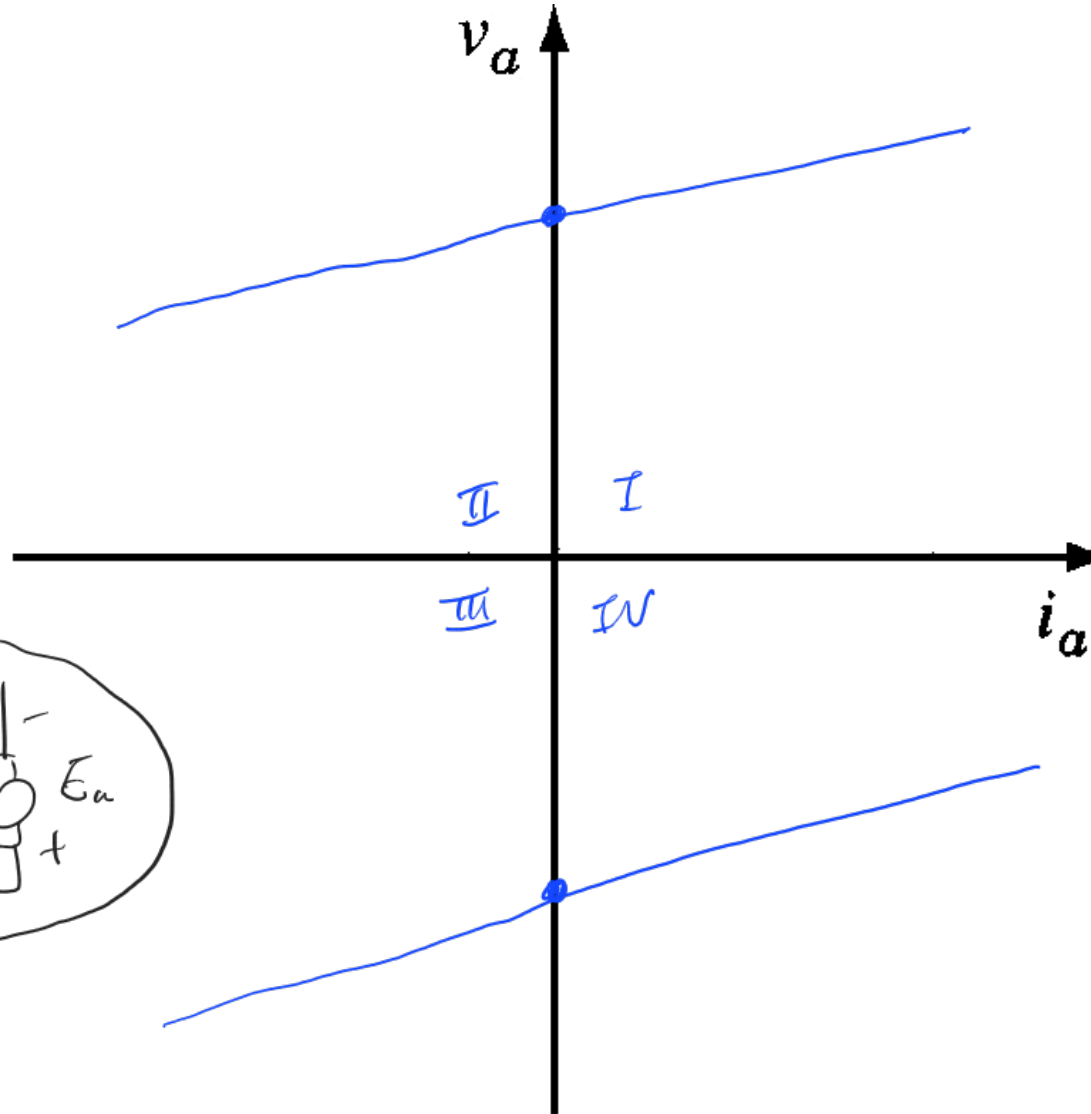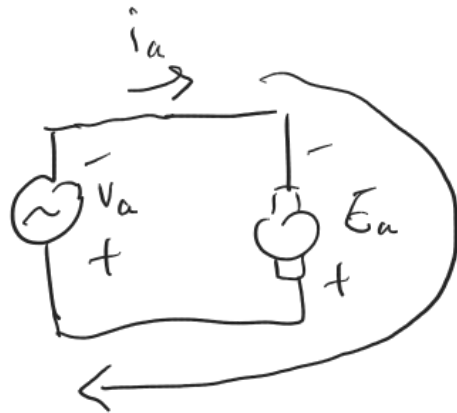
$$\bar{V}_a = \frac{1}{T} \int_0^T v_a(t) dt$$




DC-DC Converters Quadrants - Summary

	Quadrant I	Quadrant II	Quadrant III	Quadrant IV
Name	Forwarding motoring	Forward generating	Reverse motoring	Reverse <u>generating</u>
E_a, V_a	$V_a > E_a > 0$	$E_a > V_a > 0$	$V_a < E_a < 0$	$E_a < V_a < 0$
I_a	$I_a > 0$	$I_a < 0$	$I_a < 0$	$I_a > 0$
T_e	Positive (CCW)	Negative (CW)	Negative (CW)	Positive (CCW)
T_m	Negative (CW)	Positive (CCW)	Positive (CCW)	Negative (CW)
ω_r	Positive (CCW)	Positive (CCW)	Negative (CW)	Negative (CW)
Example	Car in forward (drive) mode going uphill	Car in forward (drive) mode going downhill	Car in reverse mode going uphill	Car in reverse mode going downhill

One-Quadrant DC-DC Converter (Chopper)

Pulse Width Modulation (PWM) S-ON

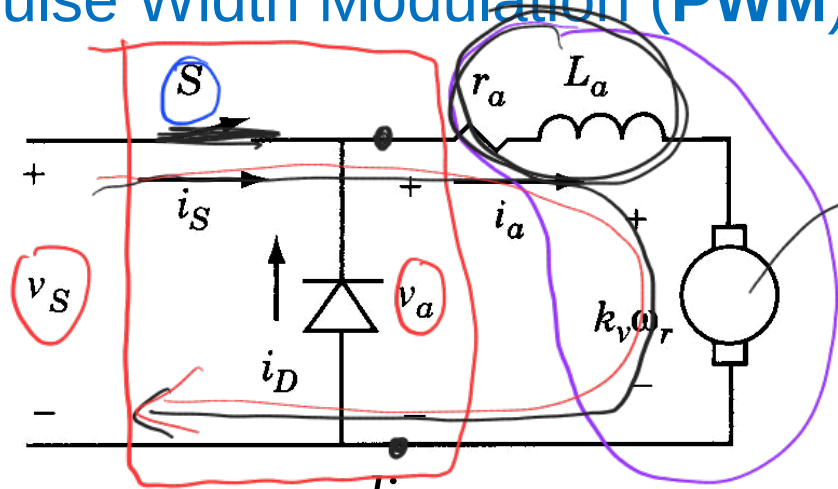


$E_a \sim \text{constant}$
 $E_a < V_s$

$$v_a = r_a i_a + L_a \frac{di_a}{dt} + e_a$$

Switching period: $T \rightarrow f = \frac{1}{T}$

t_1 : S conducting (closed)

$T - t_1 = t_2$: S nonconducting (open)

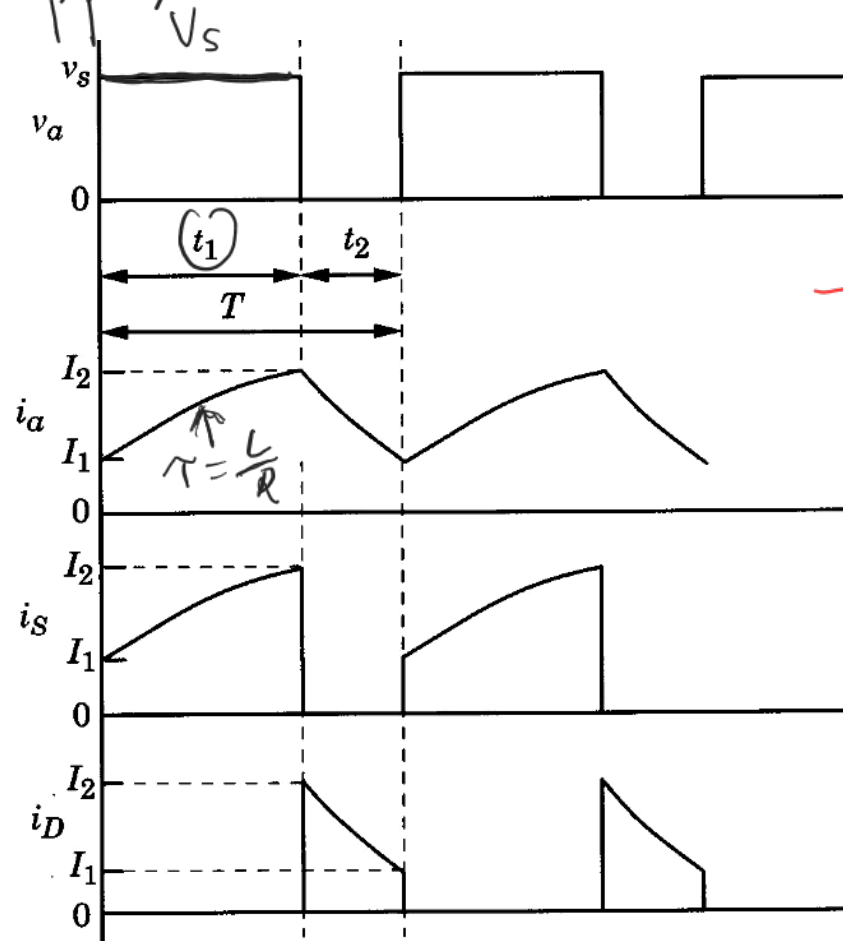

V_L
 $V = L \frac{di}{dt}$
 $\frac{di}{dt} = \frac{V}{L}$

Duty cycle




Average voltage

$$\bar{v}_a = \frac{1}{T} \int_0^T v_a(t) dt = \frac{t_1}{t_1 + t_2} V_s$$

One-Quadrant DC-DC Converter

Pulse Width Modulation (PWM)

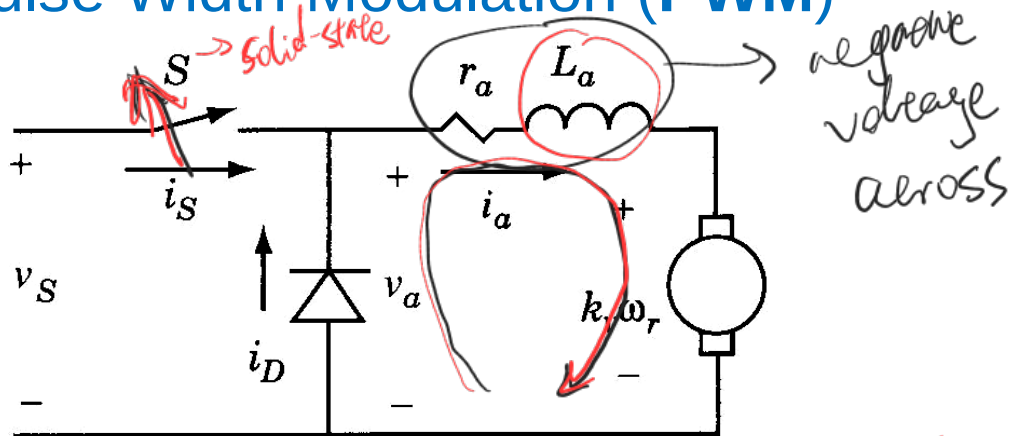

$$v_a = r_a i_a + L_a \frac{di_a}{dt} + e_a$$

$t_1 = S \text{ on}$
 $t_2 = S \text{ off}$

① i_a can only be positive

② $v_a \leq V_s$
 $\rightarrow 0 \leq D \leq 1$


③ Buck converter

④ Ripple: $i_a \propto T_e$
 $\rightarrow$ To reduce ripple
 $\rightarrow$ Inc f
 $\rightarrow$ Inc L

Duty cycle

$$D = \frac{t_1}{T}$$

$$\bar{v}_a = D V_s$$


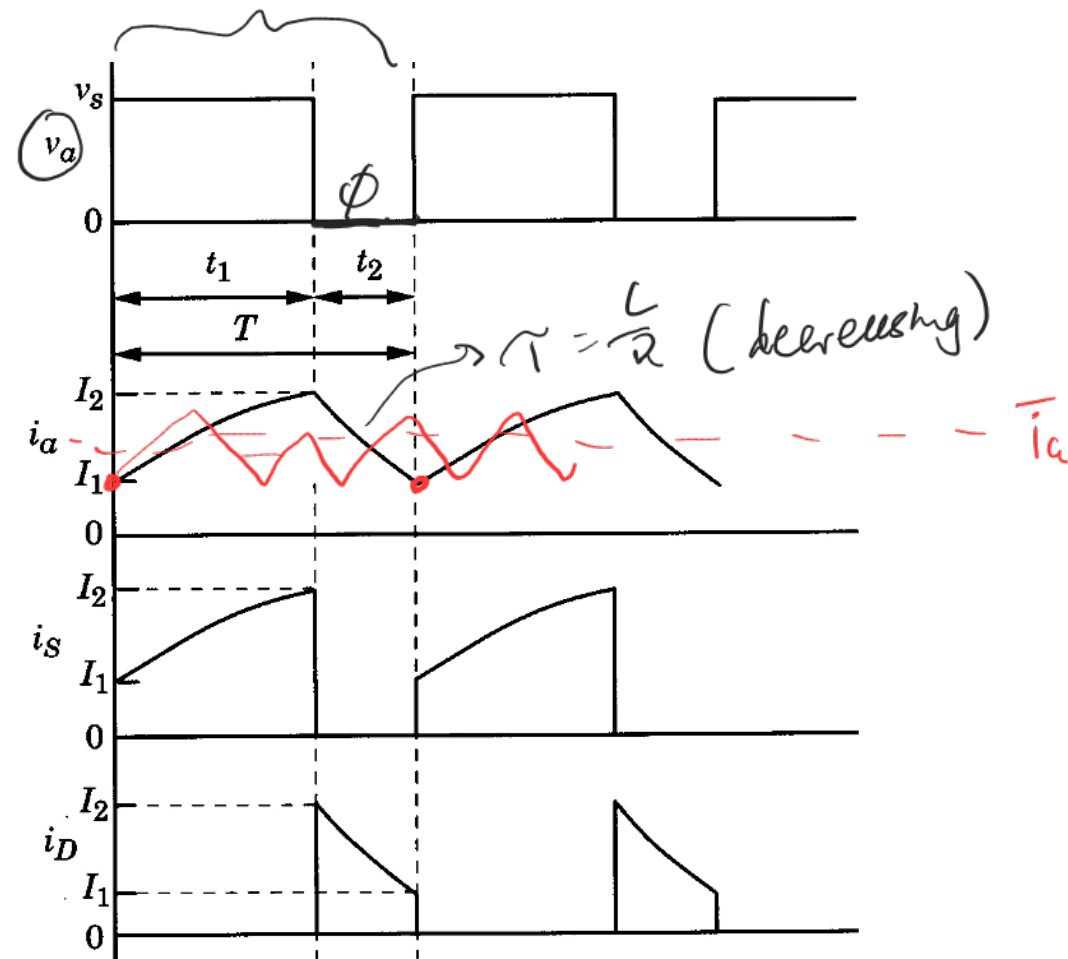


Average voltage

$$\bar{v}_a = \frac{1}{T} \int_0^T v_a(t) dt = \frac{t_1}{t_1 + t_2} V_s = \frac{t_1}{T} V_s$$

$$T \bar{v}_a = t_1 V_s + t_2 \times \phi$$

Two-Quadrant DC-DC Converter

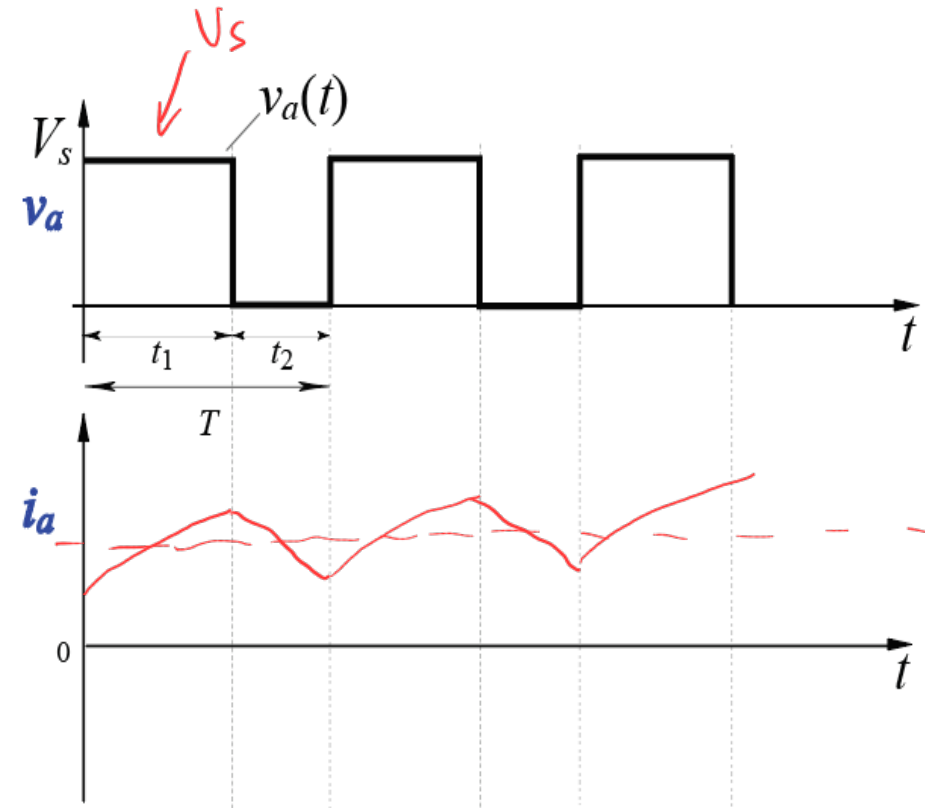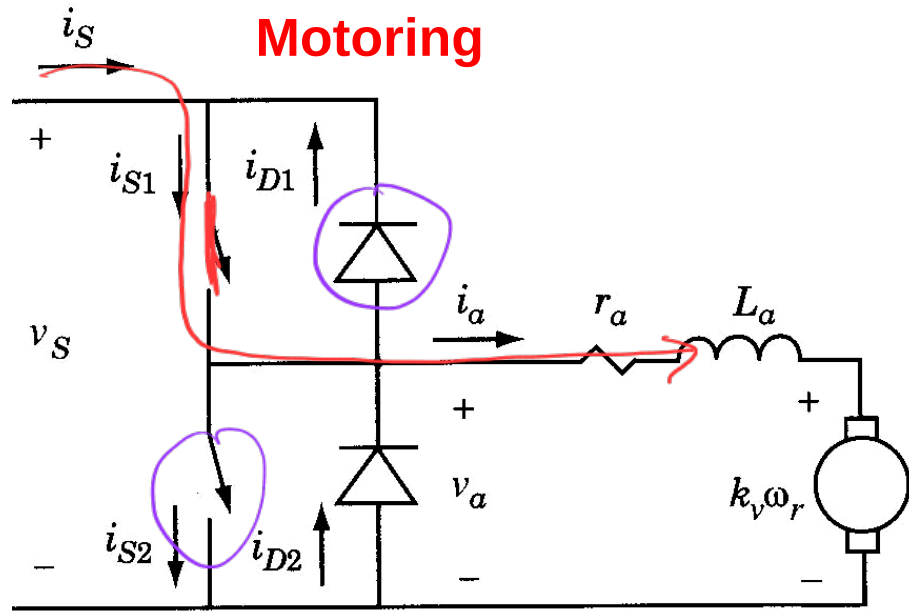

Pulse Width Modulation (PWM)

Assume complementary switching

$$S_1 = \text{NOT}(S_2)$$

$$S_2 = \text{NOT}(S_1)$$


↳ Can't have
both S_1 and S_2
On at same
time

Duty cycle

$$D = \frac{t_1}{T} = \frac{V_a}{V_s}$$

Ex. $V_s = 20V$, $V_a = 15V$
 $D = 0.75$


Two-Quadrant DC-DC Converter

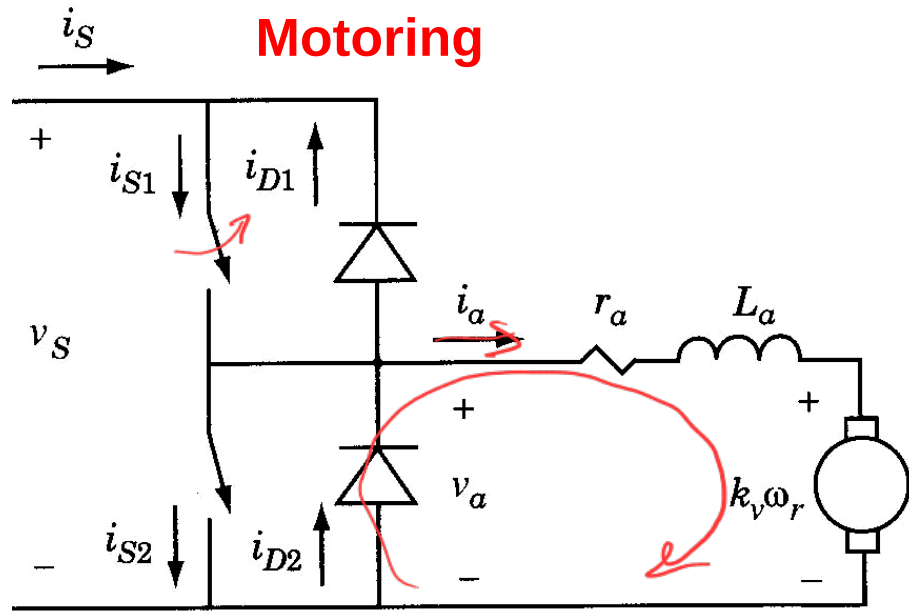


Pulse Width Modulation (PWM)

Assume complementary switching

Duty cycle

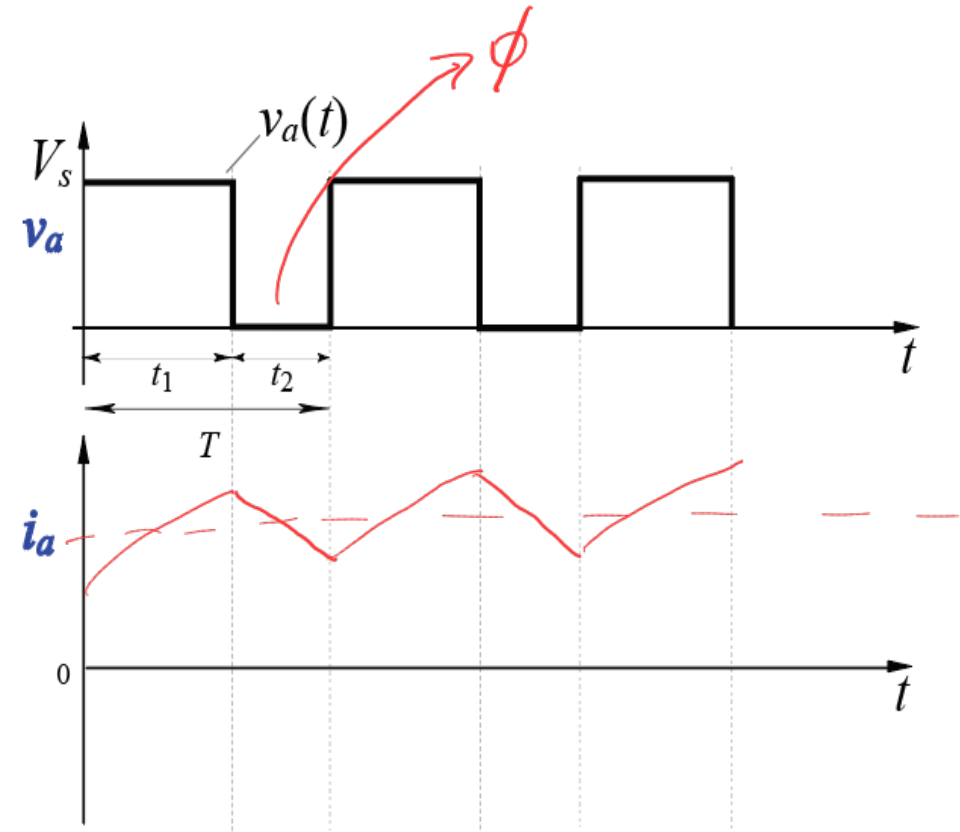

Two-Quadrant DC-DC Converter

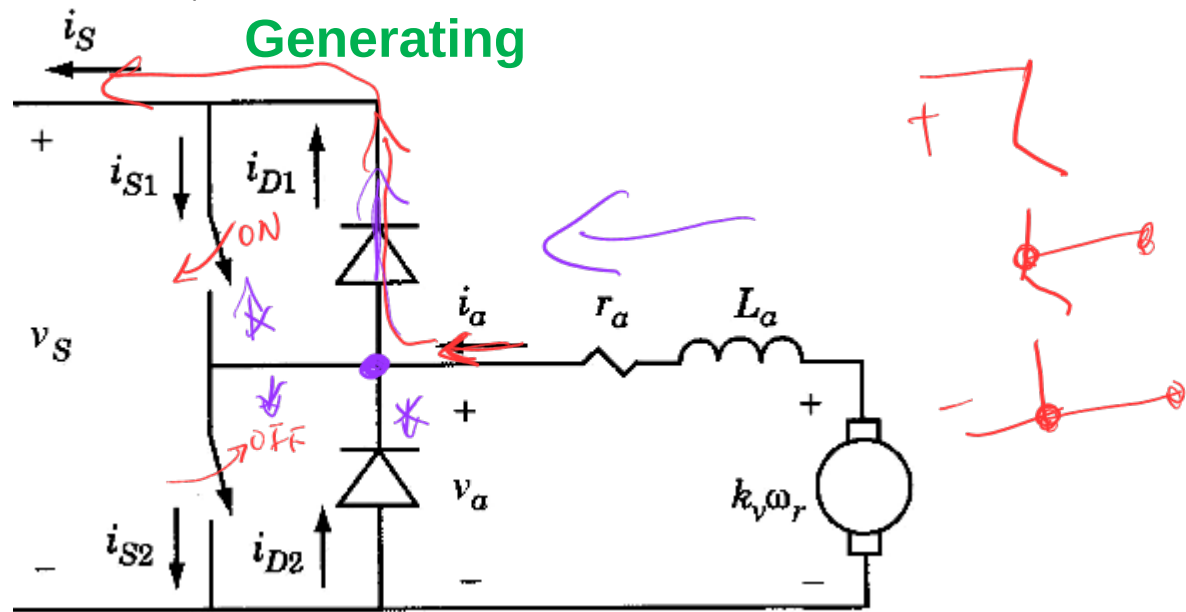


Pulse Width Modulation (PWM)

Assume complementary switching


Duty cycle

$$V_a = DV_S$$

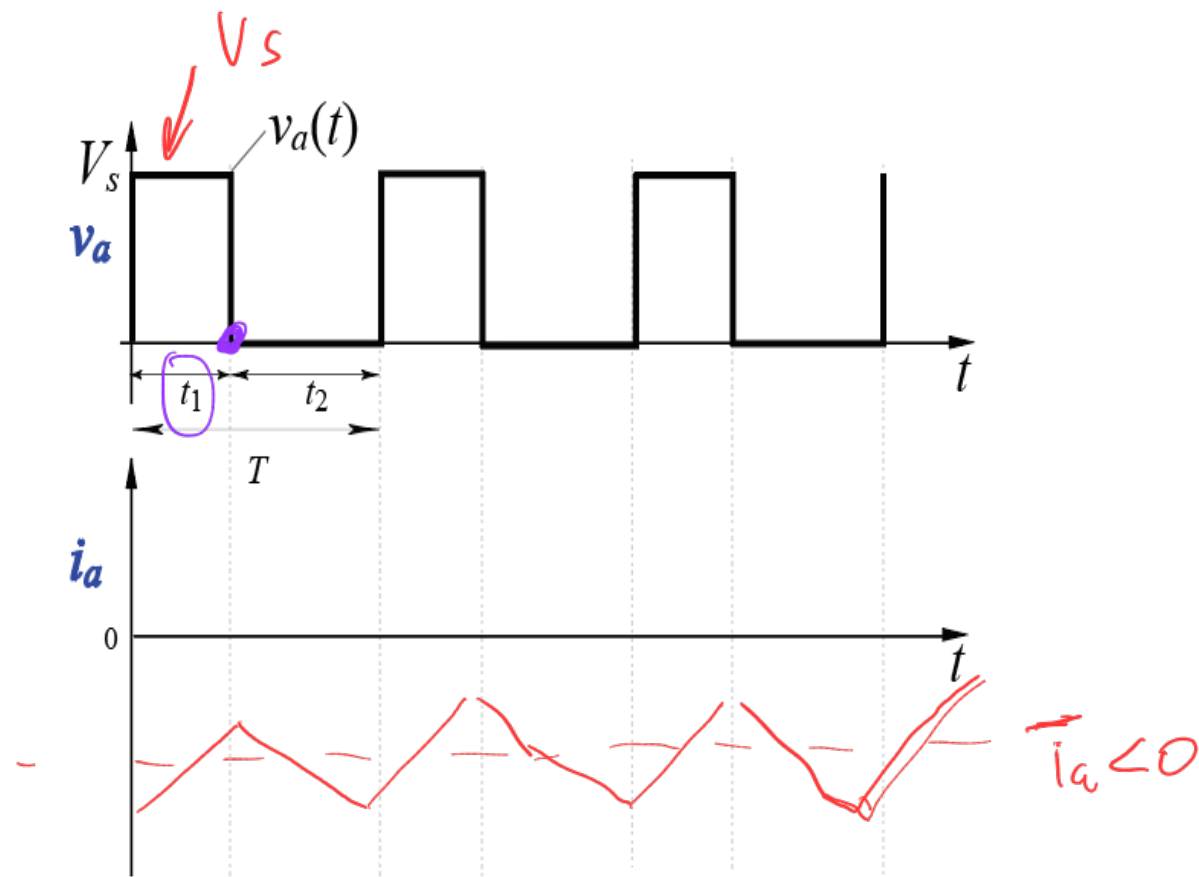


- ① Synchronous buck converter
↳ Bidirectional current flow
- ② Half bridge → only quadrants I and II

Two-Quadrant DC-DC Converter

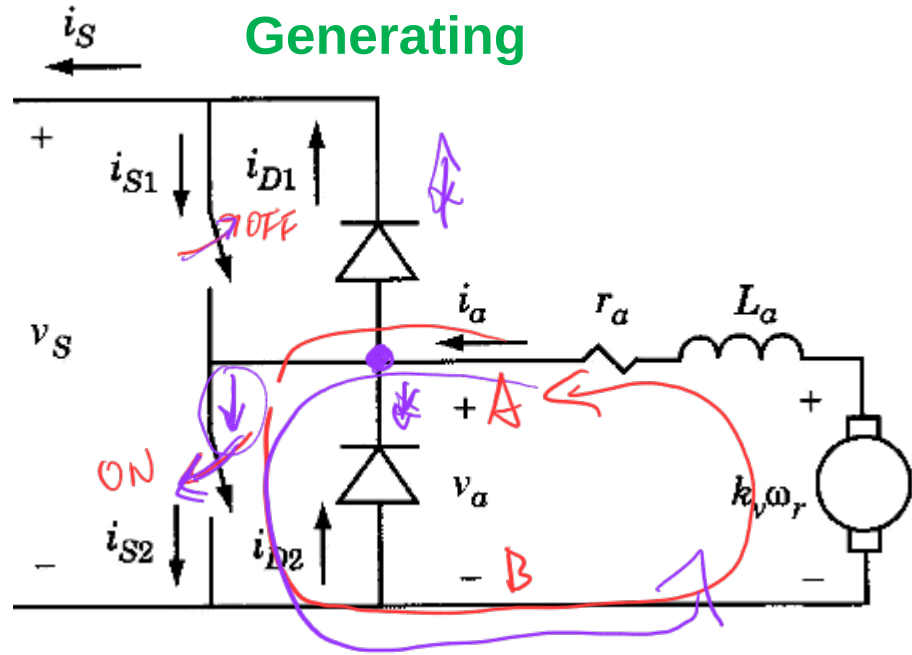

Pulse Width Modulation (PWM)


Assume complementary switching

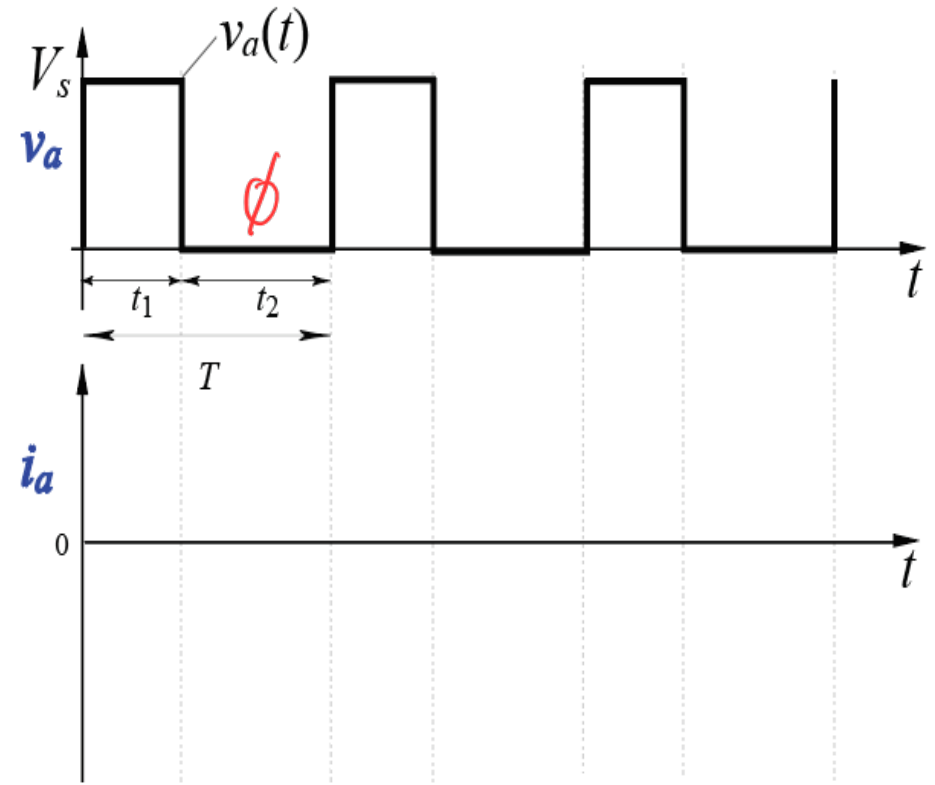

Duty cycle

Four-Quadrant DC-DC Converter

H-Bridge Converter (Full bridge)


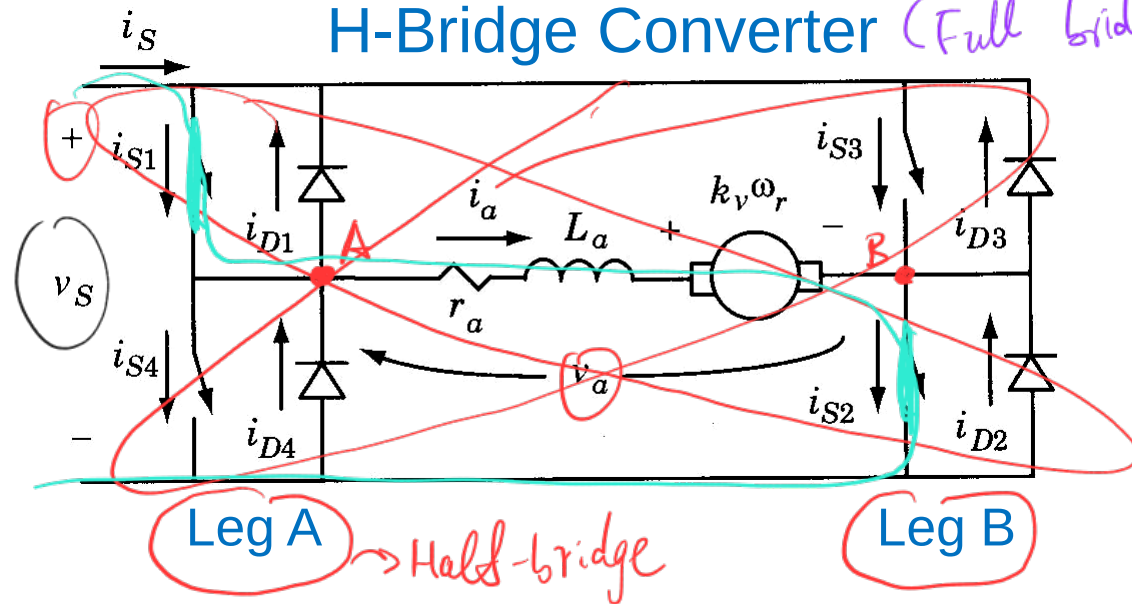


Complementary PWM

S_1 and S_2 on $\rightarrow t_1$
 S_3 and S_4 on $\rightarrow t_2$

Duty cycle
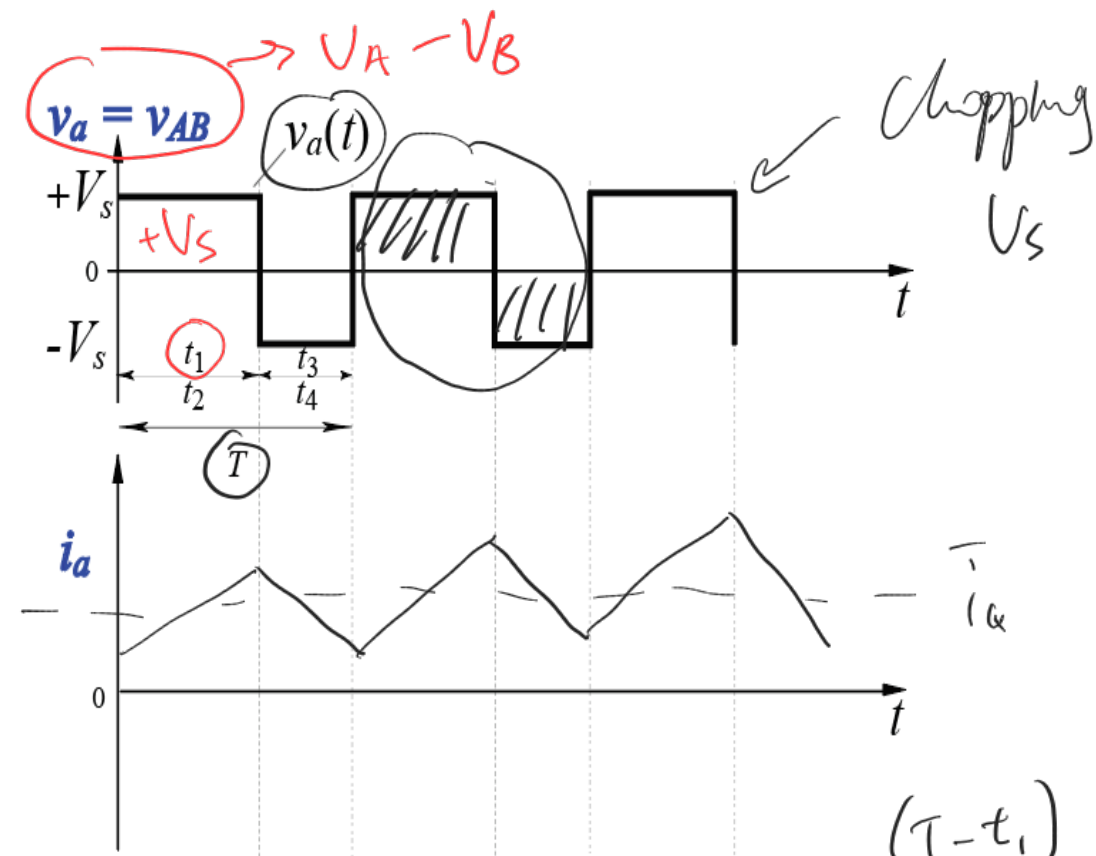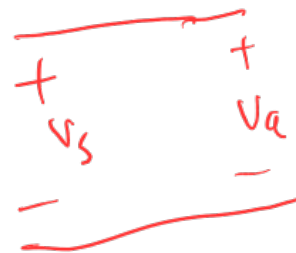
$$D = \frac{t_1}{T}, \quad 0 \leq D \leq 1$$



$$T \bar{V}_a = t_1 V_s + t_2 (-V_s)$$

$$T \bar{V}_a = t_1 V_s - V_s (T - t_1)$$




Average voltage

$$\bar{v}_a = \frac{1}{T} \int_0^T v_a(t) dt = (2D - 1) V_s$$

$$-V_s \leq v_a \leq V_s$$


Four-Quadrant DC-DC Converter

H-Bridge Converter

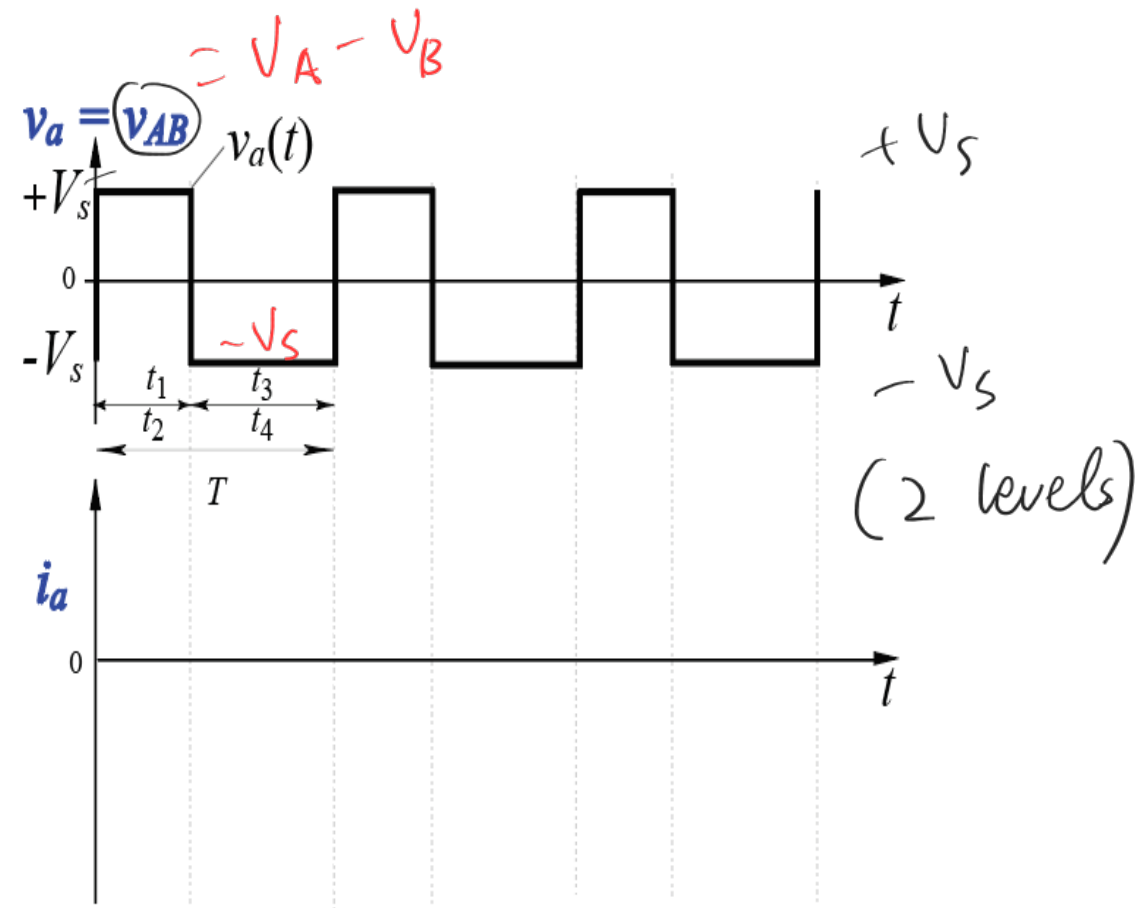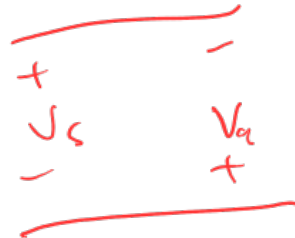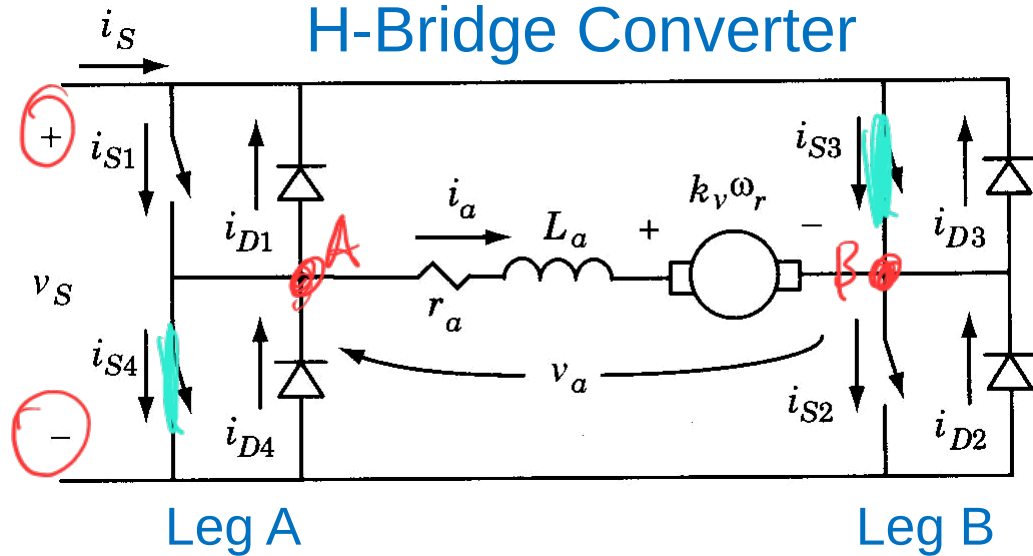

Complementary PWM

Four-Quadrant DC-DC Converter

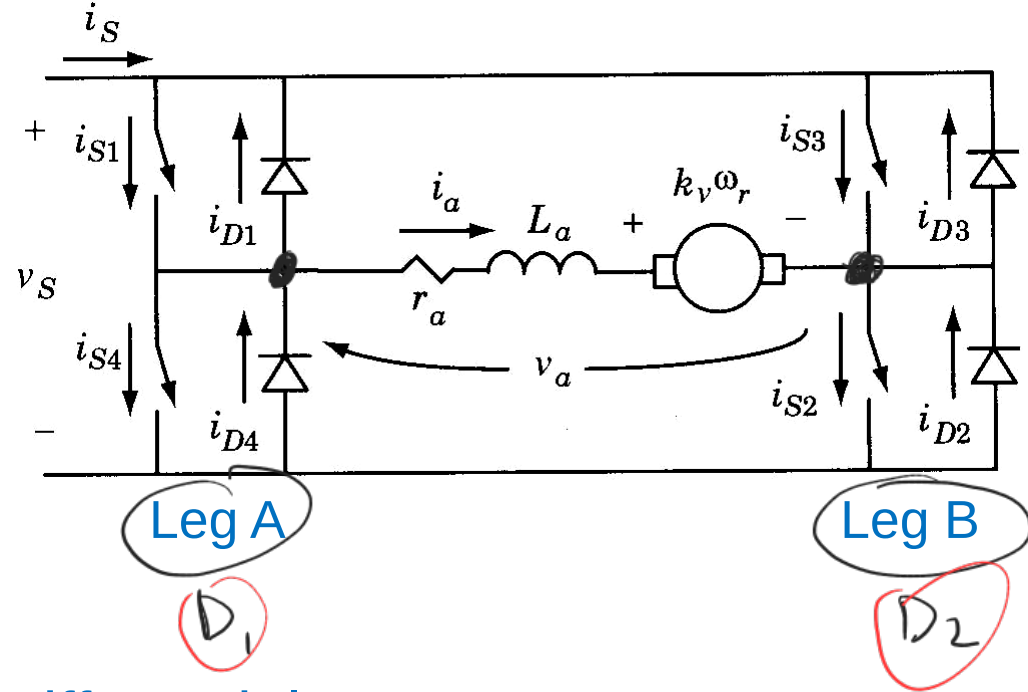


Differential PWM
(Non-complementary)


$$S_1 \rightarrow D_1 \rightarrow S_4 = \text{NOT}(S_1)$$

$$S_3 \rightarrow D_3 \rightarrow S_2 = \text{NOT}(S_3)$$

$$T_A = T_B$$

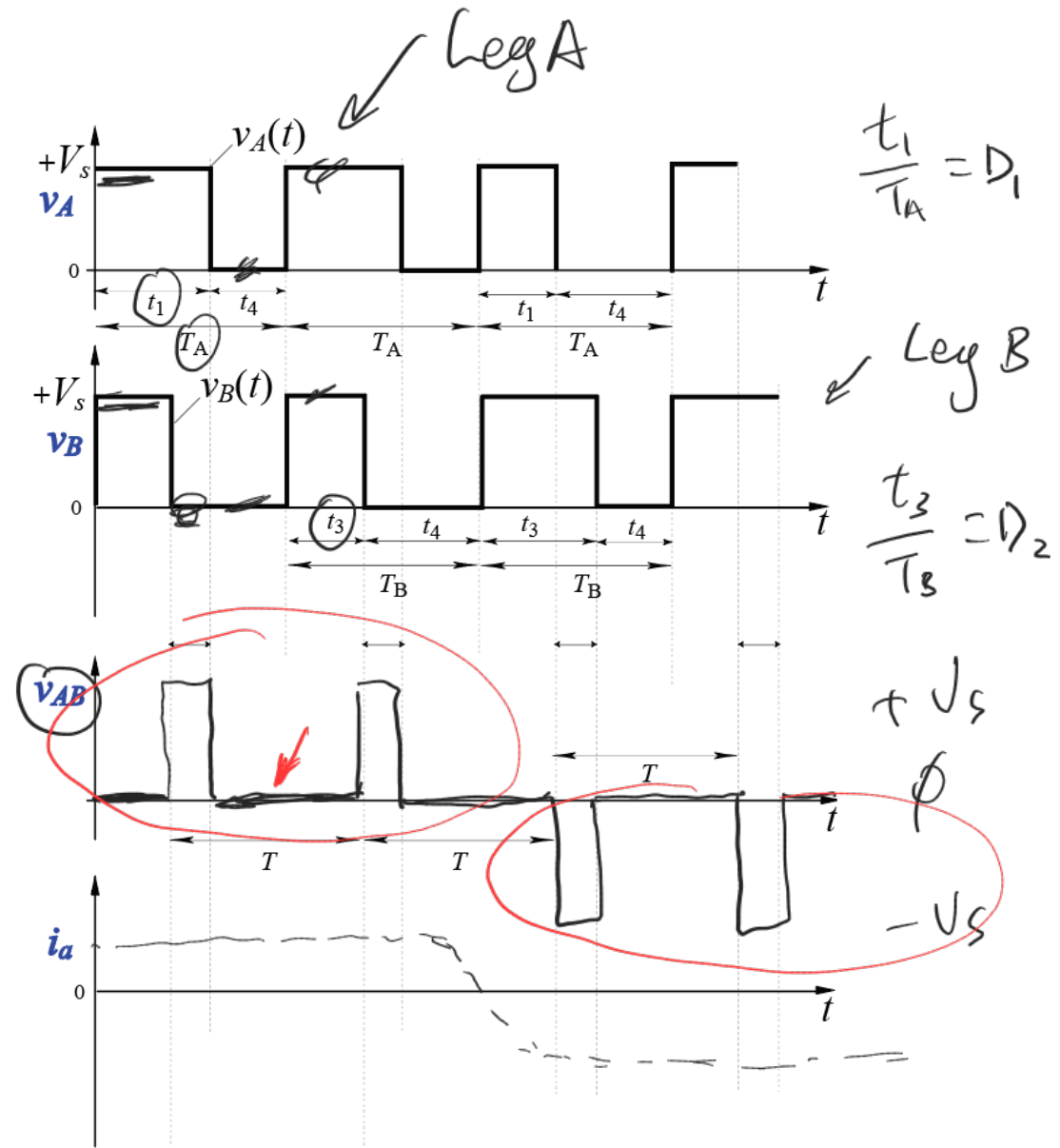

Closed-Loop Electric Drive Systems

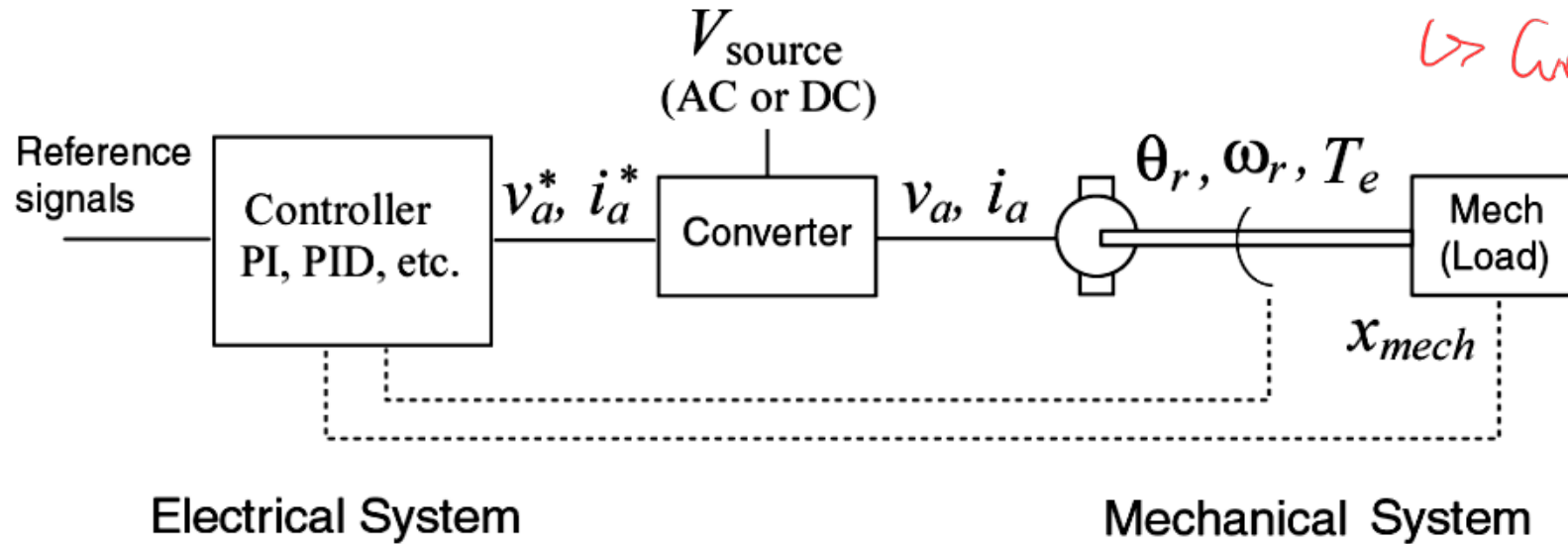


Dr Jaeskeich
↳ Grad course on
maths +
machine drives

Systems are more complicated

- Models are needed for analysis, design, tuning of controllers, and investigating interactions among components
- Simple steady state models may not be sufficient anymore

• Dynamic models (differential equations)

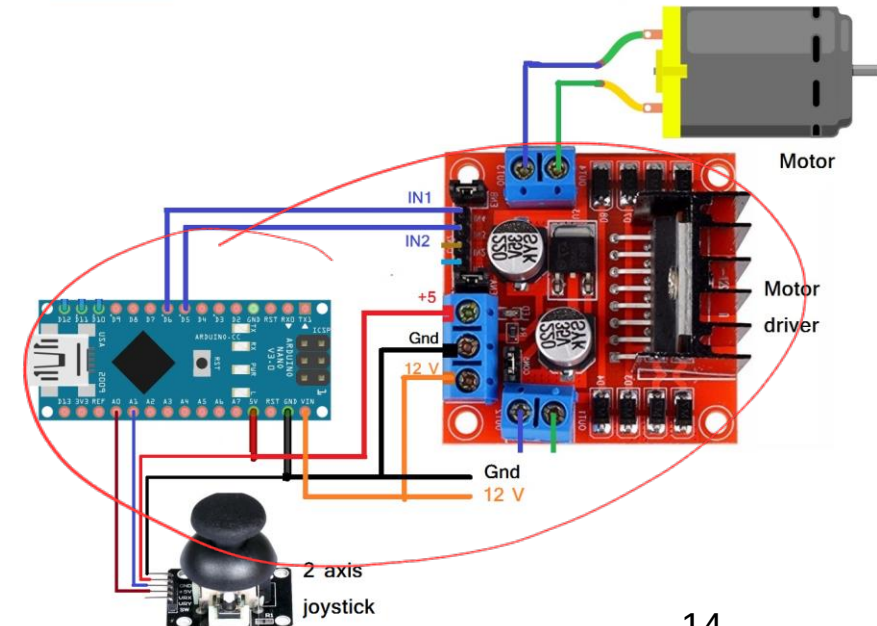
• Model → controller → simulation → Hardware



Dynamic Modeling of DC Machine with Field Winding

Circuit is valid for transient analysis:

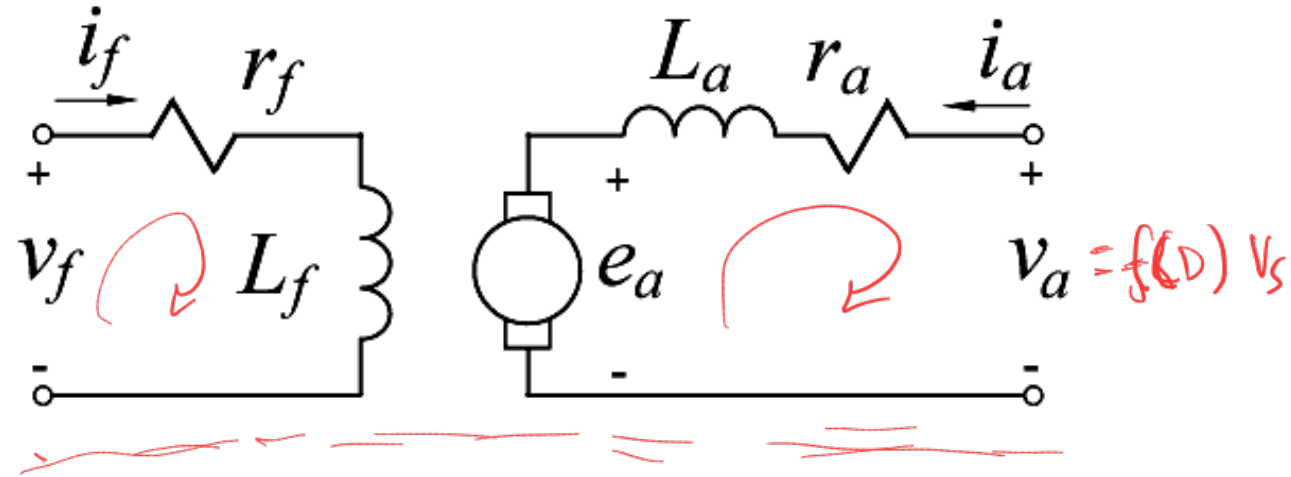→ Circuit has all equations
→ no need for formula sheet



Voltage Equations

$$v_a = r_a i_a + e_a + L_a \frac{di_a}{dt} \rightarrow \text{armature kVL}$$

$$v_f = r_f i_f + \frac{d\lambda_f}{dt} = r_f i_f + L_f \frac{di_f}{dt} \rightarrow \text{field kVL}$$

Coupling Terms

$$e_a = \omega_r L_{af} i_f$$

$$T_e = L_{af} i_f i_a$$

Speed Equation

$$T_e = J \frac{d\omega_r}{dt} + T_m + D_m \omega_r$$

↙ friction

State Variables

- i_f, i_a, ω_r
- Define the energy state of the system
 - Cannot change instantaneously

Input variables: voltage, driving torque

Re-Write the Equations to Express Derivatives

State Equations -> ODEs

$$\frac{di_a}{dt} = -\frac{r_a}{L_a} i_a - \frac{1}{L_a} e_a + \frac{1}{L_a} v_a$$

$$\frac{di_f}{dt} = -\frac{r_f}{L_f} i_f + \frac{1}{L_f} v_f$$

$$\frac{d\omega_r}{dt} = -\frac{D_m}{J} \omega_r + \frac{1}{J} (T_e - T_m)$$

Coupling Terms

$$e_a = \omega_r L_{af} i_f$$

$$T_e = L_{af} i_f i_a$$

Are these equations coupled or decoupled? *coupled*


Are these equations linear or non-linear? *non-linear → variables multiplied together*

How do we solve these equations? *Analytical → challenging*
Numerically → numerical integration → software (Simulink)

Implementation of the State Equations → Signal diagram

$$\frac{di_a}{dt} = -\frac{r_a}{L_a}i_a - \frac{1}{L_a}e_a + \frac{1}{L_a}v_a$$
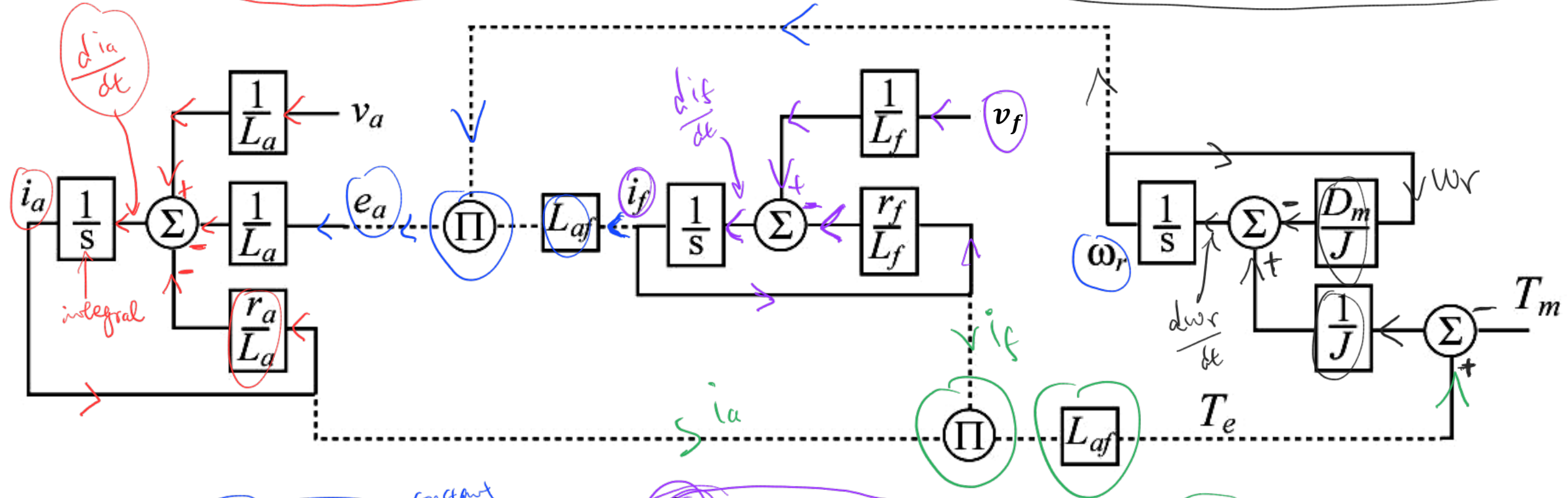
$$\frac{d\omega_r}{dt} = -\frac{D_m}{J}\omega_r + \frac{1}{J}(T_e - T_m)$$




$$e_a = \omega_r L_{af} i_f$$

$$\frac{di_f}{dt} = -\frac{r_f}{L_f}i_f + \frac{1}{L_f}v_f$$

$$T_e = L_{af} i_f i_a$$

Is this a unique implementation ? No

Implementation of the State Equations

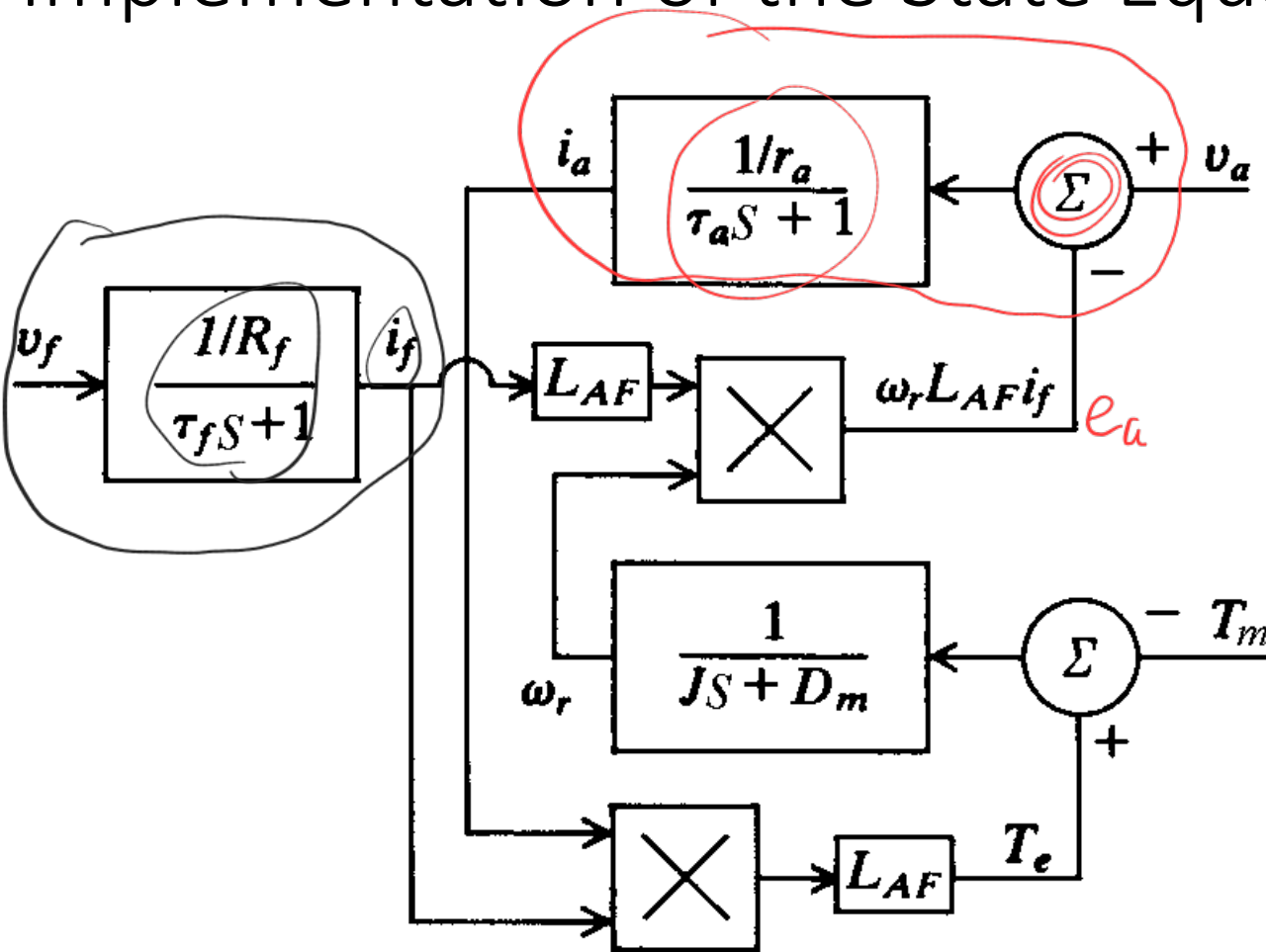

Define time constants

$$\tau_a = \frac{L_a}{r_a}$$

$$\tau_f = \frac{L_f}{r_f}$$

Re-write the equations in s-domain

$$v_f = r_f (1 + \tau_f s) i_f \Rightarrow i_f = \frac{1/r_f}{1 + \tau_f s} v_f$$

$$v_a = r_a (1 + \tau_a s) i_a + e_a$$

$$\Rightarrow (v_a + e_a) \frac{1/r_a}{\tau_a s + 1} = i_a$$


$$e_a = \omega_r L_{af} i_f$$

$$T_e - T_m = (D_m + Js) \omega_r$$


$$T_e = L_{af} i_f i_a$$

Same system
as previous slide

5-HP DC Motor (With Field Winding) Simulink Model

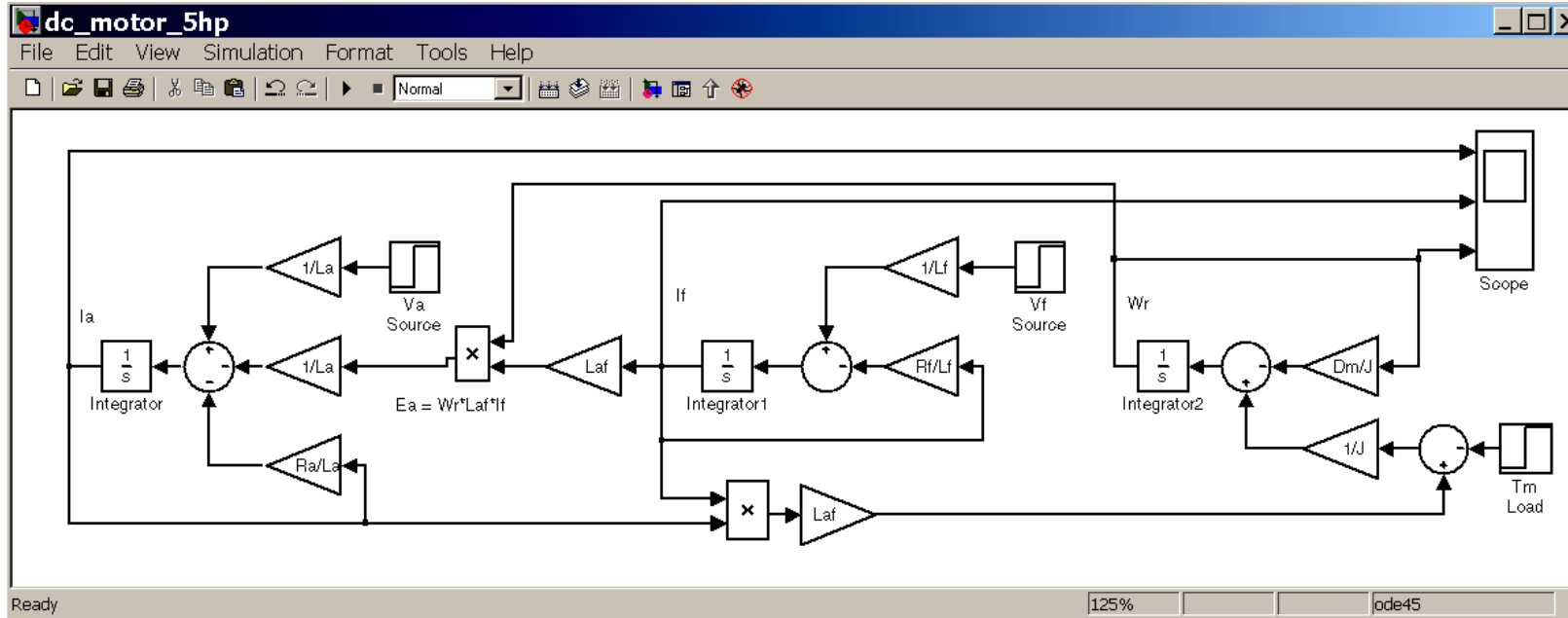

Slide 17

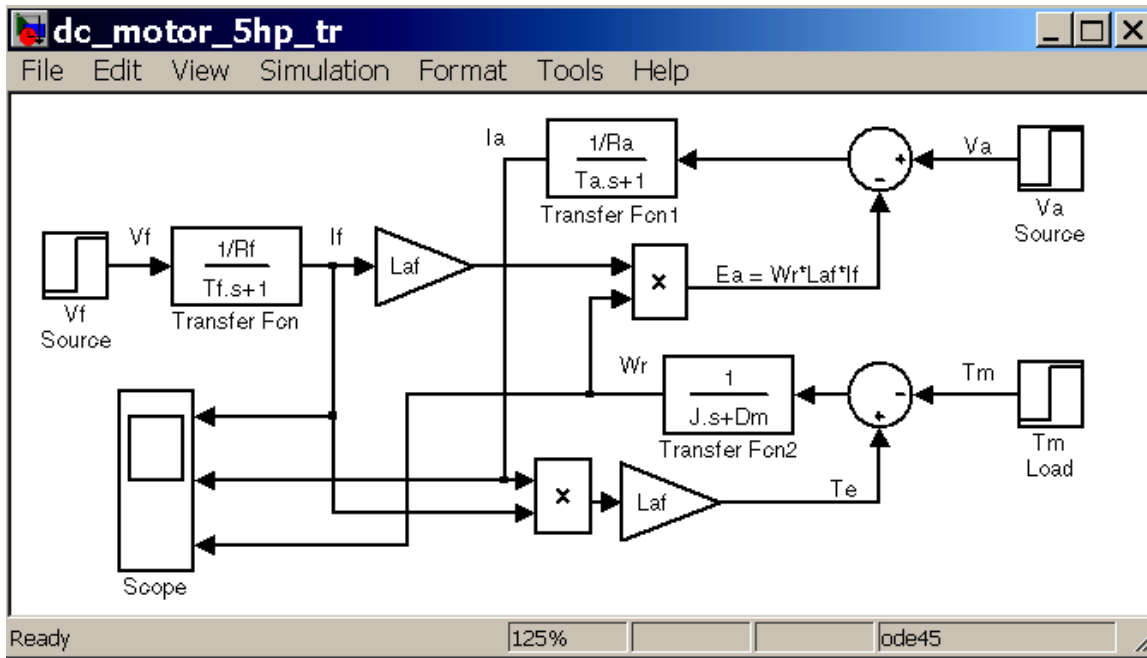

Slide 18

Try to do it yourself

- Both models are absolutely equivalent
- Models behave like “virtual” DC machine

Looking ahead...

- Finish **Module 4**