

ELEC 342

Electromechanical Energy Conversion and Transmission

2025-26 Winter Term 2

Lecture 13

February 24, 2026

Zhi Jin (Justin) Zhang

Course Logistics

- Labs:
 - Please be on time and come prepared
 - Each person needs to complete prelab and submit as a part of the final lab report
 - You need to submit all five (5) lab reports in order to write the final exam
- Midterm will take place on Feb. 26
 - Detailed logistics are already announced on Canvas
- **No Tutorial this week**

Example 5


A dc machine is connected across a 240-volt line. It rotates at 1200 rpm and is generating 230 volts. The armature current is 40 amps.

- (a) Is the machine functioning as a generator or as a motor?
- (b) Determine the resistance of the armature circuit.
- (c) Determine power loss in the armature circuit resistance and the electromagnetic power.
- (d) Determine the electromagnetic torque in newton-meters.
- (e) If the load is thrown off, what will the generated voltage and the rpm of the machine be

$$\hookrightarrow T_m = 0 = T_e \text{ (ignore friction)}$$

$$\hookrightarrow T_e = k_t I_a \Rightarrow I_a = 0 \text{ A}$$

Example 5

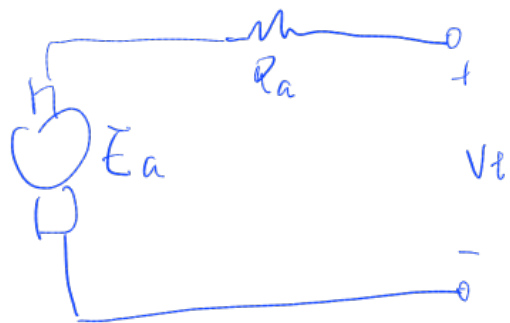

(a) $V_t = 240 \text{ V}$, $E_a = 230 \text{ V}$, $I_a = 40 \text{ A}$

$V_t > E_a$: motoring

(b) $R_a I_a + E_a = V_t \Rightarrow R_a = \frac{V_t - E_a}{I_a} = 0.25 \Omega$

(c) $P_{\text{loss}} = I_a^2 R_a = 40^2 \times 0.25 = 400 \text{ W}$

$P_e = E_a I_a = 230 \times 40 = 9200 \text{ W}$

(d) $T_e = \frac{P_e}{\omega_r} = \frac{9200}{\frac{1200}{60} \times 2\pi} = 73.21 \text{ N}\cdot\text{m}$

(e) $I_a = 0 \text{ A} \Rightarrow E_a = V_t = 240 \text{ V}$
 $\hookrightarrow \omega_r = ?$

$E_a = k_v \omega_r \Rightarrow \star$

$E_{a1} = k_v \omega_{r1}$


$E_{a2} = k_v \omega_{r2}$

$\frac{E_{a1}}{E_{a2}} = \frac{\omega_{r1}}{\omega_{r2}}$
 $\frac{230 \text{ V}}{240 \text{ V}} = \frac{1200 \text{ rpm}}{\omega_{r2}}$
 $\omega_{r2} = 1252 \text{ rpm}$
 4

Example 6


Consider the magnetic system shown below. Assume that reluctance of the core path and the air-gap are $\mathfrak{R}_c = 2 \times 10^5 \text{ At/Wb}$ and $\mathfrak{R}_g = 8 \times 10^5 \text{ At/Wb}$, respectively. The coil has 100 turns and dc resistance $r = 2 \ \Omega$.

- (a) (4pts) Assume the current direction as shown, draw an equivalent **magnetic** circuit, show the direction of mmf F and the flux Φ
- (b) (4pts) Calculate the inductance L
- (c) (12pts) Assume that coil is connected to a 10V(rms) 60-Hz ac source. Calculate the rms values of current I , flux Φ , flux linkage λ .

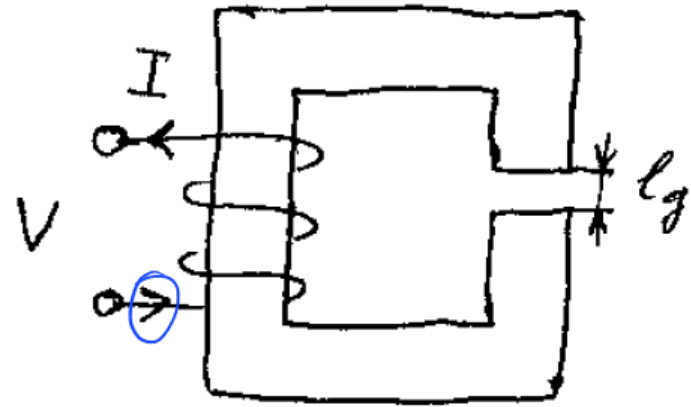

Example 6

(a)

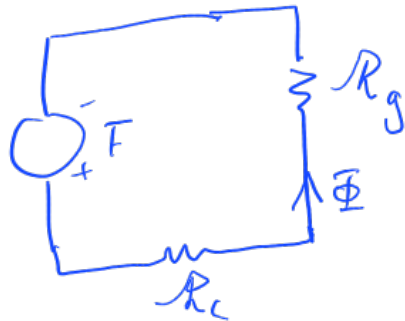

$$F = Ni = \Phi (\underbrace{R_c}_{2 \times 10^5} + \underbrace{R_g}_{8 \times 10^5})$$

$N = 100$

(b)


$$L = \frac{N^2}{R} = \frac{100^2}{R_c + R_g} = 10 \text{ mH}$$

(c) $V_{rms} = 10 \text{ V}$, $f = 60 \text{ Hz}$

$$I_{rms} = \frac{V_{rms}}{|Z|} = \frac{10}{\sqrt{2^2 + [(2\pi 60)(0.01)]^2}} = 2.34 \text{ Arms}$$

$$\rightarrow Z = 2 + j(2\pi 60)(10 \text{ mH})$$

$\uparrow \omega = 2\pi f$

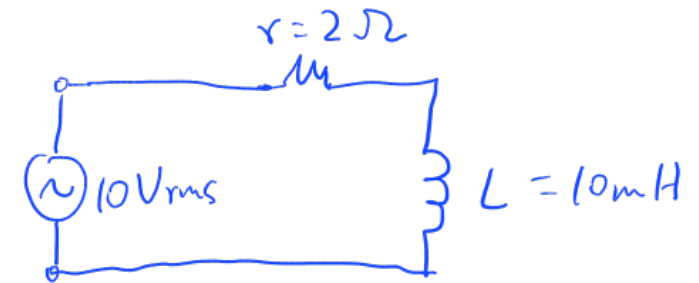



$$\Phi_{rms} = \frac{Ni_{rms}}{R_c + R_g} = \frac{100 \times 2.34}{10 \times 10^5} = 2.34 \times 10^{-4} \text{ Wb}$$

$$\lambda_{rms} = N \Phi_{rms} = 0.0234 \text{ Wb} \cdot \text{t}$$

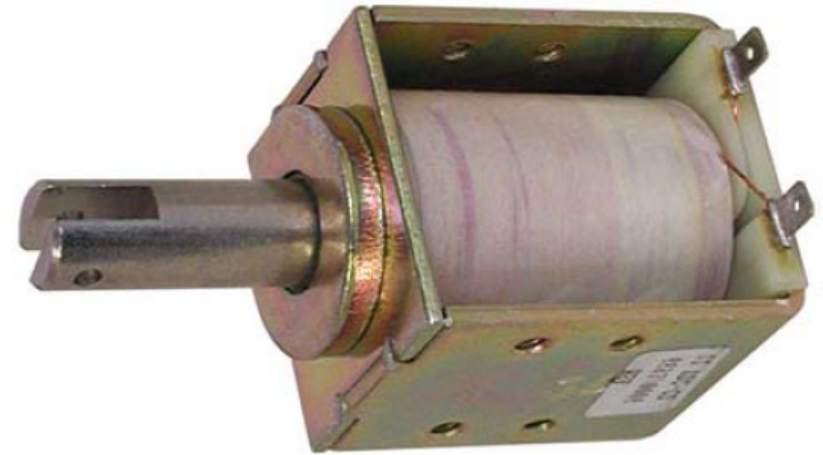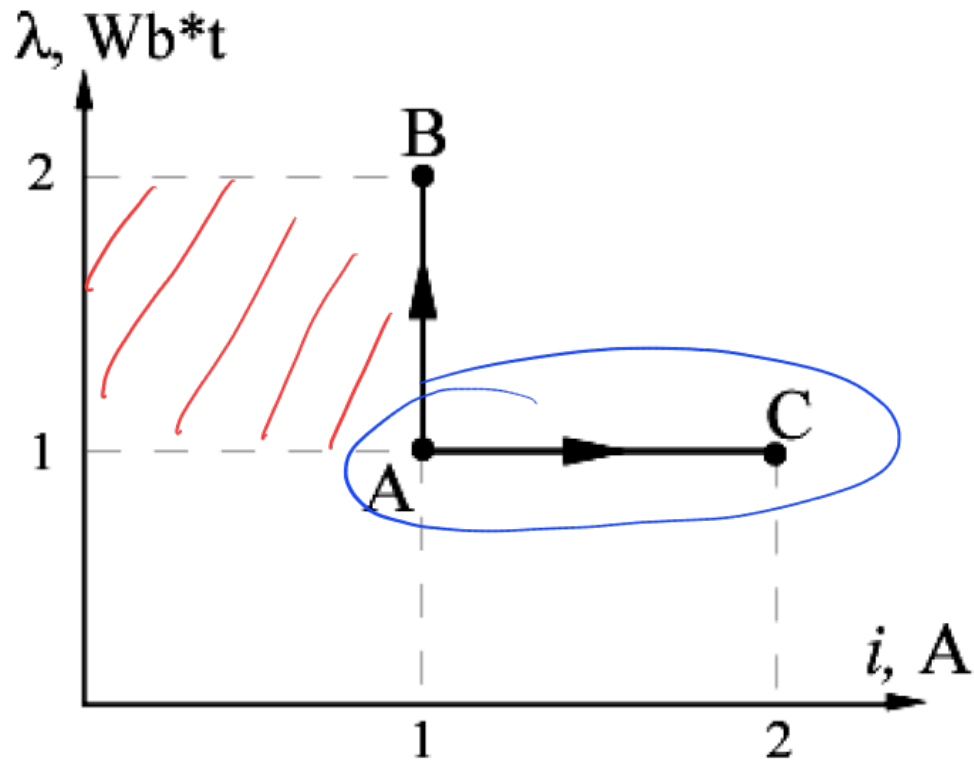Example 7

$$W_f = W_c$$

Assume an electromechanical system with one electrical and one mechanical inputs. The system may be assumed **magnetically linear** (similar to a solenoid). The system's state is shown in the $\lambda - i$ figure below, wherein the system can move from point A to point B, and from point A to point C, respectively. Using the numerical values given on this figure, **calculate the change in** W_f , W_c , W_e , and W_m for the two transitions. In other words, complete the Table given below. **Be sure to include the units and check the energy conversion balance!**



$$\Delta W_e = \int i d\lambda$$

Example 7

Transition	From A to B	From A to C
(3pts) Change in coupling field energy, ΔW_f	$1 - 0.5 = +0.5 \text{ J}$	$1 - 0.5 = +0.5 \text{ J}$
(3pts) Change in co-energy, ΔW_c	$+0.5 \text{ J}$	0.5 J
(3pts) Change in electrical input, ΔW_e	$+1 \text{ J}$	0 J
(3pts) Change in mechanical input, ΔW_m	$\Delta W_e = \Delta W_m + \Delta W_f \Rightarrow \Delta W_m = 0.5 \text{ J}$	-0.5 J
(4pts) The energy was supplied to (and how much)	Coupling field + mechanical system ↓ ↓ 0.5 J 0.5 J	Coupling field 0.5 J
(4pts) The energy was taken from (and how much)	Electrical system 1 J	Mechanical system 0.5 J

Plunger IN or OUT?

IN

OUT

Example 8



Assume that you have three identical 240/120V transformers. The transformers may be assumed ideal. These transformers are connected into Δ/Y to supply a $60\ \Omega$ (per-phase) Y-connected resistor load ~~form~~ ^{from} a 120V (line-to-neutral) source.

- (a) (10pts) Sketch the system and label the input (primary side) terminals with ***ABC*** and the load (output) terminals with ***abc***. Also label the voltages and currents including directions.
- (b) (10pts) Calculate the currents I_A , I_{AB} , the voltages V_a , V_{ab} , the power supplied from the source P_{source} , and the power consumed by the load P_{load} (show that $P_{source} = P_{load}$).

Example 8

(a)

$$a = \frac{240}{120} = 2$$

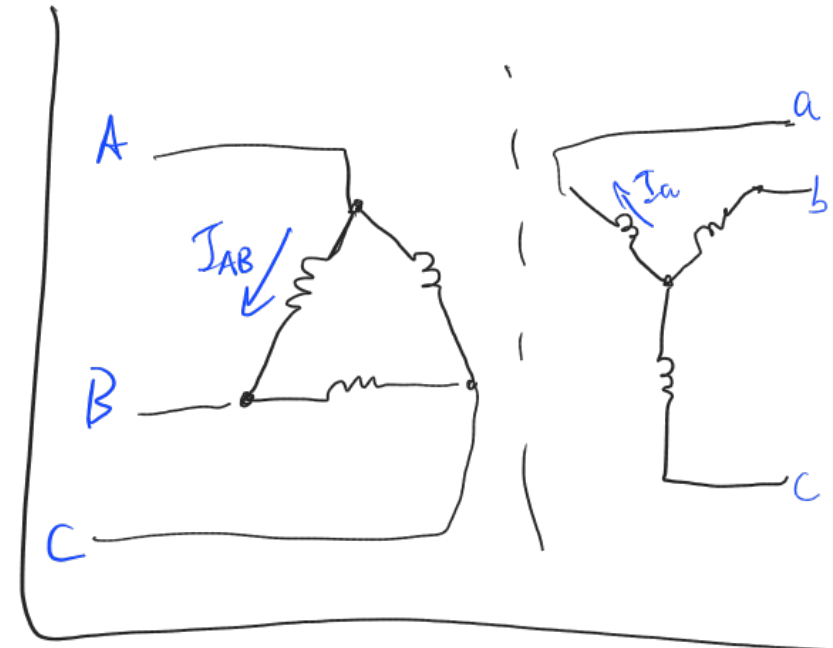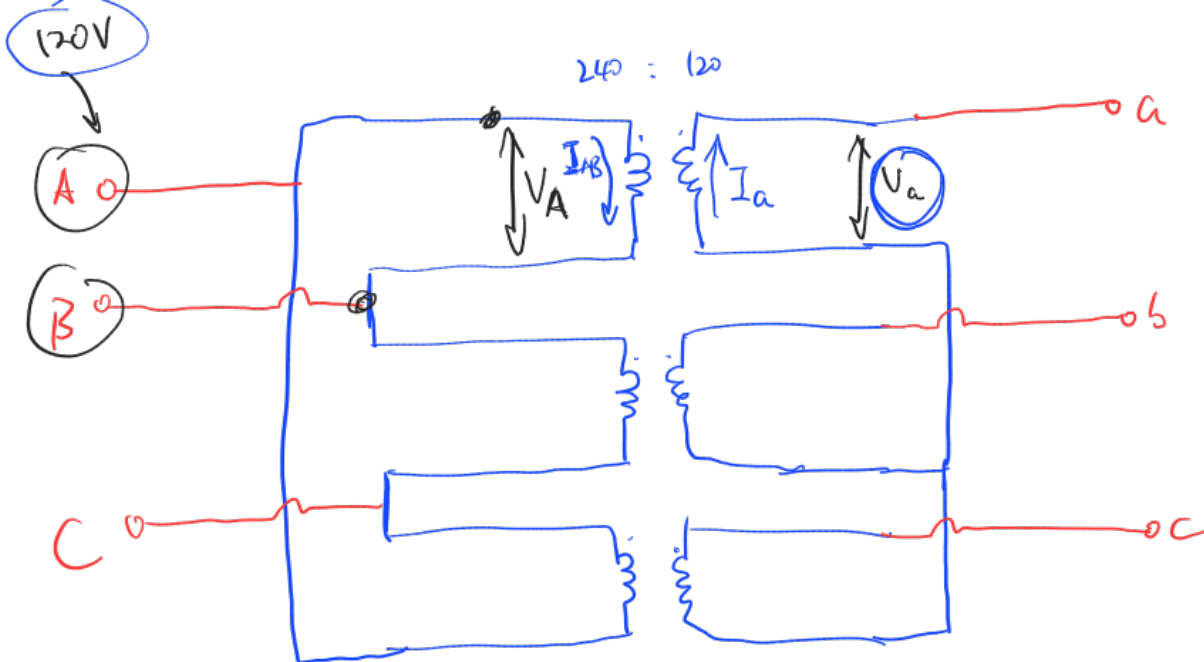

$$(b) \quad V_a = V_A \times \frac{120}{240} = 103.9V$$

$$\hookrightarrow V_{AB} = 120\sqrt{3}$$

$$V_{ab} = \sqrt{3} \times V_a = 180V$$

$$I_{AB} = I_a \times \frac{120}{240} = 0.866A$$

$$\hookrightarrow \frac{V_a}{60} = \frac{103.9}{60}$$

$$I_A = I_{AB} \sqrt{3} = 1.5A$$

$$P_{\text{source}} = V_{LN} \times I_{\text{line}} \times 3$$

$$= 120V \times 1.5A \times 3$$

$$P_{\text{primary}} = 540W$$


$$P_{\text{load}} = \left(\frac{V_a}{Z} \right)^2 \times 3$$

$$= \frac{(103.9V)^2}{60\Omega} \times 3 = 540W$$

Example 9

A 60-Hz **step-up** transformer with $N_1 = 500$ and $N_2 = 1000$ has leakage reactances are $X_1 = 1.2\Omega$, $X_2 = 4\Omega$ (each referred to its own side), and the magnetizing reactance $X_m = 238.8\Omega$ (referred to the primary side). The core and copper losses can be neglected. Assume 120V is applied to the primary side:

- (a) (10pts) Calculate the open-circuit primary current $I_{1,oc}$ and the secondary voltage $V_{2,oc}$ (their rms values)
- (b) (10pts) Assume a resistive load $R_{Load} = 20\Omega$ is connected to the secondary side. Calculate the voltage regulation (VR). Also calculate the input (primary side) power-factor angle ϕ in degrees.

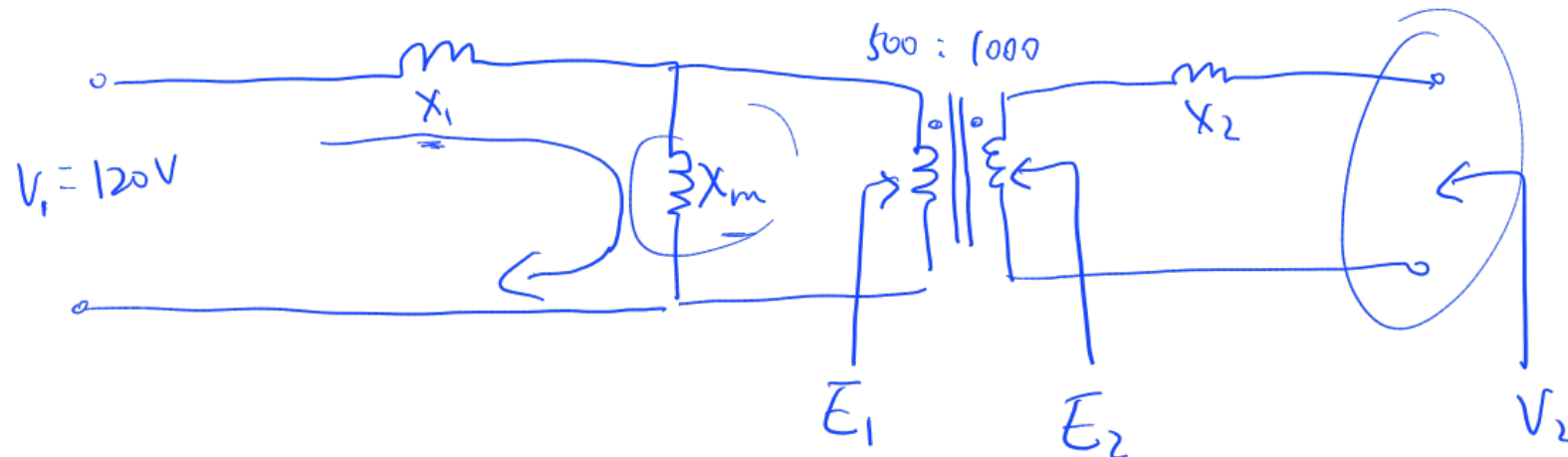


Example 9

$$(a) \quad I_{oc} = \frac{V}{|Z|} = \frac{120}{238.8 + \underline{1.2}} = 0.5 A$$

$$\bar{E}_1 = 120 - 0.5 \times 1.2 = 119.4 V$$


$$\bar{E}_2 = 119.4 \times 2 = 238.8 V \Rightarrow V_{2oc} = \bar{E}_2 = \underline{238.8 V}$$

(b)

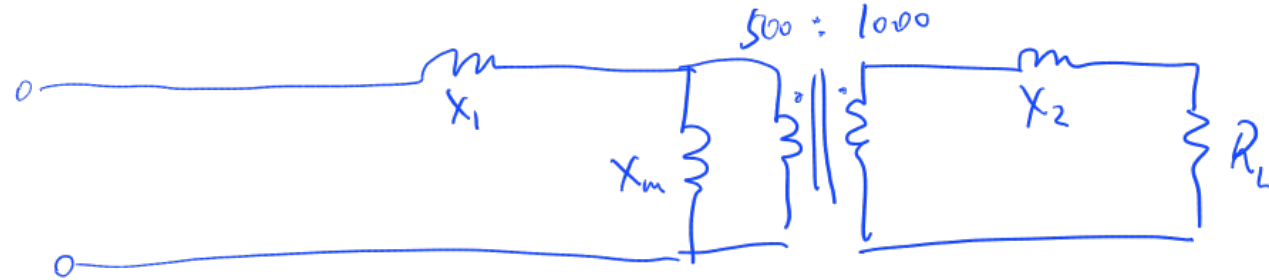

$$X_2' = X_2 \times \left(\frac{1}{2}\right)^2 = 1 \Omega$$
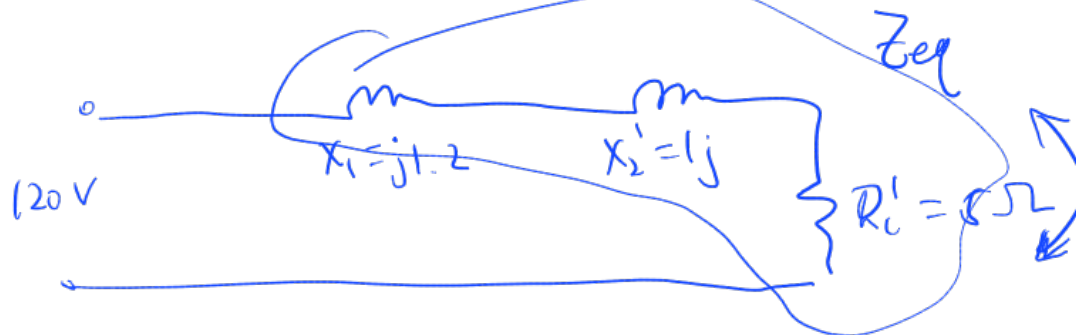
$$R_L' = R_L \times \left(\frac{1}{2}\right)^2 = 5 \Omega$$



$$V_2' \Rightarrow \underline{V_2} = V_2' \times \frac{1000}{500}$$

$$VR = \frac{V_{2oc} - V_2}{V_2}$$

$$V_1 = 120 \angle 0^\circ$$


$$Z_{eq} =$$

$$I_1 = \frac{V_1}{Z_{eq}}$$

Example 10

A DC shunt machine has $R_a = 0.25 \Omega$. The machine is connected to a 250 V DC supply, draws armature current of 40 A, and rotates at 1200 rpm.

- (a) Calculate the induced back emf E_a
- (b) Determine the useful mechanical load torque T_m . The rotational losses are 100 W.
- (c) Determine the efficiency of the motor η . The field circuit resistance is $R_f = 100 \Omega$.

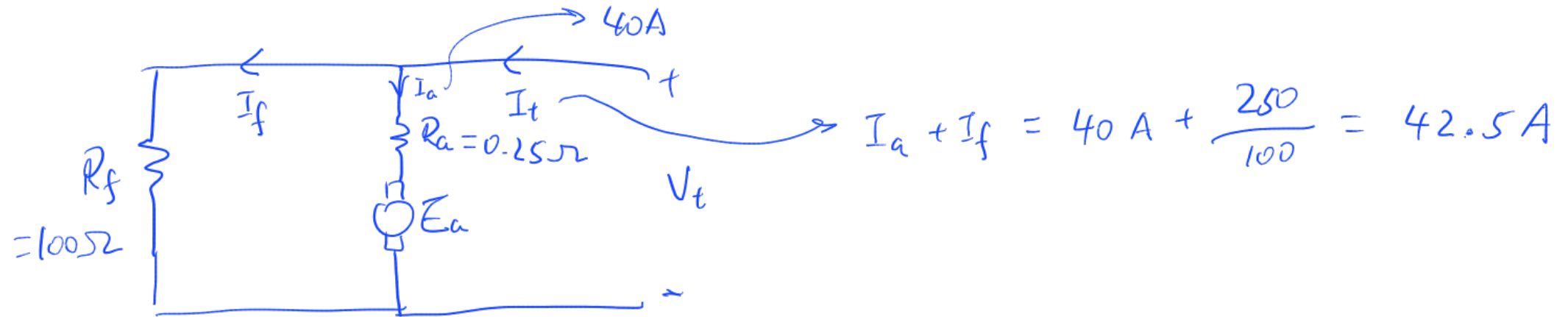

Example 10


$$(a) E_a = V_a - I_a R_a = 250V - 0.25 \times 40 = 240V$$

$$(b) P_e = P_m + P_{\text{loss}} \quad (\text{motoring mode}) \Rightarrow P_m = 9500W$$

$$\begin{array}{c} \uparrow \\ \bar{E}_a I_a \\ \uparrow \quad \uparrow \\ 240 \quad 40 \end{array}$$

$$\begin{array}{c} \uparrow \\ P_{\text{loss}} \\ 100W \end{array}$$
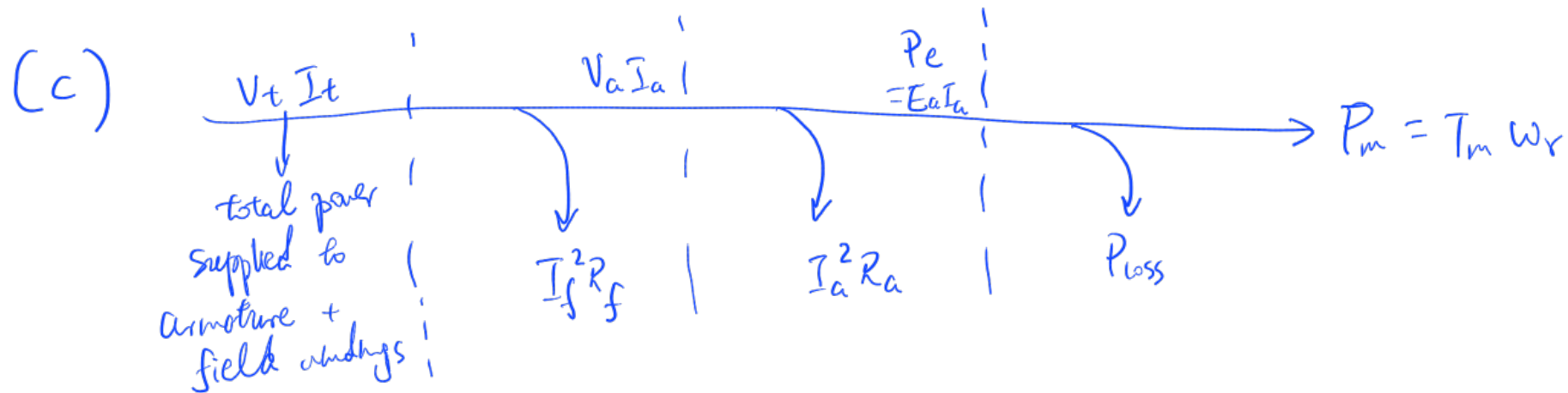
$$T_m = \frac{P_m}{\omega_r} = \frac{9500W}{\frac{1200}{60} \times 2\pi} = 25.6 \text{ Nm}$$




$$\eta = \frac{P_m}{V_t I_t} = \frac{9500}{250 \times 42.5} = \frac{9500}{10625} = 89.4\%$$

Example 11

Consider a 115V **Separately-Excited DC Machine** with the armature resistance $R_a = 1\Omega$ and field-to-armature inductance $L_{af} = 0.111\text{H}$. The machine is supplied from a constant dc source $V_t = 115\text{V}$ and the shaft is connected to a mechanical system with constant speed $n = 1800\text{ rpm}$ in **CCW** direction. Friction can be neglected.

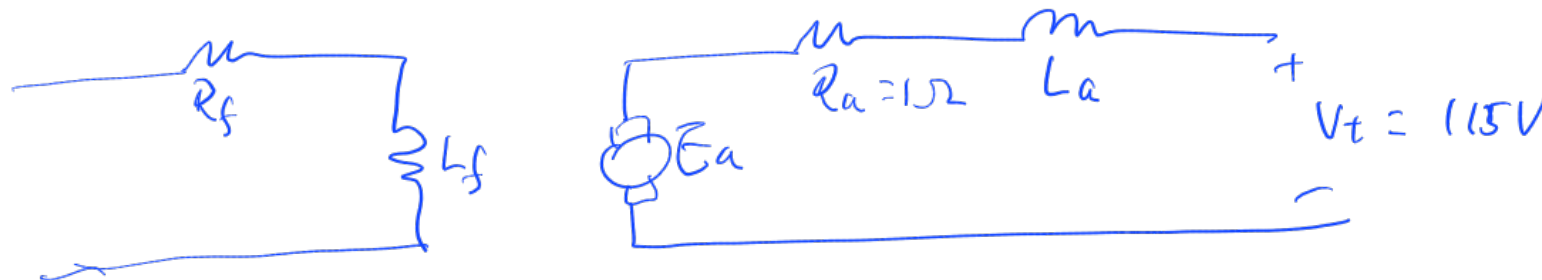- (a) (4pts) Draw an equivalent circuit
- (b) (8pts) The field current is set to $I_f = 5\text{ A}$. Calculate the armature current I_a and torque T_e . Determine whether machine is motoring or generating. Is T_e in CW or **CCW** direction? (circle one)
- (c) (8pts) The field current is increased to $I_f = 6\text{ A}$. Calculate the armature current I_a and torque T_e . Determine whether machine is motoring or generating. Is T_e in **CW** or CCW direction? (circle one)



$$L_{af} = k_a \frac{L_f}{N_f} = 0.111\text{H}$$

Example 11

$\rightarrow k_t \omega_r$ (PM)

(b) $I_f = 5 \text{ A}$


$$\bar{E}_a = L_{af} I_f \omega_r = 0.111 \times 5 \times \frac{1800 \times 2\pi}{60} = 104.6 \text{ V}$$

$$\bar{E}_a < V_t \Rightarrow \text{motoring}$$


$$I_a = \frac{V_a - \bar{E}_a}{R_a} = 10.38 \text{ A}$$

$$T_e = L_{af} I_f I_a = 0.111 \times 5 \times 10.38 = 5.76 \text{ N}\cdot\text{m}$$

$\Downarrow$
CCW

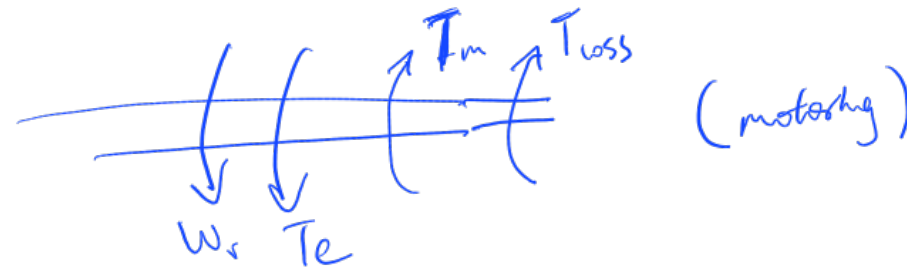

(c)
 $I_f = 6 \text{ A}$

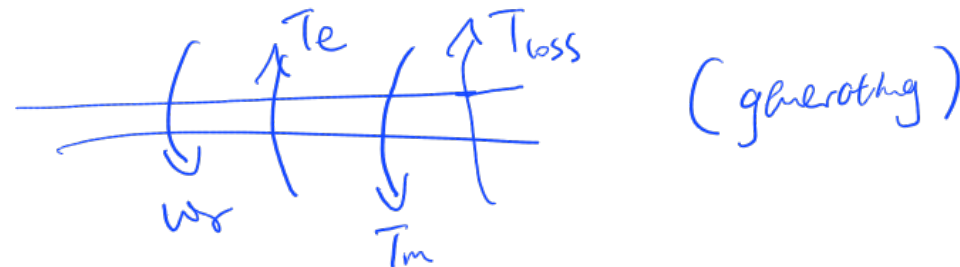

$$\bar{E}_a = 125.53 \text{ V} > 115 \text{ V} \rightarrow \text{generating}$$


$$I_a = 10.532 \text{ A} = \frac{\bar{E}_a - V_a}{R_a}$$

$$T_e = 7.014 \text{ N}\cdot\text{m} \Rightarrow \text{CW}$$

Example 12

Consider a **Permanent-Magnet DC Motor** with the following parameters: rated/nominal voltage $V_t = 12\text{ V}$; armature resistance $R_a = 1.2\ \Omega$. Under the NO-LOAD test the armature current is $I_{a_nl} = 0.2\text{ A}$ and the motor speed is $n_{nl} = 1800\text{ rpm}$.

- (a) (10pts) Calculate the induced armature emf E_{a_nl} , torque constant K_t , and the friction torque T_{fric}
- (b) (10pts) Assume T_{fric} is constant (doesn't depend on speed). A mechanical load with the torque $T_m = 4 \cdot T_{fric}$ is connected to the motor shaft. Calculate the motor speed n in rpm and speed regulation SR in %

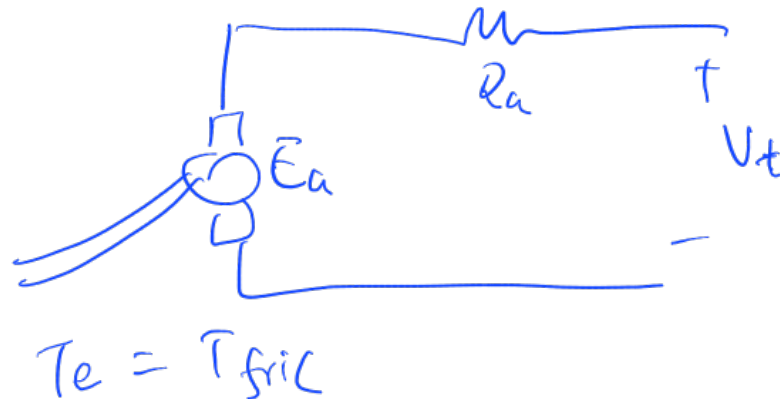

Example 12

(a) No load: $T_e = T_{fric}$

$$V_t - R_a I_a = 12 - 1.2 \times 0.2 = 11.76 V = E_a$$

$$E_a = k_t \omega_r \Rightarrow k_t = \frac{E_a}{\omega_r} = 0.0624$$

$$T_e = k_t \times I_a = 0.0125 N \cdot m = T_{fric}$$

(b) $T_{fric} = 0.0125 N \cdot m$

$$T_m = 4 \cdot T_{fric} \text{ (given)}$$

$$T_e = T_m + T_{fric} = 0.0625 N \cdot m$$

$$I_a = \frac{T_e}{k_t} = 1 A$$

$$E_a = 12 - 1.2 \times 1 = 10.8 V \Rightarrow \omega_r = \frac{E_a}{k_t} = 173.08 \text{ rad/s}$$

$$SR\% = \frac{\omega_{nl} - \omega_r}{\omega_r} = 8.9\%$$

Looking ahead...

- Start **Module 5**