

ELEC 342

Electromechanical Energy Conversion and Transmission

2025-26 Winter Term 2

Lecture 16

March 10, 2026

Zhi Jin (Justin) Zhang

Course Logistics


- Tutorial resumes this week
- Lab 3 takes place this week
- Assignment 5 posted
- Midterm available to pick up
- Quizzes
 - Quiz 3: March 20 at the beginning of the tutorial
 - Quiz 4: April 2 at the beginning of the lecture

Principle of Operation (Idle mode)

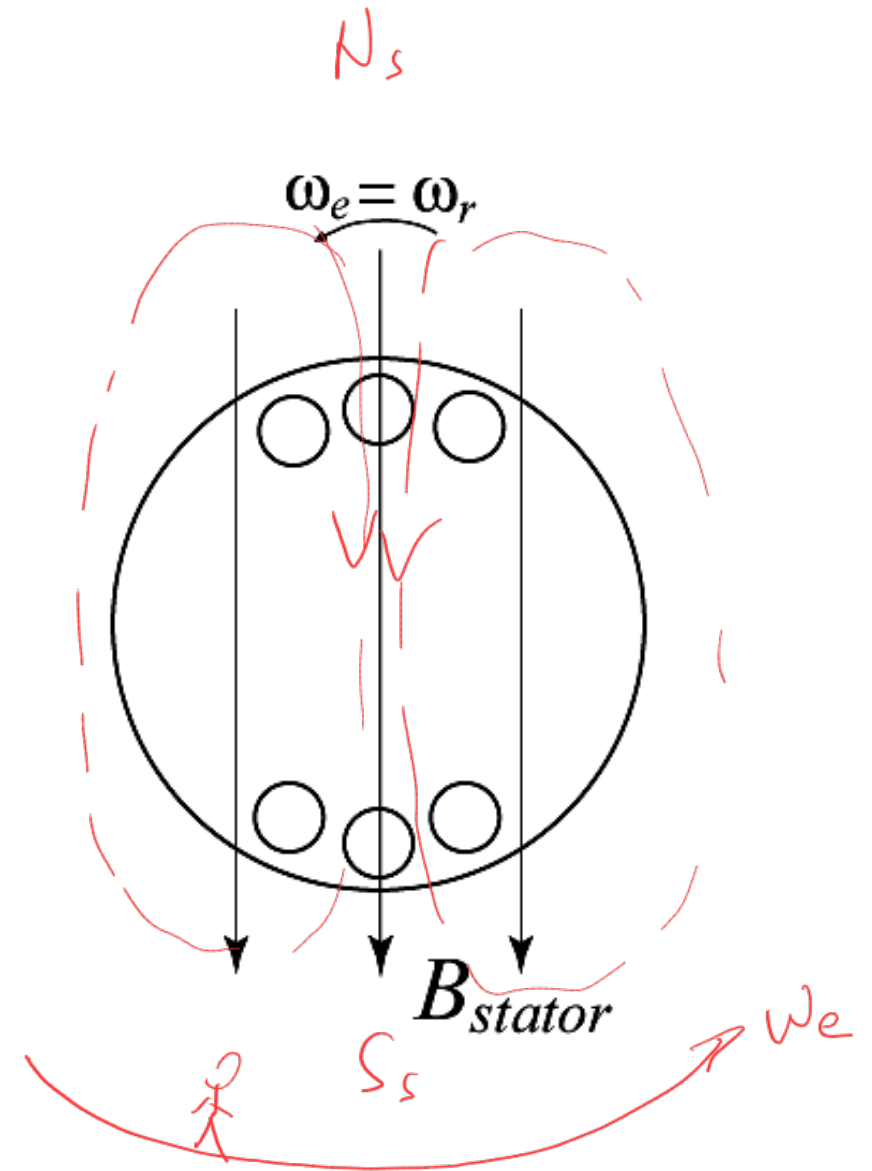a) Assume synchronous speed $\omega_r = \omega_e$

$$s = \frac{\omega_e - \omega_r}{\omega_e} = 0 \Rightarrow \omega_s = \phi$$


- Rotor bars do not cut magnetic flux - $\frac{d\lambda}{dt} = 0$
- No current induced
- No torque produced



Principle of Operation (motor)

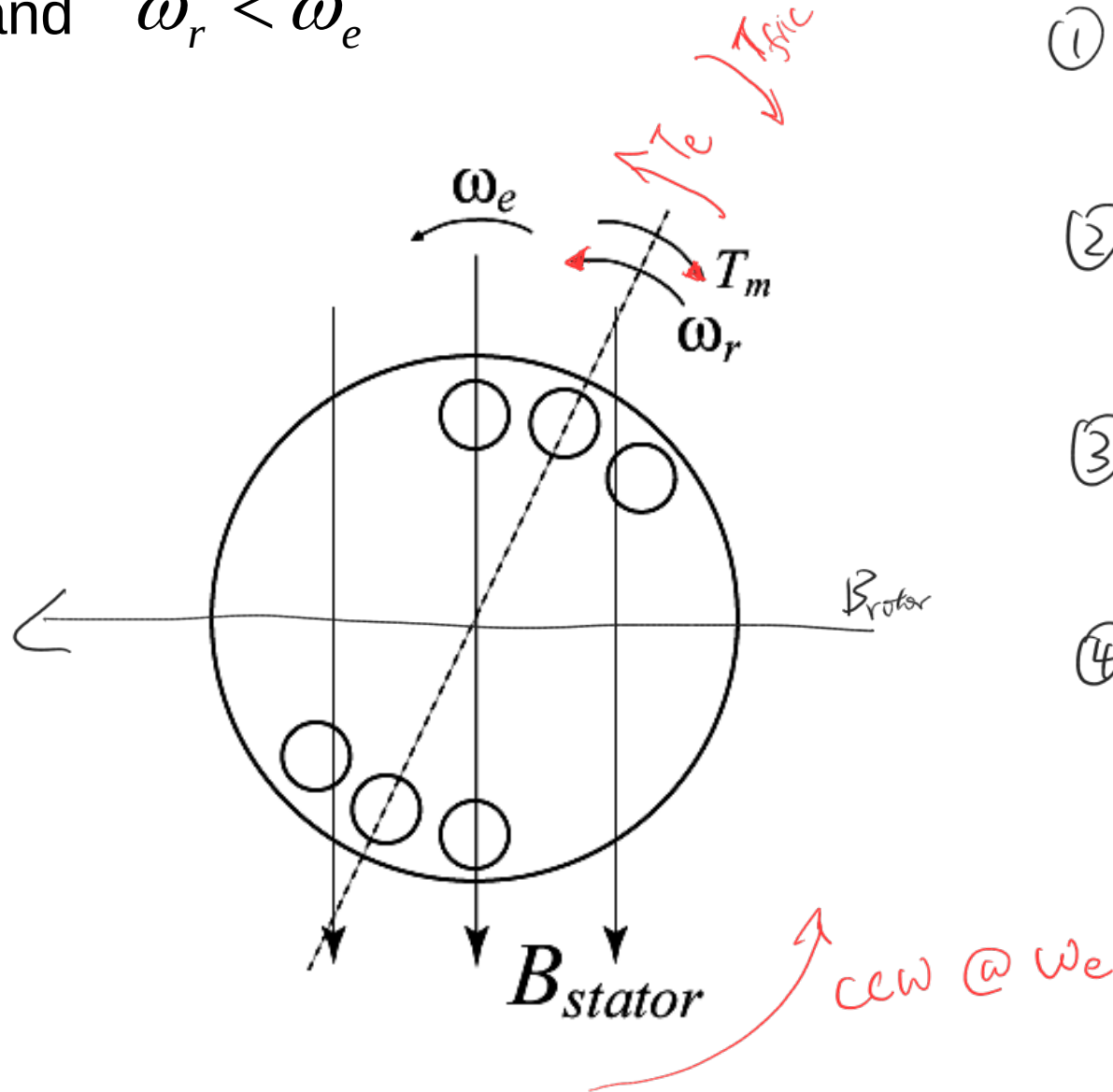b) Assume $T_m > 0$ and $\omega_r < \omega_e$

$$s = \frac{\omega_e - \omega_r}{\omega_e} > 0$$



4 speeds:



- ① Stator speed
(air gap)
- ② Rotor/shaft speed
 ω_r
- ③ Rotor current frequency
 ω_s
- ④ Rotor field speed
 - (a) Rotor frame: ω_s
 - (a) Stationary frame:
 $\omega_s + \omega_r = \omega_e$

B_r and B_s are 90° apart

Principle of Operation (generator)

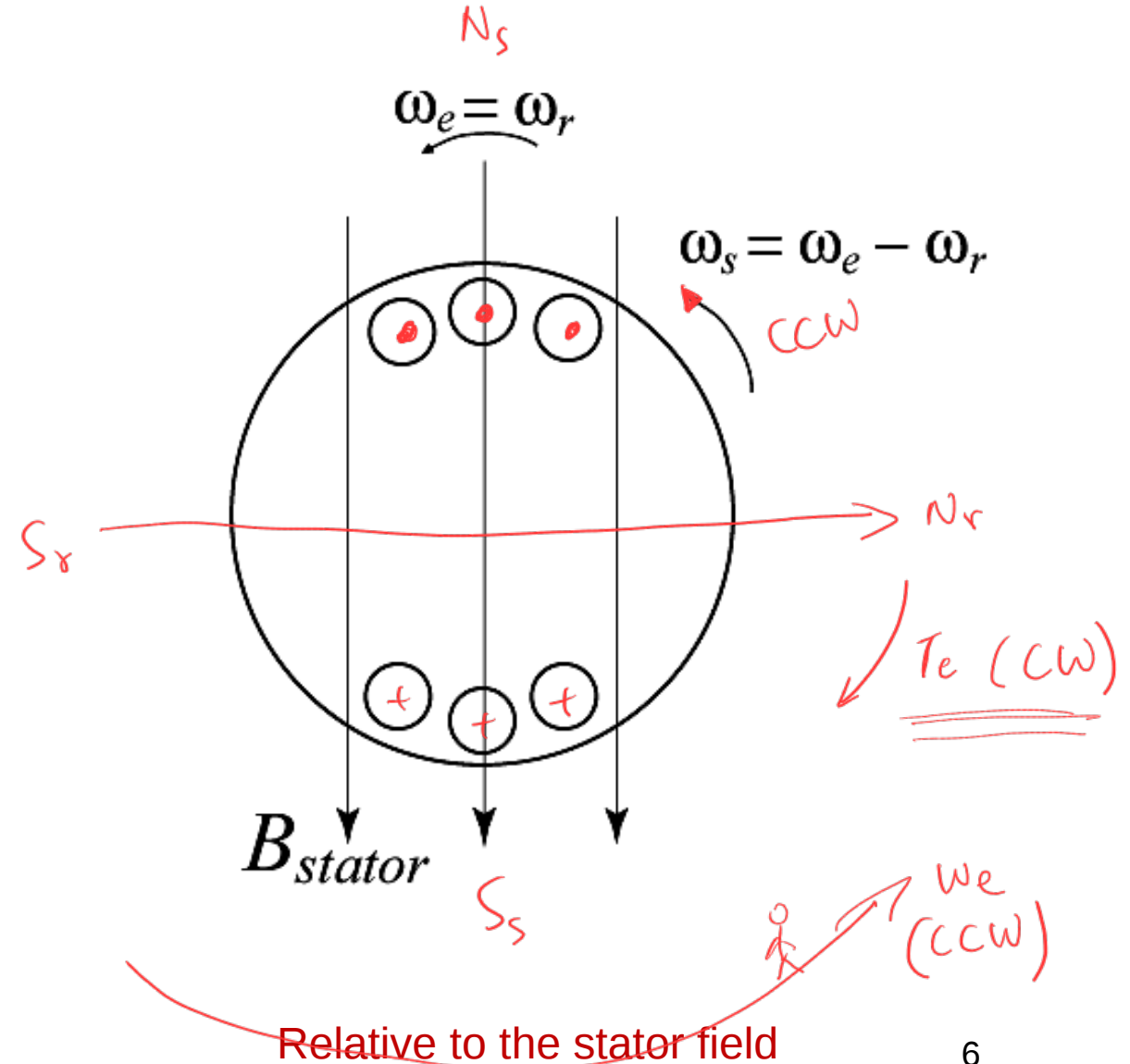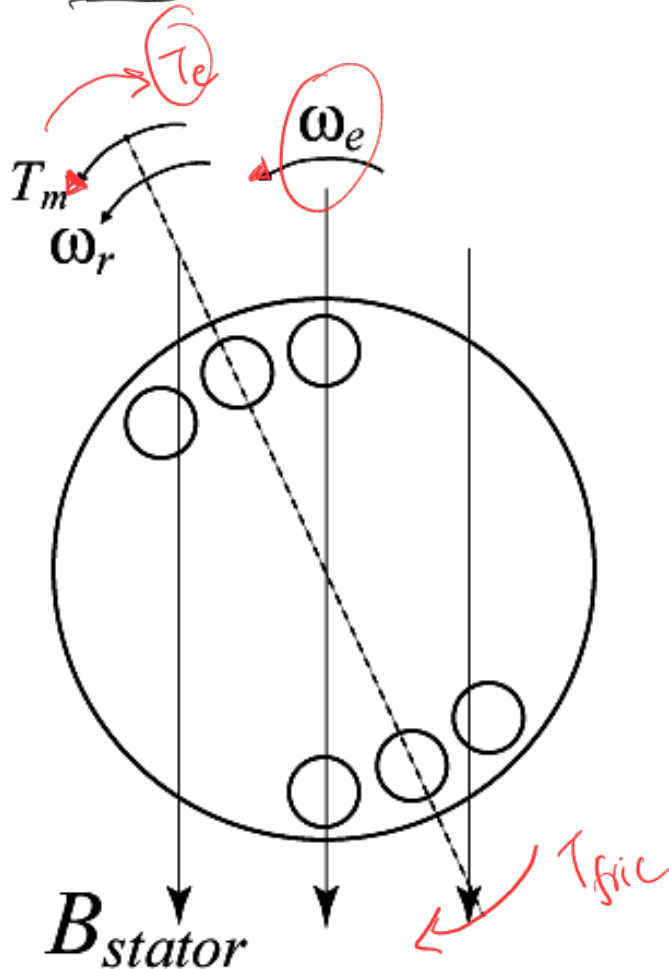c) Assume $T_m < 0$ and $\omega_r > \omega_e$

$$s = \frac{\omega_e - \omega_r}{\omega_e} < 0$$



Speeds in Induction Machines

❖ **Example 1:** A 3-phase, 60 Hz, four-pole induction **generator** operates at slip of 5%. Determine:

- ↓

Slip > 0 (motor)
Slip < 0 (gen)
- {

(a) Synchronous speed $n_{sync.} = 60 \times 60 \times \left(\frac{2}{p}\right) = 1800 \text{ rpm (CCW)}$

(b) Shaft speed $n_r = 1800 (1 + 0.05) = 1890 \text{ rpm (CCW)}$

(c) Speed of the rotating air-gap field 1800 rpm

(d) Frequency of the rotor currents $f_r = s \cdot f_s = 5\% \times 60 = 3 \text{ Hz}$

(e) Slip in rpm $n_{slip} = 90 \text{ rpm} (1800 \text{ rpm} \times 5\%)$

(f) Speed of the rotor field relative to:

(i) rotor body (you see rotor current freq = $\omega_s \Rightarrow \underline{B_r} \Rightarrow \omega_s$) $\Rightarrow \underline{90 \text{ rpm (CW)}}$

(ii) stator body $1800 \text{ rpm} \Rightarrow \omega_r + \omega_s = 1890 - 90 = 1800 \text{ rpm}$


(iii) stator rotating field $\emptyset \text{ rpm}$
- stand on rotor

stand outside


stand on B_s

Linear Induction Motors (LIM)



✓ Running Magnetic Field

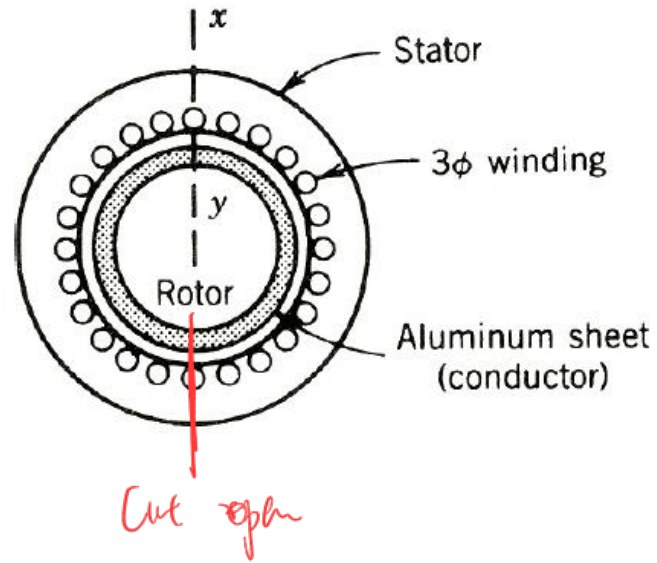

unroll the rotary machine

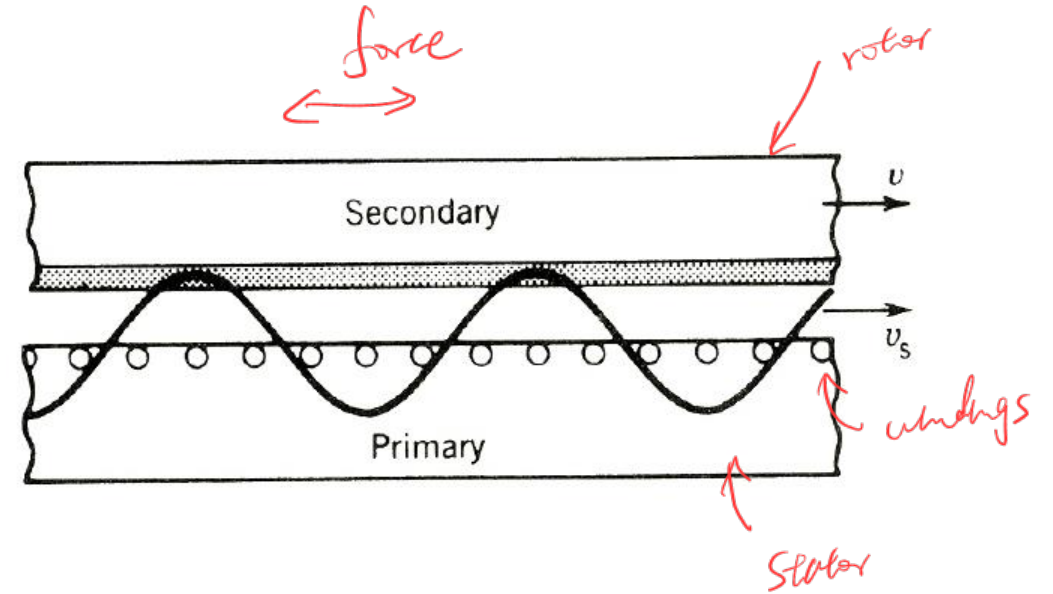

✓ Train Propulsion System

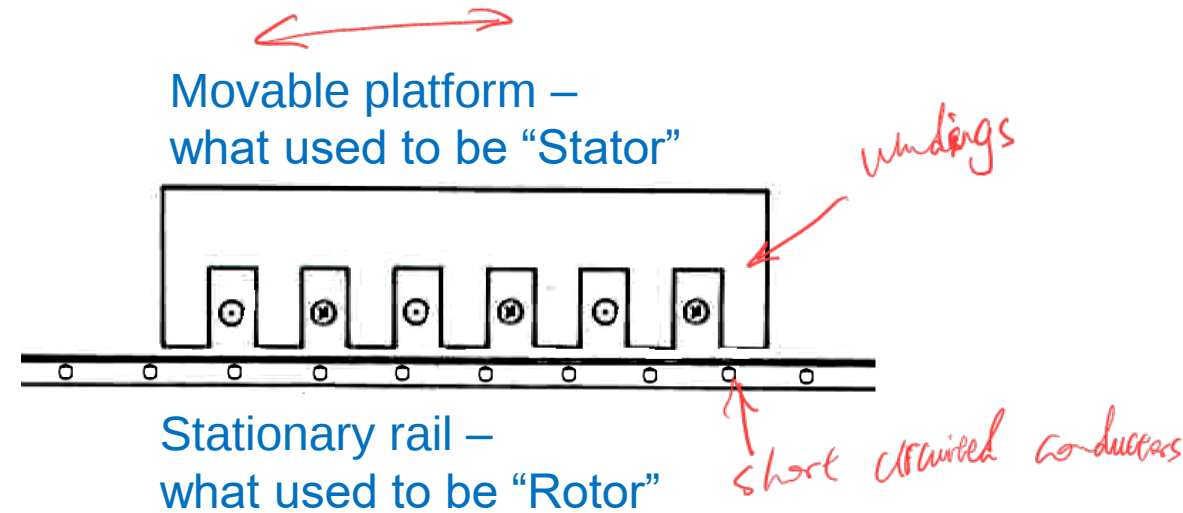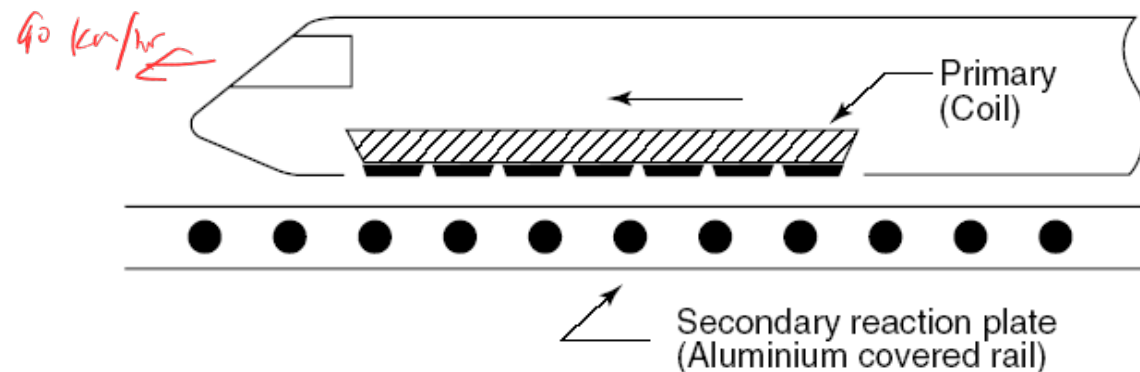

Linear Induction Motors (LIM)



Millennium Line



- Propulsion System
- Motors react with aluminum-capped steel rail on the guideway
- LIM provide both propulsion and regenerative braking
- No moving parts
- Reduced maintenance and risk of mechanical failure

reaction rails (short circuited conductors)

They can change # of poles and we on the fly (power electronics)

Basic Analysis: Example 2

Consider a 25hp, 3-phase, 220V, 60Hz Ind. Motor. At full load we have:

$$P_{in} = 20.8\text{kW}; \quad P_{out} = 25\text{hp}; \quad I_1 = 64\text{A}; \quad n = 830\text{rpm};$$

Find: number of poles p , slip s , frequency f_2 , power factor pf , torque T_m , and efficiency η

Number of poles P

$$n_{syn} = \frac{120}{p} \cdot f_e; \quad p = \frac{120 f_e}{n_{syn}} = \left\lfloor \frac{120 f_e}{n} \right\rfloor$$

rotor current *floor operator*

$$p = \left\lfloor \frac{120 \cdot 60}{830} \right\rfloor = \left\lfloor 8.67 \right\rfloor = 8; \quad n_{syn} = 900\text{rpm}$$

Slip s $s = \frac{n_{syn} - n}{n_{syn}} = \frac{900 - 830}{900} = 0.0778 = 7.78\%$

Frequency of rotor currents f_2

$$f_2 = s \cdot f_e = 0.0778 \cdot 60 = 4.67\text{Hz}$$

Power factor $\text{pf} = \cos\phi = \frac{P_{in}}{\sqrt{3} \cdot V_L \cdot I_L} = \frac{20.8\text{kW}}{\sqrt{3} \cdot 220 \cdot 64} = 0.853$

Torque T_m $T_m = \frac{P_{out}}{\omega_{rm}} = \frac{30}{\pi} \cdot \frac{25 \cdot 746}{830} = 214\text{N}\cdot\text{m}$


Efficiency η $\eta = \frac{P_{out}}{P_{in}} = \frac{25 \cdot 746}{20.8\text{kW}} = 0.8966 = 89.66\%$

P	n_{sync}
2	3600
4	1800
6	1200
8	900
10	...


Steady-State Equivalent Circuit

- Assume rotor has the same number of phases as stator (3-ph)

IM is NOT
a three-phase
transformer

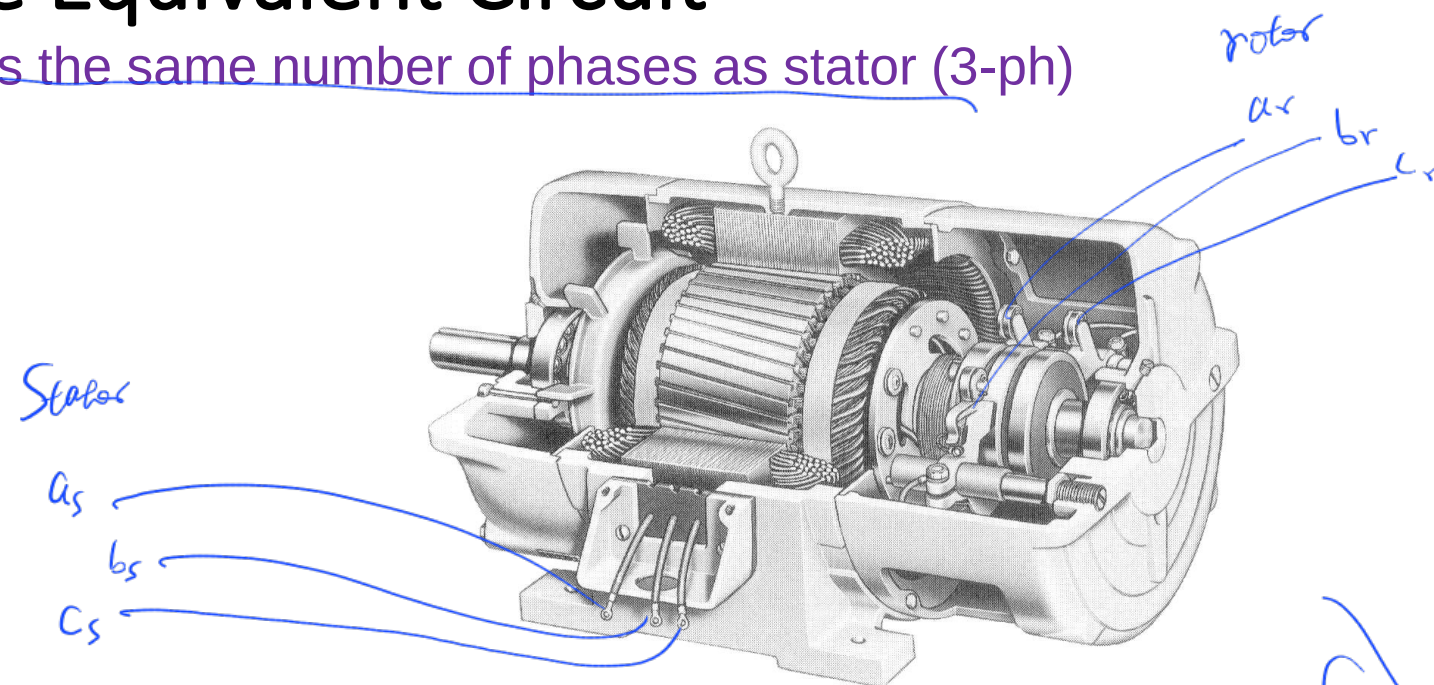


3-phase
transformer

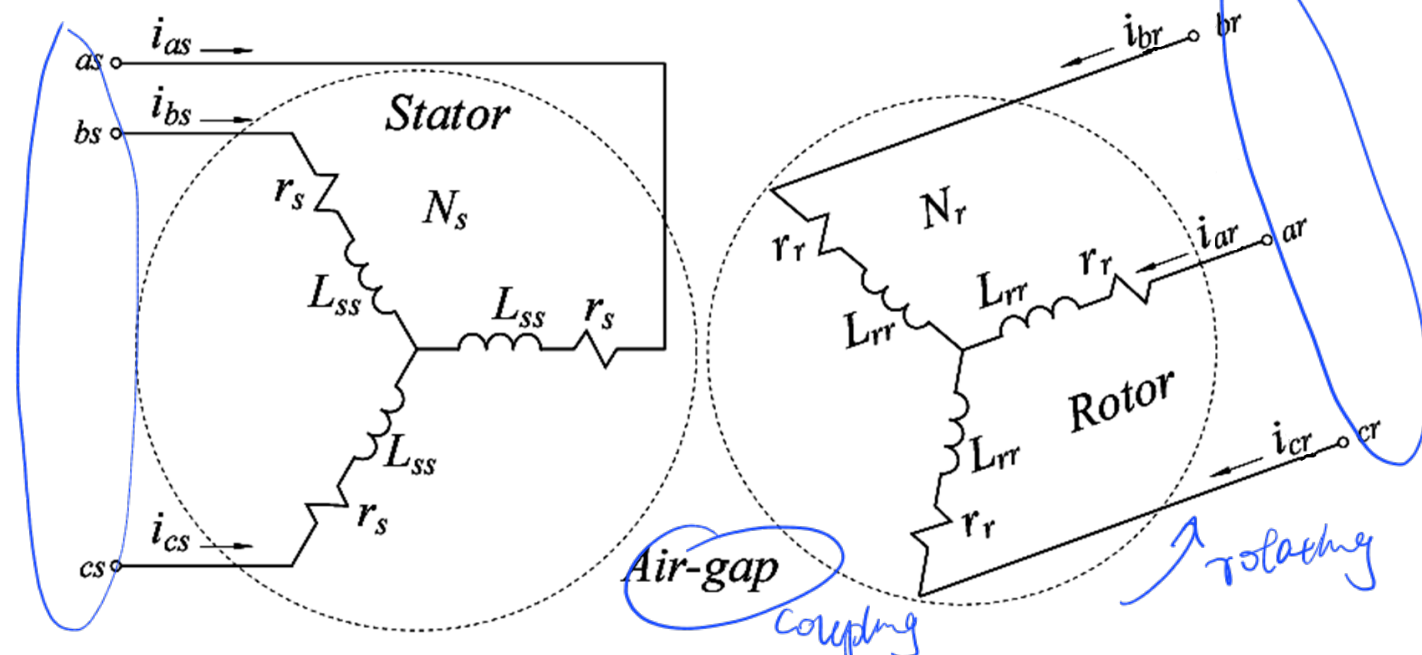

Steady-State Equivalent Circuit

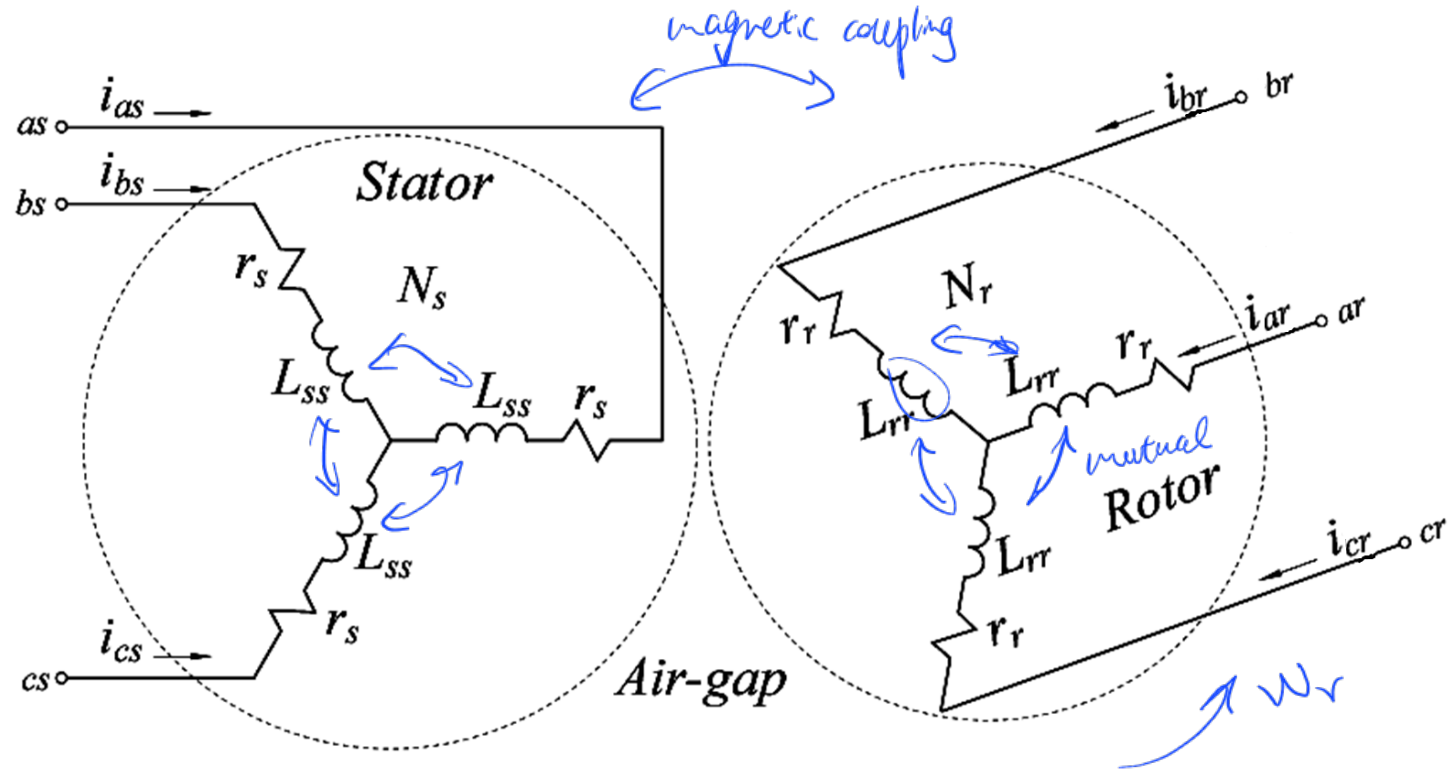- Assume rotor has the same number of phases as stator (3-ph)





- Rotor winding (circuit) operates at different frequency $f_r = s \cdot f_e$
- Rotor circuit is typically shorted (squirrel-cage)
- Motor is like a 3-phase transformer (But it is NOT a 3- ϕ TF)
- Develop equivalent circuit per-phase
- Extend the results to 3-phase

Stator Equivalent Circuit (Primary)

In order to simplify notation we can assume

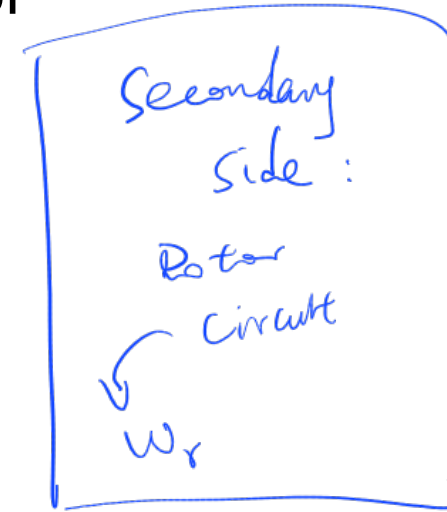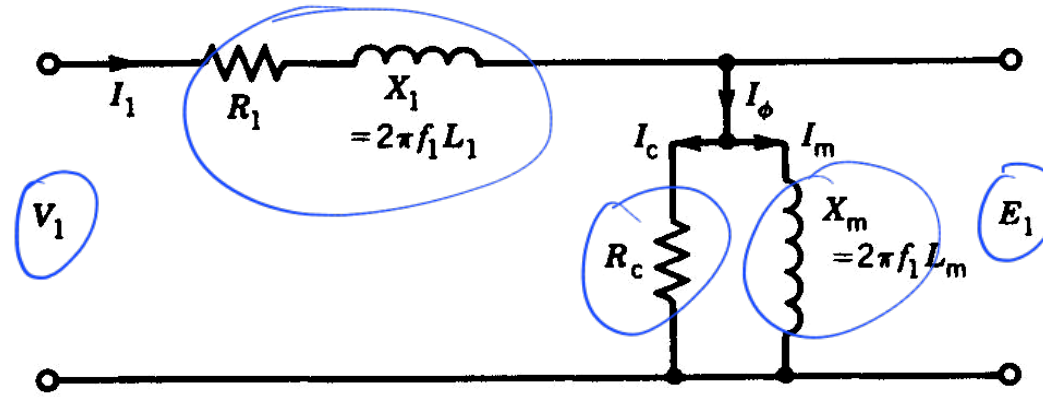- Rotor has the same number of phases as stator (3-ph)
- Rotor winding has the same number of turns as stator



V_1 = per-phase terminal voltage

R_1 = per-phase stator winding resistance

X_1 = per-phase stator winding leakage reactance


X_m = per-phase magnetizing reactance

R_c = per-phase core losses equivalent resistance

f_s


Goal: develop a
 T -circuit

Rotor Equivalent Circuit (Secondary)

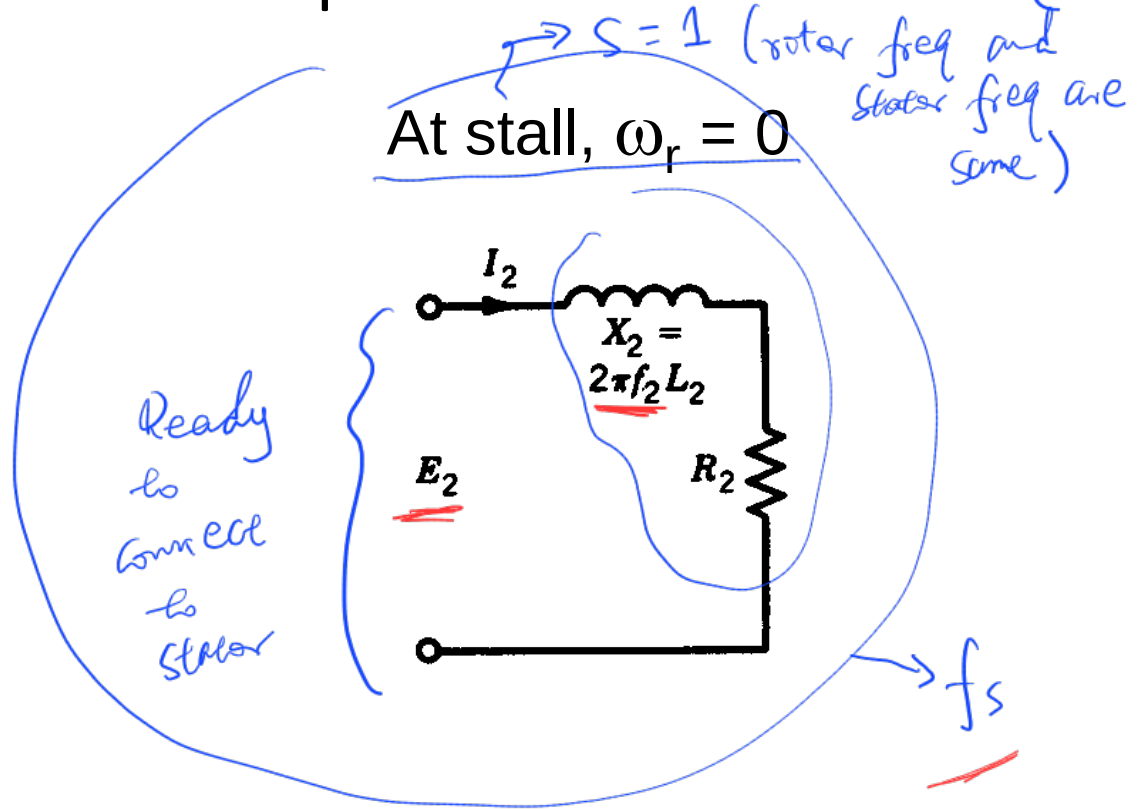

When rotor moves, ω_r

$\rightarrow$ Rotor freq = $s \cdot f_s$

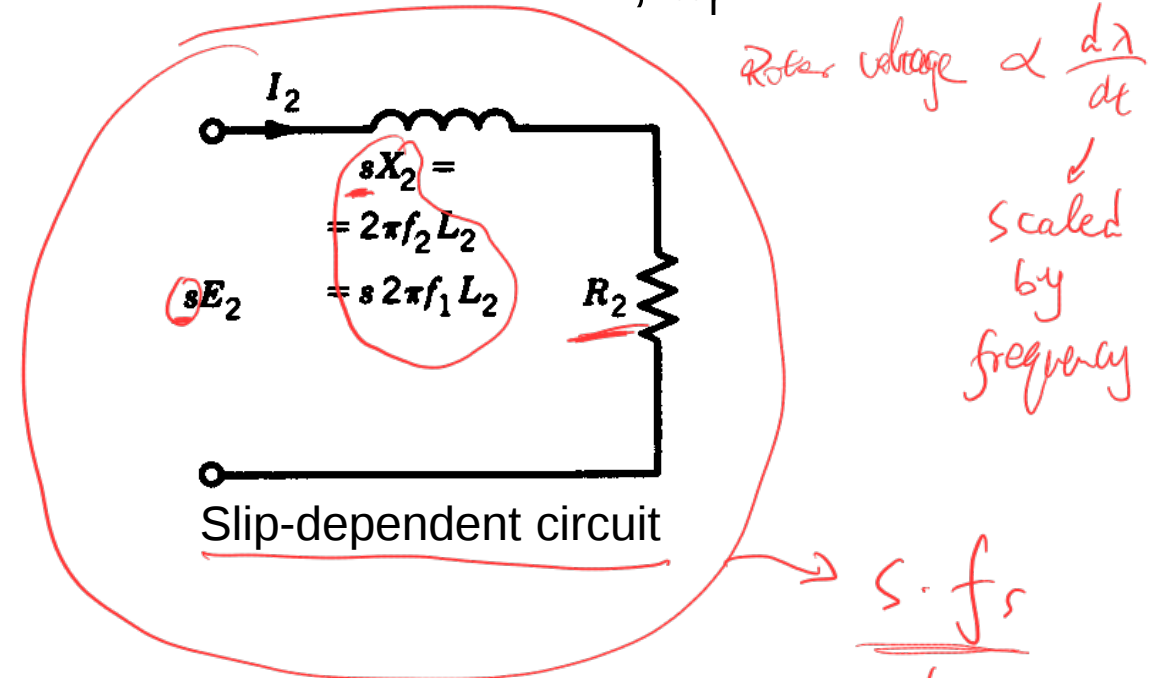

E_2 = per-phase induced voltage in the rotor at $\omega_r = 0$

R_2 = per-phase rotor winding resistance


L_2 = per-phase rotor winding leakage inductance

X_2 = per-phase rotor winding leakage reactance


to convert to stator circuit freq (f_s), divide everything by s

Overall Equivalent Circuit

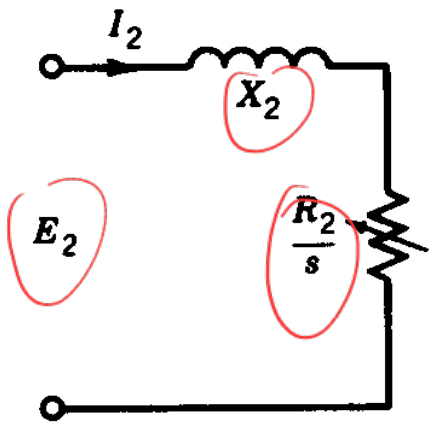Assume that the rotor rotates with speed ω_r




Normalized by the slip s

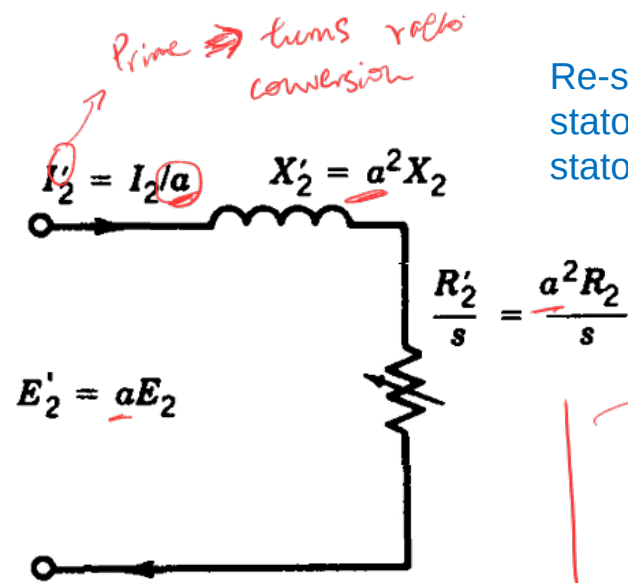

Re-scale the rotor circuit to the stator side using the equivalent stator-to-rotor turns-ratio $a = N_s/N_r$

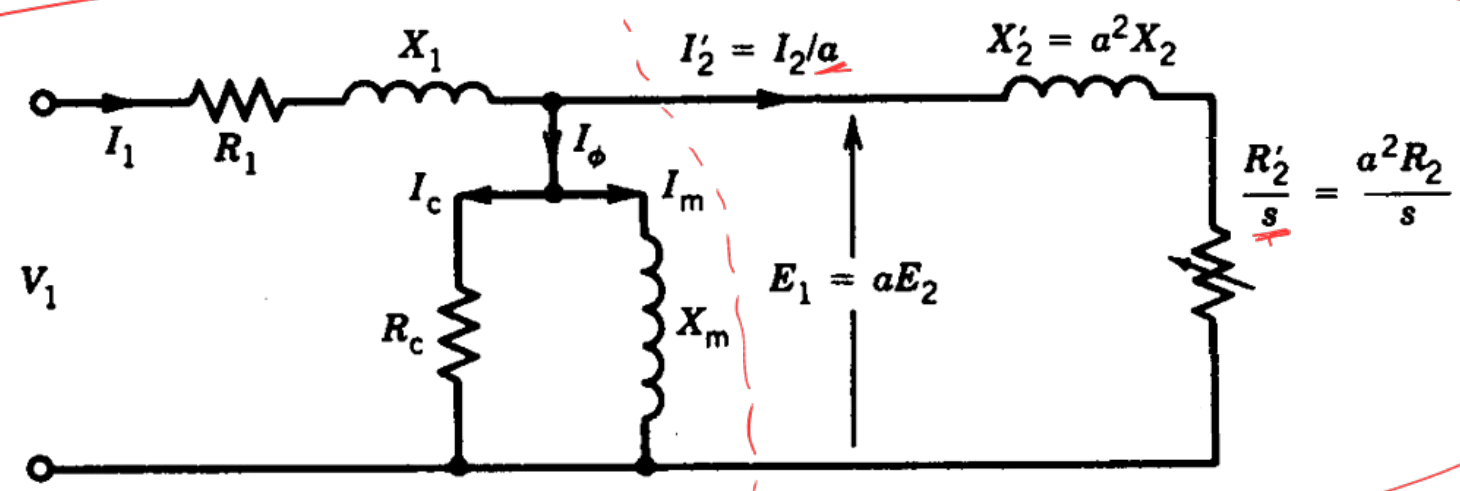
$\omega_r = 0 \Rightarrow s = 1$
 $\omega_r = \omega_e \Rightarrow s = \phi$



T - equivalent of IM per phase


Combine with the stator part of the equivalent circuit

Practical Equivalent Circuits

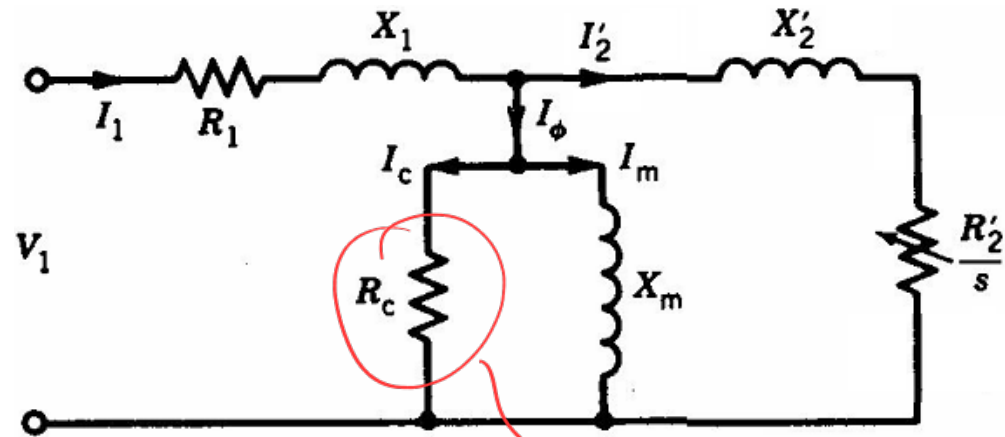

Real power consumed by the rotor (part of which is converted to creating torque, and part is dissipated as rotor winding loss)

Lumped with T_{fric}

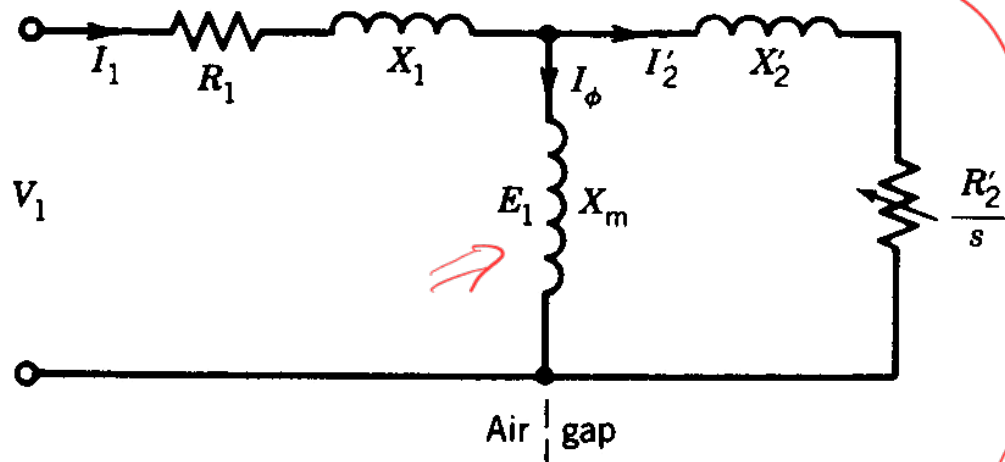

Commonly used (IEEE recommended)


T-equivalent circuit (looks just like a transformer with shorted secondary side)

without R_c

Core losses are combined with rotational losses


Thevenin Equivalent and Approximate Circuits

Full equivalent circuit

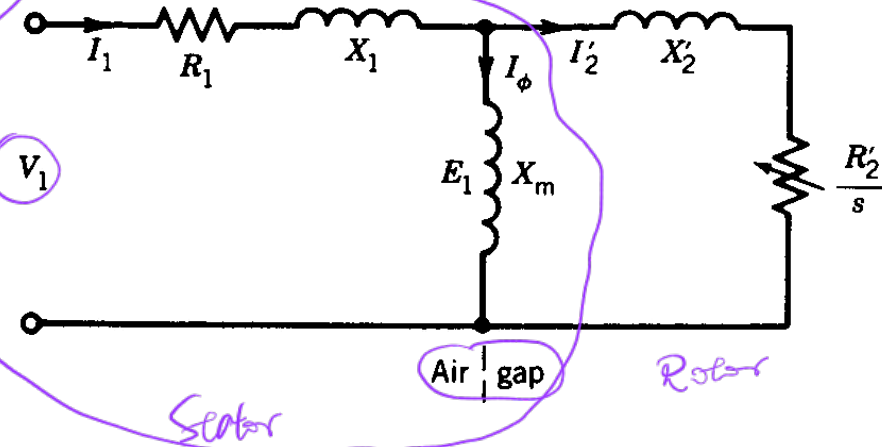


Approximate equivalent circuit

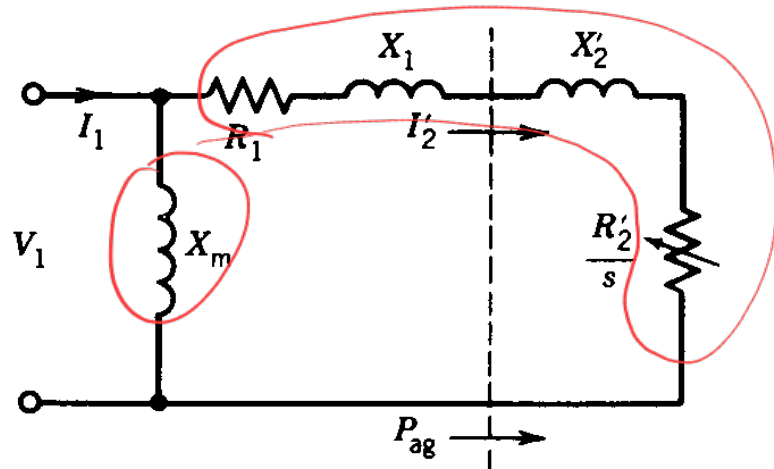Move magnetizing branch to input terminals



Thevenin equivalent circuit

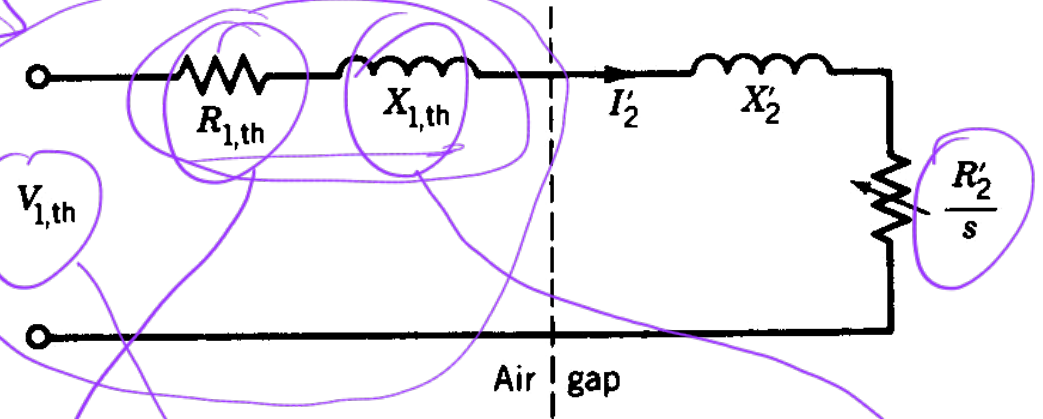Recalculate parameters to remove magnetizing branch





$$V_{1,th} = \frac{X_m}{\sqrt{R_1^2 + (X_1 + X'_m)^2}} V_1$$

$$Z_{1,th} = \frac{jX_m (R_1 + jX_1)}{R_1 + j(X_1 + X_m)} = \alpha + j\beta$$

$$= R_{1,th} + jX_{1,th}$$

Determining Machine Parameters *→ Lab 4*

Consider Full Equivalent Circuit

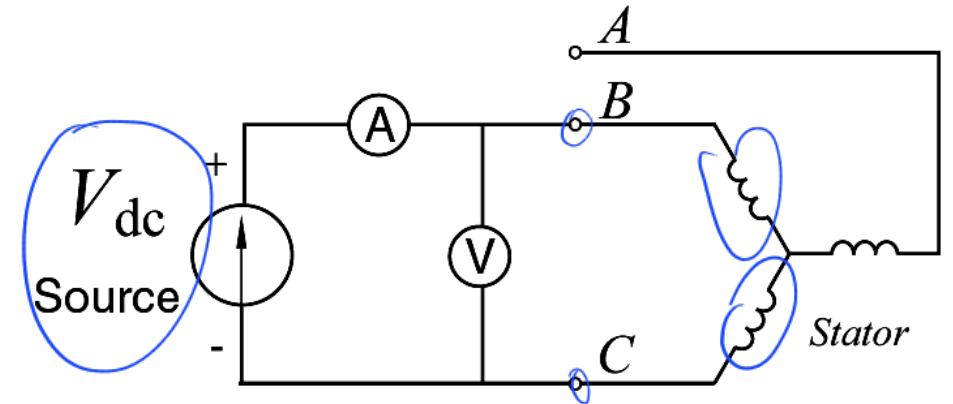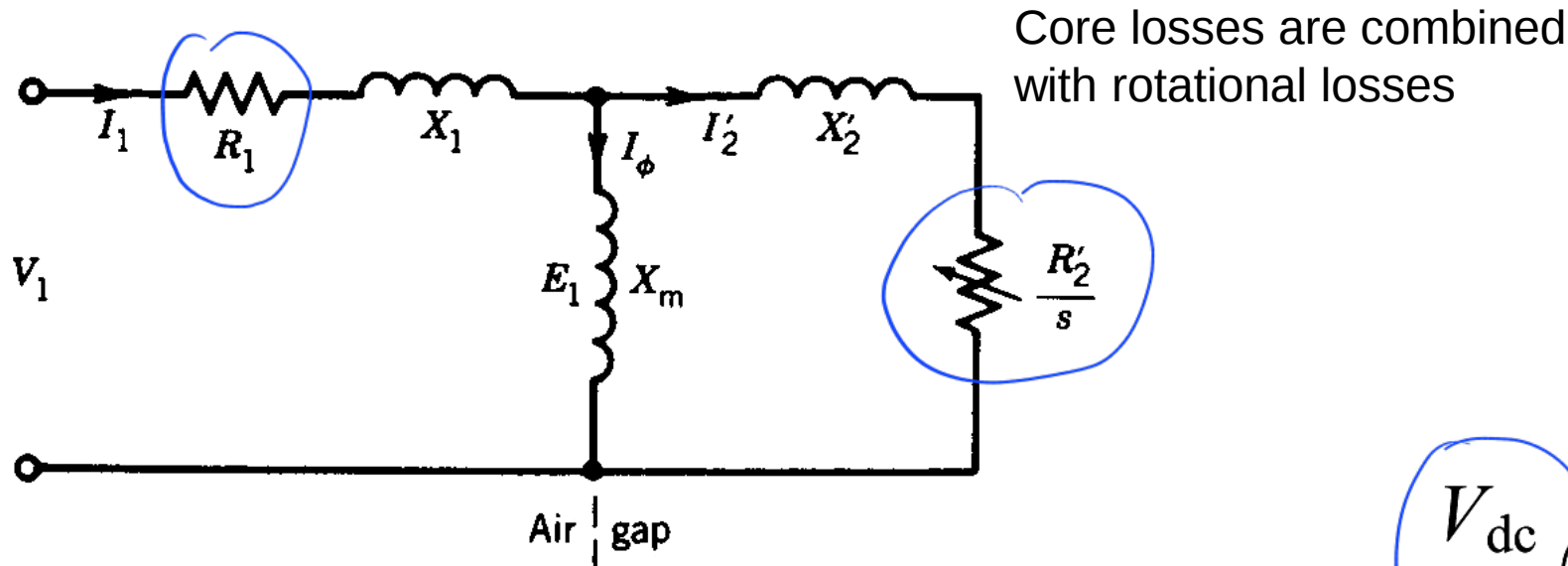

$$R_1 = \frac{V_{dc}}{2I_{dc}}$$

Tests to determine circuit parameters:


1. **DC Measurement of winding resistance** *multimeter test*
2. No Load Test (like Open-Circuit in transformer)
3. Blocked Rotor Test (like Short-Circuit in transformer)

For Wound-Rotor IM, repeat the test on the rotor

Determining Machine Parameters

2. No-Load (NL) Test

Apply rated voltage $V_{ph,NL}$

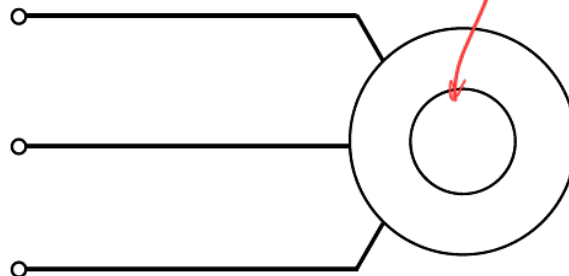

Measure

V_{ph}, P_{nl}, I_{nl}

Rotational losses

$$P_{rotational} = P_{NL} - 3R_1 I_{NL}^2$$

Combined reactance

$$X_l + X_m = X_{NL} = \frac{Q_{NL}}{3I_{NL}^2}$$


where reactive power is

$$Q_{NL} = \sqrt{S_{NL}^2 - P_{NL}^2} = \sqrt{(3I_{NL}V_1)^2 - P_{NL}^2}$$

can't separate these two

$$OR : Z_{nl} = \frac{V_{ph,nl}}{I_{ph,nl}} \Rightarrow X_{nl} = X_l + X_m = \sqrt{Z_{nl}^2 - R_1^2}$$

Assumed Equivalent Circuit

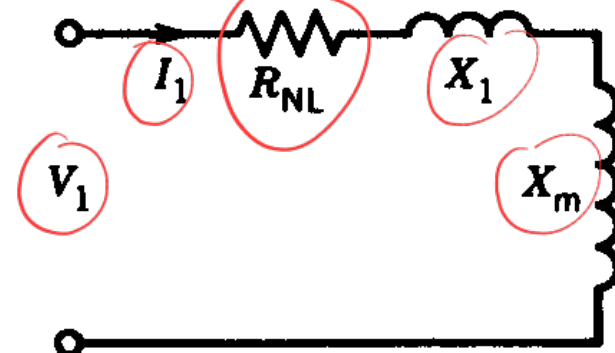

Stator $\rightarrow$ no rotor
($s = \phi$)

Determining Machine Parameters

3. Blocked-Rotor (BR) Test ($s = 1$)

Apply reduced voltage $V_{ph, BR}$
(this test may be performed at reduced frequency)

Measure V_{ph-BR} , P_{BR} , I_{BR}

Combined resistance $R_1 + R'_2 = R_{BR} = \frac{P_{BR}}{3I_{BR}^2}$

Combined reactance


$$X_{BR} = \sqrt{Z_{BR}^2 - R_{BR}^2} = \sqrt{(V_1 / I_{BR})^2 - R_{BR}^2} = X_1 + X'_2$$

Leakage reactance $X_1 \approx X'_2 = \frac{X_{BR}}{2}$


Magnetizing reactance $X_m = X_{NL} - X_1$

Rotor resistance $R'_2 = R_{BR} - R_1$

3-Phase
Source
@ 60Hz

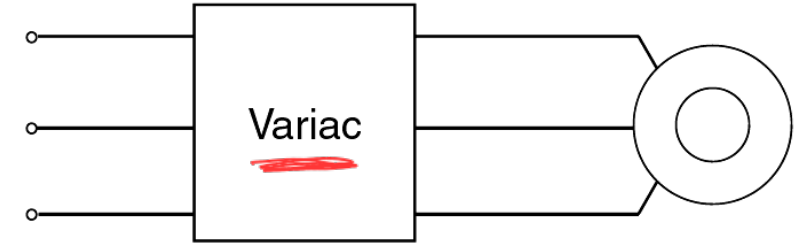

Assumed Equivalent Circuit

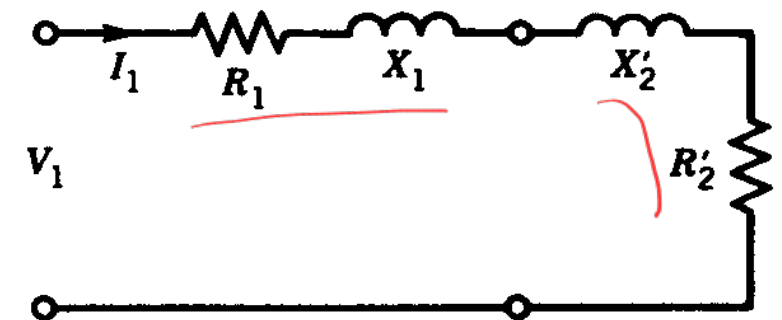

Looking ahead...

- Continue **Module 5**