

ELEC 342

Electromechanical Energy Conversion and Transmission

2025-26 Winter Term 2

Lecture 17

March 12, 2026

Zhi Jin (Justin) Zhang

Course Logistics


- Tutorial resumes this week
- Lab 3 takes place this week
- Assignment 5 posted
- Midterm available to pick up
- Quizzes
 - Quiz 3: March 20 at the beginning of the tutorial
 - Quiz 4: April 2 at the beginning of the lecture

Thevenin Equivalent and Approximate Circuits

Stator $\rightarrow f_s$ Rotor $\rightarrow sf_s$

Prime notation:
secondary (rotor)
side referred
to primary (stator)
side


Full equivalent circuit

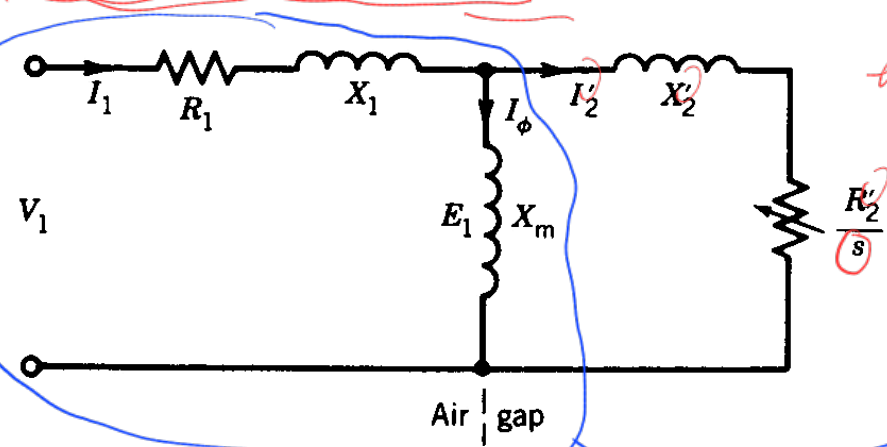

Thevenin


Thevenin equivalent circuit

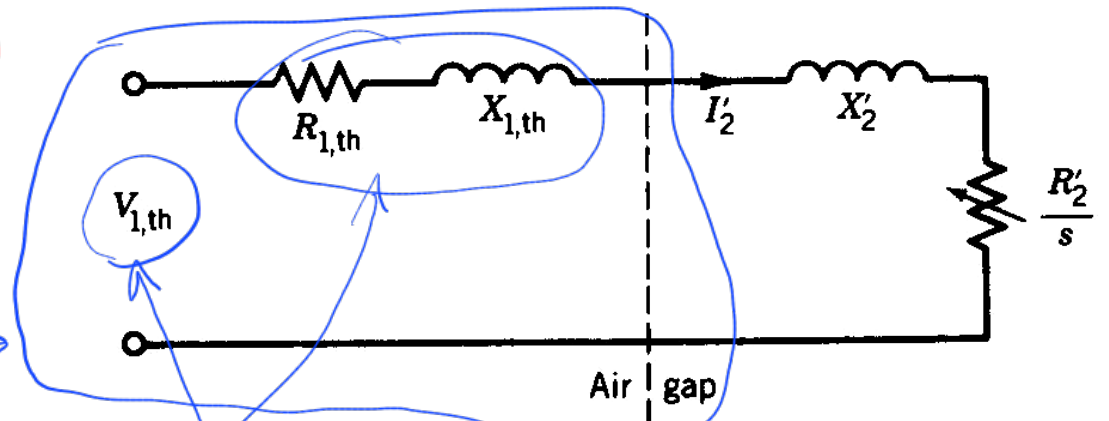Recalculate parameters to remove magnetizing branch



Approximate equivalent circuit

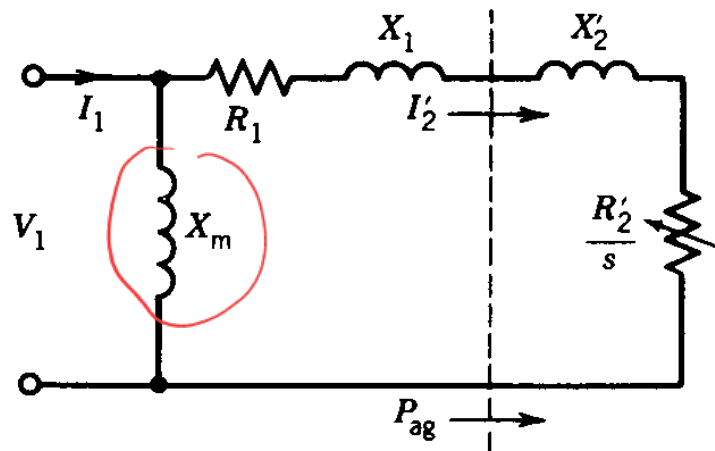Move magnetizing branch to input terminals



$$V_{1,th} = \frac{X_m}{\sqrt{R_1^2 + (X_1 + X'_m)^2}} V_1$$



$$Z_{1,th} = \frac{jX_m (R_1 + jX_1)}{R_1 + j(X_1 + X'_m)}$$

$$= \alpha + j\beta$$

$$= R_{1,th} + jX_{1,th}$$

Determining Machine Parameters

Consider Full Equivalent Circuit

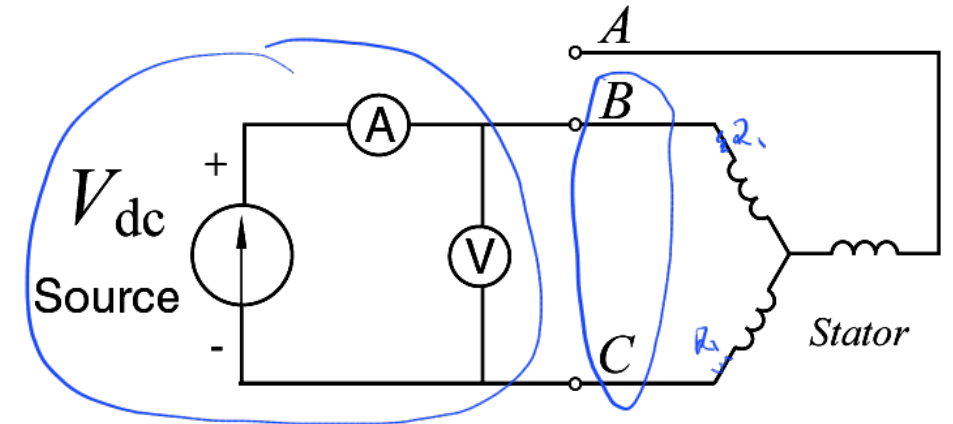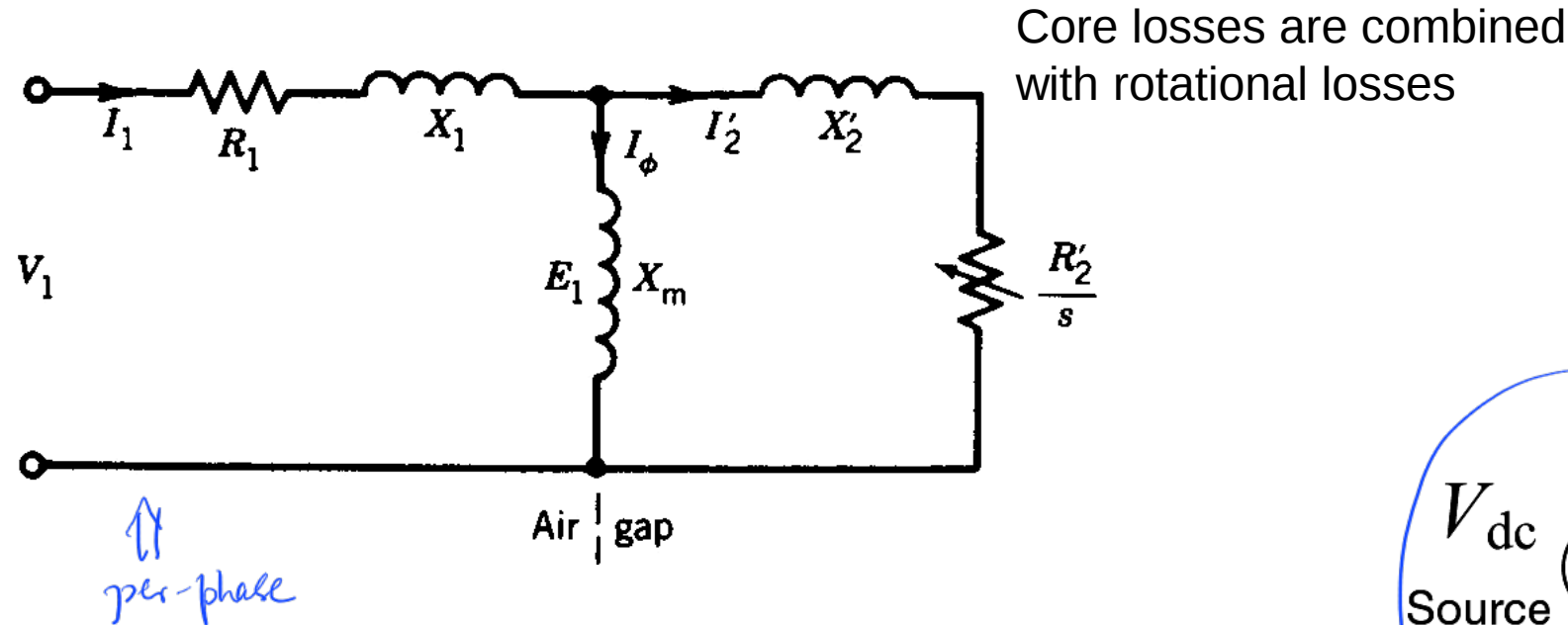

Tests to determine circuit parameters:

1. DC Measurement of winding resistance
2. No Load Test (like Open-Circuit in transformer)
3. Blocked Rotor Test (like Short-Circuit in transformer)

$$R_1 = \frac{V_{dc}}{2I_{dc}}$$


For Wound-Rotor IM, repeat the test on the rotor

Determining Machine Parameters

→ Rotor rotates $\sim V_{sync} \Rightarrow s = \phi$

2. No-Load (NL) Test

Apply rated voltage $V_{ph,NL}$

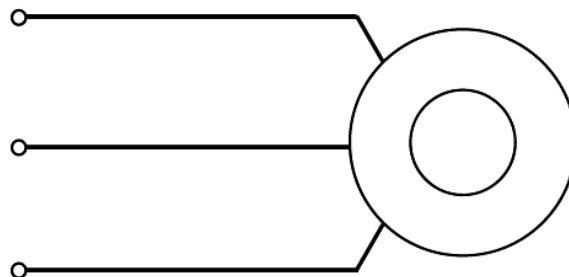

Measure V_{ph}, P_{nl}, I_{nl}
3-phase
per-phase *per-phase*


Rotational losses $P_{rotational} = P_{NL} - 3R_1 I_{NL}^2$

Combined reactance $X_l + X_m = X_{NL} = \frac{Q_{NL}}{3I_{NL}^2}$
 where reactive power is *Can't separate*

$$Q_{NL} = \sqrt{S_{NL}^2 - P_{NL}^2} = \sqrt{(3I_{NL}V_1)^2 - P_{NL}^2}$$

$O_R : Z_{nl} = \frac{V_{ph,nl}}{I_{ph,nl}} \Rightarrow X_{nl} = \sqrt{Z_{nl}^2 - R_1^2}$

Assumed Equivalent Circuit

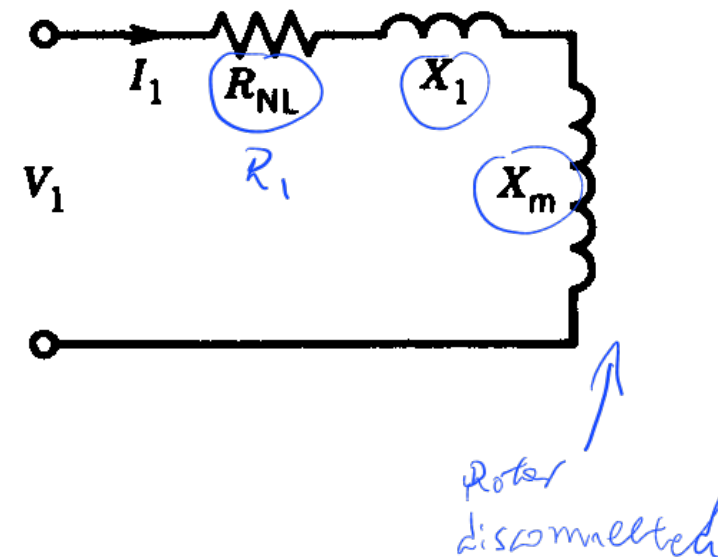

Determining Machine Parameters

3. Blocked-Rotor (BR) Test $\rightarrow s = 1$

Apply reduced voltage $V_{ph, BR}$
(this test may be performed at reduced frequency)

Measure $V_{ph-BR}, P_{BR}, I_{BR}$

Combined resistance $R_1 + R'_2 = R_{BR} = \frac{P_{BR}}{3I_{BR}^2}$



Combined reactance

$$X_{BR} = \sqrt{Z_{BR}^2 - R_{BR}^2} = \sqrt{(V_1 / I_{BR})^2 - R_{BR}^2}$$

Leakage reactance $X_1 \approx X'_2 = \frac{X_{BR}}{2} \rightarrow X_1 \Rightarrow X_m = X_{NL} - X_1$


Magnetizing reactance $X_m = X_{NL} - X_1$

Rotor resistance $R'_2 = R_{BR} - R_1$

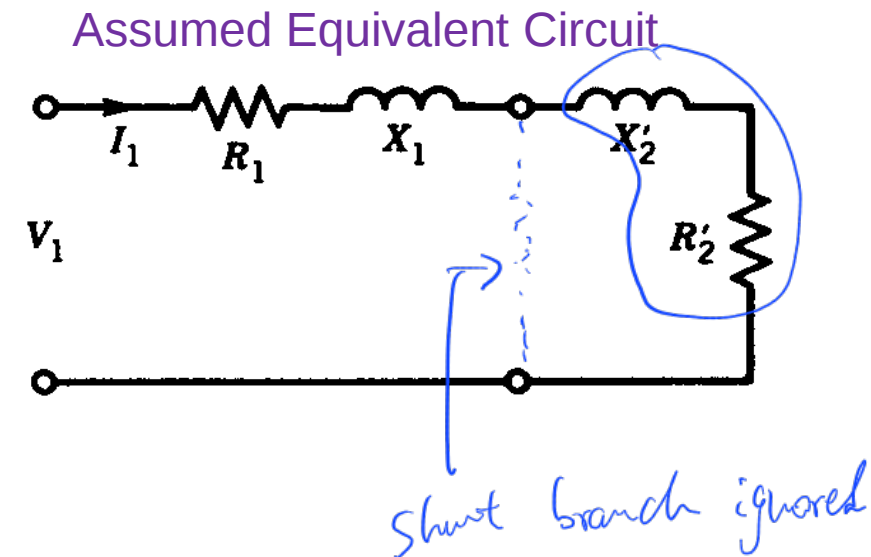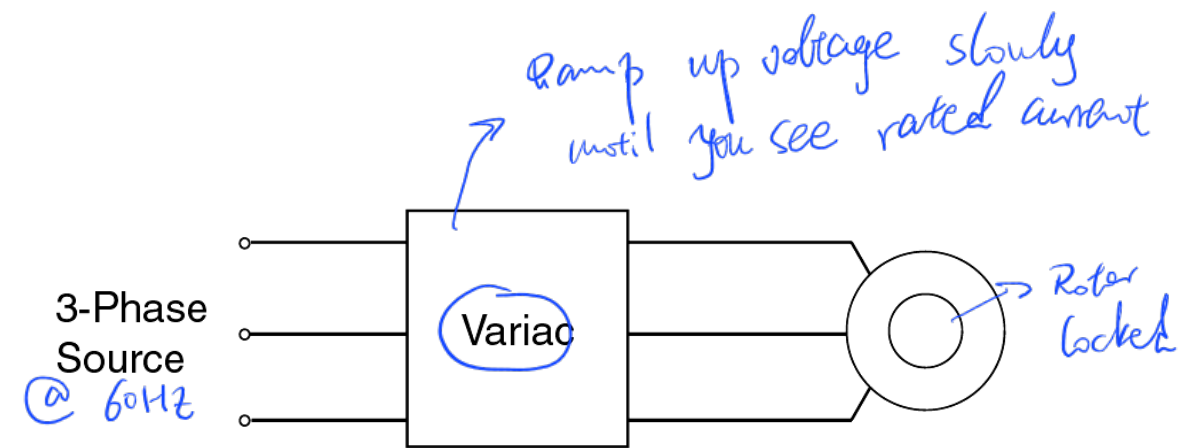

Power Conversion & Torque

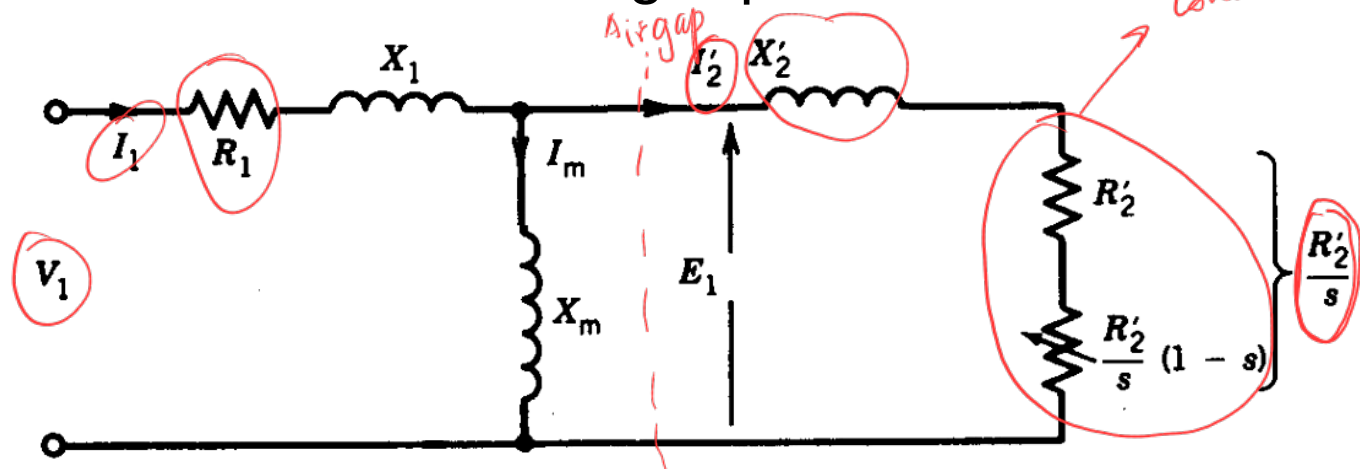Consider the following equivalent circuit



Separate the rotor winding resistance and the remaining part that represent conversion of real power into torque

$$\frac{R_2'}{s} = \underbrace{\frac{s-s+1}{s} R_2'}_{\substack{\text{Winding} \\ \text{losses in} \\ \text{rotor}}} = R_2' + \underbrace{\frac{1-s}{s} R_2'}_{\text{Creating } T_e}$$

Input Power

$$P_{in} = 3V_1 I_1 \cos(\phi)$$

Stator copper loss

$$P_{SCL} = 3I_1^2 R_1$$

Air-gap power

$$P_{ag} = 3I_2'^2 \frac{R_2'}{s}$$

Conversion power (for creating T_e)

$$P_e = 3I_2'^2 R_2' \left(\frac{1-s}{s} \right) = (1-s)P_{ag}$$

$$P_{ag} = P_e + P_{\text{rotor loss}}$$

Electromagnetic torque


$$T_e = \frac{P_e}{\omega_{rm}} = \frac{(1-s)P_{ag}}{\omega_{rm}} = \frac{P_{ag}}{\omega_{syn}} = 3 \frac{I_2'^2 R_2'}{\omega_{syn} s} = 3 \left(\frac{P}{2} \right) \frac{I_2'^2 R_2'}{\omega_e s}$$

Express in terms of V_1
 $\hookrightarrow I_2'$ is hard to determine

electrical freq.

Torque-Speed Characteristic


1) Using Thevenin Equivalent Circuit

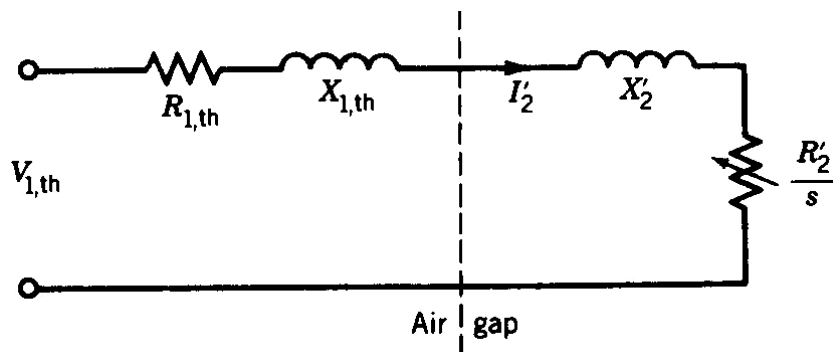

Recall $T_e = \frac{P_e}{\omega_{rm}} = 3 \frac{P}{2} \frac{I_2'^2 R_2'}{\omega_e s}$

$$I_2' = \frac{V_{1,th}}{(R_{1,th} + R_2' / s) + j(X_{1,th} + X_2')}$$

$$T_e = 3 \frac{P_{1,th}^2}{2 \omega_e} \cdot \frac{R'_2 / s}{(R_{1,th} + R'_2 / s)^2 + (X_{1,th} + X'_2)^2}$$
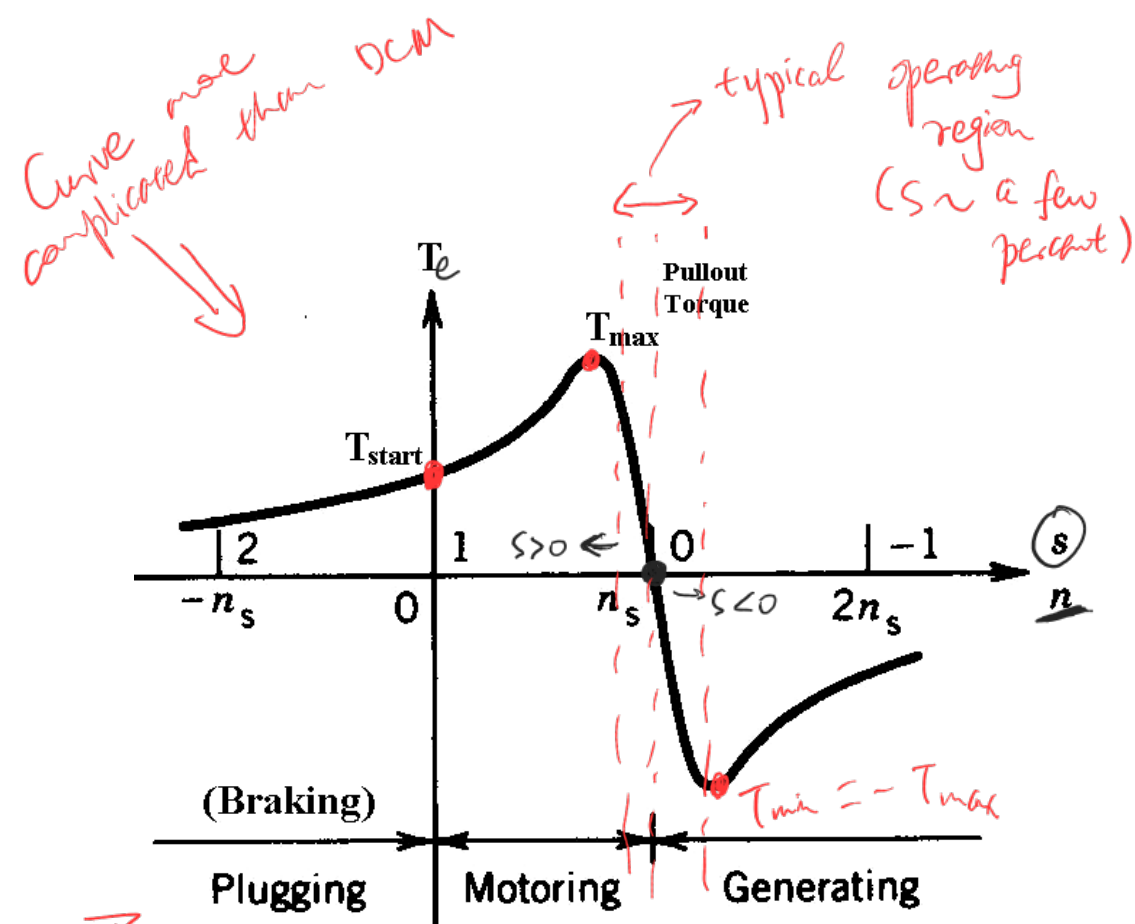
$$= f(v_{i,th}, s)$$


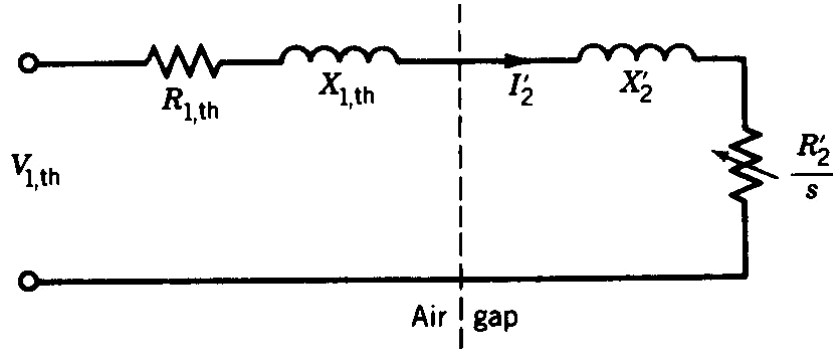
Torque-speed characteristic

$$h_s$$

 $(s=0)$

Torque-Speed Characteristic

1) Using Thevenin Equivalent Circuit




Recall
$$T_e = \frac{P_e}{\omega_{rm}} = 3 \frac{P}{2} \frac{I_2'^2 R_2'}{\omega_e s}$$

$$I_2' = \frac{V_{1,th}}{(R_{1,th} + R_2' / s) + j(X_{1,th} + X_2')}$$

$$T_e = 3 \frac{P}{2} \frac{V_{1,th}^2}{\omega_e} \cdot \frac{R_2' / s}{(R_{1,th} + R_2' / s)^2 + (X_{1,th} + X_2')^2}$$


⇒ Provide formula on test/exam

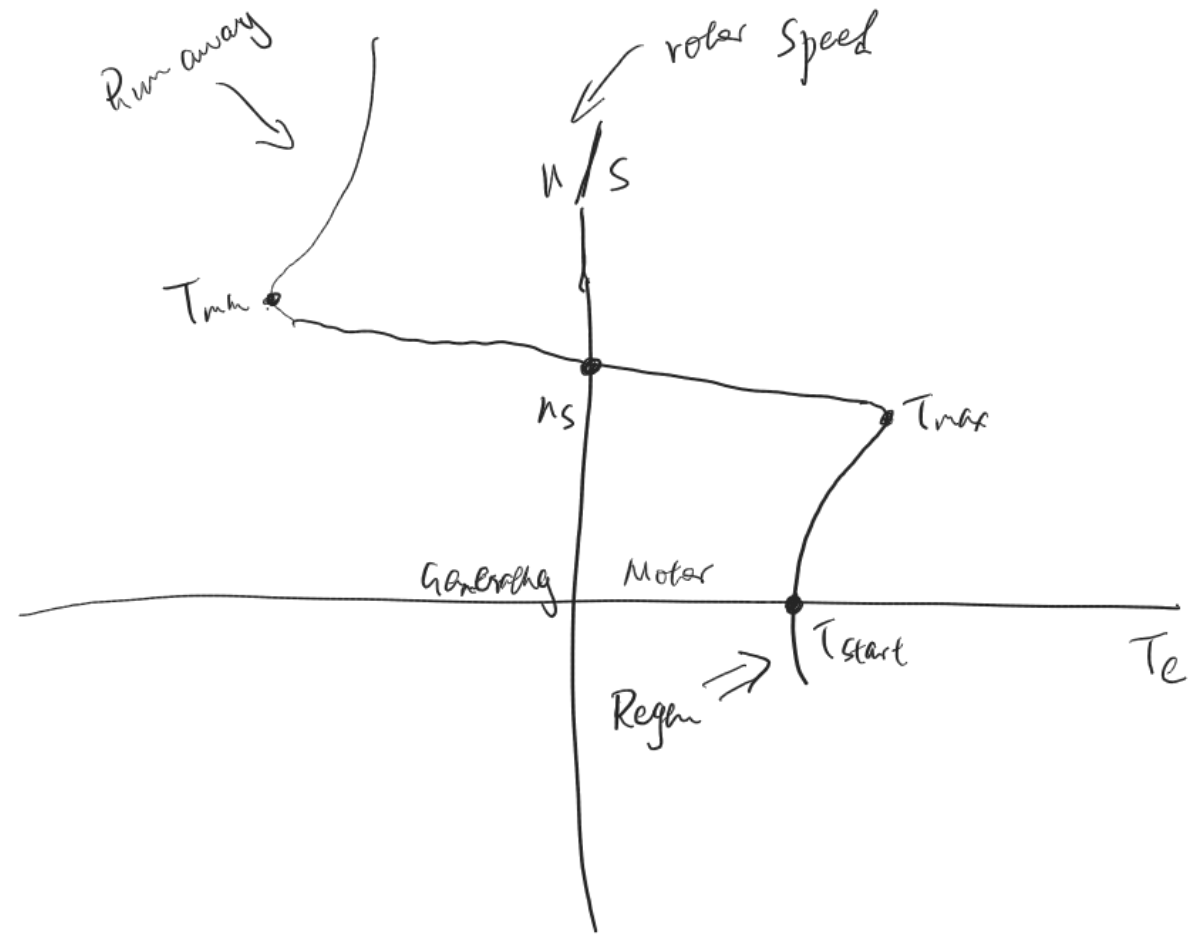

Speed-torque characteristic

Torque-Speed Characteristic


2) Using Approximate Equivalent Circuit

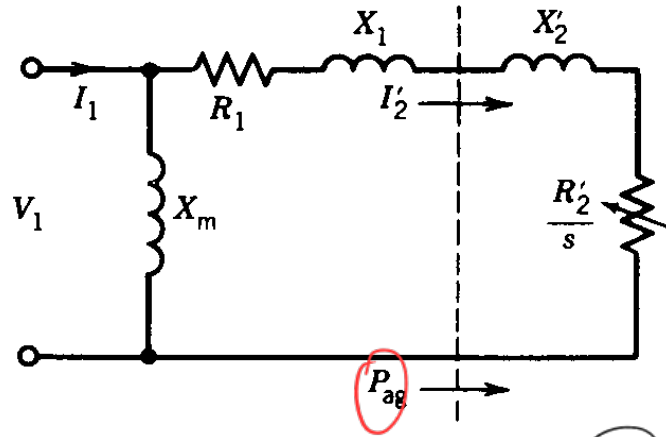

Recall $T_e = \frac{P_e}{\omega_{rm}} = 3 \frac{P}{2} \frac{I_2'^2 R_2'}{\omega_e s}$


$$I_2' = \frac{V_1}{(R_1 + R_2' / s) + j(X_1 + X_2')}$$
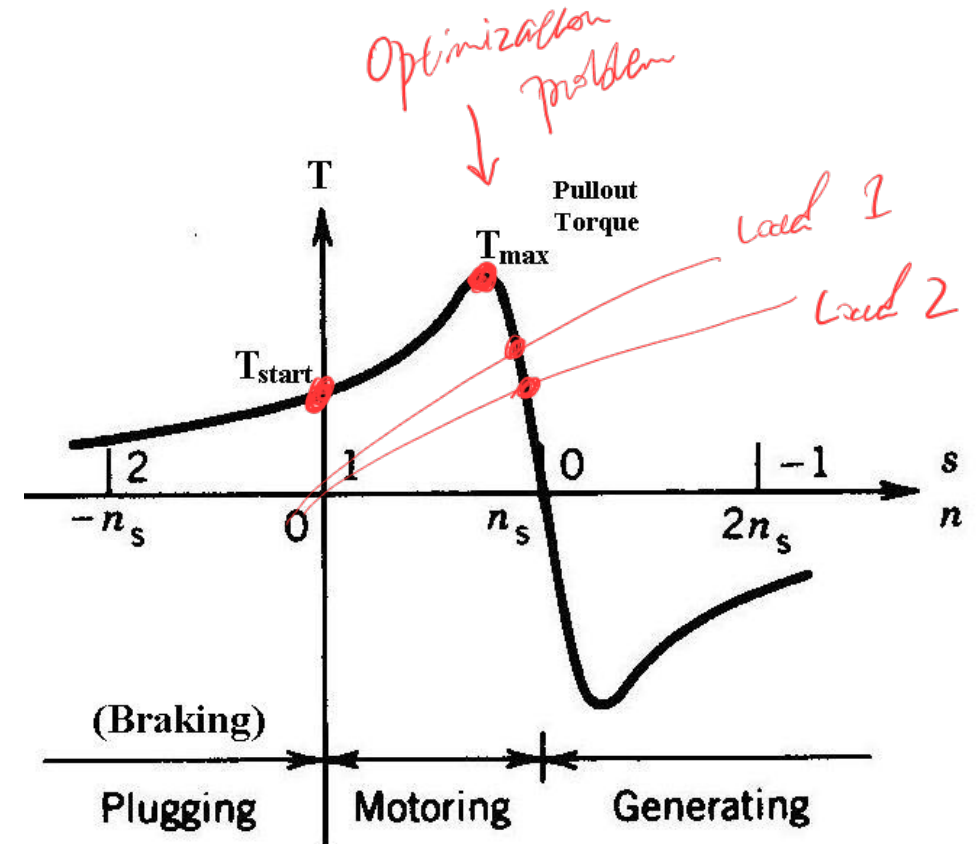
$$T_e = 3 \frac{P}{2} \frac{V_1^2}{\omega_e} \cdot \frac{R_2' / s}{(R_1 + R_2' / s)^2 + (X_1 + X_2')^2} = f(V_1, s)$$



Torque-speed characteristic

Torque-Speed Characteristic

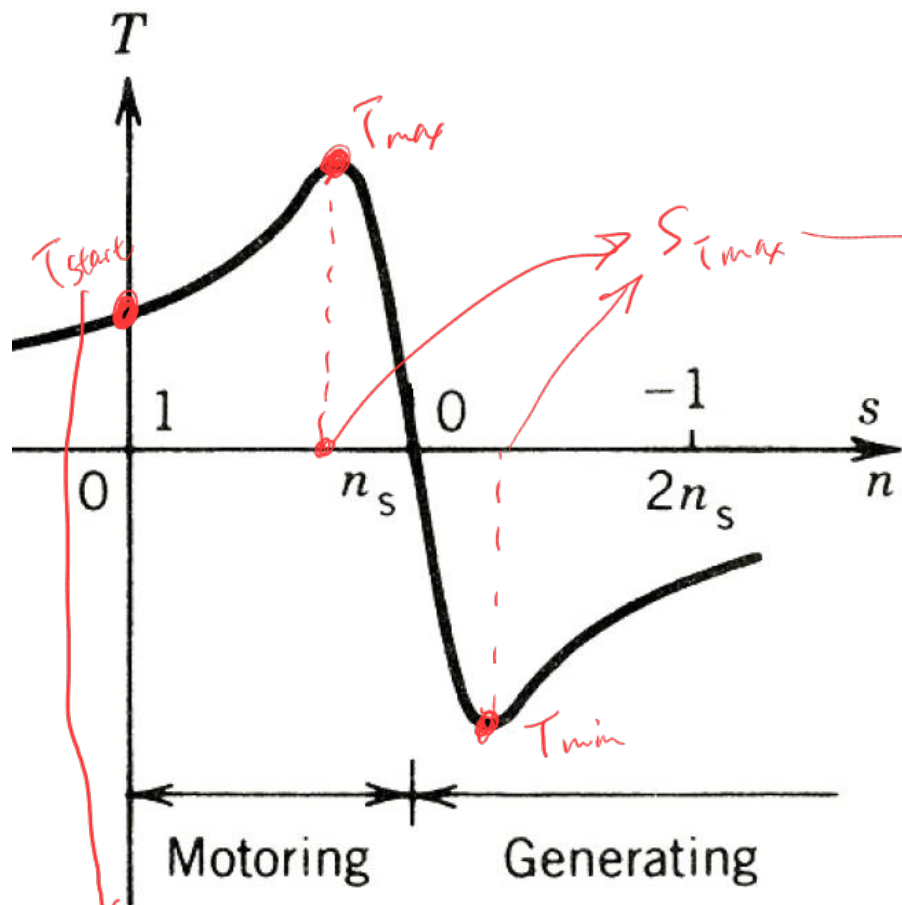

Starting torque/current



set slip $s = 1$

Maximum torque

$$\frac{\partial T}{\partial s} = 0$$



$$T_e = 3 \frac{P}{2} \frac{V_{1,th}^2}{\omega_e} \cdot \frac{R'_2 / s}{(R_{1,th} + R'_2 / s)^2 + (X_{1,th} + X'_2)^2}$$

$$S_{T \max} = \pm \frac{R'_2}{\sqrt{R_{1,th}^2 + (X_{1,th} + X'_2)^2}}$$



$$T_{\max} = 3 \frac{P}{2} \frac{V_{1,th}^2}{2\omega_e} \cdot \frac{1}{R_{1,th} + \sqrt{R_{1,th}^2 + (X_{1,th} + X'_2)^2}}$$

$$T_{\min} = 3 \frac{P}{2} \frac{V_{1,th}^2}{2\omega_e} \cdot \frac{1}{\sqrt{R_{1,th}^2 + (X_{1,th} + X'_2)^2} - R_{1,th}}$$

rotor winding resistance


Does not depend on R'_2

Torque-Speed Characteristic

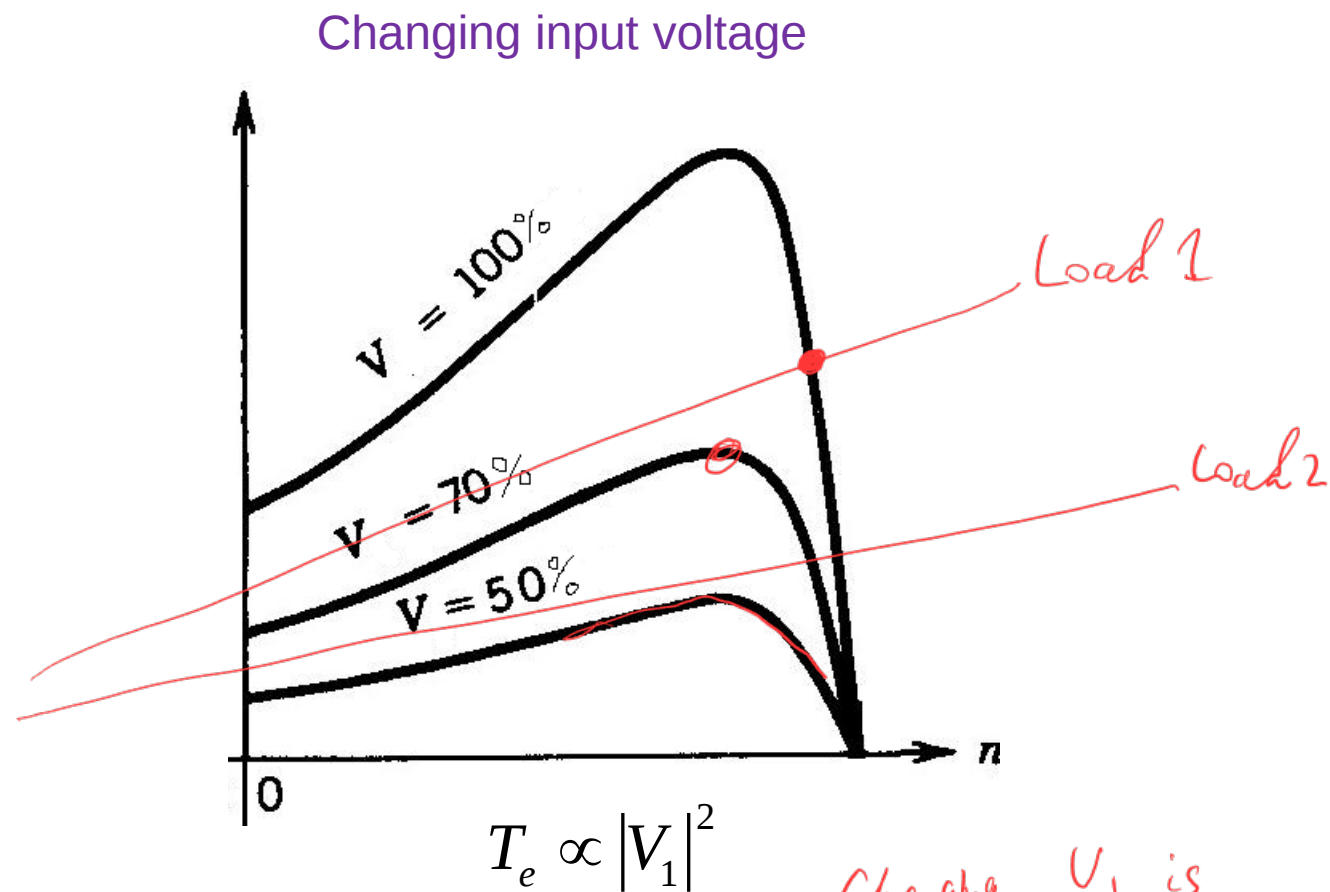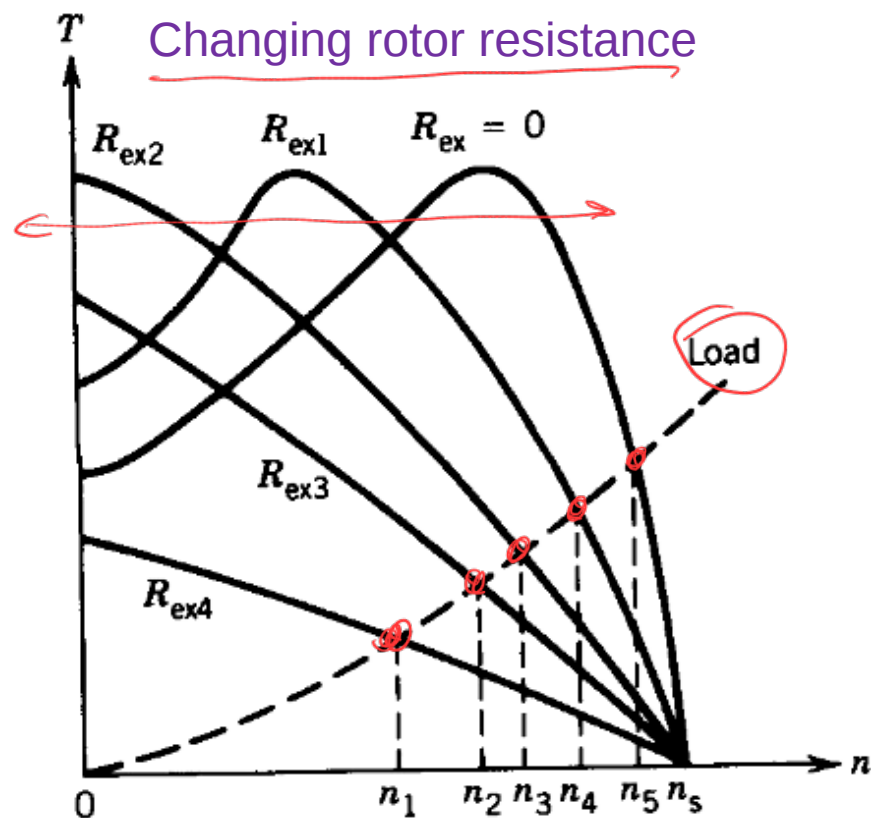

Make R_2' very large
at the start-up
to have a high
start-up torque

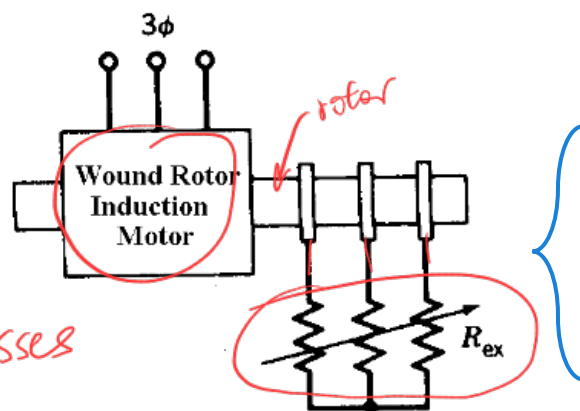↓
remove to reduce losses
at steady-state




$$s_{T_{max}} \propto R_2'$$

$$T_{max} \text{ independent of rotor resistance}$$

Changing V_1 is
not a good
way to control
IM

Starting Current $\rightarrow$ at steady-state $\sim s \sim 0.03$


Recommended T-Equivalent Circuit

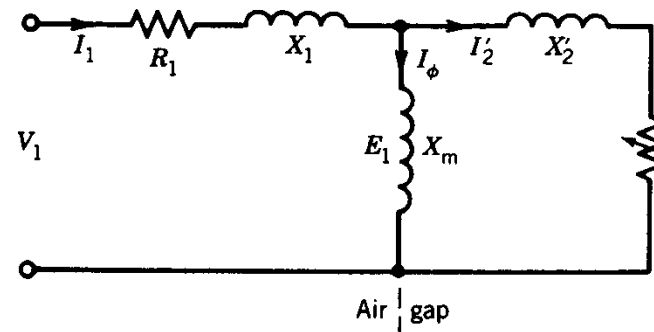

$$Z_{eq,start} = R_1 + jX_1 + \frac{jX_m(R'_2 + jX'_2)}{R'_2 + j(X_m + X'_2)}$$

$$I_{1,start} = \frac{V_1}{Z_{eq,start}}$$



Approximate Equivalent Circuit

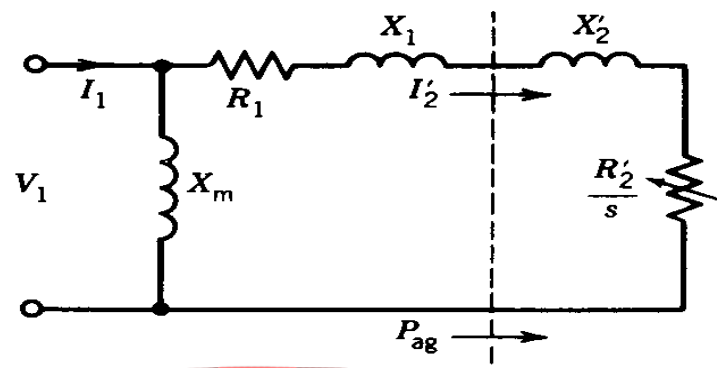



$$I_{1,start} = I_m + I'_2 = \frac{V_1}{jX_m} + \frac{V_1}{(R_1 + R'_2) + j(X_1 + X'_2)}$$

large at steady-state
small at start-up
high current

well-known
IM behavior

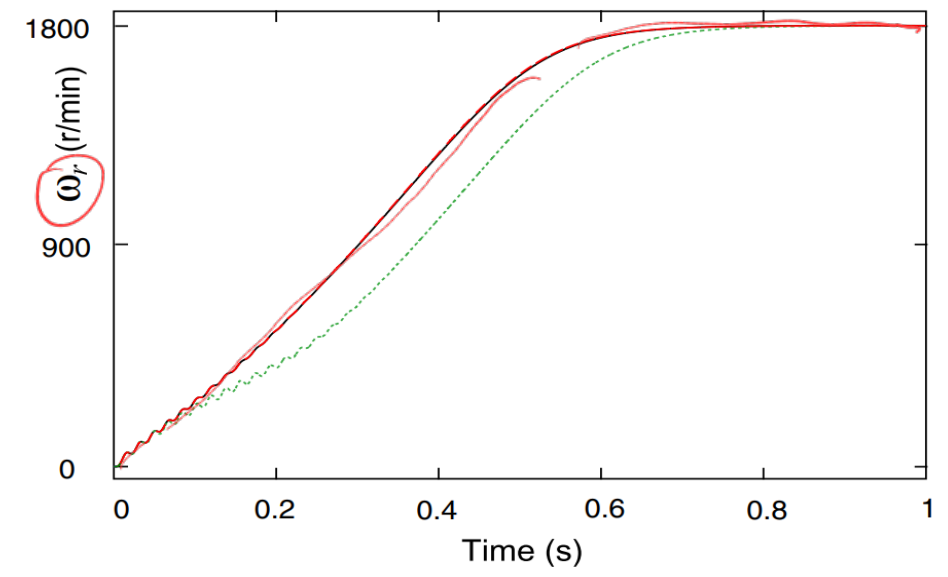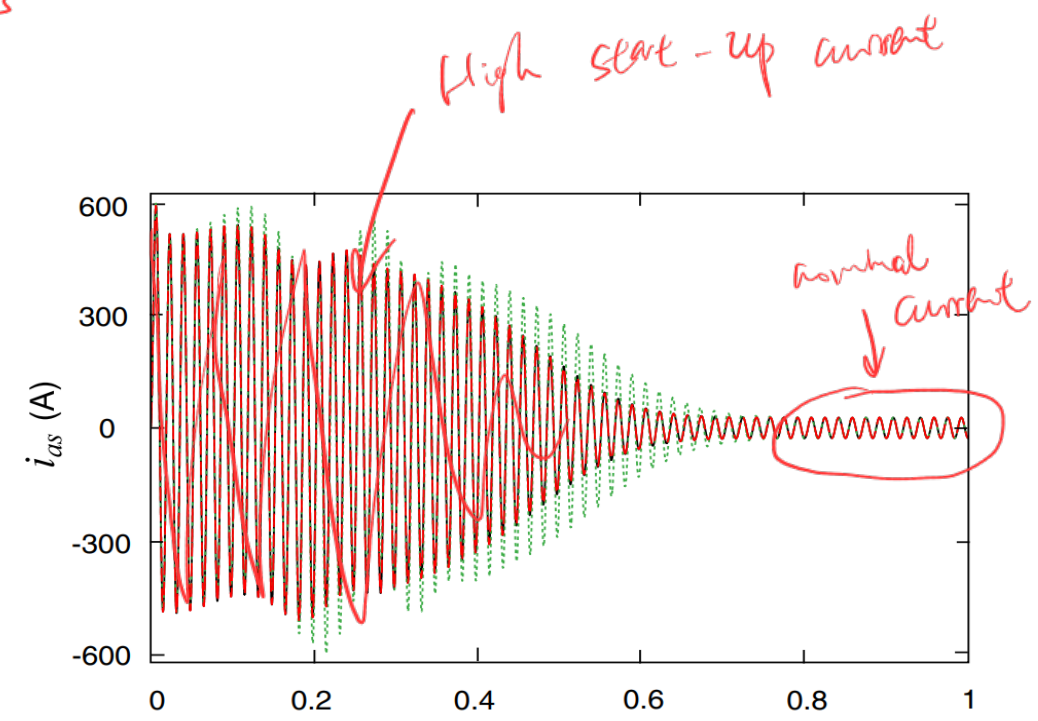


Starting Current

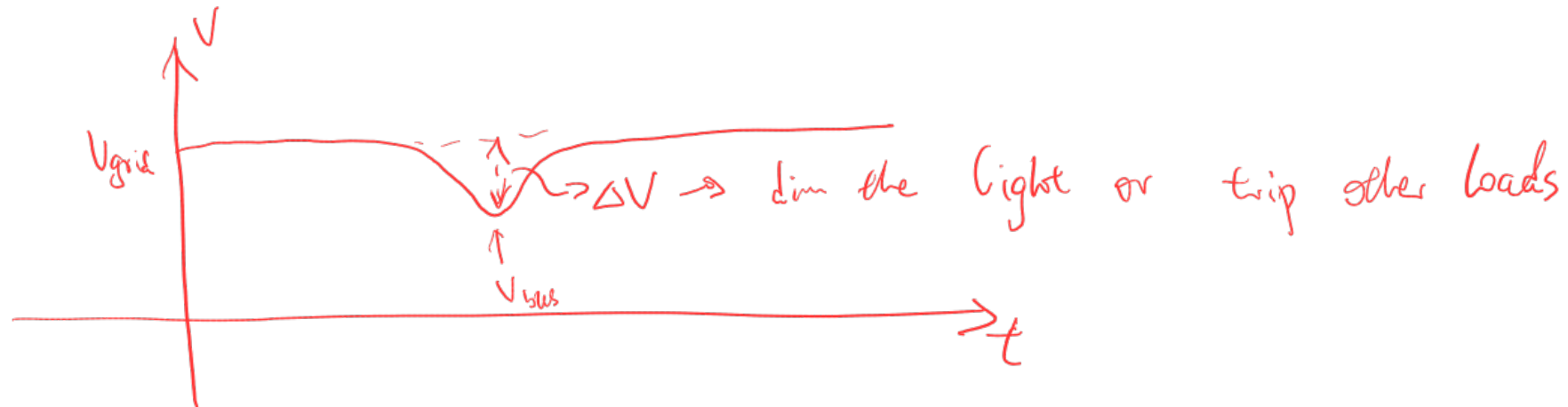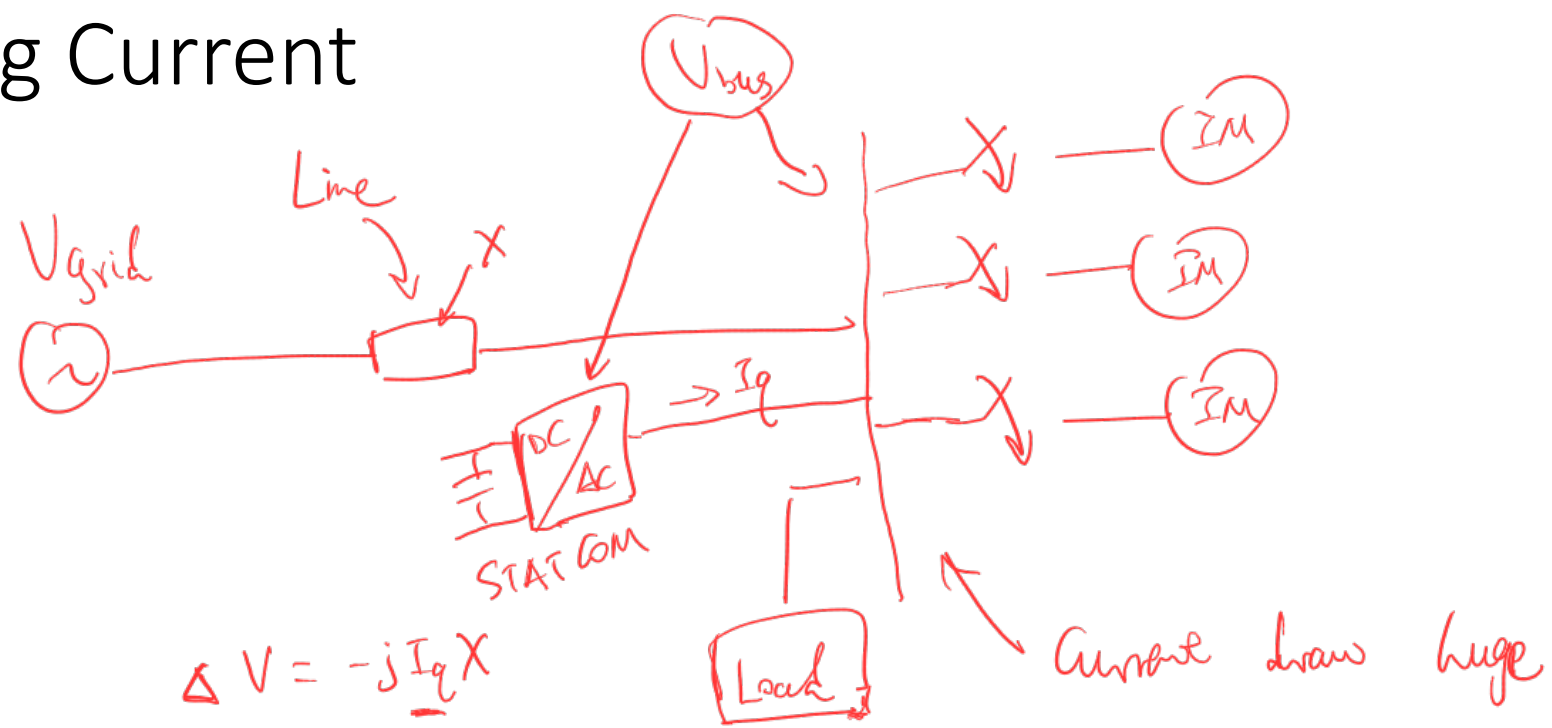



Power Flow & Efficiency

Motor Mode

$$P_{in} = 3 V_{ph} I_{ph} \cos(\phi)$$

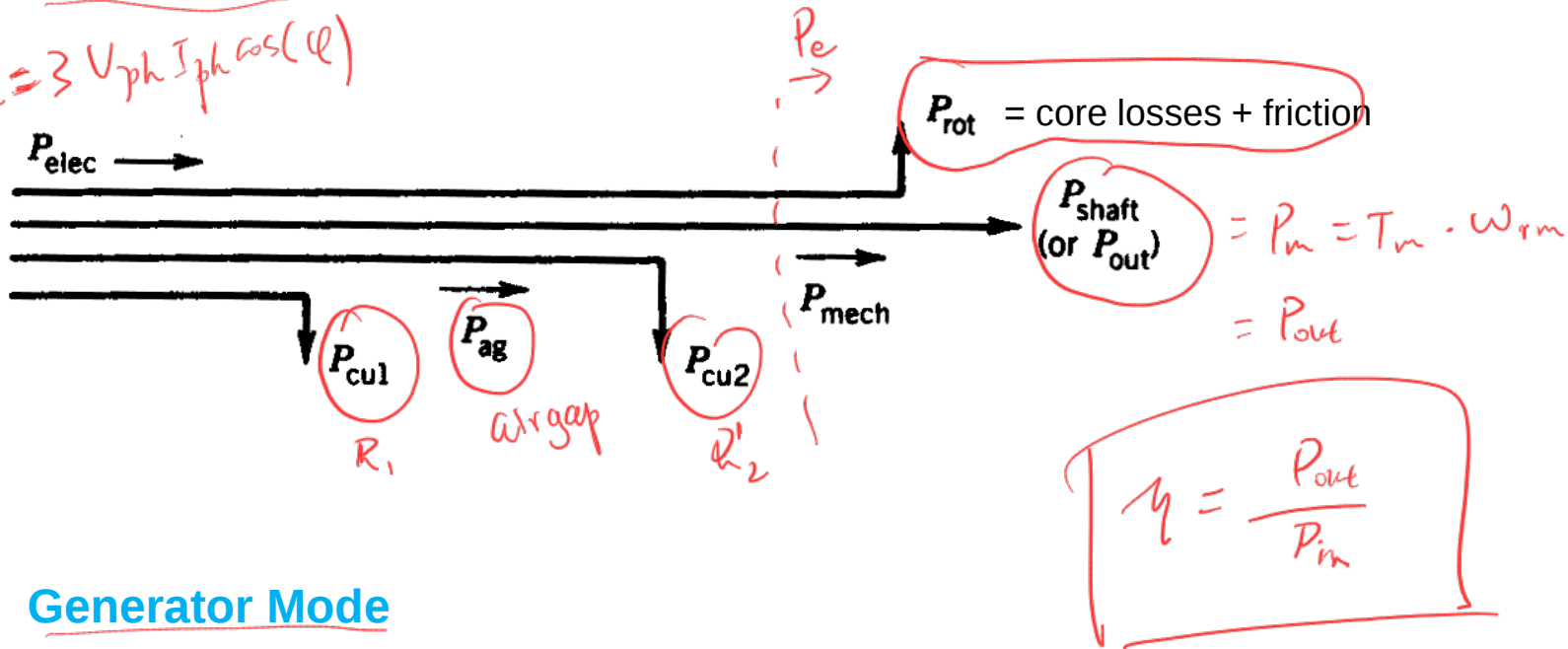


Generator Mode

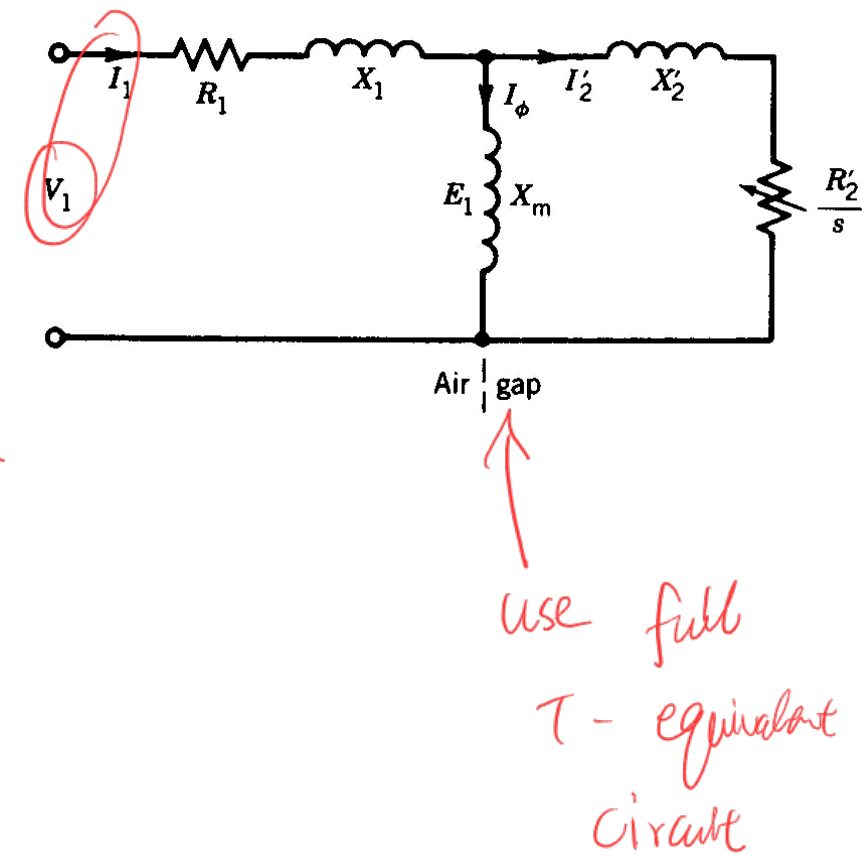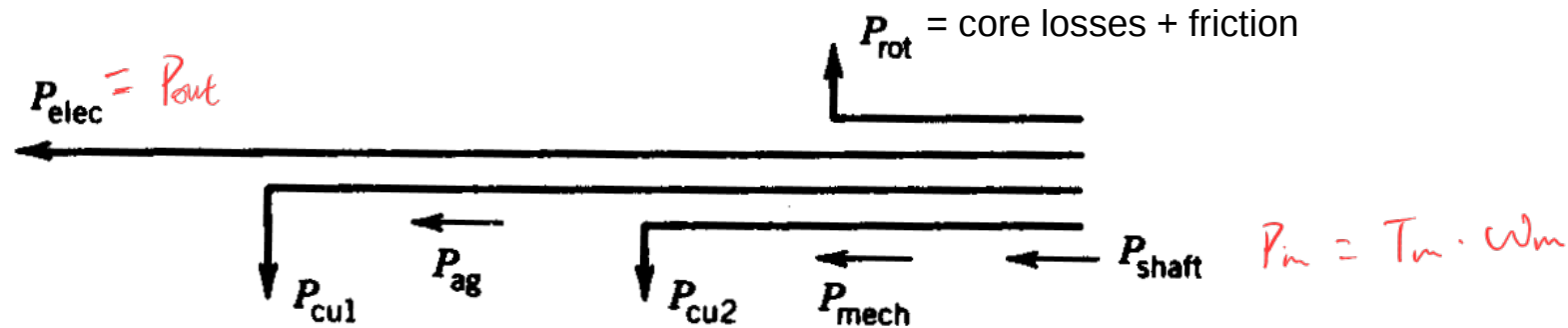

Analysis of Induction Machines (using Equivalent Circuit)

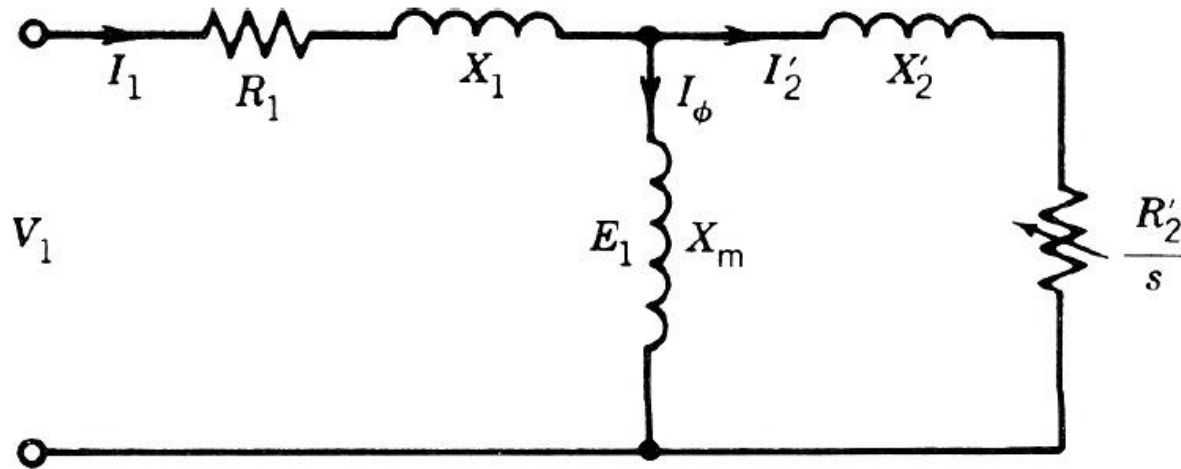❖ **Typical Question:** A 3-phase, 460 V, 1740 rpm, 60 Hz, four-pole induction motor has the following parameters per-phase:



$$\begin{cases} R_1 = 0.25 \, \Omega \\ R'_2 = 0.20 \, \Omega \\ X_1 = X'_2 = 0.5 \, \Omega \\ X_m = 30 \, \Omega \end{cases}$$

Most questions
just involve
solving circuit
↓
The equation
will be provided
to you

Rotational losses are constant 1700 W. **Calculate:**

- (a) Starting current & torque
- (b) Under given load (defined either by speed or torque), find current & torque & power factor & efficiency
- (c) Maximum torque & corresponding slip
- (d) For DFIM, find external resistance needed to get max torque at start-up

Example 3

we need phase voltage

Consider a Y-connected 7.5kW, 220V (line-line), 60Hz, 6-pole, Squirrel-cage motor with the following parameters:
 $R_1 = 0.294\Omega$, $R'_2 = 0.144\Omega$, $X_1 = 0.503\Omega$, $X'_2 = 0.209\Omega$, $X_m = 13.5\Omega$

Using original T-Equivalent Circuit

a) Compute starting current $I_{1\text{start}}$

$s = 1$

$$V_1 = \frac{V_{e-l}}{\sqrt{3}} = \frac{220}{\sqrt{3}} = 127V_{rms}$$


$$Z_{eq,st} = R_1 + jX_1 + \frac{jX_m(jX_2 + R_2)}{jX_m + jX_2 + R_2} =$$

$$= 0.4336 + j0.7103 \Omega$$

$$I_{1,st} = \frac{V_1}{Z_{eq,st}} = \frac{127}{0.4336 + j0.7103} = 79.5 - j130.3 A$$

$$= 152.63 A(rms)$$

*Sanity check:
should be lagging*

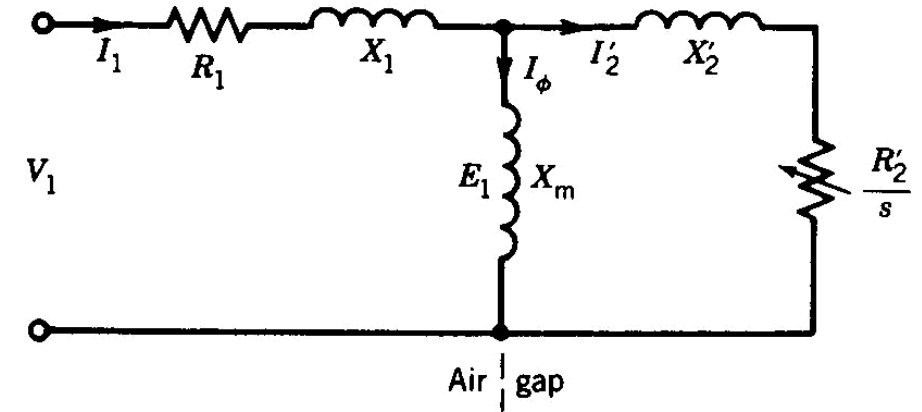


Example 3

Consider a Y-connected 7.5kW, 220V (line-line), 60Hz, 6-pole, Squirrel-cage motor with the following parameters:
 $R_1 = 0.294\Omega$, $R'_2 = 0.144\Omega$, $X_1 = 0.503\Omega$, $X'_2 = 0.209\Omega$, $X_m = 13.5\Omega$

Using Thevenin Equivalent Circuit

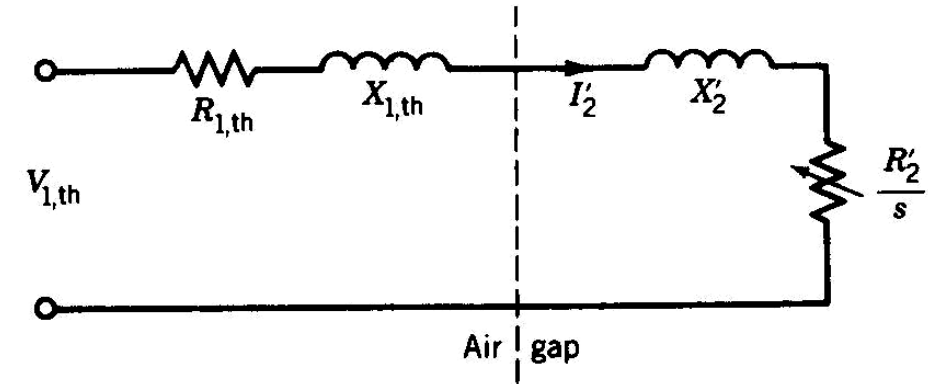b) Compute the starting torque T_{start} $\Rightarrow s = 1$



$$\omega_e = 2\pi \cdot f_e = 2\pi \cdot 60 = 376.99 \text{ rad/sec}$$

$$V_{1,th} = V_1 \cdot \frac{X_m}{\sqrt{R_1^2 + (X_1 + X_m)^2}} = 122.43 \text{ V(rms)}$$

$$Z_{1,th} = \frac{jX_m(R_1 + X_1)}{(jX_m + R_1 + jX_1)} = \underbrace{0.2731}_{R_{1,th}} + \underbrace{j0.491}_{X_{1,th}} \Omega$$

Convert to Thevenin circuit

$$\begin{aligned} T_{st} &= 3 \cdot \frac{P}{2} \cdot \frac{V_{1,th}^2}{\omega_e} = \frac{R_2}{(R_{1,th} + R_2)^2 + (X_{1,th} + X'_2)^2} = \\ &= \underline{77.65 \text{ N}\cdot\text{m}} \end{aligned}$$

Example 3

Consider a Y-connected 7.5kW, 220V (line-line), 60Hz, 6-pole, Squirrel-cage motor with the following parameters: $R_1 = 0.294\Omega$, $R'_2 = 0.144\Omega$, $X_1 = 0.503\Omega$, $X'_2 = 0.209\Omega$, $X_m = 13.5\Omega$. Assume motor operates under load with slip $s = 0.03$ (3%).


Assume T-Equivalent Circuit

c) Compute stator current I_1 *Steady-state at $s = 0.03$*

$$Z_{eq} = R_1 + jX_1 + \frac{jX_m \cdot (jX_2 + R'_2/s)}{jX_m + jX_2 + R_2/s} = 4.44 + j2.16$$

$$I_1 = \frac{V_1}{Z_{eq}} = \frac{127}{4.44 + j2.16} = 23.13 - j11.23 \text{ A} \quad \text{lagging}$$

$= 25.72 \text{ A (rms)}$ $\ll I_{\text{start-up}}$

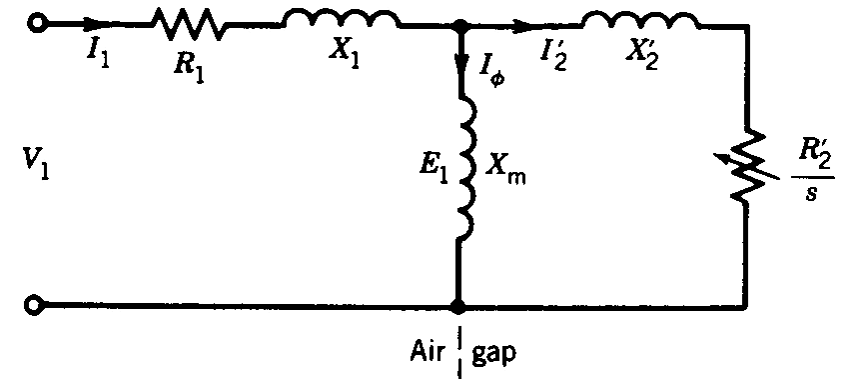

Example 3


Consider a Y-connected 7.5kW, 220V (line-line), 60Hz, 6-pole, Squirrel-cage motor with the following parameters: $R_1 = 0.294\Omega$, $R'_2 = 0.144\Omega$, $X_1 = 0.503\Omega$, $X'_2 = 0.209\Omega$, $X_m = 13.5\Omega$. Assume motor operates under load with slip $s = 0.03$ (3%).

Using Thevenin Equivalent Circuit

d) Compute the torque T_e

$$\begin{aligned} T_{e,th} &= 3 \cdot \left(\frac{P}{2}\right) \cdot \frac{V_{l,th}^2}{\omega_e} \cdot \frac{R'_2/s}{(R_{1,th} + R'_2/s)^2 + (X_{1,th} + X'_2)^2} \\ &= 3 \cdot \left(\frac{6}{2}\right) \cdot \frac{122.4^2}{377} \cdot \frac{0.144/0.03}{(0.2731 + \frac{0.144}{0.03})^2 + (0.4907 + 0.209)^2} = \\ &= 65.5 \text{ N}\cdot\text{m} \quad \text{at } s = 3\% \rightarrow \text{one point} \end{aligned}$$

Lab 4: do multiple points $\rightarrow$ T_e calculations can be simplified using a script
 $\rightarrow$ get $T_e - s$ curve

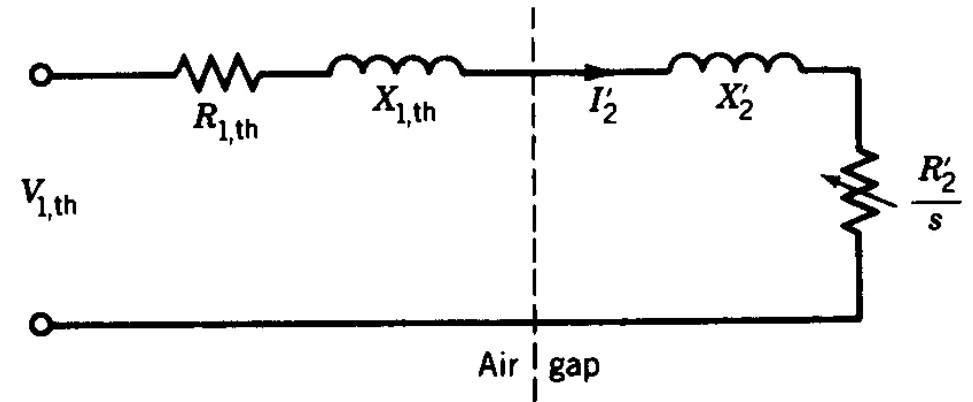

Example 3

Results of theorem = Results of Full ≠ Results of Approximate model

Consider a Y-connected 7.5kW, 220V (line-line), 60Hz, 6-pole, Squirrel-cage motor with the following parameters:
 $R_1 = 0.294\Omega$, $R'_2 = 0.144\Omega$, $X_1 = 0.503\Omega$, $X'_2 = 0.209\Omega$, $X_m = 13.5\Omega$

Using Approximate Equivalent Circuit

a) Compute starting current I_{1start}

$$Z_{12,st} = R_1 + jX_1 + R_2 + jX_2 = 0.438 + j0.712 \Omega$$

$$Z_{eq,st,ap} = \frac{jX_m \cdot Z_{12,st}}{jX_m + Z_{12,st}} = 0.3948 + j0.6885 \Omega$$

$$I_{1,st,ap} = \frac{V_1}{Z_{eq,st,ap}} = \frac{127}{0.3948 + j0.6885} = 79.6 - j138.8 A$$


$$= \underline{160.04 A (rms)} \quad (152.63 A)$$

b) Compute the starting torque T_{start}

$$T_{st,ap} = 3 \cdot \frac{P}{2} \cdot \frac{V_1^2}{\omega_e} \cdot \frac{R_2}{(R_1 + R_2)^2 + (X_1 + X_2)^2} =$$

$$= \underline{79.37 N \cdot m} \quad (77.65 N \cdot m)$$

losing accuracy

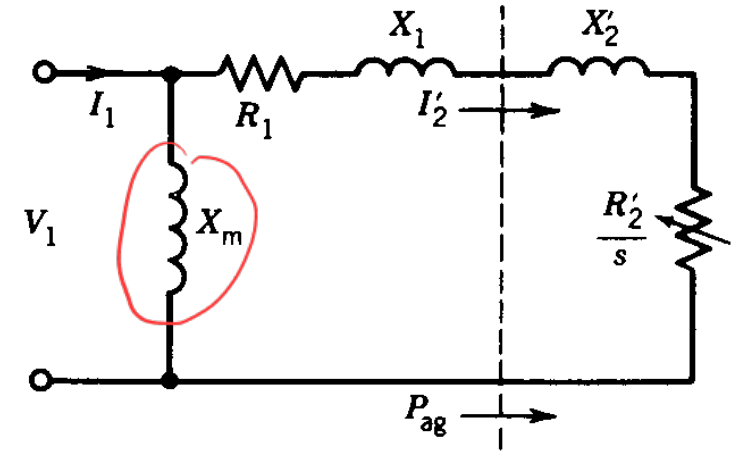

Example 3


Consider a Y-connected 7.5kW, 220V (line-line), 60Hz, 6-pole, Squirrel-cage motor with the following parameters: $R_1 = 0.294\Omega$, $R'_2 = 0.144\Omega$, $X_1 = 0.503\Omega$, $X'_2 = 0.209\Omega$, $X_m = 13.5\Omega$. Assume motor operates under load with slip $s = 0.03$ (3%).

Using Approximate Equivalent Circuit

c) Compute stator current I_1

$$\begin{aligned} \textcircled{1} \quad I'_2 &= \frac{V_1}{R_1 + jX_1 + R_2/s + jX_2} = 24.46 - j3.92 \text{ A} \\ I_m &= \frac{V_1}{jX_m} = -j9.41 \text{ A} \\ I_{1,ap} &= I_m + I'_2 = 24.46 - j12.83 \text{ A} \\ &= \underline{27.62 \text{ A (rms)}} \neq (25.72 \text{ A}) \end{aligned}$$

$$\begin{aligned} \textcircled{2} \quad Z_{eq,ap} &= \frac{jX_m(jX_1 + R_1 + jX_2 + R_2/s)}{jX_m + R_1 + jX_1 + jX_2 + R_2/s} = 4.07 + j2.14 \Omega \\ I_{1,ap} &= \frac{V_1}{Z_{eq,ap}} = \frac{127}{4.07 + j2.14} = 24.46 - j12.83 \text{ A} \\ &= \underline{27.62 \text{ A (rms)}} \end{aligned}$$

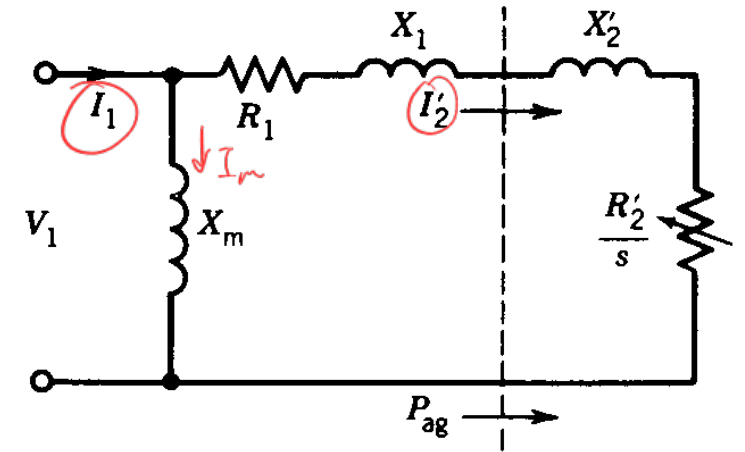


Example 3

Consider a Y-connected 7.5kW, 220V (line-line), 60Hz, 6-pole, Squirrel-cage motor with the following parameters: $R_1 = 0.294\Omega$, $R'_2 = 0.144\Omega$, $X_1 = 0.503\Omega$, $X'_2 = 0.209\Omega$, $X_m = 13.5\Omega$. Assume motor operates under load with slip $s = 0.03$ (3%).

Using Approximate Equivalent Circuit

d) Compute the torque T_e

$$\begin{aligned} T_{e,ap} &= 3 \cdot \left(\frac{P}{2}\right) \cdot \frac{V_1^2}{\omega_e} \cdot \frac{R'_2/s}{(R_1 + R'_2/s)^2 + (X_1 + X'_2)^2} \\ &= 3 \cdot \frac{6}{2} \cdot \frac{127^2}{377} \cdot \frac{0.144/0.03}{(0.294 + \frac{0.144}{0.03})^2 + (0.503 + 0.209)^2} \\ &= 69.88 \text{ N}\cdot\text{m} \quad \neq \quad 65.5 \text{ N}\cdot\text{m} \end{aligned}$$

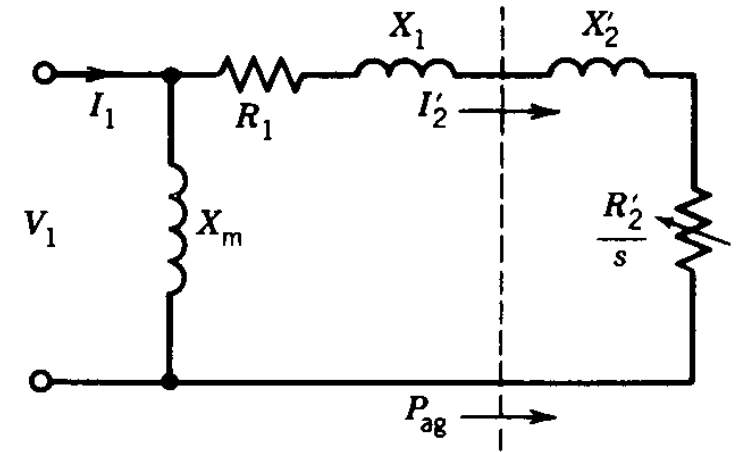

Example 3

Consider a Y-connected 7.5kW, 220V (line-line), 60Hz, 6-pole, Squirrel-cage motor with the following parameters: $R_1 = 0.294\Omega$, $R'_2 = 0.144\Omega$, $X_1 = 0.503\Omega$, $X'_2 = 0.209\Omega$, $X_m = 13.5\Omega$. Assume motor operates under load with slip $s = 0.03$ (3%).

e) Compute mechanical speed and power

Mechanical speed under load

$$n_{syn} = \frac{2}{p} \cdot 60 \cdot f_e = \frac{120}{6} \cdot 60 = 1200 \text{ rpm}$$

$$n = n_{syn} (1 - s) = 1200 \cdot 0.97 = 1164 \text{ rpm}$$

shaft speed

$$\omega_{rm} = \omega_{syn} \cdot (1 - s) = 125.66 \cdot 0.97 = 121.89 \%$$

$$P_m = T_m \cdot \omega_{rm}$$

Assume No Friction $T_{fric} = 0 \Rightarrow T_e = T_m$

$$P_m = 65.41 \cdot 121.89 = 7.9 \text{ kW} = \frac{7.9 \text{ kW}}{746 \text{ W}} = 10.69 \text{ Hp}$$

no need to convert to Horsepower

Looking ahead...

- Continue **Module 5**