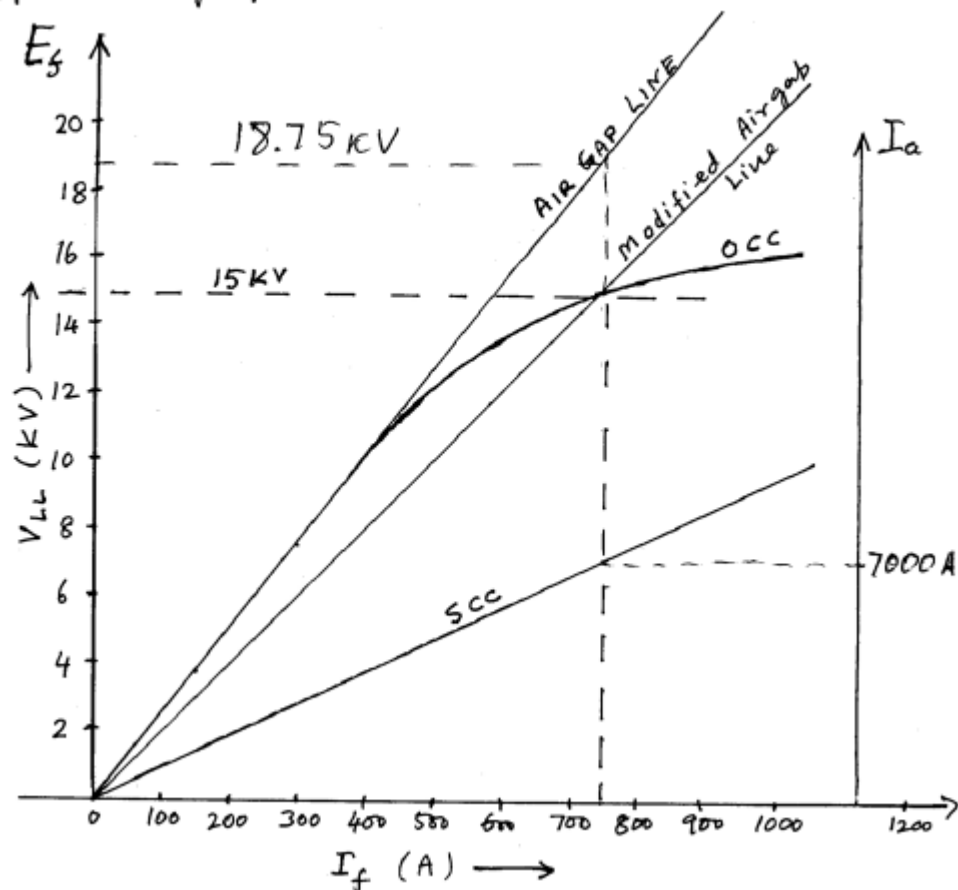


ELEC 342: Homework Assignment # 6, Synchronous Machines:

Textbook Chap. 6: Examples 6.2, 6.3, 6.5, and 6.7

Textbook Chap. 6: Problems: 6.3 only parts (a) and (b); 6.9; 6.12; 6.13; 6.30

6.3 (a) See graph



6.3 (b)

$$V_b = \frac{15 \times 10^3}{\sqrt{3}} = 8660.5 \text{ V}$$

$$I_b = \frac{195 \times 10^6}{\sqrt{3} \times 15 \times 10^3} = 7505.8 \text{ A}$$

$$Z_b = \frac{8660.5}{7505.8} = 1.1538 \text{ } \Omega$$

$$X_s|_{\text{unsat}} = \frac{18.75 \times 10^3}{\sqrt{3} \times 7000} = 1.5465 \text{ } \Omega$$

$$= \frac{1.5465}{1.1538} = 1.3404 \text{ p.u.}$$

$$X_s|_{\text{sat}} = \frac{15 \times 10^3}{\sqrt{3} \times 7000} = 1.2372 \text{ } \Omega \rightarrow 1.0723 \text{ p.u.}$$

6.9 Consider the phasor diagram of Fig. 6.17a and equivalent circuit of Fig. 6.14e.

$$V_t = \frac{11000}{\sqrt{3}} = 6350.9 \text{ V}$$

$$I_a = \frac{25 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 1312.2 \text{ A}$$

$$\theta = \cos^{-1} 0.85 = 31.8^\circ$$

$$I_a = 1312.2 \angle -31.8^\circ \text{ A}$$

The excitation voltage E_f is

$$E_f = 6350.9 \angle 0^\circ + 1312.2 \angle -31.8^\circ (0.45 + j4.5) = 11020.3 \angle 25.6^\circ \text{ V}$$

6.12 $V_t = \frac{220}{\sqrt{3}} = 127 \text{ V}$

$$I_a = \frac{10 \times 10^3}{\sqrt{3} \times 220} = 26.2 \text{ A}$$

(a) $\theta = \cos^{-1} 0.8 = 36.9^\circ$

$$I_a = 26.2 \angle -36.9^\circ \text{ A}$$

$$E_f = V_t \angle 0^\circ + I_a \angle -\theta^\circ \cdot (R_a + jX_s)$$

$$= 127 \angle 0^\circ + 26.2 \angle 0^\circ (0.25 + j5) = 233.8 \angle 25.6^\circ \text{ V}$$

(b) $E_f = V_t \angle 0^\circ + I_a \angle 0^\circ \cdot (0.25 + j5)$

$$= 127 \angle 0^\circ + 26.2 \angle 0^\circ (0.25 + j5) = 187.1 \angle 44.4^\circ \text{ V}$$

(c) $E_f = V_t \angle 0^\circ + I_a \angle \theta^\circ \cdot (0.25 + j5)$

$$= 127 \angle 0^\circ + 26.2 \angle 36.9^\circ (0.25 + j5) = 121.2 \angle 63.8^\circ \text{ V}$$

6.13 (a) $P_{\text{out}} = 10 \times 0.8 = 8 \text{ kW}$

Field current,

$$I_f = \frac{8}{187.1} \times 233.8 = 10 \text{ A}$$

Field loss,

$$P_f = 10^2 \times 5 = 500 \text{ W}$$

$$P_{\text{stator}} = 3 \times 26.2^2 \times 0.25 = 514.8 \text{ W}$$

$$P_{\text{core}} = 250 \text{ W}$$

$$P_{\text{rotation}} = 200 \text{ W}$$

$$P_{\text{loss}} = 200 + 250 + 514.8 + 500 = 1464.8 \text{ W}$$

$$P_{\text{in}} = 8000 + 1464.8 = 9464.8 \text{ W}$$

$$\text{Eff} = \frac{8000}{9464.8} \times 100\% = 84.3\%$$

(b) $P_{\text{out}} = 10 \times 1.0 = 10 \text{ kW}$

$$I_f = 8 \text{ A}$$

$$P_f = 8^2 \times 5 = 320 \text{ W}$$

$$P_{\text{loss}} = 200 + 250 + 514.4 + 320 = 1284.8 \text{ W}$$

$$P_{\text{in}} = 10000 + 1284.8 = 11284.8 \text{ W}$$

$$\text{Eff} = \frac{10000}{11284.8} \times 100\% = 88.6\%$$

(c) $P_{\text{out}} = 10 \times 0.8 = 8 \text{ kW}$

$$I_f = \frac{8}{187.1} \times 121.2 = 5.18 \text{ A}$$

$$P_f = 5.18^2 \times 5 = 134.3 \text{ W}$$

$$P_{\text{loss}} = 200 + 250 + 514.4 + 134.3 = 1099.1 \text{ W}$$

$$P_{\text{in}} = 8000 + 1099.1 = 9099.1 \text{ W}$$

$$\text{Eff} = \frac{8000}{9099.1} \times 100\% = 87.9\%$$

6.30 (a) $P=1 = \frac{V_t E_f}{0.95} \sin 25^\circ + \frac{V_t^2}{2} \left(\frac{1}{0.45} - \frac{1}{0.95} \right) \sin 50^\circ$
 $Q=0 = \frac{V_t E_f}{0.95} \cos 25^\circ - V_t^2 \left(\frac{\sin^2 25^\circ}{0.45} + \frac{\cos^2 25^\circ}{0.95} \right)$

Solving for E_f & V_t

$V_t = 0.9823 \text{ p.u.}$ $E_f = 1.299 \text{ p.u.}$

(Or From phasor diagram, $V_t \sin \delta = I_g X_g$ $V_t = \frac{0.9226 \times 0.45}{\sin 25^\circ} = 0.9824 \text{ p.u.}$

$E_f = V_t \cos \delta + I_d X_d = 0.9824 \cos 25^\circ + 0.4302 \times 0.95 = 1.299 \text{ p.u.}$)

(b) $P = V_t I_a \cos \theta$
 $1 = 0.9823 \times I_a \times 1.0$
 $I_a = 1.018 \text{ p.u.}$
 $I_d = 1.018 \sin 25^\circ = 0.4302 \text{ p.u.}$
 $I_g = 1.018 \cos 25^\circ = 0.9226 \text{ p.u.}$

