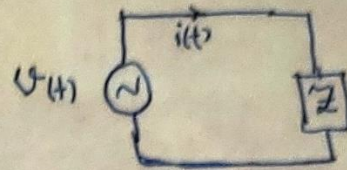




* The voltage source is connected to a load and draws current.

Let $\begin{cases} v(t) = \sqrt{2} \times 20 \times \cos(\omega t) \\ i(t) = \sqrt{2} \times 4 \times \cos(\omega t - 60^\circ) \\ \omega = 2\pi \times 60 \text{ Rad/s} \end{cases}$



- Calculate:
- 1) Phasor of voltage: $V = |V| \angle \theta_v$ $\begin{cases} |V| = ? & 20 \text{ V} \\ \theta_v = ? & 0^\circ \end{cases}$
 - 2) Phasor of current: $I = |I| \angle \theta_i$ $\begin{cases} |I| = ? & 4 \text{ A} \\ \theta_i = ? & -60^\circ \end{cases}$
 - 3) Active power: $|V||I|\cos\phi = 20 \times 4 \times \cos(60^\circ) = 40 \text{ W}$
 - 4) Reactive power: $|V||I|\sin\phi = 20 \times 4 \times \sin(60^\circ) = 40\sqrt{3} = 69.3 \text{ VAR}$
 - 5) Apparent power: $|V||I| = 20 \times 4 = 80 \text{ V.A}$
 - 6) Complex power: $S = P + jQ = 40 + j40\sqrt{3}$
 - 7) power factor: $\cos(60^\circ) = 40/80 = 0.5$
 - 8) power factor angle: $\phi = \theta_v - \theta_i = 60^\circ$
 - 9) Impedance Z : $Z = |Z| \angle \theta_z$ $\begin{cases} |Z| = ? & |V|/|I| = 20/4 = 5 \\ \theta_z = ? & \theta_v - \theta_i = 60^\circ \end{cases}$
 $Z = 5 \angle 60^\circ$

* Consider the following systems:

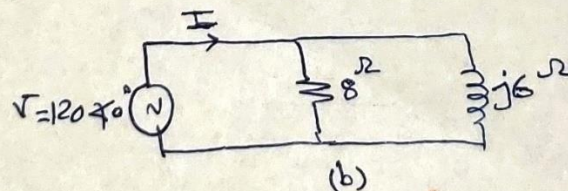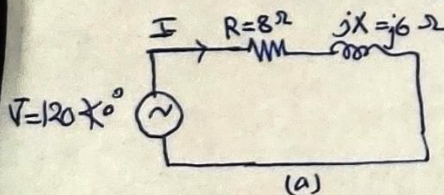

- For each case, calculate:
- 1) Phasor of current I :

(a) $I = \frac{120 \angle 0^\circ}{8 + j6} = \frac{120 \angle 0^\circ}{10 \angle 36.87^\circ} = 12 \angle -36.87^\circ$

(b) $I = \frac{120}{8} + \frac{120}{j6} \Rightarrow I = 15 - j20 = 25 \angle -53.13^\circ$
 - 2) Active power $|V||I|\cos\phi = 120 \times 12 \times \cos(36.87^\circ) = 1152 \text{ W}$



(b) $120 \times 25 \times \cos(53.13^\circ) = 1800 \text{ W}$
 - 3) Reactive power $|V||I|\sin\phi = 120 \times 12 \times \sin(36.87^\circ) = 864 \text{ VAR}$

(b) $120 \times 25 \times \sin(53.13^\circ) = 2400 \text{ VAR}$
 - 4) Apparent power $|V||I| = 120 \times 12 = 1440 \text{ V.A}$

(b) $120 \times 25 = 3000 \text{ V.A}$
- $\begin{cases} \cos(36.87^\circ) = 0.8 \\ \sin(36.87^\circ) = 0.6 \end{cases}$

$\begin{cases} \cos(53.13^\circ) = 0.6 \\ \sin(53.13^\circ) = 0.8 \end{cases}$

Consider one phase:

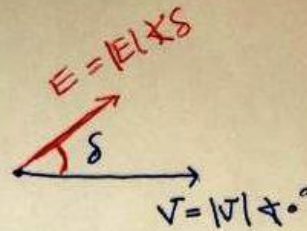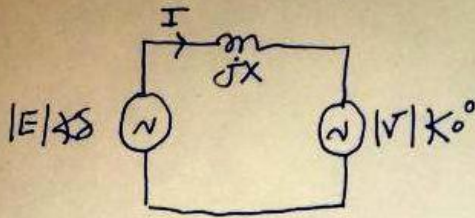

Solution

Complex power from left to right: $S = E \cdot I^*$

$$I = \frac{E - V}{jX} = \frac{|E| \angle \delta - |V| \angle 0^\circ}{jX} = \frac{|E| \angle (\delta - 90^\circ) - \frac{|V|}{X} \angle (-90^\circ)}{jX}$$

$$I^* = \frac{|E|}{X} \angle (90^\circ - \delta) - \frac{|V|}{X} \angle 90^\circ$$

$$S = EI^* = (|E| \angle \delta) \times \left(\frac{|E|}{X} \angle (90^\circ - \delta) - \frac{|V|}{X} \angle 90^\circ \right) =$$

$$\frac{|E|^2}{X} \angle 90^\circ - \frac{|E| \cdot |V|}{X} \angle (\delta + 90^\circ)$$

$$S = j \frac{|E|^2}{X} - \frac{|E| \cdot |V|}{X} \cos(\delta + 90^\circ) - j \frac{|E| \cdot |V|}{X} \sin(\delta + 90^\circ)$$

$$= \frac{|E| \cdot |V|}{X} \sin(\delta) + j \left(\frac{|E|^2 - |E| \cdot |V| \cos \delta}{X} \right)$$

$$S = P + jQ$$


$$\Rightarrow \begin{cases} P = \frac{|E| \cdot |V|}{X} \sin \delta \\ Q = \frac{|E|^2 - |E| \cdot |V| \cos \delta}{X} \end{cases}$$

for the three-phase system:

$$\begin{cases} P = 3 \left(\frac{|E| \cdot |V|}{X} \sin \delta \right) \\ Q = 3 \left(\frac{|E|^2 - |E| \cdot |V| \cos \delta}{X} \right) \end{cases}$$

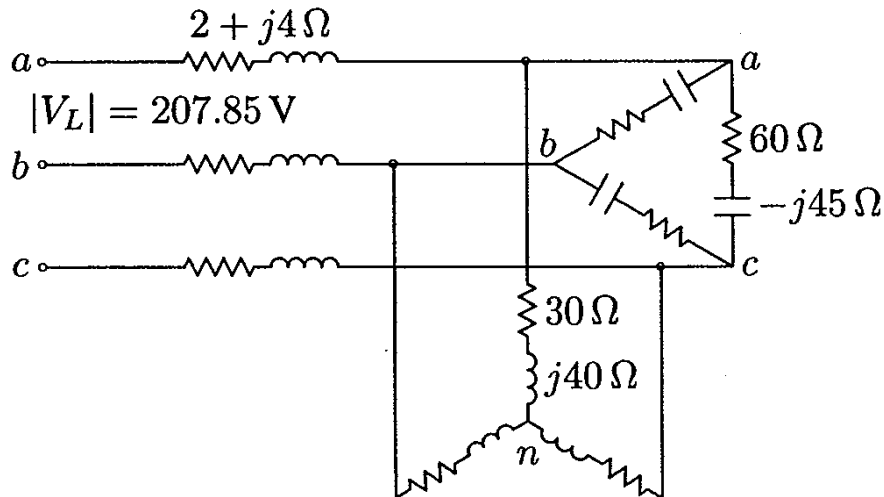Problem:

A three-phase line has an impedance of $2 + j4 \Omega$ as shown in Figure .



The line feeds two balanced three-phase loads that are connected in parallel. The first load is Y-connected and has an impedance of $30 + j40 \Omega$ per phase. The second load is Δ -connected and has an impedance of $60 - j45 \Omega$. The line is energized at the sending end from a three-phase balanced supply of line voltage 207.85 V. Taking the phase voltage V_a as reference, determine:

- The current, real power, and reactive power drawn from the supply.
- The line voltage at the combined loads.
- The current per phase in each load.
- The total real and reactive powers in each load and the line.

Solution:


(a) The Δ -connected load is transformed into an equivalent Y. The impedance per phase of the equivalent Y is

$$Z_2 = \frac{60 - j45}{3} = 20 - j15 \, \Omega$$

The phase voltage is

$$V_1 = \frac{207.85}{\sqrt{3}} = 120 \, \text{V}$$

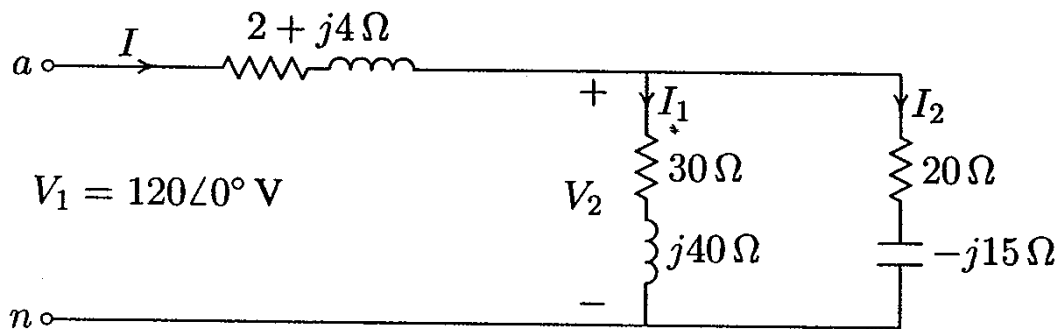The single-phase equivalent circuit is shown in Figure



The total impedance is

$$\begin{aligned} Z &= 2 + j4 + \frac{(30 + j40)(20 - j15)}{(30 + j40) + (20 - j15)} \\ &= 2 + j4 + 22 - j4 = 24 \, \Omega \end{aligned}$$

With the phase voltage V_{an} as reference, the current in phase a is

$$I = \frac{V_1}{Z} = \frac{120\angle 0^\circ}{24} = 5 \, \text{A}$$

The three-phase power supplied is

$$S = 3V_1 I^* = 3(120\angle 0^\circ)(5\angle 0^\circ) = 1800 \, \text{W}$$

(b) The phase voltage at the load terminal is

$$\begin{aligned} V_2 &= 120\angle 0^\circ - (2 + j4)(5\angle 0^\circ) = 110 - j20 \\ &= 111.8\angle -10.3^\circ \text{ V} \end{aligned}$$

The line voltage at the load terminal is

$$V_{2ab} = \sqrt{3} \angle 30^\circ V_2 = \sqrt{3} (111.8)\angle 19.7^\circ = 193.64\angle 19.7^\circ \text{ V}$$

(c) The current per phase in the Y-connected load and in the equivalent Y of the Δ load is

$$\begin{aligned} I_1 &= \frac{V_2}{Z_1} = \frac{110 - j20}{30 + j40} = 1 - j2 = 2.236\angle -63.4^\circ \text{ A} \\ I_2 &= \frac{V_2}{Z_2} = \frac{110 - j20}{20 - j15} = 4 + j2 = 4.472\angle 26.56^\circ \text{ A} \end{aligned}$$

The phase current in the original Δ -connected load, i.e., I_{ab} is given by

$$I_{ab} = \frac{I_2}{\sqrt{3}\angle -30^\circ} = \frac{4.472\angle 26.56^\circ}{\sqrt{3}\angle -30^\circ} = 2.582\angle 56.56^\circ \text{ A}$$

(d) The three-phase power absorbed by each load is

$$\begin{aligned} S_1 &= 3V_2I_1^* = 3(111.8\angle -10.3^\circ)(2.236\angle 63.4^\circ) = 450 \text{ W} + j600 \text{ var} \\ S_2 &= 3V_2I_2^* = 3(111.8\angle -10.3^\circ)(4.472\angle -26.56^\circ) = 1200 \text{ W} - j900 \text{ var} \end{aligned}$$

The three-phase power absorbed by the line is

$$S_L = 3(R_L + jX_L)|I|^2 = 3(2 + j4)(5)^2 = 150 \text{ W} + j300 \text{ var}$$

It is clear that the sum of load powers and line losses is equal to the power delivered from the supply, i.e.,

$$\begin{aligned} S_1 + S_2 + S_L &= (450 + j600) + (1200 - j900) + (150 + j300) \\ &= 1800 \text{ W} + j0 \text{ var} \end{aligned}$$