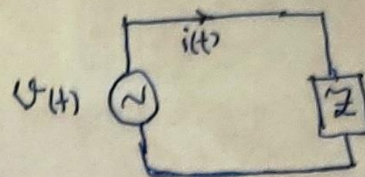




* The voltage source is connected to a load and draws current.

Let $\begin{cases} v(t) = \sqrt{2} \times 20 \times \cos(\omega t) \\ i(t) = \sqrt{2} \times 4 \times \cos(\omega t - 60^\circ) \\ \omega = 2\pi \times 60 \text{ Rad/s} \end{cases}$



- Calculate:
- 1) Phasor of voltage: $V = |V| \angle \theta_v$ $\begin{cases} |V| = ? \\ \theta_v = ? \end{cases}$
 - 2) Phasor of current: $I = |I| \angle \theta_i$ $\begin{cases} |I| = ? \\ \theta_i = ? \end{cases}$
 - 3) Active power:
 - 4) Reactive power:
 - 5) Apparent power:
 - 6) Complex power:
 - 7) power factor:
 - 8) power factor angle:
 - 9) Impedance Z : $Z = |Z| \angle \theta_z$ $\begin{cases} |Z| = ? \\ \theta_z = ? \end{cases}$


* Consider the following systems:

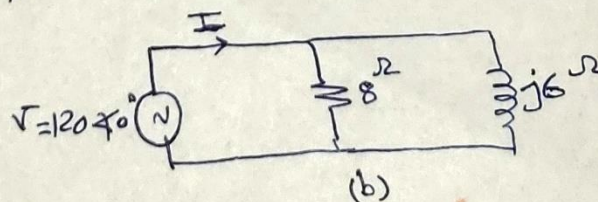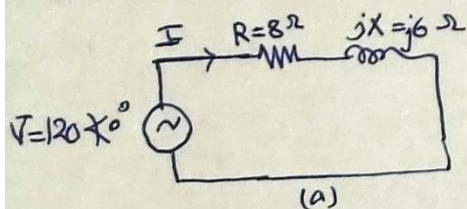

For each case, calculate:

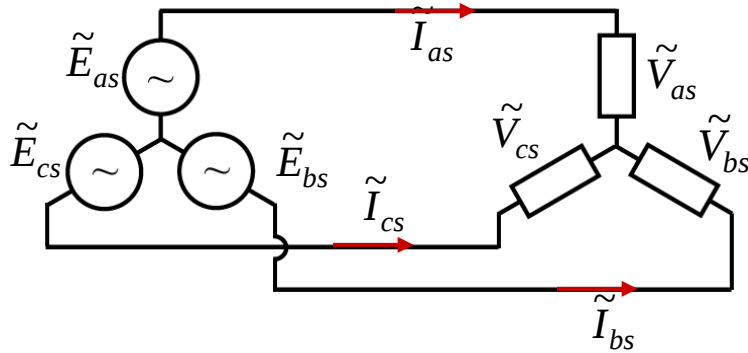- 1) Phasor of current I .
- 2) Active power
- 3) Reactive power
- 4) Apparent power

Assume that we have the following circuit and the line is purely inductive with reactance X . Formulate the active and reactive power if the phasors of voltage on the left-side lead the phasors of the voltage on the right-side, by the angle δ .



B.4 Δ -Y TRANSFORMATION OF LOAD

Sometimes it might be necessary to transform a Δ load to a Y load and vice versa. Consider the equivalent Δ load and Y load shown in Fig. B.8. For the Δ load,

$$\begin{aligned}
 I_a &= I_{ab} - I_{ca} = \frac{V_{ab} - V_{ca}}{Z_{\Delta}} \\
 &= \frac{(V_a - V_b) - (V_c - V_a)}{Z_{\Delta}} \\
 &= \frac{3V_a - (V_a + V_b + V_c)}{Z_{\Delta}} \\
 &= \frac{V_a}{Z_{\Delta}/3}
 \end{aligned} \tag{B.59}$$

For the Y load,

$$I_a = \frac{V_a}{Z_Y} \tag{B.60}$$

From Eqs. B.59 and B.60,

$$Z_Y = \frac{Z_{\Delta}}{3} \tag{B.61}$$

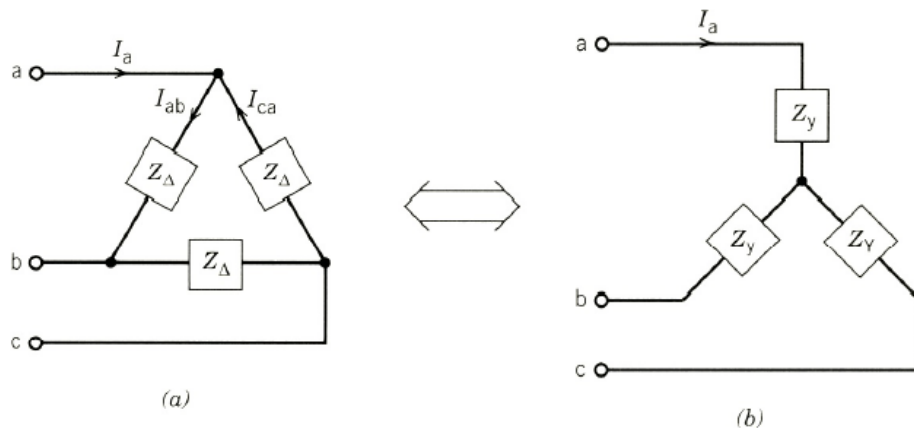


FIGURE B.8 Equivalent Δ load and Y load.

B.5 PER-PHASE EQUIVALENT CIRCUIT

Consider the three-phase balanced power system shown in Fig. B.9a, in which the source and the load are connected in delta, and they are connected through the transmission line impedances Z_l . This three-phase system can be analyzed by deriving a “per-phase” equivalent circuit as shown in Fig. B.9b, in which the source is represented by an equivalent Y voltage, V_a , and the load is represented by an equivalent Y load, Z_Y .

If the line voltage, V_{ab} , is the reference voltage, then

$$V_a = \frac{|V_{ab}|}{\sqrt{3}} \angle -30^\circ \quad (\text{B.62})$$

and

$$Z_Y = \frac{Z_\Delta}{3} \quad (\text{B.63})$$


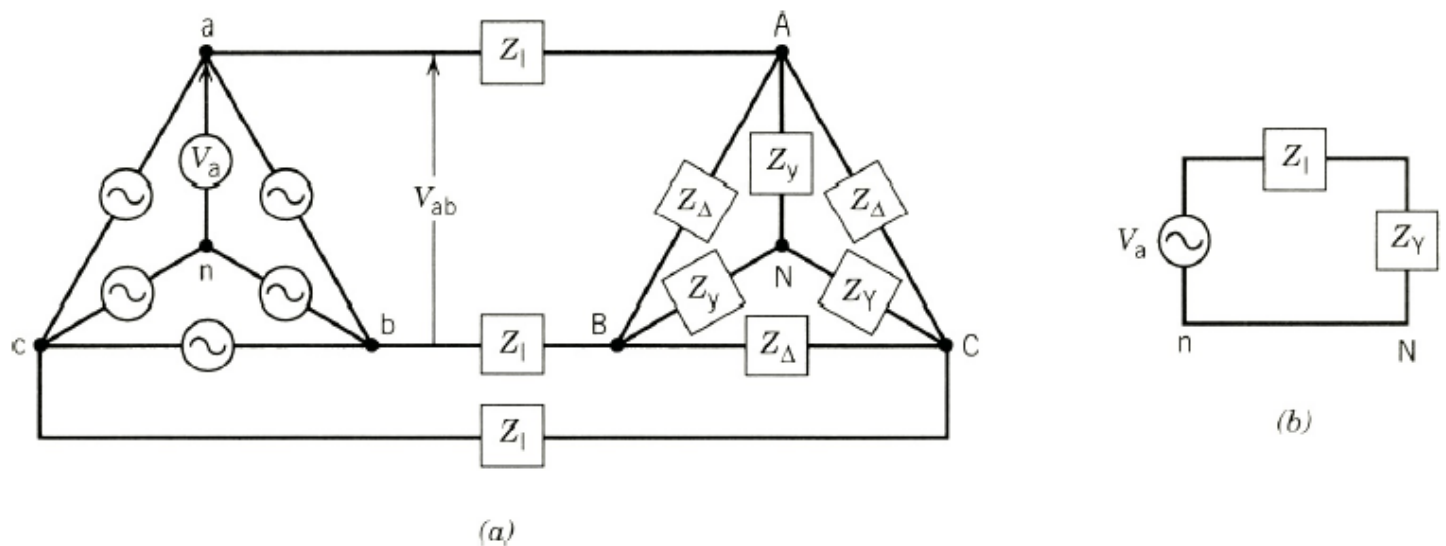


FIGURE B.9 Three-phase power system. (a) Circuit. (b) Per-phase equivalent circuit.

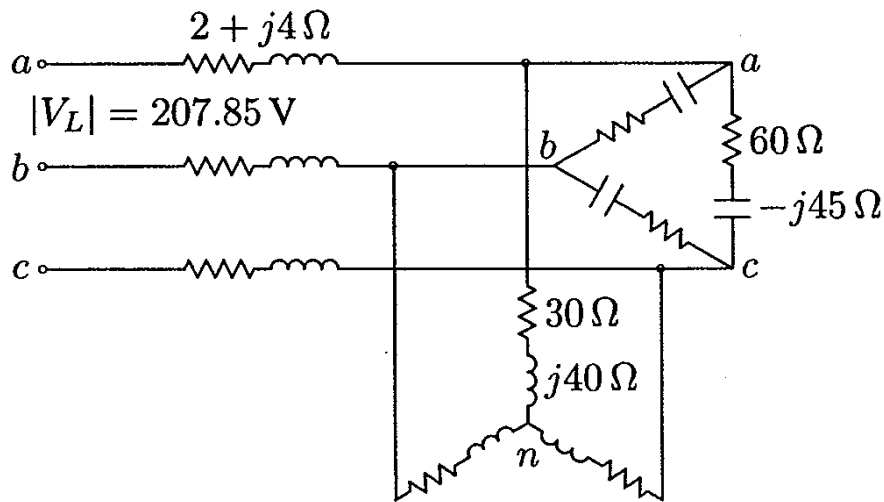Problem:

A three-phase line has an impedance of $2 + j4 \Omega$ as shown in Figure .



The line feeds two balanced three-phase loads that are connected in parallel. The first load is Y-connected and has an impedance of $30 + j40 \Omega$ per phase. The second load is Δ -connected and has an impedance of $60 - j45 \Omega$. The line is energized at the sending end from a three-phase balanced supply of line voltage 207.85 V. Taking the phase voltage V_a as reference, determine:

- The current, real power, and reactive power drawn from the supply.
- The line voltage at the combined loads.
- The current per phase in each load.
- The total real and reactive powers in each load and the line.