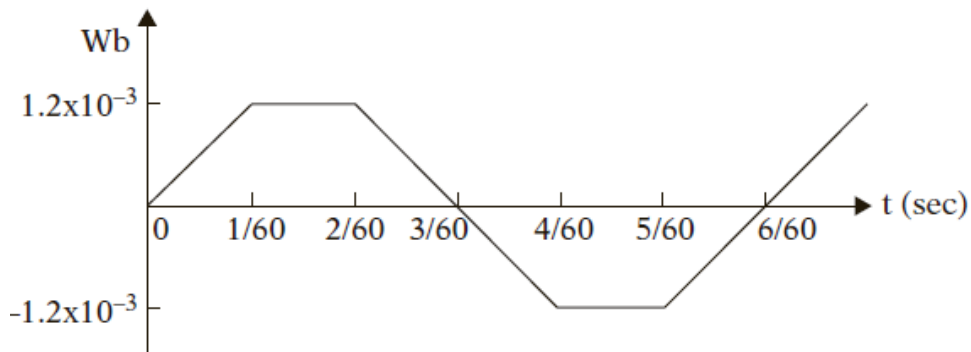


P 2.2):

The flux in the core of a 1 ϕ transformer varies with time as shown in Fig. P2.2. The primary coil has 400 turns and the secondary coil has 100 turns. Sketch the waveform of the induced voltage e_1 in the primary winding.

**FIGURE P2.2****Solution:**

$$0 < t < \frac{1}{60} \text{ sec}$$


$$e = N \frac{d\Phi}{dt} = 400 \times \frac{1.2 \times 10^{-3}}{\frac{1}{60}} = 28.8 \text{ V}$$

$$\frac{1}{60} < t < \frac{2}{60} \text{ sec}$$

$$e = N \times 0 = 0$$

$$\frac{2}{60} < t < \frac{4}{60} \text{ sec}$$

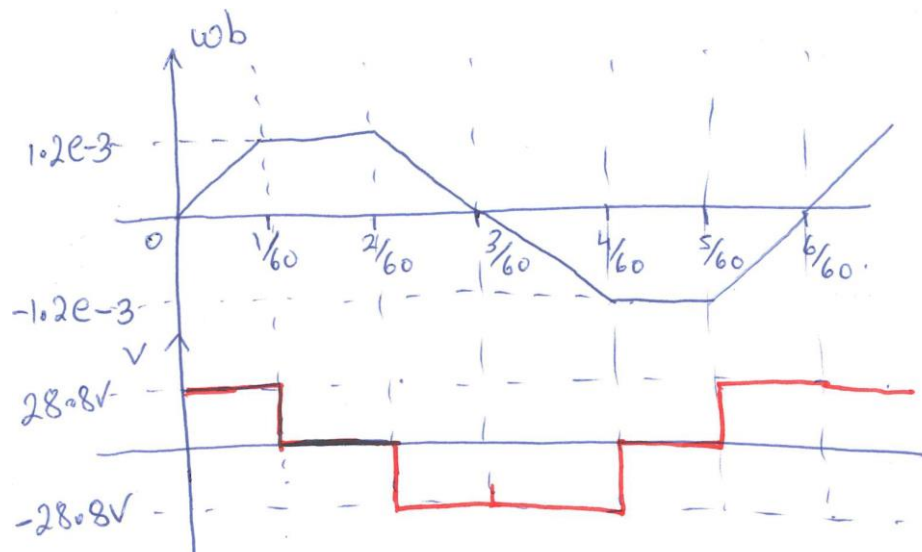
$$e = -400 \times \frac{2 \times 1.2 \times 10^{-3}}{\frac{2}{60}} = -28.8 \text{ V}$$



Q2):

An iron “doughnut” (toroid) with two coils is shown in
 $N_1 = 100$ turns and $N_2 = 200$ turns, $\mu_r = 10^4/4\pi$. Calculate L_{12} .

Also calculate L_{21}, L_{11}, L_{22} .

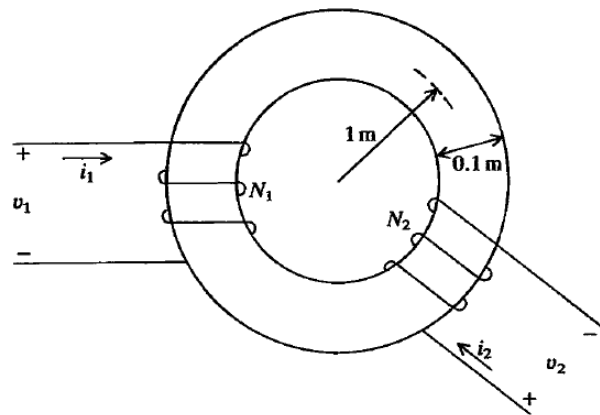

Remember:

$$\lambda_1 = L_{11}i_1 + L_{12}i_2$$

$$\lambda_2 = L_{21}i_1 + L_{22}i_2$$

Solution:

$$\mathcal{R}_m = \frac{1}{\mu A} = \frac{(2\pi)(1)}{(4\pi \times 10^{-7})\left(\frac{1}{4\pi} \times 10^4\right)\pi(0.05)^2} = 8 \times 10^5 \text{ H}^{-1}$$

$$L_{12} = -\frac{N_1 N_2}{\mathcal{R}_m} = -\frac{(100)(200)}{8 \times 10^5} = -25 \text{ mH}$$


$$\lambda_1 = L_{11} i_1 + L_{12} i_2$$

$$\lambda_1 \Big|_{i_1=0} = L_{12} i_2$$

$$L_{12} = \frac{\lambda_1}{i_2} = \frac{N_1 \phi_1}{i_2} = - \frac{N_1 N_2 i_2}{i_2 R}$$

$$\lambda_1 \Big|_{i_2=0} = L_{11} i_1$$
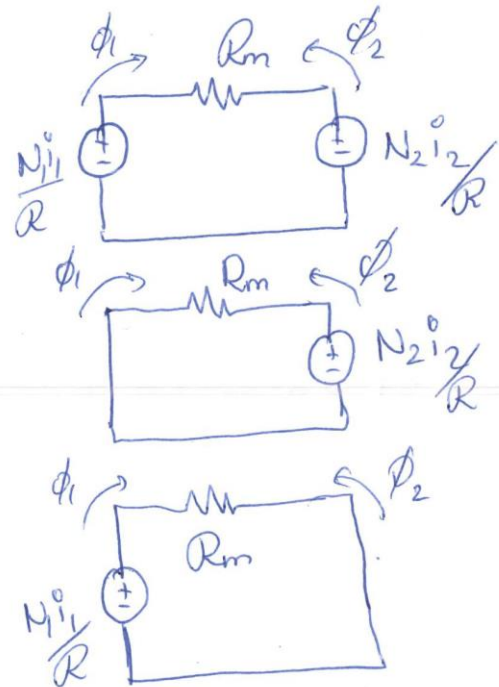
$$L_{11} = \frac{\lambda_1}{i_1} = \frac{N_1 \phi_1}{i_1} = \frac{N_1 \cdot N_1 i_1}{i_1 R}$$



$$\lambda_2 = L_{22} i_2 + L_{21} i_1$$

$$\lambda_2 \Big|_{i_1=0} = L_{22} i_2$$

$$L_{22} = \frac{\lambda_2}{i_2} = \frac{N_2 \phi_2}{i_2} = \frac{N_2 \cdot N_2 i_2}{i_2 \cdot R}$$

$$\lambda_2 \Big|_{i_2=0} = L_{21} i_1$$

$$L_{21} = \frac{\lambda_2}{i_1} = \frac{N_2 \phi_2}{i_1} = - \frac{N_2 N_1 i_1}{i_1 R}$$

$$\begin{array}{l|l|l|l} L_{11} = \frac{N_1^2}{R} & L_{12} = -\frac{N_1 N_2}{R} & L_{21} = -\frac{N_1 N_2}{R} & L_{22} = \frac{N_2^2}{R} \\ \hline = \frac{100^2}{8 \times 10^5} & = -\frac{100 \times 200}{8 \times 10^5} & = -\frac{2 \times 10^4}{8 \times 10^5} & = \frac{4 \times 10^4}{8 \times 10^5} \\ \hline = 12.5 \text{ mH} & = -25 \text{ mH} & = -25 \text{ mH} & = 50 \text{ mH} \end{array}$$

Q3):

Two coupled coils have the following parameters: $r_1 = 10\ \Omega$, $L_{l1} = 0.1 L_{11}$, $r_2 = 2.5\ \Omega$, $L_{l2} = 0.1 L_{22}$, $L_{11} = 100\text{ mH}$, $N_1 = 100$ turns, $L_{22} = 25\text{ mH}$, $N_2 = 50$ turns. Develop an equivalent T circuit with (a) winding 1 as the reference winding and (b) winding 2 as reference winding.

Solution:

$$(a) \quad L_{m1} = L_{11} - L_{l1} = 90\text{ mH}$$

$$L'_{l2} = \left(\frac{N_1}{N_2}\right)^2 L_{l2} = \left(\frac{100}{50}\right)^2 (2.5 \times 10^{-3}) = 10\text{ mH}$$

$$r'_2 = \left(\frac{N_1}{N_2}\right)^2 r_2 = \left(\frac{100}{50}\right)^2 (2.5) = 10\ \Omega$$

$$(b) \quad L_{m2} = L_{22} - L_{l2} = 22.5\text{ mH}$$

$$L'_{l1} = \left(\frac{N_2}{N_1}\right)^2 L_{l1} = \left(\frac{50}{100}\right)^2 (10 \times 10^{-3}) = 2.5\text{ mH}$$

$$r'_1 = \left(\frac{N_2}{N_1}\right)^2 r_1 = \left(\frac{50}{100}\right)^2 (10) = 2.5\ \Omega$$

P 2.16):

A 1 ϕ , 100 kVA, 11000/2200 V, 60 Hz transformer has the following parameters.

$$R_{HV} = 6.0 \, \Omega$$

$$R_{LV} = 0.28 \, \Omega$$

$$L_{HV} = 0.08 \, \text{H}$$

$$L_{LV} = 0.0032 \, \text{H}$$

$$L_{m(HV)} = 160 \, \text{H}$$

$$R_{c(HV)} = 125 \, \text{k}\Omega$$

Obtain an equivalent circuit of the transformer:

- (a) Referred to the high-voltage side.
- (b) Referred to the low-voltage side.



Solution:

(a) $n = \frac{11000}{2200} = 5$

$$X_{L1} = 377 \times 0.08 = 30.16 \, \Omega, \quad X_{L2}' = 5^2 \times 377 \times 0.0032 = 30.16 \, \Omega$$

$$X_{m1} = 377 \times 160 = 60.32 \, \text{k}\Omega, \quad R_{c1} = 125 \, \text{k}\Omega$$
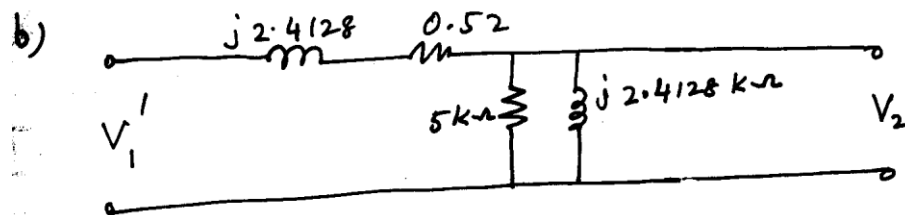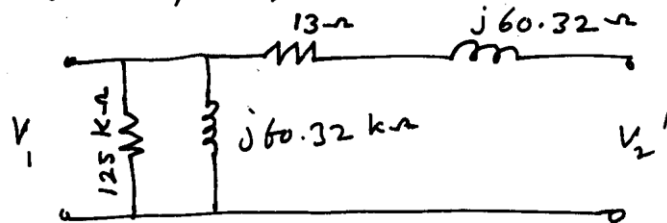
$$R_1 = 6.0 \, \Omega, \quad R_2' = 5^2 \times 0.28 = 7.0 \, \Omega$$



Q5):

A 1 ϕ , 100 kVA, 1000/100 V transformer gave the following test results:

open-circuit test (HV side open)

100 V, 6.0 A, 400 W

short-circuit test

50 V, 100 A, 1800 W

- Determine the rated voltage and rated current for the high-voltage and low-voltage sides.
- Derive an approximate equivalent circuit referred to the HV side.

Solution:

$$a) V_{H(\text{rated})} = 1000 \text{ V}, I_{H(\text{rated})} = \frac{100 \times 10^3}{1000} = 100 \text{ A.}$$

$$V_{L(\text{rated})} = 100 \text{ V}, I_{L(\text{rated})} = \frac{100 \times 10^3}{100} = 1000 \text{ A.}$$

b) From open circuit test,

$$R_{CL} = \frac{100^2}{400} = 25 \Omega.$$

$$I_{CL} = \frac{100}{25} = 4 \text{ A.}$$

$$I_{mL} = \sqrt{6^2 - 4^2} = 4.47 \text{ A}$$

$$X_{mL} = \frac{100}{4.47} = 22.37 \Omega$$

$$\text{Turns ratio } a = \frac{1000}{100} = 10$$

Refer to high voltage side,

$$R_{CH} = 25 \times 10^2 = 2500 \Omega, X_{mH} = 2237 \Omega$$

From short circuit test,

$$R_{eqH} = \frac{1800}{100^2} = 0.18 \Omega.$$

$$Z_{eqH} = \frac{50}{100} = 0.5 \Omega$$

$$X_{eqH} = \sqrt{0.5^2 - 0.18^2} = 0.4665 \Omega$$

Equivalent circuit referred to H.V. side

