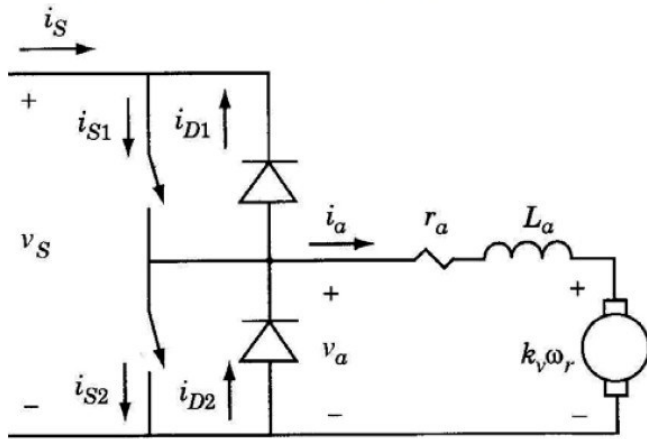


Assume a PM DC motor is driven by a PWM converter shown below. The motor shaft is connected to a constant speed mechanical system (load) with $\omega_r = 10 \text{ r/s}$. The motor parameters are $k_v = 0.5 \text{ Vs/r}$ and $r_a = 1\Omega$. The converter is supplied from a 10 V dc source. Initially, in **Mode 1**, the duty cycle $d = 0.6$ (60% on and 40% off). The corresponding voltage and current waveforms are depicted on the figure below (first interval), wherein the average values of the voltage $\bar{v}_a = 6\text{V}$ and current $\bar{i}_a = 1\text{A}$ are also shown. Assume that the duty cycle has


changed to 0.4 (40% on and 60% off), as shown on the figure. This is a new steady-state operation in **Mode 2**:



(a) (5pts): Determine whether machine is **Motoring** or **Generating** in each **Mode**? and circle appropriate

(b) (5pts): Find the value of the average voltage $\bar{v}_a$ for the **Mode 2** and show it on the figure

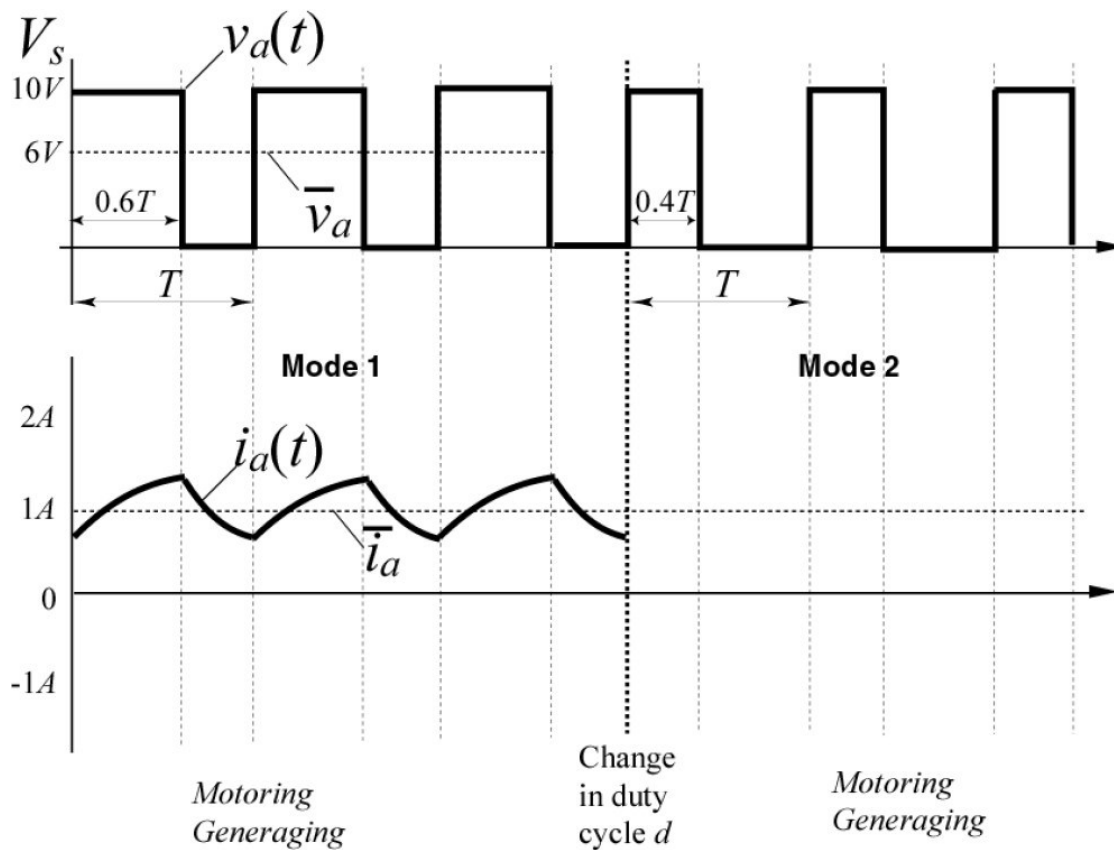(c) (5pts): Sketch the steady-state waveform of the current $\bar{i}_a$ in Mode 2 and find/show its average value



A dc shunt machine (10 kW, 250 V, 1200 rpm) has $R_a = 0.25 \, \Omega$. The machine is connected to a 250 V dc supply, draws rated armature current, and rotates at 1200 rpm.

- (a) Determine the generated voltage, the electromagnetic power developed, and the torque developed.
 - (b) The mechanical load on the motor shaft is thrown off, and the motor draws 4 A armature current.
 - (i) Determine the rotational loss.
 - (ii) Determine speed
-

P 4.38):

A dc motor is mechanically connected to a constant-torque load. When the armature is connected to a 120 V dc supply, it draws an armature current of value 8 A and runs at 1800 rpm. The armature resistance is $R_a = 0.08 \, \Omega$. Accidentally, the field circuit breaks and the flux drops to the residual flux, which is only 5% of the original flux.

- (a) Determine the value of the armature current immediately after the field circuit breaks (i.e., before the speed has had time to change from 1800 rpm).
- (b) Determine the theoretical final speed of the motor after the field circuit breaks.