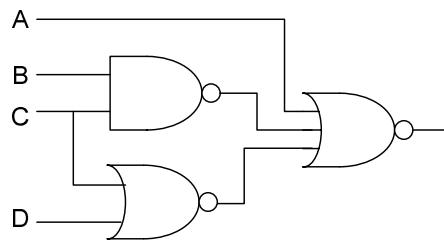


10) Consider the following circuit.



a) Assuming the vectors $(A=0, B=0, C=0, D=0)$ and $(A=0, B=1, C=1, D=1)$ are applied (in that order). During testing, you only have access to the single output signal. What is the fault coverage obtained (assuming a single stuck-at fault model)? Show your work. [4 marks]