

Radio-Frequency IC Design

Lecture 2: Passive RLC Networks

ELEC 404

Acknowledgement: *RF Microelectronics*. B. Razavi



©Sudip Shekhar

Not to be copied, used, or revised without explicit written permission from the copyright owner.

Passive RLC Networks


Applications of Resonant Networks

- **Tuning**
- **Matching and Impedance Transformation**

Examples

- **Low Noise Amplifiers (LNAs)**
- **Voltage Controlled Oscillators (VCOs)**
- **Mixers**
- **Power Amplifiers (PAs)**
- **Band Pass Filters (BPFs)**
- **Duplexers**
- **Baluns**

Parallel RLC Network

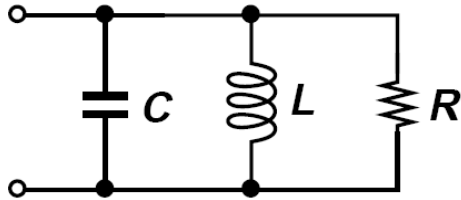

@low freq. @high freq. @ ω_0

At resonance,


- 1pF & 1nH \rightarrow 5GHz
- Remember the 2π !

Quality Factor, Q

$$Q = \omega \frac{\textit{Energy Stored}}{\textit{Average Power Dissipated}}$$


At resonance,

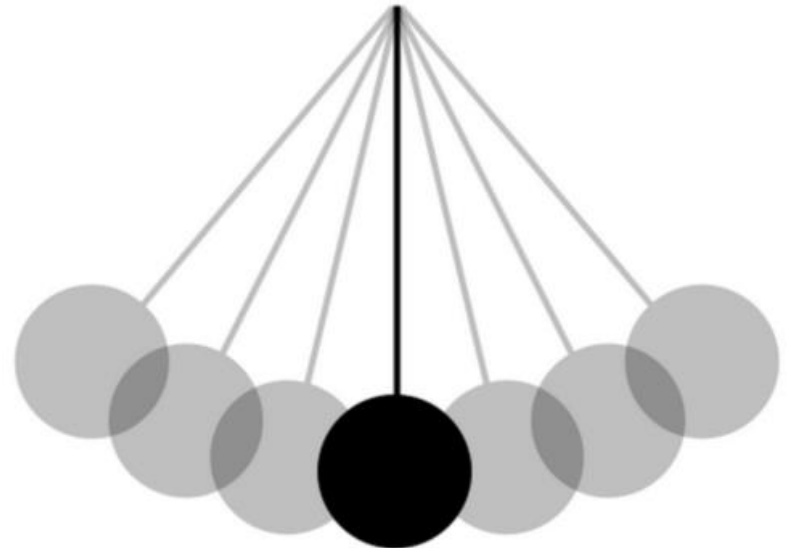- Dimensionless
- Defined at both resonance and non-resonance



Q for a Parallel RLC Network
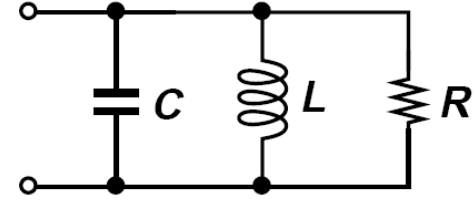
$$E_{Total} = E_{PK,L} = E_{PK,C} = E_{inst,L} + E_{inst,C}$$




Current in L,C for a || RLC Network

At resonance,

- **Large currents ($Q \uparrow$) may flow**
- **Functionality and Reliability Concerns**

Series RLC Network

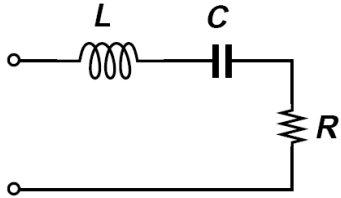

@low freq. @high freq. @ ω_0

$$Z(\omega) = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

At resonance,

$$\omega_0 = \frac{1}{\sqrt{LC}} \cdot |Z_L| = |Z_C| = \sqrt{\frac{L}{C}}$$

Expressions for Q:

Voltage across L,C for a Series RLC


At resonance,

- **Large voltages ($Q \uparrow$) may appear**
- **High Field \rightarrow Breakdown \rightarrow Functionality and Reliability Concerns**
- **Utilize smartly for voltage amplification – eg. in LNA**

Maximum Power Transfer Theorem

-
- If Z_L is constrained or specified already (say, 50Ω) insert an impedance transformer or a matching-network to match with Z_s .

Impedance Transformation


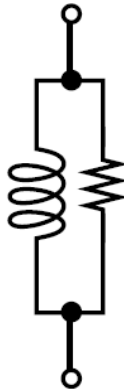


Proof for two Q's to be the same
Equating Real and imaginary parts,
$$R_s = \frac{R_p \omega^2 L_p^2}{R_p^2 + (\omega L_p)^2}; \omega L_s = \frac{\omega L_p R_p^2}{R_p^2 + (\omega L_p)^2}$$
$$Q_{series} = \frac{\omega L_s}{R_s} = \frac{\omega L_p R_p^2}{R_p \omega^2 L_p^2} = \frac{R_p}{\omega L_p} = Q_{||}$$

- **Generic formula for narrowband transformation:**

$$R_p = R_s(1 + Q^2)$$
$$X_p = X_s(1 + Q^{-2})$$

Series/Parallel Transformation

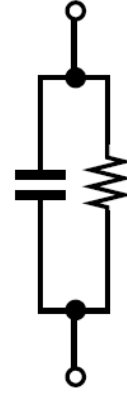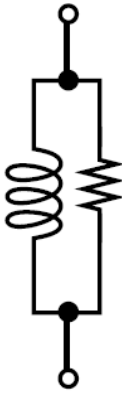

$$R_p = R_s(1 + Q^2)$$
$$X_p = X_s(1 + Q^{-2})$$





Impedance Transformation: L-Match

- **Upconvert 50Ω to 200Ω @ 5GHz:**

$$R_p = R_s(1 + Q^2)$$
$$X_p = X_s(1 + Q^{-2})$$

Choice of Matching Network

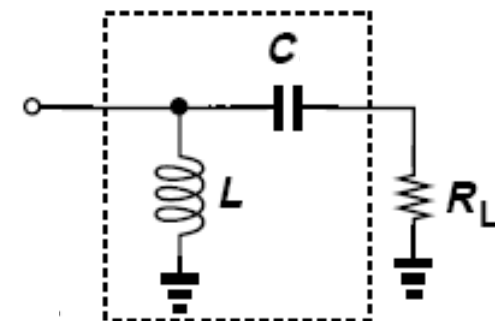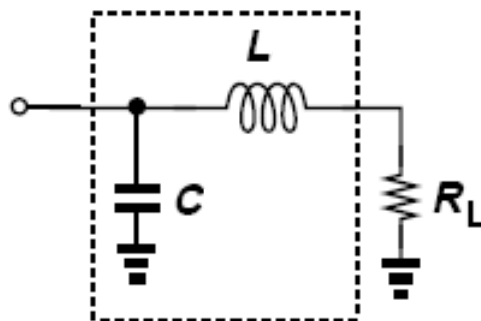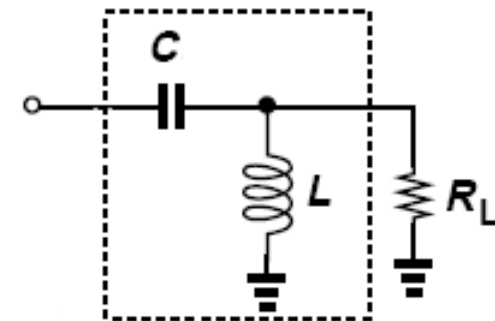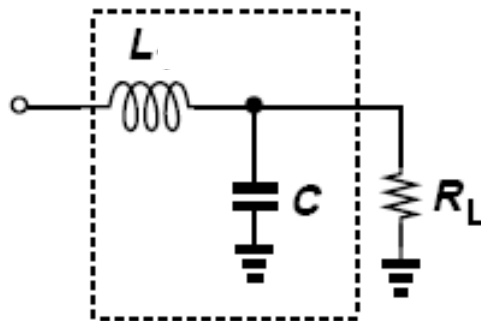- Degrees of Freedom
- High-pass or low-pass
- Smallest area
- Parasitics
- Quality of the match (S_{11})



Tapped-Capacitor Match - I

- Used in Colpitts Oscillator, LNA O/P Match
- 3 degrees of freedom (η , ω_0 , Q)

$$Z_{2s} = \frac{R_2 \frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}} = \frac{R_2}{1 + sC_2R_2}$$

$$Z_{in} = \frac{1}{sC_1} + \frac{R_2}{1 + sC_2R_2} = \frac{1 + sC_2R_2 + sC_1R_2}{sC_1 + s^2C_2C_1R_2} = \frac{1 + j\omega R_2(C_1 + C_2)}{j\omega C_1 - \omega^2 C_2 C_1 R_2}$$

$$Y_{in} = \frac{\omega^2 R_2 C_1^2}{1 + \omega^2 R_2^2 (C_1 + C_2)^2} + \frac{j\omega C_1 [1 + \omega^2 C_2 R_2^2 (C_1 + C_2)]}{1 + \omega^2 R_2^2 (C_1 + C_2)^2}$$

- **At high frequency,**

$$Y_{in} = \frac{1}{R_2} \left(\frac{C_1}{C_1 + C_2} \right)^2 + j\omega \frac{C_1 C_2}{C_1 + C_2} = \frac{\eta^2}{R_2} + j\omega C_{series}$$


Tapped-Capacitor Match - II



Tapped-Inductor Match

- **Used in Hartley Oscillator**
- **Uses two inductors**

π -Match

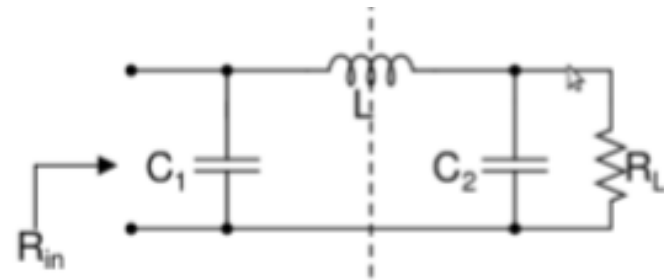

- Analyze by splitting L into L_1 and L_2 .
- Consider the network as two L-match networks, both transforming R_L and R_{in} to an intermediate resistance R_I
- $Q_{\text{overall}} = Q_{\text{left}} + Q_{\text{right}}$