

Integrated Circuits for Phase-Locked Loops

Lecture : Device Noise


Adapted from *The Design of CMOS Radio-Frequency Integrated Circuits*. T. Lee. Copyright 2004 Cambridge.
Adapted from *RF Microelectronics*. B. Razavi. Copyright 2012 Prentice Hall




©Sudip Shekhar

Not to be copied, used, or revised without explicit written permission from the copyright owner.

Noise – Random Process

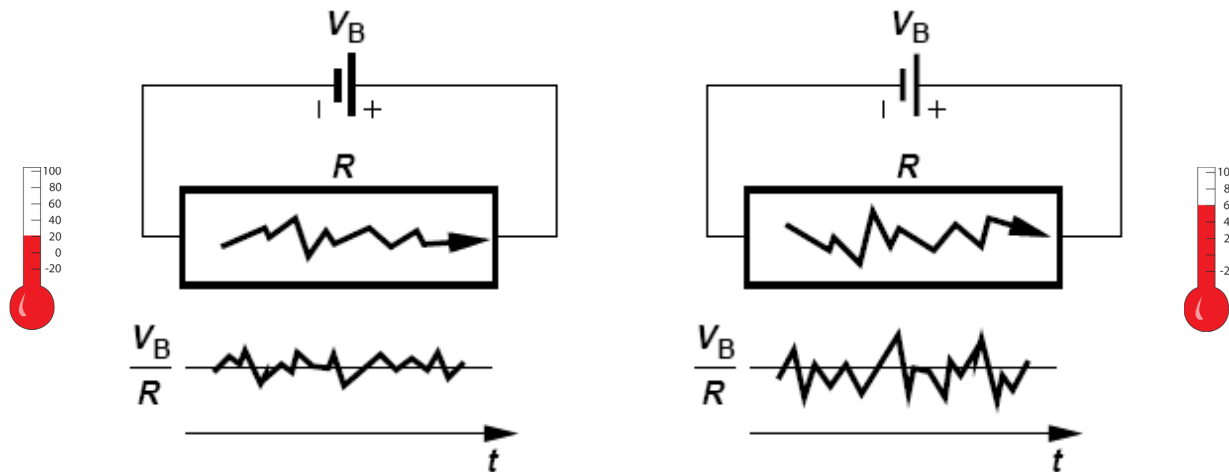

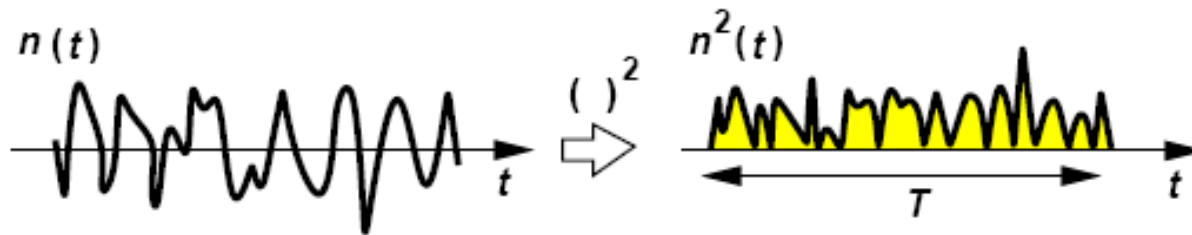
- Avg. current = V_B/R but the instantaneous current displays random values
- Avg. Power of noise:




$$P_n = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T n^2(t) dt$$

- T must be long enough to accommodate several cycles of the lowest frequency.

Measurement of Spectrum & PSD

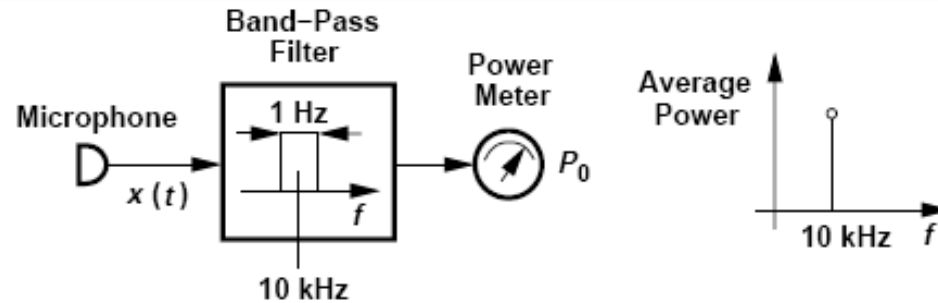

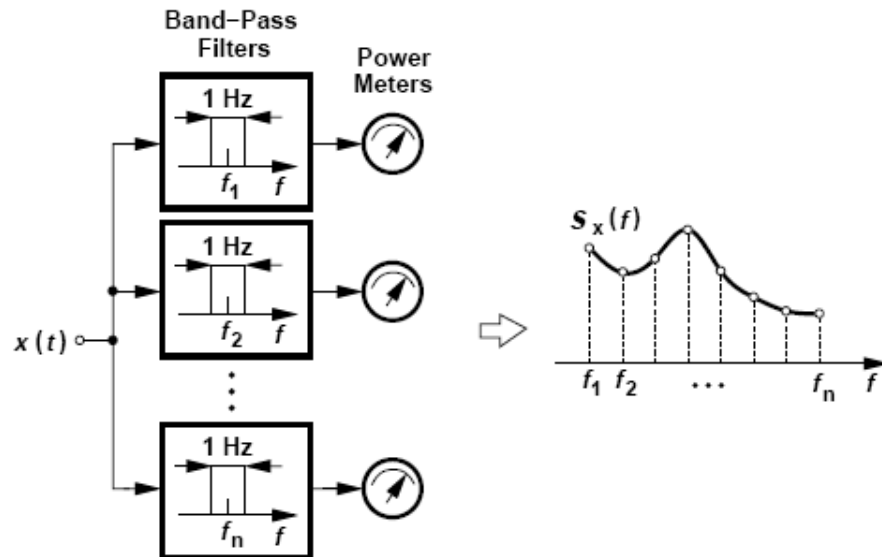- To measure frequency content at 10kHz, filter out the remainder of the spectrum and measure the average power of the 10kHz component.




$$\int_0^{\infty} S_x(f) df = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T x^2(t) dt$$


- Total area under $S_x(f)$ represents the average power carried by $x(t)$
- PSD is defined as the Fourier Transform of the autocorrelation of a signal

Two-sided/One-sided PSD

Two-Sided

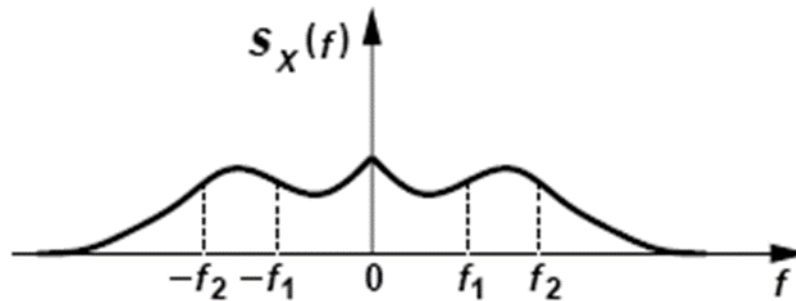


One-Sided

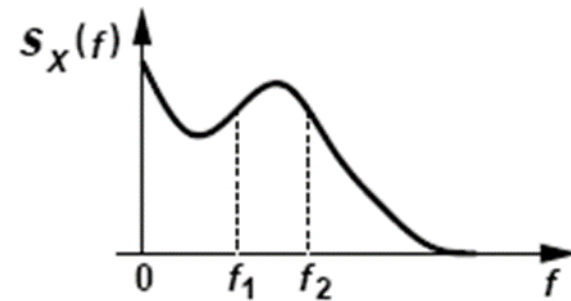

- Scale the single-sided spectrum by $\frac{1}{2}$ to get the double-sided spectrum


Noise and Transfer Function

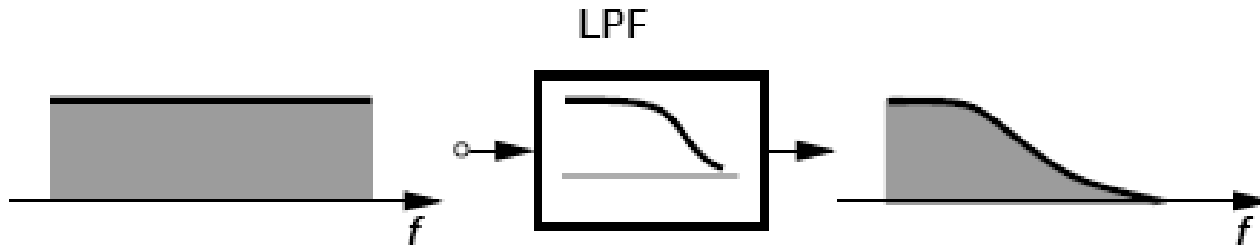

$$S_y(f) = S_x(f)|H(f)|^2$$

- $|H(f)|$ for the LTI system must be squared because $S_x(f)$ is a squared quantity

Thermal Noise of Resistors

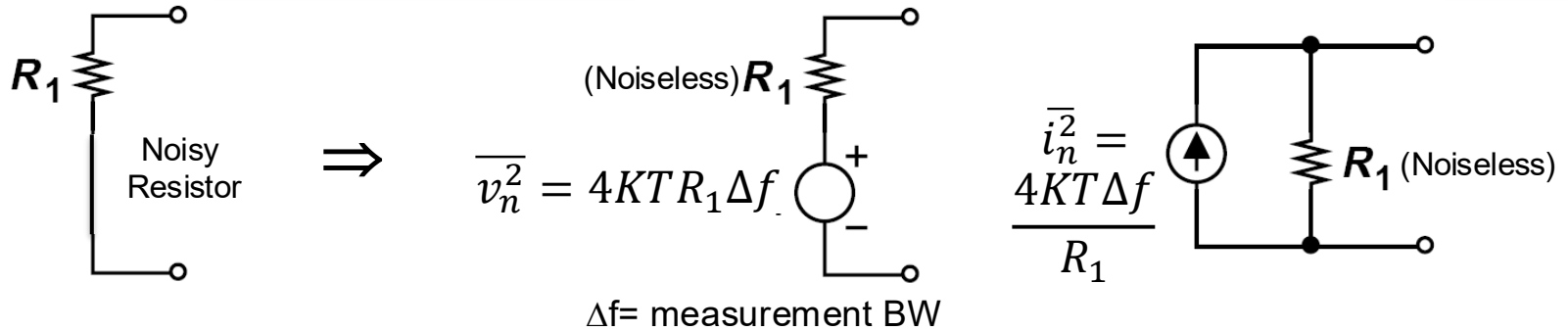

- **Mean-square noise voltage density**

$$\frac{\overline{v_n^2}}{\Delta f} = 4KTR_1 = 4 \frac{KT}{q} qR_1 = 4(25mV)(1.6 \times 10^{-19})R_1 = (1.6 \times 10^{-20})R_1 V^2/Hz \quad @ \text{ Room Temp.}$$

- **RMS noise voltage density**

$$\frac{\overline{v_n}}{\sqrt{\Delta f}} = \sqrt{4KTR_1} = 0.9 nV/\sqrt{Hz} \quad R_1 = 50\Omega$$

- **Mean-square noise current density**

$$\frac{\overline{i_n^2}}{\Delta f} = \frac{\overline{v_n^2}}{R_1^2 \Delta f} = 4 \frac{KT}{R_1} A^2/Hz$$

- **RMS noise current density**

$$\frac{\overline{i_n}}{\sqrt{\Delta f}} = \sqrt{\frac{4KT}{R_1}}$$


- **Source Polarity kept same throughout the calculations**

Spot Noise and White Noise

- Spot noise → Mean-square noise voltage density for 1Hz BW @ frequency of interest

$$\overline{v_n^2}(\Delta f = 1\text{Hz}) = 4KTR_1 = (1.6 \times 10^{-20})R_1V^2$$

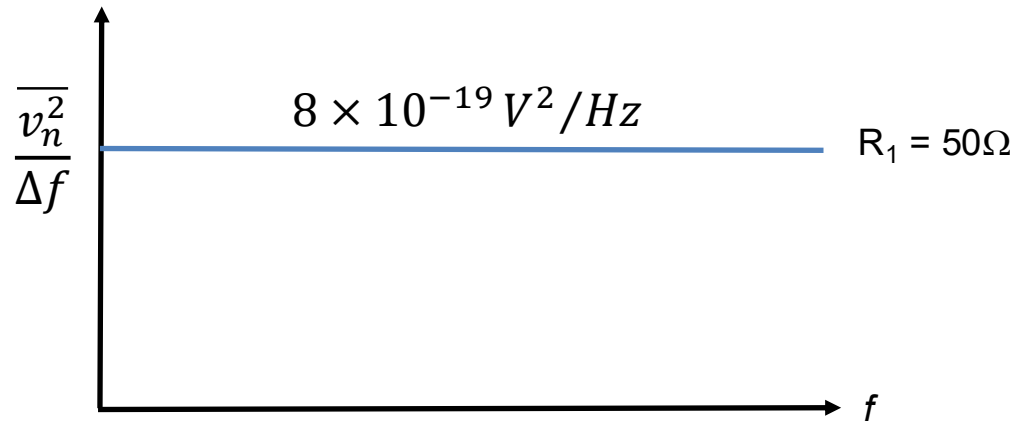- White noise → Mean-square spectral density is constant with frequency → spot noise is independent of frequency




- Falls at $f > 1\text{THz}$ → finite total energy.

Noise Power

- Noise power delivered to the load resistor under conjugate match condition

Suppose R_2 is held at $T = 0$ K

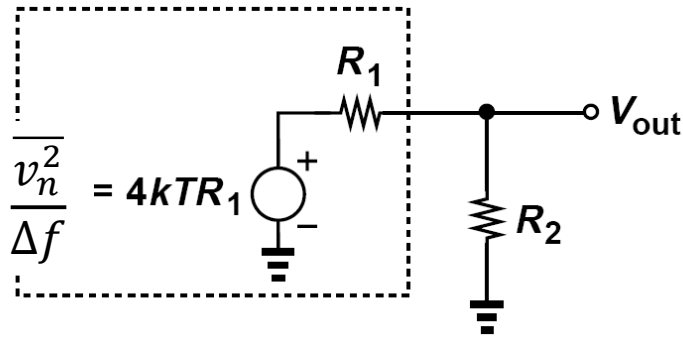

$$P_{R2} = \frac{\overline{V_{out}^2}}{R_2}$$

$$= \overline{V_n^2} \left(\frac{R_2}{R_1 + R_2} \right)^2 \frac{1}{R_2}$$

$$\frac{P_{R2}}{\Delta f} = 4kT \frac{R_1 R_2}{(R_1 + R_2)^2}$$

This quantity reaches a maximum if $R_2 = R_1$:



$$P_{R2,max} = P_{avn} = kTB$$

- Proportional to absolute temperature and BW \rightarrow keep them minimum possible for low-noise

$$P_{avn}/\text{Hz} = 4.143 \times 10^{-21} \text{ W/Hz} = -174 \text{ dBm/Hz}$$

Thermal Noise: MOSFET in Triode

- Operating as a resistor

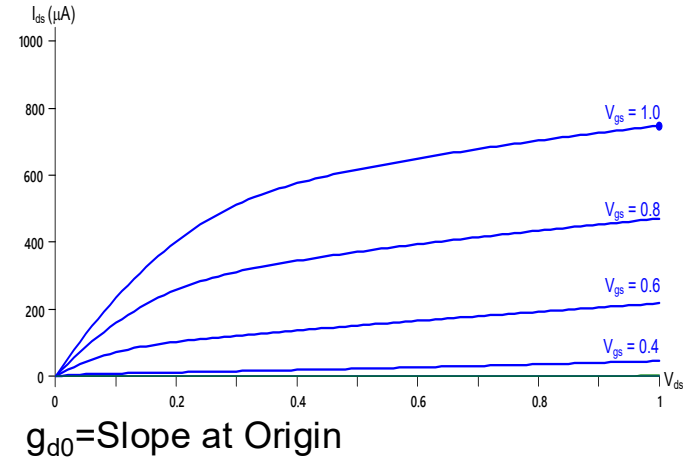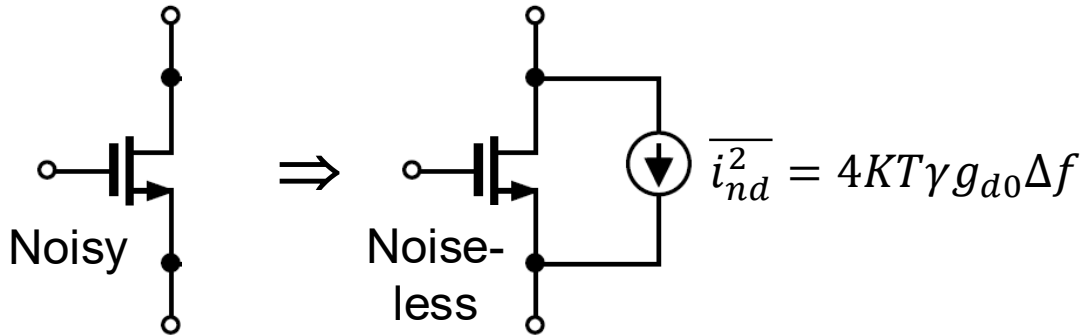


$$I_d = \beta[(V_{gs} - V_T)V_{ds} - V_{ds}^2/2]$$

$$g_d = \frac{\partial I_d}{\partial V_{ds}} = \beta[V_{gs} - V_T - V_{ds}]$$

$$g_{d0}|_{V_{ds}=0} = \beta[V_{gs} - V_T]$$


- $\gamma = \text{Empirical drain current noise parameter} \approx 1$

Thermal Noise: MOSFET in Saturation


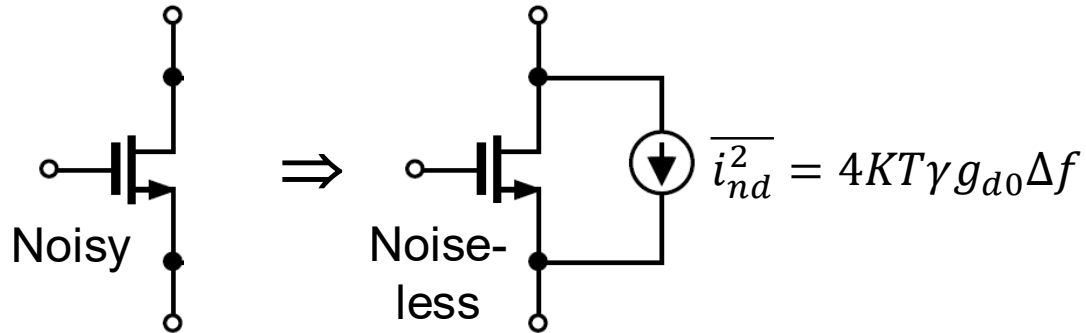


- $\gamma \approx 2/3$ (long channel)
- $\gamma \approx 2-3$ (short channel) [Hot-carrier and substrate effects]
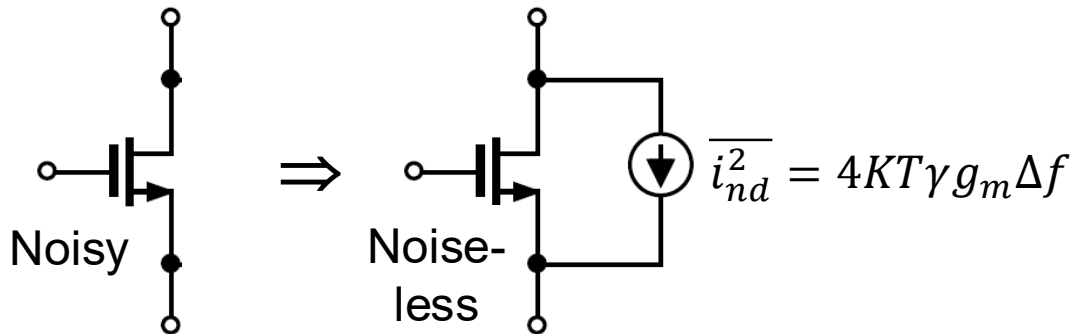
$$g_m = \frac{\partial I_d}{\partial V_{gs}} = \beta[V_{gs} - V_T] = g_{d0}$$



Induced Gate-noise

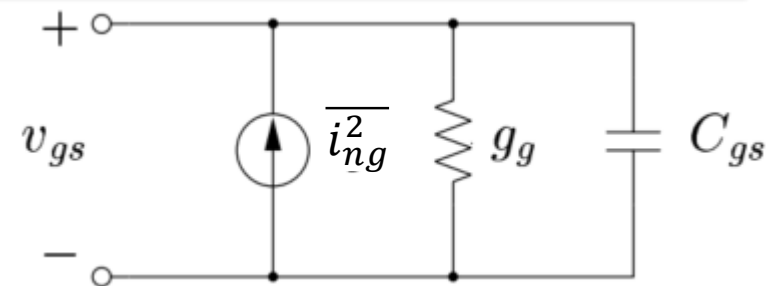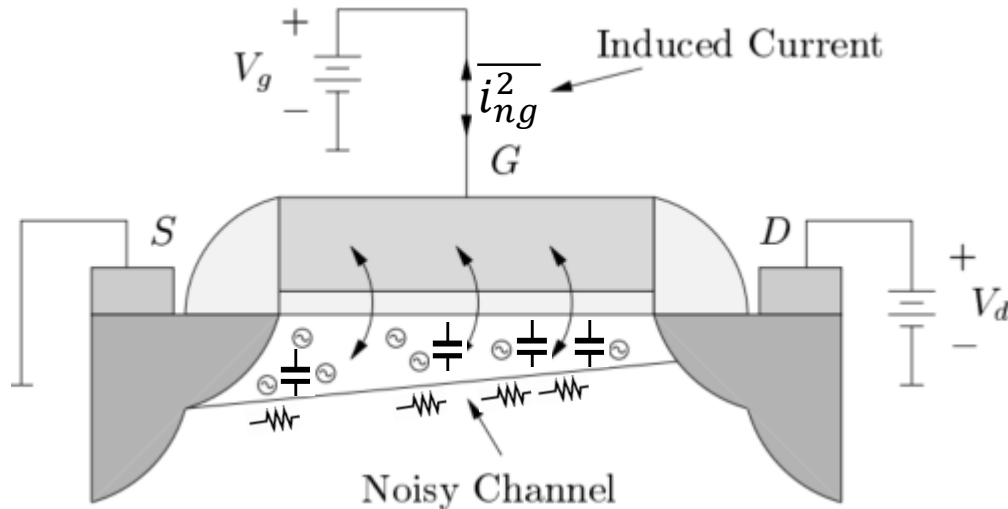

$$\overline{i_{ng}^2} = 4KT\delta g_g \Delta f$$

$$g_g = \frac{\omega^2 C_{gs}^2}{5g_{d0}}$$


$$\delta = 2\gamma$$

[D. Shaeffer]

- Channel charge variations cause local potential variations in the channel. These couple through the gate oxide capacitance to produce gate noise (displacement current).
- Not white
- Important at high frequency

D. Shaeffer & T. Lee, "A 1.5V, 1.5GHz CMOS low noise amplifier," JSSC 1997.

Induced Gate-noise: Transformation

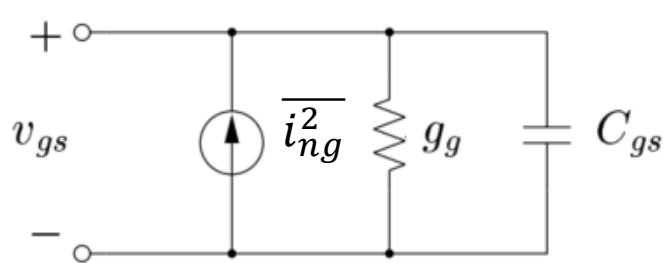


$$\overline{i_{ng}^2} = 4KT\delta g_g \Delta f$$

$$g_g = \frac{\omega^2 C_{gs}^2}{5g_{d0}}$$

$$\delta = 2\gamma$$

[D. Shaeffer]

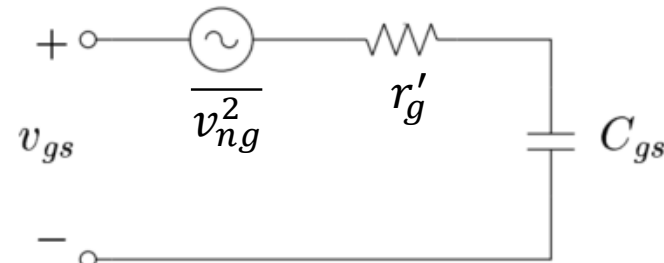

$$\overline{v_{ng}^2} = 4KT\delta r_g' \Delta f$$


$$r_g' = \frac{1}{5g_{d0}}$$

$$\delta = 2\gamma$$

- Transformation results in white noise!
- Narrowband transformation, $Q \gg 1$
- Important at high frequency

D. Shaeffer & T. Lee, "A 1.5V, 1.5GHz CMOS low noise amplifier," JSSC 1997.

Gate-noise

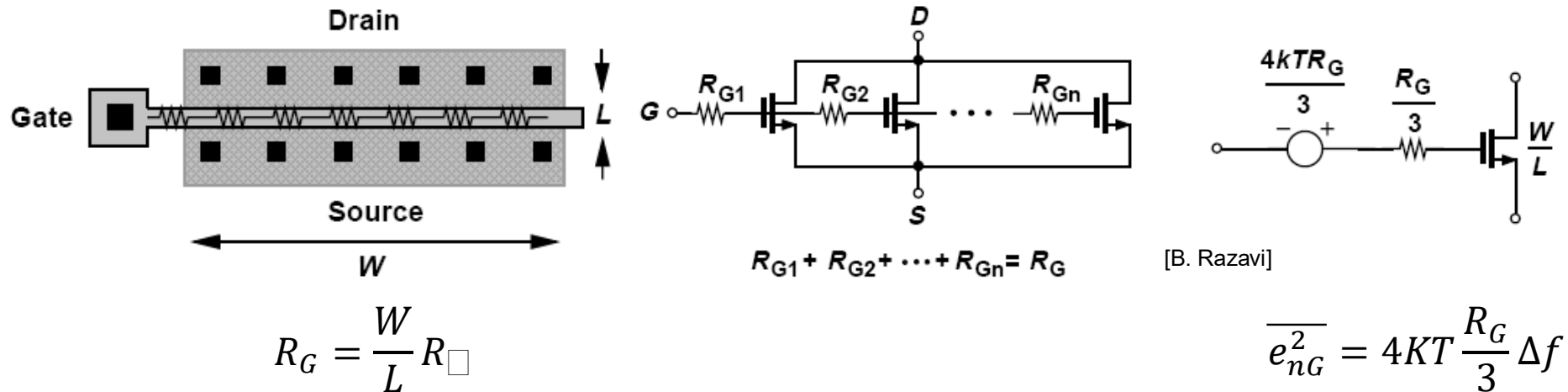

- Noisy resistive gate material (polysilicon) also produces gate noise.
- Important at high frequency, and for short-channel devices.
- Gate and drain terminal exhibit physical resistance too.

B. Razavi, "Impact of distributed gate resistance on the performance of MOS devices," *TCAS-I* 1994.

Correlation between Drain/Gate-Noise

- Drain noise creates gate noise \rightarrow they are partially correlated.
- Correlation coefficient $c = \frac{\overline{i_{ng} i_{nd}^*}}{\sqrt{i_{ng}^2 i_{nd}^2}} \approx 0.395j$
- Notice the reference polarity of the correlated component



D. Shaeffer & T. Lee, "A 1.5V, 1.5GHz CMOS low noise amplifier," JSSC 1997.

Flicker Noise


- Flow of DC current in resistors and transistors result in “1/f” noise
- In MOSFETs, random trapping and release of charge carriers is given as one reason

$$\overline{v_n^2} = \frac{k_{1/f}}{C_{ox}WL} \frac{\Delta f}{f}$$

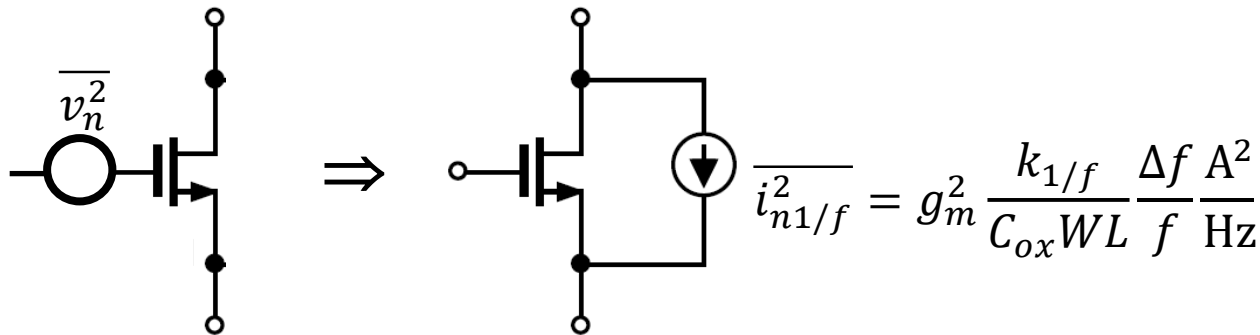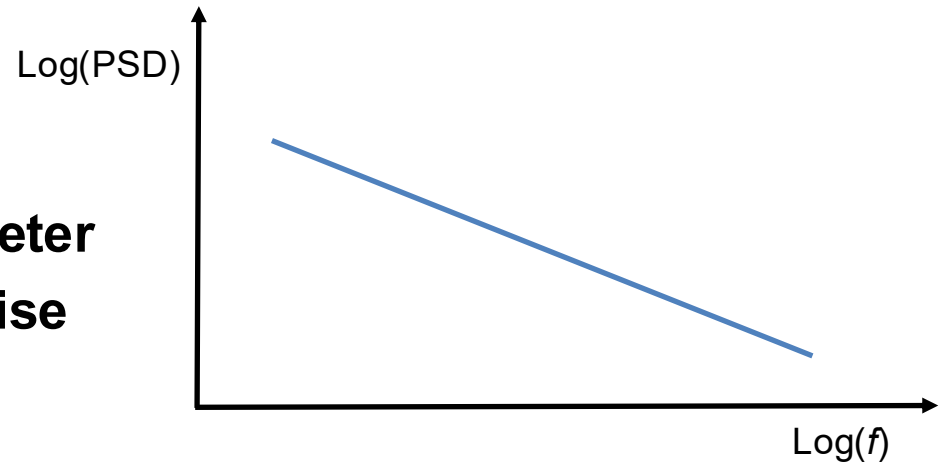- $k_{1/f}$ is process dependent parameter
- Increase area to decrease 1/f noise



Flicker Noise Corner Frequency

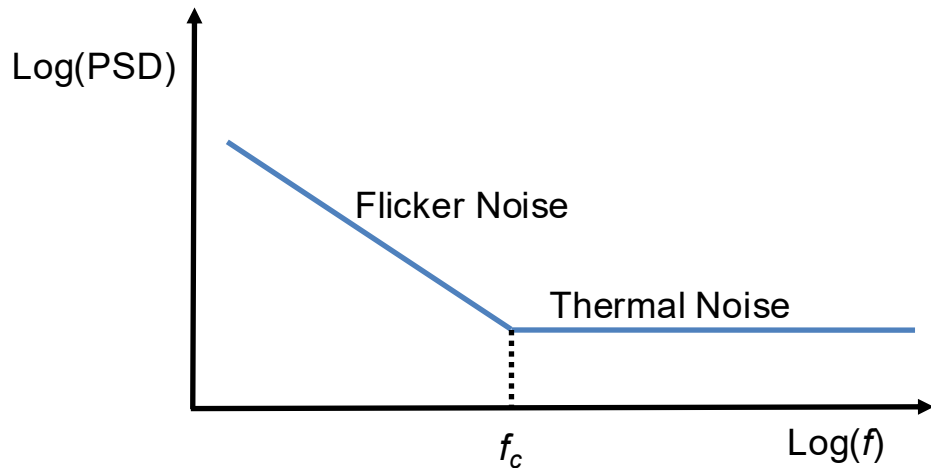

$$4KT\gamma g_m = \frac{k_{1/f} g_m^2}{C_{ox}WL f_c}$$

$$f_c = \frac{k_{1/f} g_m}{4KT\gamma C_{ox}WL}$$

$$f_c \approx \frac{2\pi k_{1/f}}{4KT\gamma} f_T$$

$$f_T \approx \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

- f_T = unity current gain $[i_d/i_{in}]$ frequency
- Faster process \rightarrow Larger corner frequency for same area

Overall MOSFET Noise Model

