

Radio-Frequency IC Design

Lecture 5: Noise Factor

ELEC 404


Acknowledgement: *The Design of CMOS Radio-Frequency Integrated Circuits*. T. Lee



©Sudip Shekhar


Not to be copied, used, or revised without explicit written permission from the copyright owner.

Classical 2-Port Noise Theory

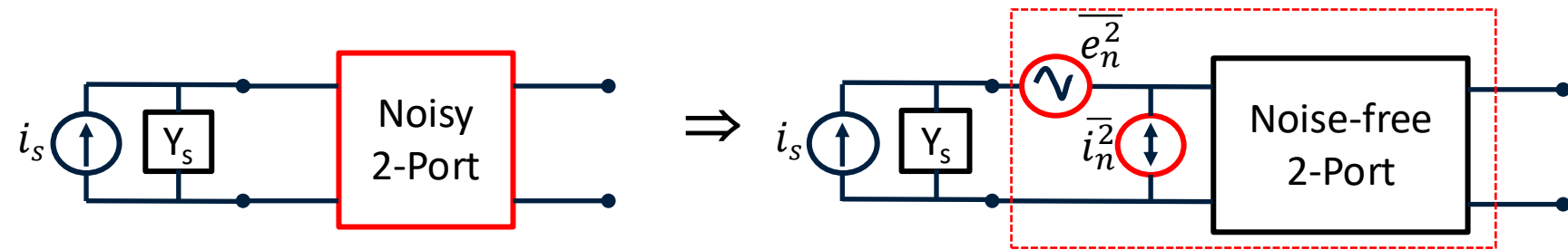

- Why both e_n and i_n ?
-
-
- For any arbitrary Y_s , both contribute
- e_n and i_n may be correlated with each other
- i_s considered independent (uncorrelated) from e_n and i_n .

Noise Factor

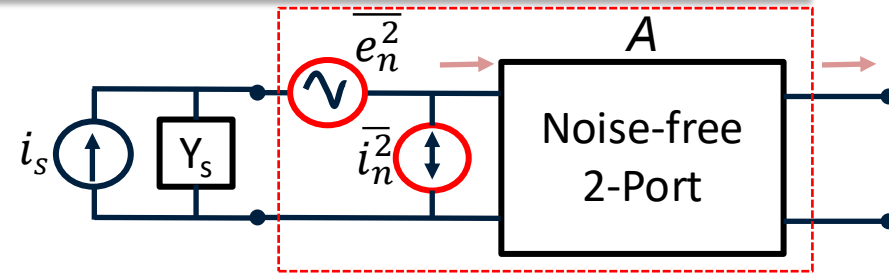

- **Noise current input to the 2-port network**

$$i = [i_s + (i_n + e_n Y_s)] \frac{Y_{in}}{Y_s + Y_{in}}$$

- **Noise Factor:**

$$F = \frac{\text{Total output noise power}}{\text{Output noise power due to source only}} = \frac{\overline{i_{no,total}^2}}{\overline{i_{no,source}^2}} = \frac{\overline{v_{no,total}^2}}{\overline{v_{no,source}^2}}$$

$$F = \frac{\overline{|i_s + (i_n + e_n Y_s)|^2} \left| \frac{Y_{in}}{Y_s + Y_{in}} \right|^2}{\overline{|i_s|^2} \left| \frac{Y_{in}}{Y_s + Y_{in}} \right|^2} = \frac{\overline{i_s^2} + \overline{|i_n + e_n Y_s|^2}}{\overline{i_s^2}} = 1 + \frac{\overline{|i_n + e_n Y_s|^2}}{\overline{i_s^2}}$$


$$F = 1 + \frac{\overline{|i_u + e_n(Y_s + Y_c)|^2}}{\overline{i_s^2}} = 1 + \frac{\overline{i_u^2} + \overline{e_n^2} \overline{|Y_s + Y_c|^2}}{\overline{i_s^2}}$$

$$\overline{|X + Y|^2} = \overline{(X + Y)(X + Y)^*} = \overline{|X|^2} + \overline{|Y|^2} + \overline{XY^*} + \overline{YX^*} = \overline{|X|^2} + \overline{|Y|^2} + 2\text{Re}(\overline{XY^*})$$

Noise Factor – Some Comments

- e_n , i_n , and i_u , Y_c may be difficult to calculate and measure
- Referring voltages and currents to output (or input) port at high frequency easier \rightarrow F or NF is a popular metric.
- Noise Figure, $NF = 10 \log_{10}(F)$ in dB
- F is defined with respect to a source impedance.

Noise Factor as SNR Ratio

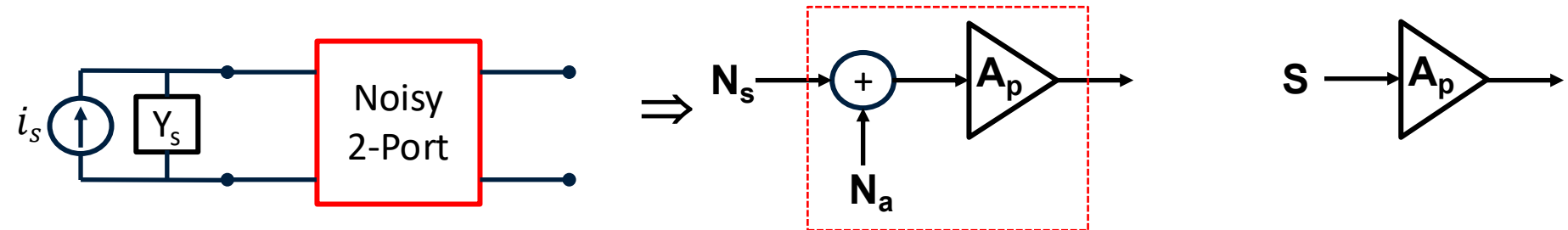


- N_a = Input-referred noise power of the amplifier
- A_p = Available power gain of the amplifier
= Power that the amplifier would deliver to a conjugate-matched load

$$F = \frac{\text{Total noise power}}{\text{noise power due to source only}} = \frac{N_a + N_s}{N_s} = \frac{A_p(N_a + N_s)}{A_p N_s}$$

$$F = \frac{SNR_{in}}{SNR_{out}}$$

Cascaded Network Noise Factor

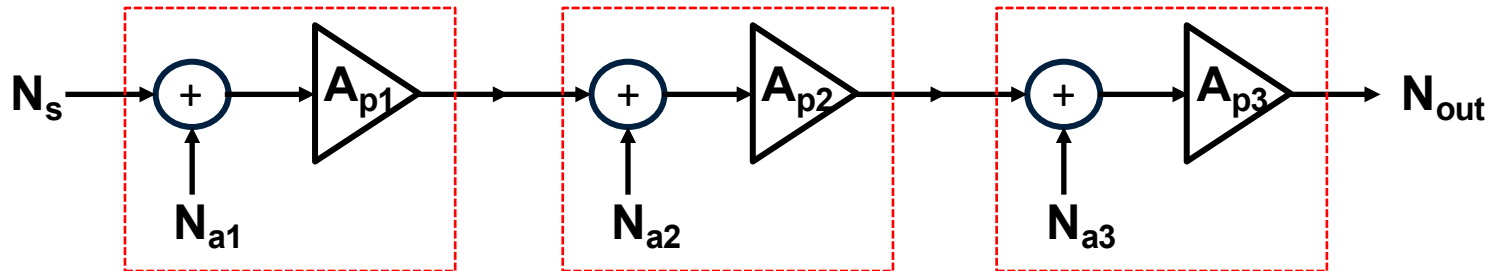

- **Assume all input and output impedances equal**

$$N_{out,total} =$$

$$N_{out,s} =$$

$$F = 1 + \frac{N_{a1}}{N_s} + \frac{N_{a2}}{N_s A_{p1}} + \frac{N_{a3}}{N_s A_{p1} A_{p2}} = 1 + (F_1 - 1) + \frac{F_2 - 1}{A_{p1}} + \frac{F_3 - 1}{A_{p1} A_{p2}}$$

- **First few stages must be low noise**
- **Loss in first few stages *amplifies* noise**