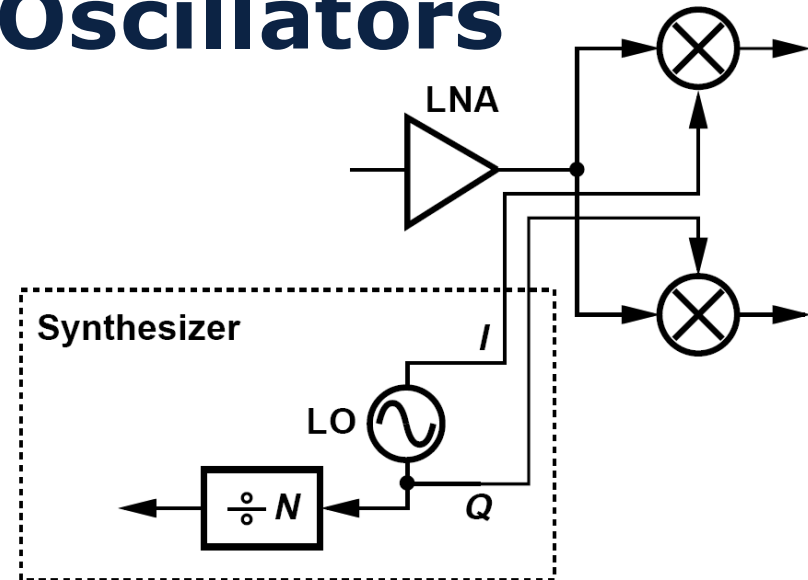


Radio-Frequency IC Design

Lecture 10: Voltage Controlled Oscillators



ELEC 404


Acknowledgement: *RF Microelectronics*. B. Razavi



©Sudip Shekhar

Not to be copied, used, or revised without explicit written permission from the copyright owner.

VCO: Tuning Curve

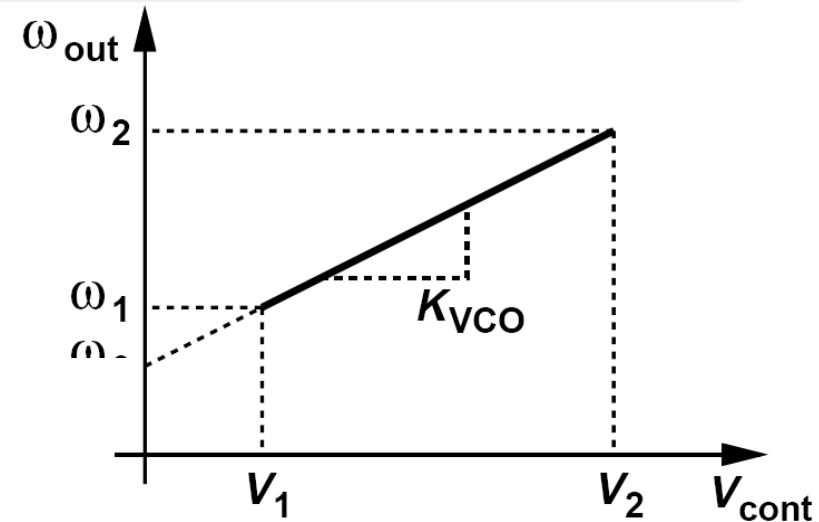


$$\omega_{out} = K_{VCO}V_{cont} + \omega_0$$

- **Center Frequency:** $(\omega_1 \text{ to } \omega_2)/2$
- **VCO Gain/Sensitivity:** $K_{VCO} = \text{Slope}$ expressed in rad/s/V.
- **Tuning Range:** $\omega_2 - \omega_1$
- **Tuning Range Includes:**
 - (1) the system specification;
 - (2) additional margin to cover process & temperature variations and errors due to modeling inaccuracies.

Tuning Range Example

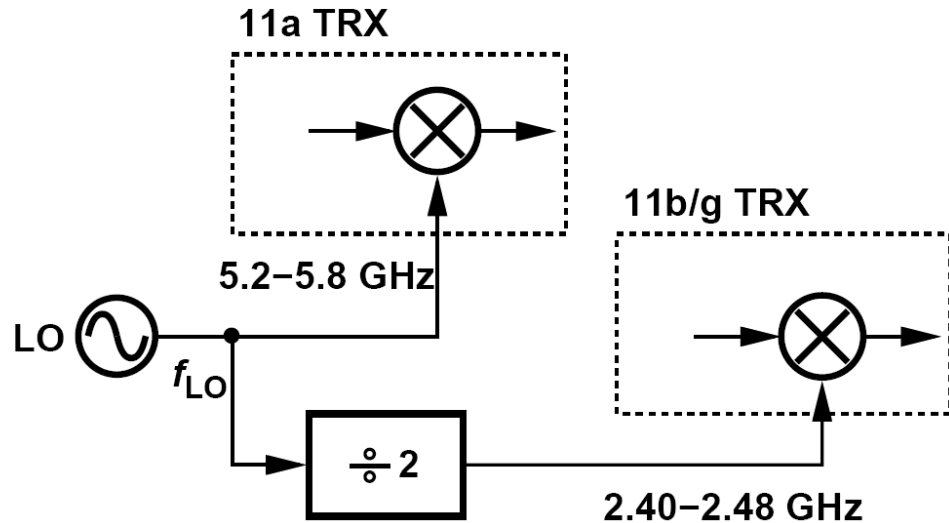A direct-conversion transceiver must cover both the 2.4-GHz and 5-GHz wireless bands with a single LO. What is the minimum acceptable tuning range?




For the lower band, $4.8 \text{ GHz} \leq f_{LO} \leq 4.96 \text{ GHz}$.

Thus, total tuning range of 4.8 GHz to 5.8 GHz $\sim 20\%$ \rightarrow difficult in LC oscillators.




Drive Capability

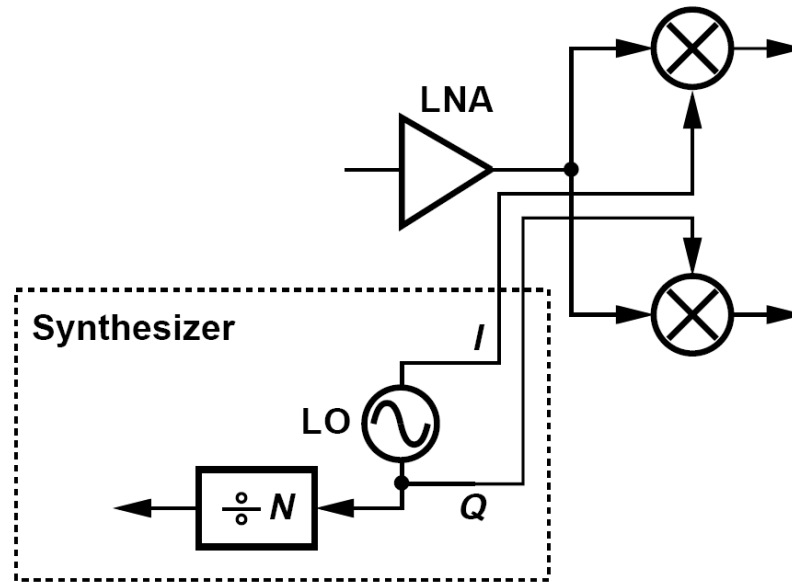- LO has output swing and drive capability tradeoff, for mixers and dividers as load.






Drive Capability

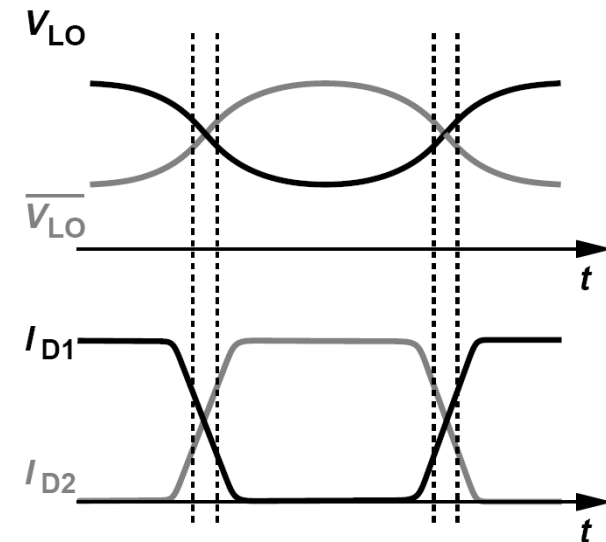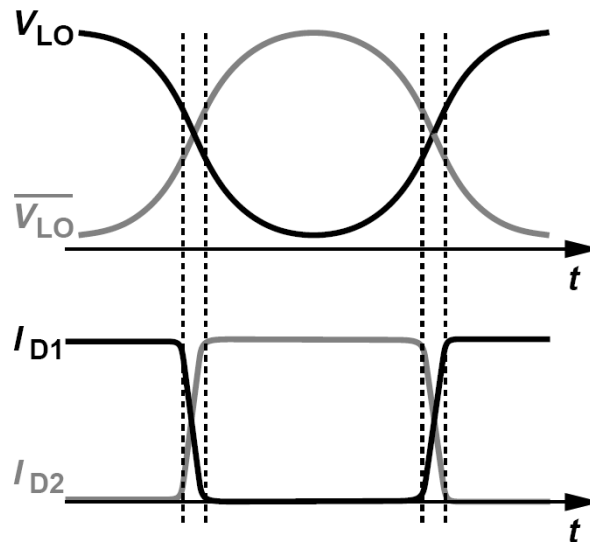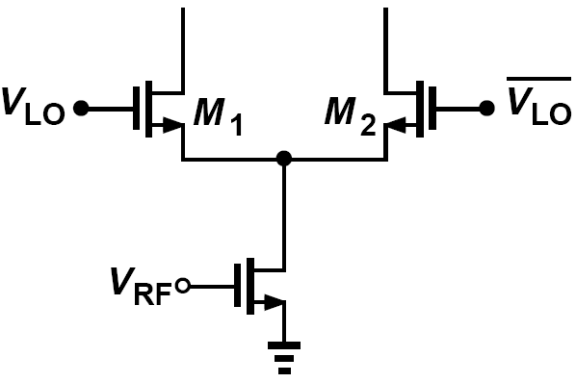- LO has output swing and drive capability tradeoff, for mixers and dividers as load.



- Select large LO swings so that $V_{GS1} - V_{GS2}$ rapidly reaches a large value, turning off one transistor.
- Or, employ smaller LO swings but wider transistors so that they steer their current with a smaller differential input.
- To alleviate the loading presented by mixers and dividers and perhaps amplify the swings, follow the LO with a buffer.



Ideal Output Waveform

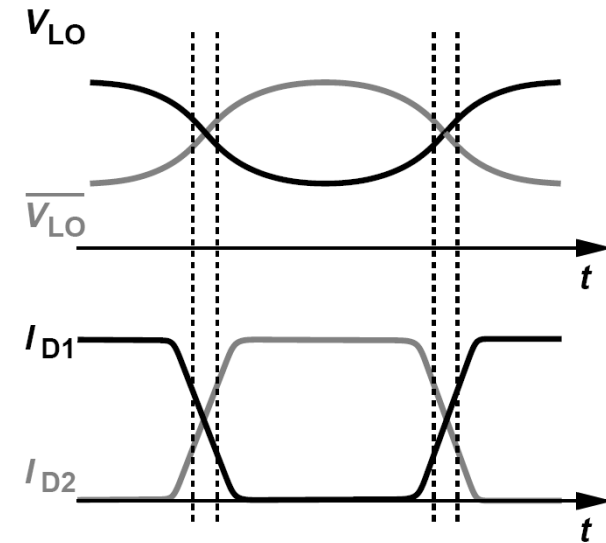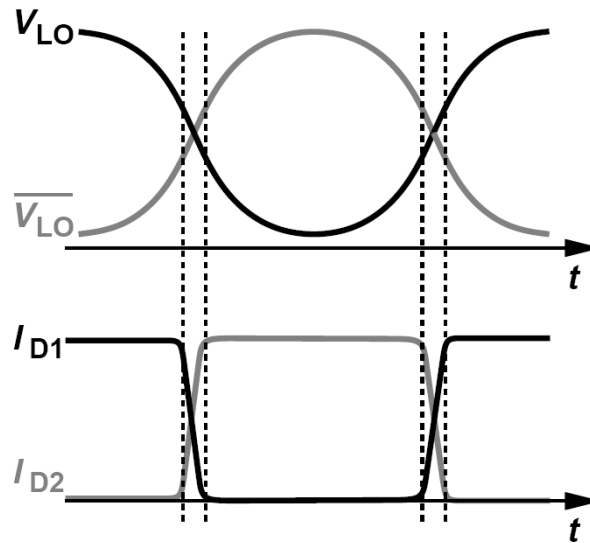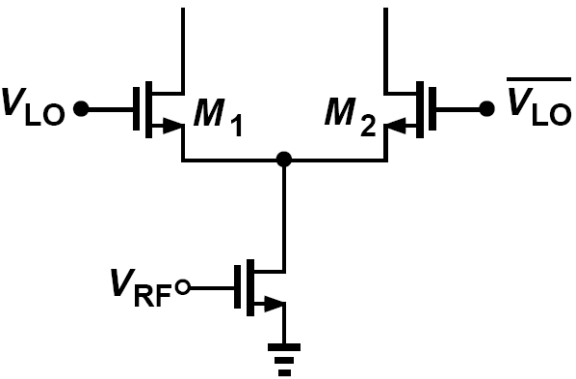

- Sharp, abrupt LO transitions reduce the noise and increase the conversion gain of Mixers.
- Sharp transitions also improve the performance of frequency dividers.
- 50% duty cycle LO to suppress direct feedthrough.
- Ideal LO waveform in most cases is a square wave.


Output Waveform in Practice

- Difficult to generate square LO waveforms in practice.
- Differential LO waveforms for a number of considerations.
- LO spectrum in practice deviates from an impulse and is “broadened” by the noise of its constituent devices, called “phase noise”.
- Phase noise trade-offs with the tuning range and power dissipation
- Very low output swings exacerbate the effect of the internal noise of the oscillator.

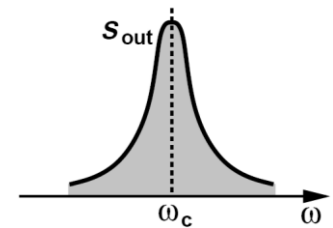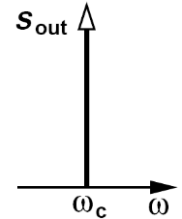

Supply Sensitivity

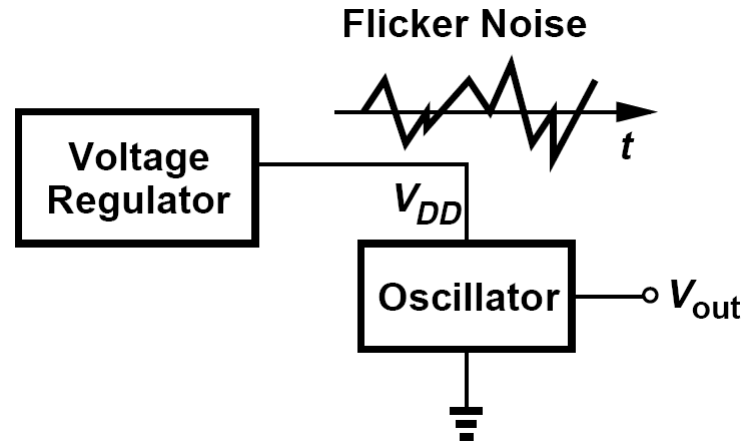
- If LO frequency varies with the supply voltage, it can translate supply noise to frequency (and phase) noise.



Feedback Model of Oscillators

- An oscillator may be viewed as a “badly-designed” negative-feedback amplifier—so badly designed that it has a zero or negative phase margin.
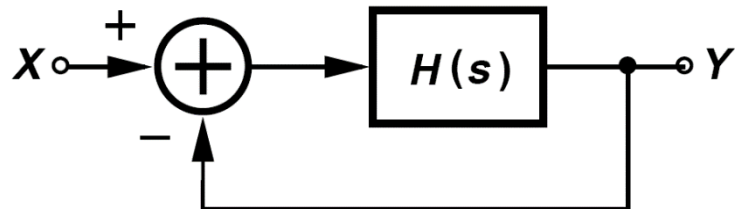
$$\frac{Y}{X}(s) = \frac{H(s)}{1 + H(s)}$$



- When will this system oscillate?
 - Barkhausen Criteria

$$|H(s = j\omega_1)| = 1$$



$$\angle H(s = j\omega_1) = 180^\circ$$

- Total phase shift experienced by signal at $\omega_1 = 360^\circ$.

Barkhausen's Criteria

$$|H(s = j\omega_1)| = 1$$


$$\angle H(s = j\omega_1) = 180^\circ$$

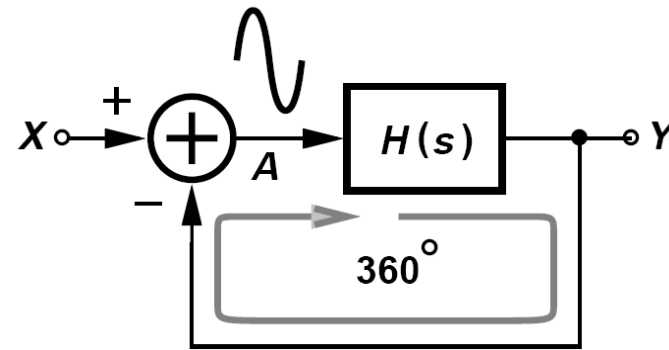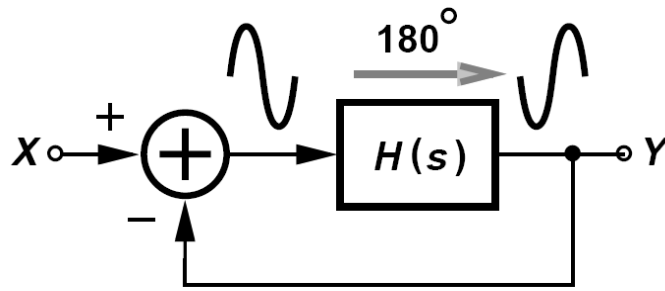

- For the circuit to reach steady state, the signal returning to A must exactly coincide with the signal that started at A.
- 180° phase due to negative feedback
- 180° “frequency-dependent” phase shift due to $\angle H(j\omega_1)$,
→ Changes original negative feedback system to positive feedback at ω_1 !


Significance of $|H(j\omega_1)| = 1$

- For a noise component at ω_1 to “build up” as it circulates around the loop with positive feedback, the loop gain must be at least unity.
- $|H(j\omega_1)| = 1$ is called the “startup” condition.

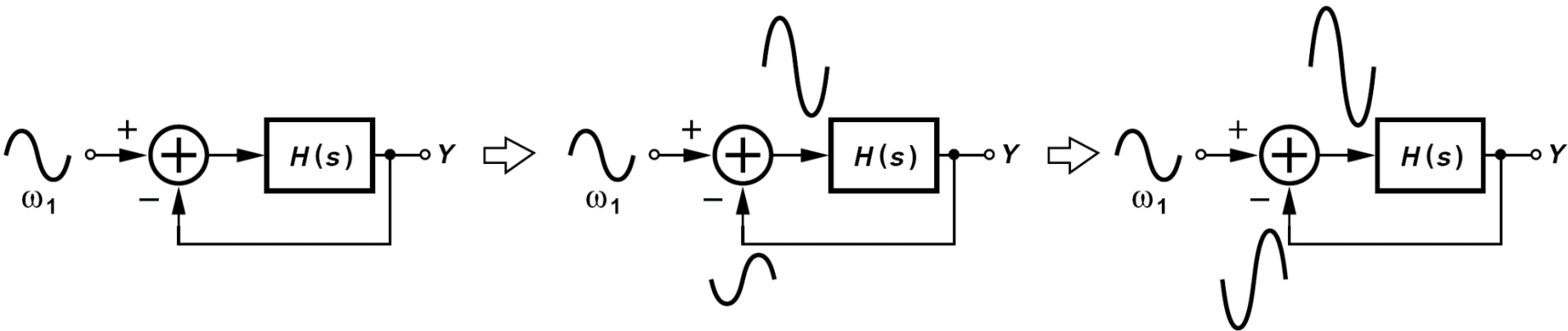


- If $|H(j\omega_1)| > 1$ and $\angle H(j\omega_1) = 180^\circ$, growth occurs at a faster rate because the returning waveform is amplified by the loop.
- Note that the closed-loop poles now lie in the right half plane.

One-Port Model of Oscillators

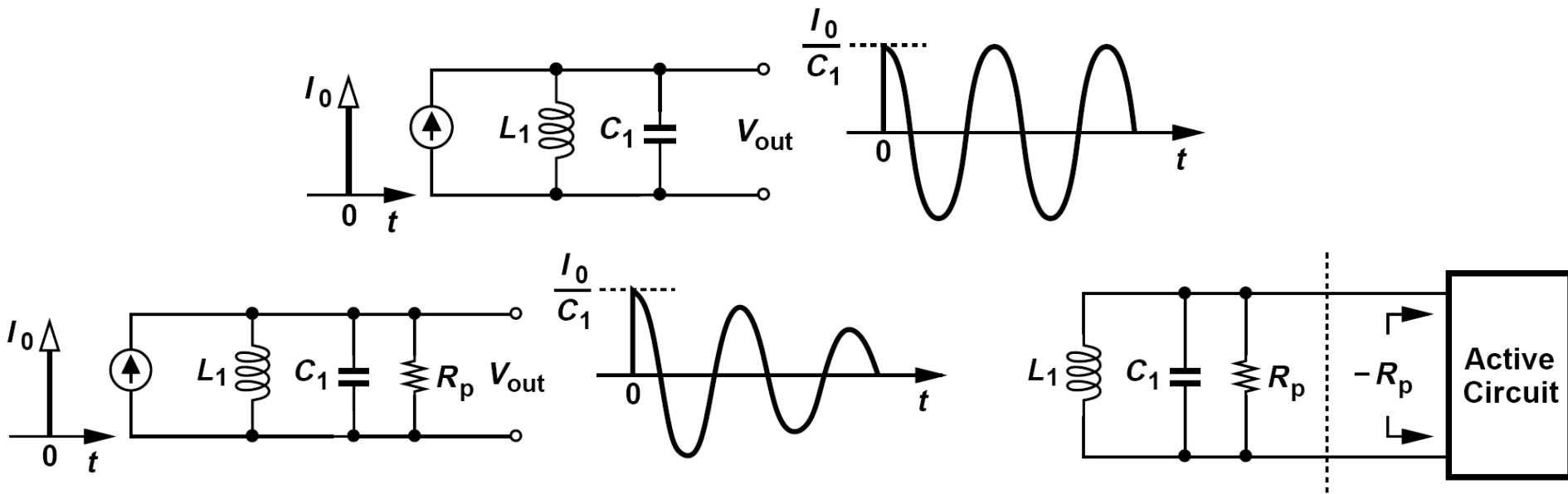

- If an active circuit replenishes the energy lost in each period, then the oscillation can be sustained.


One-Port Model of Oscillators

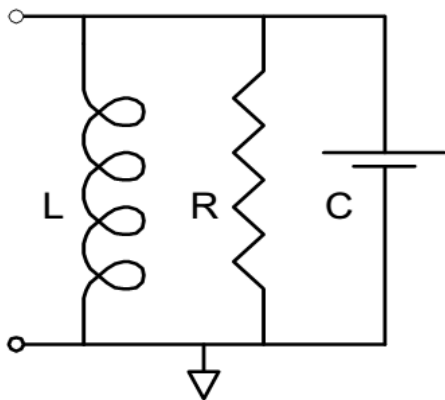


$$Z_{RLC} = \frac{sL}{1 + s^2LC + sGL}$$

$$p_{1,2} = \frac{-GL \pm \sqrt{(GL)^2 - 4LC}}{2LC}$$
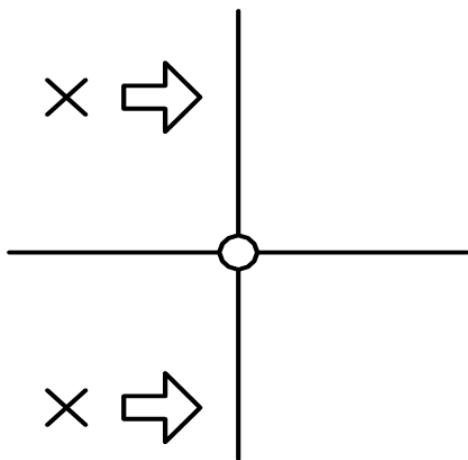
$$p_{G \rightarrow 0} = \pm j \frac{1}{\sqrt{LC}}$$



Generating -ve Resistance

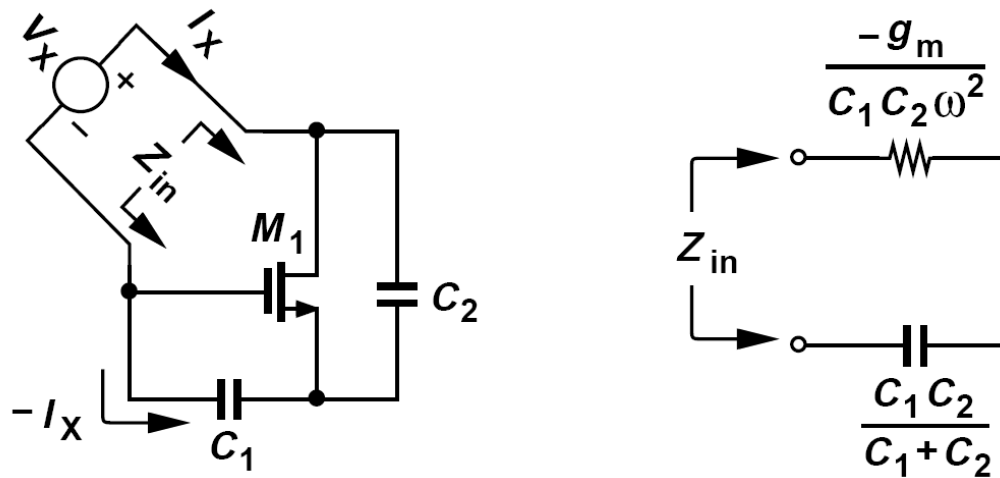

$$-\frac{I_X}{C_1 s} + V_X = \left(I_X + I_X \frac{g_m}{C_1 s} \right) \frac{1}{C_2 s}$$

$$\frac{V_X}{I_X}(s) = \frac{1}{C_1 s} + \frac{1}{C_2 s} + \frac{g_m}{C_1 C_2 s^2}$$


$$\frac{V_X}{I_X}(j\omega) = \frac{1}{jC_1 \omega} + \frac{1}{jC_2 \omega} - \frac{g_m}{C_1 C_2 \omega^2}$$

- The negative resistance varies with frequency.

Connecting Inductor to -ve Res. Ckt

$$R_S = \frac{g_m}{C_1 C_2 \omega^2}$$
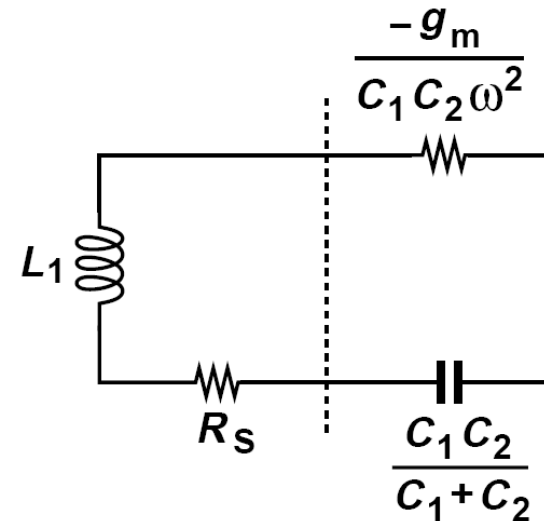
$$\omega_{osc} = \frac{1}{\sqrt{L_1 \frac{C_1 C_2}{C_1 + C_2}}}$$



$$R_p = R_S \left(1 + \left(\frac{\omega L_1}{R_S} \right)^2 \right) \approx \frac{(\omega L_1)^2}{R_S}$$




$$\rightarrow \frac{L_1^2 \omega^2}{R_p} = \frac{g_m}{C_1 C_2 \omega^2}$$

The startup condition:

$$\begin{aligned} g_m R_p &= \frac{(C_1 + C_2)^2}{C_1 C_2} \\ &= \frac{C_1}{C_2} + \frac{C_2}{C_1} + 2 \end{aligned}$$

Three-Point Oscillators

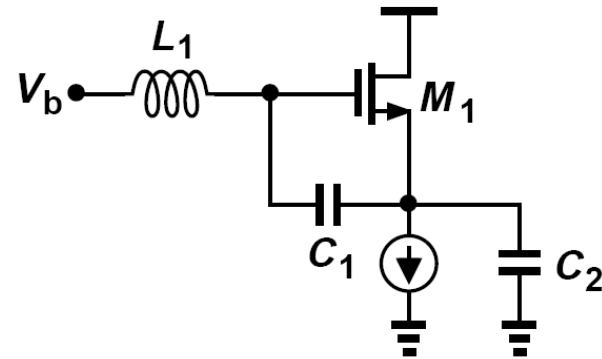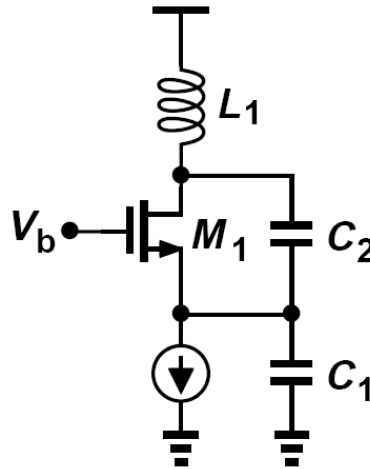
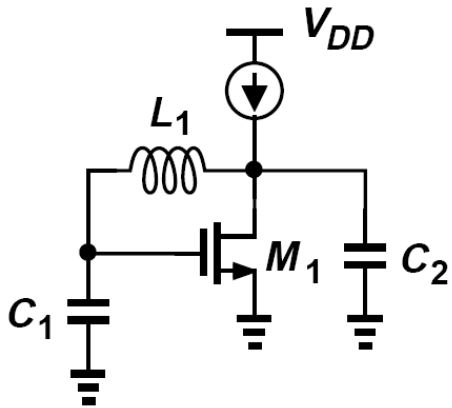
AC ground each terminal \rightarrow 3 different oscillator topologies.



If $C_1 = C_2$, startup condition dictates $g_m R_p \geq 4$

- Higher power consumption compared to cross-coupled LC VCOs.

Tuned Amplifier

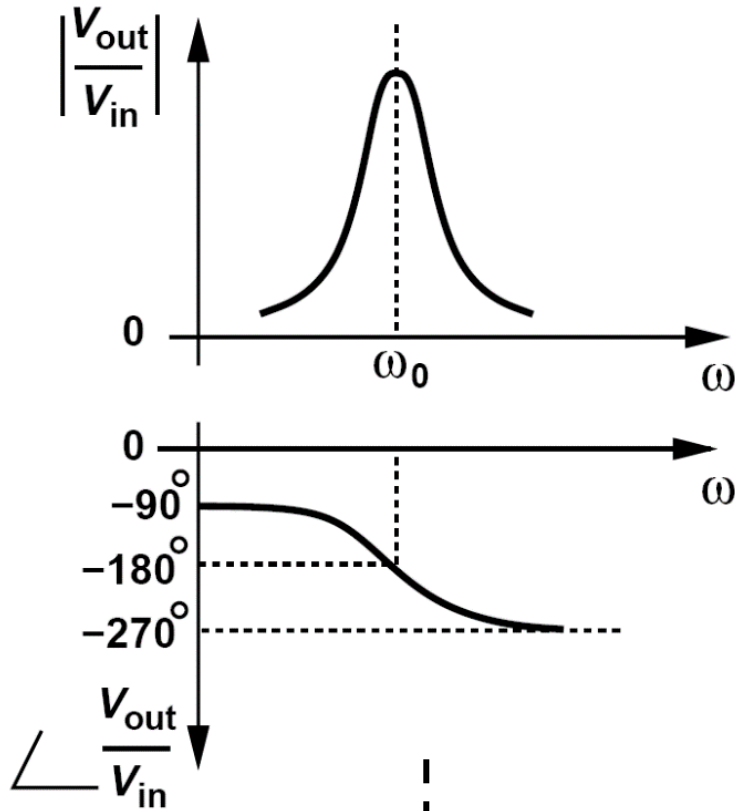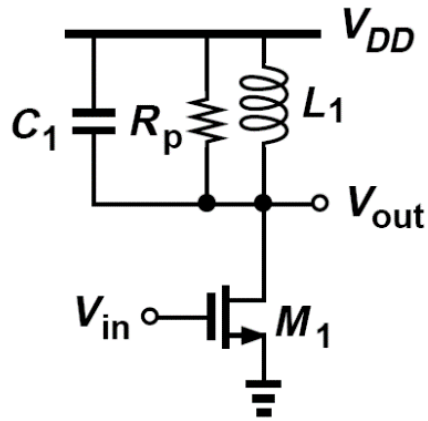

At very low frequencies

$$\frac{V_{out}}{V_{in}} \approx -g_m L_1 s$$

$$\left| \frac{V_{out}}{V_{in}} \right| \rightarrow 0$$

$$\angle \left(\frac{V_{out}}{V_{in}} \right) \rightarrow -90^\circ$$

At ω_0

$$\frac{V_{out}}{V_{in}} = -g_m R_p$$

$$\angle \left(\frac{V_{out}}{V_{in}} \right) = 180^\circ$$

At very high frequencies



$$\frac{V_{out}}{V_{in}} \approx -g_m \frac{1}{C_1 s}$$

$$\left| \frac{V_{out}}{V_{in}} \right| \rightarrow 0$$

$$\angle \left(\frac{V_{out}}{V_{in}} \right) \rightarrow +90^\circ$$

Cascaded Tuned Amp with Feedback

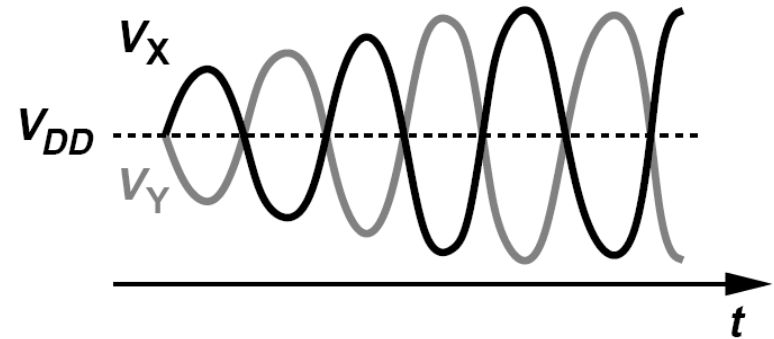
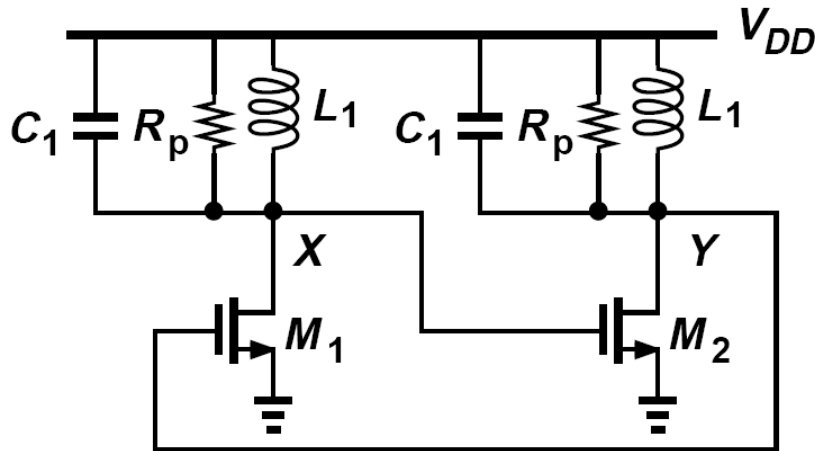
Cascade two phase shifts of 180° to get 360° around the loop.



$$(g_m R_p)^2 \geq 1$$

- Inductive loads \rightarrow peak voltages above the supply.
- The growth of V_X and V_Y ceases when M_1 and M_2 enter the triode region for part of the period, reducing the loop gain.

Cross-Coupled Oscillator

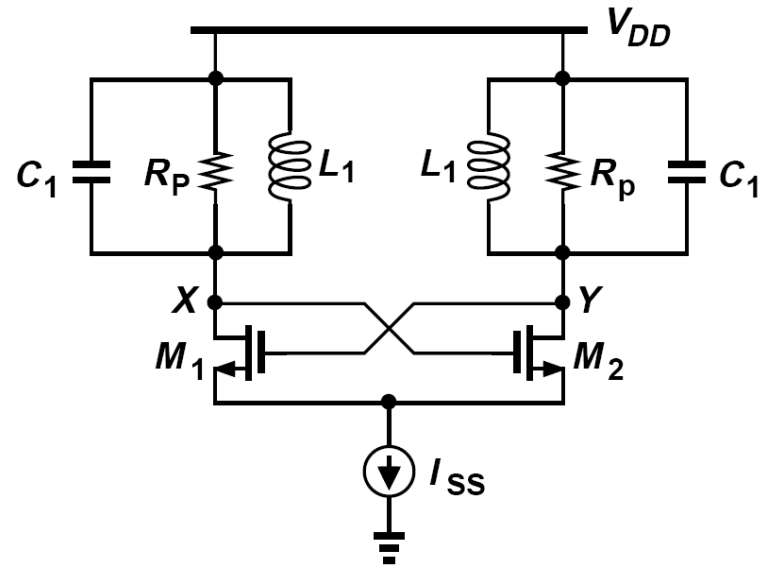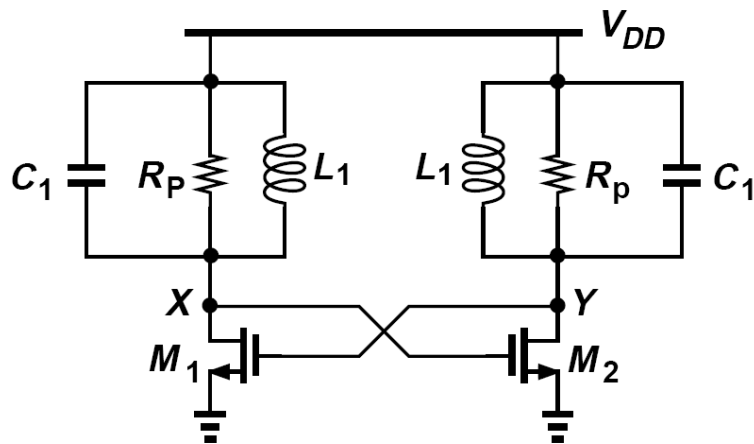


$$\omega_{osc} = \frac{1}{\sqrt{L_1(C_{GS2} + C_{DB1} + 4C_{GD} + C_1)}}$$

Tail current source defines a bias current \rightarrow more robust and can be viewed as an inductively-loaded differential pair with positive feedback. If M_1 and M_2 experience complete current switching with abrupt edges, peak differential o/p swing

$$V_{XY} \approx \frac{4}{\pi} I_{SS} R_p$$

CC Oscillator: One-Port View

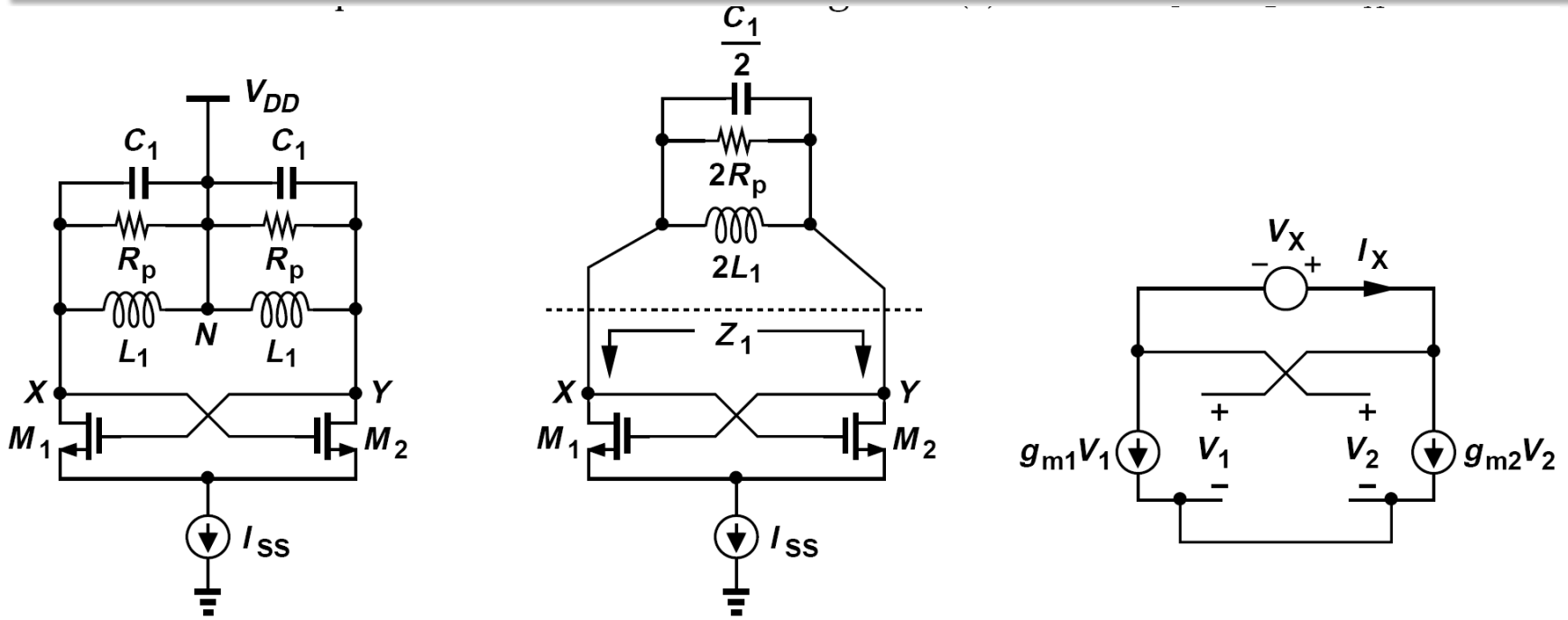



$$I_X = -g_{m1}V_1 = g_{m2}V_2 \quad \Rightarrow \quad \frac{V_X}{I_X} = - \left(\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \right)$$

For $g_{m1} = g_{m2} = g_m$ $\frac{V_X}{I_X} = -\frac{2}{g_m}$

Startup condition: $\frac{2}{g_m} \leq 2R_p \Rightarrow g_m R_p \geq 1$

CC-VCO Using MOS Varactors

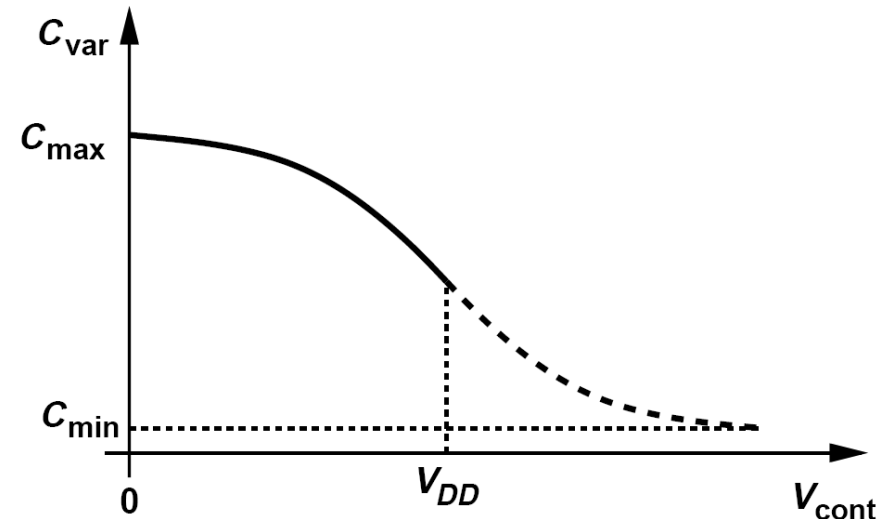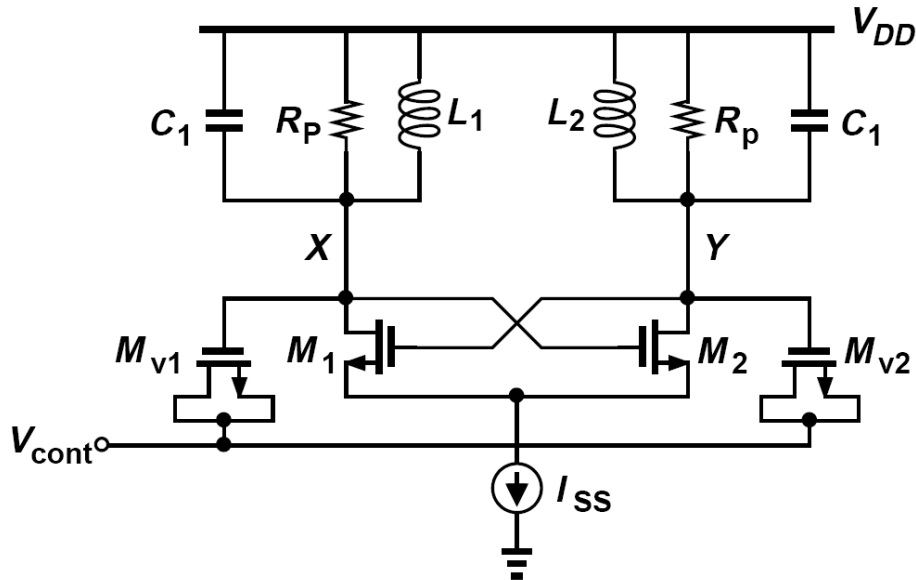- Changing cap easier than inductor for VCO
- MOS varactors are more commonly used than *pn* junctions, especially in low-voltage design.




$$\omega_{osc} = \frac{1}{\sqrt{L_1(C_1 + C_{var})}}$$

- Varactors are stressed for part of the period if V_{cont} is near ground and V_X (or V_Y) rises significantly above V_{DD} .
- Only about half of $C_{max} - C_{min}$ is utilized in the tuning.


Tuning Range Limitations

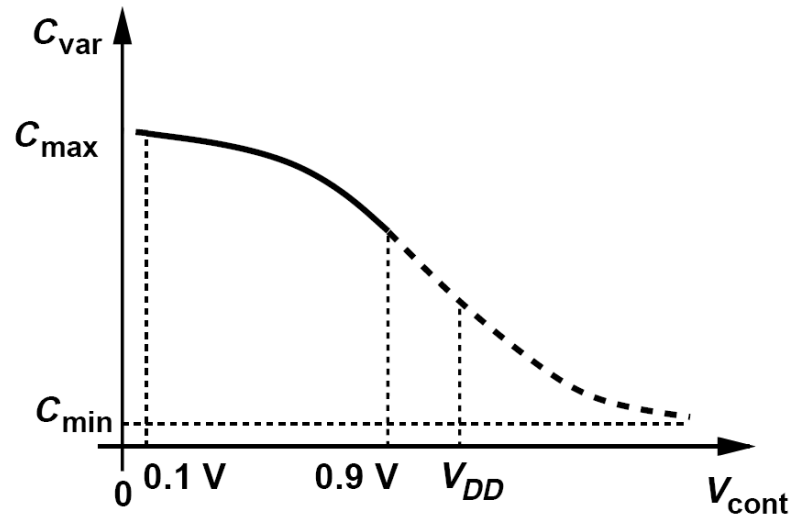- The tuning range trades with the overall tank Q .
- Another limitation on $C_{var2} - C_{var1}$ arises from the available range for the control voltage of the oscillator, V_{cont} .



Effect of Varactor's Finite Q:
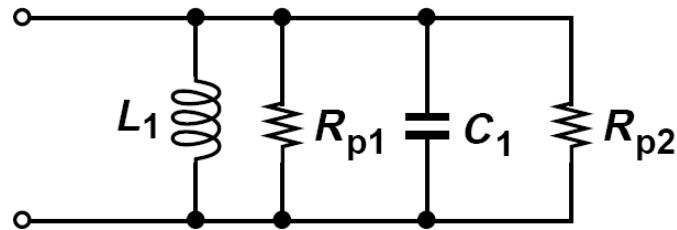
$$Q_L = \frac{R_{p1}}{L_1\omega}$$
$$Q_C = R_{p2}C_1\omega$$



Merging R_{p1} and R_{p2} yields the overall Q:


$$Q_{tot} = \frac{R_{p1}R_{p2}}{R_{p1} + R_{p2}} \cdot \frac{1}{L_1\omega}$$
$$= \frac{1}{\frac{L_1\omega}{R_{p1}} + \frac{L_1\omega}{R_{p2}}}$$
$$= \frac{1}{\frac{L_1\omega}{R_{p1}} + \frac{1}{R_{p2}C_1\omega}}$$

➔

$$\frac{1}{Q_{tot}} = \frac{1}{Q_L} + \frac{1}{Q_C}$$

LC VCOs with Wide Tuning Range

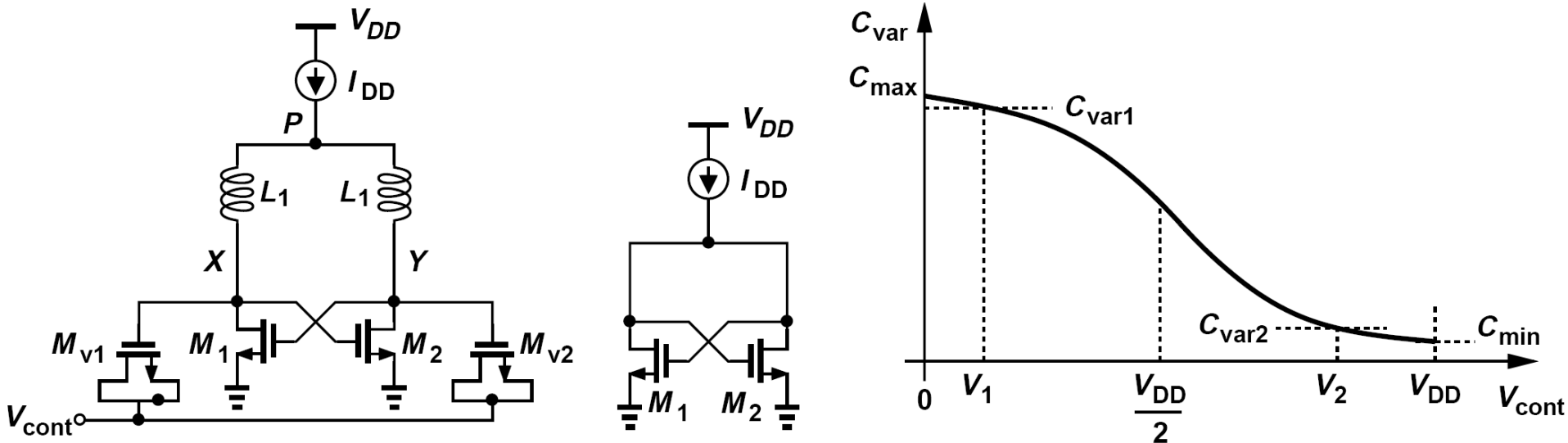- Allowing both positive and negative (average) voltages across the varactors \rightarrow utilizing almost the entire range from C_{min} to C_{max} .




$CM = V_{GS}$ of a diode-connected transistor carrying a current of $I_{DD}/2$.

$$V_{GS1,2} = \sqrt{\frac{I_{DD}}{\mu_n C_{ox} (W/L)}} + V_{TH}$$

Select W/L for $CM = V_{DD}/2$.


\rightarrow As V_{cont} varies from 0 to V_{DD} , $V_{GS,var}$ goes from $+V_{DD}/2$ to $-V_{DD}/2$

Complimentary Cross-Coupled VCO

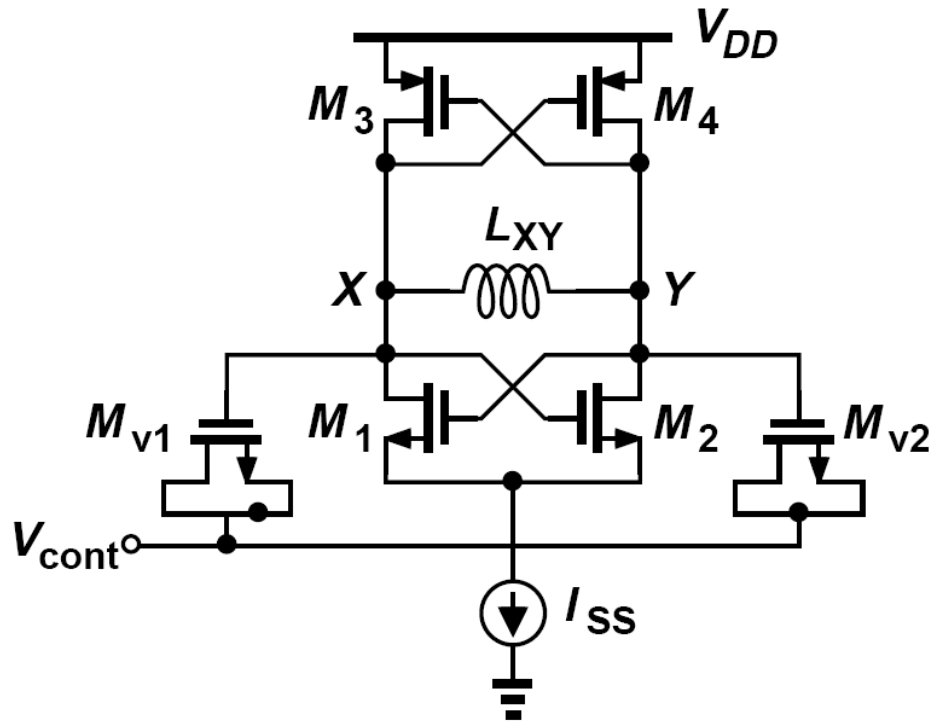



- A cross-coupled NMOS pair and a cross-coupled PMOS pair sharing the same bias current.
- Choose W/L and I_{SS} for $CM = V_{DD}/2$ at X and $Y \rightarrow$ maximizing the tuning range.

CCC-VCO: Voltage Swing

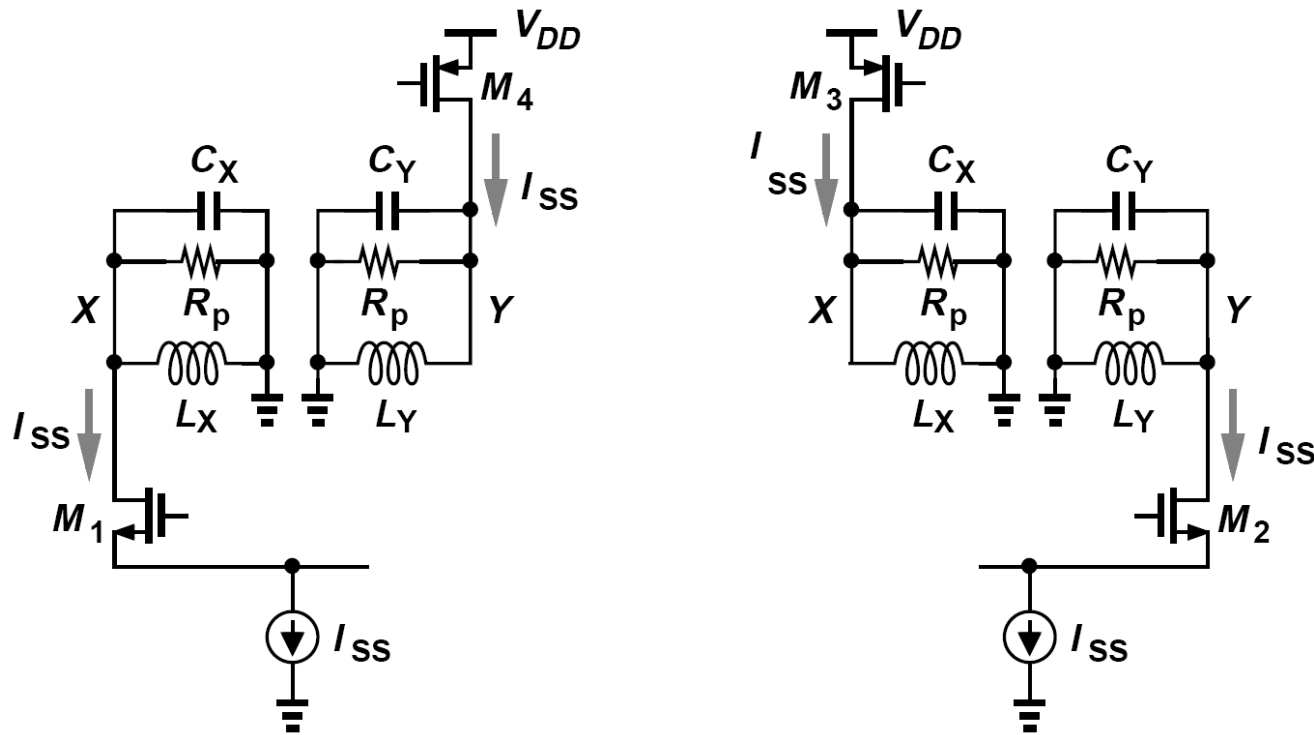

- The current in each tank swings between $+I_{SS}$ and $-I_{SS}$ whereas in previous topologies it swings between I_{SS} and zero.
- The output voltage swing is therefore doubled.

CCC-VCO: Headroom, Tuning Range

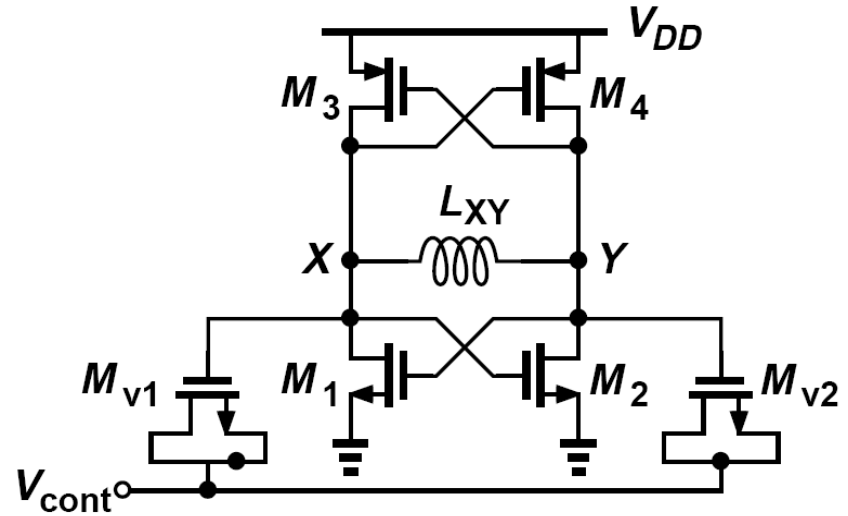
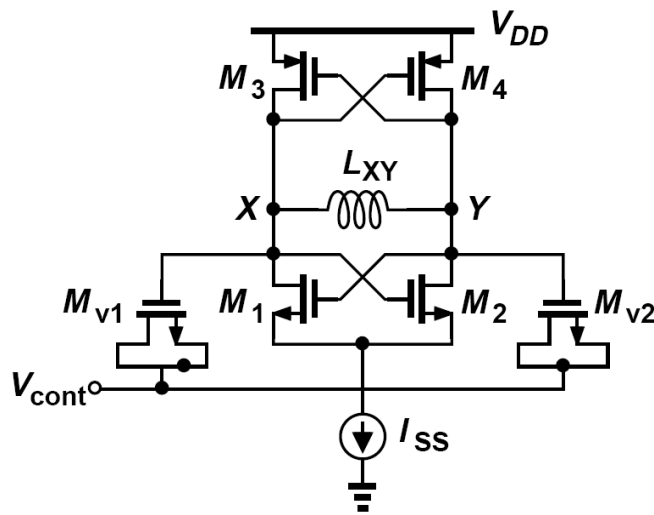


- $|V_{GS3}| + V_{GS1} + V_{ISS} = V_{DD} \rightarrow$ Wide PMOS, degrading the tuning range.
- Noise of the bias current source modulates the output CM level and hence the capacitance of the varactors, producing frequency and phase noise.
- Remove the tail current source?
 - Supply noise sensitivity increases
 - Bias current varies with PT.

Eg.: A volt. regulator providing V_{DD} may exhibit significant flicker noise, thus modulating the frequency (by modulating the CM level).

Discrete Tuning

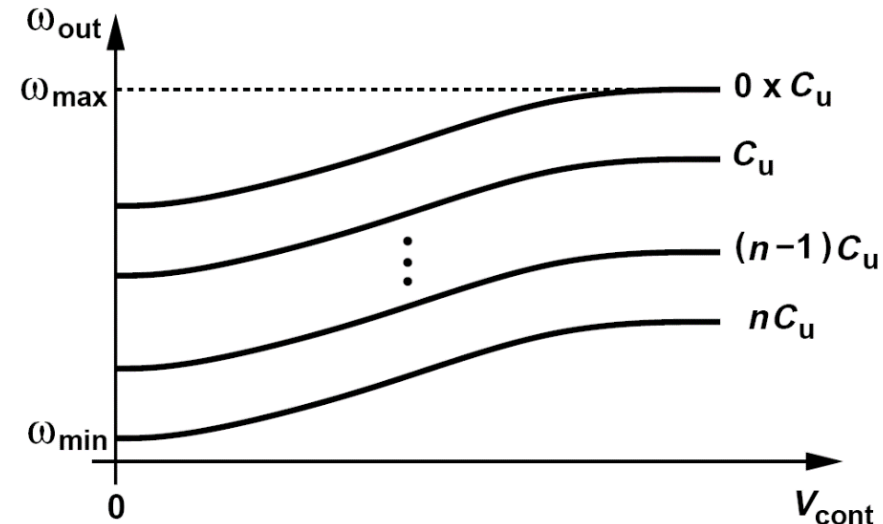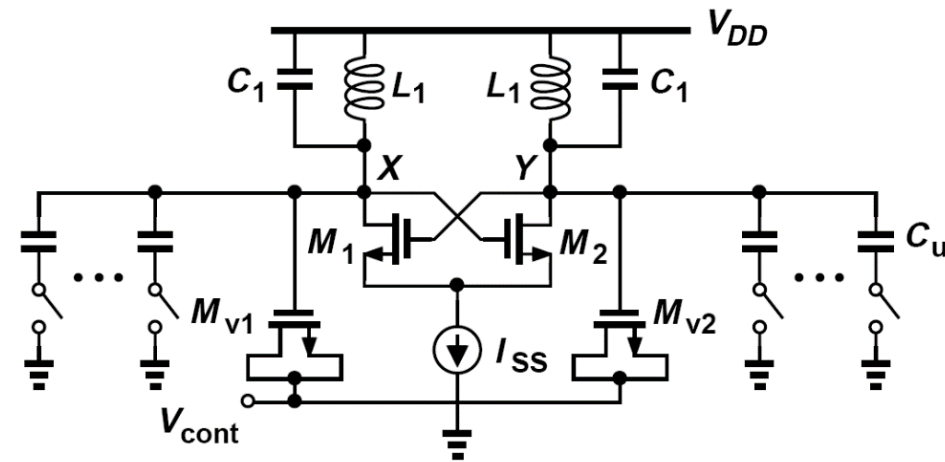- Add “discrete tuning” to achieve a capacitance range well beyond C_{max}/C_{min} of varactors.



Lowest frequency : all unit capacitors switched in and max varactor value,


$$\omega_{min} = \frac{1}{\sqrt{L_1(C_1 + C_{max} + nC_u)}}$$

Highest frequency : all unit capacitors switched out and min varactor value,

$$\omega_{max} = \frac{1}{\sqrt{L_1(C_1 + C_{min})}}$$


Discrete Tuning: R_{on} degrades Q

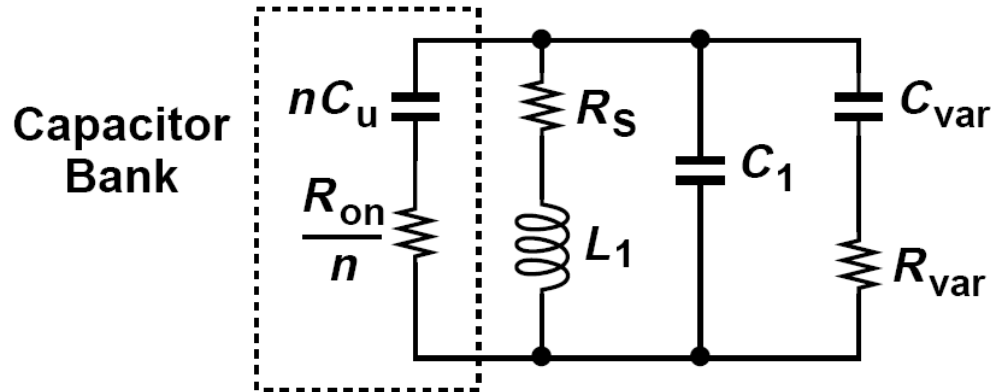- R_{on} of the switches that control the unit caps degrades the tank-Q.



- Increase the width of the switch transistors to minimize R_{on} ?



Discrete Tuning: Switch Parasitic Cap

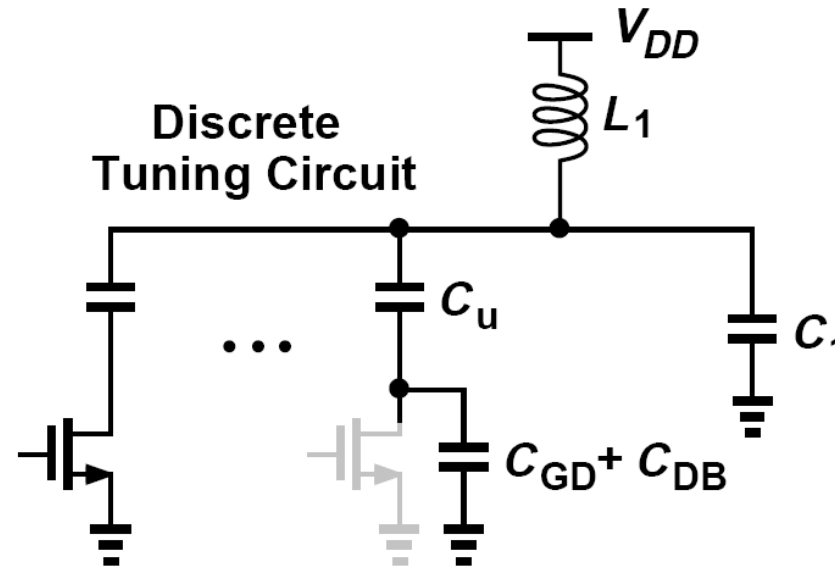

- Wider switches \rightarrow larger bottom plate cap for the unit capacitors to ground \rightarrow substantial cap to the tank when the switches are off.
- $R_{on} \times C_{off}$ is usually constant for a given technology.
- Trade-off between the Q and FTR

F. Cararra et al., "A 2.4-GHz 24-dBm SOI CMOS Power Amplifier With Fully Integrated Reconfigurable Output Matching Network," *Tran. MTT*, Sep. 2009.



Discrete Tuning: Blind Zone

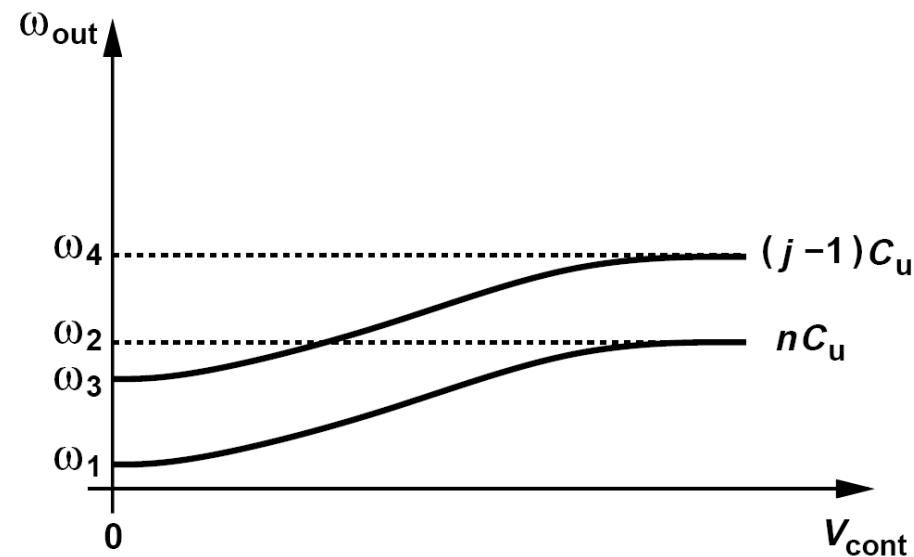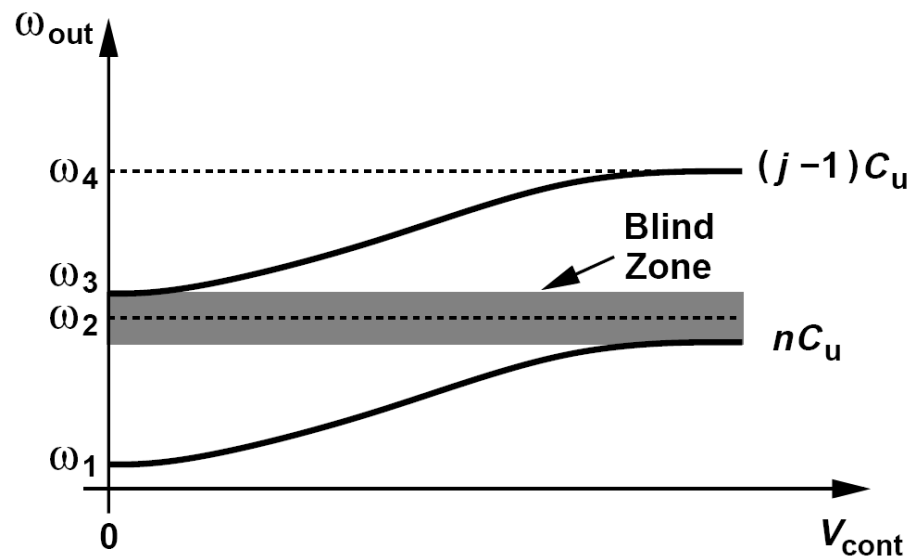

The oscillator fails to cover the range between ω_2 and ω_3 for any combination of fine and coarse controls.

- To avoid blind zones, each two consecutive tuning characteristics must have some overlap.
- \rightarrow Smaller C_u and larger $n \rightarrow$ complex layout.

VCO Design Procedure – I

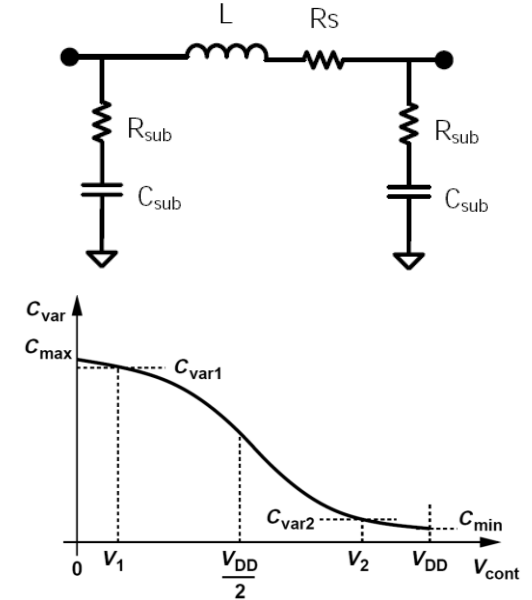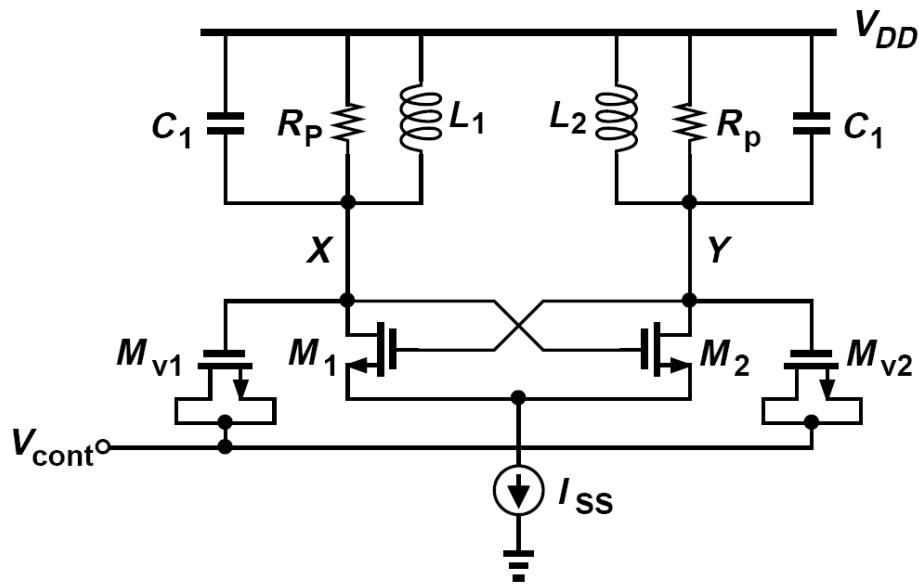

What are the given constraints? What is desired? Which topology to choose?
 For a given center frequency ω_0 , load capacitance C_L , and

- FTR, phase noise, minimize power consumption
- FTR, power budget, minimize phase noise
- power budget, phase noise, maximize FTR

VCO Design Procedure – II

- Find the inductor with max Q at ω_0 . [Select the smallest L that yields a parallel resistance of R_p at ω_0]
- With Q and R_p known, find I_{SS} from the phase noise specification. Or, based on the power budget and hence the maximum allowable I_{SS} , select the R_p so as to obtain the required differential voltage peak swing, $(4/\pi)I_{SS}R_p$.

$$S(\Delta\omega) = \frac{\pi^2 kT}{R_p I_{SS}^2} \left(\frac{3}{8}\gamma + 1 \right) \frac{\omega_0^2}{4Q^2\Delta\omega^2}$$

- Assuming a startup factor of 2, calculate the g_m of the cc-transistors.
- From g_m and I_{SS} , determine the dimensions of cc-transistors. Ensure that they experience nearly complete switching with the given voltage swings.
- Calculate $C_{var,max}$, that can be added to reach the lower end of the FTR, ω_{min}

$$\frac{1}{\sqrt{L_0(C_{GS} + 4C_{GD} + C_{DB} + C_p + C_L + C_{var,max})}}$$

- Using proper varactor models, determine $C_{var,min}$, and compute the upper end of the FTR, ω_{max}

$$\frac{1}{\sqrt{L_0(C_{GS} + 4C_{GD} + C_{DB} + C_p + C_L + C_{var,min})}}$$

- If ω_{max} is quite higher than necessary, increase $C_{var,max}$ to center the FTR around ω_0 .