

Radio-Frequency IC Design

Lecture 14: Transmitters

ELEC 404

Acknowledgement: *RF Microelectronics*. B. Razavi



©Sudip Shekhar

Not to be copied, used, or revised without explicit written permission from the copyright owner.

Direct-Conversion TX


A narrowband modulated signal:

$$\begin{aligned}x(t) &= A(t) \cos[\omega_c t + \phi(t)] \\ &= A(t) \cos \omega_c t \cos[\phi(t)] - A(t) \sin \omega_c t \sin[\phi(t)]\end{aligned}$$

Quadrature baseband signals:

$$x_{BB,I}(t) = A(t) \cos[\phi(t)]$$


$$x_{BB,Q}(t) = A(t) \sin[\phi(t)]$$

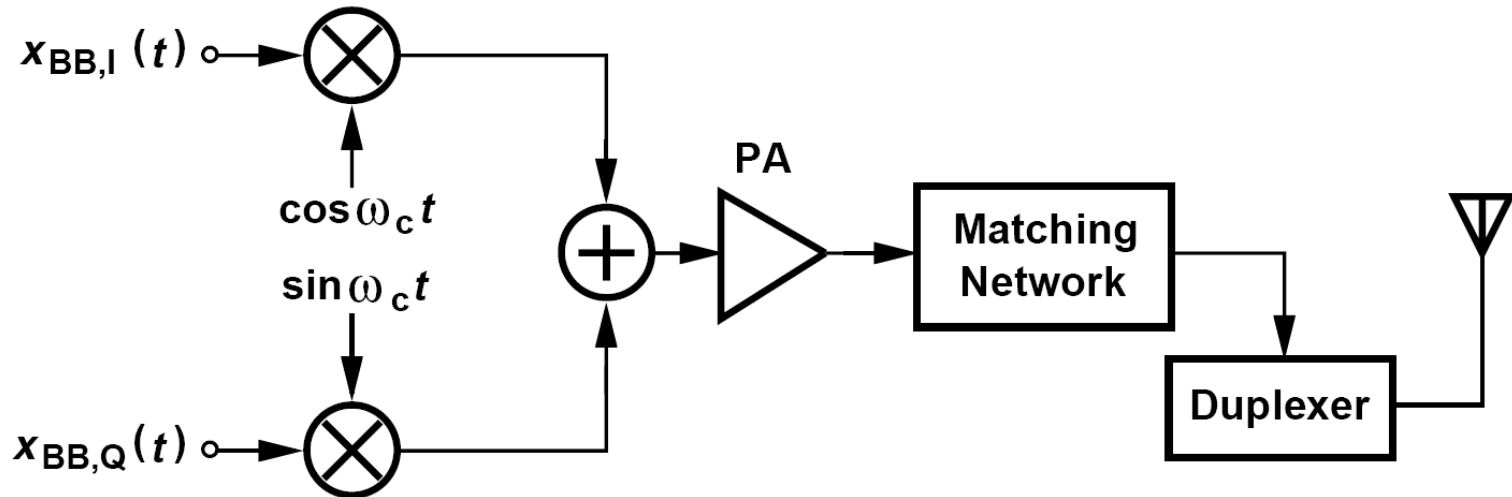

Directly translates the BB spectrum to the RF carrier by means of a “quadrature upconverter”.

Baseband Pulse Shaping

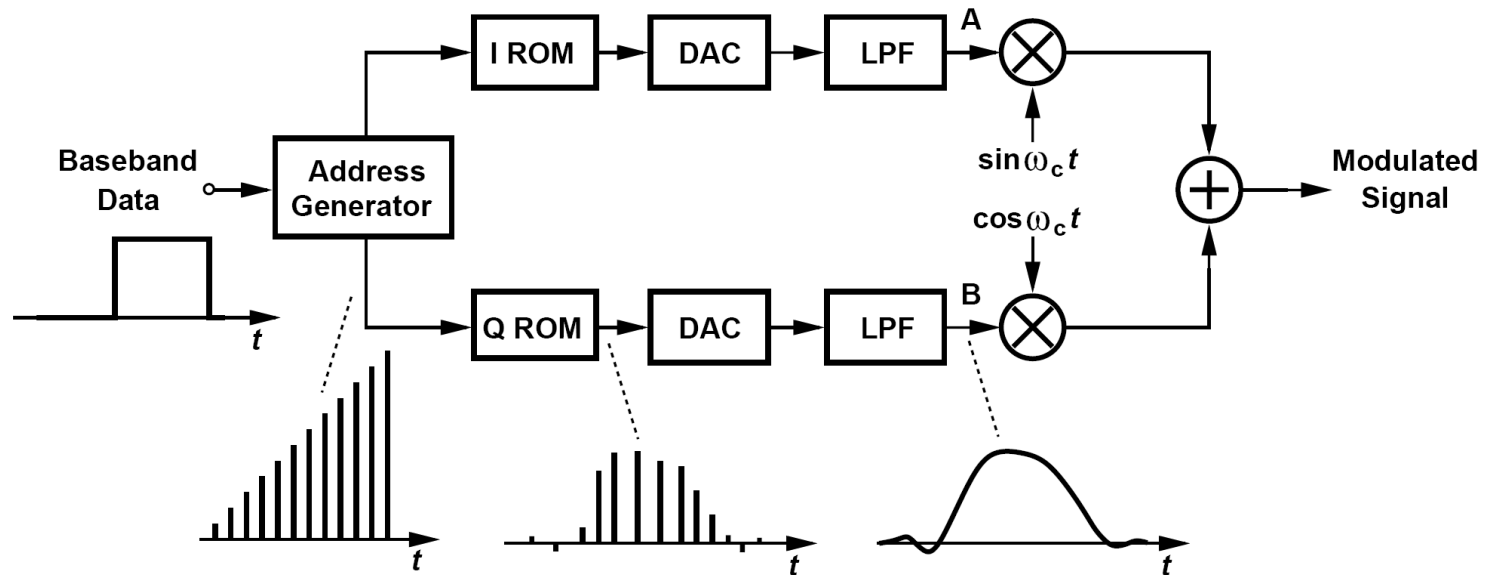
- RF TX performs modulation, upconversion, and power amplification.
- Quadrature BB signals generated by the digital BB processor & converted to analog form by D/A converters.
- Each incoming pulse is smoothed (shaped) to reduce BW
- Mapping to the desired shape preferred in digital domain to avoid bulky analog filters at low BB frequency.



Direct Conversion TX Problems

- **I/Q mismatch & unwanted sideband**
- **I/Q mismatch & constellation distortion**
- **Carrier leakage and constellation distortion**
- **Carrier leakage and power control**
- **Mixer nonlinearity & signal corruption or ACP increase (spectral regrowth)**
- **TX nonlinearity & signal distortion or ACP increase (spectral regrowth)**
- **Oscillator pulling**
- **Noise in RX band transmitted by the TX (Eg. GSM spec)**

Direct-Conversion TX: I/Q Mismatch

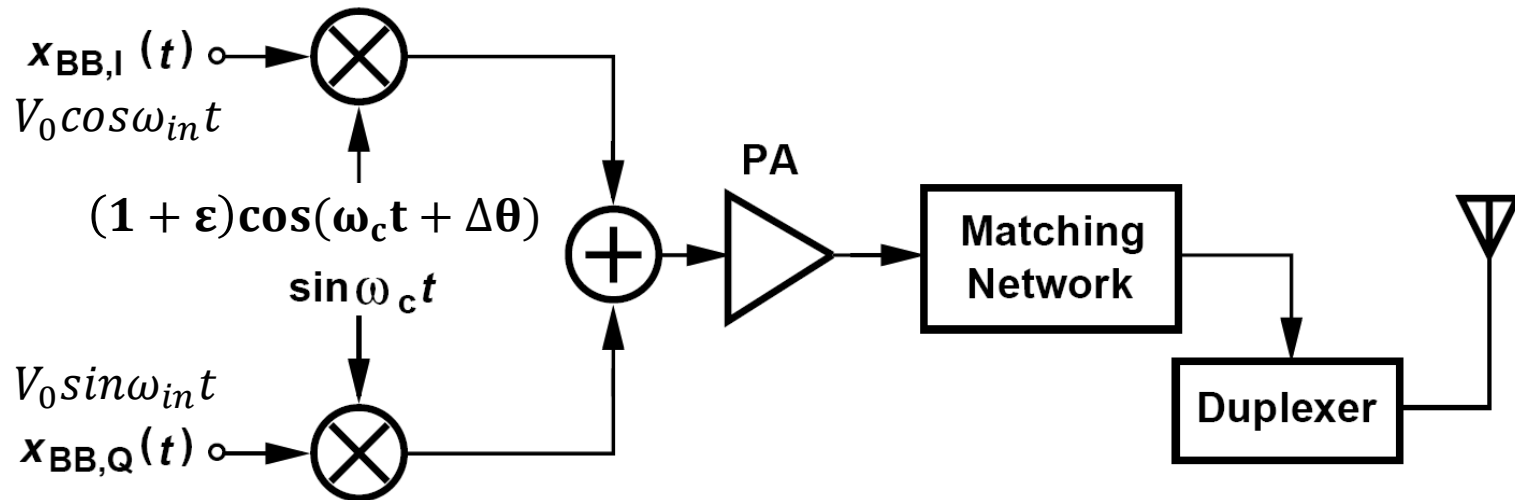



$$\begin{aligned}
 V_{out}(t) &= V_0(1 + \epsilon) \cos \omega_{in} t \cos(\omega_c t + \Delta\theta) - V_0 \sin \omega_{in} t \sin \omega_c t \\
 &= \frac{V_0}{2} [(1 + \epsilon) \cos \Delta\theta + 1] \cos(\omega_c t + \omega_{in}) t - \frac{V_0}{2} (1 + \epsilon) \sin \Delta\theta \sin(\omega_c + \omega_{in}) t \\
 &\quad + \frac{V_0}{2} [(1 + \epsilon) \cos \Delta\theta - 1] \cos(\omega_c - \omega_{in}) t - \frac{V_0}{2} (1 + \epsilon) \sin \Delta\theta \sin(\omega_c - \omega_{in}) t.
 \end{aligned}$$

- Results in unwanted sideband, e.g., at $\omega_c - \omega_{in}$ versus wanted sideband at $\omega_c + \omega_{in}$. For amplitude error ϵ and phase error θ ,

$$\frac{P_-}{P_+} = \frac{(1 + \epsilon)^2 - 2(1 + \epsilon) \cos \Delta\theta + 1}{(1 + \epsilon)^2 + 2(1 + \epsilon) \cos \Delta\theta + 1}$$

Direct-Conversion TX: I/Q Mismatch

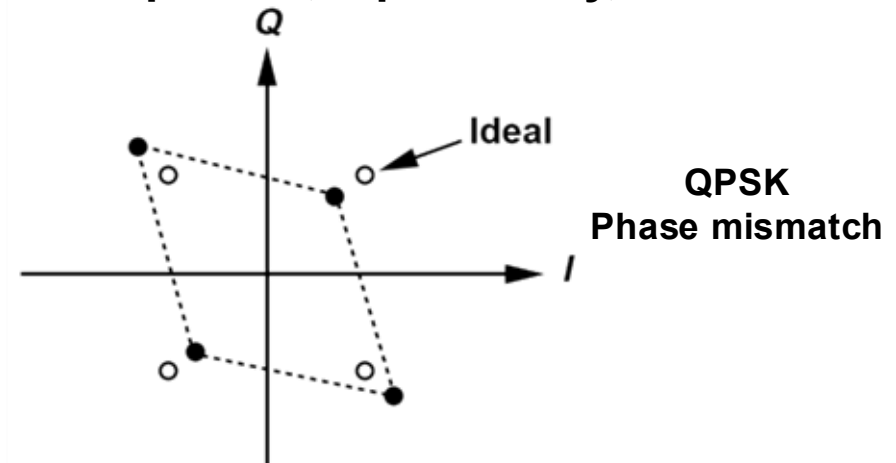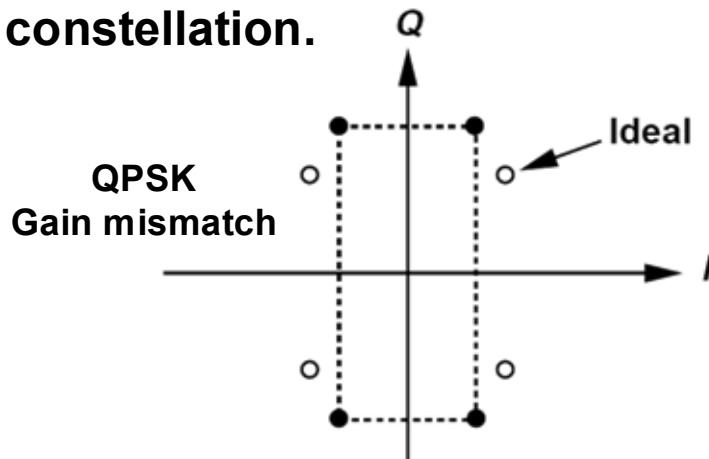- Results in “xtalk” between the quadrature outputs or, equivalently, distortion in the constellation.



$$\begin{aligned}
 x(t) &= \alpha_1(A_c + \Delta A_c) \cos(\omega_c t + \Delta\theta) + \alpha_2 A_c \sin \omega_c t \\
 &= \alpha_1(A_c + \Delta A_c) \cos \Delta\theta \cos \omega_c t + [\alpha_2 A_c - \alpha_1(A_c + \Delta A_c) \sin \Delta\theta] \sin \omega_c t.
 \end{aligned}$$

For the four points in the constellation:

$$\beta_1 = + \left(1 + \frac{\Delta A_c}{A_c}\right) \cos \Delta\theta, \quad \beta_2 = 1 - \left(1 + \frac{\Delta A_c}{A_c}\right) \sin \Delta\theta$$

$$\beta_1 = + \left(1 + \frac{\Delta A_c}{A_c}\right) \cos \Delta\theta, \quad \beta_2 = -1 - \left(1 + \frac{\Delta A_c}{A_c}\right) \sin \Delta\theta$$

$$\beta_1 = - \left(1 + \frac{\Delta A_c}{A_c}\right) \cos \Delta\theta, \quad \beta_2 = 1 + \left(1 + \frac{\Delta A_c}{A_c}\right) \sin \Delta\theta$$

$$\beta_1 = - \left(1 + \frac{\Delta A_c}{A_c}\right) \cos \Delta\theta, \quad \beta_2 = -1 + \left(1 + \frac{\Delta A_c}{A_c}\right) \sin \Delta\theta.$$


Carrier Leakage & Signal Constellation

DC offsets in the analog BB circuitry and BB port of each Upconversion mixer → upconverter output contains a fraction of the *unmodulated* carrier.

$$V_{out}(t) = [A(t) \cos \phi + V_{OS1}] \cos \omega_c t - [A(t) \sin \phi + V_{OS2}] \sin \omega_c t$$

$$V_{out}(t) = A(t) \cos(\omega_c t + \phi) + V_{OS1} \cos \omega_c t - V_{OS2} \sin \omega_c t$$

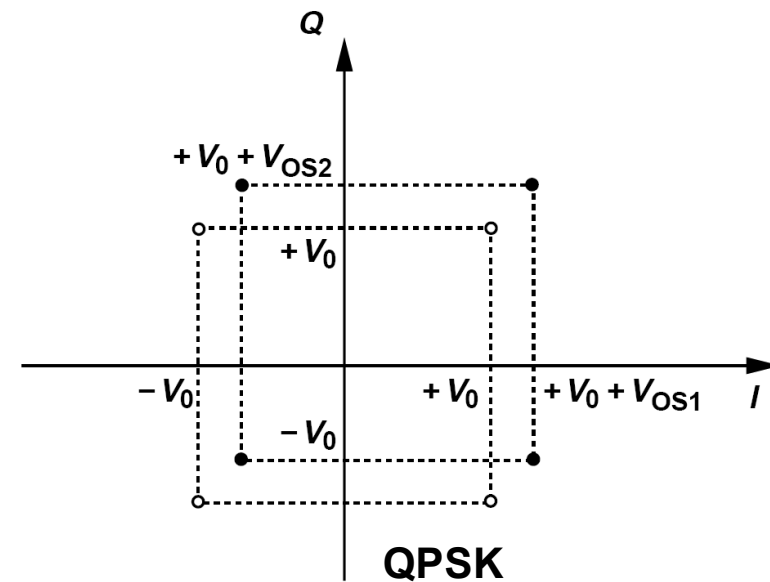
$$\text{Relative Carrier Leakage} = \frac{\sqrt{V_{OS1}^2 + V_{OS2}^2}}{\sqrt{A^2(t)}}$$



- Distorts the signal constellation, raising the EVM @ TX output, and complicates TX power control.


Carrier Leakage & PA Power Control

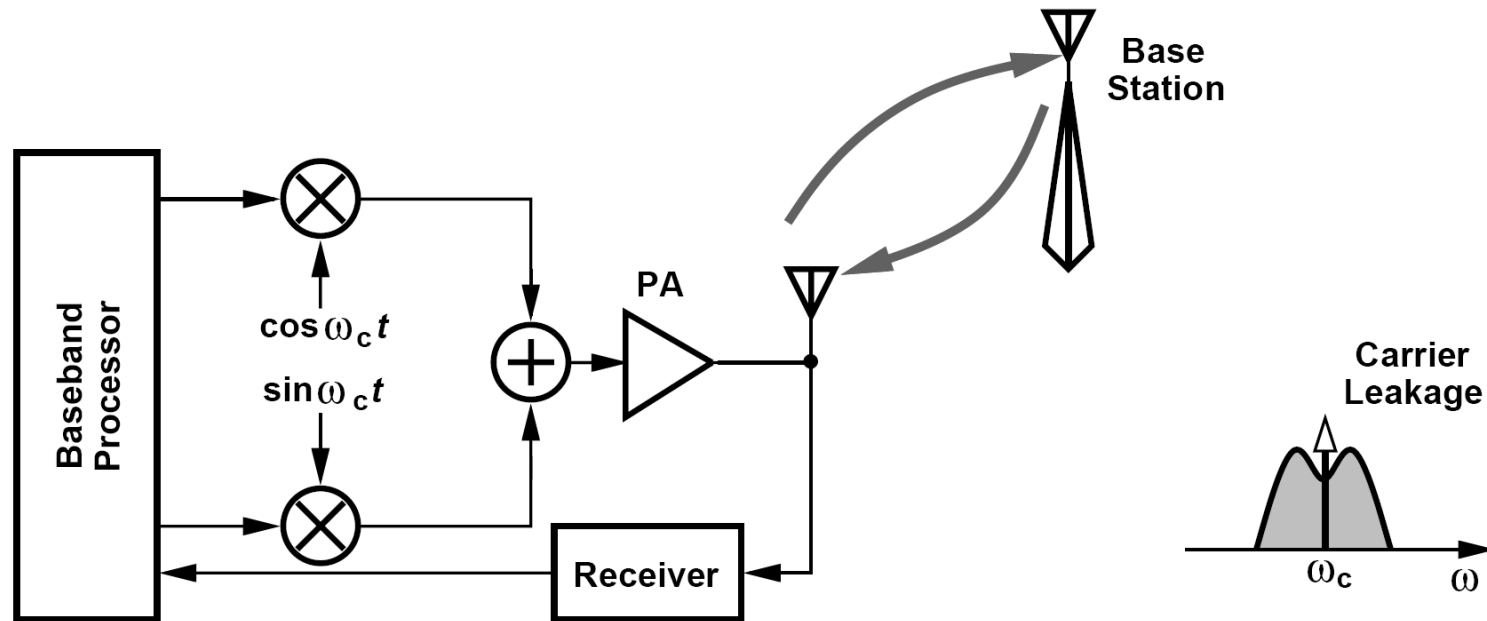- If the output power of the TX must be varied across a wide range by varying the amplitude of the BB signals (& not PA itself), for ex, when CDMA mobiles come closer to the base station to avoid the near-far effect,



Close proximity of BS-UE \rightarrow BS requests UE to reduce its transmitted power \rightarrow carrier leakage power dominates in the TX spectrum, making it difficult to measure the actual signal power.

Carrier Leakage Reduction

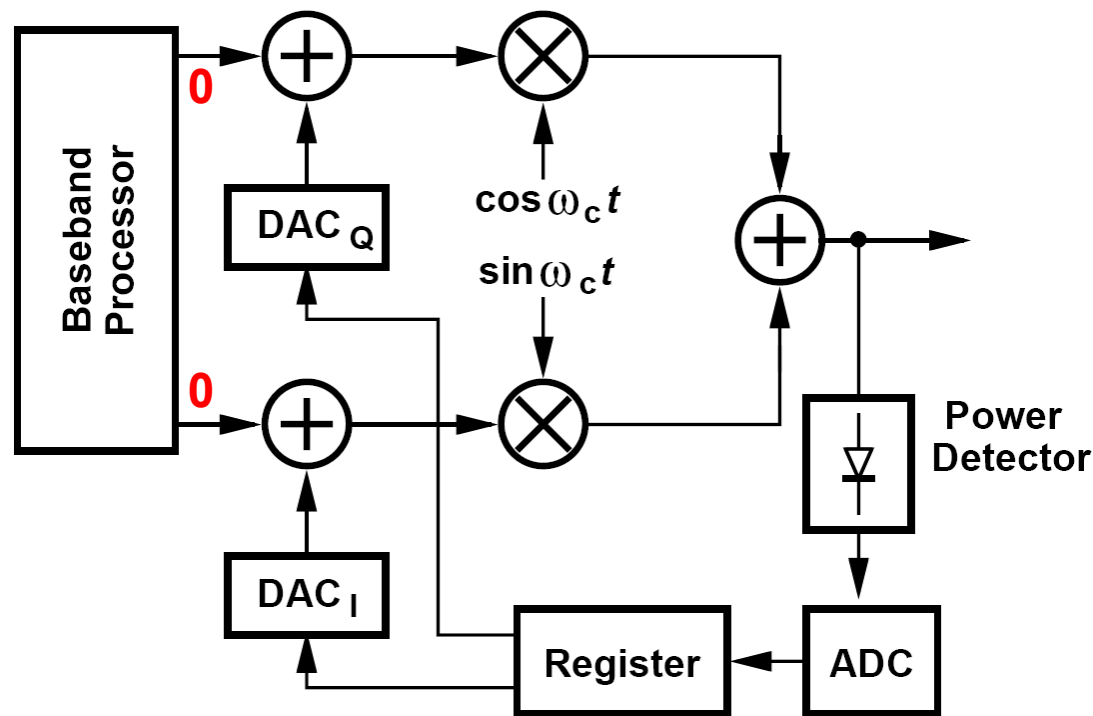

- BB processor produces a zero output \rightarrow detector measures leakage only
- Loop consisting of the TX, the detector, and the DACs drives the leakage toward zero, with the final settings of the DACs stored in the register.
- LMS or exhaustive search calibration

Upconversion of Mixer Non-Linearity

- Excessive nonlinearity in the BB port can corrupt the signal or raise the adjacent channel power (ACP).

Consider GMSK signal

$$V_{out}(t) = A(t) \cos \omega_c t \cos[\phi(t)] - A(t) \sin \omega_c t \sin[\phi(t)]$$


If BB I/Q inputs experience a nonlinearity given by $\alpha_1 x + \alpha_3 x^3$,

$$\begin{aligned} V_{out}(t) &= (\alpha_1 A \cos \phi + \alpha_3 A^3 \cos^3 \phi) \cos \omega_c t - (\alpha_1 A \sin \phi + \alpha_3 A^3 \sin^3 \phi) \sin \omega_c t \\ &= \left(\alpha_1 A + \frac{3}{4} \alpha_3 A^3 \right) \cos(\omega_c t + \phi) + \frac{\alpha_3 A^3}{4} \cos(\omega_c t - 3\phi). \end{aligned}$$

- 2nd term also represents a GMSK signal but with 3X modulation index → occupying a larger BW.
- For variable-envelope signals, $A^3(t)$ appears in both terms, exacerbating the effect.

TX Linearity

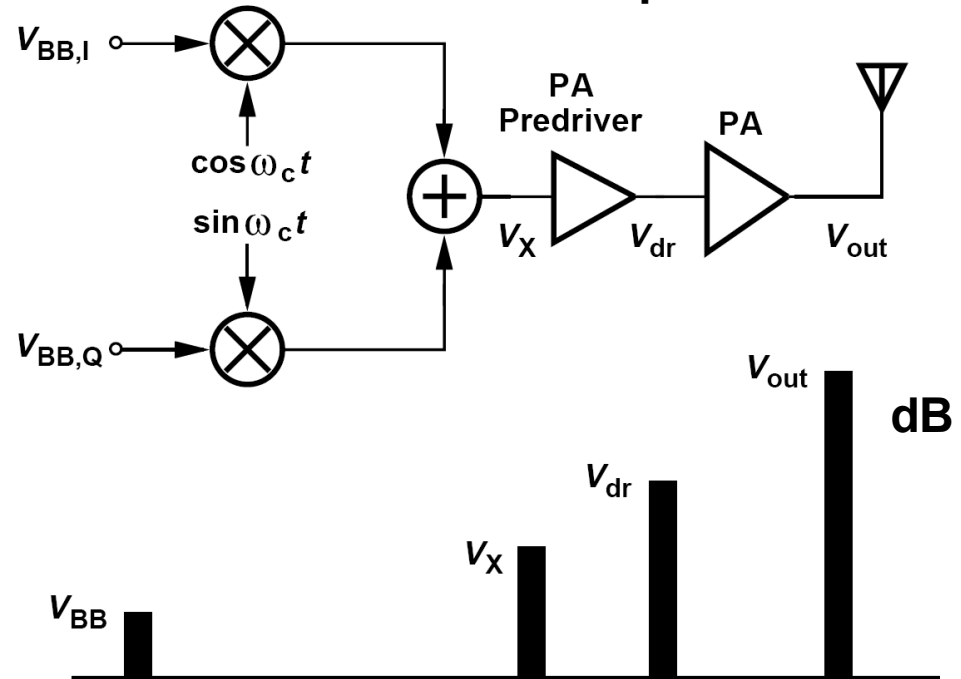
- Distortion of a variable-envelope signal is characterized by the compression that it experiences.
- Largest voltage swing occurs at PA o/p \rightarrow PA dominates TX compression
- In a good design, preceding stages must remain well below compression as the PA o/p approaches P_{1dB} .




- For linearity, *maximize* the PA gain and *minimize* the output swing of the predriver and the stages preceding it \rightarrow makes PA design difficult
- Operating at *back-off*: Average power must remain XdB below P_{1dB} .

Back-off Example

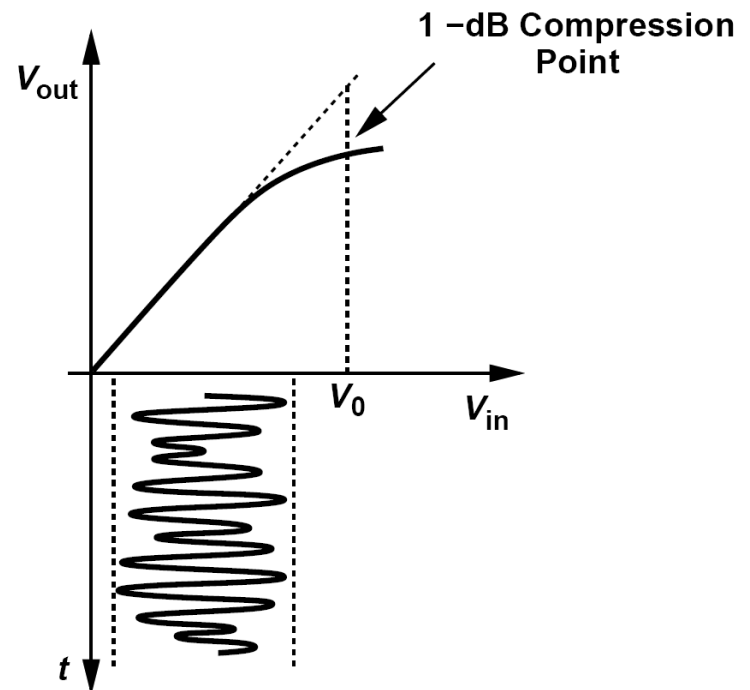- In 802.11a, the average power of the 64-QAM OFDM signal must remain about 8dB below P_{1dB} of a given circuit → circuit must operate at 8-dB back-off.
- If a peak swing of V_0 places the circuit at the 1dB compression point, then the average signal swing must not exceed $V_0/2.51$.




LO Pulling (esp. in Direct Conv. TX)

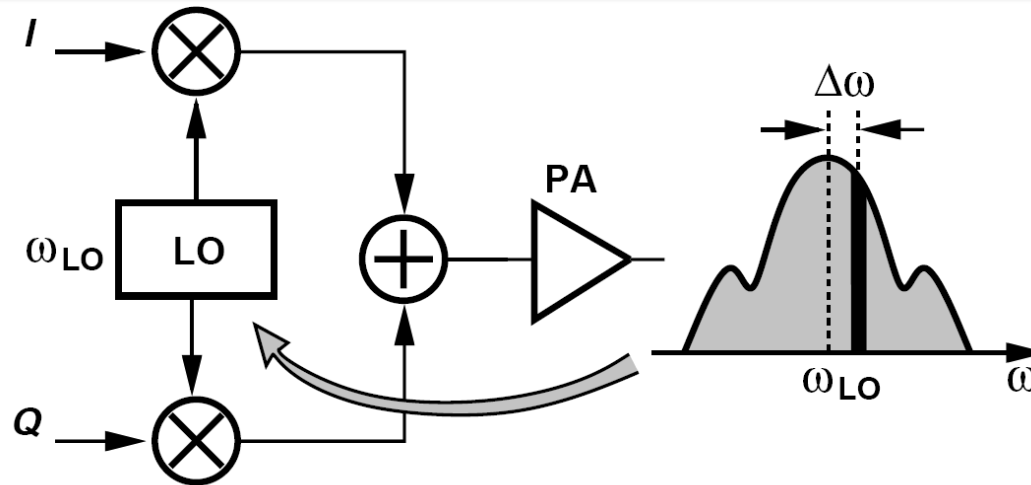



- PA output exhibits very large swings ($20V_{pp}$ for 1W into 50Ω load)
- Couples to LO through the silicon substrate, package parasitics, and PCB traces, even if PA is off-chip.
- In Direct-conversion TX, PA center frequency $\omega_c = \omega_{LO}$.
- To avoid injection pulling, make the two frequencies different \rightarrow derive ω_c from ω_{LO} through frequency division or mixing.

Modern Direct-Conversion TX

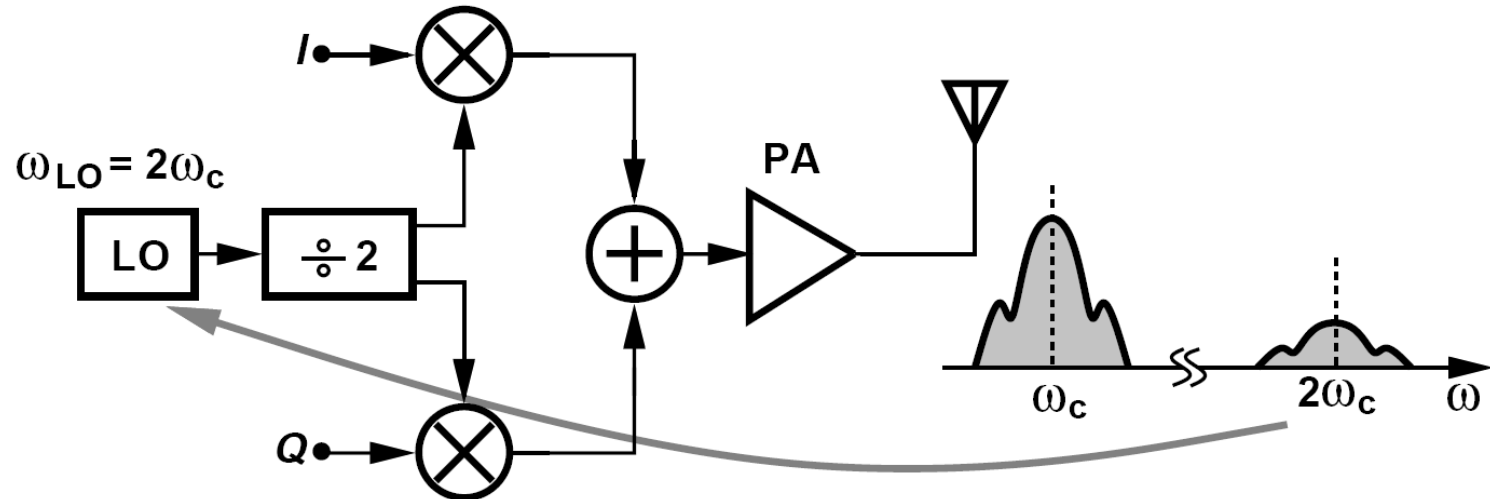


- **Popular architecture:**
 - (1) injection pulling is greatly reduced
 - (2) divider readily provides quadrature phases of the carrier
- **Divider speed critical, operating at twice of ω_c**

Use Mixing to Derive Frequencies?

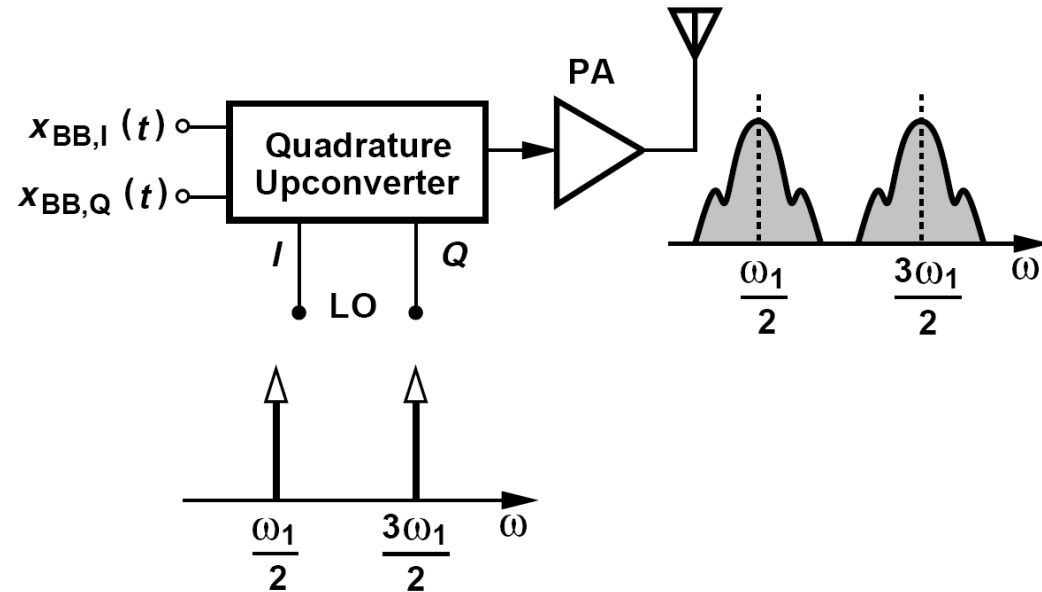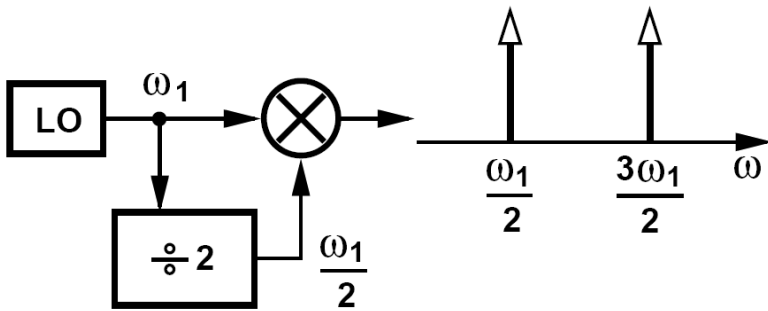


- Suppress one component to avoid corrupting communication in other channels or bands
- Suppression difficult by filtering (only 3X frequency difference) – only 25-30dB
- Use single-sideband mixing (SSB mixing) – 30-40dB or even another 25-30dB by SSB followed by 2nd order filtering

Single-Sideband Mixing

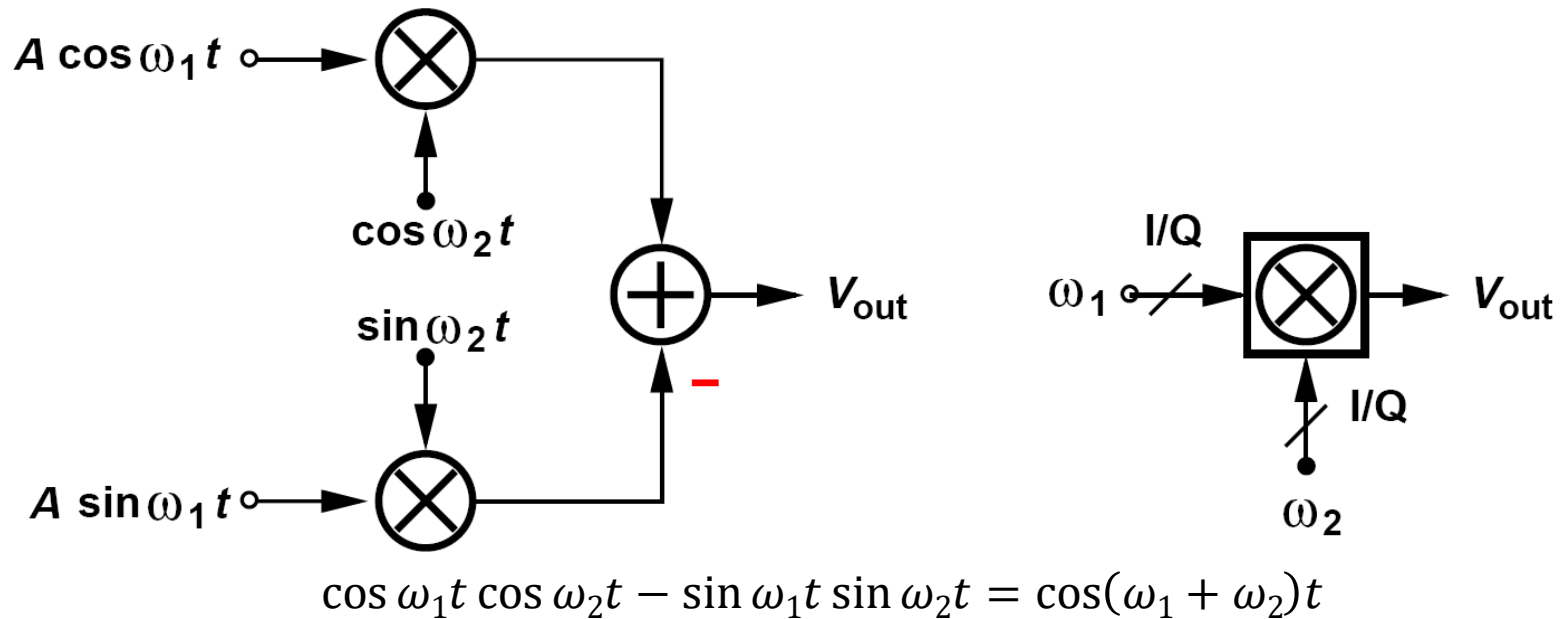


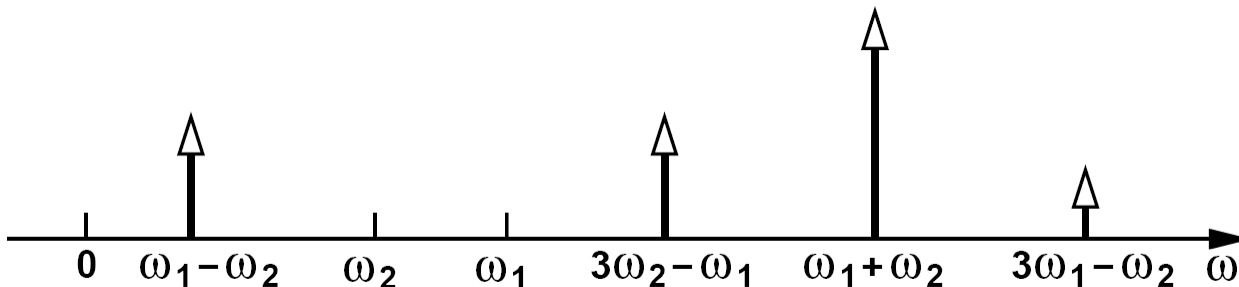- Gain and phase mismatches lead to an unwanted sideband
- Harmonics due to nonlinearity on either port result in mixer spurs




SSB Mixer with Quad Outputs for DCTX

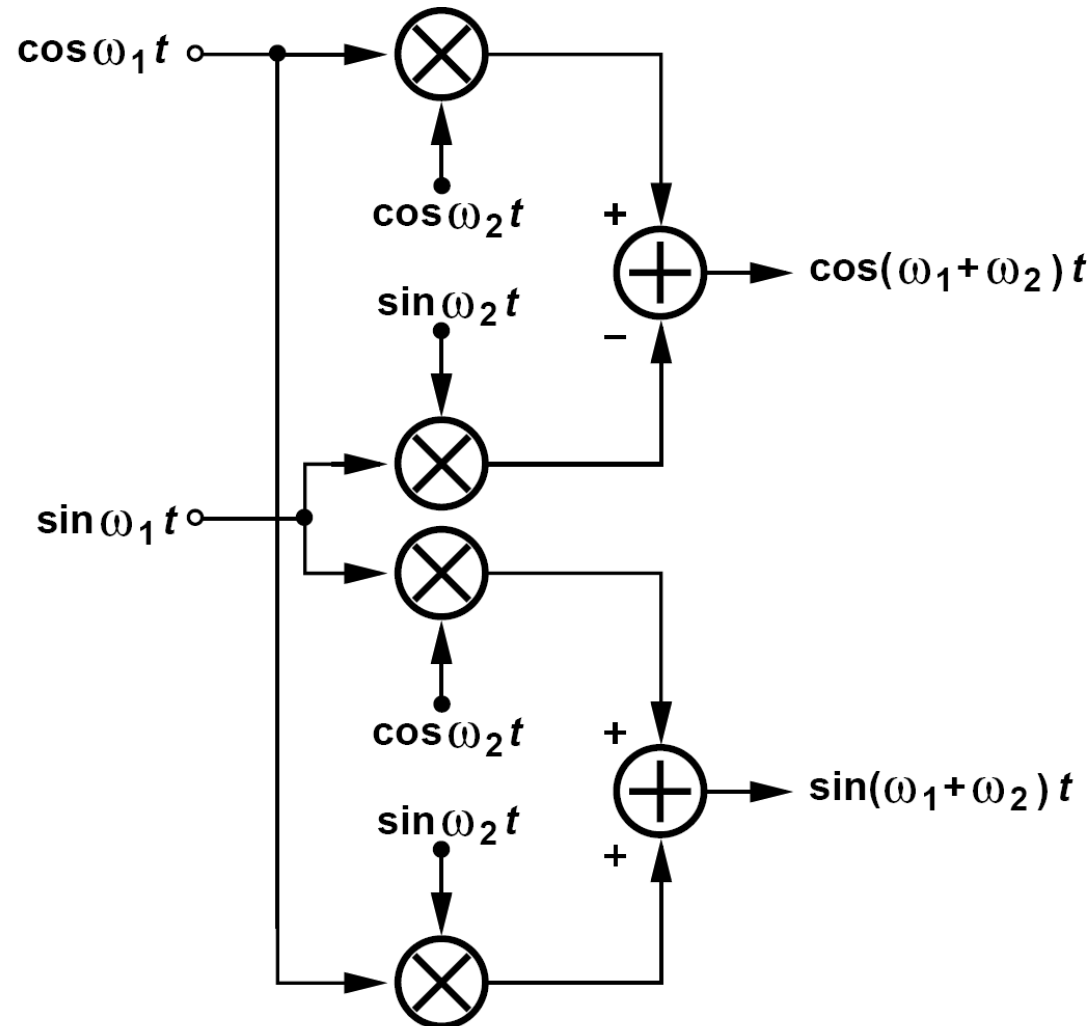- As $\sin \omega_1 t \cos \omega_2 t + \cos \omega_1 t \sin \omega_2 t = \sin(\omega_1 + \omega_2)t$, duplicate the SSB mixer.




DCTX Using SSB Mixing in LO Path

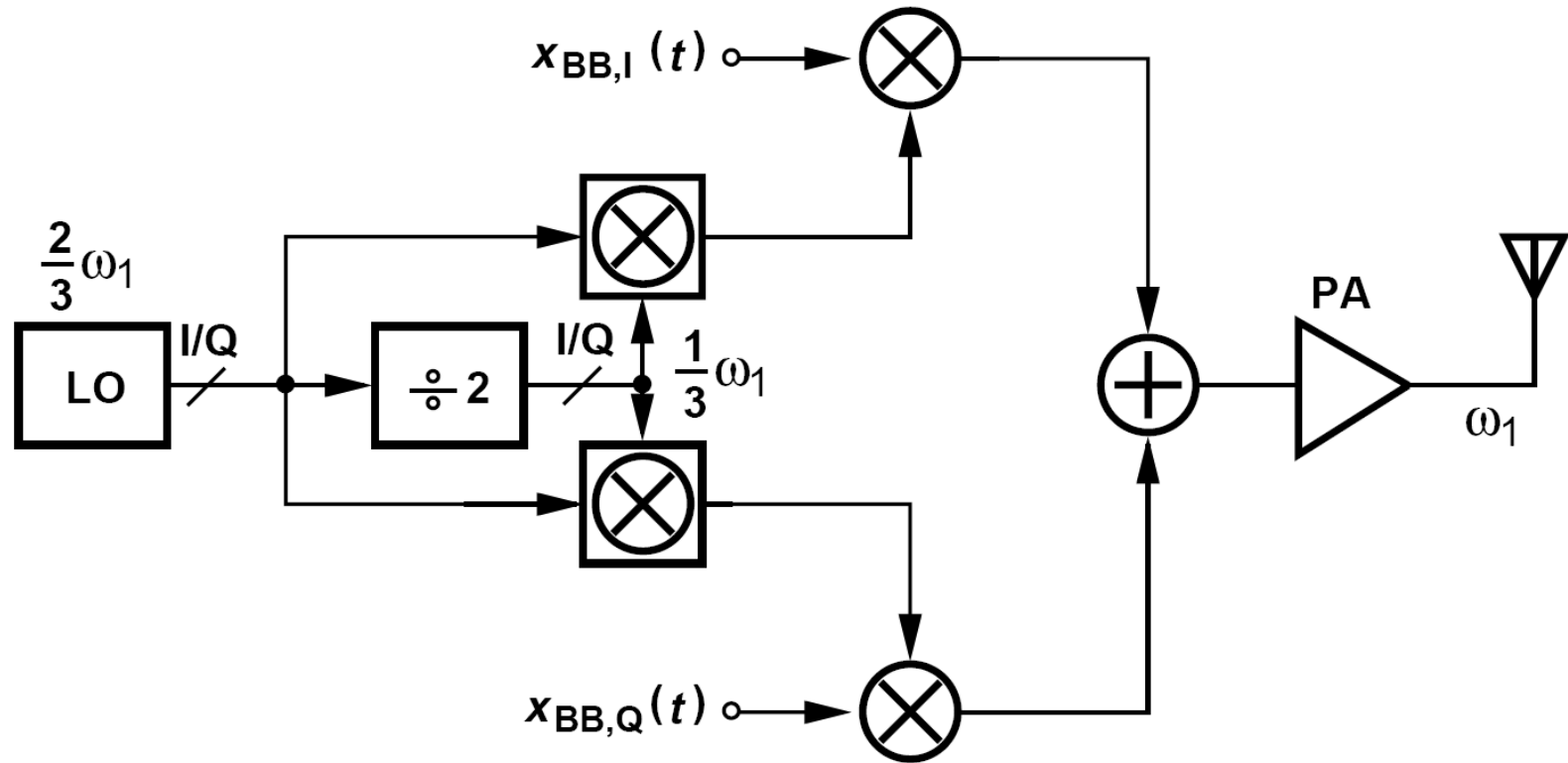

- Carrier and LO sufficiently different \rightarrow free from injection pulling.
- Spurs at $5\omega_1/3$ and other harmonic-related frequencies
- LO must provide quadrature phases

Heterodyne TX

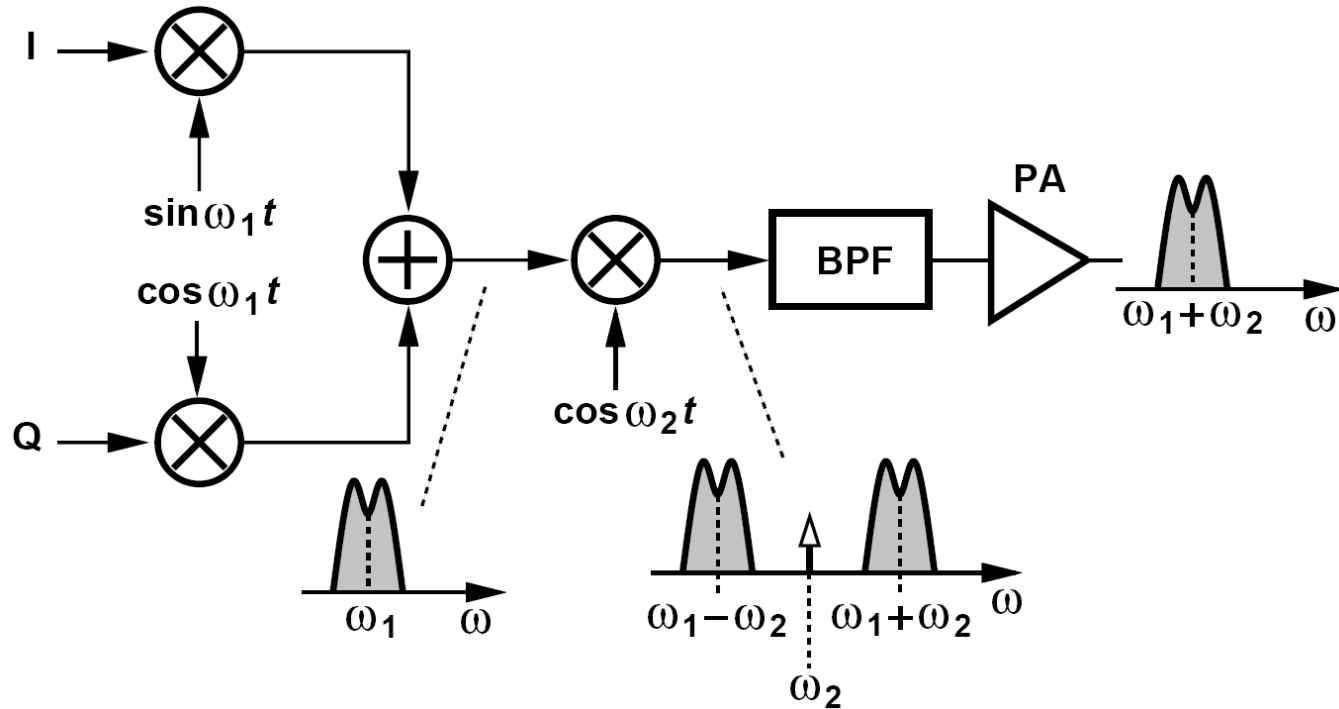
2-step signal upconversion \rightarrow LO frequency far from the PA output spectrum



- I/Q upconversion occurs at a significantly lower frequency than the carrier, exhibiting smaller gain and phase mismatches.
- Two LO, BPF needed.
- Spurs from harmonics of LO1 and LO2.

Sliding-IF TX


Derive the required LO1 phases from LO2

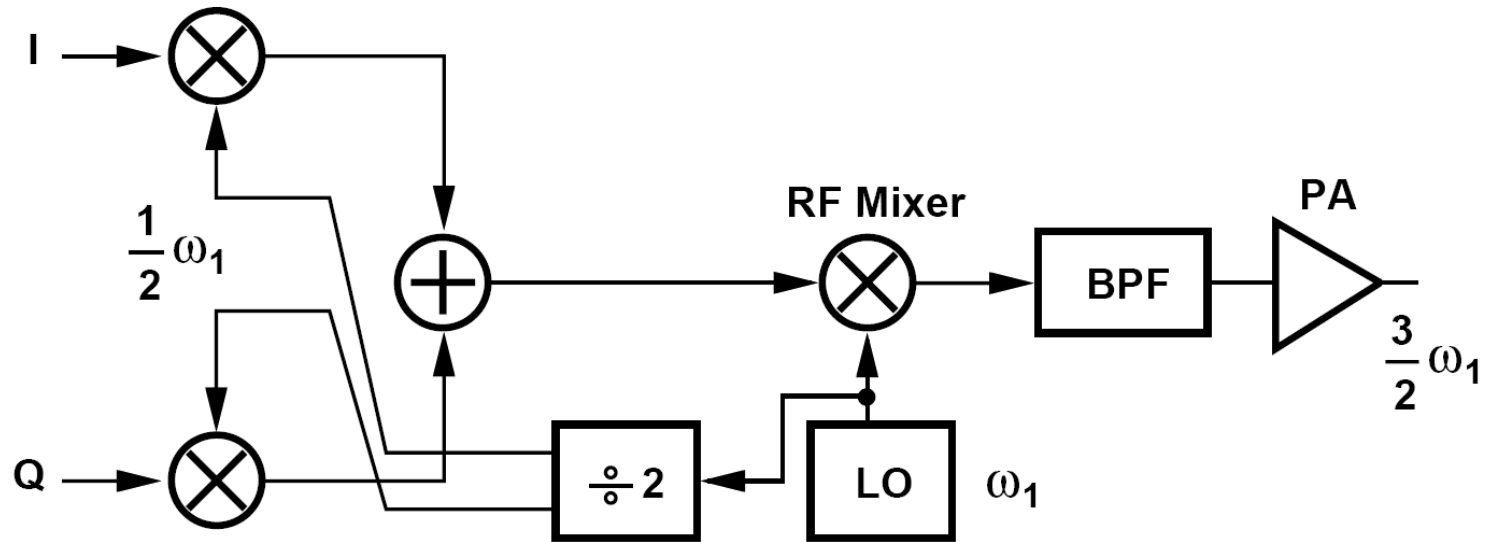

- **Mixing spurs limit usage of heterodyne TX to modulation schemes with moderate SNR (10–12dB) (e.g., QPSK) or systems with a moderate BER (10^{-2})**


OOK Transceivers: Low-power

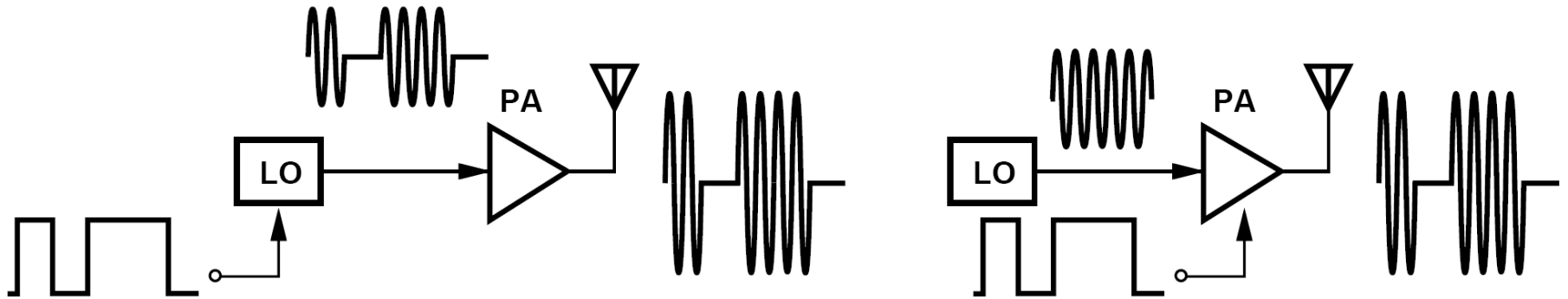- “On-off keying” (OOK) modulation is a special case of ASK where the carrier amplitude is switched between zero and maximum.



- LO is directly turned ON/OFF by the binary BB data → If the LO swings are large enough, the PA also experiences relatively complete switching and delivers an OOK waveform to the antenna. LO cannot be easily controlled by a PLL.

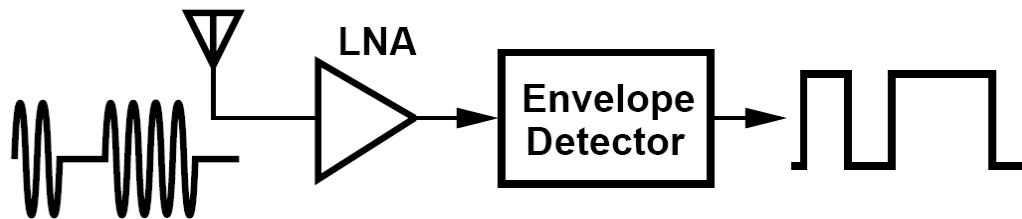- PA directly turned ON/OFF by the binary BB data



An LNA followed by an envelope detector can recover the binary data.