

Switched-Capacitor Circuits

**Reference: Chapter 10 of the text
“Analog Integrated Circuit Design”
by
David Johns and Ken Martin**

Chapter 14 of the 2nd Edition of the text by Tony Chan Carusone, David Johns, and Ken Martin

The material of this presentation is courtesy of Dr. Ken Martin.


Basic Building Blocks

Opamps


- Ideal opamps usually assumed.
- Important non-idealities
 - dc gain: sets the accuracy of charge transfer, hence, transfer-function accuracy.
 - unity-gain freq, phase margin & slew-rate: sets the max clocking frequency. A general rule is that unity-gain freq should be 5 times (or more) higher than the clock-freq.
 - dc offset: Can create dc offset at output. Circuit techniques to combat this which also reduce $1/f$ noise.

Basic Building Blocks

Double-Poly Capacitors

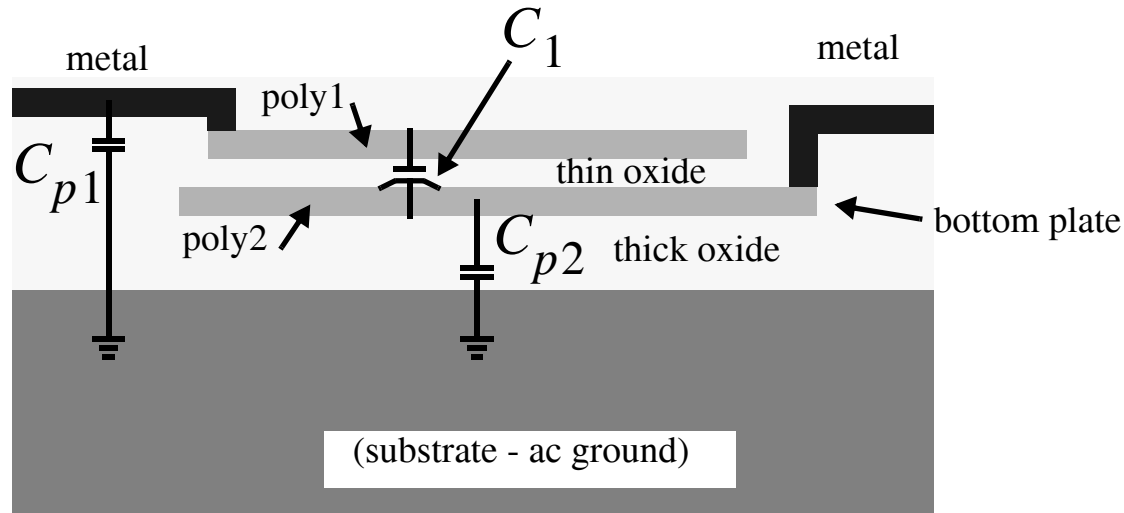

cross-section view

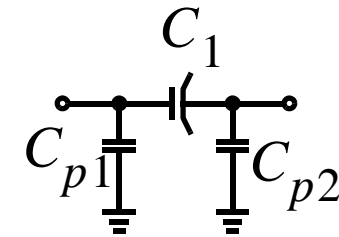


equivalent circuit

- Substantial parasitics with large bottom plate capacitance (20 percent of C_1)
- Also, metal-metal capacitors are used but they also have parasitic capacitances.


Basic Building Blocks

Switches



Symbol

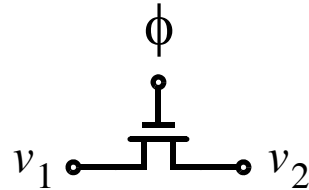

n-channel

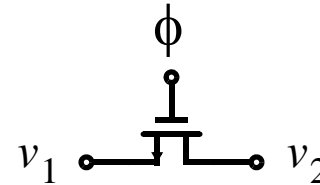


p-channel

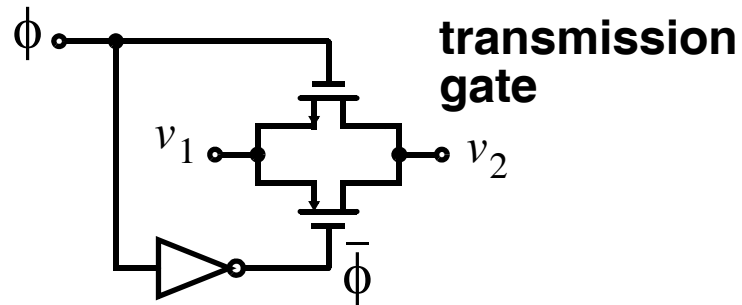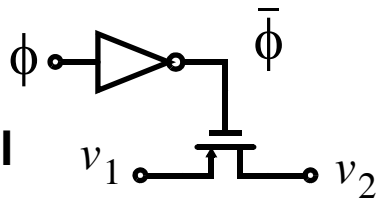


- MOSFET switches are good switches.
 - large off-resistance
 - low on-resistance in the range of few tens of Ω to a few $k\Omega$ (depending on transistor sizing)
- However, have non-linear parasitic capacitances.

Basic Building Blocks

Non-Overlapping Clocks

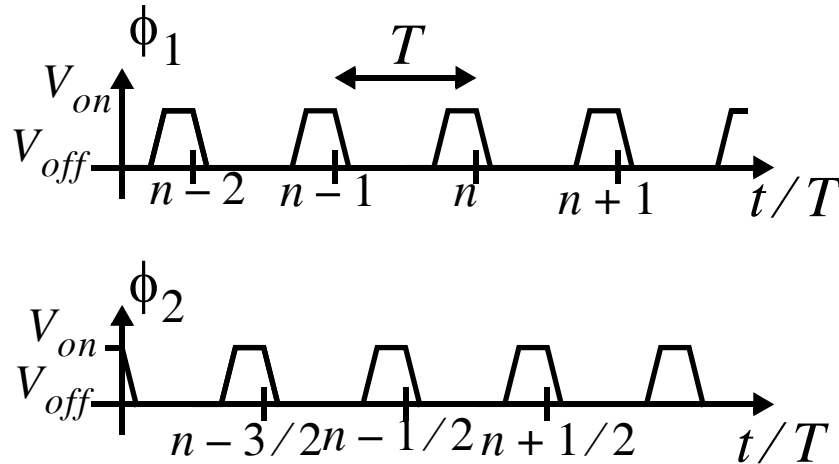


$$f_s \equiv \frac{1}{T}$$

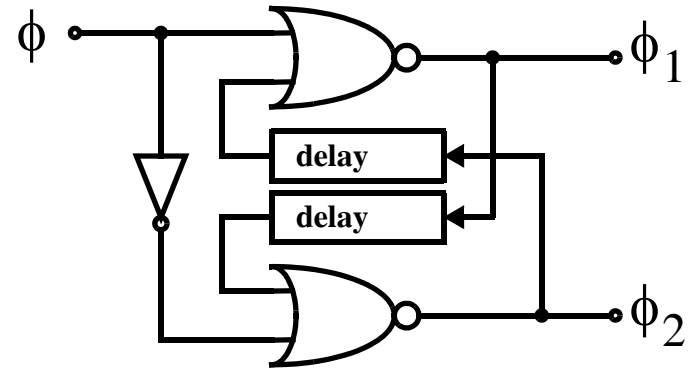

- Non-overlapping clocks — both clocks are never on at same time
- Needed to ensure charge is not inadvertently lost.
- Integer values occur at end of ϕ_1 .
- End of ϕ_2 is 1/2 off integer value.

Switched-Capacitor Resistor Equivalent

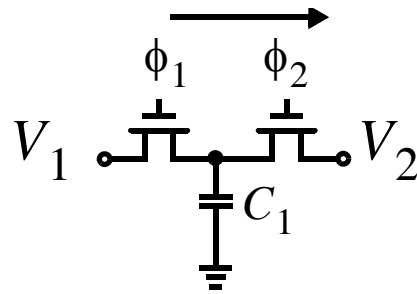

$$\Delta Q = C_1(V_1 - V_2) \text{ every clock period}$$



$$R_{eq} = \frac{T}{C_1}$$

$$Q_x = C_x V_x \tag{1}$$

- C_1 charged to V_1 and then V_2 during each clk period.

$$\Delta Q_1 = C_1(V_1 - V_2) \tag{2}$$

- Find equivalent average current

$$I_{avg} = \frac{C_1(V_1 - V_2)}{T} \tag{3}$$

where T is the clock period.

Switched-Capacitor Resistor Equivalent

- For equivalent resistor circuit

$$I_{eq} = \frac{V_1 - V_2}{R_{eq}} \quad (4)$$

- Equating two, we have

$$R_{eq} = \frac{T}{C_1} = \frac{1}{C_1 f_s} \quad (5)$$

- This equivalence is useful when looking at low-frequency operation of a SC-circuit.
- For higher frequencies, discrete-time analysis is used.


Resistor Equivalence Example

- What is the equivalent resistance of a $5pF$ capacitance sampled at a clock frequency of $100kHz$.
- Using (5), we have

$$R_{eq} = \frac{1}{(5 \times 10^{-12})(100 \times 10^3)} = 2M\Omega$$



- Note that a very large equivalent resistance of $2M\Omega$ can be realized.
- Requires only 2 transistors, a clock and a relatively small capacitance.
- In a typical CMOS process, such a large resistor would normally require a huge amount of silicon area.

Parasitic-Sensitive Integrator

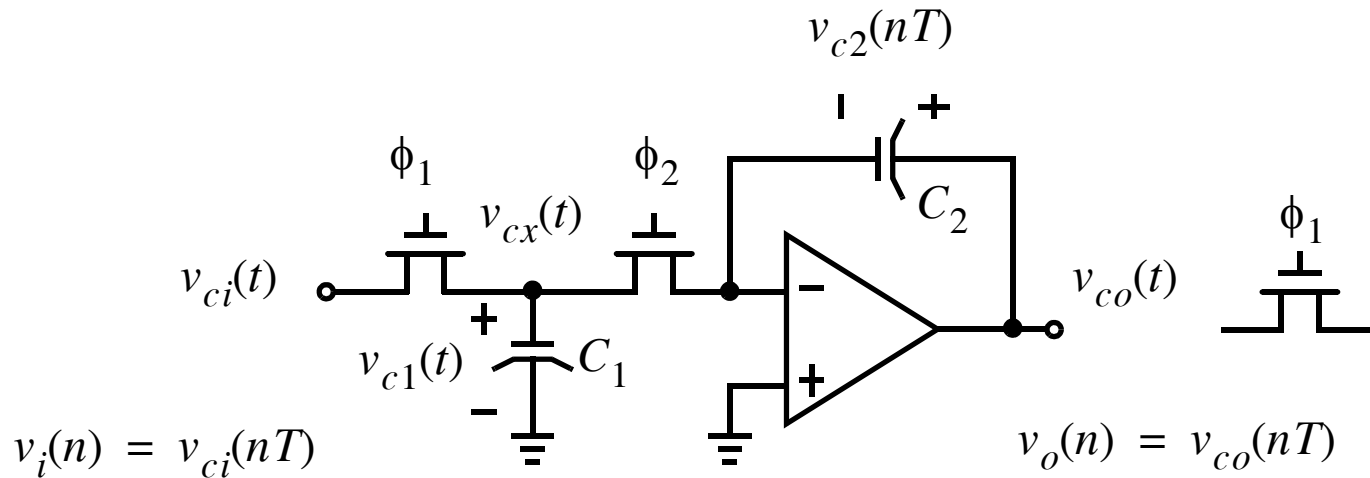

- Start by looking at a simple integrator (note: this structure is sensitive to parasitic capacitances)
- Want to find output voltage at end of ϕ_1 in relation to input sampled at end of ϕ_1 .

Parasitic-Sensitive Integrator

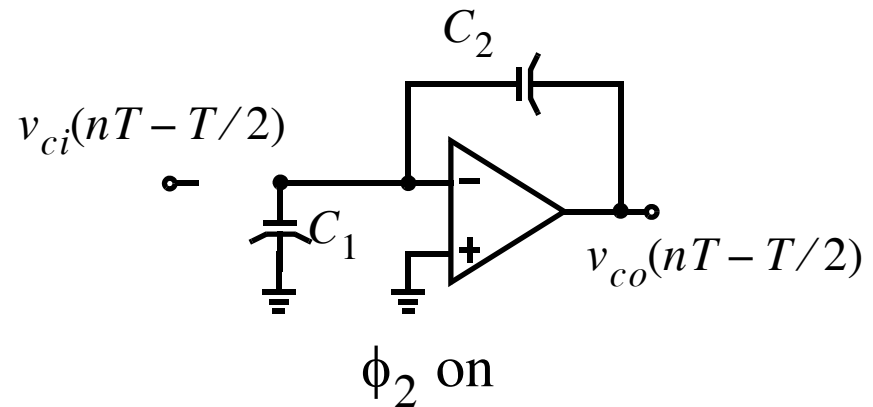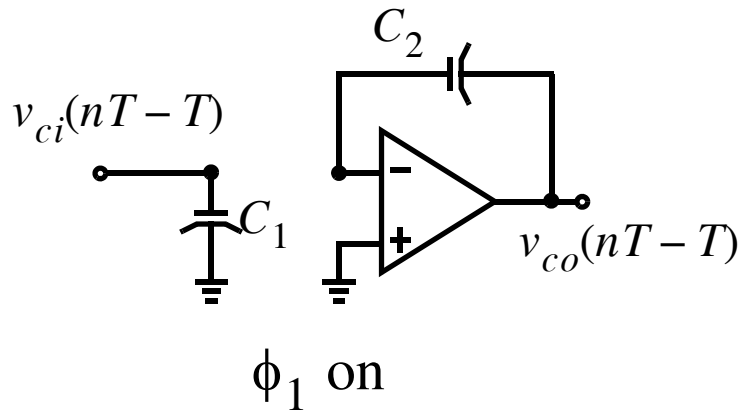

- At end of ϕ_2

$$C_2 v_{co}(nT - T/2) = C_2 v_{co}(nT - T) - C_1 v_{ci}(nT - T) \quad (6)$$

- But would like to know the output at end of ϕ_1

$$C_2 v_{co}(nT) = C_2 v_{co}(nT - T/2) \quad (7)$$

- leading to

$$C_2 v_{co}(nT) = C_2 v_{co}(nT - T) - C_1 v_{ci}(nT - T) \quad (8)$$

Parasitic-Sensitive Integrator

- Modify above to write


$$v_o(n) = v_o(n-1) - \frac{C_1}{C_2} v_i(n-1) \quad (9)$$

and taking z-transform and re-arranging, leads to

$$H(z) \equiv \frac{V_o(z)}{V_i(z)} = -\left(\frac{C_1}{C_2}\right) \frac{1}{z-1} \quad (10)$$

- Note that gain-coefficient is determined by a ratio of two capacitance values.
- Ratios of capacitors can be set very accurately on an integrated circuit (within 0.1 percent)
- Leads to very accurate transfer-functions.

Typical Waveforms

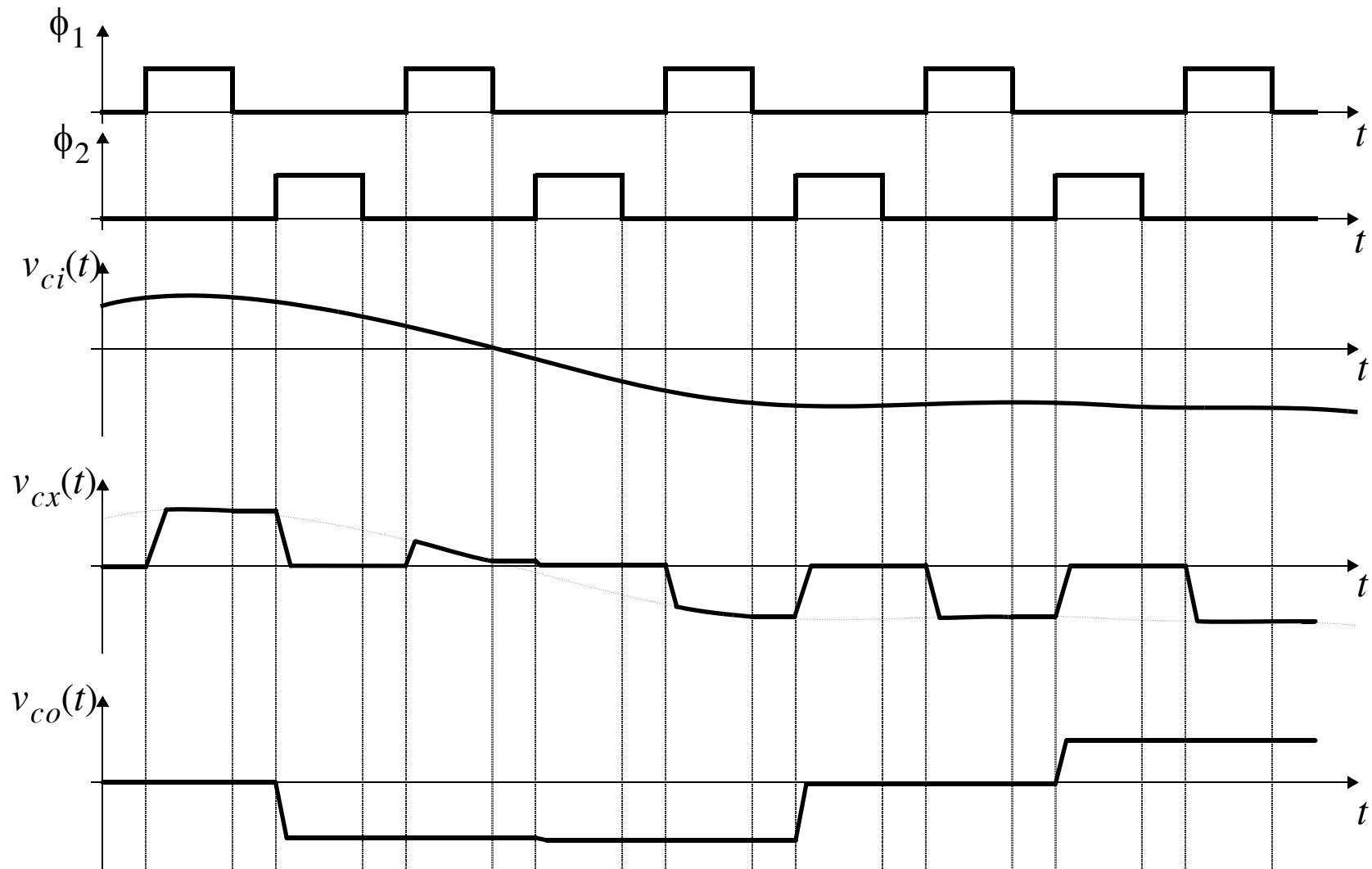

Low Frequency Behavior

- From Equation (10) :

$$H(z) = -\left(\frac{C_1}{C_2}\right)\frac{1}{z-1} \quad (11)$$

- To find frequency response, recall

$$z = e^{j\omega T} = \cos(\omega T) + j\sin(\omega T) \quad (12)$$

$$H(e^{j\omega T}) = -\left(\frac{C_1}{C_2}\right)\frac{1}{\cos(\omega T) + j\sin(\omega T) - 1} \quad (13)$$

Low Frequency Behavior

- Above is exact but when $\omega T \ll 1$ (i.e., at low frequencies)


$$H(e^{j\omega T}) \cong -\left(\frac{C_1}{C_2}\right)\frac{1}{j\omega T} \quad (14)$$

- Thus, the transfer function is same as a continuous-time integrator having a gain constant of

$$K_I \cong \frac{C_1}{C_2} \frac{1}{T} \quad (15)$$

which is to the first order approximation is only a function of the integrator capacitor ratio and clock frequency.

Parasitic Capacitance Effects

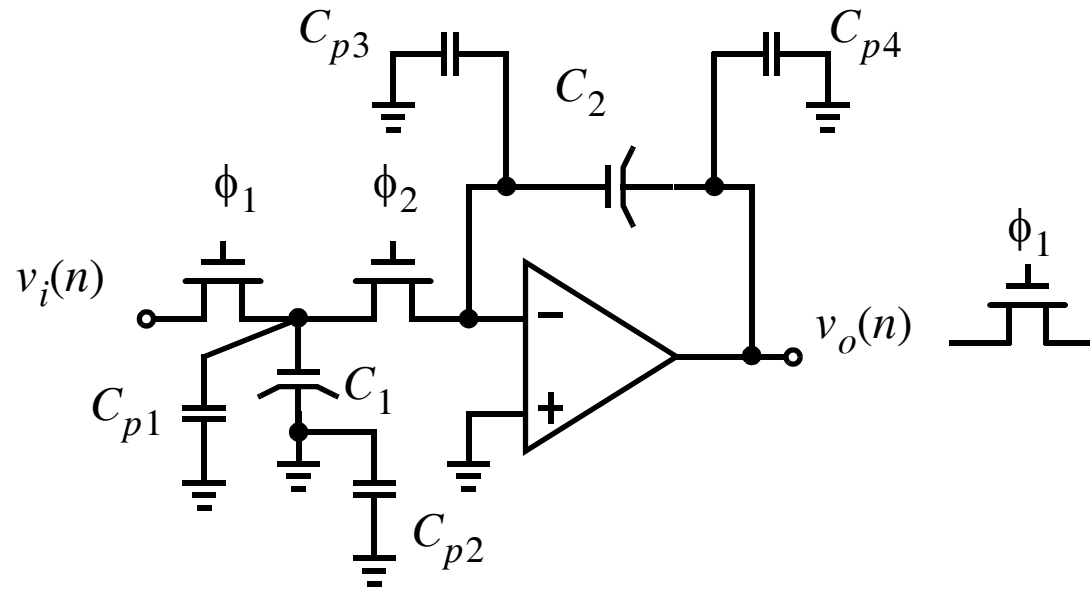


- Accounting for parasitic capacitances, we have

$$H(z) = -\left(\frac{C_1 + C_{p1}}{C_2}\right) \frac{1}{z-1} \quad (16)$$


- Thus, gain coefficient is not well controlled and partially non-linear (due to C_{p1} being non-linear).

Parasitic-Insensitive Integrators

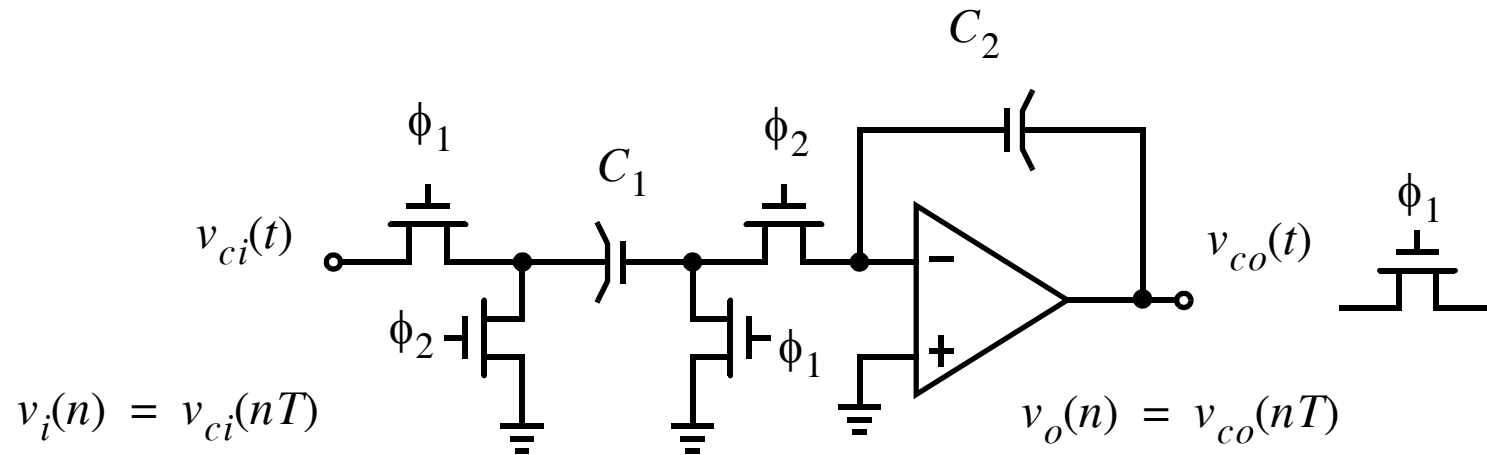

- By using 2 extra switches, integrator can be made insensitive to parasitic capacitances
 - more accurate transfer-functions
 - better linearity (since non-linear capacitances become unimportant)

Parasitic-Insensitive Integrators

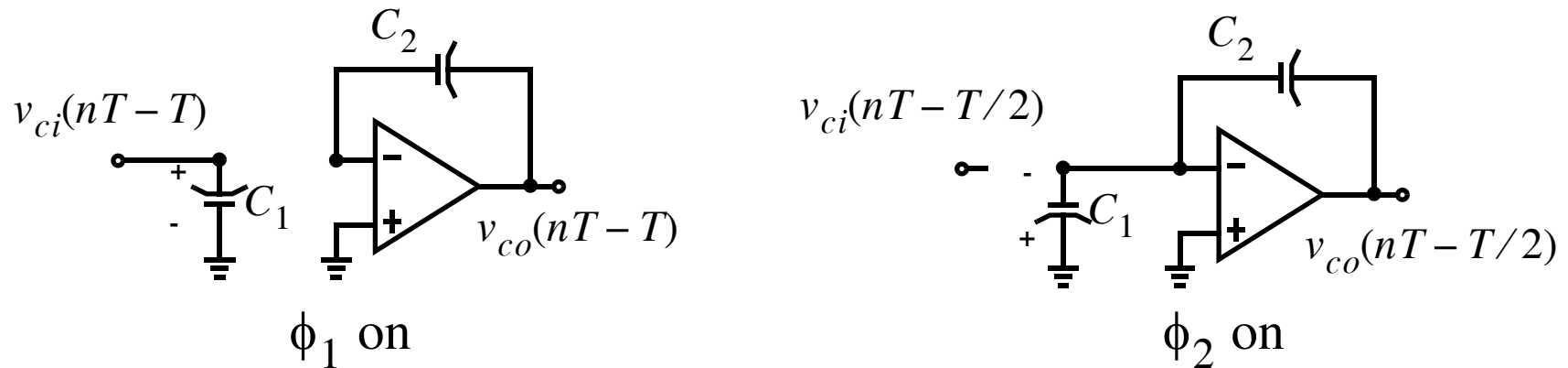


- Same analysis as before except that C_1 is switched in polarity before discharging into C_2 .

$$H(z) \equiv \frac{V_o(z)}{V_i(z)} = \left(\frac{C_1}{C_2} \right) \frac{1}{z - 1} \quad (17)$$

- A positive integrator (rather than negative as before)

Parasitic-Insensitive Integrators

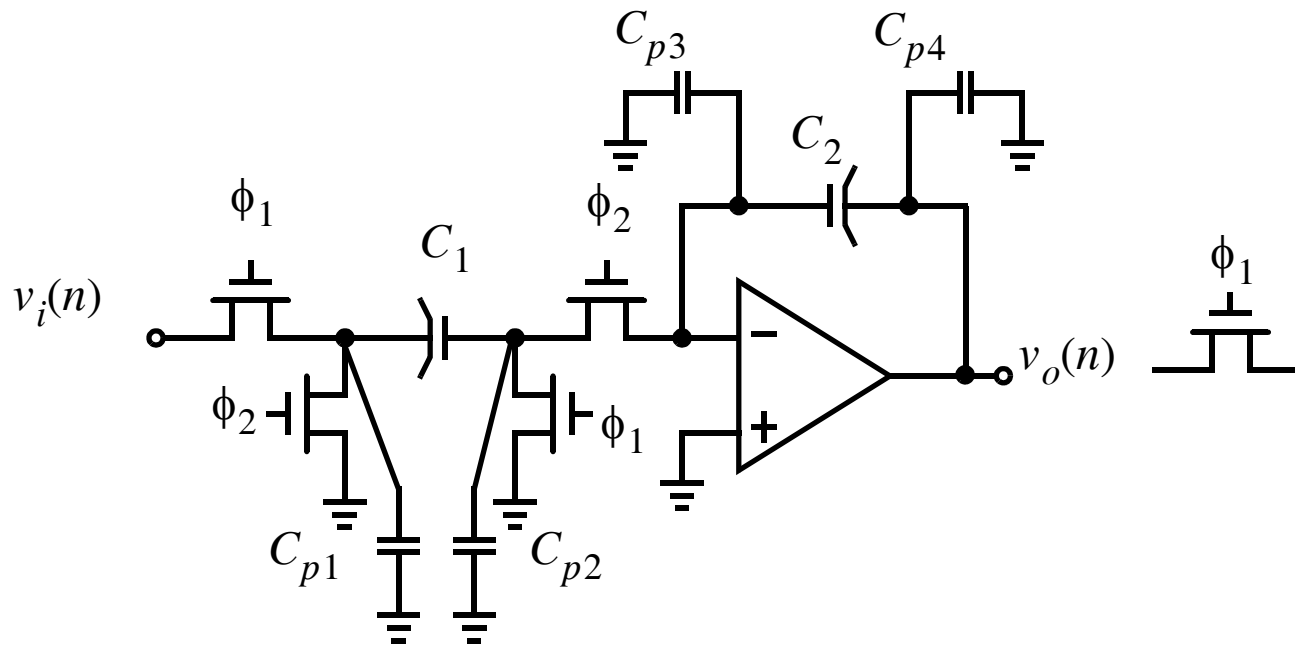


- C_{p3} has little effect since it is connected to virtual gnd
- C_{p4} has little effect since it is driven by output
- C_{p2} has little effect since it is either connected to virtual gnd or physical gnd.

Parasitic-Insensitive Integrators

- C_{p1} is continuously being charged to $v_i(n)$ and discharged to ground.
- ϕ_1 on — both C_1 and C_{p1} are charged to $v_i(n-1)$.
- ϕ_2 on — C_{p1} is discharged through the ϕ_2 switch attached to its node and does not affect the charge accumulating on C_2 .
- While the parasitic capacitances may slow down settling time behavior, they do not affect the discrete-time difference equation.

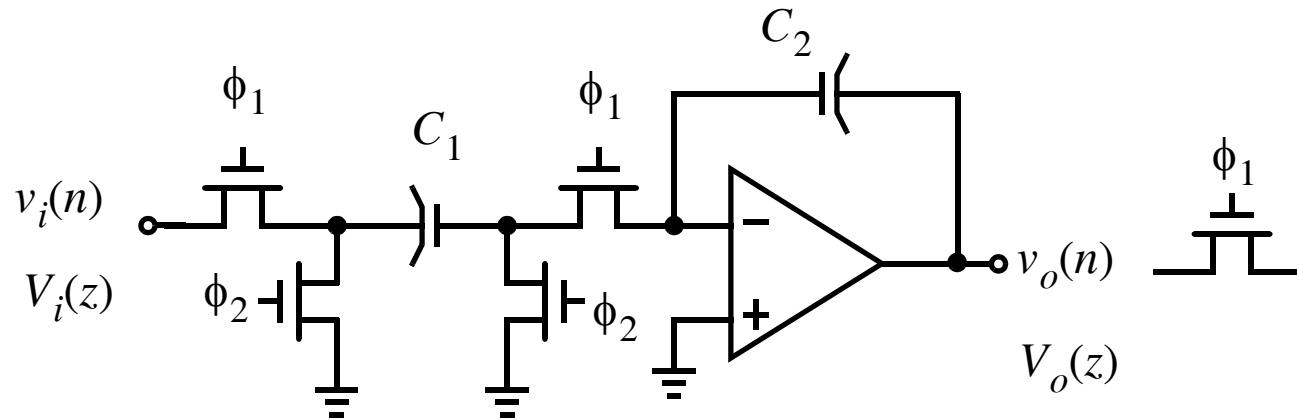Parasitic-Insensitive Inverting Integrator



- The charge on C_2 does not change when ϕ_2 turns on

$$C_2 v_{co}(nT - T/2) = C_2 v_{co}(nT - T) \quad (18)$$



$$C_2 v_{co}(nT) = C_2 v_{co}(nT - T/2) - C_1 v_{ci}(nT) \quad (19)$$

- Present output depends on present input (**delay-free**)


$$H(z) \equiv \frac{V_o(z)}{V_i(z)} = -\left(\frac{C_1}{C_2}\right) \frac{z}{z-1} \quad (20)$$

- Delay-free integrator has negative gain while delaying integrator has positive gain.

Signal-Flow-Graph Analysis

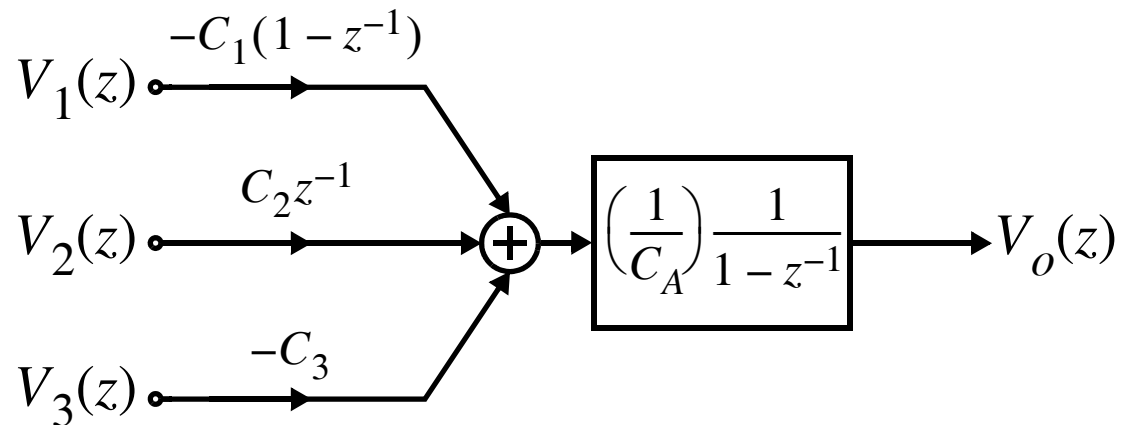
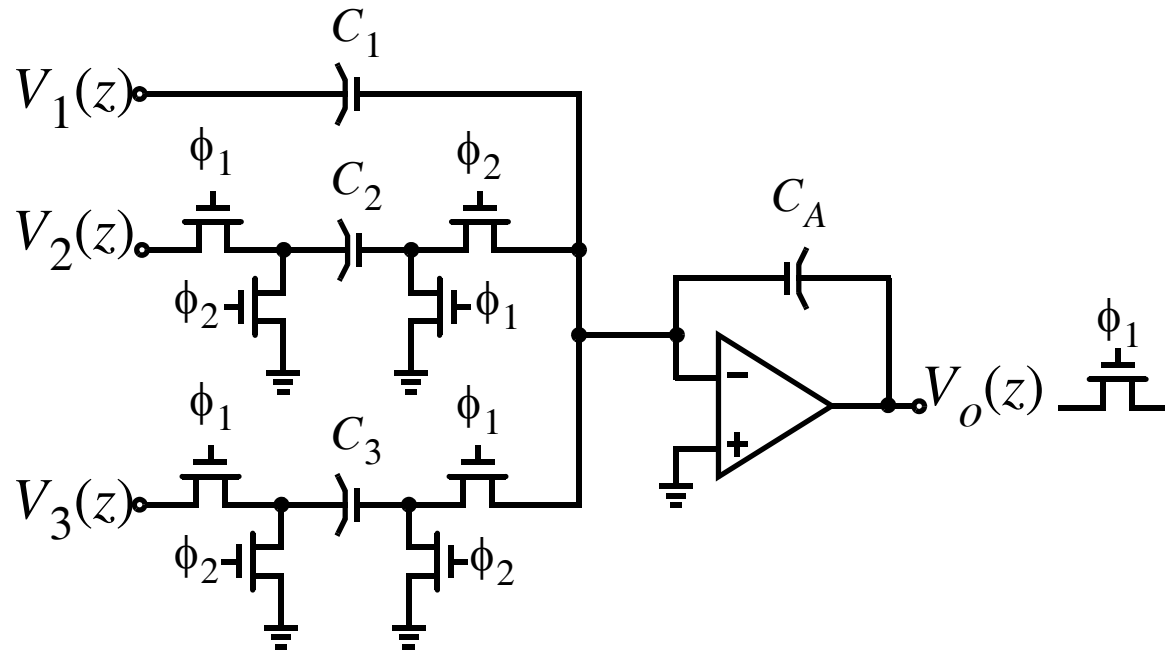


First-Order Filter

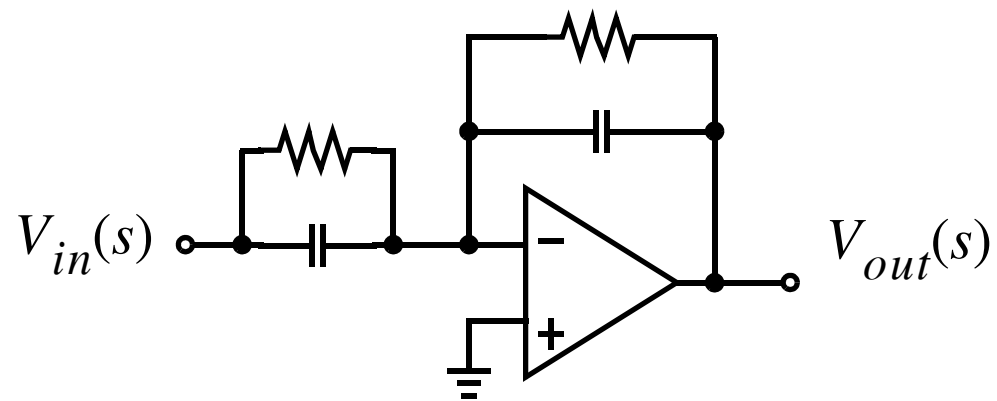

- Start with an active-RC structure and replace resistors with SC equivalents.
- Analyze using discrete-time analysis.

First-Order Filter

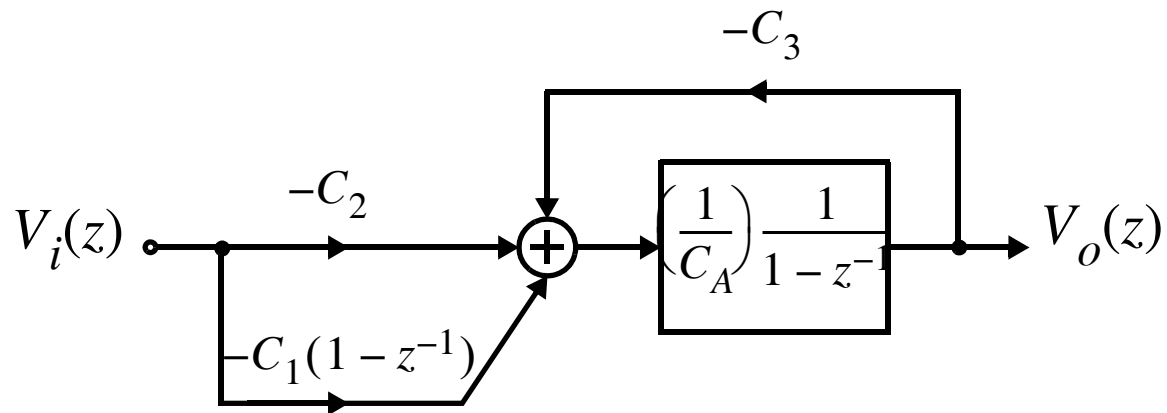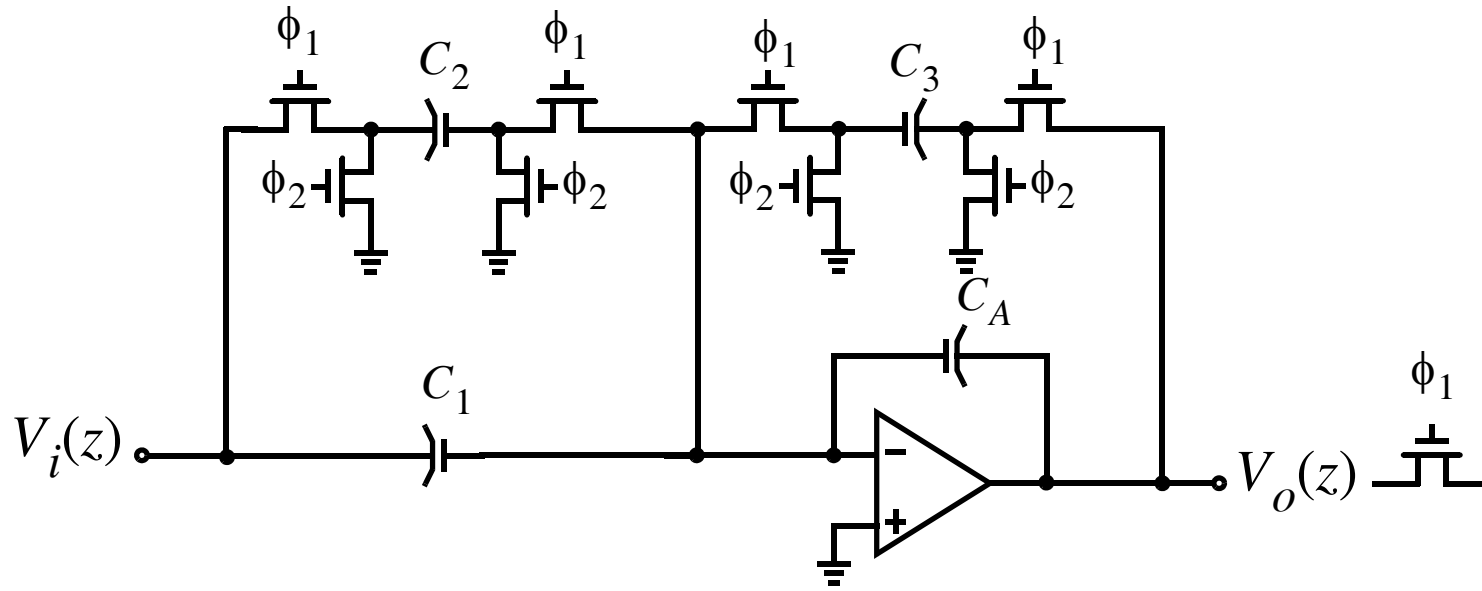

First-Order Filter

$$C_A(1 - z^{-1})V_o(z) = -C_3V_o(z) - C_2V_i(z) - C_1(1 - z^{-1})V_i(z) \quad (21)$$

$$H(z) \equiv \frac{V_o(z)}{V_i(z)} = \frac{\left(\frac{C_1}{C_A}\right)(1 - z^{-1}) + \left(\frac{C_2}{C_A}\right)}{1 - z^{-1} + \frac{C_3}{C_A}} \quad (22)$$
$$= \frac{\left(\frac{C_1 + C_2}{C_A}\right)z - \frac{C_1}{C_A}}{\left(1 + \frac{C_3}{C_A}\right)z - 1}$$

First-Order Filter

- The pole of (22) is found by equating the denominator to zero

$$z_p = \frac{C_A}{C_A + C_3} \quad (23)$$

- For positive capacitance values, this pole is restricted to the real axis between 0 and 1
— circuit is always stable.
- The zero of (22) is given by

$$z_z = \frac{C_1}{C_1 + C_2} \quad (24)$$

- Also restricted to real axis between 0 and 1.

First-Order Filter

- The dc gain is found by setting $z = 1$ which results in

$$H(1) = \frac{-C_2}{C_3} \quad (25)$$

- Note that in a fully-differential implementation, effective negative capacitances for C_1 , C_2 and C_3 can be achieved by simply interchanging the input wires.
- In this way, a zero at $z = -1$ could be realized by setting

$$C_1 = -0.5C_2 \quad (26)$$

First-Order Example

- Find the capacitance values needed for a first-order SC-circuit such that its 3dB point is at $10kHz$ when a clock frequency of $100kHz$ is used.
- It is also desired that the filter have zero gain at $50kHz$ (i.e. $z = -1$) and the dc gain be unity.
- Assume $C_A = 10pF$.

Solution

- Making use of the bilinear transform $s = (z - 1)/(z + 1)$ the zero at -1 is mapped to $\Omega = \infty$.
- The frequency warping maps the -3dB frequency of $10kHz$ (or 0.2π rad/sample) to

First-Order Example

$$\Omega = \tan\left(\frac{0.2\pi}{2}\right) = 0.3249 \quad (27)$$

- in the continuous-time domain leading to the continuous-time pole, s_p , required being

$$s_p = -0.3249 \quad (28)$$

- This pole is mapped back to z_p given by

$$z_p = \frac{1 + s_p}{1 - s_p} = 0.5095 \quad (29)$$

- Therefore, $H(z)$ is given by

$$H(z) = \frac{k(z + 1)}{z - 0.5095} \quad (30)$$

First-Order Example

- where k is determined by setting the dc gain to one (i.e. $H(1) = 1$) resulting

$$H(z) = \frac{0.24525(z + 1)}{z - 0.5095} \quad (31)$$

- or equivalently,

$$H(z) = \frac{0.4814z + 0.4814}{1.9627z - 1} \quad (32)$$


- Equating these coefficients with those of (22) (and assuming $C_A = 10pF$) results in

$$C_1 = 4.814pF \quad (33)$$

$$C_2 = -9.628pF \quad (34)$$

$$C_3 = 9.628pF \quad (35)$$


Switch Sharing

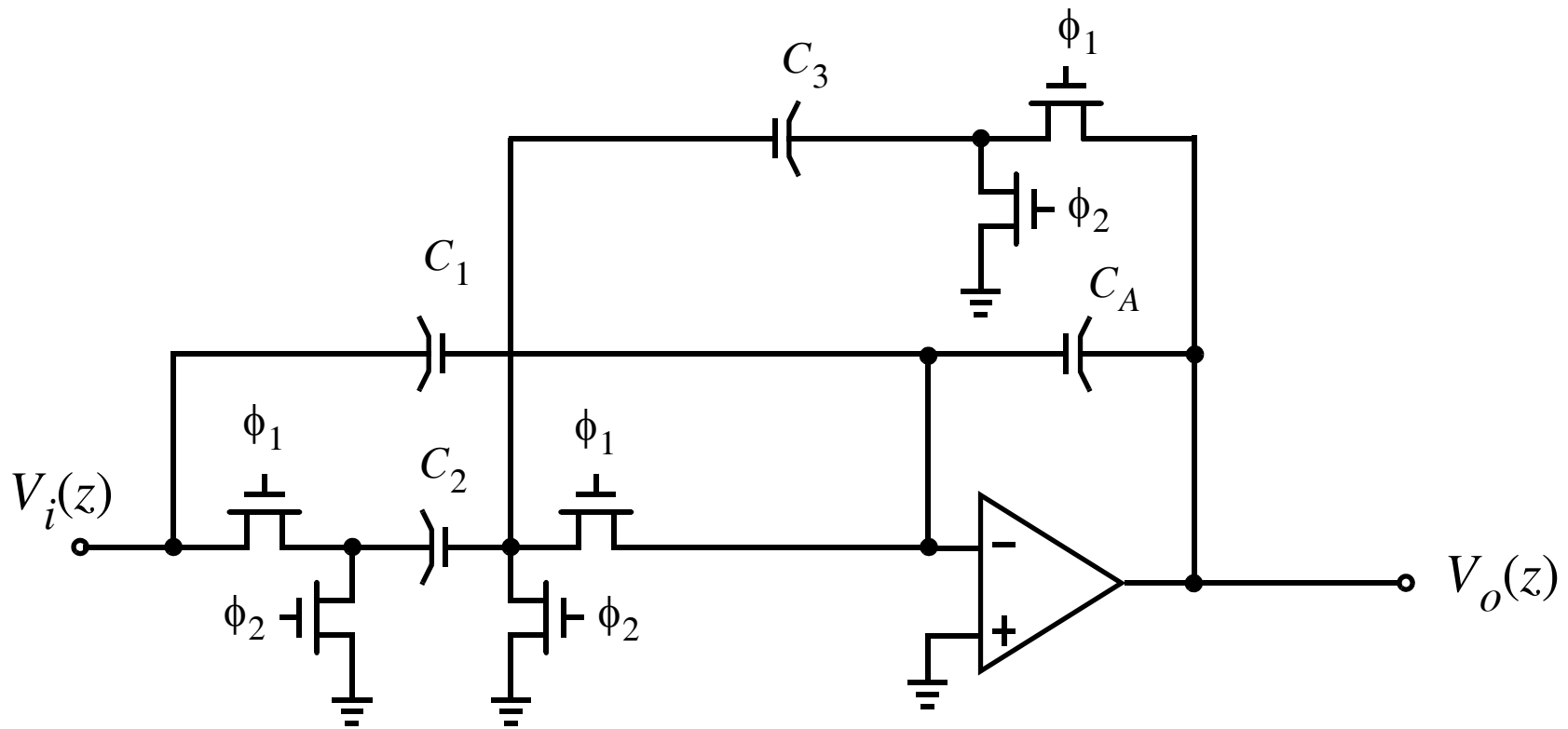


- Share switches that are always connected to the same potentials.

Fully Differential Filters

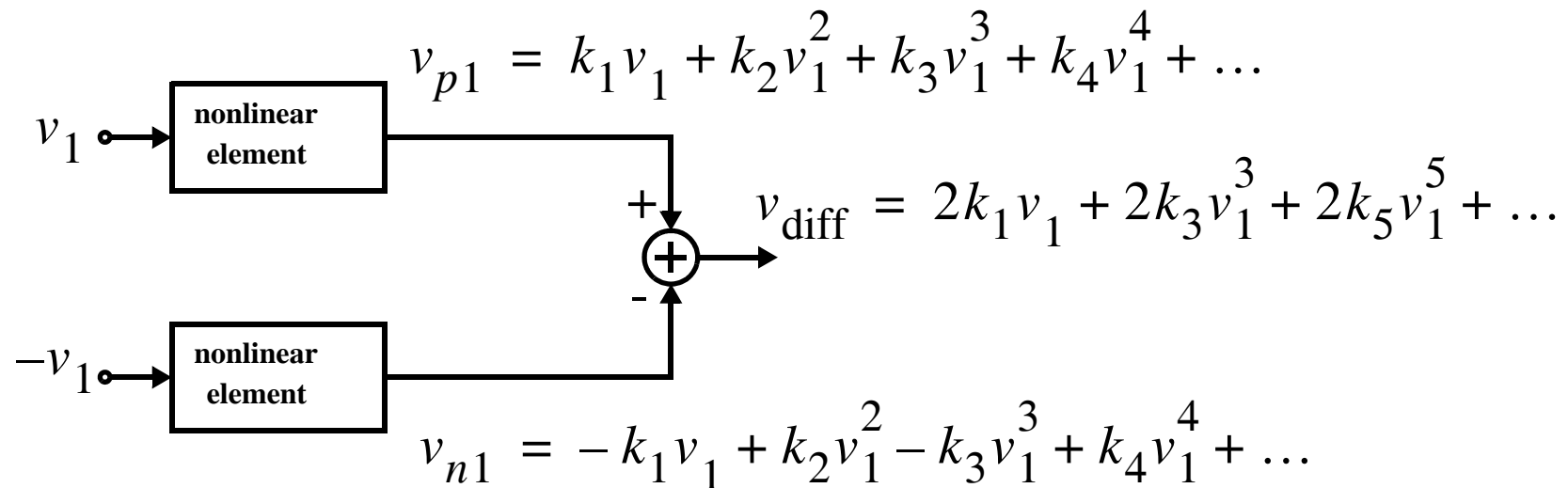- Most modern SC filters are fully differential
- Common-mode noise is rejected.
- Even order distortion terms cancel




Fully Differential Filters

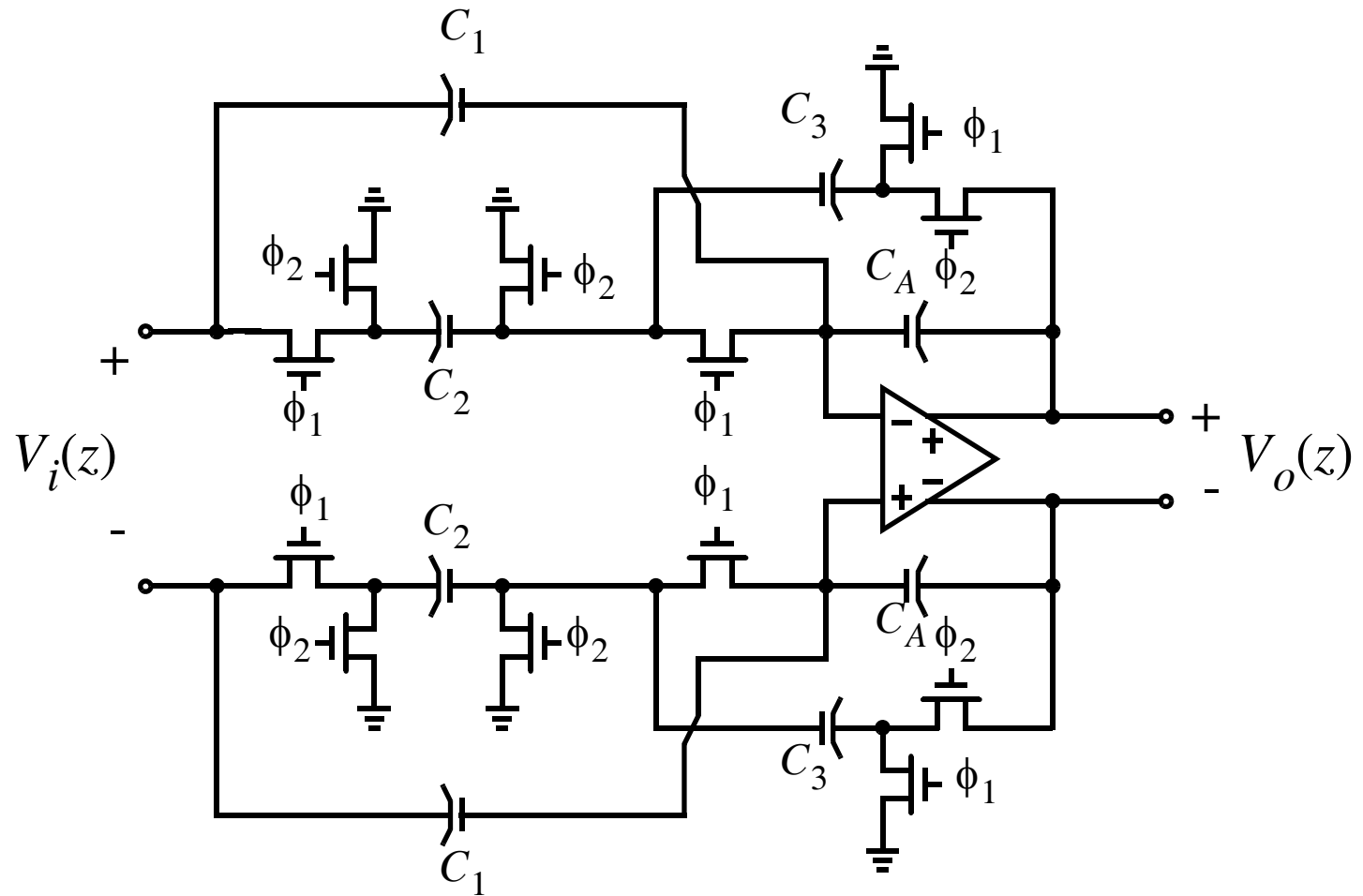

Fully Differential Filters

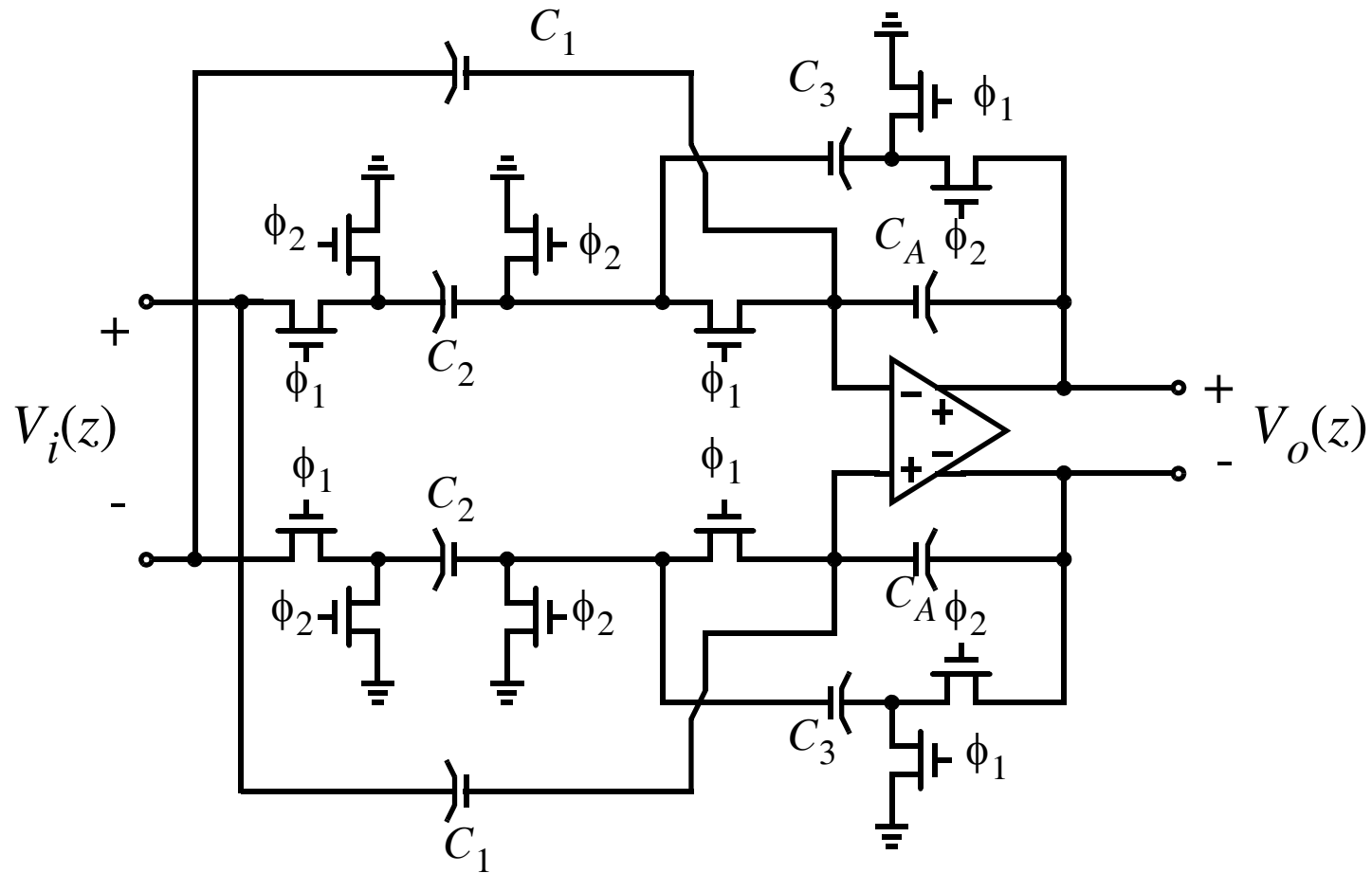- Switching the input connection to C_1
 — equivalent to a negative C_1




Fully Differential Filters

- Note that fully differential version is essentially two copies of single-ended version (area penalty).
- Only one opamp needed (though common-mode circuit also needed)
- Input and output signal swings have been doubled so that same dynamic range can be achieved with half capacitor sizes (from kT/C analysis)
- Switches can be reduced in size since small caps used.
- Although there is more wiring in fully differential version it has better noise and distortion performance.

Charge Injection

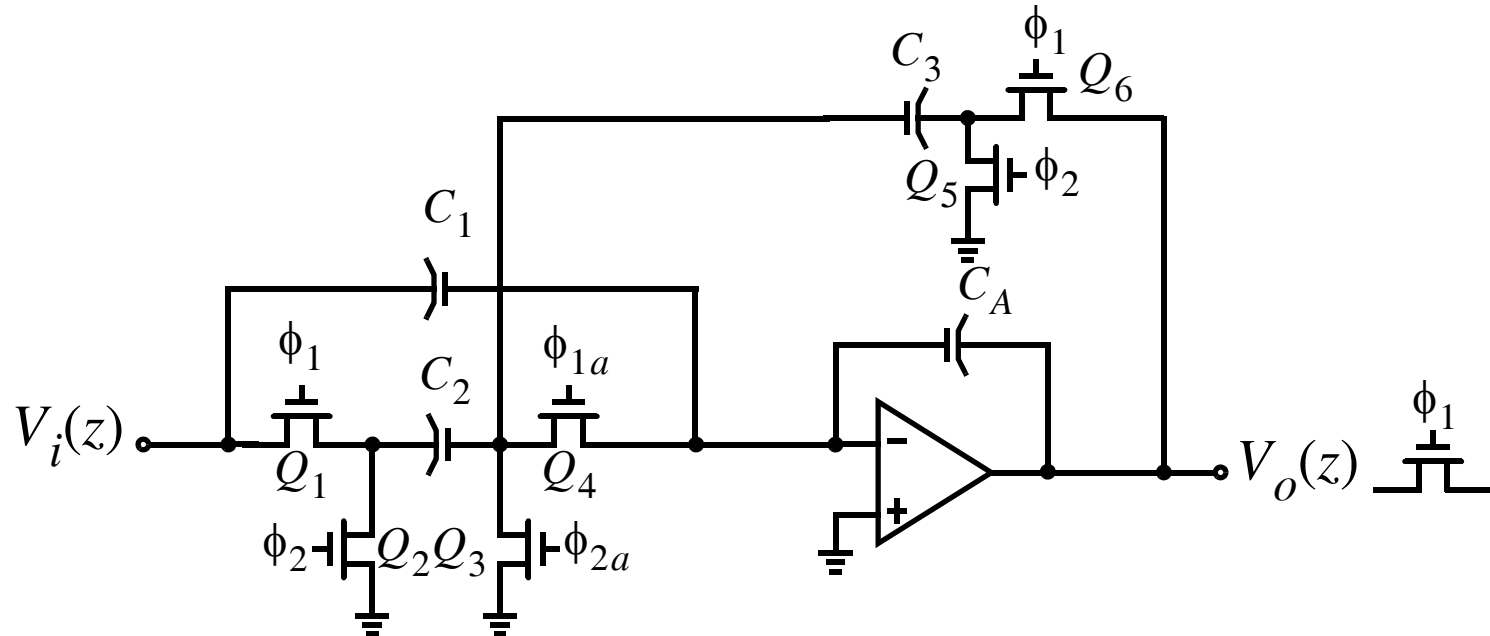- To reduce charge injection (thereby improving distortion), turn off certain switches first.



- Advance ϕ_{1a} and ϕ_{2a} so that only their charge injection affect circuit (result is a dc offset)

Charge Injection

- Note: ϕ_{2a} connected to ground while ϕ_{1a} connected to virtual ground, therefore ...
 - can use single n-channel transistors
 - charge injection NOT signal dependent

$$Q_{CH} = -WLC_{ox}V_{eff} = -WLC_{ox}(V_{GS} - V_t) \quad (36)$$

- Charge related to V_{GS} and V_t and V_t related to substrate-source voltage.
- Source of Q_3 and Q_4 remains at ground — amount of charge injected by Q_3, Q_4 is not signal dependent and can be considered as a dc offset.

Charge Injection Example

- Estimate dc offset due to channel-charge injection when $C_1 = 0$ and $C_2 = C_A = 10C_3 = 10pF$.
- Assume switches Q_3, Q_4 have $V_{tn} = 0.8V$, $W = 30\mu m$, $L = 0.8\mu m$, $C_{ox} = 1.9 \times 10^{-3} pF/\mu m^2$, and power supplies are $\pm 2.5V$.
- Channel-charge of Q_3, Q_4 (when on) is

$$\begin{aligned} Q_{CH3} = Q_{CH4} &= -(30)(0.8)(0.0019)(2.5 - 0.8) & (37) \\ &= -77.5 \times 10^{-3} pC \end{aligned}$$

- dc feedback keeps virtual opamp input at zero volts.

Charge Injection Example

- Charge transfer into C_3 given by

$$Q_{C_3} = -C_3 v_{out} \quad (38)$$

- We estimate half channel-charges of Q_3 , Q_4 are injected to the virtual ground leading to



$$\frac{1}{2}(Q_{CH3} + Q_{CH4}) = Q_{C_3} \quad (39)$$

which leads to



$$v_{out} = \frac{77.5 \times 10^{-3} \text{ pC}}{1 \text{ pF}} = 78 \text{ mV} \quad (40)$$

- dc offset affected by the capacitor sizes, switch sizes and power supply voltage.

SC Gain Circuits — Parallel RC

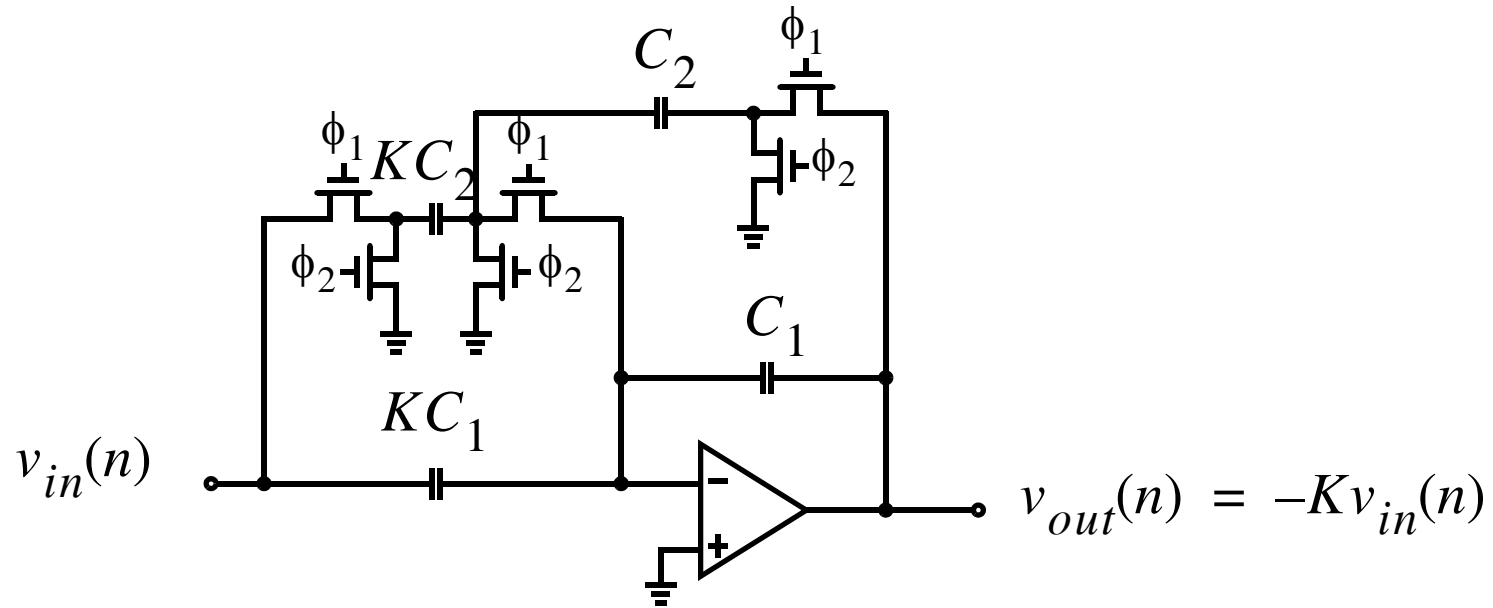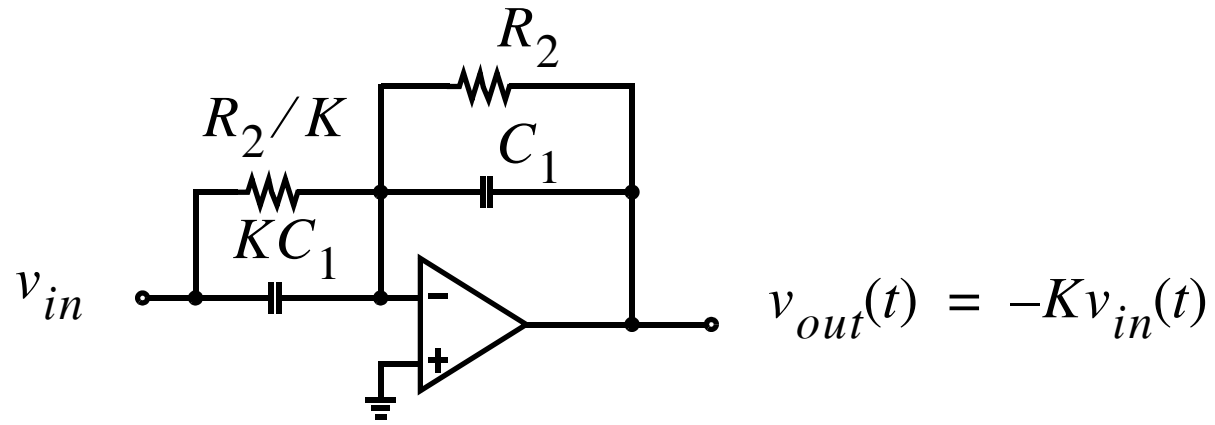

SC Gain Circuits — Resettable Gain

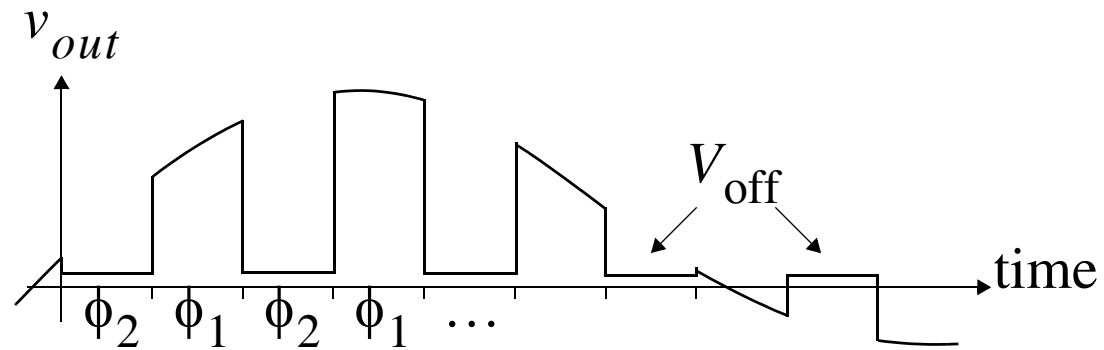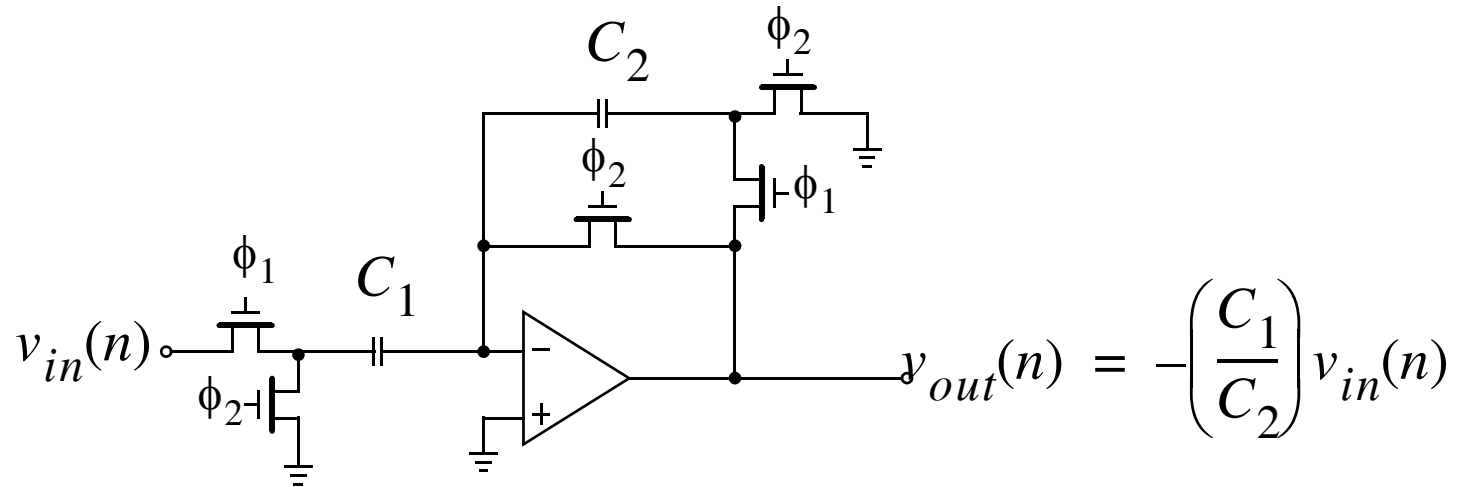



SC Gain Circuits

Parallel RC Gain Circuit

- circuit amplifies 1/f noise as well as opamp offset voltage

Resettable Gain Circuit

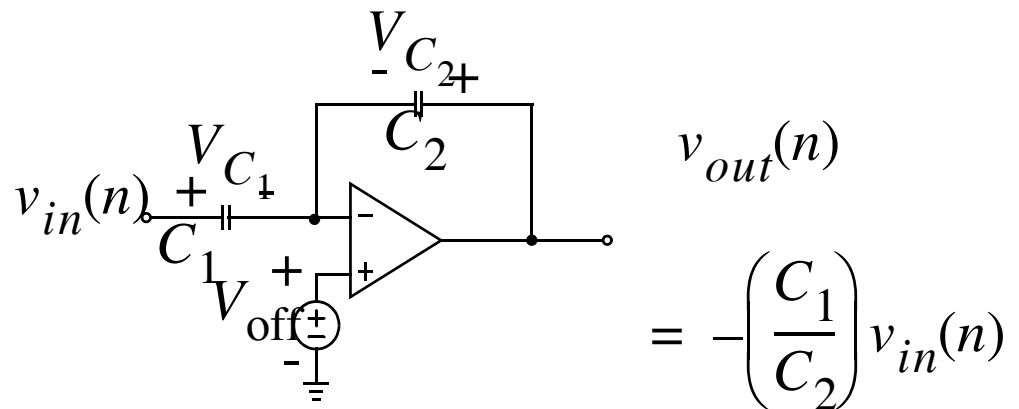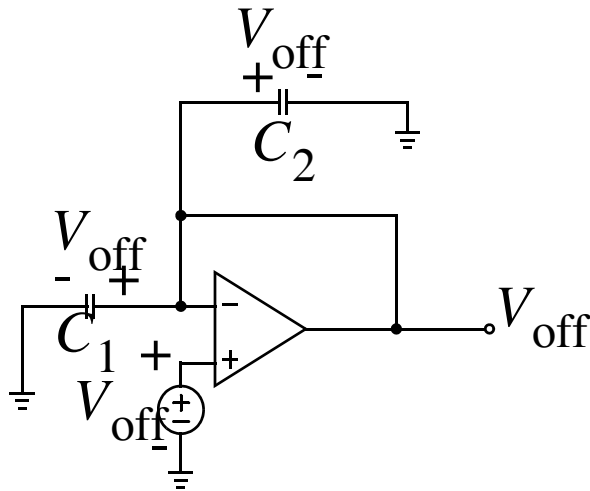
- performs offset cancellation
- also highpass filters 1/f noise of opamp
- However, requires a high slew-rate from opamp



$$v_{out}(n) = -\left(\frac{C_1}{C_2}\right)v_{in}(n)$$



SC Gain Circuits — Capacitive-Reset

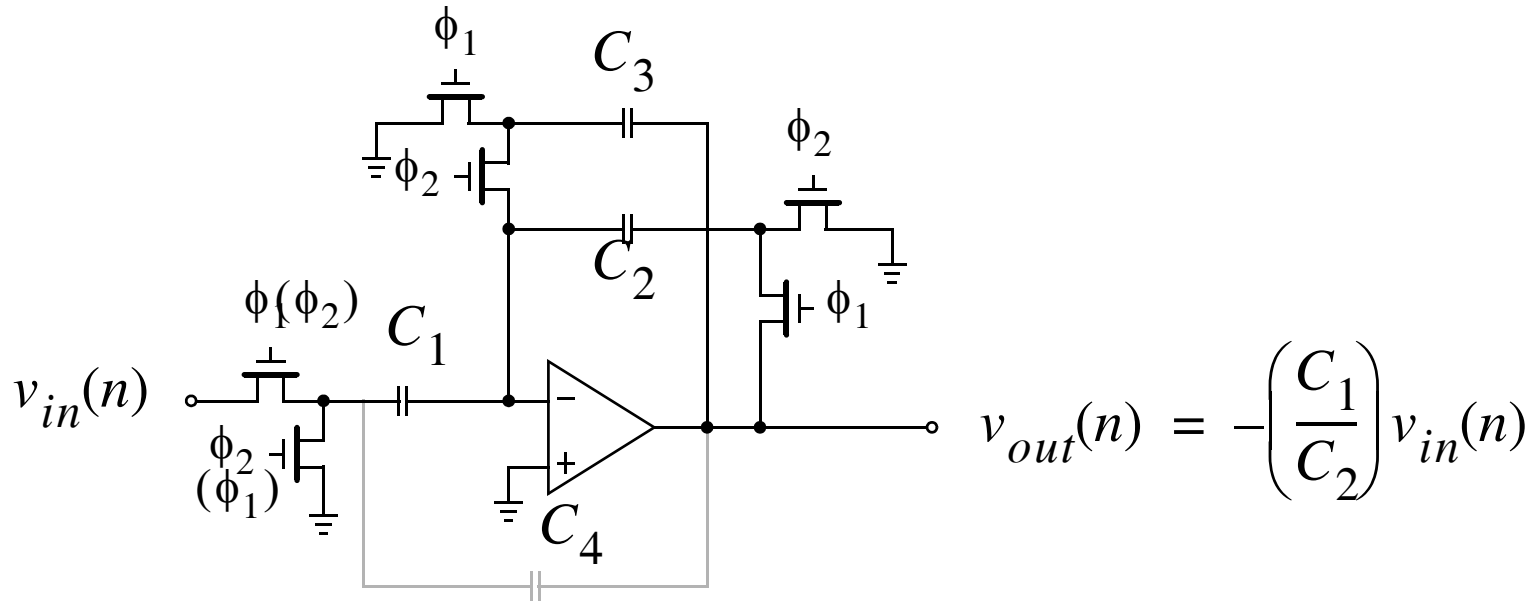- Eliminate slew problem and still cancel offset by coupling opamp's output to inverting input




- C_4 is optional de-glitching capacitor

SC Gain Circuits — Capacitive-Reset

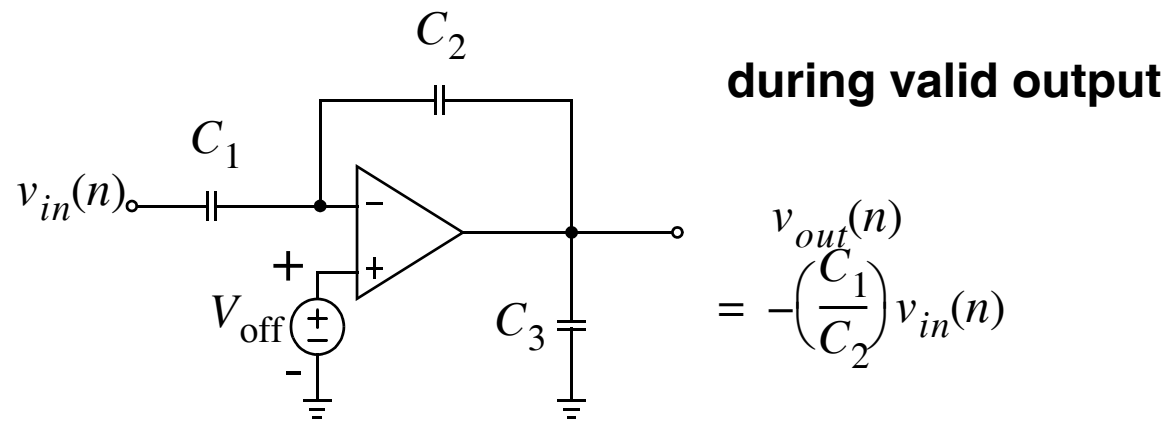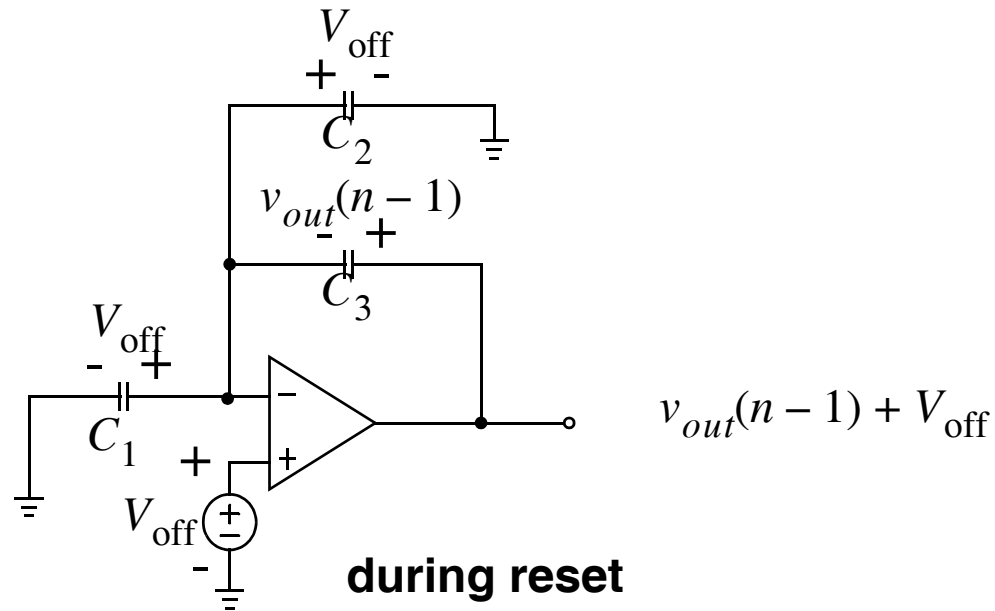

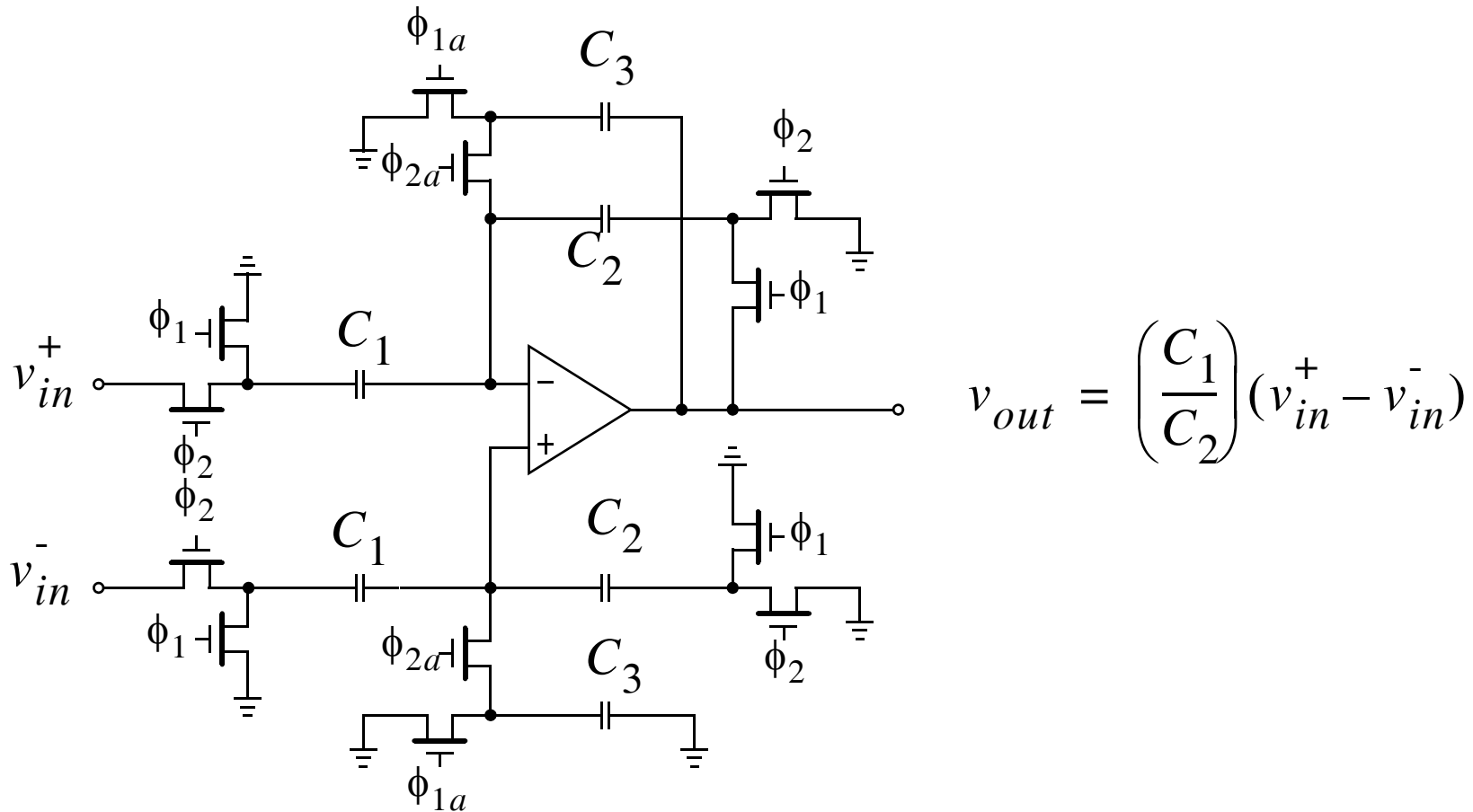SC Gain Circuits — Differential Cap-Reset




- Accepts differential inputs and partially cancels switch clock-feedthrough

Correlated Double-Sampling (CDS)


- Preceding SC gain amp is an example of CDS
- Minimizes errors due to opamp offset and $1/f$ noise
- When CDS used, opamps should have low thermal noise (often use n-channel input transistors)
- Often use CDS in only a few stages
 - input stage for oversampling converter
 - some stages in a filter (where low-freq gain high)
- Basic approach:
 - Calibration phase: store input offset voltage
 - Operation phase: error subtracted from signal

Better High-Freq CDS Amplifier

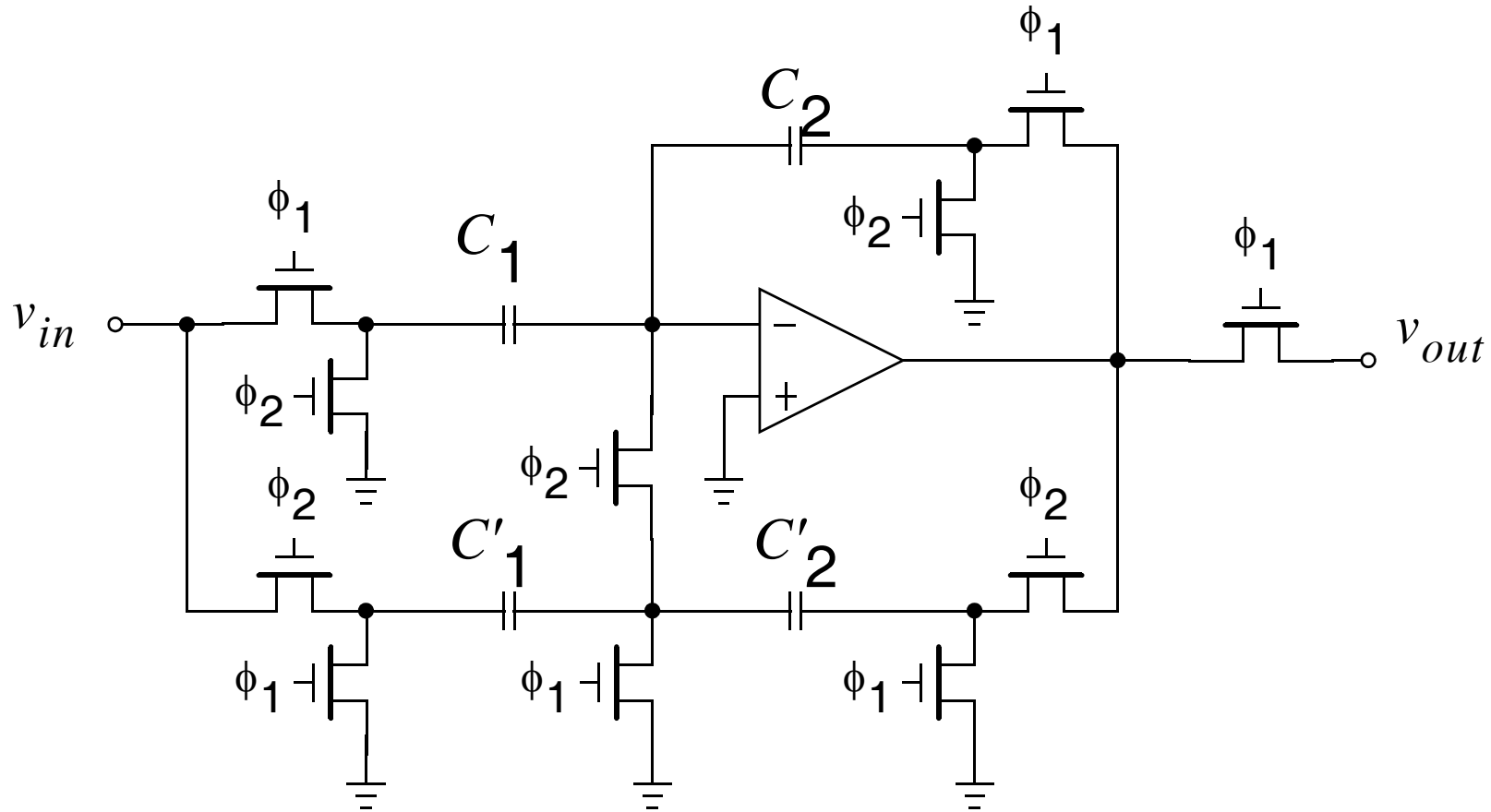

- ϕ_2 — C_1', C_2' used but include errors
- ϕ_1 — C_1, C_2 used but here no offset errors


CDS Integrator

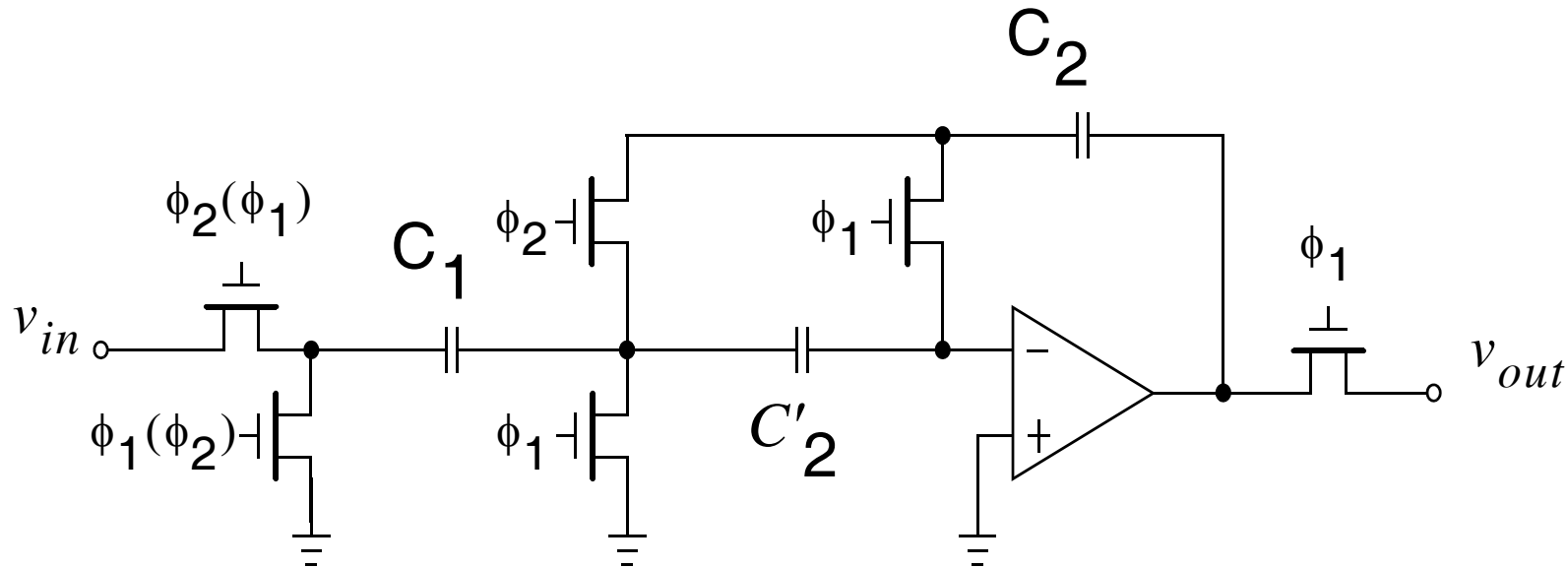

- ϕ_1 — sample opamp offset on C_2'
- ϕ_2 — C_2' placed in series with opamp to reduce error
- Offset errors reduced by opamp gain
- Can also apply this technique to gain amps


SC Amplitude Modulator

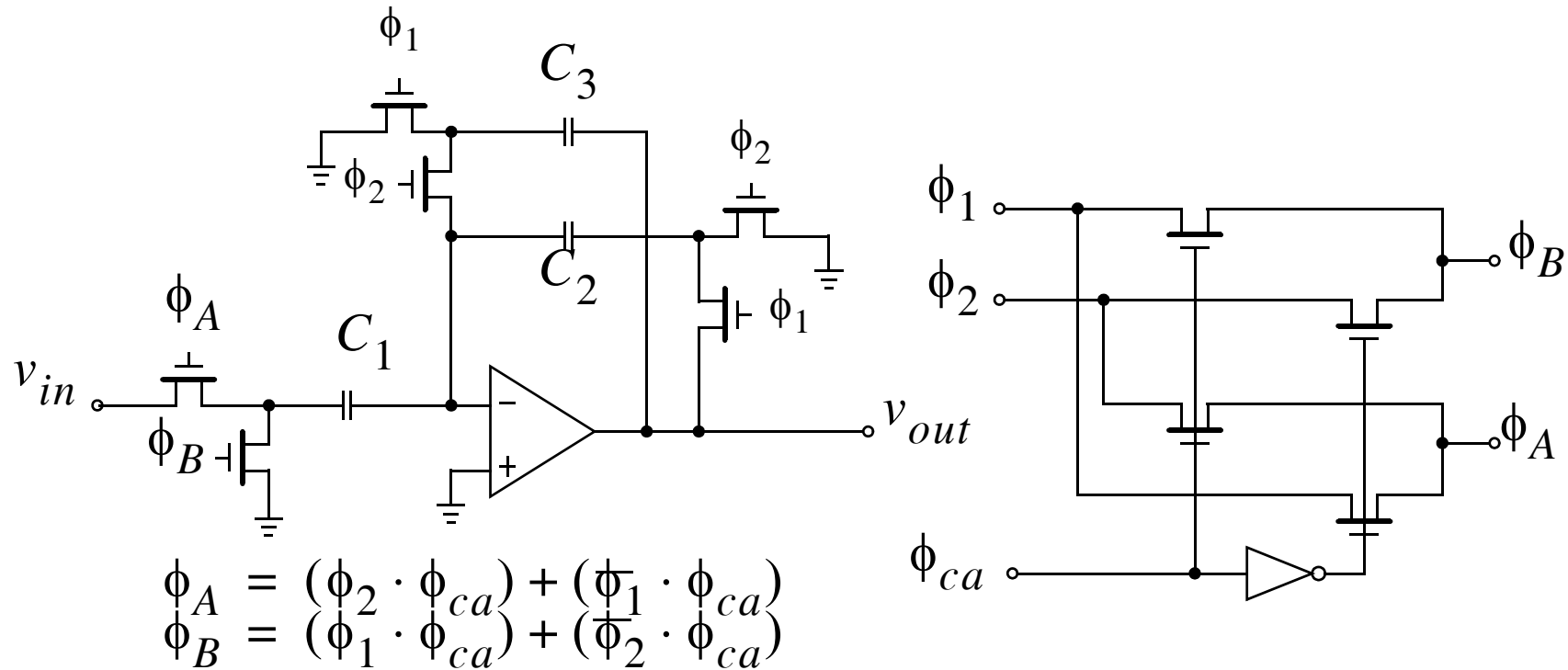- Square wave modulate by ± 1 (i.e. $V_{out} = \pm V_{in}$)





- Makes use of cap-reset gain circuit.
- ϕ_{ca} is the modulating signal

SC Full-Wave Rectifier

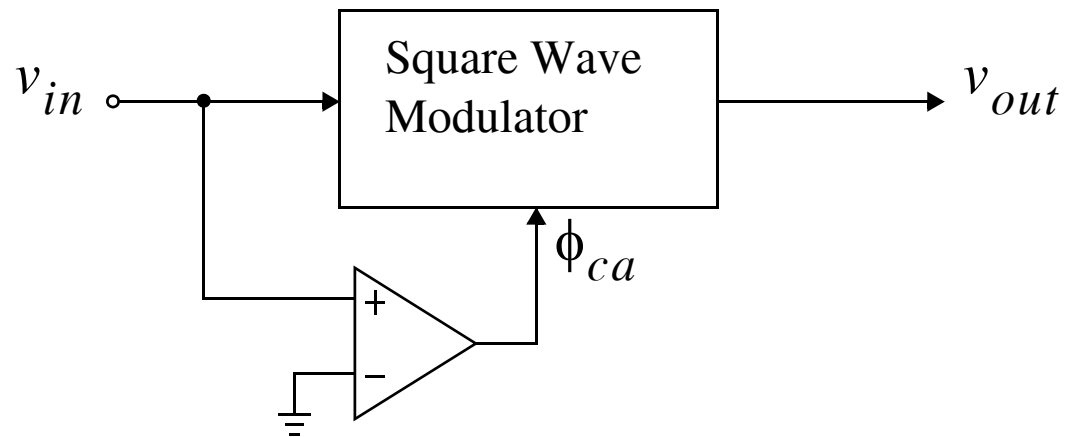

- Use square wave modulator and comparator to make
- For proper operation, comparator output should changes synchronously with the sampling instances.

SC Peak Detector

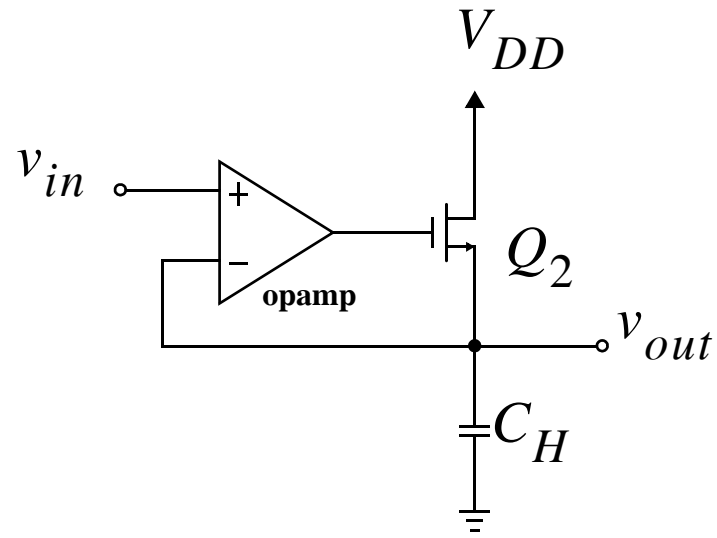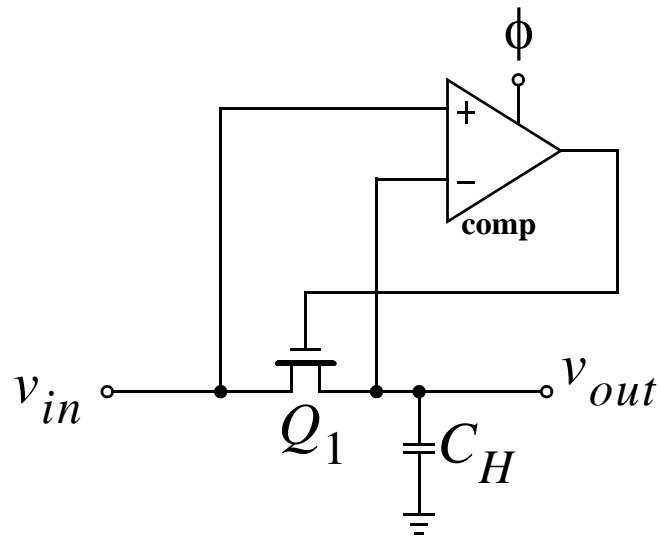

- Left circuit can be fast but less accurate
- Right circuit is more accurate due to feedback but slower due to need for compensation (circuit might also slew so opamp's output should be clamped)