


Nyquist-Rate D/A Converters

**Reference: Chapter 12 of the text
“Analog Integrated Circuit Design”
by
David Johns and Ken Martin**

Chapter 16 of the 2nd Edition of the text by Tony Chan Carusone, David Johns, and Ken Martin


The material of this presentation is courtesy of Dr. Ken Martin.

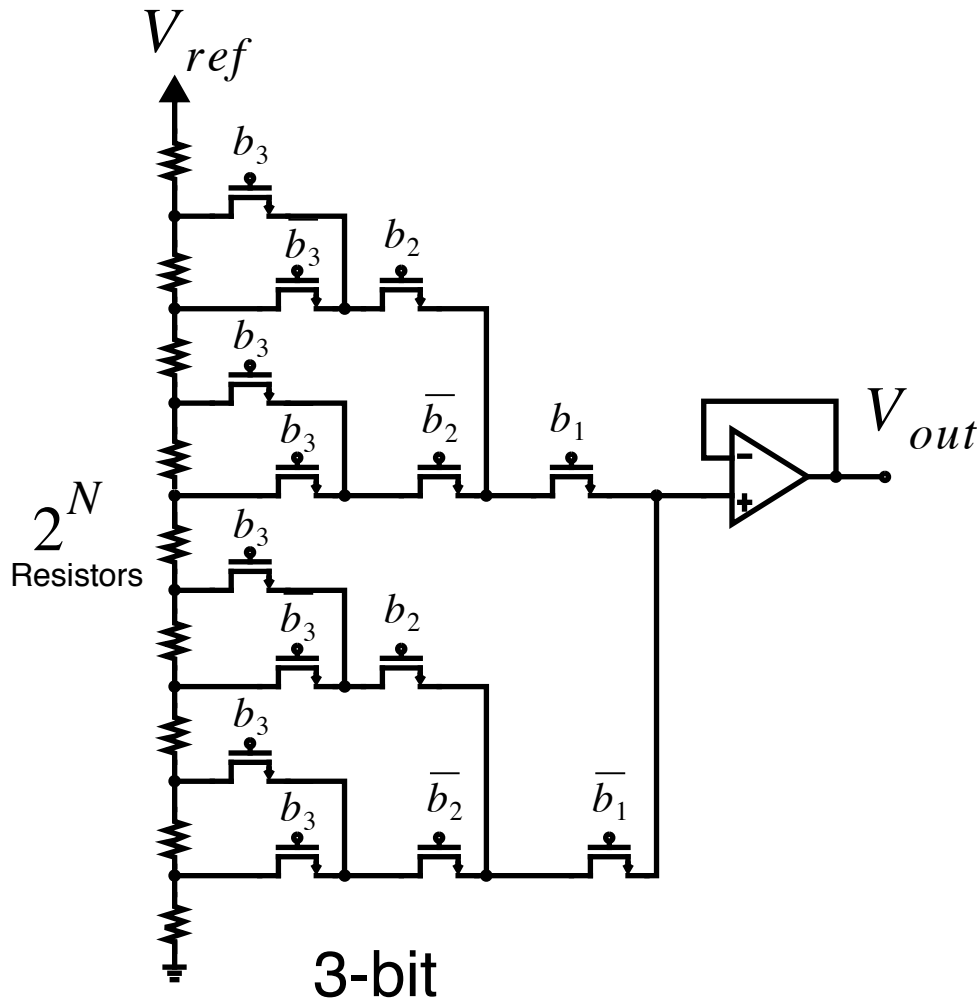Resistor-String D/A (Hamadé, JSSC, Dec. 1978)



- Guaranteed monotonic
- Integrated with better than 10-bit absolute accuracy.
- Delay through the switch network major speed limitation
- Resistors might be realized using polysilicon
- If n-channel only used, can be laid out small
- Requires 2^N resistors


D/A Resistor-String – Digital Decoding

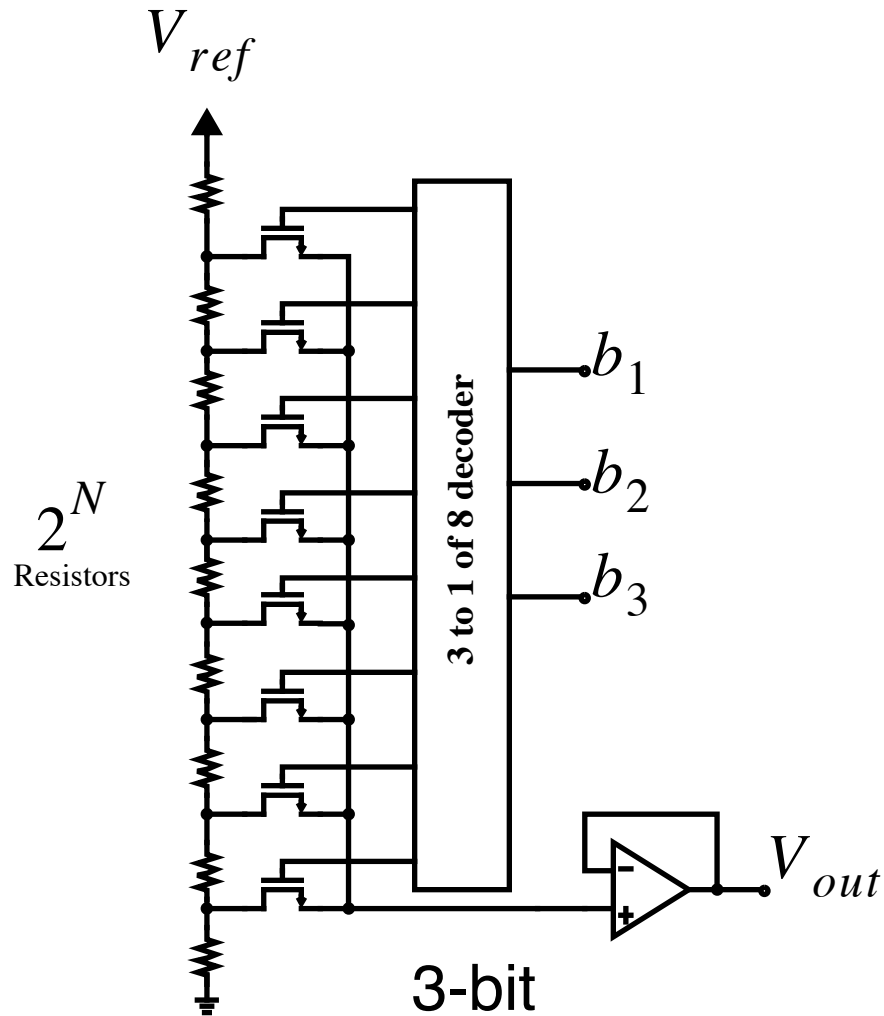

- Higher speed implementation (less resistance thru transistors)
- Large cap load on buffer input
- Requires 2^N resistors


Folded-resistor-string D/A

- (Abrial, JSSC, Dec. 1988)

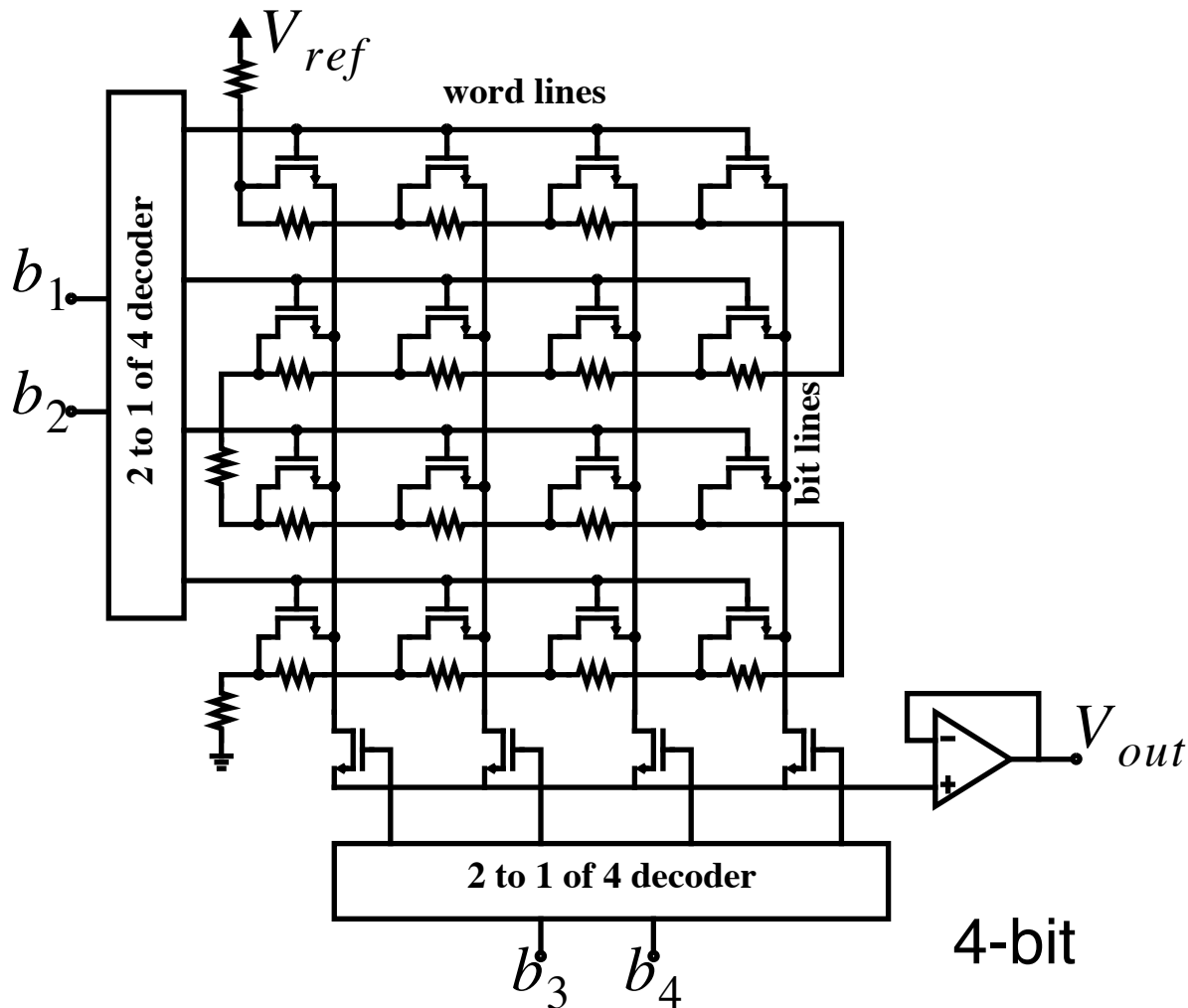

- Less capacitance load over the single bus approach
- Requires 2^N resistors


Binary-Weighted Resistor D/A's

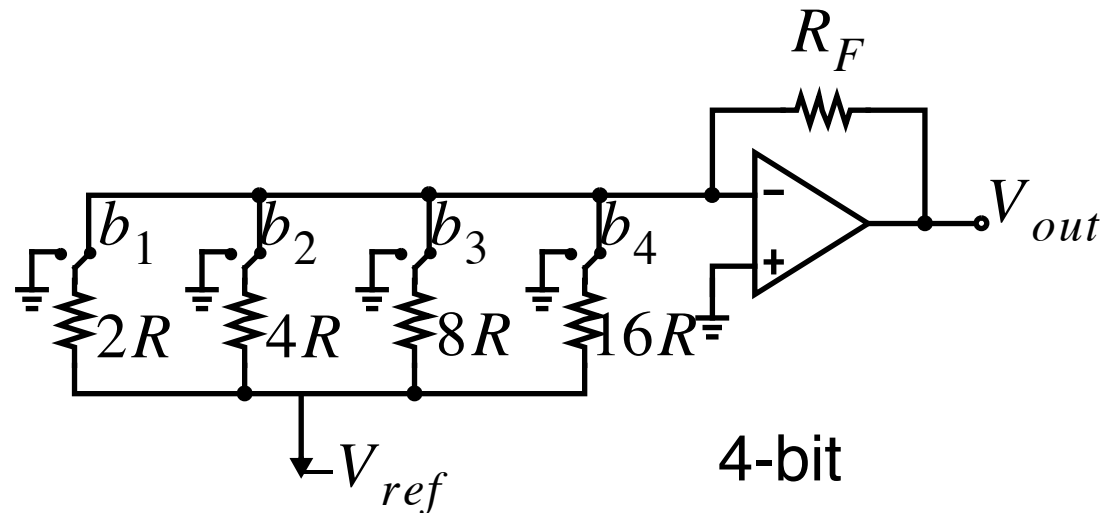

$$V_{out} = -R_F V_{ref} \left(-\frac{b_1}{2R} - \frac{b_2}{4R} - \frac{b_3}{8R} - \dots \right) \quad (1)$$


- Only N resistors
- Resistor and current ratios are on the order of 2^N
- Prone to glitches (more later).

Reduced Spread Binary Resistor D/A

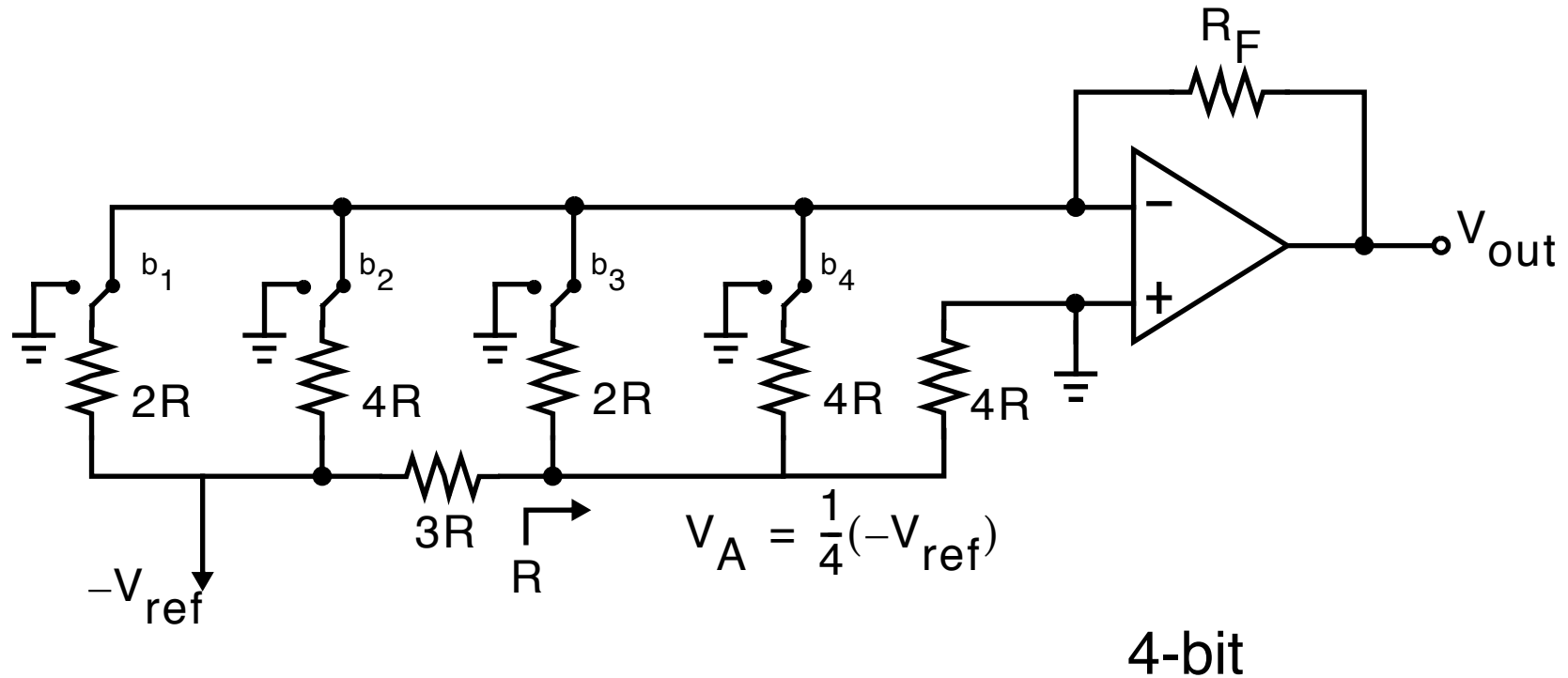

- Reduced resistor spread

R-2R Based D/A Converters

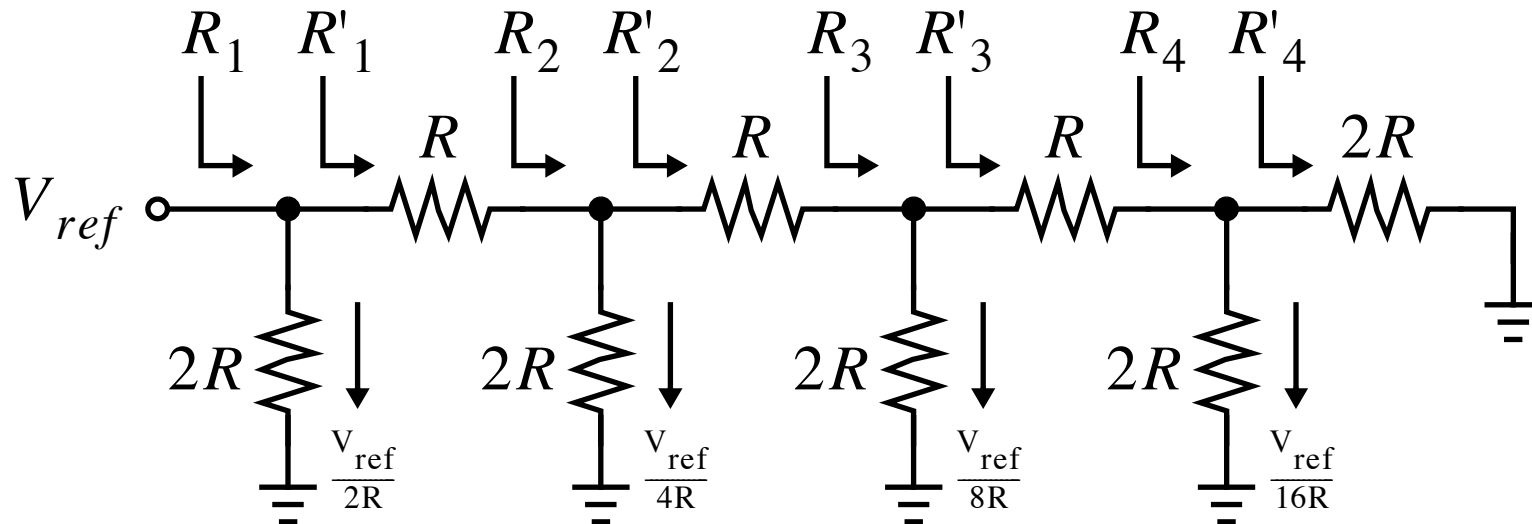


$$\begin{aligned}
 R'_4 &= 2R \\
 R_4 &= 2R \parallel 2R = R \\
 R'_3 &= R + R_4 = 2R \\
 R_3 &= 2R \parallel R'_3 = R
 \end{aligned}$$

(2)

- Small size, good matching (only R and 2R)

R-2R Based Resistor Ladders


- Example D/A converter

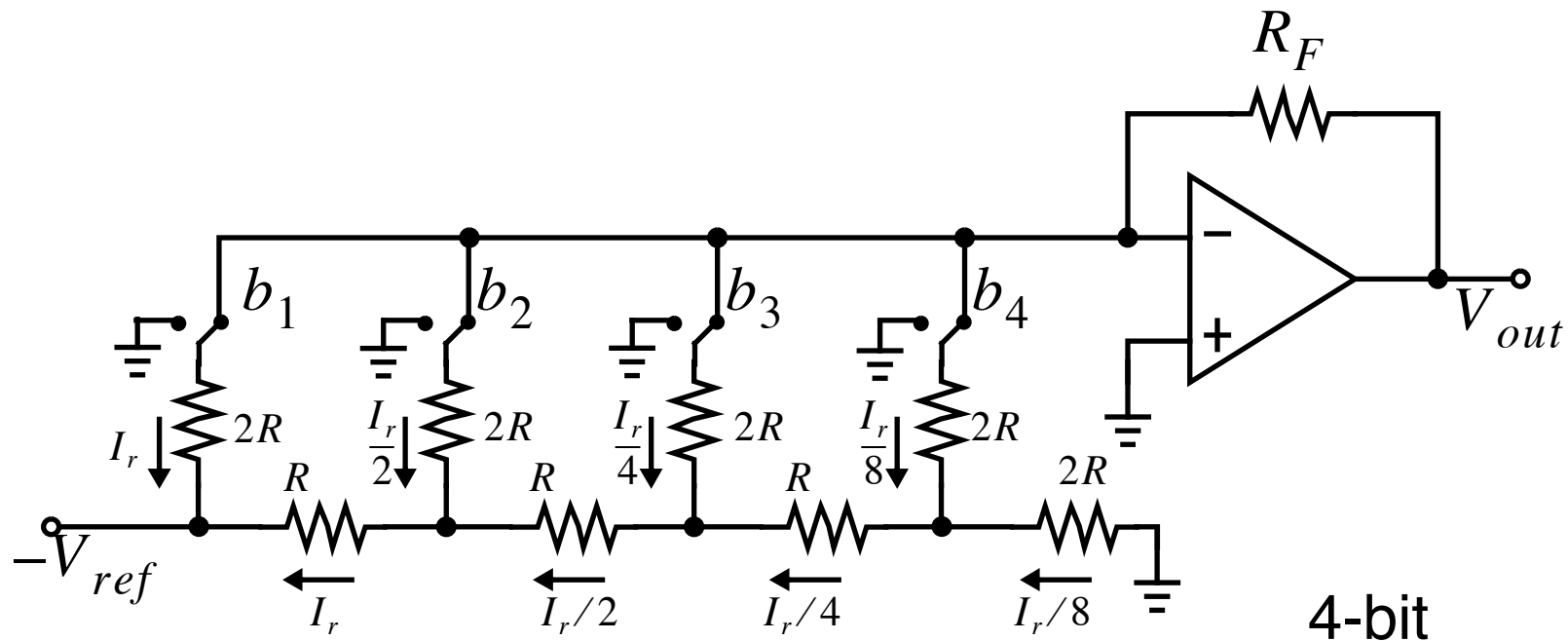

- Currents through the switches are scaled
- Should scale switch sizes for good accuracy
- No node voltage changes except for output \rightarrow fast

Glitches

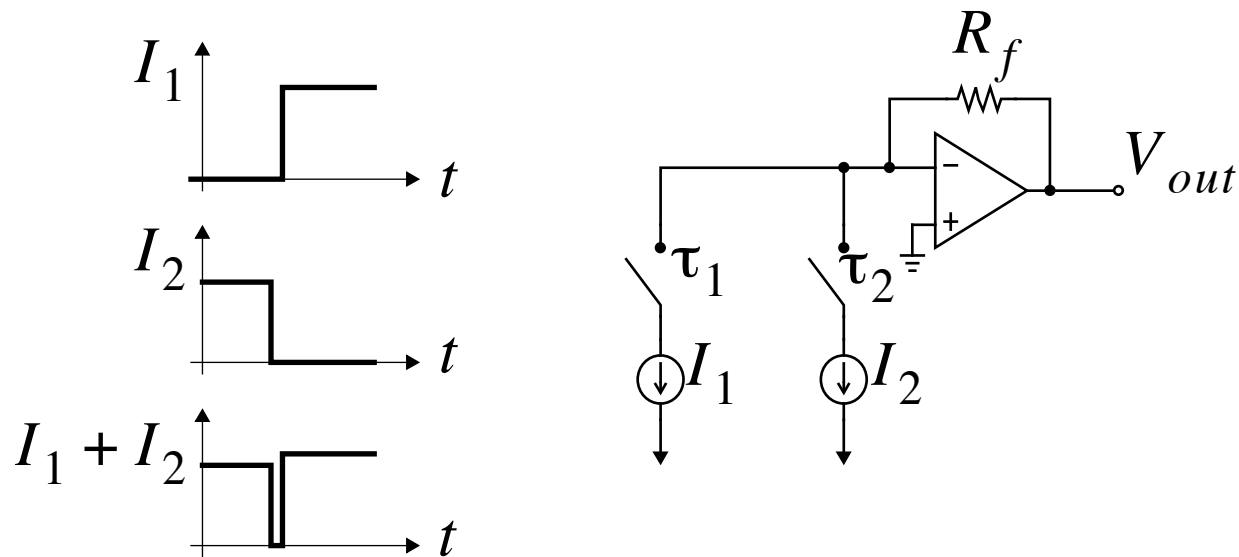
- Different delays for switching the different currents
- MSB change often worst case




- Glitches can be minimized by limiting the bandwidth but that slows down circuit
- Use thermometer code to reduce glitches

Thermometer D/A Converters

Decimal	Binary			Thermometer Code						
	b_1	b_2	b_3	d_1	d_2	d_3	d_4	d_5	d_6	d_7
0	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1
2	0	1	0	0	0	0	0	0	1	1
3	0	1	1	0	0	0	0	1	1	1
4	1	0	0	0	0	0	1	1	1	1
5	1	0	1	0	0	1	1	1	1	1
6	1	1	0	0	1	1	1	1	1	1
7	1	1	1	1	1	1	1	1	1	1


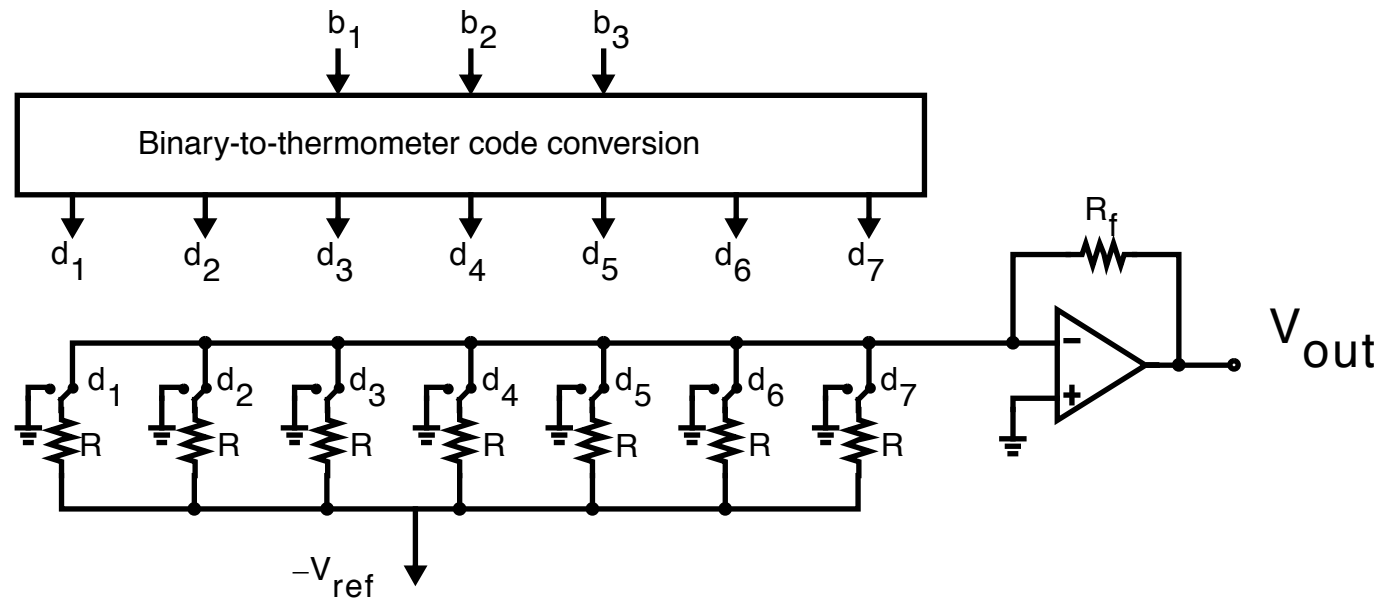


Thermometer Code D/A Converter

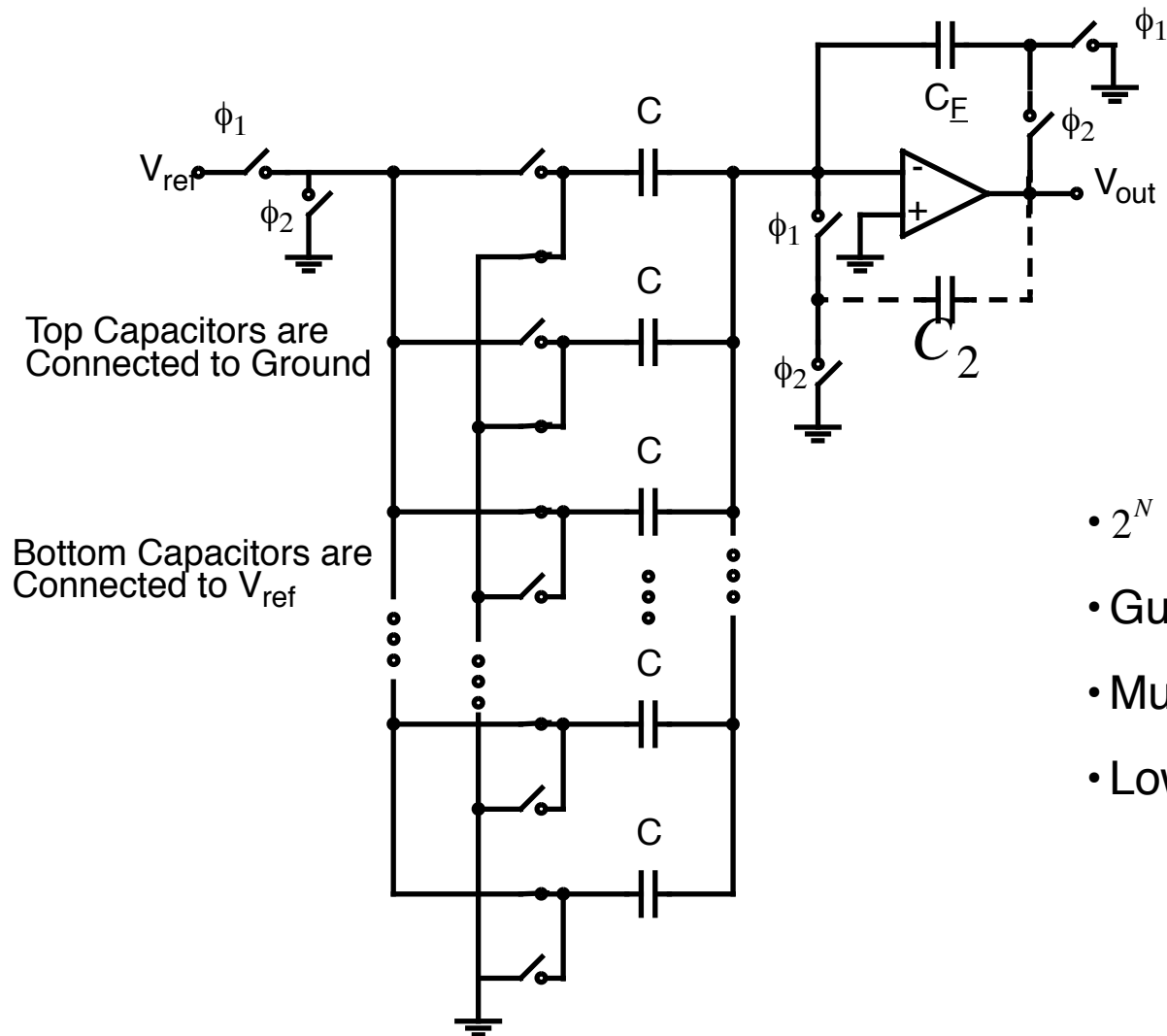

- 2^N unit sized caps
- Guaranteed monotonic
- Much lower glitching
- Low DNL


Current-Mode D/A's

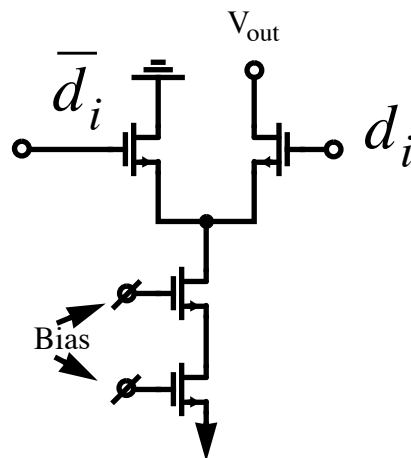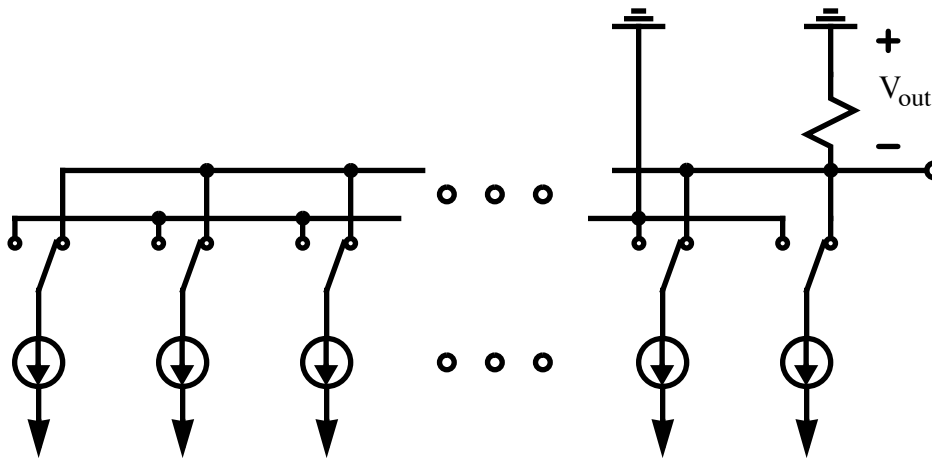

- Thermometer-code
- High-speed, output feeds directly to resistor


Current-Steered D/A [Colles, 88]

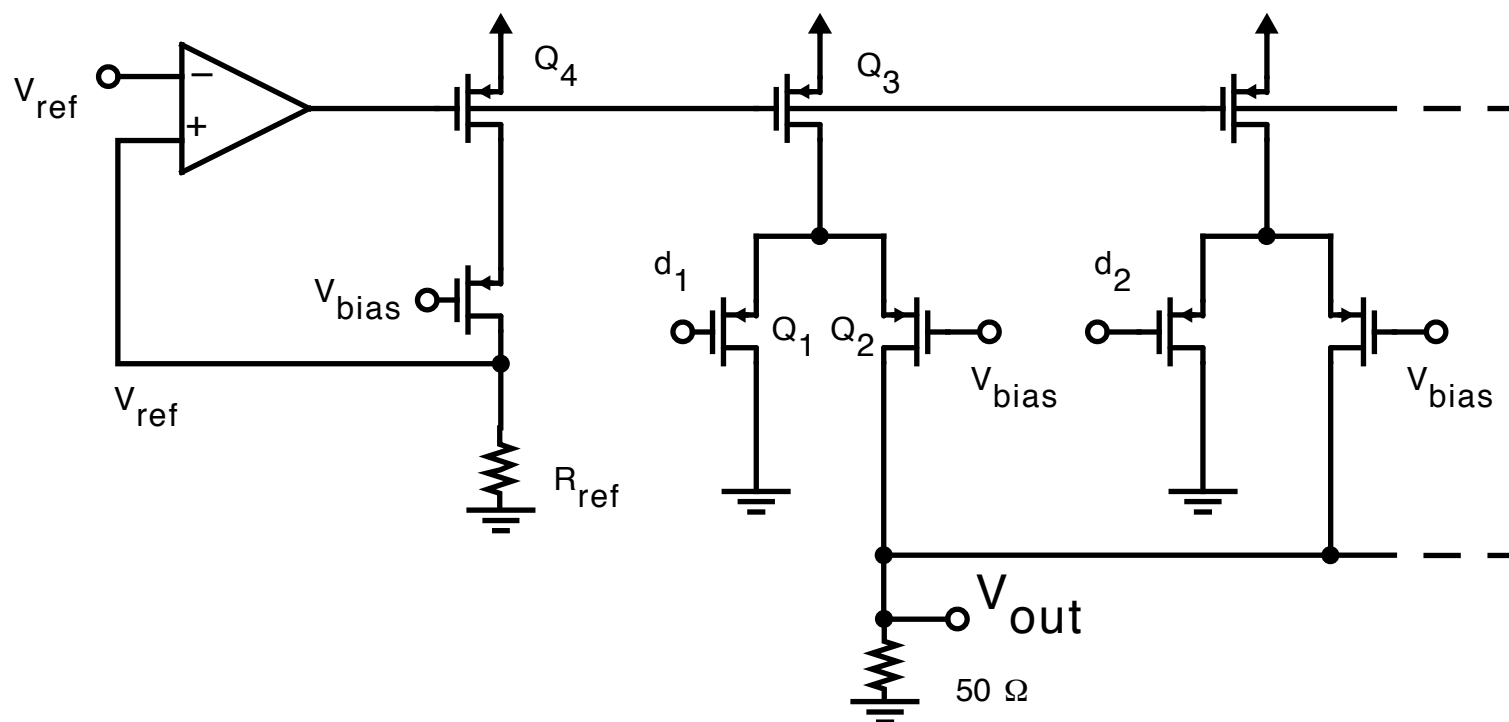- Operates as cascode current sources.
- Note that although opamp input connections appear to be reversed but they are correct
- For max speed, keep voltage swing at the common connections of the switches small (just turned off).



Segmented D/A


- Schoeff, 79; Saul, 85; Grebene, 84

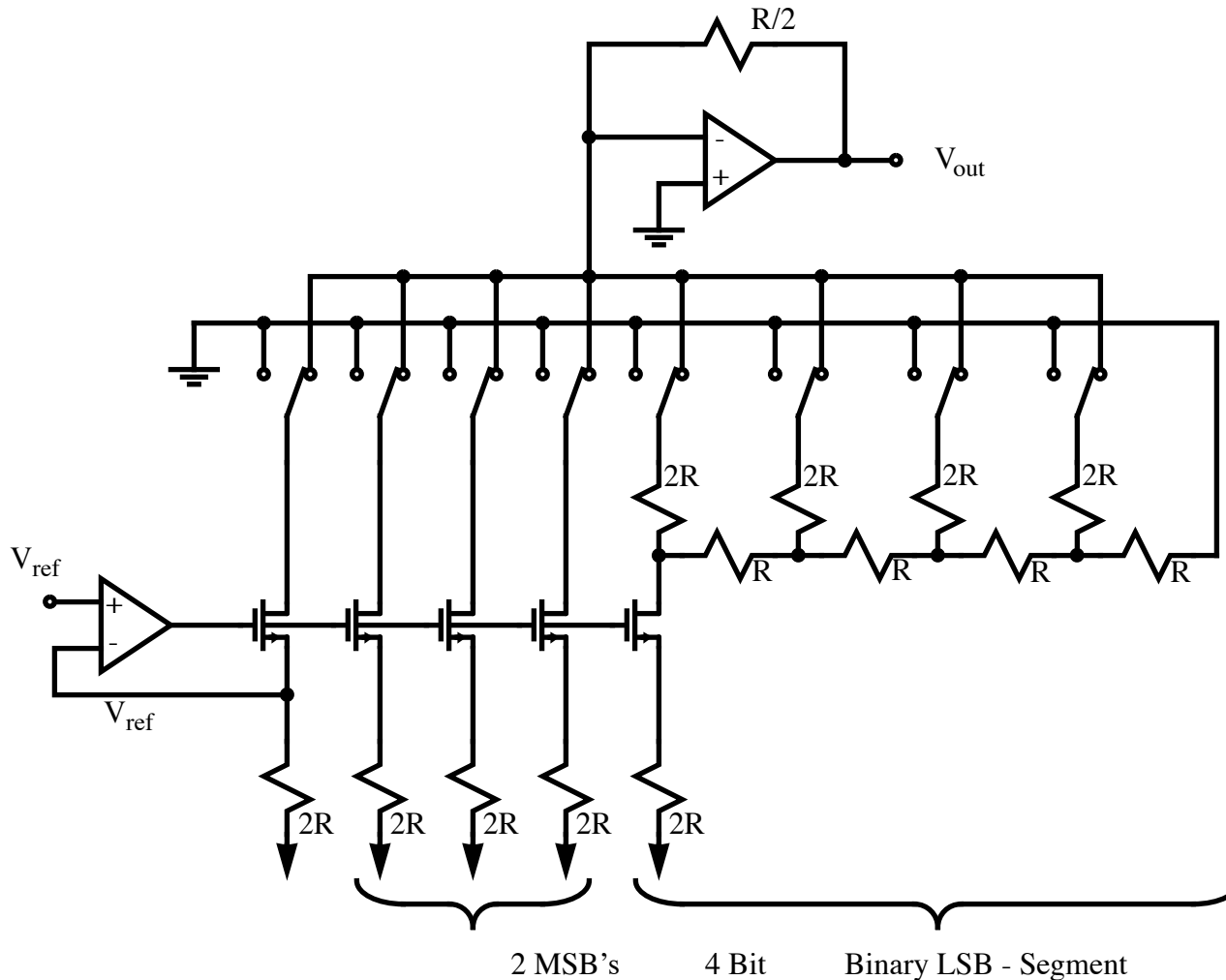

- Combine thermometer and binary
- Accuracy needed for LSB reduced
- Glitches reduced
- Very popular

Dynamically-Matched Current Sources


- Schouwenaar, 88

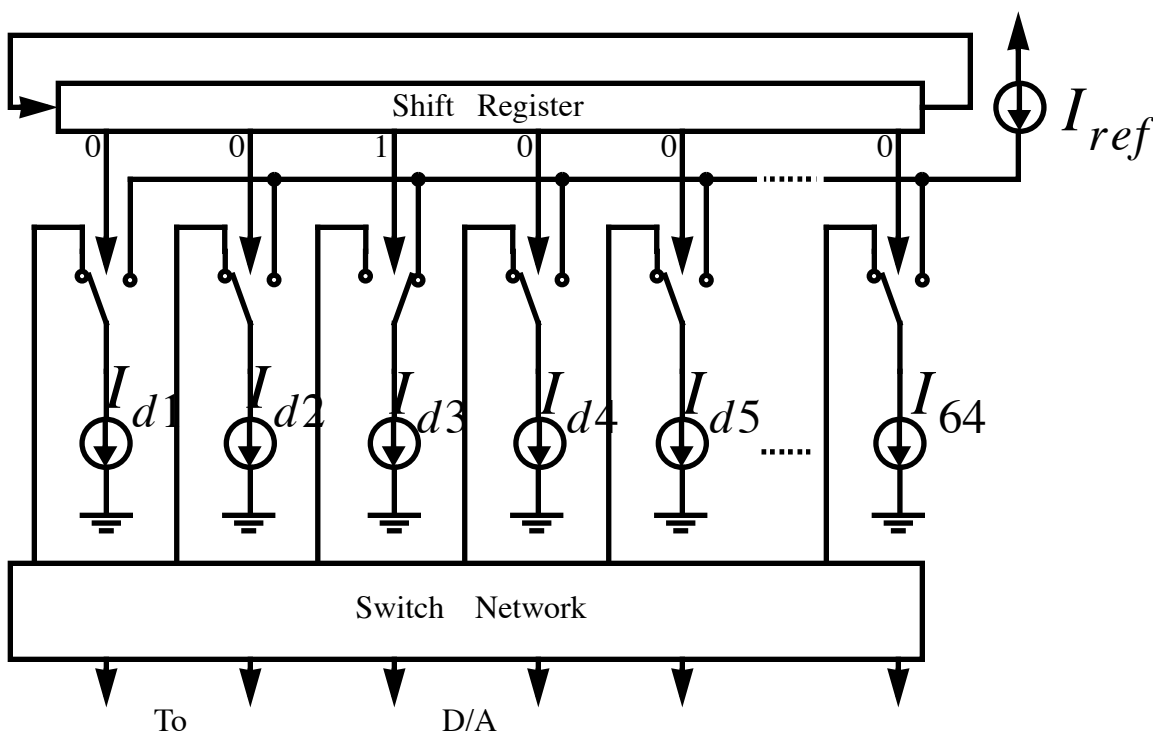


- Dynamic technique with current switching for realizing very well-matched current sources
- Up to 16 bit accuracy

- Each current source is calibrated with a single reference
- 64 used so D/A can continue operating
- Achieved 92 dB SNDR, and 20 mW with 3V.
- Used for audio

Dynamically-Matched Current Sources

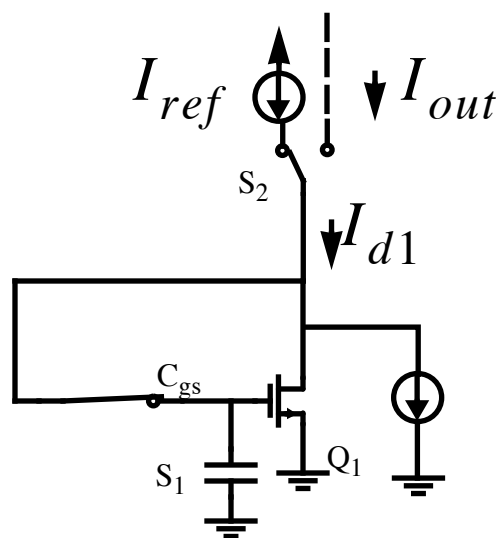

Calibration

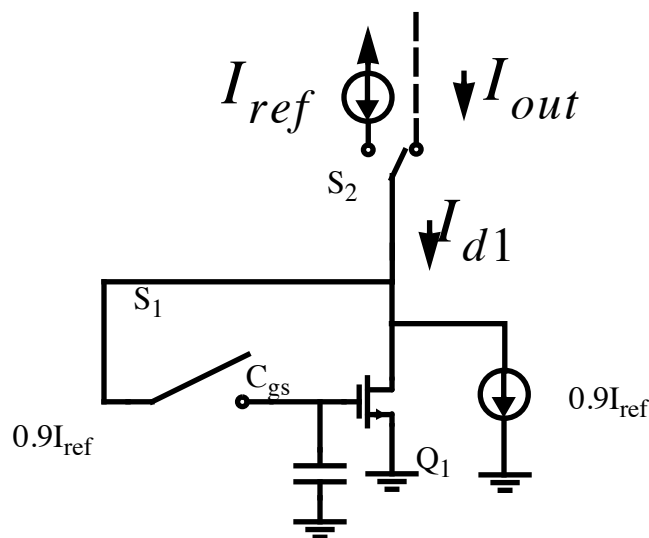

Regular Usage

- Current source $0.9I$ added so a low g_m device used (W/L equal to $10/75$)
- Re-calibrate before leakage causes 0.5LSB error

- Minimize clock-feedthrough and charge-injection by having capacitance C_{gs} and bias voltage V_{GS} large
- Implies voltage error causes less current deviation.