

Oversampling Converters

***Reference: Chapter 14 of the text
“Analog Integrated Circuit Design”
by
David Johns and Ken Martin***

Chapter 18 of the 2nd Edition of the text by Tony Chan Carusone, David Johns, and Ken Martin

The material of this presentation is courtesy of Dr. Ken Martin.

Motivation

- Popular approach for high resolution A/D and D/A (typically low to medium speed)


Easier Analog

- reduced requirement on matching tolerances and amplifier gains
- relaxed anti-aliasing specifications
- relaxed smoothing filters

Catch: More complicated digital signal processing


- More suitable for deep submicron technologies

Quantization Noise

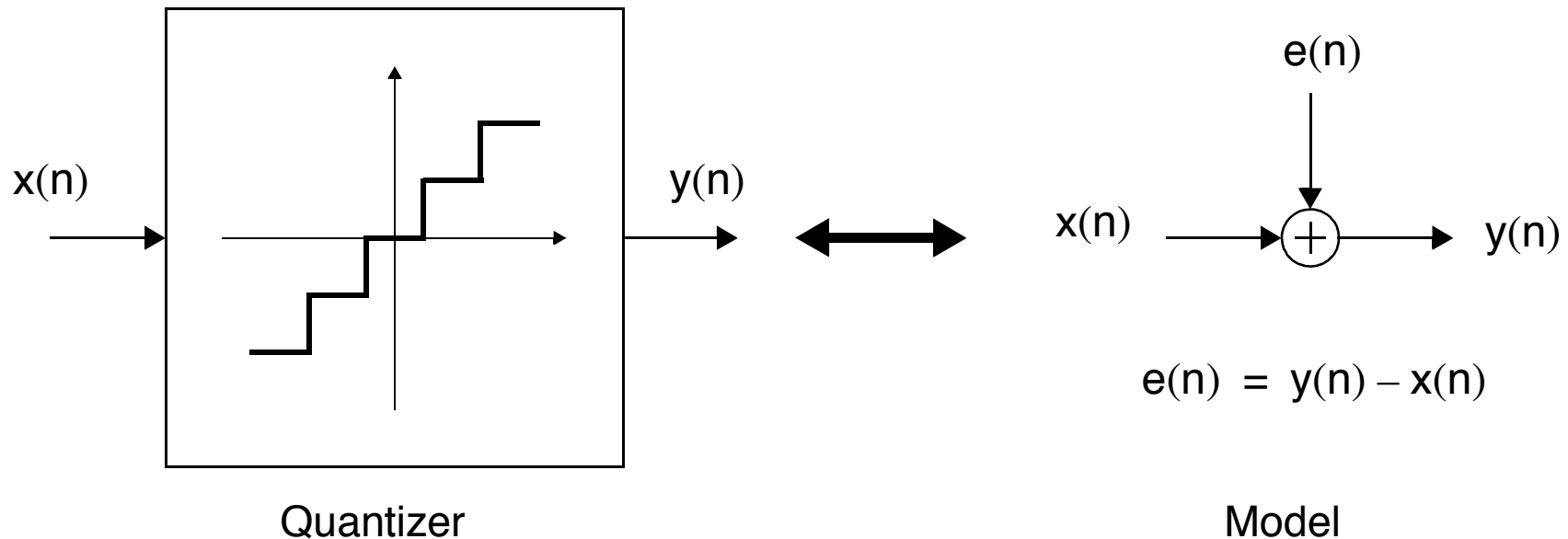

- Above model is exact
 - approximate when assumptions made about $e(n)$
- Often assume $e(n)$ is white, uniformly distributed number between $\pm\Delta/2$
- Δ is difference between two quantization levels


Quantization Noise

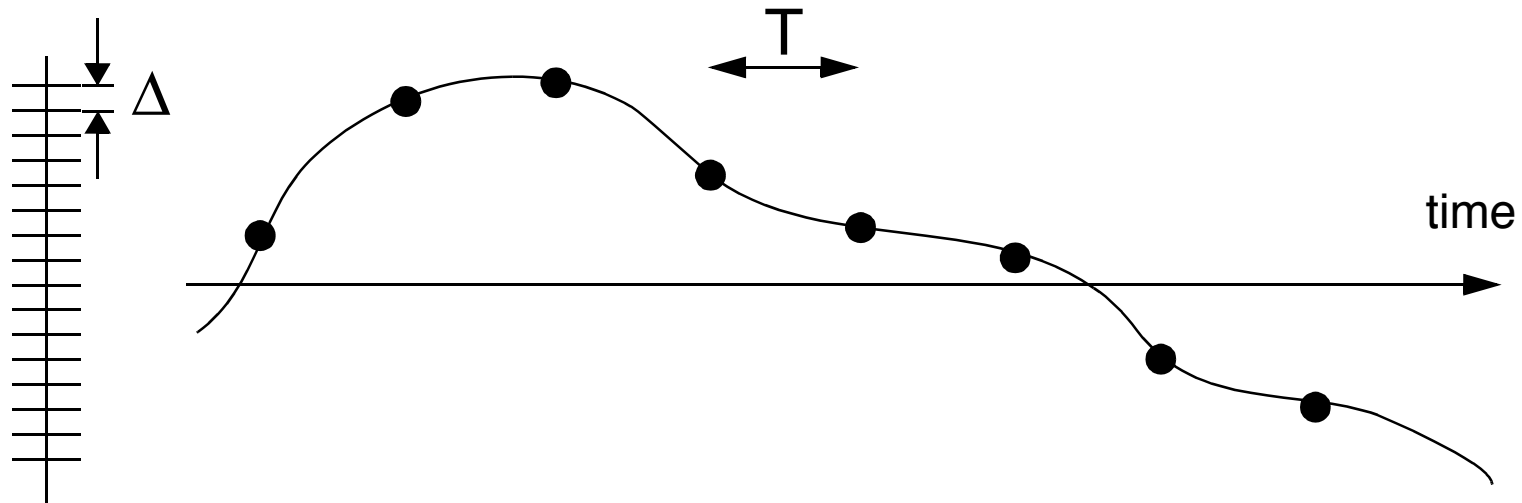

- White noise assumption reasonable when:
 - fine quantization levels
 - signal crosses through many levels between samples
 - sampling rate not synchronized to signal frequency
- Sample lands somewhere in quantization interval leading to random error of $\pm\Delta/2$

Quantization Noise

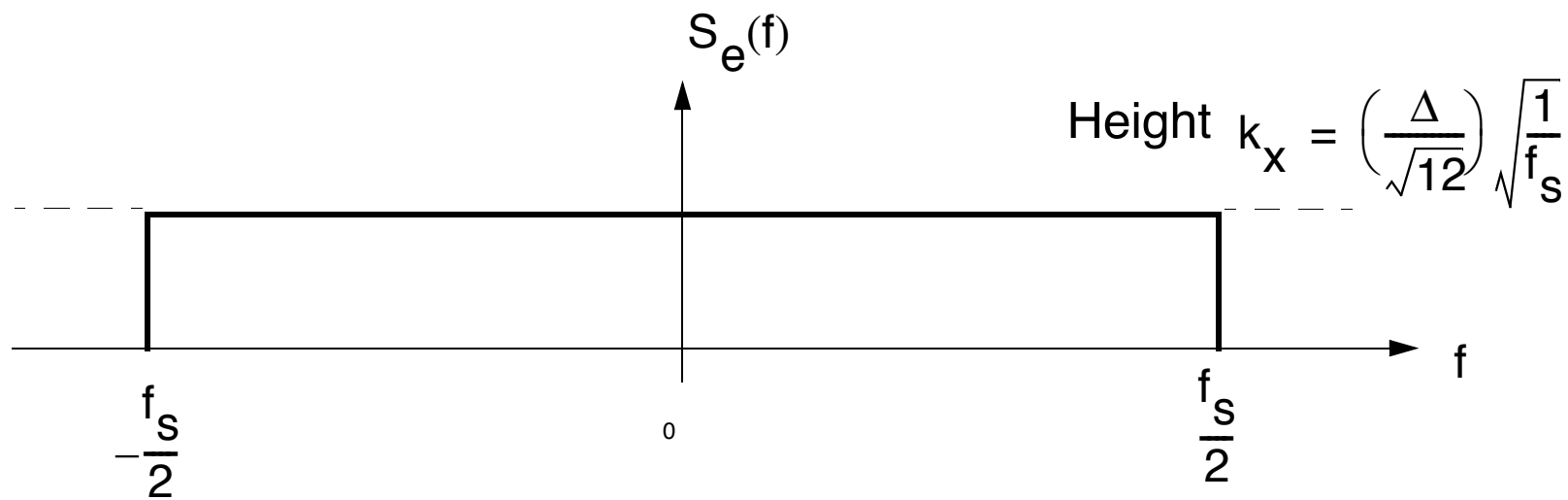- Quantization noise power can be shown to be $\Delta^2/12$ and is ***independent of sampling frequency***
- If white, then spectral density of noise, $S_e(f)$, is constant.




Oversampling Advantage

- Oversampling occurs when signal of interest is bandlimited to f_0 but we sample higher than $2f_0$
- Define oversampling-rate

$$\text{OSR} = f_s / (2f_0) \quad (1)$$

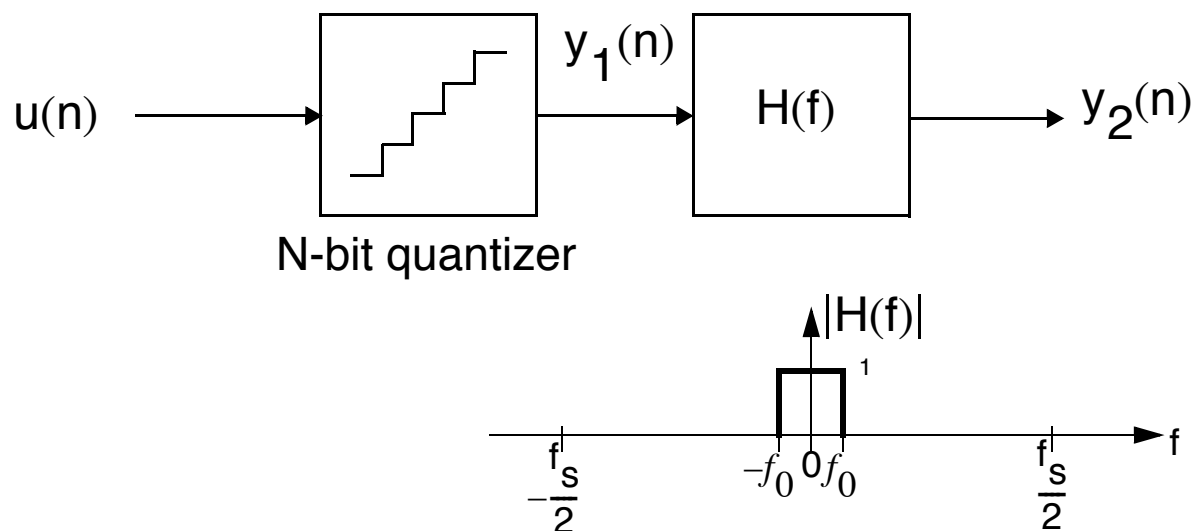- After quantizing input signal, pass it through a brickwall digital filter with passband up to f_0



Oversampling Advantage

- Output quantization noise after filtering is:

$$P_e = \int_{-f_s/2}^{f_s/2} S_e^2(f) |H(f)|^2 df = \int_{-f_0}^{f_0} k_x^2 df = \frac{\Delta^2}{12} \left(\frac{1}{OSR} \right) \quad (2)$$

- Doubling OSR reduces quantation noise power by 3dB (i.e., 0.5 bits/octave)
- Assuming peak input is a sinusoidal wave with a peak value of $2^N (\Delta/2)$ leading to

$$P_s = ((\Delta 2^N) / (2\sqrt{2}))^2$$

- Can also find peak SNR as:

$$SNR_{max} = 10 \log\left(\frac{P_s}{P_e}\right) = 10 \log\left(\frac{3}{2} 2^{2N}\right) + 10 \log(OSR) \quad (3)$$

Oversampling Advantage

Example

- A dc signal with 1V is combined with a noise signal uniformly distributed between $\pm\sqrt{3}$ giving 0 dB SNR.
— {0.94, -0.52, -0.73, 2.15, 1.91, 1.33, -0.31, 2.33}.
- Average of 8 samples results in 0.8875
- Signal adds linearly while noise values add in a square-root fashion — noise filtered out.

Example



- 1-bit A/D gives 6dB SNR.
- To obtain 96dB SNR requires 30 octaves of oversampling ((96-6)/3 dB/octave)
- If $f_0 = 25$ kHz, $f_s = 2^{30} \times f_0 = 54,000$ GHz !

Advantage of 1-bit D/A Converters

- Oversampling improves SNR but not linearity
- To achieve 16-bit linear converter using a 12-bit converter, 12-bit converter must be linear to 16 bits
 - i.e. integral nonlinearity better than $1/2^4$ LSB
- A 1-bit D/A is ***inherently linear***
 - 1-bit D/A has only 2 output points
 - 2 points always lie on a straight line
- Can achieve better than 20 bits linearity without trimming (will likely have gain and offset error)
- Second-order effects (such as D/A memory or signal-dependent reference voltages) will limit linearity.

Oversampling with Noise Shaping

- Place the quantizer in a feedback loop

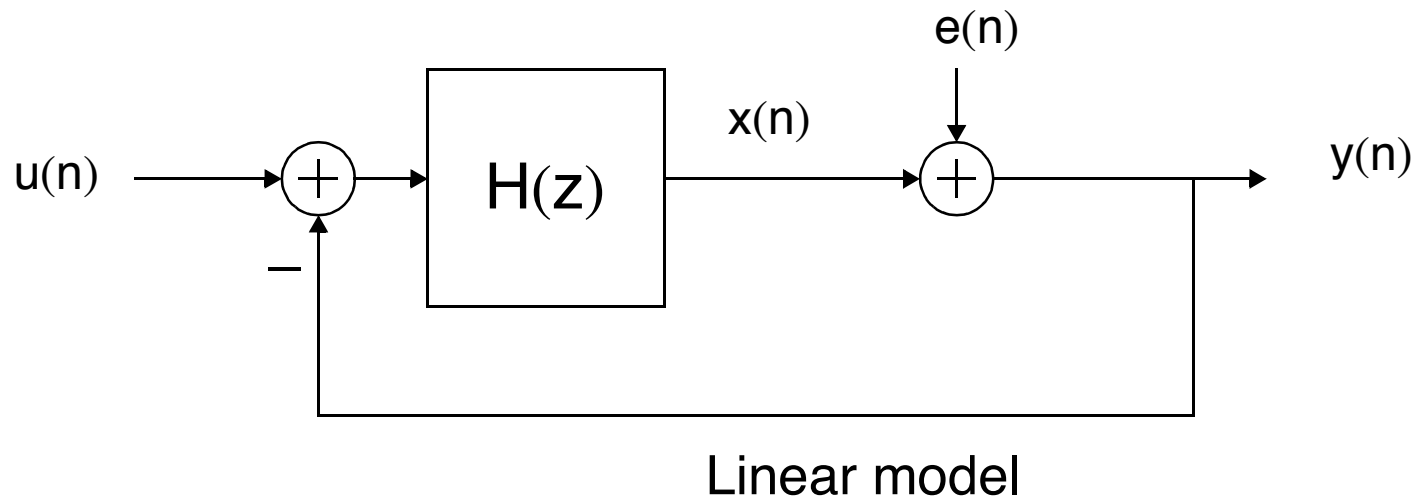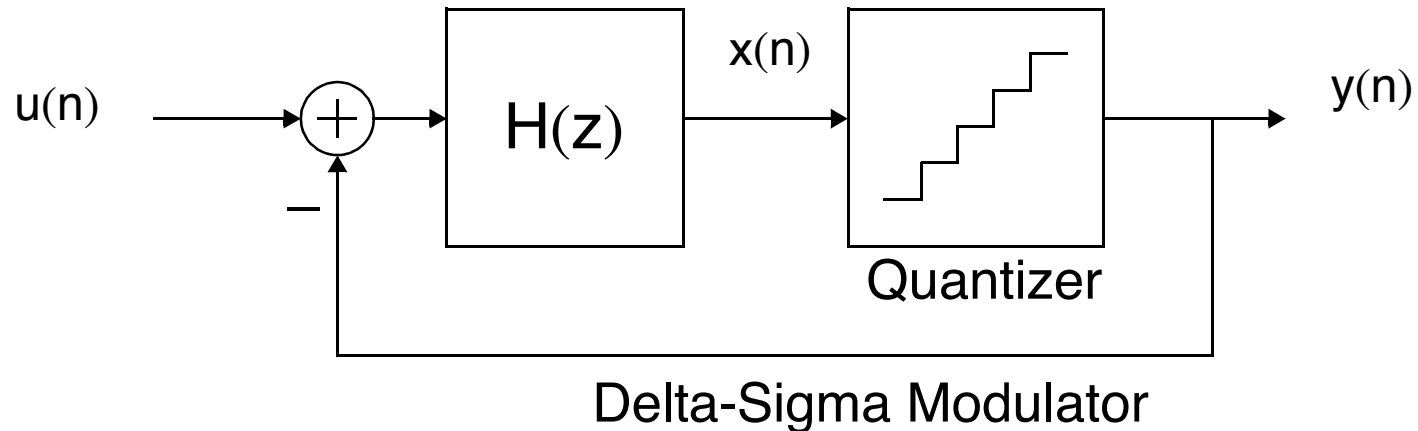

Oversampling with Noise Shaping

- Shapes quantization noise away from signal band of interest

Signal and Noise Transfer-Functions

$$S_{TF}(z) \equiv \frac{Y(z)}{U(z)} = \frac{H(z)}{1 + H(z)} \quad (4)$$

$$N_{TF}(z) \equiv \frac{Y(z)}{E(z)} = \frac{1}{1 + H(z)} \quad (5)$$

$$Y(z) = S_{TF}(z)U(z) + N_{TF}(z)E(z) \quad (6)$$

- Choose $H(z)$ to be large over 0 to f_0
- Resulting quantization noise near 0 where $H(z)$ large
- Signal transfer-function near 1 where $H(z)$ large


Oversampling with Noise Shaping

- Input signal is limited to range of quantizer output when $H(z)$ large
- For 1-bit quantizers, input often limited to 1/4 quantizer outputs
- Out-of-band signals can be larger when $H(z)$ small
- Stability of modulator can be an issue (particularly for higher-orders of $H(z)$)
- Stability defined as when input to quantizer becomes so large that quantization error is greater than $\pm\Delta/2$ — referred to as “overload the quantizer”

First-Order Noise Shaping

- Choose $H(z)$ to be a discrete-time integrator

$$H(z) = \frac{1}{z-1} \quad (7)$$

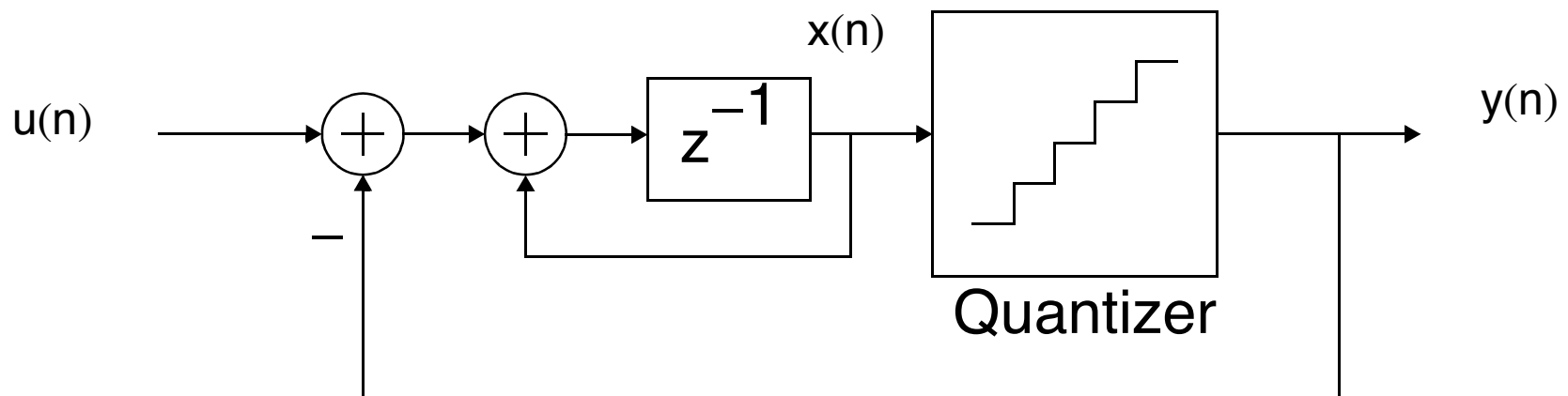

- If stable, average input of integrator must be zero
- Average value of $u(n)$ must equal average of $y(n)$

Example

- The output sequence and state values when a dc input, $u(n)$, of $1/3$ is applied to a 1'st order modulator with a two-level quantizer of ± 1.0 . Initial state for $x(n)$ is 0.1.

n	x(n)	x(n + 1)	y(n)	e(n)
0	0.1	-0.5667	1.0	0.9
1	-0.5667	0.7667	-1.0	-0.4333
2	0.7667	0.1	1.0	0.2333
3	0.1	-0.5667	1.0	0.9
4	-0.5667	0.7667	-1.0	-0.4333
5

- Average of $y(n)$ is $1/3$ as expected
- Periodic quantization noise in this case

Transfer-Functions

Signal and Noise Transfer-Functions

$$S_{TF}(z) = \frac{Y(z)}{U(z)} = \frac{1/(z-1)}{1 + 1/(z-1)} = z^{-1} \quad (8)$$

$$N_{TF}(z) = \frac{Y(z)}{E(z)} = \frac{1}{1 + 1/(z-1)} = (1 - z^{-1}) \quad (9)$$

- Noise transfer-function is a discrete-time differentiator (i.e., a high-pass filter)

$$\begin{aligned} N_{TF}(f) &= 1 - e^{-j2\pi f/f_s} = \frac{e^{j\pi f/f_s} - e^{-j\pi f/f_s}}{2j} \times 2j \times e^{-j\pi f/f_s} \\ &= \sin\left(\frac{\pi f}{f_s}\right) \times 2j \times e^{-j\pi f/f_s} \end{aligned} \quad (10)$$

Signal to Noise Ratio

Magnitude of noise transfer-function

$$|N_{TF}(f)| = 2 \sin\left(\frac{\pi f}{f_s}\right) \quad (11)$$

Quantization noise power

$$P_e = \int_{-f_0}^{f_0} S_e^2(f) |N_{TF}(f)|^2 df = \int_{-f_0}^{f_0} \left(\frac{\Delta^2}{12}\right) \frac{1}{f_s} \left[2 \sin\left(\frac{\pi f}{f_s}\right)\right]^2 df \quad (12)$$

- Assuming $f_0 \ll f_s$ (i.e., $OSR \gg 1$)

$$P_e \cong \left(\frac{\Delta^2}{12}\right) \left(\frac{\pi^2}{3}\right) \left(\frac{2f_0}{f_s}\right)^3 = \frac{\Delta^2 \pi^2}{36} \left(\frac{1}{OSR}\right)^3 \quad (13)$$

Max SNR

- Assuming peak input is a sinusoidal wave with a peak value of $2^N (\Delta/2)$ leading to

$$P_s = ((\Delta 2^N) / (2\sqrt{2}))^2$$



- Can find peak SNR as:

$$\begin{aligned} \text{SNR}_{max} &= 10 \log\left(\frac{P_s}{P_e}\right) \\ &= 10 \log\left(\frac{3}{2} 2^{2N}\right) + 10 \log\left[\frac{3}{\pi^2} (\text{OSR})^3\right] \end{aligned} \quad (14)$$


$$\text{SNR}_{max} = 6.02N + 1.76 - 5.17 + 30 \log(\text{OSR}) \quad (15)$$

- Doubling OSR gives an SNR improvement 9 dB or, equivalently, a benefit of 1.5 bits/octave

SC Implementation

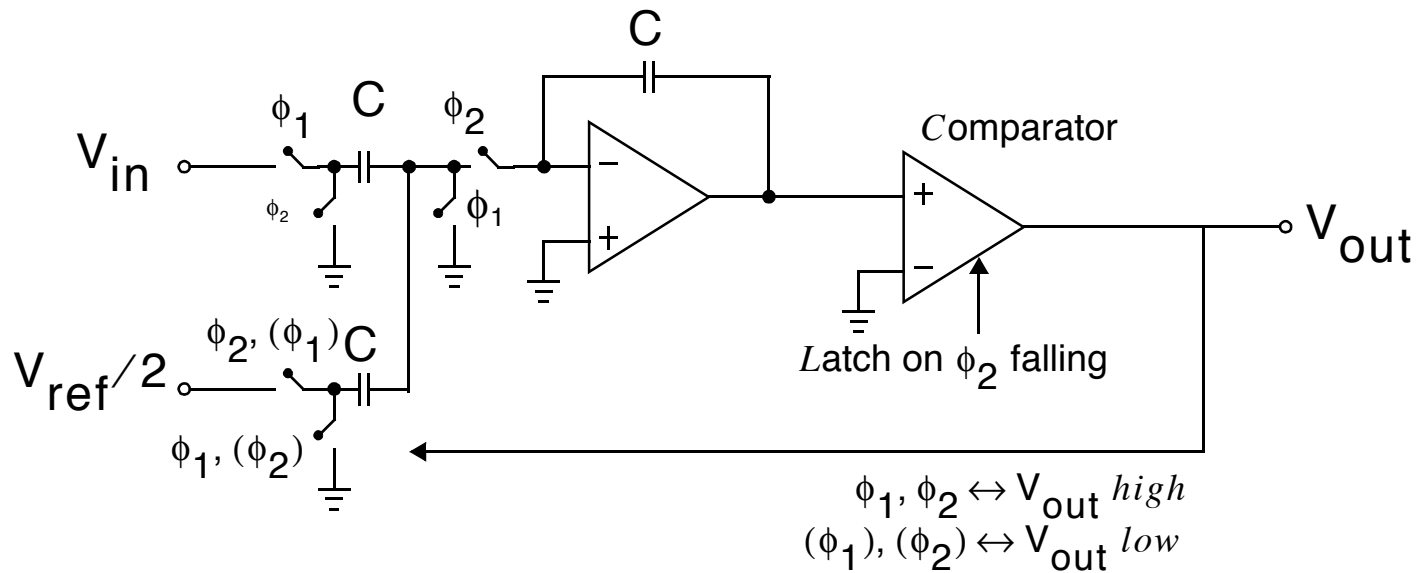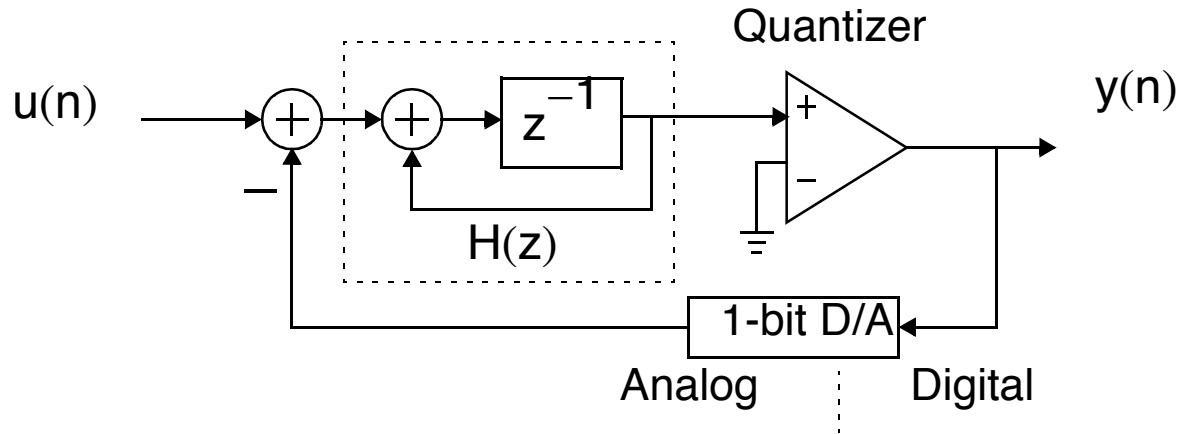

Second-Order Noise Shaping

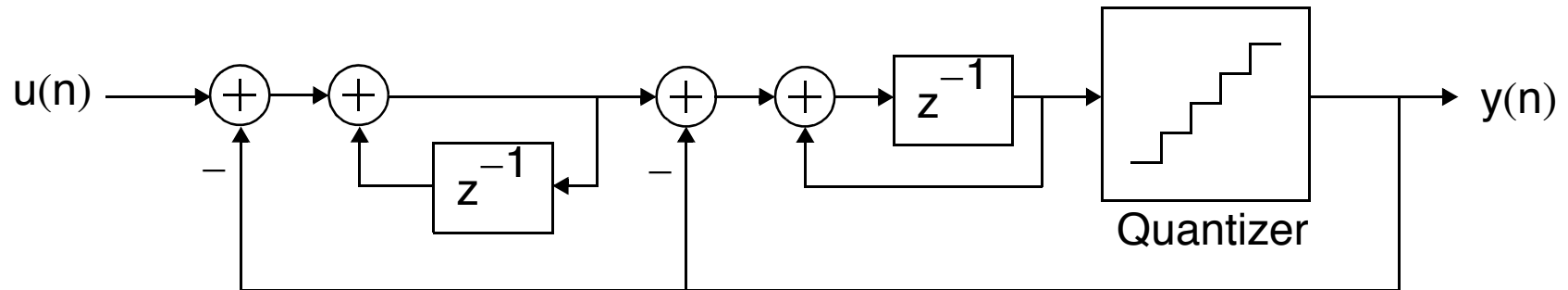


$$S_{TF}(f) = z^{-1} \quad (16)$$

$$N_{TF}(f) = (1 - z^{-1})^2 \quad (17)$$

$$SNR_{max} = 6.02N + 1.76 - 12.9 + 50 \log(OSR) \quad (18)$$

- Doubling OSR improves SNR by 15 dB (i.e., a benefit of 2.5 bits/octave)

Noise Transfer-Function Curves

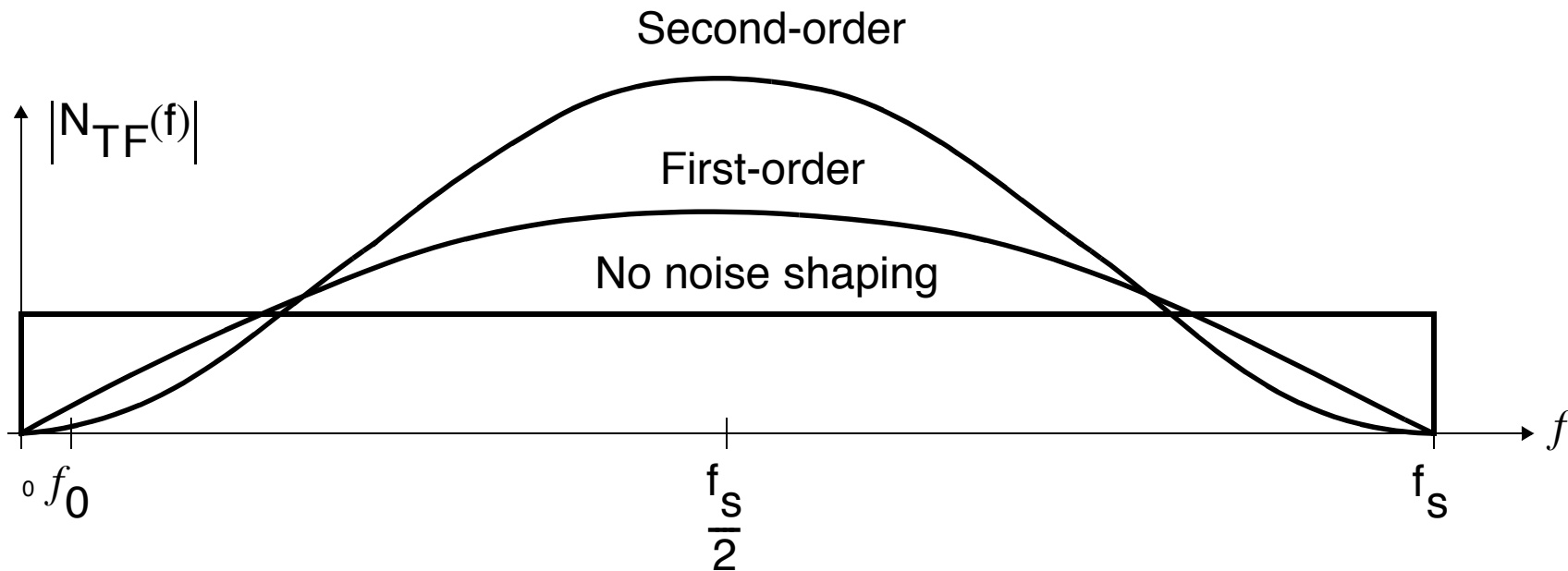

- Out-of-band noise increases for high-order modulators
- Out-of-band noise peak controlled by poles of noise transfer-function
- Can also spread zeros over band-of-interest

Example

- 90 dB SNR improvement from A/D with $f_0 = 25$ kHz

Oversampling with no noise shaping

- From before, straight oversampling requires a sampling rate of 54,000 GHz.

First-Order Noise Shaping

- Lose 5 dB (see (15)), require 95 dB divided by 9 dB/octave, or 10.56 octaves — $f_s = 2^{10.56} \times 2f_0 \cong 75$ MHz


Second-Order Noise Shaping

- Lose 13 dB, required 103 dB divided by 15 dB/octave, $f_s = 5.8$ MHz
- In general, an L'th order 1-bit modulator improves SNR by $6L+3$ dB/octave

Quantization Noise Power of 1-bit Modulators

- If output of 1-bit mod is ± 1 , total power of output signal, $y(n)$, is normalized power of 1 watt.
- Signal level often limited to well below ± 1 level in higher-order modulators to maintain stability
- For example, if maximum peak level is ± 0.25 , max signal power is 62.5 mW.
- Max signal is approx 12 dB below quantization noise (but most of the noise is in different frequency region)
- Quantization filter must have dynamic range capable of handling full power of $y(n)$ at input.
- Easy for A/D — digital filter
- More difficult for D/A — analog filter

Zeros of NTF are poles of $H(z)$

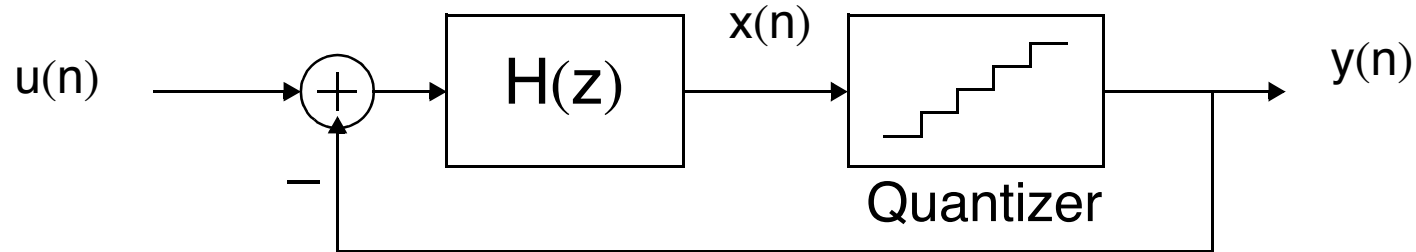

- Write $H(z)$ as



$$H(z) = \frac{N(z)}{D(z)} \quad (19)$$

- NTF is given by:






$$\text{NTF}(z) = \frac{1}{1 + H(z)} = \frac{D(z)}{D(z) + N(z)} \quad (20)$$

- If poles of $H(z)$ are well-defined then so are zeros of NTF

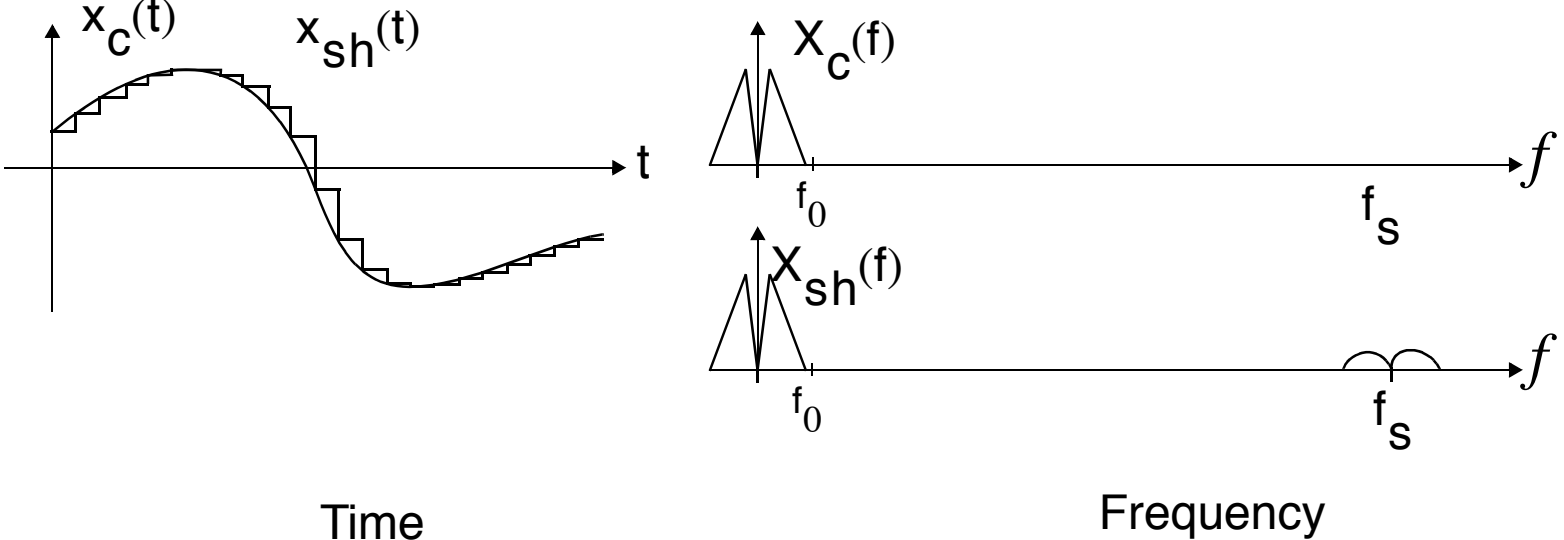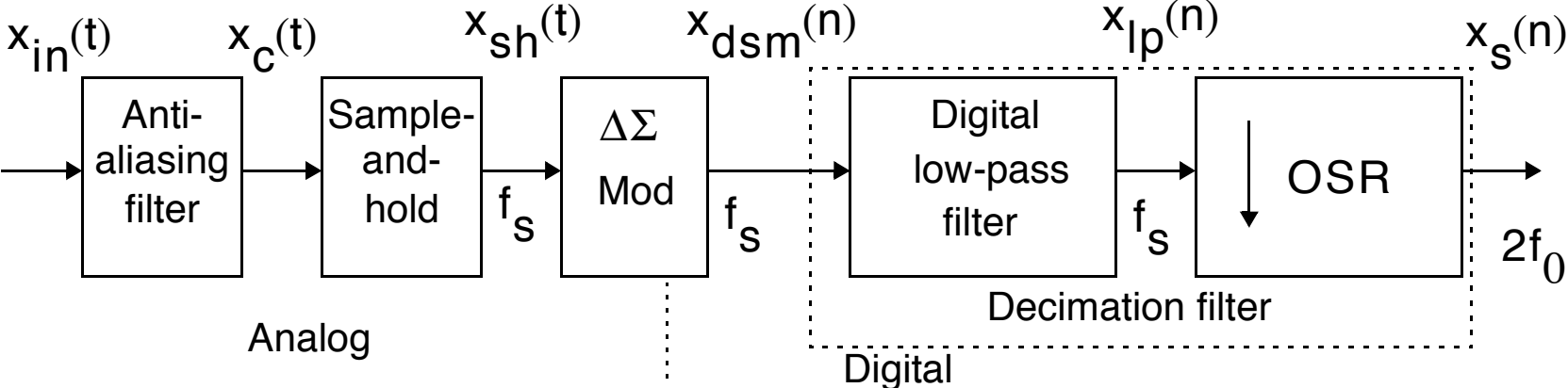Architecture of Delta-Sigma A/D Converters



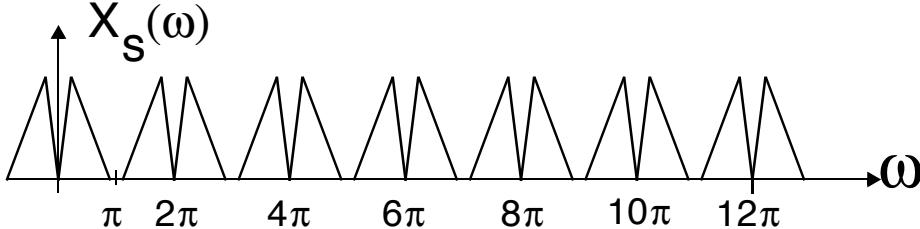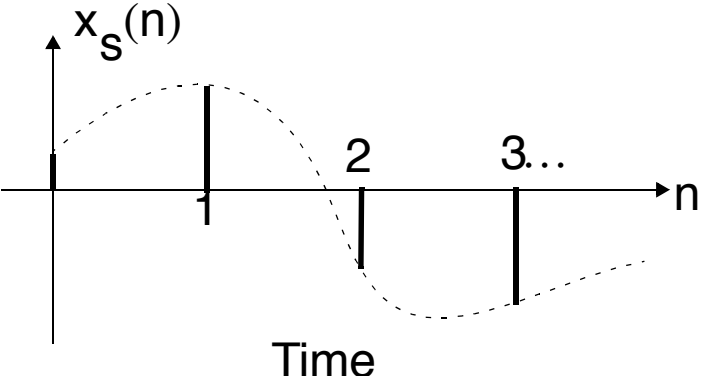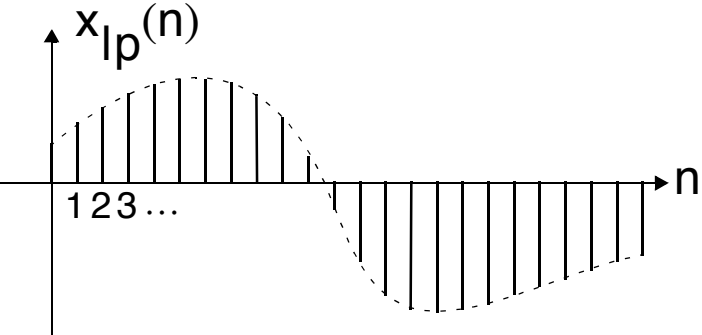
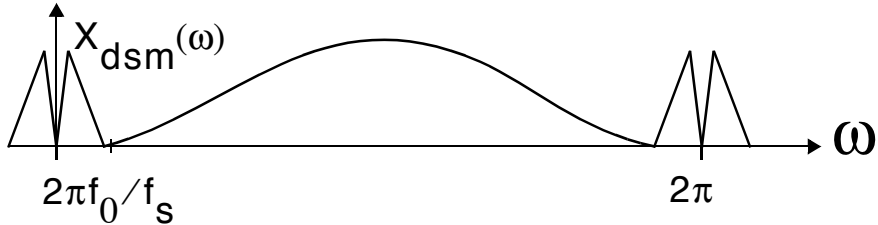
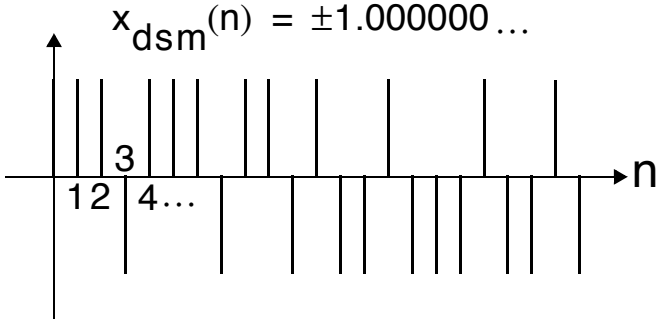
Architecture of Delta-Sigma A/D Converters



Architecture of Delta-Sigma A/D Converters

- Relaxes analog anti-aliasing filter
- Strict anti-aliasing done in digital domain
- Must also remove quantization noise before downsampling (or aliasing occurs)
- Commonly done with a multi-stage system
- Linearity of D/A in modulator important — results in overall nonlinearity
- Linearity of A/D in modulator unimportant (effects reduced by high gain in feedback of modulator)

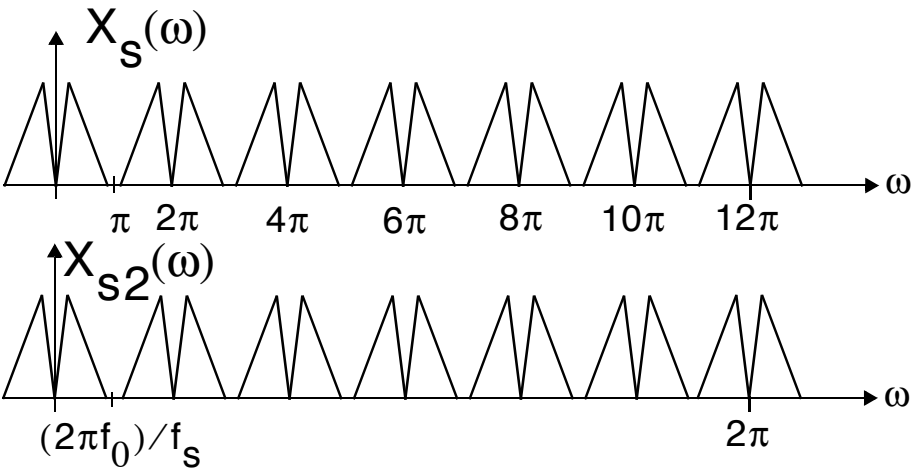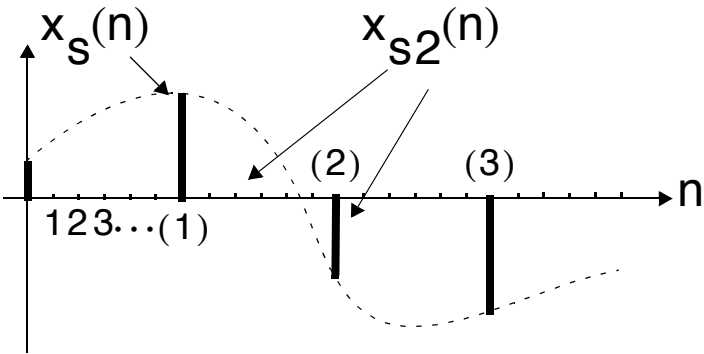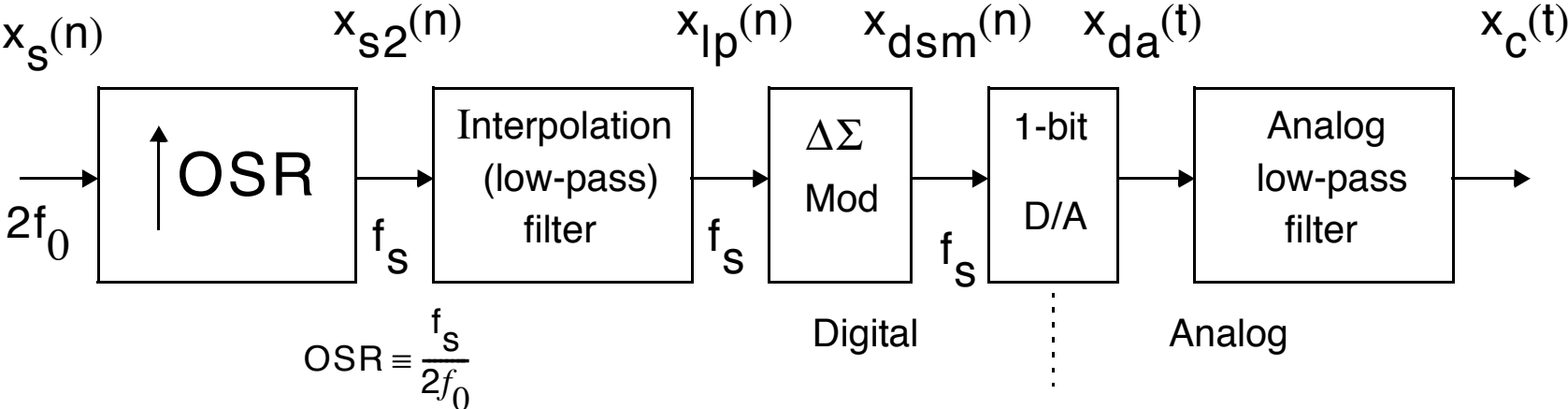
Architecture of Delta-Sigma D/A Converters




Time

Frequency

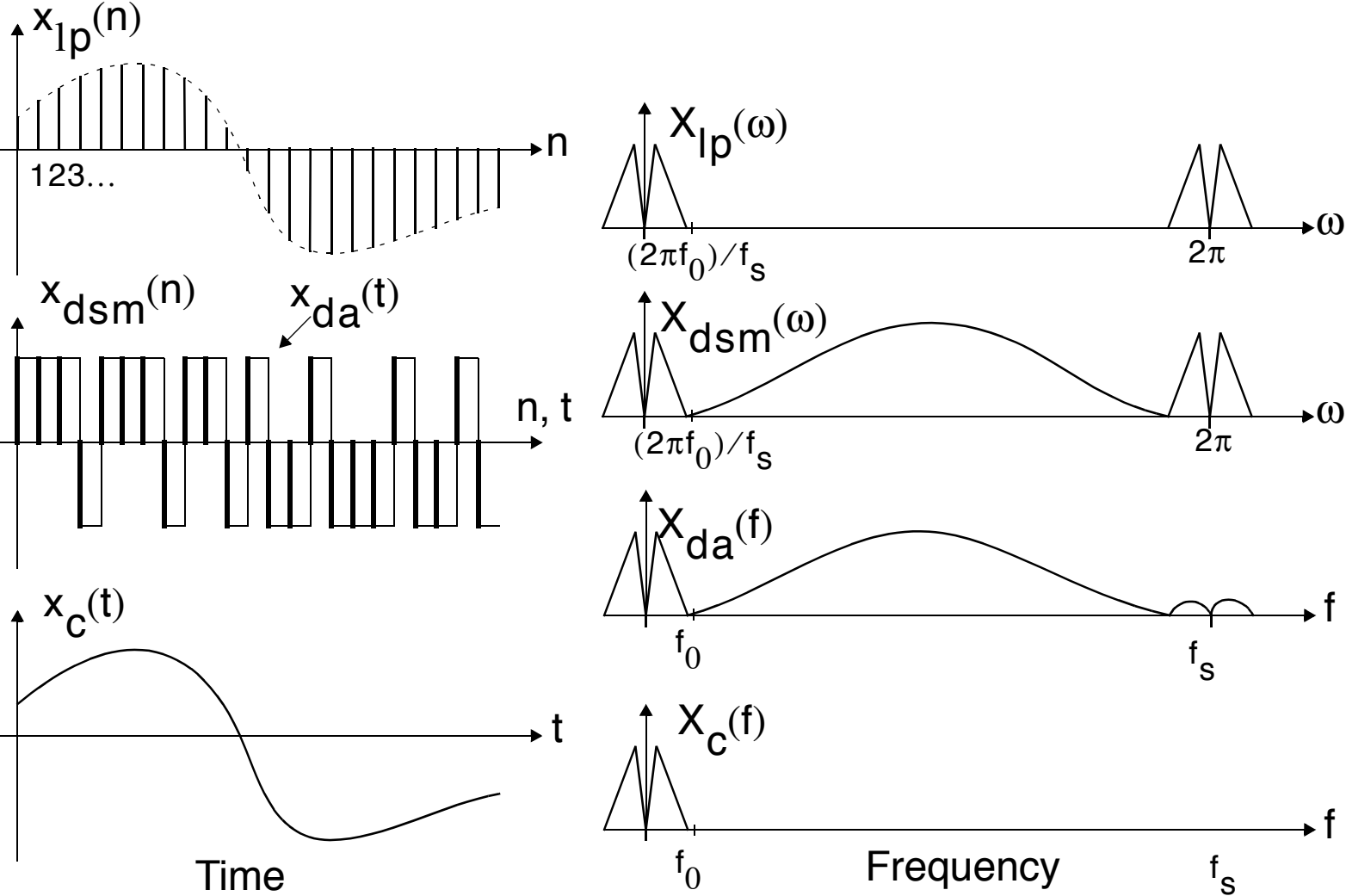Architecture of Delta-Sigma D/A Converters



Multi-Stage Digital Decimation

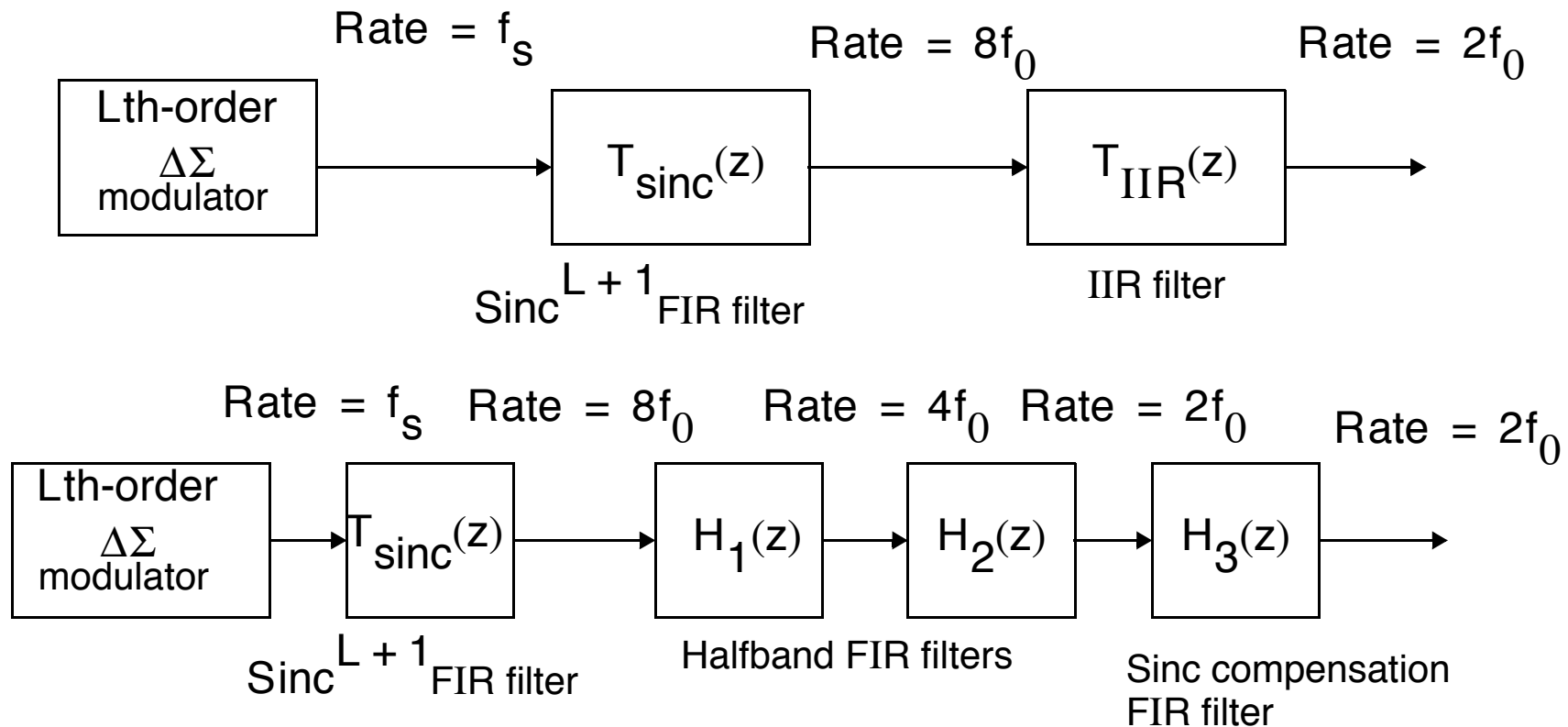

- Sinc filter removes much of quantization noise
- Following filter(s) — anti-aliasing filter and noise

Sinc Filter


- sinc^{L+1} is a cascade of $L+1$ averaging filters

$$T_{avg}(z) = \frac{Y(z)}{U(z)} = \frac{1}{M} \sum_{i=0}^{M-1} z^{-i} \quad (21)$$

- M is integer ratio of $f_s / (8f_0)$
- It is a linear-phase filter (symmetric coefficients)
- If M is power of 2, easy division (shift left)
- Can not do all decimation filtering here since not sharp enough cutoff

Sinc Filter

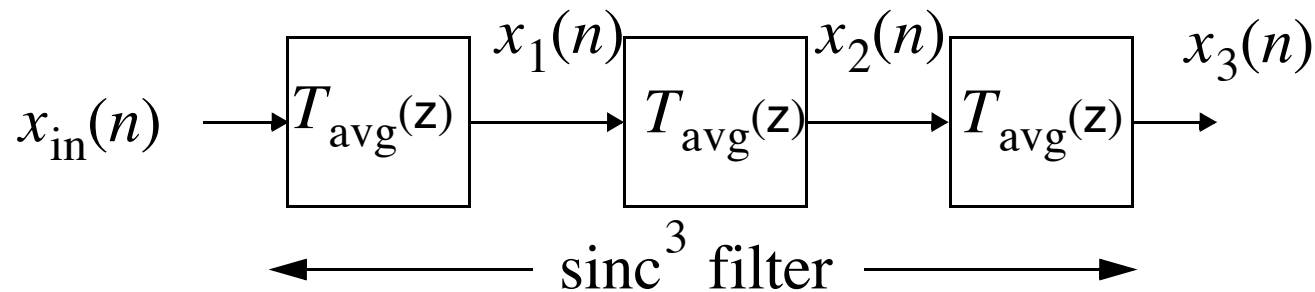- Consider $x_{\text{in}}(n) = \{1, 1, -1, 1, 1, -1, \dots\}$ applied to $M = 4$ averaging filters in cascade



- $x_1(n) = \{0.5, 0.5, 0.0, 0.5, 0.5, 0.0, \dots\}$
- $x_2(n) = \{0.38, 0.38, 0.25, 0.38, 0.38, 0.25, \dots\}$
- $x_3(n) = \{0.34, 0.34, 0.31, 0.34, 0.34, 0.31, \dots\}$
- Converging to sequence of all $1/3$ as expected

Sinc Filter Response

- Can rewrite averaging filter in recursive form as

$$T_{avg}(z) = \frac{Y(z)}{U(z)} = \frac{1}{M} \left(\frac{1 - z^{-M}}{1 - z^{-1}} \right) \quad (22)$$

and a cascade of $L + 1$ averaging filters results in

$$T_{sinc}(z) = \frac{1}{M^{L+1}} \left(\frac{1 - z^{-M}}{1 - z^{-1}} \right)^{L+1} \quad (23)$$


- Use $L + 1$ cascade to roll off quantization noise faster than it rises in L 'th order modulator

Sinc Filter Frequency Response

- Let $z = e^{j\omega}$



$$T_{avg}(e^{j\omega}) = \frac{\text{sinc}\left(\frac{\omega M}{2}\right)}{\text{sinc}\left(\frac{\omega}{2}\right)} \quad (24)$$

where $\text{sinc}(x) \equiv \sin(x)/x$

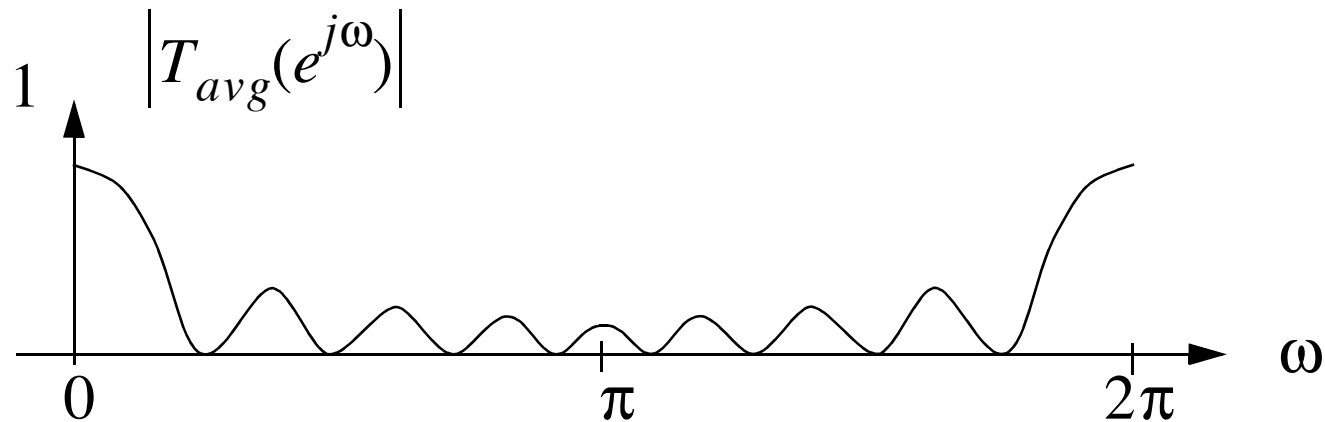

Sinc Implementation

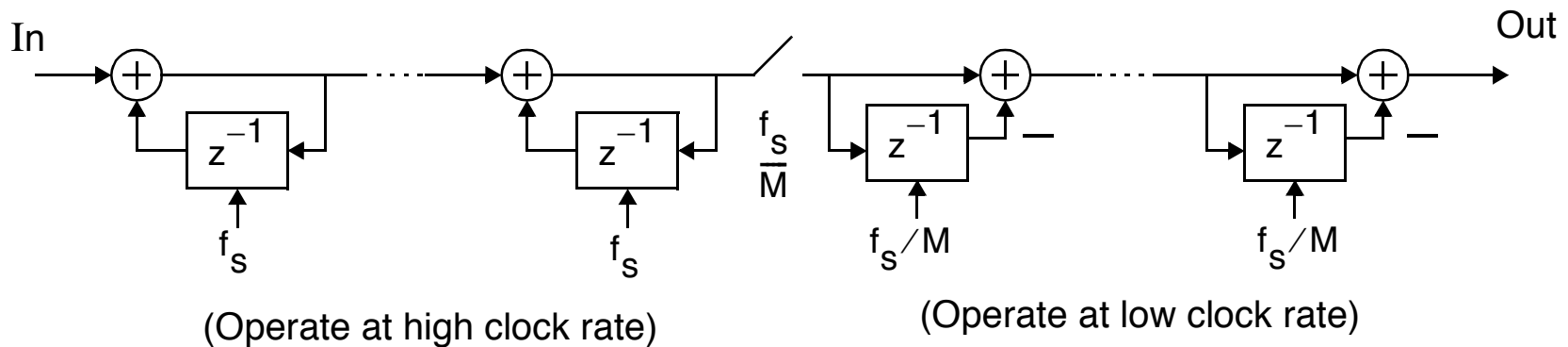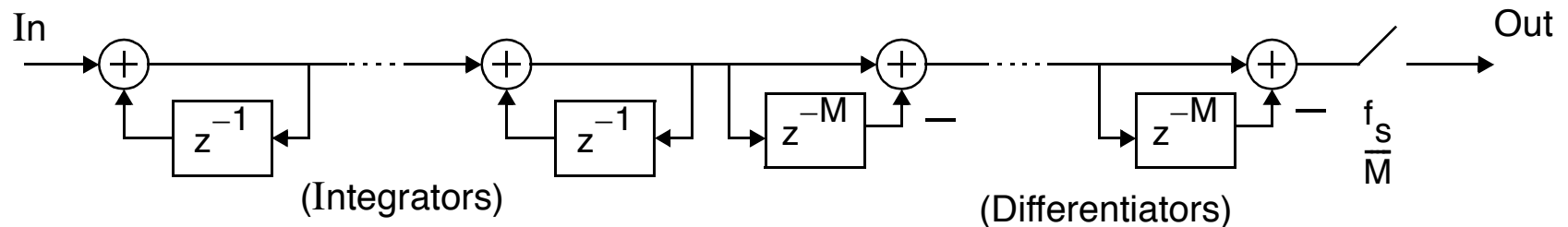
$$T_{\text{sinc}}(z) = \left(\frac{1}{1 - z^{-1}} \right)^{L+1} (1 - z^M)^{L+1} \frac{1}{M^{L+1}} \quad (25)$$



- If 2's complement arithmetic used, wrap-around okay since followed by differentiators

MASH Architecture

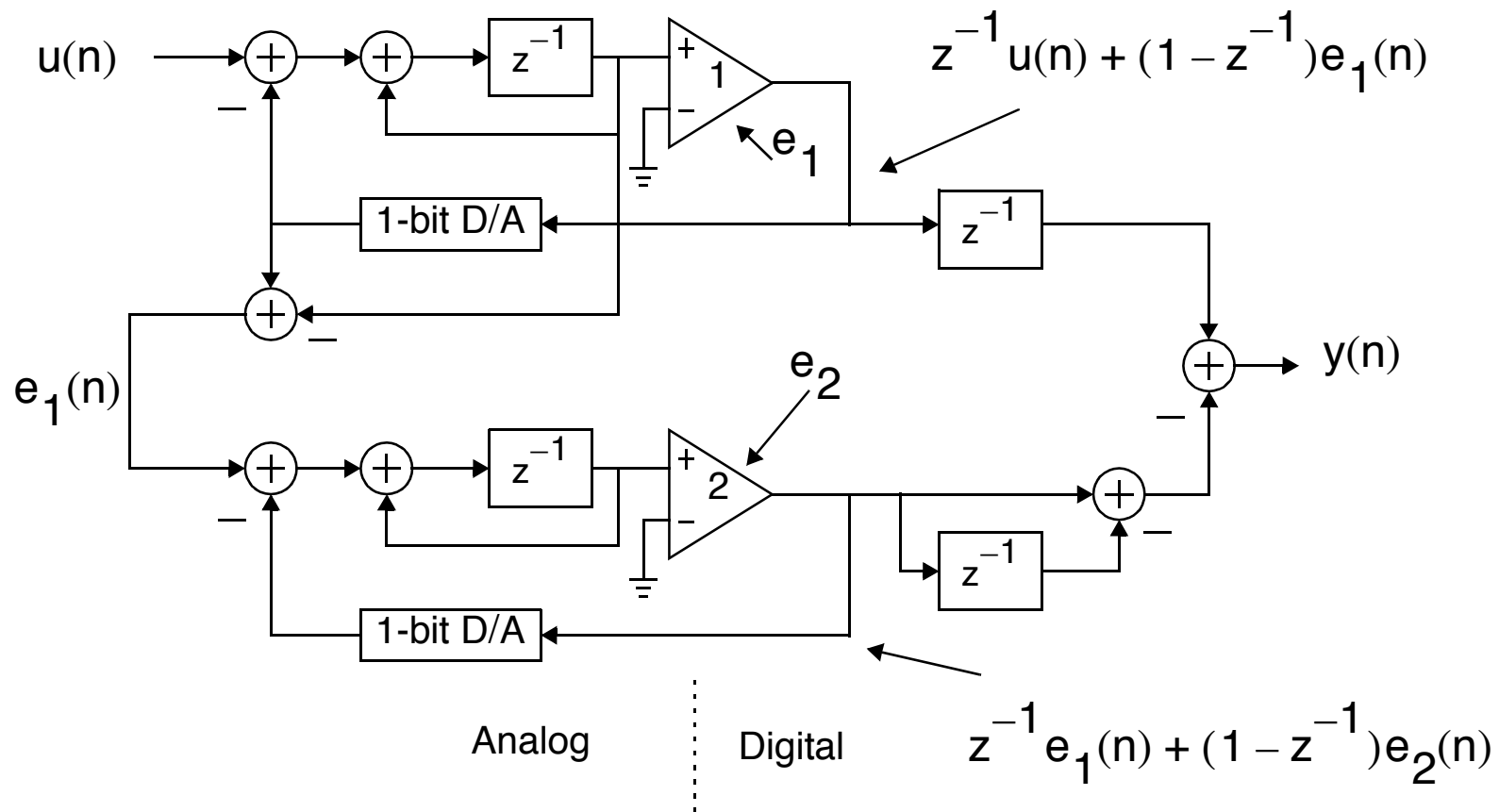- Multi-stAge noise SHaping - MASH
- Use multiple lower order modulators and combine outputs to cancel noise of first stages



MASH Architecture

- Output found to be:

$$Y(z) = z^{-2}U(z) - (1 - z^{-1})^2 E_2(z) \quad (26)$$

Multibit Output



- Output is a 4-level signal though only single-bit D/A's
 - if D/A application, then linear 4-level D/A needed
 - if A/D, slightly more complex decimation

A/D Application


- Mismatch between analog and digital can cause first-order noise, e_1 , to leak through to output
- Choose first stage as higher-order (say 2'nd order)

Bandpass Oversampling Converters

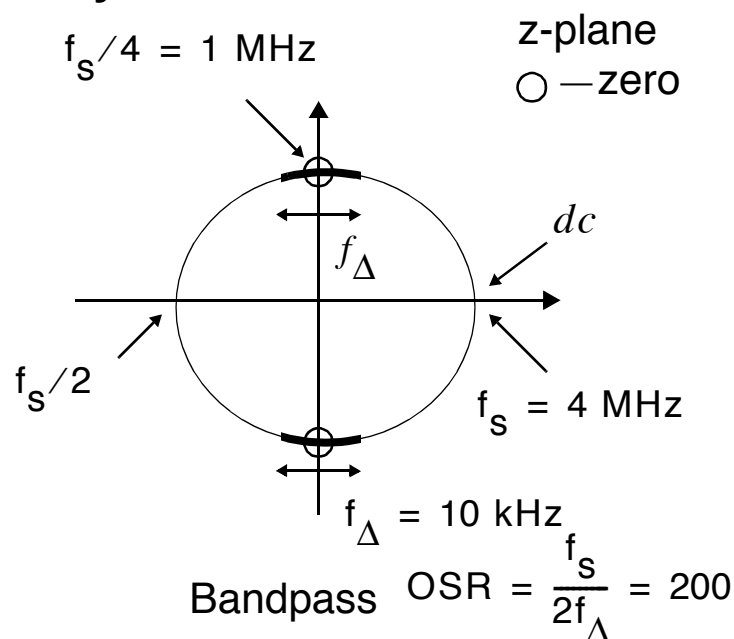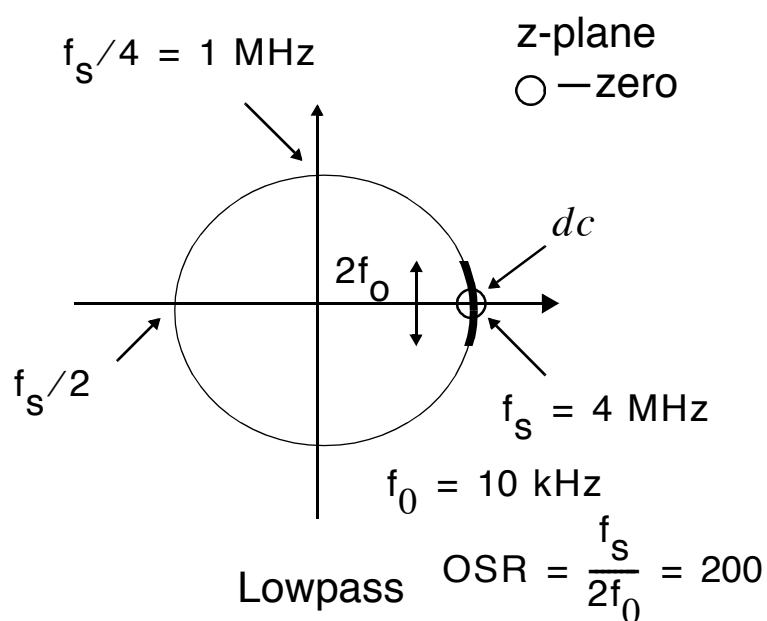- Choose $H(z)$ to have high gain near freq f_c
- NTF shapes quantization noise to be small near f_c
- OSR is ratio of sampling-rate to twice bandwidth — not related to center frequency



Bandpass Oversampling Converters

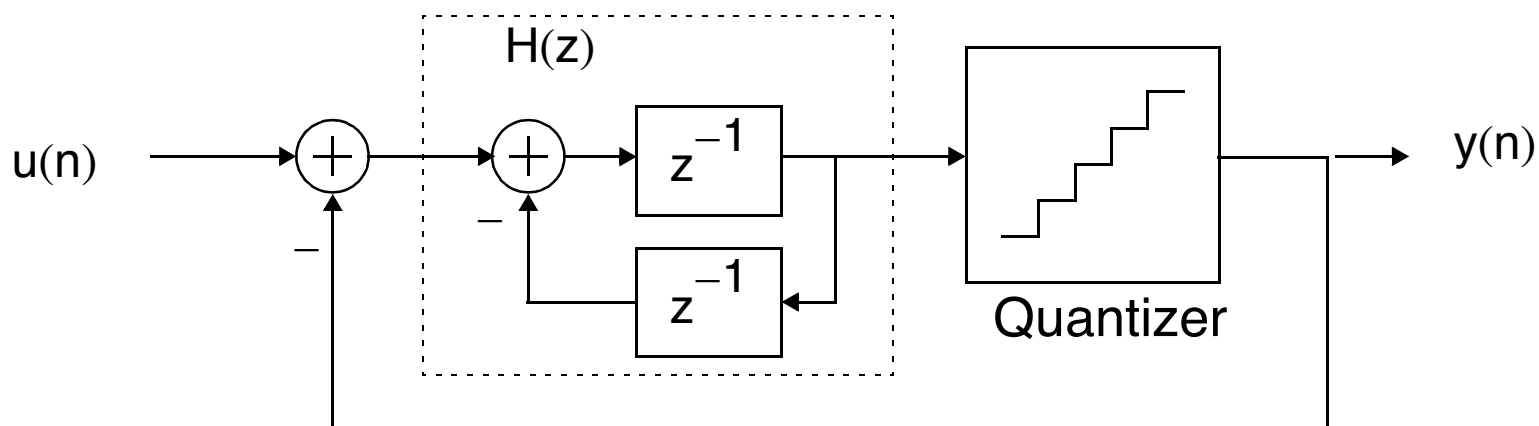

- Above $H(z)$ has poles at $\pm j$ (which are zeros of NTF)
 - $H(z)$ is a resonator with infinite gain at $f_s/4$
 - $H(z) = z/(z^2 + 1)$
- Note one zero at $+j$ and one zero at $-j$
 - similar to lowpass first-order modulator
 - only 9 dB/octave
- For 15 dB/octave, need 4'th order BP modulator


Modulator Stability

- Since feedback involved, stability is an issue
- Considered stable if quantizer input does not **overload** quantizer
- Non-trivial to analyze due to quantizer nonlinearity
- There are rigorous tests to guarantee stability but they are too conservative
- For a 1-bit quantizer, heuristic test is:

$$\left| N_{TF}(e^{j\omega}) \right| \leq 1.5 \quad \text{for } 0 \leq \omega \leq \pi \quad (27)$$

- Peak of NTF should be less than 1.5

Modulator Stability

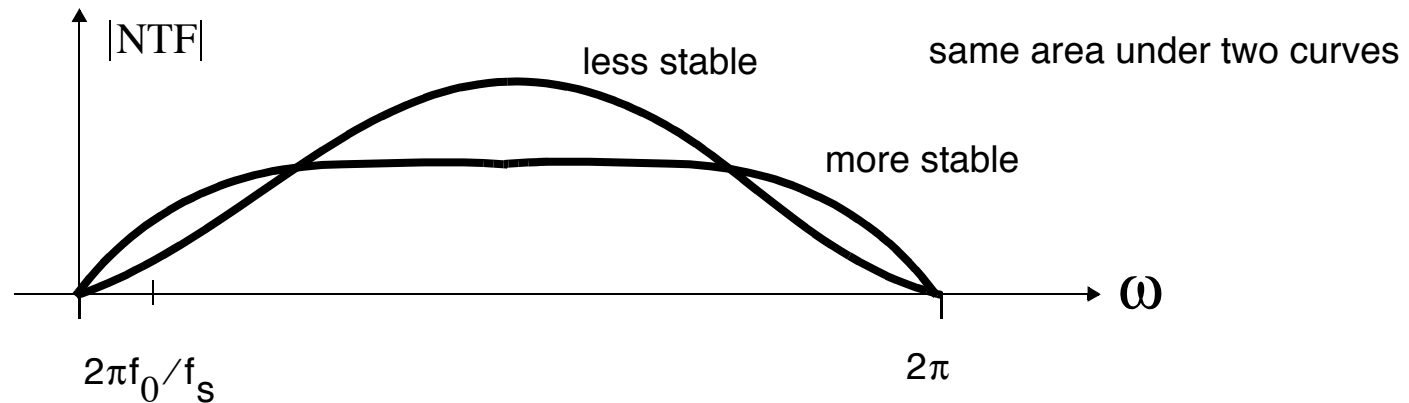

Stability Detection

- Might look at input to quantizer
- Might look for long strings of 1s or 0s at comp output

When instability detected ...

- reset integrators
- Damp some integrators to improve stable

Idle Tones


- $1/3$ into 1'st order modulator results in output

$$y(n) = \{1, 1, -1, 1, 1, -1, 1, 1, \dots\} \quad (28)$$

- Fortunately, tone is out-of-band at $f_s/3$
- $(1/3 + 1/24) = 3/8$ into modulator has tone at $f_s/16$
- Similar examples can cause tones in band-of-interest and are not filtered out — say $f_s/256$
- Also true for higher-order modulators
- Tones might not lie at single frequency but be short term periodic patterns.

Dithering



Dither signal

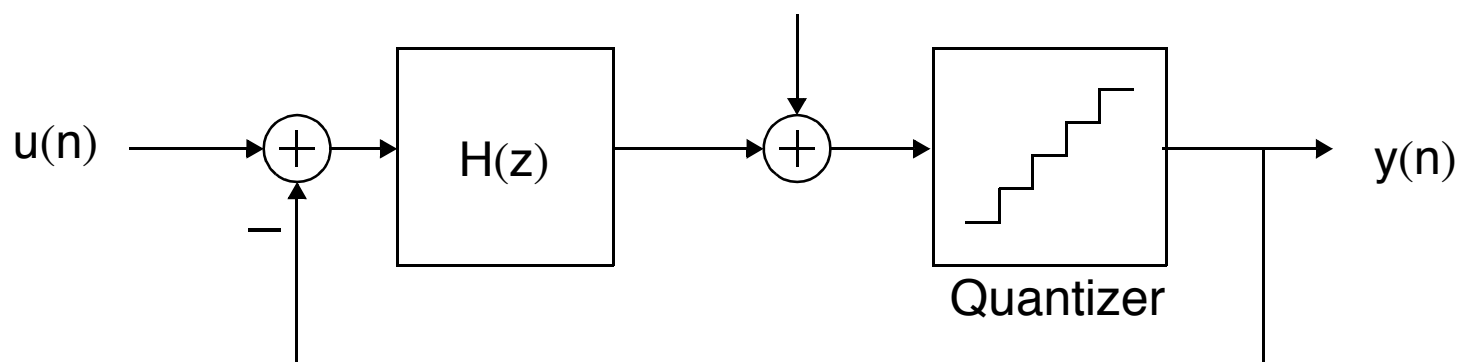

- Add pseudo-random signal into modulator to break up idle tones (not just mask them)
- If added before quantizer, it is noise shaped and large dither can be added.
 - A/D: few bit D/A converter needed
 - D/A: a few bit adder needed
- Might affect modulator stability

Opamp Gain

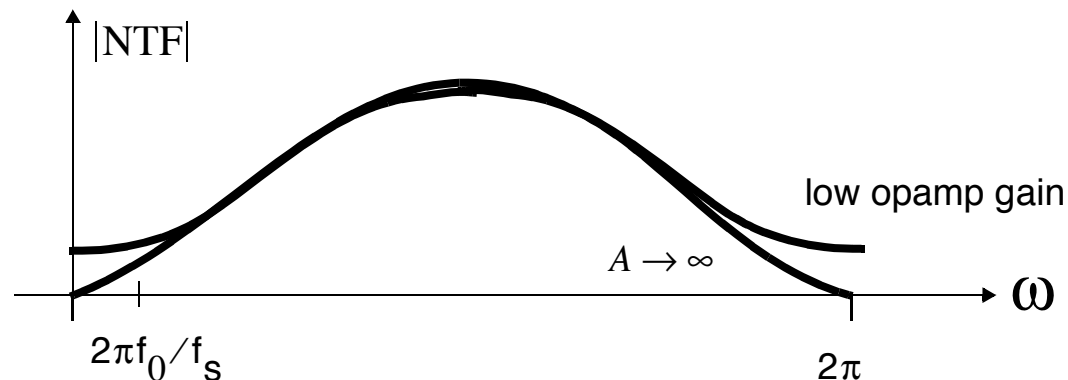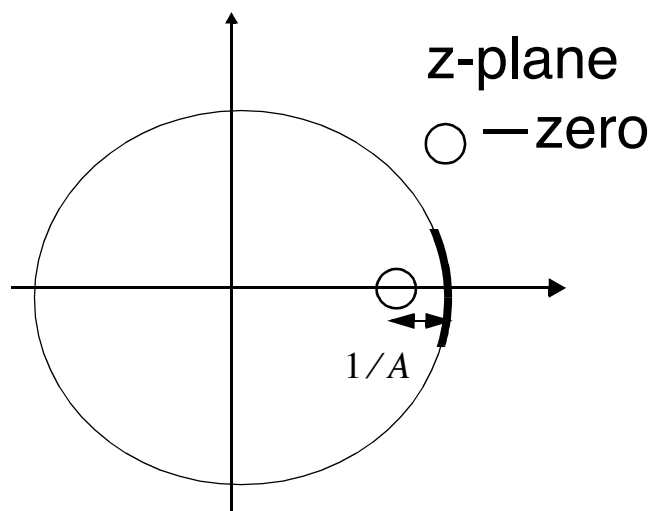- Finite opamp gain, A , moves pole at $z = 1$ left by $1/A$



- Flattens out noise at low frequency
— only 3 dB/octave for high OSR
- Typically, require

$$A > OSR/\pi \quad (29)$$

Multi-bit Oversampled Converters

- A multi-bit DAC has many advantages
 - more stable - higher peak $|NTF|$
 - higher input range
 - less quantization noise introduced
 - less idle tones (perhaps no dithering needed)
- Need highly linear multi-bit D/A converters

Example

- A 4-bit DAC has 18 dB less quantization noise, up to 12 dB higher input range — perhaps 30 dB improved SNR over 1-bit