

ELEC301 Homework Set #4

P. 1

1) For the circuit shown in figure 1, find I_1 , I_2 , I_C , I_E , g_m , and r_π .

2) For the circuit shown in figure 2, find A_M , $\omega_{3dB L}$, and $\omega_{3dB H}$ given that $\beta = 100$ and that the hybrid- model has the following parameters $c_\pi = 10\text{pF}$, $c_\mu = 2\text{pF}$, and $r_o = \infty$.

3) For the circuit shown in figure 3:

- Draw the low frequency circuit, the mid band circuit and the high frequency circuit and
- Derive the mid band gain, A_M , and $F_L(s)$.

4) For the circuit shown in figure 4, use the $1/3^{\text{rd}}$ rule (your choice) to bias the circuit and find C_E , C_{C1} , and C_{C2} that will put the low frequency poles at $1000/\text{s}$, $100/\text{s}$ and $10/\text{s}$. Choose the lowest cost combination of capacitors.

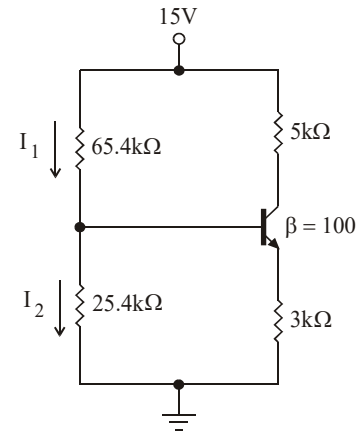


Figure 1.

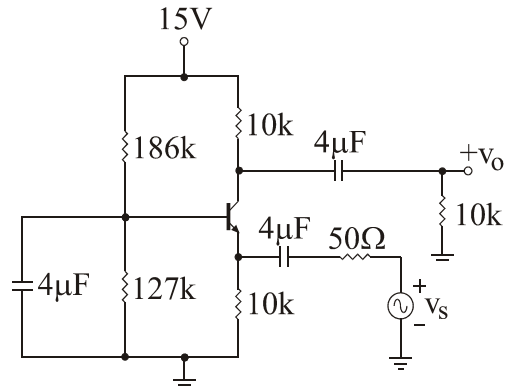


Figure 2.

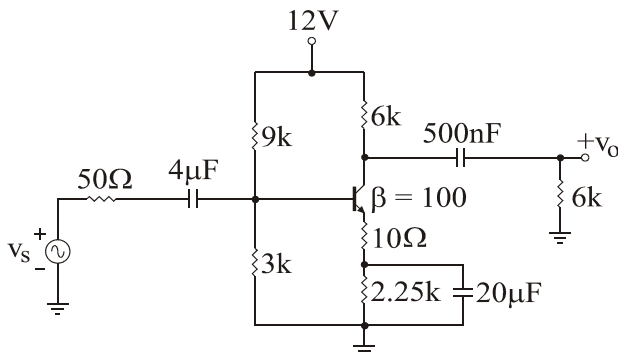


Figure 3.

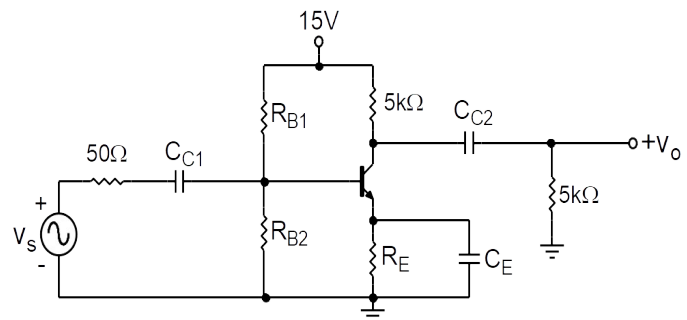


Figure 4.