
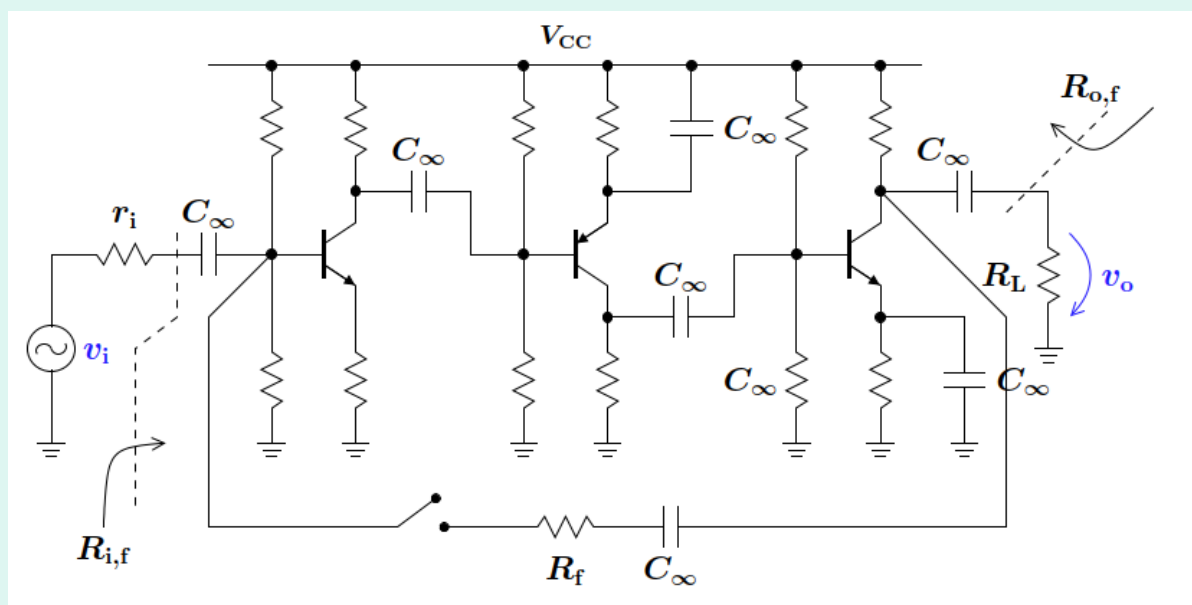


ELEC 301 - Feedback circuit analysis

L23 - Nov 03


Instructor: Edmond Cretu

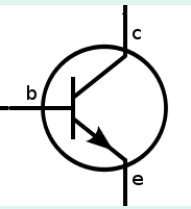



Last time

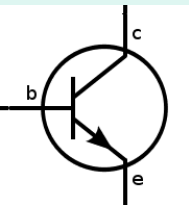
- From feedback in signal flows (information flow) to feedback in circuits (energy flow) - effects on gain, R_{in} , R_{out}
- Ideal feedback networks - 4 topologies
- Non-ideal feedback networks - reduce to the ideal feedback case by “loading” the amplifier with the non-ideal components from the source, load and feedback network



Four feedback topologies


- Summary of closed-loop parameters

Topology	Closed-Loop Gain A_f	Input Resistance R_{i_f}	Output Resistance R_{o_f}
Voltage-Sampling Series-Mixing	$A / (1 + A\beta)$	$R_i(1 + A\beta)$	$R_o / (1 + A\beta)$
Current-Sampling Series-Mixing	$A / (1 + A\beta)$	$R_i(1 + A\beta)$	$R_o(1 + A\beta)$
Voltage-Sampling Shunt-Mixing	$A / (1 + A\beta)$	$R_i / (1 + A\beta)$	$R_o / (1 + A\beta)$
Current-Sampling Shunt-Mixing	$A / (1 + A\beta)$	$R_i / (1 + A\beta)$	$R_o(1 + A\beta)$

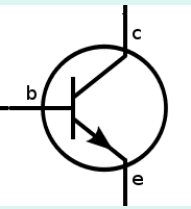


Systematic approach


- Procedure:
 - 1 Identify the forward path, the feedback path (A and β subsystems), and the type of feedback
 - 2 Build the equivalent diport model for the feedback network (usually neglect the forward path parameter)
 - 3 Transform the feedback network into an ideal one, by loading the forward path
 - 4 Compute A' , R_i' , R_o' (equivalent diport parameters for the loaded amplifier, neglecting the inner feedback path) and β
 - 5 Apply (ideal) feedback formulas to find A_f' , R_{if}' , R_{of}'

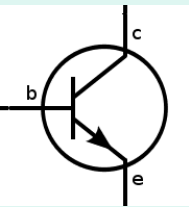

Series-shunt topology (voltage amplifier)


- Series-shunt \rightarrow h-parameters

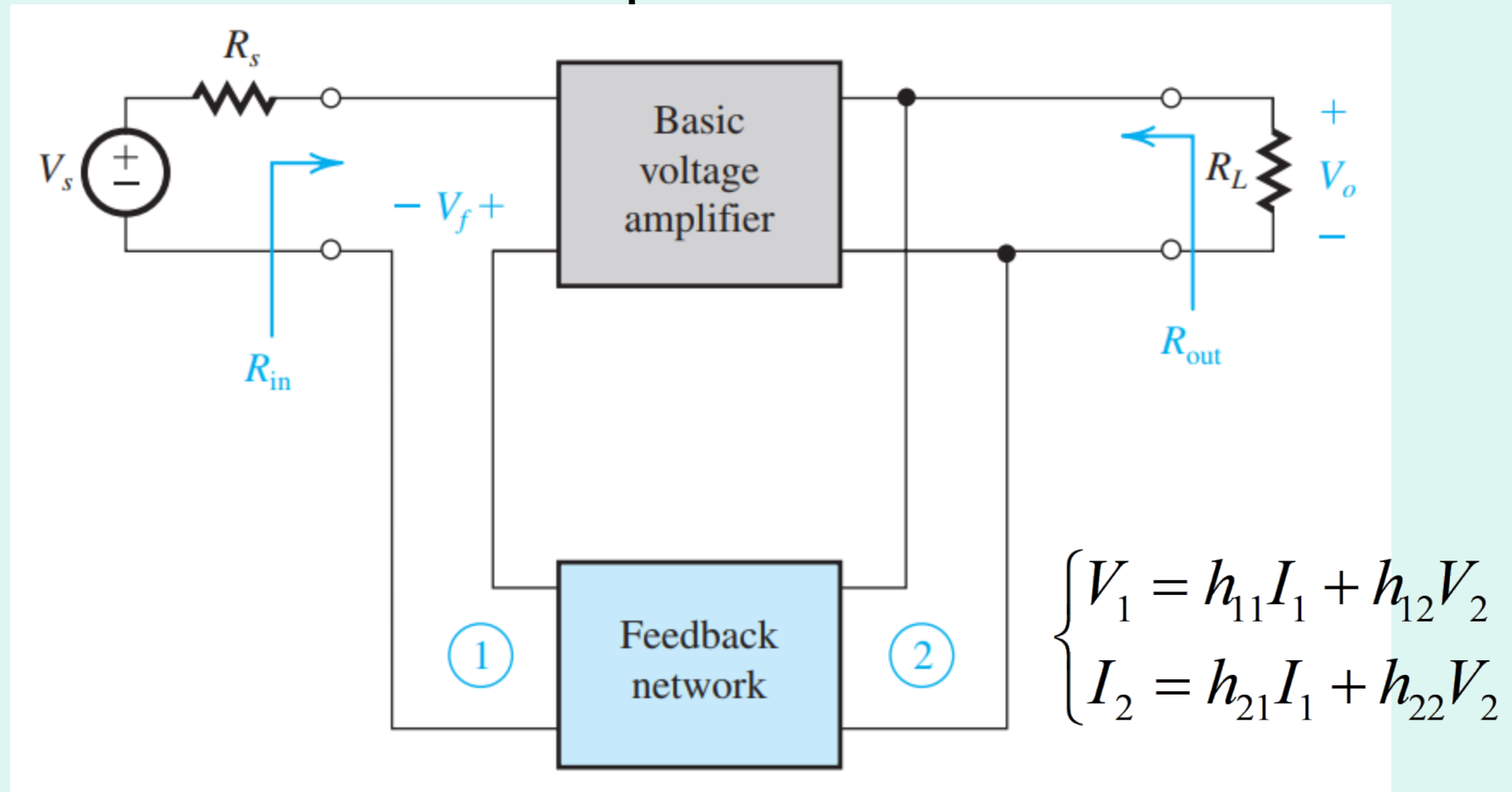

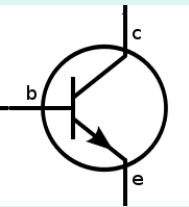

Shunt-series topology (current amplifier)

- Shunt-series → g-parameters

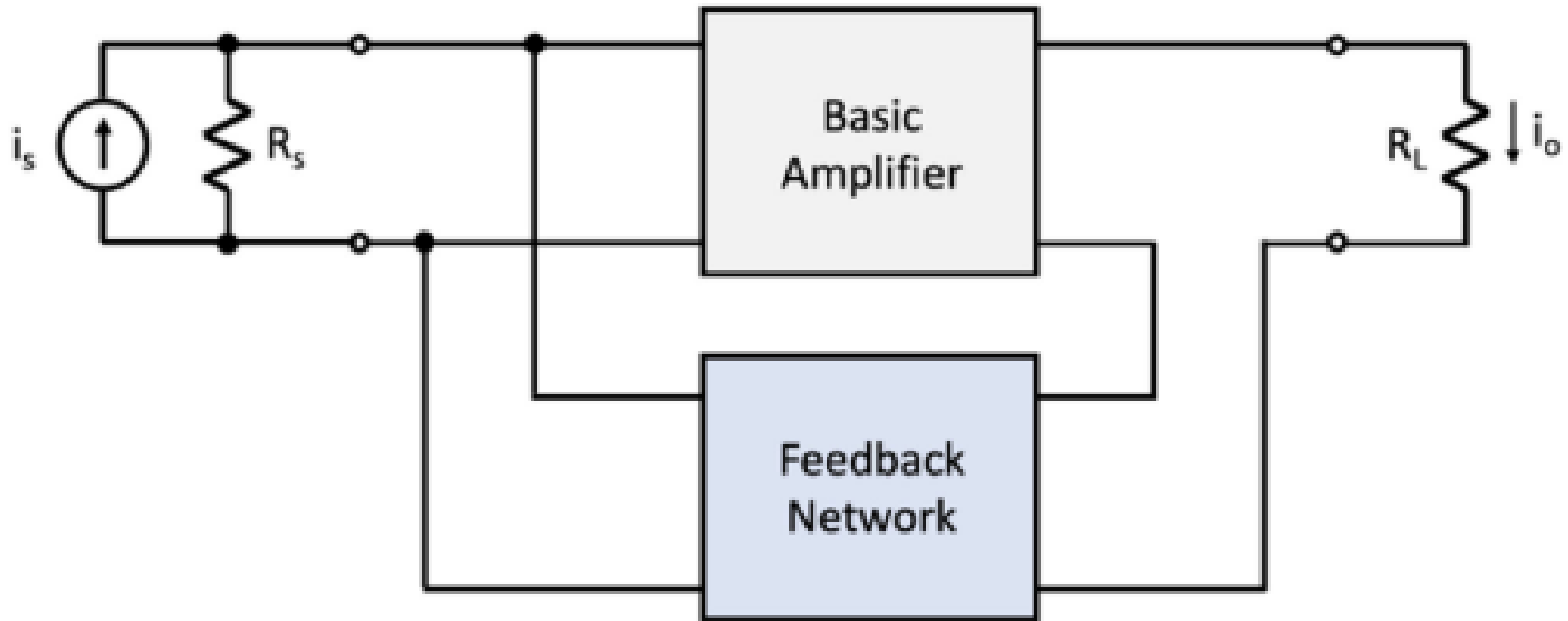


$$g - \text{parameters} : \begin{cases} I_1 = g_{11}V_1 + g_{12}I_2 \\ V_2 = g_{21}V_1 + g_{22}I_2 \end{cases}$$




Shunt-shunt topology (transimpedance amplifier)

- Shunt-shunt \rightarrow y -parameters

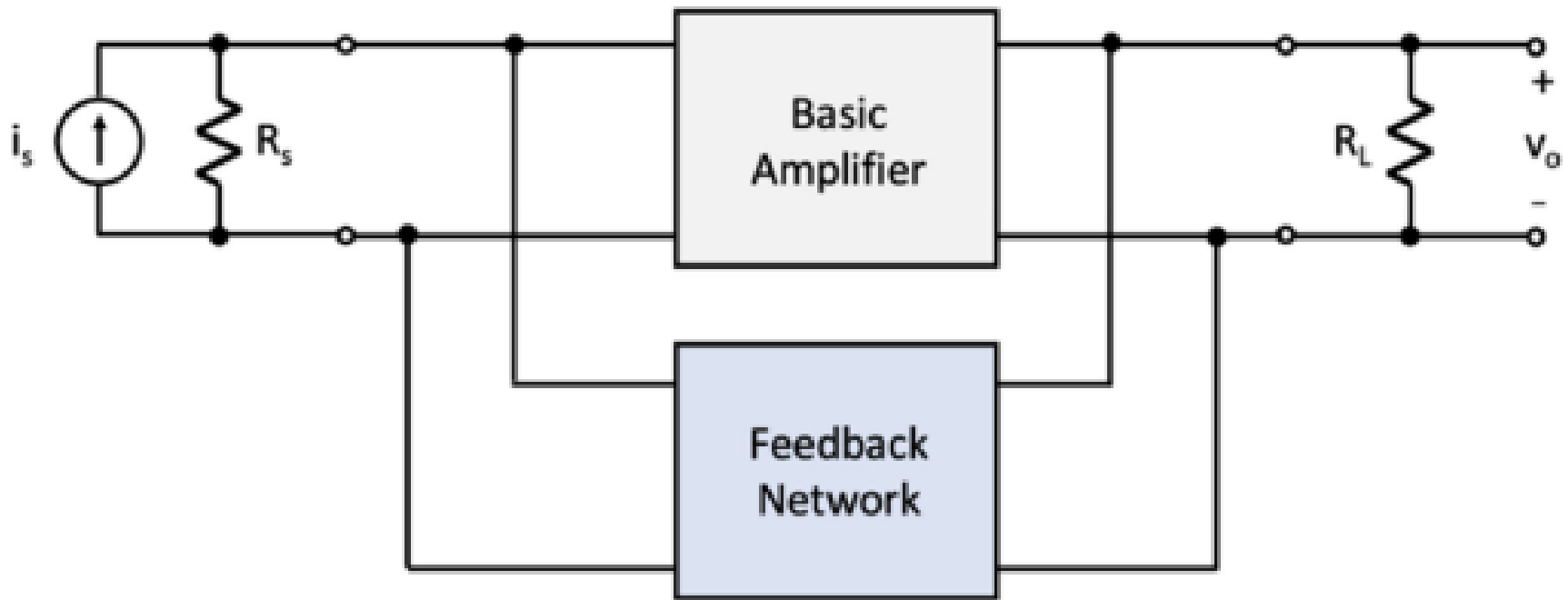

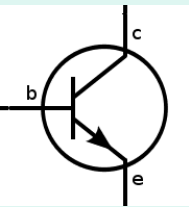
$$y - parameters : \begin{cases} I_1 = y_{11}V_1 + y_{12}V_2 \\ I_2 = y_{21}V_1 + y_{22}V_2 \end{cases}$$




Series-series topology (Transadmittance amplifier)

- series-series \rightarrow z-parameters

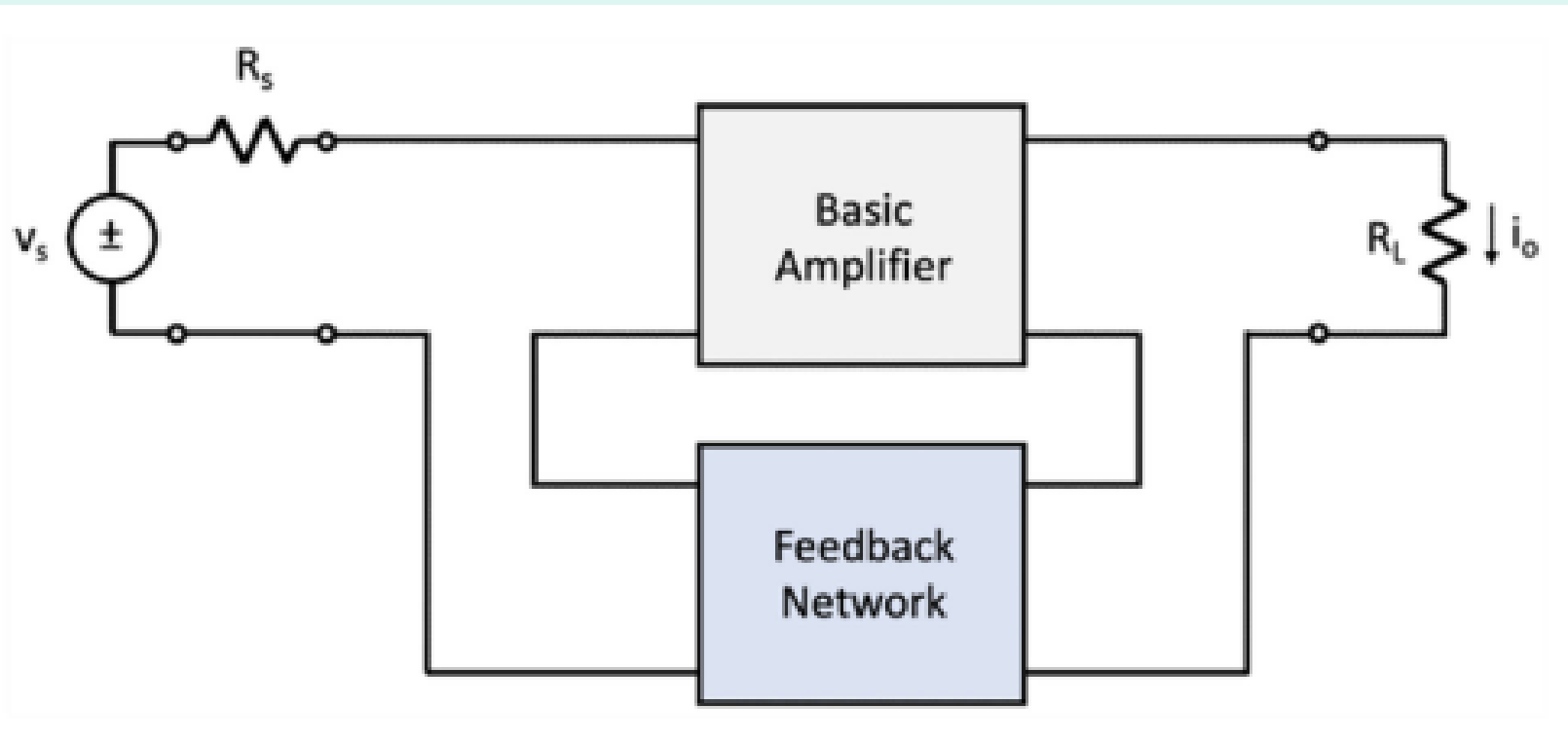
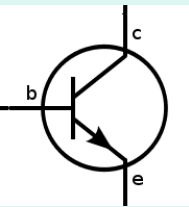
$$z - \text{parameters} : \begin{cases} V_1 = z_{11}I_1 + z_{12}I_2 \\ V_2 = z_{21}I_1 + z_{22}I_2 \end{cases}$$



Example: non-inverting amplifier

- Introduce non-idealities: R_i , R_o

