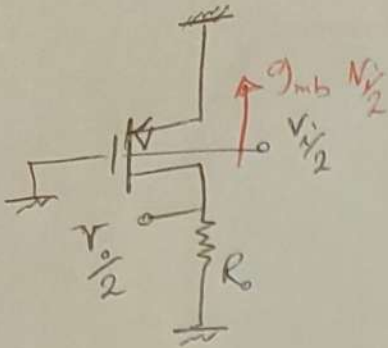


① Half-circuit differential equivalent:




$$\frac{V_o}{2} = -R_o (g_{mb} \frac{V_i}{2})$$

$$\Rightarrow \frac{V_o}{V_i} = -g_{mb} R_o$$

$$I_{D0} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_0 (V_{SG_0} - |V_{th1}|)^2 = \frac{1}{2} \times 0.1 \frac{\text{mA}}{\text{V}^2} \times 40 \times (3 - 1.4 - 0.6)^2 = 2 \text{ mA}$$

$$I_{D1} = \frac{I_{D0}}{2} = 1 \text{ mA}, \quad g_{m1} = \sqrt{2 \times \mu_p C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}} = \sqrt{2 \times 0.1 \times 20 \times 1 \text{ mA}} = 2 \text{ mS}$$
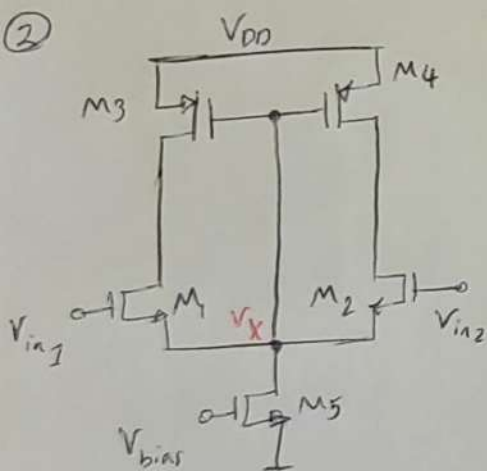
$$g_{mb1} = \eta g_{m1} = 0.2 \times 2 \text{ mS} = 0.4 \text{ mS} \quad \Rightarrow \quad \frac{V_o}{V_i} = -0.4 \text{ mS} \times 1 \text{ k} = \boxed{-0.4}$$



when operating in deep triode:

$$R_{on} = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right) (V_{SG} - |V_{th}|)}$$

$$\frac{W}{L} = \frac{7 \mu\text{m}}{0.35 \mu\text{m}} = 20$$

$$2 \text{ k} = \frac{1}{0.1 \times 20 \times (V_{SG3} - 0.6)} \Rightarrow V_{SG3} = 0.6 + \frac{1}{0.1 \times 20 \times 2} = 0.85 \text{ V}$$

$$\Rightarrow V_X = V_{DD} - V_{SG3} = 3 - 0.85 = 2.15 \text{ V}$$

$$I_5 = 40 \mu\text{A} \Rightarrow I_1 = 20 \mu\text{A} \quad I_1 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 V_{eff1}^2 \Rightarrow V_{eff1} = \sqrt{\frac{2 \times 0.02}{0.2 \times 20}} = 0.1$$


$$\Rightarrow V_{GS1} = V_{eff1} + V_{th} = 0.1 + 0.5 = 0.6$$

$$V_{DCin} = V_X + V_{GS1} = 2.15 + 0.6 = \boxed{2.75 \text{ V}}$$

$$g_1 = \frac{2 I_1}{V_{eff1}} = \frac{2 \times 0.02}{0.1} = 0.4 \text{ mS}$$

$$A_{vs} = -g_1 R_{D3} = -0.4 \text{ mS} \times 2 \text{ k} = \boxed{-0.8}$$

3

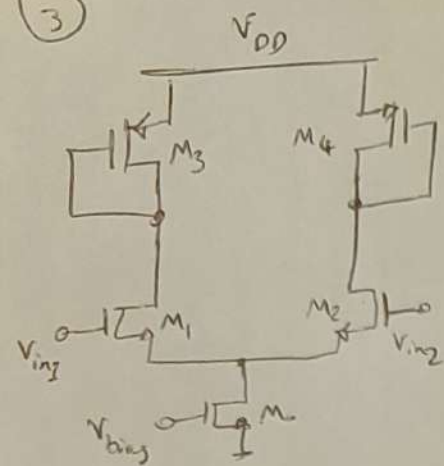

$$P = 3 \text{ mW} \Rightarrow I_{DC} = \frac{P}{V_{DD}} = \frac{3 \text{ mW}}{3} = 1 \text{ nA}$$

$$V_{eff0} = V_{GS0} - V_{thN} \Rightarrow V_{bias} = V_{eff0} + V_{th} = 0.2 + 0.5 = 0.7 \text{ V}$$

$$I_0 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_0 V_{eff0}^2 \Rightarrow \left(\frac{W}{L} \right)_0 = \frac{2 \times 1 \text{ nA}}{1 \text{ nA} \times 0.04} = 50$$

$$\Rightarrow W_0 = 50 \times L = 50 \times 0.4 \mu\text{m} = 20 \mu\text{m}$$

$$V_{DD} = 1.5 \Rightarrow V_{S_{3,4}} = 3 - 1.5 = 1.5 \text{ V} \quad I_{3,4} = 0.5 \text{ nA}$$

$$\left(\frac{W}{L} \right)_{3,4} = \frac{2 \times 0.5 \text{ nA}}{0.25 \text{ nA} \times (1.5 - 0.5)^2} = 4 \Rightarrow W_{3,4} = 4 \times 0.4 \mu\text{m} = 1.6 \mu\text{m}$$


$$|A_v| = 40 \Rightarrow A_v = -\frac{g_m}{g_3} = -40 \Rightarrow \frac{\sqrt{2} \times 1 \text{ nA} \times \left(\frac{W}{L} \right)_1 \times \frac{1}{L_1}}{\sqrt{2} \times 0.25 \text{ nA} \times \left(\frac{W}{L} \right)_3 \times \frac{1}{L_3}} = 40 \Rightarrow \sqrt{\frac{\left(\frac{W}{L} \right)_1}{\left(\frac{W}{L} \right)_3}} = 20$$

$$\Rightarrow \left(\frac{W}{L} \right)_{1,2} = 400 \times 4 = 1600 \Rightarrow W_{1,2} = 1600 \times 0.4 = 640 \mu\text{m}$$

$$\text{minimum input CM level: } V_{GS1} + V_{eff0} = 0.5 + \sqrt{\frac{2 \times 0.5 \text{ nA}}{1 \text{ nA} \times 1600}} + 0.2 = 0.725 \text{ V}$$

$$\text{maximum input CM level: } V_{DS1} \geq V_{GS1} - V_{th} \Rightarrow V_{GS1, \text{max}} = V_{DS1} + V_{th} = 1.5 + 0.5 = 2 \text{ V}$$


4

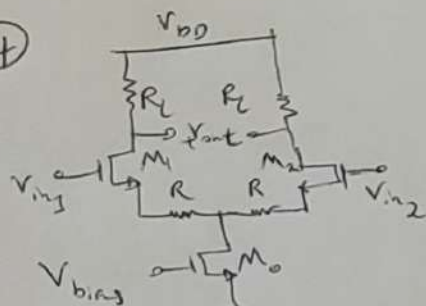

$$I_0 = \frac{1}{2} \times 1 \text{ nA} \times (V_{bias} - V_{th})^2 \times \left(\frac{W}{L} \right)_0 = \frac{1}{2} \times 1 \text{ nA} \times 32 \times (0.75 - 0.5)^2 = 1 \text{ nA}$$

$$\Rightarrow I_1 = I_2 = 0.5 \text{ nA}$$

Half-circuit to find differential gain:

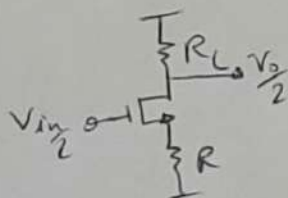

$$A_v = \frac{v_{o2}}{v_{in2}} = \frac{v_o}{v_{in}} = \frac{-R_L}{R + 1/g_1} = -4$$

$$g_1 = \sqrt{2 \times \mu_n C_{ox} \times \left(\frac{W}{L} \right)_1 \times I_1} = \sqrt{2 \times 1 \text{ nA} \times 16 \times 0.5 \text{ nA}} = 4 \text{ mS}$$

$$\Rightarrow \frac{R_L}{100 + 4 \text{ m}} = 4 \Rightarrow R_L = 4(100 + 250) = 1.4 \text{ k}\Omega$$

$$\text{maximum input CM level: } V_{D1} \geq V_{G1} - V_{th} \Rightarrow V_{G1} \leq V_{DD} - I_1 R_L + V_{th} = 3 - 0.7 + 0.5 = 2.8 \text{ V}$$

$$\text{minimum input CM level: } V_{GS1} + I_1 R + V_{eff0} = \sqrt{\frac{2 \times 0.5}{1 \text{ nA} \times 16}} + 0.5 + 0.5 \times 0.1 + 0.25 = 1.05 \text{ V}$$