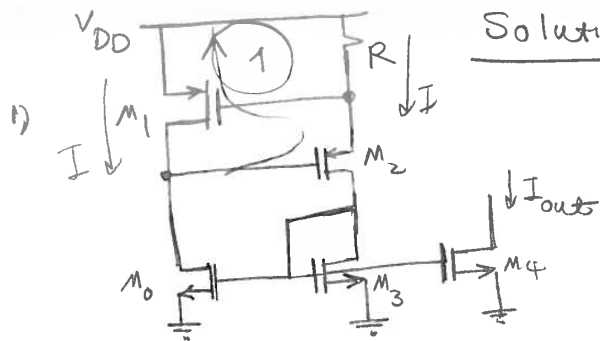


Solutions to Assignment 4



Assuming all trans. are in sat. $\lambda = 0$, $V_{DD} = 3V$
 $V_{tn} = 0.5V$, $V_{tp} = -0.5V$ $k'_n = \mu_n C_{ox} = 0.2 \frac{mA}{V^2}$, $k'_p = \mu_p C_{ox} = 0.1 \frac{mA}{V^2}$

$$\left(\frac{W}{L}\right)_{0,3,4} = \frac{W}{L} \quad , \quad \left(\frac{W}{L}\right)_1 = 16 \quad , \quad I_{out} = 50 \mu A \Rightarrow \text{find } R:$$

$$\textcircled{*} \text{ Since } \lambda = 0 \Rightarrow V_{gs0} = V_{gs3} = V_{gs4} \Rightarrow I = I_0 = I_3 = I_4 = I_{out} = 50 \mu A$$


$$\text{Having a KVL around loop 1: } V_{sg1} = RI = RI_{out}$$

$$\text{Moreover: } I = \frac{1}{2} k'_p \left(\frac{W}{L}\right)_1 (V_{sg1} - |V_{tp}|)^2 \Rightarrow 50 \mu = \frac{1}{2} \times 100 \times 16 \times (V_{sg1} - |V_{tp}|)^2$$

$$\Rightarrow V_{sg1} - |V_{tp}| = \sqrt{\frac{2 \times 50}{100 \times 16}} = 0.25V \Rightarrow V_{sg1} = 0.5 + 0.25 = 0.75V$$

$$\Rightarrow V_{sg1} = 0.75 = R \times 50 \mu A \Rightarrow R = \frac{0.75}{50} \times 1000 = 15 k\Omega$$

2)

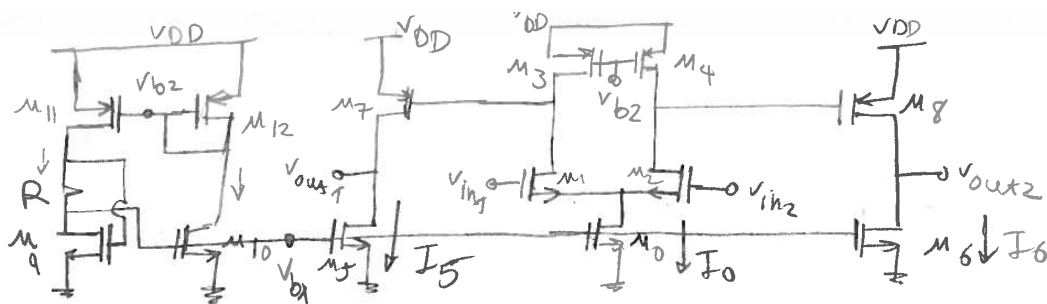

$$V_{DD} = 1.8V, P_{de_total} = 1.98, A_{v_total} = 4000, L = 4\mu m, w_{11} = w_{12}$$

$$w_{10} = 4w_9, R = 1k\Omega, I_0 = I_5 + I_6, V_{ov4} = V_{ov6} = V_{ov8}, I_{11} = 0.1I_0$$

$$\lambda_n = \lambda_p = 0.1V^{-1}, \gamma = 0, V_{tn} = -V_{tp} = 0.4V, k_n' = 1mA/V^2, k_p' = 5mA/V^2$$

Find $w_0, w_1, w_2, w_3, w_4, w_5, w_6, w_7, w_8, w_9, w_{10}, w_{11}, w_{12}$

$$\text{Since } \left(\frac{w}{L}\right)_1 = \left(\frac{w}{L}\right)_{12} \Rightarrow I_9 = I_{10}, P_{de} = 1.98 = V_{DD} \{2 \times I_{10} + 2I_5 + I_0\}$$

$$\Rightarrow \frac{1.98}{1.8} = 2I_{10} + 2I_5 + I_0 \Rightarrow \frac{1.98}{1.8} = 2 \times 0.1I_0 + I_0 + I_0 \Rightarrow 2.2I_0 = \frac{1.98}{1.8}$$

$$\Rightarrow I_0 = 0.5mA \Rightarrow I_{10} = 0.1 \times 0.5 = 0.05mA$$

$$\text{Back to the last question: } 0.05 = \left\{ \sqrt{\frac{2}{1 \times \left(\frac{w}{L}\right)_9}} - \sqrt{\frac{2}{1 \times 4 \left(\frac{w}{L}\right)_9}} \right\}^2$$

$$\Rightarrow \left(\frac{w}{L}\right)_9 = \frac{1}{0.05} \times \left\{ \sqrt{2} - \sqrt{\frac{2}{4}} \right\}^2 = \frac{1}{0.05} \times \left\{ 2 + \frac{1}{2} - 2 \right\} \Rightarrow \left(\frac{w}{L}\right)_9 = 10$$

$$\Rightarrow \left(\frac{w}{L}\right)_{10} = 10 \times 4 = 40$$

$$A_{v_total} = g_{m1} (r_{o3} \parallel r_{o1}) \times g_{m7} \times (r_{o7} \parallel r_{o5})$$

$$r_{o1} = r_{o3} = \frac{1}{\lambda I_{D2}} = \frac{1}{0.1 \times \frac{0.5}{2}} = 40k\Omega, r_{o7} = r_{o5} = \frac{1}{\lambda I_{D5}} = \frac{1}{0.1 \times \frac{0.5}{2}} = 40k\Omega$$

$$A_{v_total} = 4000 \Rightarrow g_{m1} \times g_{m7} = 10$$

$$V_{b1} = V_{tn} + \sqrt{\frac{2I_{D10}}{k_n' \left(\frac{w}{L}\right)_{10}}} \Rightarrow V_{b1} = 0.45V \Rightarrow I_{D5} = \frac{1}{2} k_n' \left(\frac{w}{L}\right)_5 (V_{b1} - V_{tn})^2$$

$$\Rightarrow \left(\frac{w}{L}\right)_5 = \frac{2 \times 0.05}{0.05^2} = 40 = \left(\frac{w}{L}\right)_6, \left(\frac{w}{L}\right)_0 = 2 \left(\frac{w}{L}\right)_5 = 80$$

Since $V_{ov4} = V_{ov6} = V_{ov8} = 0.05^V$, $I_8 = I_6 = \frac{I_0}{2} = 0.25^{mA}$

$$\Rightarrow 0.25 = \frac{1}{2} K'_P \left(\frac{W}{L}\right)_8 (0.05)^2 \Rightarrow 0.25 = \frac{1}{2} \times 5 \times \left(\frac{W}{L}\right)_8 \times 0.0025 \Rightarrow \left(\frac{W}{L}\right)_8 = 400$$

$$\Rightarrow \left(\frac{W}{L}\right)_8 = \left(\frac{W}{L}\right)_7 = \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = 400$$

$$\Rightarrow g_{m7} = \sqrt{2 \times K'_P \times \left(\frac{W}{L}\right)_7 \times I_7} = \sqrt{2 \times 5 \times 400 \times 0.25} = 10^{mV}$$

$$\Rightarrow g_{m1} \times g_{m7} = 10 \Rightarrow g_{m1} = \frac{10}{10} = 1^{mV}$$

$$\Rightarrow 1 = \sqrt{2 K'_n \times \left(\frac{W}{L}\right)_1 \times \frac{I_0}{2}} \Rightarrow \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 2$$

$$V_{ov4} = 0.05 \Rightarrow V_{S9} = 4 + 0.05 = 4.05^V \Rightarrow V_{b2} = V_{DD} - V_{S9} = 1.8 - 4.05 = -2.25^V$$

$$\Rightarrow V_{S9} = 1.8 - 1.35 = 0.45^V \Rightarrow I_D = \frac{1}{2} K'_P \left(\frac{W}{L}\right)_{11,12} (0.05)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_{11} = \left(\frac{W}{L}\right)_{12} = 80$$